

The McGraw-Hill Companies

Basic Electrical Engineering

premier12

Abhijit Chakrabarti
Sudipta Nath
Chandan Kumar Chanda



Urheberrechtlich geschütztes Material



Tata McGraw-Hill

Published by the Tata McGraw-Hill Publishing Company Limited,
7 West Patel Nagar, New Delhi 110 008.

Copyright © 2009, by Tata McGraw-Hill Publishing Company Limited.

No part of this publication may be reproduced or distributed in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise or stored in a database or retrieval system without the prior written permission of the publishers. The program listings (if any) may be entered, stored and executed in a computer system, but they may not be reproduced for publication.

This edition can be exported from India only by the publishers,
Tata McGraw-Hill Publishing Company Limited

ISBN (13): 978-0-07-066930-7

ISBN (10): 0-07-066930-9

Managing Director: *Ajay Shukla*

General Manager: Publishing—SEM & Tech Ed: *Vibha Mahajan*

Sponsoring Editor: *Shalini Jha*

Senior Copy Editor: *Dipika Dey*

Senior Production Manager: *P L Pandita*

General Manager: Marketing—Higher Education & School: *Michael J Cruz*

Product Manager: SEM & Tech Ed: *Biju Ganesan*

Controller—Production: *Rajender P Ghansela*

Asst. General Manager—Production: *B L Dogra*


Information contained in this work has been obtained by Tata McGraw-Hill, from sources believed to be reliable. However, neither Tata McGraw-Hill nor its authors guarantee the accuracy or completeness of any information published herein, and neither Tata McGraw-Hill nor its authors shall be responsible for any errors, omissions, or damages arising out of use of this information. This work is published with the understanding that Tata McGraw-Hill and its authors are supplying information but are not attempting to render engineering or other professional services. If such services are required, the assistance of an appropriate professional should be sought.

Typeset at The Composers, 260, C.A. Apt., Paschim Vihar, New Delhi 110 063 and
printed at Avon Printers, 271, F.I.E. Patparganj, Delhi 110 092

Cover: SDR Printers

RYXRRRQXDCCY

The McGraw-Hill Companies

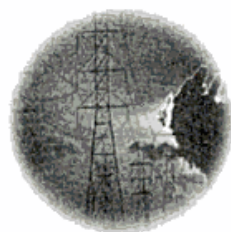

CONTENTS

<i>Preface</i>	<i>xv</i>
----------------	-----------

1. Fundamentals	1
------------------------	----------

1.1	System of Units	1
1.2	Fundamental and Derived Units in SI system	1
1.3	Definitions of Fundamental Units and Derived Units	2
1.4	Concept of Per Unit (p.u.) System	4
1.5	Concept of Current Flow	11
1.6	Concept of Source and Load	11
1.7	Sign Notation for Voltages	12
1.8	Concept of Positive and Negative Currents and Voltages	12
1.9	Ohm's Law and Concept of Resistance	13
1.10	Concept of Resistivity	13
1.11	Expressions of Power and Energy in Resistive Circuits	14
1.12	Temperature Coefficient of Resistance	17
	<i>Additional Examples</i>	22
	<i>Exercises</i>	30

2. Electrostatics	36
--------------------------	-----------

2.1	Introduction	36
2.2	Coulomb's Law and Concept of Permittivity	36
2.3	Permittivity	37
2.4	Electric Potential and Potential Difference	38
2.5	Expression for Potential at a Point within an Electric Field	38
2.6	Electric Field Intensity	39
2.7	Electric Field Intensity and Potential of Isolated Point Charge (+q)	40
2.8	Electric Field Intensity and Potential Gradient	41
2.9	Electric Potential Energy	42
2.10	Relation between Electric Field Strength and Potential	43
2.11	Electric Field Inside a Conductor	43

2.12	Gauss' Law and its Derivation	44
2.13	Electric Dipole	45
2.14	Electric Field and Potential due to a Dipole at an Axial Point	46
2.15	Electric Field and Potential due to Dipole on Equatorial Line	46
2.16	Capacitor and Capacitance	54
2.17	Series and Parallel Connection of Capacitors	55
2.18	Concept of Dielectric Strength	56
2.19	Types of Capacitors Commonly Used	56
2.20	Capacitance of a Parallel-plate Capacitor	57
2.21	Capacitance of a Multi-plate Capacitor	58
2.22	Capacitance of a Parallel-plate Capacitor with Composite Dielectrics	58
2.23	Capacitance of an Isolated Sphere	60
2.24	Capacitance of Concentric Spheres	60
2.25	Capacitance of a Parallel Plate Capacitor when an Uncharged Metal Slab is Introduced between Plates	62
2.26	Expression of Instantaneous Current and Voltage in a Capacitor	74
2.27	Charging and Discharging of Capacitance	75
2.28	Energy Store in Capacitor	82
	<i>Additional Examples</i>	84
	<i>Exercises</i>	98
3.	Electromagnetism and Magnetic Circuits	109
3.1	Introduction	109
3.2	Magnetic Field around a Current-carrying Conductor	112
3.3	Force on a Current-carrying Conductor in a Magnetic Field	113
3.4	Force between Two Parallel Current-carrying Conductors	113
3.5	Biot Savart's (or Laplace's) Law	117
3.6	Application of Biot-Savart Laws	118
3.7	Electromagnetic Induction	123
3.8	Concept of Self-inductance and Mutual Inductance	125
3.9	Concept of Magnetic Coupling	126
3.10	Calculation of Self-inductance	129
3.11	Energy Stored in Inductor	129
3.12	Magnetic Energy Density (U_M)	130
3.13	Combination of Inductances	131
3.14	Lifting Power of a Magnet	138
3.15	Concept of Magnetic Circuit	139
3.16	Concept of Magneto-motive Force (MMF)	139
3.17	Magnetic Field Intensity	140
3.18	Concept of Reluctance	140
3.19	Permeability and Relative Permeability	140
3.20	Definition of Ampere	144
3.21	B-H Characteristics	145
3.22	Ferromagnetic Materials	146
3.23	Types of Magnetic Materials	147

3.24	Magnetic Circuit Laws	147
3.25	Comparison between Electric and Magnetic Circuits	148
3.26	Distinction between Magnetic and Electric Circuits	150
3.27	Leakage Flux in Magnetic Circuit and Fringing and Staking	155
3.28	Magnetic Hysteresis	156
3.29	Hysteresis Loss	158
3.30	Eddy Currents (or Foucault's Currents) and Eddy Current Loss	159
3.31	Rise and Decay of Current in Inductive Circuit	160
3.32	Ampere's Circuital Law	167
	<i>Additional Examples</i>	167
	<i>Exercises</i>	175

4. DC Network Analysis 180

4.1	Introduction	180
4.2	Characteristics of Network Elements	180
4.3	Series Resistive Circuits	181
4.4	Parallel Resistance Circuits	187
4.5	Series-Parallel Circuits	191
4.6	Kirchhoff's Laws	196
4.7	Nodal Analysis	201
4.8	Mesh Analysis (or Loop Analysis)	207
4.9	Star Delta Conversion	217
4.10	Voltage Sources and Current Sources	225
4.11	Superposition Theorem	232
4.12	Thevenin's Theorem	242
4.13	Norton's Theorem	256
4.14	Equivalence of Thevenin's and Norton's Theorems	266
4.15	Maximum Power Transfer Theorem	268
	<i>Additional Examples</i>	274
	<i>Exercises</i>	325

5. Steady State Analysis of AC Circuit 336

5.1	Generation of Alternating emf	336
5.2	Definitions Relating to Alternating Quantity	337
5.3	Phasor Representation of an Alternating Quantity	343
5.4	AC Voltage as Applied to Pure Resistance, Pure Inductance and Pure Capacitance	346
5.5	Series RL Circuit	348
5.6	Series RC Circuit	349
5.7	Series RLC Circuit	350
5.8	Impedances in Series	352
5.9	Parallel AC Circuit	357
5.10	Admittance, Conductance and Susceptance of AC Circuit	358
5.11	Average Power in ac Circuits	359
5.12	Complex Notation Applied to ac Circuits	376
5.13	Series Parallel ac Circuits	377

5.14	Series Resonance	382
5.15	Q factor in Series Resonance	383
5.16	Different Aspects of Resonance	384
5.17	Resonance in Parallel Circuit	391
5.18	Properties of Parallel Resonant Circuits	392
5.19	Q Factor in Parallel Circuit	393
5.20	Parallel Resonance in RLC Circuit	393
5.21	Parallel Resonance in RC-RL Circuit	394
	Additional Problems	397
	Exercises	439
6.	AC Network Analysis	444
6.1	Superposition Theorem (AC Application)	444
6.2	Thevenin's Theorem (AC Application)	448
6.3	Norton's Theorem (AC Application)	453
6.4	Maximum Power Transfer Theorem (AC Application)	457
	Additional Problems	461
	Exercises	482
7.	Three-phase Circuits	485
7.1	Three-phase System	485
7.2	Advantages of a Three-phase System	485
7.3	Generation of a Three-phase Supply	485
7.4	Interconnection of Phases	486
7.5	One Line Equivalent Circuit for Balanced Loads	491
7.6	Measurement of Power in a Three-phase Three-wire System	496
7.7	Measurement of Power for a Three-phase System using Two Wattmeters (Assuming Balanced Load and Sinusoidal Voltages and Currents)	498
7.8	Unbalanced Four-Wire Star	499
7.9	Unbalanced Delta Connected Load	499
7.10	Unbalanced Three-Wire Star Connected Load	499
	Additional Problems	504
	Exercises	527
8.	Transformers	530
8.1	Definition	530
8.2	Principle of Operation	530
8.3	EMF Equation	531
8.4	Construction of Single-phase Transformers	531
8.5	Transformation Ratio (or Turns Ratio)	532
8.6	Impedance Transformation	533
8.7	No Load Operation of a Transformer	537
8.8	Working of a Transformer on Load	538
8.9	Equivalent Circuit of Transformer	541
8.10	Regulation of a Transformer	544
8.11	Condition for Zero (minimum) Regulation	546
8.12	Losses and Efficiency of Transformer	552

8.13	Condition for Maximum Efficiency	554
8.14	Expression for Load at which Efficiency is Maximum	554
8.15	Testing of Transformers	560
8.16	Parallel Operation of Two-single Phase Transformers	566
8.17	Single-phase Auto Transformer	568
8.18	Transformer Cooling	569
8.19	Conservator and Breather	570
8.20	Distribution Transformers and Power Transformers	570
8.21	Name Plate and Ratings	570
8.22	All Day Efficiency	571
8.23	Three-phase Transformer	571
	<i>Additional Problems</i>	578
	<i>Exercises</i>	592

9. DC Machines 598

9.1	Introduction	598
9.2	Principal Parts of a DC Machine	598
9.3	Magnetic Flux Path in a DC Generator	599
9.4	Equivalent Circuit of a DC Machine	599
9.5	Different Types of Excitations in DC Machine	600
9.6	Process of Voltage Build up in Self-excited Generator	602
9.7	EMF Equation of a DC Machine	603
9.8	Types of Windings	603
9.9	Armature Reaction	605
9.10	Commutation	606
9.11	Characteristics of DC Generators	607
9.12	Principle of Operation of a DC Motor	611
9.13	Back EMF	611
9.14	Torque Equation of a DC Motor	611
9.15	Speed Equation of a DC Motor	616
9.16	Speed Regulation of DC Motor	617
9.17	Speed vs. Armature Current Characteristic of DC Motor (N/I_a Characteristics)	617
9.18	Speed Torque Characteristic of DC Motors	619
9.19	Speed Control of DC Motors	622
9.20	Losses in a DC Machine	629
9.21	Need for Starter in a DC Motor	638
9.22	Reversal of Rotation of DC Motor	639
9.23	DC Machine Applications	639
	<i>Additional Examples</i>	640
	<i>Exercises</i>	655

10. Three-Phase Induction Motors 660

10.1	Introduction	660
10.2	Construction of Induction Machines	661
10.3	Comparison of Squirrel Cage and Wound Rotors	663
10.4	Advantages and Disadvantages of a Three-phase Induction Motor	663

10.5	Principle of Operation	663
10.6	Concept of Production of Rotating Field	664
10.7	The Concept of Slip	666
10.8	Frequency of Rotor Voltages and Currents	667
10.9	Torque Expression of an Induction Motor	670
10.10	Torque Slip Characteristics of a Three-phase Induction Motor	678
10.11	Equivalent Circuit of Induction Motor	680
10.12	Losses and Efficiency	681
10.13	Determination of Motor Efficiency	686
10.14	Starting of Three-phase Induction Motors	695
10.15	Comparison Among Direct on Line Starter, Star Delta starter and Auto-transformer Starter	699
10.16	Speed Control of a Three-phase Induction Motor	700
10.17	Reversal of Rotation	701
	Additional Examples	703
	Exercises	719

11. Synchronous Machines **728**

11.1	Introduction	728
11.2	Operating Principle	729
11.3	Types of Rotors	729
11.4	Stator	730
11.5	Field and Armature Configurations	730
11.6	Advantages of Rotating Field	730
11.7	Expression of Frequency	731
11.8	Distributed Armature Winding	731
11.9	Short-pitch Armature Winding	731
11.10	Single and Double Layer Windings	732
11.11	Expression for Induced EMF in a Synchronous Machine	732
11.12	Armature Reaction and Armature Winding Reactance	737
11.13	Armature Leakage Reactance and Synchronous Impedance	738
11.14	Equivalent Circuit and Phasor Diagram	738
11.15	Voltage Regulation of a Synchronous generator	739
11.16	Phasor Diagram for a Salient Pole Alternator: Two-reaction Theory	743
11.17	Steady State Parameters	745
11.18	Power Angle Characteristic of Salient Pole and Cylindrical Pole Machines	745
11.19	Synchronous Motor	749
11.20	Principle of Operation	749
11.21	Effect of Change of Excitation of a Synchronous Motor (V-curves) for the Motor Driving a Constant Load	750
11.22	Starting of Synchronous Motors	751
11.23	Application of Synchronous Motor	752
11.24	Comparison between Synchronous and Induction Motor	752
11.25	Hunting of Synchronous Machine	753

11.26	Equivalent Circuit and Phasor Diagram of Synchronous Motor	753
11.27	Power and Torque Developed in a Cylindrical Rotor Motor	755
11.28	Power and Torque Developed in Salient Pole Motor	756
	Additional Examples	760
	Exercises	765
12.	Single-phase Induction Motors	770
12.1	Introduction	770
12.2	Production of Torque	770
12.3	Equivalent Circuit of a Single-Phase Induction Motor	772
12.4	Determination of Parameters of Equivalent Circuit	774
12.5	Starting of Single-phase Induction Motors	777
12.6	Split Phase Induction Motors	778
12.7	Capacitor Start Motor	779
12.8	Capacitor Start Capacitor-Run Motor	781
12.9	Shaded Pole Motors	784
	Exercises	786
13.	Electrical Measuring Instruments	788
13.1	Introduction	788
13.2	Types of Instruments	788
13.3	Working Principle of Electrical Instruments	789
13.4	Different Torques in Indicating Instruments	789
13.5	Damping Torque (T_d)	792
13.6	Types of Indicating Instruments	794
13.7	Measurement of Resistance	809
13.8	Rectifier Type Instruments	810
	Exercises	812
14.	Review Problems	813
15.	Multiple Choice Questions	923
15.1	Circuit Elements, Kirchhoff's Laws, and Network Theorems	923
15.2	Electromagnetic Induction and Inductance	925
15.3	Fundamentals of AC Circuits	927
15.4	DC Machine	930
15.5	Transformer	935
15.6	Induction Motor	941
15.7	Synchronous Machine	947
15.8	Basic Circuit; Capacitance; AC Circuit	949
15.9	Magnetic Circuits	950
15.10	Electrical Machines	951



PREFACE

A well established, huge, and an exciting field, Electrical Engineering broadly involves working with various electronic devices ranging from pocket calculators to super computers. A growing presence of electronic devices and instrumentation in all aspects of engineering design and analysis greatly emphasizes the importance of the study of Electrical Engineering.

Basic Electrical Engineering is a compulsory course in all Engineering Colleges, Institutes and Universities. The book, targeted at the undergraduate level, presents the fundamental concepts of the subject in a comprehensive manner. Offering a lucid explanation of theory, supported by illustrations and large number of worked out examples; the text has been structured in a logical sequence as per syllabi of Engineering Colleges and Universities.

Key Features

The text not only lays strong emphasis on basic principles, but also incorporates topics and contents with advanced concepts. A careful selection of the text material and worked out examples (using a 'simple to more complex topic' approach) enable the students to gradually master the course of Basic Electrical Engineering. Examples throughout the text have been solved in detail so that the reader can follow each example thoroughly. Exercises, including a number of problems, are given at the end of each chapter, to evaluate the understanding of topics. All the problems have answers, wherein some of them contain hints to assist the reader in solving the problem.

The book has been written utilising the long experience of the authors in teaching Electrical Engineering. In relevant portions of the text, additional discussions and illustrative examples have been presented to make the pursuit of the study of Electrical Engineering a stimulating experience for the students.

The major highlights of this book can be summarized as

- The subject has been presented in a graded manner, and contains a detailed exposition of the fundamentals.

- Clearly illustrated examples demonstrate relevant applications of electrical engineering.
- Step-by-step and simple problem solving methodology enables the students to sharpen their problem solving skills.
- The figures and diagrams support the concepts and aid in the understanding of the subject.

Chapter Organisation

This book contains fifteen chapters, out of which the first thirteen chapters have been developed on the important topics, to include fundamental laws, concepts in electrical circuits, basic principles on electrical machines, and electrical measurements and measuring instruments. Chapter 14 on Review Problems contains a substantial number of well chosen, worked out examples. Another unique feature is Chapter 15 on Multiple Choice (objective type) Questions, covering the whole syllabus of Basic Electrical Engineering.

Web Supplements

To complement the contents of the book, an exhaustive online learning centre has been designed. Students can access additional Solved Problems and Links for further reference, enabling them to explore practical engineering applications of the devices and systems, in greater detail. The website also features Model Question Papers. A collection of resources available to teachers include detailed Solutions Manual and PowerPoint Slides that serve as valuable teaching tools. The site will be updated regularly and any suggestion towards this end is welcome.

Acknowledgements

The authors express their appreciation of the in-depth feedback received from the following reviewers.

A Mouleeshwaran
*Maharaja College of Engineering,
Coimbatore*

K Chandra Sekhar
*RVR and JC College of Engineering,
Guntur*

P A Keni
*Yadavrao Tasgaonkar College of
Engineering, Raigad*

K K Ghosh
*College of Engineering and
Management, Midnapur*

Anirudha Mukherjee
*Hooghly Engineering College and
Technology, Hooghly*

B Shanmugham
*St. Peter's Engineering College,
Chennai*

B R Patil
*Mumbai University,
Mumbai*

A R Bakshi
*B P Poddar Institute of Management and
Technology, Kolkata*

Sanjoy Kr Saha
*Dr B.C Roy Engineering College
Jemua Road, Fuljhore*

Vineet Mendiratta
*Dehradun Institute of Technology,
Dehradun*

The authors also acknowledge the interest and effort of the entire editorial and marketing teams of McGraw-Hill Education and particularly the initiative taken by Vibha Mahajan, Suman Sen, Nirjhar Mukherjee and Sandhya Chandrasekhar for publishing this book within a short span of time. The authors also appreciate the patience and inspiration provided by their family members.

Constructive criticism and/or comments about the book are welcome.

Authors



FUNDAMENTALS

1.1 SYSTEM OF UNITS

In our daily life as well as in commerce, science and engineering, the system of units have been devised to designate the standards of reference of physical quantities and used to quantify (or measure) them in that standard frame of reference. In fact, everything we see, feel, buy, sell, use is measured and compared by means of units. The units also bear a direct numerical relationship to each other, usually expressed as a whole number. In the English system of units (*FPS system*), they are related to each other by multiples of 3, 12 and 36 while in the Metric system (*CGS system*), the units are related to each other by multiples of 10. In conversion, this system (also known as the *decimal system*) is thus more advantageous than the English system.

Nowadays the International system of units (abbreviated as *SI*) is a commonly acceptable metric system. It possesses the following remarkable features:

- (a) It is a decimal system.
- (b) It is versatile and diversified (e.g., it can measure weights as kilogram, power as kilowatt, potential as volt, current as ampere, length as metre, time as second, temperature as Kelvin, etc.).
- (c) It is used by common people as well as by specialists and is very simple.

1.2 FUNDAMENTAL AND DERIVED UNITS IN SI SYSTEM

Table 1.1 represents the fundamental units in SI system.

From these seven fundamental units in SI system, we can derive any number of derived units to express physical quantities such as area, force, flux, potential, charge, pressure, etc.

Table 1.2 represents a list of a few electrical derived units in SI system which are commonly in use.

Table 1.1 Fundamental units in SI system

Physical Quantity	Unit	Symbol
Mass	Kilogram	kg
Length	Metre	m
Time	Second	s (or sec.)
Temperature	Kelvin	K
Electric Current	Ampere	A (or Amp.)
Luminous Intensity	Candela	Cd
Amount of substance	Mole	mol

Table 1.2 Derived electrical units in SI system

Capacitance (C)	Farad (F)
Inductance (L)	Henry (H)
Conductance (G)	Siemens (S) [also in use Mho]
Resistance (R)	Ohm (Ω)
Susceptance (B)	Mho (\mathcal{U}) or Siemens (S)
Impedance (Z)	Ohm (Ω)
Admittance (Y)	Mho (\mathcal{U}) or Siemens (S)
Potential (V)	Volt (V)
Energy	Joule (J)
Magnetic flux (ϕ)	Weber (Wb)
Flux density (B)	Tesla (T)
Power (P)	Watt (W)
Frequency (f)	Hertz (Hz)
Phase Angle (δ)	Radian (rad)

1.3 DEFINITIONS OF FUNDAMENTAL UNITS AND DERIVED UNITS

A few commonly used fundamental units are defined as under:

- Metre (m):** Length of the path travelled by a light ray in space during a time interval of $1/299792458$ of a second.
- Kilogram (kg):** Unit of mass that is equal to the mass of the international prototype of the kilogram. (It is a particular cylinder of platinum-iridium alloy that is preserved at France by the International Bureau of Weights and Measures.)
- Second (s):** Unit of time defined as the duration of 9192631770 periods of radiation corresponding to the transition between the two hyperfine levels of the ground state of "Cesium-133" atom.
- Kelvin (K):** Unit of temperature expressed as the fraction ($1/273.16$) of the thermodynamic temperature of the "triple point" of water [triple point is equal to 0.01 degree Celsius ($^{\circ}\text{C}$)]. Thus a temperature of 0°C is equal to 273.16 Kelvin.
- Ampere (A):** It is the constant current which, if passed through two straight parallel conductors of infinite length (of negligible cross sectional area), and

if placed in vacuum at 1 metre apart, would produce a force of 2×10^{-7} Newton/metre length of conductors and between these two conductors.

(f) *Candela* (Cd): It is the luminous intensity of a source in a given direction emitting monochromatic light of frequency 540×10^{12} Hz and it has an intensity of 1/683 watts per steradian in that direction.

(g) *Mole* (mol): It is the amount of substance of a system that has as many elementary entities as there are atoms in 0.012 kg of "Carbon-12" element.

A few commonly used derived units are defined as under:

(a) *Coulomb* (Q): It is defined as the quantity of electric charge passed in one second by a current of strength one ampere

$$1 \text{ coulomb} = 1 \text{ A/sec.}$$

(b) *Henry* (H): It is the inductance of a closed circuit in which an emf of one volt is produced when the circuit current varies at a uniform rate of 1 A/sec.

$$1 \text{ Henry} = 1 \text{ V. sec./A}$$

(c) *Ohm* (Ω): It is the electrical resistance offered by a passive current carrying element across its two terminal points when a constant potential difference of one volt is maintained across their two terminal points and the current passing through this conductor is one ampere.

$$1 \text{ ohm} = 1 \text{ V/A}$$

(d) *Siemens* (S): It is the unit of electric conductance, equal to reciprocal of ohm. Siemen is also represented by mho.

(e) *Farad* (F): It is the capacitance between the plates of a capacitor having a p.d. of one volt across them and when it is equal by one coulomb of electricity.

$$1 \text{ F} = 1 \text{ coulomb/volt}$$

(f) *Hertz* (Hz): Frequency of a periodic wave; when the time period of the periodic wave is one sec., frequency is one Hz.

$$f = \frac{1}{T}$$

(g) *Tesla* (T): It is defined as the flux density in a medium equal to one weber per square metre.

$$1 \text{ T} = 1 \text{ Wb/m}^2$$

(h) *Volt* (V): It is the electric potential difference between two points of a conductor when a constant current of one ampere passes through it with a power dissipation of one watt.

$$1 \text{ V} = 1 \text{ W/A.}$$

(i) *Watt* (W): It is the unit of electrical power that produces energy at the rate of one Joule in one second.

$$1 \text{ W} = 1 \text{ joule/sec}$$

(j) *Radian* (rad): It is the unit of phase angle that measures a plane angle with its vertex at the centre of a circle and subtended by an arc equal to the length of the radius.

$$1 \text{ rad} = \frac{\pi^\circ}{180}$$

1.4 CONCEPT OF PER UNIT (P.U.) SYSTEM

The SI system is enough to specify the magnitude of any physical quantity. However, we can get a better idea by comparing the physical quantity in question to the size (or quantity) of "something" very similar to it. This in fact is another concept of creating a new unit and specify the size (or quantity) of similar quantities compared to this new unit. This unit gives rise to the concept of *per unit* (p.u.) system of expressing the magnitude of a physical quantity. It is extensively expressed in electrical engineering.

In representing p.u. quantities, it is important to select a "base" unit against which the physical quantities would be expressed. Though this method is applicable in all systems, in the present text we will explain the application of this concept to electrical engineering only.

Let us say we have three bulbs of 25 W, 100 W and 200 W. We arbitrarily select a base power 100 W. We can then represent the corresponding bulb power ratings as 0.25 p.u., 1 p.u. and 2 p.u. respectively. If we select another base, say 50 W, the corresponding powers become 0.5 p.u., 2 p.u., and 4 p.u. respectively. It is thus important to first decide the base unit in the p.u. system. If we do not know its magnitude, the actual values cannot be calculated.

An illustration

Let us assume that the base value of impedance for the elements, represented in Fig. 1.1(a), be 100 ohm. Figure 1.1(b) then represents the same network configuration but with a p.u. representation.

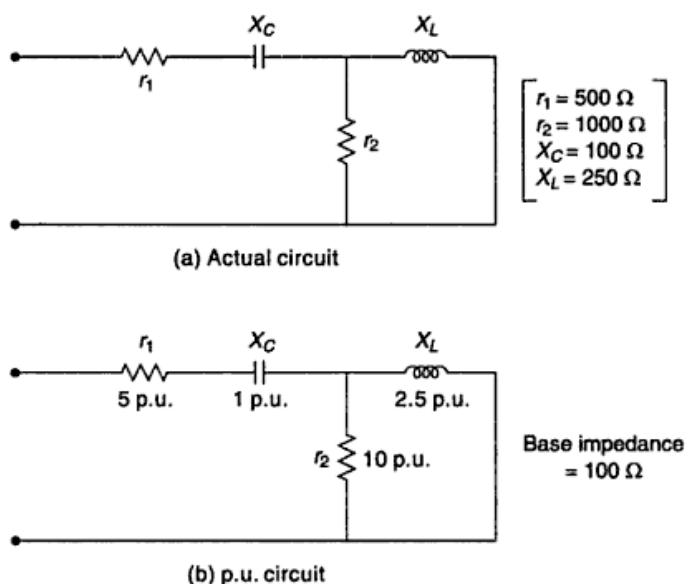


Fig. 1.1 (a) Actual circuit (b) p.u. circuit

In order to maintain the consistency in the p.u. system, two base quantities have been chosen in electrical engineering—voltage (V) and voltamperes (VA).

The base voltage is normally the nominal (i.e. rated) system voltage and the voltampere base may be selected as some integral multiple of one equipment rating. (In power system engineering, the largest rotating machine rating is normally chosen as the base VA power).

If the selected voltage base is (V_B) and the selected VA base is $(VA)_B$, then the remaining base quantities may be derived as:

$$I_B = \frac{(VA)_B}{V_B} \quad (1.1)$$

$$Z_B = \frac{V_B}{I_B} \quad \text{or} \quad \frac{V_B^2}{(VA)_B} \quad (1.2)$$

(The three-phase systems are generally represented as single-phase quantities, in which case the base quantities are all phase values.)

If an equipment in a system has a different base value than that of the system, we can represent the equipment p.u. impedance $Z_{e(p.u.)}$ in terms of its own base $[Z_{e(base)}]$

$$Z_{e(p.u.)} = \frac{Z}{Z_{e(base)}}$$

$$\text{i.e.} \quad Z = Z_{e(p.u.)} \times Z_{e(base)} \quad (1.3)$$

Equipment p.u. impedance on system base $(Z_{s(base)})$ is represented as

$$Z_{s(p.u.)} = \frac{Z}{Z_{s(base)}} = Z_{e(p.u.)} \times \frac{Z_{e(base)}}{Z_{s(base)}}$$

$$\text{i.e.,} \quad Z_{s(p.u.)} = Z_{e(p.u.)} \times \left(\frac{V_e}{V_s} \right)^2 \times \left(\frac{VA_s}{VA_e} \right) \quad (1.4a)$$

These formulae can be used to convert the p.u. (Z) obtained in one base to p.u. (Z) of another base. Here

$$Z_{\text{new}(p.u.)} = Z_{\text{old}(p.u.)} \times \left(\frac{V_{\text{old base}}}{V_{\text{new base}}} \right)^2 \times \left(\frac{VA_{\text{new base}}}{VA_{\text{old base}}} \right) \quad (1.4b)$$

In order to clarify the concept of per unit representation, we include two more illustrations as given below.

Illustration 1

Let us assume that in an electrical system the base voltage is 3 kV while the base power is 300 kVA. The base current would be

$$I_B = \frac{\text{Base power}}{\text{Base voltage}} = \frac{300 \times 10^3}{3 \times 10^3} = 100 \text{ A}$$

The base impedance is

$$Z_B = \frac{V_B}{I_B} = \frac{3 \times 10^3}{100} = 300 \, \Omega$$

Once we have selected the base quantities, we can find the p.u. resistance, p.u. current, p.u. voltage drop and the p.u. power dissipated across a 500 Ω resistor (say) carrying a current of 50 A.

We can write:

$$\text{p.u. } (R) = \frac{R}{Z_B \text{ (or } R_{\text{base}})} = \frac{500}{300} = 1.67$$

$$\text{p.u. } (I) = \frac{I}{I_B} = \frac{50}{100} = 0.5$$

$$\begin{aligned} \text{p.u. } (V_{\text{drop}}) \text{ across } (R) &= I_{(\text{p.u.})} \times R_{(\text{p.u.})} \\ &= 0.5 \times 1.67 = 0.835 \end{aligned}$$

$$\begin{aligned} \text{p.u. power} &= V_{(\text{p.u.})} \times I_{(\text{p.u.})} \\ &= 0.835 \times 0.5 = 0.4175 \end{aligned}$$

Illustration 2

Let us suppose that the voltage drop in the referred resistor of the previous illustration is 0.835 p.u. (given) while the power dissipated is 0.4175 p.u. (given). We would like to know the actual values of the voltage drop and power dissipated using the base values. We can do it as follows:

$$V = V_B \times V_{(\text{p.u.})} \quad \left[\because V_{(\text{p.u.})} = \frac{V}{V_B} \right]$$

$$= 3 \times 10^3 \times 0.835 = 2.505 \times 10^3 \text{ V } (= 2.505 \text{ kV})$$

Here (V) represents the actual drop across the resistor.

Actual power dissipated (S) is obtained as:

$$S = S_{(\text{p.u.})} \times S_B, \text{ where } S \text{ stands for VA power}$$

$$\text{Here, } S = 0.4175 \times 300 \times 10^3$$

$$[\because \text{VA}(\text{p.u.}) = 0.475, \text{ given } \text{VA}(\text{base}) = 300 \text{ kVA}]$$

$$= 125.25 \times 10^3 \text{ VA} = 125.25 \text{ kVA.}$$

1.1 A 6 kV energy source delivers power to a 100 Ω resistor and a 250 kVA electric heater. Find the p.u. currents to the 100 Ω resistor and the electric heater. Also find the total p.u. current from the source. What is the p.u. power of the resistor and the heater? Also determine the actual power loss in the resistance and find the actual line current. Assume base voltage is 3 kV and base power is 100 kVA.

Solution

Let us first draw the circuit diagram (Fig. 1.2).

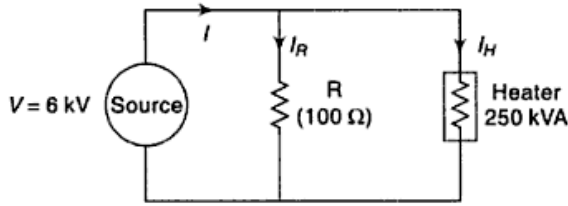


Fig. 1.2 Circuit of Ex. 1.1

From the given data,

$$V_{(p.u.)} = \frac{V}{V_B} = \frac{6 \times 10^3}{3 \times 10^3} = 2 \text{ p.u.}$$

$$R_{(p.u.)} = \frac{R}{Z_B} = \frac{100}{90} = 1.111$$

$$\left[\because Z_B = \frac{V_B}{I_B} = \frac{V_B}{(VA)_B / V_B} = \frac{V_B^2}{(VA)_B} = \frac{(3 \times 10^3)^2}{100 \times 10^3} = 90 \Omega \right]$$

Heater $(VA)_{p.u.} = S_{(p.u.)} = \frac{S}{S_B} = \frac{250 \times 10^3}{100 \times 10^3} = 2.5;$

p.u. current of (R) is given by

$$I_{R(p.u.)} = \frac{V_{(p.u.)}}{R_{(p.u.)}} = \frac{2.000}{1.111} = 1.8$$

$$I_{H(p.u.)} = \frac{\text{Heater power (p.u.)}}{V_{(p.u.)}} = \frac{S_{(p.u.)}}{V_{(p.u.)}} = \frac{2.5}{2.0} = 1.25$$

\therefore p.u. currents of the 100 ohm resistor is 1.8 p.u. while that of the heater is 1.25 p.u.

Total p.u. current $I_{(p.u.)}$ drawn from the supply is $1.8 + 1.25 = 2.05$

Per unit power of (R) is obtained as $S_{(p.u.)}$ of resistor $= V_{(p.u.)} \times I_{R(p.u.)} = 2 \times 1.8 = 3.6$, while the p.u. power of heater is $S_{(p.u.)}$ [of heater] $= V_{(p.u.)} \times I_{H(p.u.)} = 2 \times 1.25 = 2.5$

Actual power loss in the resistor is obtained as

$$\begin{aligned} S_H &= S_B \times S_{H(p.u.)} \\ &= 100 \text{ kVA} \times 2.5 = 250 \text{ kVA} (= 250 \text{ kW}) \end{aligned}$$

$$[\text{Also } S_H = (I_H(p.u.) \times I_b)^2 \times R_H(p.u.) \times Z_B \quad (\because \text{loss} = I^2 R)]$$

$$= \left(1.25 \times \frac{(VA)_B}{V_B} \right)^2 \frac{V(p.u.)}{I_H(p.u.)} \times R_B \quad (\because Z_B = R_B)$$

$$= \left(1.25 \times \frac{100 \times 10^3}{3 \times 10^3} \right)^2 \times \frac{2}{1.25} \times 90$$

$$= 250 \text{ kVA} (= 250 \text{ kW}) \text{ (for a resistive circuit)}$$

Actual line current is

$$\begin{aligned}
 I &= I(\text{p.u.}) \times I_B \\
 &= 2.05 \times \frac{(VA)_B}{V_B} = 2.05 \times \frac{100 \times 10^3}{3 \times 10^3} \\
 &= 68.333 \text{ A.}
 \end{aligned}$$

1.2 A sample 3-phase power system is displayed in Fig. 1.3. The component ratings are as shown in Table 1.3.

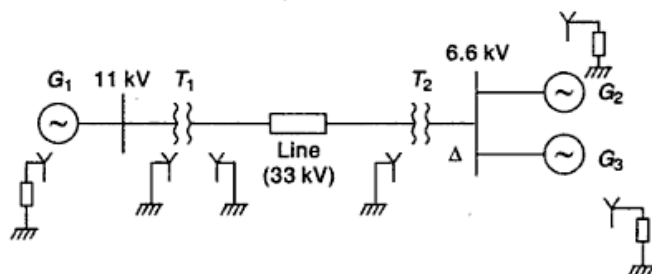


Fig. 1.3 A sample power system

Table 1.3 Component rating

Item	Power	Voltage (L-L)	Reactance
Generator no. 1 (G_1)	30 MVA	10.5 kV	2 Ω
Generator no. 2 (G_2)	20 MVA	6.6 kV	1.8 Ω
Generator no. 3 (G_3)	10 MVA	6.6 kV	1.2 Ω
Transformer no. 1 (T_1)	20 MVA	11 kV/33 kV	15 Ω on HT side
Transformer no. 2 (T_2)	20 MVA	6.6 kV/33 kV	18 Ω on HT side
Line	—	—	20 Ω /phase

Assuming 25 MVA is the base power and 33 KV the base voltage, find the p.u. reactances of the sample system components on a common base and hence draw the reactance diagram.

Solution

The voltage base of G_1 is 11 kV while the voltage base of G_2 and G_3 is 6.6 kV.

\therefore for G_1 , $X_{G1} = 2 \Omega$ (given), $MVA_B = 25 \text{ MVA}$, and $V_B = 11 \text{ kV}$.

$$\therefore I_B = \frac{MVA_B \times 10^6}{KV_B \times 10^3} = \frac{25 \times 10^6}{11 \times 10^3} = 2272.73 \text{ A}$$

$$\text{Thus, } X_{\text{base}(G_1)} = \frac{V_B}{I_B} = \frac{11 \times 10^3}{2272.73} = 4.84 \Omega$$

$$\text{while } X(\text{p.u.})_{G_1} = \frac{X_{G1}}{X_{\text{base}(G_1)}} = \frac{2}{4.84} = 0.413.$$

Next, for G_2 and G_3 ,

$$I_B = \frac{MVA_B \times 10^6}{KV_B \times 10^3} = \frac{25 \times 10^6}{6.6 \times 10^3} = 3.788 \times 10^3 \text{ A}$$

$$X_{\text{base}(G_2)} = \frac{V_B}{I_B} = \frac{6.6 \times 10^3}{3.788 \times 10^3} = 1.742 \Omega$$

$$\therefore X_{(\text{p.u.})G_2} = \frac{X_{s_2}}{X_{\text{base}(G_2)}} = \frac{1.8}{1.792} = 1.034$$

$$\text{and } X_{(\text{p.u.})G_3} = \frac{X_{s_3}}{X_{\text{base}(G_3)}} = \frac{1.2}{1.792} = 0.689.$$

For T_1 and T_2 ,

$$V_B = 33 \text{ KV, } MVA_B = 25 \text{ MVA}$$

$$\therefore I_B = \frac{MVA_B}{V_B} = \frac{25 \times 10^6}{33 \times 10^3} = 0.758 \times 10^3 \text{ A}$$

$$X_{\text{base}(T_1)} = X_{\text{base}(T_2)} = \frac{V_B}{I_B} = \frac{33 \times 10^3}{0.758 \times 10^3} = 43.54 \Omega.$$

$$\text{For } T_1, X_{T_1(\text{p.u.})} = \frac{X_{T_1}}{X_{\text{base}(T_1)}} = \frac{15}{43.54} = 0.345.$$

$$\text{For } T_2, X_{T_2(\text{p.u.})} = \frac{X_{T_2}}{X_{\text{base}(T_2)}} = \frac{18}{43.54} = 0.413.$$

For transmission line,

$$V_B = 33 \text{ KV; } MVA_B = 25 \text{ MVA}$$

$$\therefore I_B = \frac{25 \times 10^6}{33 \times 10^3} = 0.758 \times 10^3 \text{ A}$$

$$X_{\text{base}(\text{line})} = \frac{V_B}{I_B} = \frac{33 \times 10^3}{0.758 \times 10^3} = 43.54 \Omega$$

$$\text{Thus, } X_{\text{line}(\text{p.u.})} = \frac{X_L}{X_{\text{base}(\text{line})}} = \frac{20}{43.54} = 0.459.$$

The reactance diagram is shown in Fig. 1.4. (Figures are in p.u. reactances)

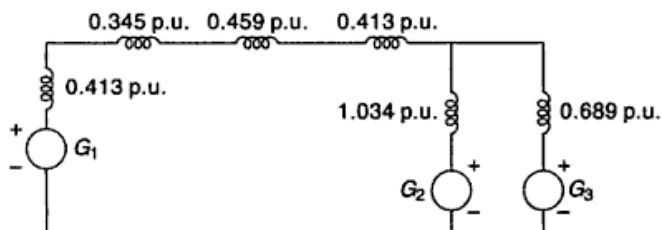


Fig. 1.4 Reactance diagram

1.3 Express the p.u. impedance ($Z_{p.u.}$) and the p.u. admittance ($Y_{p.u.}$) of an electric power network in terms of the base voltage (V_B) and base voltamperes ($(VA)_B$).

Solution

$$Z_B = \frac{V_B}{I_B} = \frac{V_B}{\left(\frac{(VA)_B}{V_B}\right)} = \frac{V_B^2}{(VA)_B}$$

Also
$$Z_{p.u.} = \frac{Z_{(actual)}}{Z_{base}} \left(= \frac{Z}{Z_B} \right) = \frac{Z (VA)_B}{V_B^2}$$

$$Y_{p.u.} = \frac{1}{Z_{p.u.}} = \frac{Y V_B^2}{(VA)_B}$$

1.4 A 11 kV overhead line has a series impedance of 25Ω and shunt admittance of 0.02 mho. Assuming the base power to be 25 MVA and line voltage as base voltage, find the p.u. impedance and p.u. admittance of the line.

Solution

$$Z_{p.u.} = \frac{Z}{Z_B}$$

but
$$Z_B = \frac{V_B}{I_B} = \frac{V_B^2}{(VA)_B}$$

Here,
$$Z_B = \frac{(11 \times 10^3)^2}{25 \times 10^6} = 4.84 \Omega$$

\therefore
$$Z(p.u.) = \frac{25 \Omega}{4.84 \Omega} = 5.165$$

$$Y(p.u.) = \frac{Y}{Y_B} = Y \times Z_B = 0.02 \times 4.84 = 0.097 \text{ mho.}$$

1.5 A 5 kVA, 220 V alternator has a reactance of 10 Ω . Using the rated kVA and voltage as base values, obtain the p.u. reactance. Then refer this p.u. value to a 230 V, 7.5 kVA base.

Solution

For the first base (5 kVA, 220 V),

$$V_B = 220 \text{ V} = 1 \text{ p.u.}; S_B = (VA)_B = 5 \text{ kVA}$$

$$\therefore I_B = \frac{S_B}{V_B} = \frac{5 \times 10^3}{220} = 22.73 \text{ A} = 1 \text{ p.u.}$$

$$X_{B(\text{base reactance})} = \frac{V_B}{I_B} = \frac{220}{22.73} = 9.679 \Omega;$$

$$\text{p.u. reactance} = X(\Omega)/X_B = 10/9.679 = 1.033.$$

For 230 V, 7.5 kVA base, we obtain

$$\begin{aligned} X_{\text{p.u. (new base)}} &= X_{\text{old (p.u.)}} \times \left(\frac{V_{\text{old}}}{V_{\text{new}}} \right)^2 \left(\frac{(VA)_B(\text{new})}{(VA)_B(\text{old})} \right) \\ &= 1.033 \times (220/230)^2 \times (7500/5000) = 1.418. \end{aligned}$$

.....

1.5 CONCEPT OF CURRENT FLOW

In an energy source (say, a battery) there is a potential difference (p.d.) between the positive (“+ve” or “+”) and negative (“-ve” or “-”) terminals measured in volts. When there is no external connection between these two terminals, this potential difference is the “emf” of the cell. The potential difference is due to an excess of electrons at the negative terminal with respect to the positive terminal.

As soon as these two terminals (+ve and -ve) are connected by a conductor, the p.d. causes an electric current to flow in the circuit. This current is composed of a steady stream of electron coming out of the negative terminal and passing through the wire and re-entering the battery through its positive terminal. Though the direction of flow of the electrons in the circuit is from -ve to +ve terminal, the conventional direction of current flow is just taken as in the direction opposite to electron flow. Thus the flow of current in the circuit is always assumed to be from the +ve to the -ve polarity.

1.6 CONCEPT OF SOURCE AND LOAD

A ‘source’ delivers electric power (or energy) while a ‘load’ absorbs it. Usually a resistor, an inductor, a motor, etc. can be treated as loads while a generator, battery, etc. can be treated as source. However, it is interesting to note that a number of devices like a motor, a capacitor, and inductor and some other electric devices can act both as source and load (only exception is a resistor which can act as a load only; similarly a photocell can act as a source only). Take the example of a capacitor; when it is charged, it acts as a load, but during discharging it acts as a source. During charging current enters into it through a particular terminal which develops +ve polarity. During discharging current comes out from the +ve

polarity and it then acts as a source. Similar things happens for a battery. During charging, current enters through the positive polarity and the battery becomes a load while during discharging, current comes out of this positive polarity and the battery acts as a source. Thus, in a general sense we can say:

- in a load current enters the device through the positive terminal and
- in a source current comes out of the device from positive terminal.

In both the cases, the '+ve' polarity remains the same.

1.7 SIGN NOTATION FOR VOLTAGES

Usually we represent the positive terminal by (+) and having the higher potential while the negative terminal by (-) having the lower potential. If we use subscript, then it represents the potential of a particular point in the circuit (i.e., the node); i.e., we denote the voltage at point 'A' (say) in a circuit as (V_A) or (E_A). If $V_A = 10$ V it means point A has potential of 10 V (+ve). If (V_A) = -10 V, it means that polarity of point A is -ve and the magnitude of the potential is still 10 V. If we use double subscript we then represent the potential of that point with respect to another point; e.g., (V_{AB}) = 10 V means the potential difference between points A and B in a circuit is 10 V while point A is at a higher potential than that at point B. This means potential at A is higher and (+10) V with respect to the lower potential point B. If we say (V_{AB}) = -10 V, it means, the voltage between A and B is still 10 V but point A is negative with respect to point B (i.e., point B has higher potential than point A). It may be remembered that a voltage (V_{AB}) can always be represented by the voltage ($-V_{BA}$).

1.8 CONCEPT OF POSITIVE AND NEGATIVE CURRENTS AND VOLTAGES

A current flow is said to be +ve when the current comes out from the +ve polarity of the device while it is said to be -ve when it enters the device through the +ve polarity. Thus in a junction point in a circuit, a current is positive when it comes out of the junction and is negative when it approaches the junction, the voltage at the junction being +ve. In Fig. 1.5(a), (I_1) and (I_2) are +ve currents while (I_3) and (I_4) are -ve currents.

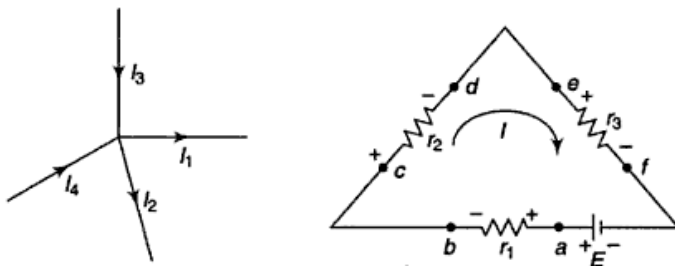


Fig. 1.5(b)

Fig. 1.5(a) Illustration of +ve and -ve currents and voltage drops

We next focus our attention to a closed loop circuit as shown in Fig. 1.5(b). A battery of emf E circulates a current I through a circuit having series resistances r_1 , r_2 and r_3 . The drops (Ir_1) , (Ir_2) and (Ir_3) are taken as the +ve voltages as current through the resistors r_1 , r_2 and r_3 passes from the +ve to -ve polarity of each of the elements (since current passes from higher potential to lower potential, points a , c and e are higher potentials than their corresponding points b , d and f respectively). Thus, the voltage drop in a load is +ve provided current flows within the device through its +ve to -ve polarity. On the other hand, for the battery, current flows through -ve to +ve terminal within the battery and thus this voltage (E) is -ve. These conventions are important in understanding and dealing with Kirchhoff's current and voltage laws described in the chapter 'DC Network Analysis' later in this book.

1.9 OHM'S LAW AND CONCEPT OF RESISTANCE

Ohm's law states that electric current flowing through a conductor is directly proportional to the potential difference between its two ends when the temperature and other physical parameters of the conductor remains unchanged.

Assuming (V_{AB}) be the p.d. between the two ends A and B of a conductor, with terminal A at higher potential, current (I) being flowing through the conductor, we can write as per Ohm's law

$$V_{AB} \propto I$$

or, $V_{AB} = R.I$ (1.5)

(R) being the *resistance* of the conductor (the constant in the equation of proportionality).

Thus, $R = V/I$; (V_{AB}) being generalised as (V), i.e., resistance = volt/ampere

Ohm is the unit of resistance, the symbol being Ω (Greek capital letter "omega"). If 1 ampere flows through a conductor, the voltage difference being 1 V across its two ends, the resistance of the conductor is then said to be 1 Ω .

[The reciprocal of resistance is called *conductance* (G). The resistance of the conductor being the property of it which opposes the current flow through it, conductance is the property that assists current flow through it. Obviously,

$$G = \frac{1}{R}.$$

The unit of conductance is mho or Siemens and following Ohm's law,

$$V = IR \quad \text{or,} \quad I = \frac{V}{R} = VG \quad (1.6)$$

1.10 CONCEPT OF RESISTIVITY

Let us consider a conductor of length ' l ' m and area of cross-section ' a ' m^2 having the resistance (R) ohm. It can be written,

$$R \propto l, \text{ when 'a' is constant}$$

$$R \propto \frac{1}{a}, \text{ when 'l' is constant.}$$

Combining the two equations of proportionality,

$$R \propto \frac{l}{a} \text{ when both 'l' and 'a' are not constant (i.e. varying)}$$

$$\therefore R = \rho \frac{l}{a} \quad (1.7)$$

(ρ) being the constant of proportionality; ρ (rho) is known as *resistivity* of the material.

$$\text{If } l = 1 \text{ m; } a = 1 \text{ m}^2, R = \rho.$$

Also, $\rho = \frac{R \cdot a}{l} = \frac{\Omega \times \text{m}^2}{\text{m}} = \Omega \cdot \text{m}$ (unit of resistivity is thus $\Omega \cdot \text{m}$). We also introduce another term here, known as *conductivity* (σ) (reciprocal of resistivity).

$$\sigma = \frac{1}{\rho}$$

The unit of conductivity is Siemens (or mho)

$$\text{Also, } \sigma = \frac{1}{\rho} = \frac{1}{\frac{lG}{a}} = \frac{lG}{a} \quad (1.8)$$

Unit of conductivity is Siemens/m.

1.11 EXPRESSIONS OF POWER AND ENERGY IN RESISTIVE CIRCUITS

If I be the strength of current in a resistive circuit, (V) being the potential difference across the terminals of the conductor having resistance (R) in the circuit, the power absorbed by the resistor is given by

$$P = VI = (IR) I = I^2 R = \frac{V^2}{R} \text{ W} \quad (1.9)$$

and the energy dissipated in the resistance (in form of heat) is then obtained as

$$W = \int_0^t P \cdot dt = Pt = I^2 R \times t = \left(\frac{V^2}{R} \times t \right) \text{ Joule} \quad (1.10)$$

Joule is the basic unit of electrical energy but commercially we frequently use a bigger unit kWhr; it is a practical unit of electrical energy and is called *Board of Trade Unit* (BOT), 1 kWhr = BOT. Also, 1 kWhr = 1 kW \times 1 Hr = 1000 \times 60 \times 60 W.sec = 36 \times 10⁵ W.sec = 36 \times 10⁵ J.

[It may be noted here that if the power absorbed by an element (or device) is found to be -ve, we can say that the element is delivering power to the circuit without absorbing power in real sense. Power is absorbed when current enters through the positive polarity of the device while power is delivered when the current comes out of the device from its positive terminal.]

1.6 A copper conductor of circular cross-section has length 10 m and diameter 2 mm. Calculate its resistance if the resistivity of copper is given as $1.72 \times 10^{-8} \Omega \cdot \text{m}$.

Solution

$$R = \frac{\rho l}{a} = \frac{1.72 \times 10^{-8} \times 10}{\frac{\pi \times (2 \times 10^{-3})^2}{4}} = \frac{6.88 \times 10^{-7}}{12.56 \times 10^{-6}} = 0.0548 \Omega$$

1.7 A cube has resistivity of its material as $1.1 \times 10^{-6} \Omega \cdot \text{m}$. If it has all sides of length 2 cm each, determine the resistance of the cube between any two faces.

Solution

$$R = \frac{\rho l}{a} = \frac{1.1 \times 10^{-6} \times 2 \times 10^{-2}}{(2 \times 10^{-2})^2} = \frac{1.1 \times 10^{-6}}{2 \times 10^{-2}} \\ = 0.55 \times 10^{-4} \Omega = 55 \mu\Omega.$$

1.8 A conductor is 50 m long. It has a cross-sectional area of 2 mm^2 while it offers a resistance of 10Ω . Find the conductivity of the material.

Solution

$$\sigma = \frac{1}{\rho} = \frac{l}{R \cdot a} = \frac{50}{10 \times 2 \times (10^{-3})^2} \\ = 2.5 \times 10^6 \text{ Siemens/m} \\ = 2.5 \text{ MS/m} \quad [\because 10^6 = 1 \text{ Mega} = 1 \text{ M}]$$

1.9 Among two cubes, the first one has a length of $l \text{ m}$ while the second one has a length of $2l \text{ m}$. Find the ratio of conductivities of the materials of the cubes so that the resistance between any two faces of one cube is the same as that of the other cube.

Solution

We have seen in the text that.

$$\sigma (\text{conductivity}) = \frac{1}{\rho}$$

$$\therefore \sigma = \frac{l}{R \cdot a} \quad \text{or} \quad R = \frac{l}{\sigma \cdot a}$$

Here, for the cubes,

$$R_1 = \frac{l}{\sigma_1 l^2} = \frac{1}{l \sigma_1}$$

$$\text{and} \quad R_2 = \frac{2l}{\sigma_2 (2l)^2} = \frac{1}{2l \sigma_2}$$

$$\therefore \frac{R_1}{R_2} = \frac{2 \sigma_2}{\sigma_1} = 1 \quad [\because \text{as per given question } R_1 = R_2]$$

$$\therefore \frac{\sigma_1}{\sigma_2} = 2.$$

1.10 A rectangular bus bar is made of aluminium and is 90 cm long, 10 cm wide and 1 cm thick. If the bus bar current flows along its length, find the bus bar conductance provided the bus bar conductivity is 3.6×10^8 S/m.

Solution

$$R = \frac{l}{\sigma \cdot a} = \frac{0.9}{(3.6 \times 10^8)(0.1 \times 1 \times 10^{-2})} = 2.5 \times 10^{-6} \Omega$$

$$\therefore G(\text{Conductance}) = \frac{1}{R} = 0.4 \times 10^6 \text{ S.}$$

.....

1.11 How many electrons pass a given point in a conductor in 10 sec if the current strength is 18 A? Assume charge of electron as 1.6×10^{-19} C.

Solution

Charge (Q) = $I \times t$ (I = Current strength; t = time in sec)

Here $Q = 18 \times 10 = 180$ C.

$\therefore 1.6 \times 10^{-19}$ C corresponds to charge of one electron, 180 C of charge would have

$$\left(\frac{1}{1.6 \times 10^{-19}} \times 180 \right), \text{ i.e. } 112.5 \times 10^{19}.$$

.....

1.12 A charge of 400 C passes through a conductor in 40 sec. What is the corresponding current in amperes?

Solution

$$Q = I \times t$$

$$\therefore I = \frac{Q}{t} = \frac{400}{40} = 10 \text{ A.}$$

.....

1.13 What is the p.d. across a resistance dissipating 50 W of power while the strength of current is 5 A? What is the ohmic value of the resistance?

Solution

$$V = \frac{\text{Watt}}{\text{Current}} = \frac{50}{5} = 10 \text{ V}$$

Watt (power dissipated) = $I^2 R$

$$\therefore R = \frac{W}{I^2} = \frac{50}{5^2} = 2 \Omega$$

.....

1.14 A current of 10 A flows in a resistor for 10 sec. How many coulombs of charge pass within this time?

Solution

$$Q = I \times t = 10 \times 10 = 100 \text{ C}$$

.....

1.15 An electric heater consumes 1 kWhr of energy in 30 min at 220 V. What is the current rating of the heating element?

Solution

$$\begin{aligned}
 \text{Current, } I &= \frac{\text{Power}}{\text{Voltage}} = \frac{\text{Energy/Time}}{\text{Voltage}} \\
 &= \frac{1 \times 10^3 / 0.5}{220} \quad [\because \text{time} = 30 \text{ min} = \frac{1}{2} \text{ hr}] \\
 &= 9.09 \text{ A.}
 \end{aligned}$$

1.16 An energy source supplies 500 J of energy at 100 V for a certain period of time. Determine the quantity of charge passed through.

Solution

$$Q = I \times t = \frac{\text{Power}}{\text{Voltage}} \times \text{Time} = \frac{\text{Energy}}{\text{Voltage}} = \frac{500}{100} = 5 \text{ C}$$

1.12 TEMPERATURE COEFFICIENT OF RESISTANCE

The resistance of almost all electricity conducting materials changes with the variation in temperature. This variation of resistance with change in temperature is governed by a property of a material called *temperature coefficient of resistance* (α). The temperature coefficient of resistance can be defined as the change in resistance per degree change in temperature and expressed as a fraction of the resistance at the reference temperature considered.

If suffix 1 indicates the initial condition and suffix 2 the final condition, we can write, from the definition of the temperature coefficient of resistance,

$$\begin{aligned}
 \alpha_1 &= \frac{\text{Change in resistance/Change in temperature}}{\text{resistance at the reference temperature}} \\
 &= \frac{(R_2 - R_1)/(t_2 - t_1)}{R_1}
 \end{aligned} \tag{1.11}$$

while α_1 is the *temperature coefficient* of the material at t_1 °C.

Similarly, at temperature t_2 °C, the temperature coefficient of resistance being expressed as α_2 , we can write

$$\alpha_2 = \frac{(R_2 - R_1)/(t_2 - t_1)}{R_2} \tag{1.12}$$

It is usual to specify the reference temperature as 0 °C while the temperature coefficient of resistance is α_0 . If t °C is the rise in temperature and the resistance changes from R_0 (at 0 °C) to R_t and t °C, we can write

$$\alpha_0 = \frac{(R_t - R_0)/(t - 0)}{R_0} = \frac{R_t - R_0}{R_0 t}$$

$$\begin{aligned} \text{or, } (R_t - R_0) &= R_0 \alpha_0 t \\ \therefore R_t &= R_0 + \alpha_0 R_0 t \\ &= R_0(1 + \alpha_0 t) \end{aligned} \quad (1.13)$$

Again from equations (1.11) and (1.12) we find

$$\begin{aligned} \frac{\alpha_2}{\alpha_1} &= \frac{R_1}{R_2} = \frac{R_1}{R_1 [1 + \alpha_1 (t_2 - t_1)]} \\ \therefore \alpha_2 &= \frac{\alpha_1}{1 + \alpha_1 (t_2 - t_1)} = \frac{1}{\frac{1}{\alpha_1} + (t_2 - t_1)} \end{aligned} \quad (1.14)$$

In general, if the reference temperature is 0°C , for $t^\circ\text{C}$ rise in temperature we can write

$$\alpha_t = 1 / \frac{1}{\alpha_0} + (t - 0) = 1 / \frac{1}{\alpha_0} + t \quad (1.15)$$

The unit of α is $\Omega/\Omega^\circ\text{C}$, i.e. per $^\circ\text{C}$; e.g the temperature coefficient of resistance of copper is

$$\alpha_0 = \frac{1}{234.5} / ^\circ\text{C}$$

[It may be noted here that though the temperature coefficient of resistance has a +ve value for all metallic conductors, some of the non-metallic conductors (e.g carbon) has -ve temperature coefficient of resistance; α is -ve for these elements.]

Effect of Temperature on Resistance

The temperature coefficient of resistance (α) being given by

$$\alpha_0 = \frac{R_t - R_0}{R_0 t}$$

t will be positive for rise in temperature of the resistance from 0°C to $t^\circ\text{C}$. If $R_t > R_0$, α_0 is +ve and the profile of R_t versus t can be plotted as show in Fig. 1.6.

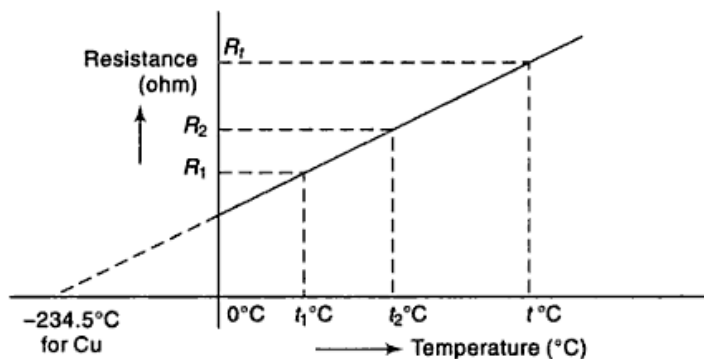


Fig 1.6 Resistance-temperature graph

The profile of R_t vs t is a straight line. If we assume $\alpha_0 = 0$, $(R_t - R_0)$ tends to zero and this given $R_t = R_0$, then we can say if the temperature coefficient of resistance for a conductor is negligible, the resistance of that conductor remains same for any variation of temperature. All metallic conductors have a positive temperature coefficient of resistance while non-metals, electrolytes and liquid conductors have a negative temperature coefficient of resistance. Semiconductors and insulators also have negative temperature coefficients. A few alloys like constantan, nickel chromium, manganin and eureka have almost zero temperature coefficient of resistance. The resistance of those conductors increase with increase in temperature whose temperature coefficient of resistance is +ve while the resistance of those conductors decrease with increase in temperatures whose temperature coefficient of resistance is -ve.

1.17 A piece of copper wire has a resistance of 25Ω at 10°C . What is the maximum operating temperature if the resistance of the wire is to be increased by 20%? Assume α at $10^\circ\text{C} = 0.0041^\circ\text{C}^{-1}$.

Solution

$$R_1 = 25 \Omega; t_1 = 10^\circ\text{C}; \alpha_1 = 0.0041/^\circ\text{C}$$

$$R_2 = 25 + 0.2 \times 25 = 30 \Omega$$

t_2 = the unknown temp. at which R will be 30Ω .

Since $R_2 = R_1 [1 + \alpha_{t_1}(t_2 - t_1)]$,

here we have

$$R_2 = R_1 [1 + \alpha_{t_1}(t_2 - t_1)]$$

$$\therefore 30 = 25 [1 + 0.0041 \times (t_2 - 10)]$$

$$\text{or } t_2 - 10 = \left(\frac{30}{25} - 1\right) \times \frac{1}{0.0041}$$

$$\therefore t_2 = 58.78^\circ\text{C}.$$

.....

1.18 A particular metal filament has a resistance of 10Ω at 0°C . At 20°C the resistance become 12Ω . Calculate the temperature coefficient of resistance of that filament at 20°C . What is the temperature coefficient at 0°C ?

Solution

In the text we have seen

$$\alpha_t = \frac{R_t - R_0}{R_0 \cdot t}$$

On simplification we may write

$$R_0 = R_t (1 - \alpha_t \cdot t)$$

Here, $R_0 = 10 \Omega$; $R_t = 12 \Omega$

$$t = 20^\circ\text{C} [= (t_2 - t_1) = (20 - 0)^\circ\text{C}]$$

Hence $10 = 12 (1 - \alpha_t \cdot 20)$

or $10 = 12 - 12 \times 20 \times \alpha_t$

$$\therefore \alpha_t = \frac{12 - 10}{12 \times 20} = 0.00833/^\circ\text{C},$$

i.e. $\alpha_{20} = 0.00833/^{\circ}\text{C}$.

Also, $R_t = R_0(1 + \alpha_0 t)$

[as derived in the text.]

Here, $12 = 10(1 + \alpha_0 \times 20)$

$$\therefore \alpha_0 = \left(\frac{12}{10} - 1 \right) \times \frac{1}{20} = 0.01/^{\circ}\text{C}^{-1}$$

i.e. temperature coefficient at 0°C is $0.01/^{\circ}\text{C}$.

1.19 The temperature coefficient of carbon at 0°C is $-0.000515/^{\circ}\text{C}^{-1}$ and that of platinum is $0.00357/^{\circ}\text{C}^{-1}$ at 40°C . A carbon filament has a resistance of $10\ \Omega$ while the platinum foil has a resistance of $8\ \Omega$ at 0°C . At what temperature will the two elements have the same resistance?

Solution

$$\alpha_0 = \frac{R_t - R_0}{R_0 t}$$

$$\text{or } \alpha_0 R_0 t = R_t - R_0 \quad R_t = R_0(1 + \alpha_0 t) \quad (1)$$

$$\text{and } \alpha_t = \frac{R_t - R_0}{R_t \cdot t}$$

$$\therefore R_t \cdot \alpha_t \cdot t = R_t - R_0 \quad \text{or } R_0 = R_t(1 - \alpha_t t) \quad (2)$$

We can write, using equation (1) in (2)

$$R_0 = R_0(1 + \alpha_0 t)(1 - \alpha_t t)$$

$$\text{or } \alpha_0 - \alpha_t - \alpha_0 \alpha_t t = 0 \quad (3)$$

$$\text{or } \alpha_0 = \alpha_t(1 + \alpha_0 t) \quad (4)$$

$$\therefore \alpha_t = \frac{\alpha_0}{1 + \alpha_0 t}$$

Also, from (3),

$$\alpha_0(1 - \alpha_t \cdot t) = \alpha_t$$

$$\therefore \alpha_0 = \frac{\alpha_t}{1 - \alpha_t \cdot t} \quad (5)$$

In this problem the (α) value at 0° is given for carbon but the α value of platinum is provided for 40°C . Thus (α) of platinum at 40°C is to be converted to (α) at 0°C for platinum.

\therefore For platinum,

$$\alpha_0 = \frac{0.00357}{1 - 40 \times 0.00357} = 0.00416/^{\circ}\text{C}^{-1}.$$

Let the resistances of the carbon and platinum filaments be equal at $t^{\circ}\text{C}$.

$\therefore R_t = R_0(1 + \alpha_0 t)$, we can write

$$8(1 + 0.00416 t) = 10(1 - 0.000515 \cdot t).$$

[Note that α_0 for platinum is $0.00416/^{\circ}\text{C}$ as obtained and that of carbon is given as $(-0.000515/^{\circ}\text{C})$]

$$\text{or } 8 + 0.03328t = 10 - 0.00515 t$$

$$\text{or } 0.03843t = 2 \quad \therefore t = 52.043^{\circ}\text{C}.$$

Then at 52.043°C , the resistances of both the filaments are equal.

1.20 The power consumed by a heating element made of copper wire is 250 W at 220 V and at 30 °C. Obtain the power consumed by the same element at 220 V and 100 °C. The temperature coefficient of the element at 30 °C is 0.004 °C⁻¹.

Solution

$$\text{Power loss at } 30^\circ\text{C} (P_{30}) = \frac{V^2}{R_{30}}$$

$$\therefore R_{30} = \frac{V^2}{P_{30}} = \frac{220^2}{250} = 193.6 \Omega.$$

We know,

$$R_{100^\circ\text{C}} = R_{30^\circ\text{C}} [1 + \alpha_{30}(100^\circ\text{C} - 30^\circ\text{C})].$$

From the given data

$$R_{100^\circ\text{C}} = 193.6(1 + 0.004 \times 70) = 247.81 \Omega.$$

\therefore Power loss at 100 °C is obtained as

$$\begin{aligned} P_{100^\circ\text{C}} &= \frac{220^2}{247.81} \quad (\because \frac{V^2}{R} \text{ is power loss}) \\ &= 195.31 \text{ W.} \end{aligned}$$

[Note that with increase of temperature, voltage applied being the same, power dissipated is reduced though the resistance term in (I^2R) is increased. Since current has predominant effect in power loss than resistance hence with increase of temperature when resistance increases, current decreases and hence power loss decreases.]

1.21 A resistor is made up of Alloy 1 dissipating 50 W of electrical power at 110 V at 20°C. Another resistance of Alloy 2 is made having the same resistance as the first resistor but consuming double amount the power of the first one. What is the current flowing through Alloy 2 resistor? Assume temperature remain constant during the entire process.

Solution

$$R_{\text{alloy 1}} = \frac{V^2}{P} = \frac{110^2}{50} = 242 \Omega$$

As per question, $R_{\text{alloy 2}} = R_{\text{alloy 1}}$

Let I be the current flowing through the Alloy 2 resistor.

$\therefore I^2 R_2 = 2 \times 50$. [$\because P_{\text{loss}}$ in the second one is twice than that of alloy-1.]

$$\therefore I^2 = \frac{100}{242}.$$

and $I = 0.643 \text{ A}.$

1.22 A heat-dissipating wire dissipates 100 W at 50°C when subjected to applied voltage of 220 V. If the wire diameter is 0.01 mm and resistivity is $2 \times 10^{-8} \Omega \cdot \text{m}$, find the length of the wire assuming the temperature coefficient of resistance at 20°C as 0.005°C⁻¹.

Solution

$$\text{At } 50^\circ\text{C}, \quad R_{50} = \frac{V^2}{P} = \frac{220^2}{100} = 484 \Omega.$$

$$\text{Also} \quad R_{50} = R_{20}[1 + \alpha_{20}(50 - 20)]$$

or $484 = R_{20}[1 + 0.005 \times 30].$

$\therefore R_{20} = \frac{484}{3.42} = 141.52 \, \Omega.$

But $R_{20} = \frac{\rho l}{a} = \frac{2 \times 10^{-8} \times l}{\frac{\pi}{4}[(0.01)^2 \times 10^{-6}]}$

$[\because d = 0.01 \text{ mm} = 0.01 \times 10^{-3} \text{ m}.]$

$\therefore l = \frac{141.52 \times \frac{\pi}{4}[(0.01)^2 \times 10^{-6}]}{2 \times 10^{-8}}$

$= 0.5555 \text{ m}.$

Thus, the required length is 0.5555 m.

1.23 A non-metallic resistor has temperature coefficient of resistance of $-0.0005/^\circ\text{C}$ at 20°C . It dissipates 50 W power while drawing 1 A current at 20°C . It is now connected to a 230 V source at 100°C . What will be the power dissipation?

Solution

At 20°C , $P_{20} = I^2 R_{20}$

$\therefore R_{20} = \frac{50}{1.0^2} = 50 \, \Omega$

At 100°C , $R_{100} = R_{20}[1 + \alpha_{20} \cdot t]$

Here $R_{100} = 50[1 - 0.0005(100 - 20)]$
 $= 48 \text{ ohm}.$

$\therefore P \text{ (Power loss at } 100^\circ\text{C)} = \frac{V^2}{R_{100}} = \frac{(230)^2}{48} \approx 1102 \text{ W}.$

■ ADDITIONAL EXAMPLES ■

1.24 A heater is operated at 220 V and has an efficiency of 99%. The energy consumed is 1.5 kWhr in one hour. If it is required to boil a liquid that requires 100 kJ of energy, find the time needed to boil it. What is the resistance of the heater?

Solution

Let I be the input current to the heater.

$$I = \frac{\text{Power}}{\text{Voltage}} = \frac{(\text{Energy/time})}{\text{Voltage}} = \frac{1.5 \times 10^3 / 1}{220} = 6.82 \text{ A}$$

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}} \times 100$$

Here $\frac{99}{100} = \frac{\text{Output}}{\text{Input}}$

To have an output energy of 100 kJ, the input is (Output \div 0.99), i.e. $100/0.99 = 101.01$ kJ.

But Energy = Power \times Time

\therefore Time = Energy \div Power

$$= \frac{101.01 \times 10^3}{220 \times 6.82} \quad [\because P = V \times I = 220 \times 6.82]$$

$$= 67.32 \text{ sec.}$$

Thus it will take 67.32 sec to boil the liquid. The heater resistance is obtained as

$$R = \frac{V}{I} = \frac{220}{6.82} = 32.26 \Omega.$$

1.25 The resistivity of a material at 0°C is $8 \times 10^{-8} \Omega \cdot \text{m}$, while it is $10 \times 10^{-8} \Omega \cdot \text{m}$ at 30°C . Assuming the resistivity versus temperature profile of the material to linear, find its resistivity at 10°C .

Solution

Since the resistivity-temperature curve of the given material is linear, hence the slope (m) can be expressed as

$$m = \frac{\rho_{30} - \rho_0}{t_{30} - t_0} = \frac{(10 - 8)10^{-8}}{30 - 0} = 0.067 \times 10^{-8}$$

Also, from this equation $m = \frac{\rho_{30} - \rho_0}{t_{30} - t_0}$, we get

$$\rho_{30} = \rho_0 + m(t_{30} - t_0).$$

Generalising this for temperature t_2 and t_1 when $t_2 > t_1$, we can write

$$\rho_{t_2} = \rho_{t_1} + m(t_2 - t_1)$$

where
$$m = \frac{\rho_{t_2} - \rho_{t_1}}{t_2 - t_1}.$$

Then for 10°C ,

$$\begin{aligned} \rho_{10} &= \rho_{20} + m(10 - 20) \\ &= 10 \times 10^{-8} + 0.067 \times 10^{-8} \times (-10) \\ &= 9.33 \times 10^{-8} \Omega \cdot \text{m}. \end{aligned}$$

Thus the resistivity of the material at 10°C is $9.33 \times 10^{-8} \Omega \cdot \text{m}$.

1.26 A given conductor has a resistor of 5Ω . What is the resistance of another conductor of the same material, which has one-half the diameter and five times the length of the given conductor?

Solution

$$R_1 = \rho \frac{l_1}{a_1}; \quad R_2 = \rho \frac{l_2}{a_2}$$

$$\therefore \frac{R_2}{R_1} = \frac{l_2}{l_1} \times \frac{a_1}{a_2}.$$

Here $a_1 = \pi \frac{d_1^2}{4}$; $a_2 = \pi \frac{d_2^2}{4}$

Also $d_2 = \frac{d_1}{2}$ (given)

$$\therefore \frac{a_1}{a_2} = \frac{d_1^2}{d_2^2} = \left(\frac{d_1}{d_2}\right)^2 = \left(\frac{d_1}{d_1/2}\right)^2 = 4$$

Also $l_2 = 5l_1$ or $\frac{l_2}{l_1} = 5$

$$\therefore \frac{R_2}{R_1} = \frac{l_2}{l_1} \times \frac{a_1}{a_2} = 5 \times 4 = 20.$$

$$\therefore R_1 = 5 \Omega \quad \therefore R_2 = R_1 \times 20 = 100 \Omega.$$

1.27 Obtain the ratio of powers lost in two resistors when

- each being connected across the same voltage
- each resistor is to carry the same current.

Assume same length and material for each resistor but the first one having a diameter twice that of the other. The cross-section of each of the resistor wire is circular.

Solution

- Voltage applied remains same for each resistor:

$$P_1 = \frac{V^2}{R_1} = \frac{V^2}{\rho l / a_1} = \frac{V^2 a_1}{\rho l} = \frac{\pi V^2 d_1^2}{4 \rho l}$$

Similarly, $P_2 = \frac{V^2}{R_2} = \frac{\pi V^2 d_2^2}{4 \rho l}$

Since $d_1 = 2d_2$,

$$\frac{P_1}{P_2} = \frac{\frac{\pi V^2 d_1^2}{4 \rho l}}{\frac{\pi V^2 d_2^2}{4 \rho l}} = \frac{d_1^2}{d_2^2} = \frac{4d_2^2}{d_2^2} = 4.$$

- Each resistor carries same current:

$$P_1 = I^2 R_1 = I^2 \times \rho \times \frac{l}{a_1} = \frac{4}{\pi} \cdot I^2 \cdot \frac{\rho l}{d_1^2}$$

Similarly, $P_2 = I^2 R_2 = \frac{4}{\pi} \cdot I^2 \cdot \frac{\rho l}{d_2^2}$

$\therefore d_1 = 2d_2$,

$$\frac{P_1}{P_2} = \frac{\frac{4}{\pi} \cdot I^2 \cdot \rho l / d_1^2}{\frac{4}{\pi} \cdot I^2 \cdot \rho l / d_2^2} = \frac{d_2^2}{d_1^2} = \frac{d_2^2}{4d_2^2} = \frac{1}{4}.$$

1.28. A copper wire having a cross-sectional area of 0.5 mm^2 and a length of 0.1 m is initially at 25°C and is thermally insulated from the surroundings. If a current of 10 A is set up in this wire,

- (a) Find the time in which the wire will start melting.
 (b) What will this time be, if the length of the wire is doubled?

Assume the resistance of the wire remains unaffected with variation in temperature. Density of copper is $9 \times 10^3 \text{ K/m}^3$; specific heat of copper = $9 \times 10^{-2} \text{ cal/(kg } ^\circ\text{C)}$ and melting point of copper is 1075°C . Specific resistance of copper is $1.6 \times 10^{-8} \Omega\text{m}$.

Solution

$$\begin{aligned} \text{(a) Mass of copper} &= \text{Volume} \times \text{Density} \\ &= 0.5 \times 10^{-6} \times 0.1 \times 9 \times 10^3 \\ &= 45 \times 10^{-5} \text{ kg.} \end{aligned}$$

Rise in temperature (0°C) is $(1075 - 25)^\circ\text{C}$, i.e. 1050°C .

Heat required (H) to melt the copper wire is

$$H = \frac{I^2 R t}{4.2}$$

[I = current in the wire having resistance R and t is the time in sec for which current flows]

However, from the concept of calorimetry,

$$H = ms\theta$$

[m = mass of wire, s = specific heat, θ = temp. rise].

$$\begin{aligned} \text{Also, } R &= \rho \frac{l}{a} = 1.6 \times 10^{-8} \times \frac{0.1}{0.5 \times 10^{-6}} \\ &= 3.2 \times 10^{-3} \Omega. \end{aligned}$$

$$\text{Since } \frac{I^2 R t}{4.2} = ms\theta, \text{ we have}$$

$$\frac{10^2 \times 3.2 \times 10^{-3} \times t}{4.2} = 45 \times 10^{-5} \times 9 \times 10^{-2} \times 1050$$

$$\text{or } t = 558 \text{ sec.}$$

- (b) Electric energy = $I^2 R t$. When the length of the wire is doubled, R is also doubled. However the mass remaining constant, H is also doubled. Hence the wire will melt in the same time.

1.29. A heating element is made of some material having the temperature coefficient of resistance an $0.00065^\circ\text{C}^{-1}$ at 0°C . What will be the ratio of its resistance at temperatures 50°C and 30°C ?

Solution

Ler R_0 be the resistance at 0°C for the element. At temperature θ_1° ; we can write

$$R_{\theta_1} = R_0[1 + \alpha_0(\theta_1^\circ - 0^\circ)]$$

while at temperature θ_2° we can write

$$R_{\theta_2} = R_0[1 + \alpha_0(\theta_2^\circ - 0^\circ)]$$

$$\begin{aligned} \therefore \frac{R_{\theta_1}}{R_{\theta_2}} &= \frac{1 + \alpha_0 \theta_1^\circ}{1 + \alpha_0 \theta_2^\circ} (1 + \alpha_0 \theta_1^\circ)(1 + \alpha_0 \theta_2^\circ)^{-1} \\ &= (1 + \alpha_0 \theta_1^\circ)[1 - \alpha_0 \theta_2^\circ + (\alpha_0 \theta_2^\circ)^2 - \dots] \end{aligned}$$

(1)

Since α_0 is small, we can neglect higher power of α_0 . Then we can write from eqn (1)

$$\frac{R_{\theta_1}}{R_{\theta_2}} = 1 + \alpha_0(\theta_1^\circ - \theta_2^\circ).$$

Here $\frac{R_{\theta_1}}{R_{\theta_2}} = 1 + 0.00065 (50^\circ - 80^\circ) = 0.9805$, where

$$\theta_1 = 50^\circ\text{C}; \quad \theta_2 = 80^\circ\text{C}.$$

1.30 A rectangular metal strip has dimensions $x = 100$ cm; $y = 1$ cm and $z = 0.5$ cm. Obtain the ratio of resistances R_x , R_y and R_z between respective pairs of opposite faces.

Solution

In Fig. 1.7, R_x = resistance along the length

$$= \rho \frac{x}{y \times z} \quad \left[\because R = \rho \frac{l}{a} \right]$$

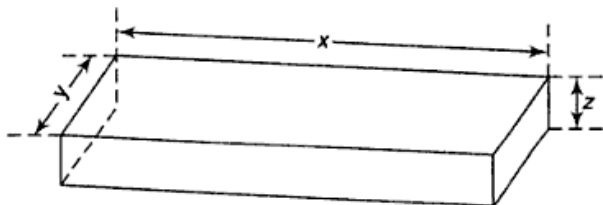


Fig. 1.7 A rectangular metal strip

$$R_y = \rho \frac{y}{zx} \quad [R_y = \text{resistance along the breadth}]$$

and $R_z = \frac{z}{x \times y} \quad [R_z = \text{resistance along the thickness}]$

$$\begin{aligned} \therefore R_x : R_y : R_z &= \frac{\rho x}{yz} : \frac{\rho y}{zx} : \frac{\rho z}{xy} = \frac{x}{yz} : \frac{y}{zx} : \frac{z}{xy} \\ &= \frac{100}{1 \times 0.5} : \frac{1}{0.5 \times 100} : \frac{0.5}{100 \times 1} \\ &= 200 : \frac{1}{50} : \frac{1}{200} \\ &= 40,000 : 4 : 1. \end{aligned}$$

1.31 Temperature of a heating element is governed by the relation $\theta^\circ\text{C} = 20t$, t being expended in seconds. The temperature coefficient of the material at 0°C is $0.0005^\circ\text{C}^{-1}$. If the initial resistance of the heating element is $5\ \Omega$, find the energy dissipated in the heating element over 10 sec period of time. The applied voltage is $220\ \text{V}$ (dc).

Solution

At $t = 0$, $\theta^\circ\text{C} = 20 \times 0 = 0^\circ\text{C}$ [$\because \theta = 20t$, given]

Resistance at any temperature $\theta_x^\circ\text{C}$ is given by

$$R_{\theta_x} = R_0[1 + \alpha_0(\theta_x^\circ - 0^\circ)]$$

i.e., $R_{\theta_x} = R_0[1 + \alpha_0\theta_x^\circ] = R(t)$, in this case.

Given $R_0 = 5\Omega$, $\alpha_0 = 0.005^\circ\text{C}^{-1}$, $\theta_x = 20t$

$\therefore R(t) = 5(1 + 0.005 \times 20t) = (5 + 0.5t)\Omega$.

$$\begin{aligned}\text{However, Energy} &= \int_0^t P \cdot dt = \int_0^t \frac{V^2}{R(t)} \cdot dt \\ &= \int_0^{10} \frac{220^2}{(5 + 0.5t)} \cdot dt \\ &= 220^2 \int_0^{10} \frac{dt}{(5 + 0.5t)} = \frac{220^2}{0.5} [\ln(5 + 0.5t)]_0^{10} \\ &= 96800[\ln(5 + 5) - \ln(5 + 0)] = 67.1 \text{ kJ.}\end{aligned}$$

1.32 In a current carrying conductor the current density is expressed in $\delta \text{ A/mm}^2$ while its resistivity is $\rho \times 10^{-6} \Omega \text{ cm}$. If the specific gravity is (S), find the power loss expressed in W/kg .

Solution

$$P_{\text{loss}} = RI^2 = \rho \frac{l}{a} \cdot I^2 \times 10^{-6} = \rho \frac{l}{a} \cdot a^2 \left(\frac{I}{a}\right)^2 \times 10^{-6}$$

[\because current density = current/area; area is expressed by a cm^2 .]

$$\text{or } P_{\text{loss}} = \rho \left(\frac{I}{a}\right)^2 \times la \times 10^{-6}$$

However, ($l \times a$) represents the volume of the conductor.

$$\therefore P_{\text{loss}} = \rho \left(\frac{I}{a}\right)^2 \times 10^{-6} \text{ W/cm}^3.$$

However, mass of 1 cm^3 of material = $S \text{ gm}$

$$\therefore \text{Loss in watts for } S \text{ gm} = \rho \left(\frac{I}{a}\right)^2 \times 10^{-6}$$

$$\text{i.e., loss in watts for one gm} = \rho \left(\frac{I}{a}\right)^2 \times \frac{1}{S} \times 10^{-6}$$

$$\text{or loss in watts per kg} = \frac{\rho \times 10^{-6} \times (\sigma \times 10^2)^2 \times 10^3}{S}$$

$$\left[\because \sigma = \frac{I}{a} \text{ A/cm}^2 = \frac{I}{a} \times 10^2 \text{ A/mm}^2 \right]$$

$$= \frac{10\rho\sigma^2}{S}$$

1.33 For a particular element the temperature coefficient of resistance is $0.005\text{ }^{\circ}\text{C}^{-1}$ at $0\text{ }^{\circ}\text{C}$. The temperature varies linearly with time and is given by the relation $\theta\text{ }^{\circ}\text{C} = (10 + 10t)$, where t is expressed in seconds. If the initial resistance of the element is 1 ohm , find its resistance after 30 sec . The element does not melt up to $500\text{ }^{\circ}\text{C}$.

Solution

At $t = 0$; $\theta_0 = 10\text{ }^{\circ}\text{C}$, as obtained from the relation $\theta\text{ }^{\circ}\text{C} = (10 + 10t)$. Also, $R_{10} = 1\text{ }\Omega$

At $t = 30\text{ sec}$, $\theta\text{ }^{\circ}\text{C} = 10 + 10 \times 30 = 310\text{ }^{\circ}\text{C}$

$$\therefore R_{310} = R_{10}[1 + \alpha_{10}(310 - 10)] \quad (1)$$

$$\text{But } \alpha_{10} = \frac{\alpha_0}{1 + \alpha_0(\theta_0 - 0)}$$

[We derived this relation earlier in Ex. 1.26]

$$\text{Here } \alpha_{10} = \frac{0.005}{1 + 0.005 \times 10} = 0.0048/^{\circ}\text{C}.$$

Thus from (1),

$$R_{310} = 1[1 + 0.0048 \times 300] \\ = 2.44\text{ }\Omega.$$

Thus, after 30 sec , the temperature of the element would be $2.44\text{ }\Omega$

1.34 A heating element is subjected to a voltage of 220 V . The resistance of the element is a function of time when voltage is applied across it and follows the relation $R(t) = 5e^{2t}\text{ }\Omega$ (t being expressed in seconds). How much heat energy would it generate after 10 seconds ?

Solution

$$\begin{aligned} \text{Energy} &= \int_0^t P \cdot dt = \int_0^t \frac{V^2}{R(t)} \cdot dt \\ &= \int_0^t \frac{220^2}{5e^{2t}} \cdot dt = \frac{(220^2)}{5} \int_0^t (e^{-2t}) \cdot dt \\ &= 9680 (1 - e^{-2t}) \text{ Joule.} \end{aligned}$$

After 10 seconds the energy generation is

$$9680 (1 - e^{-10 \times 2}) = 9680 \text{ Joule.} \quad \dots\dots\dots$$

1.35 Find the current flowing through a 60 W bulb at the instant of switching across a 220 V dc supply if the incandescent bulb filament temperature is $2020\text{ }^{\circ}\text{C}$ and the temperature coefficient at $20\text{ }^{\circ}\text{C}$ is 0.005 . Also assume the room temperature is $20\text{ }^{\circ}\text{C}$.

Solution

Just at the moment of switching the filament temperature is $2020\text{ }^{\circ}\text{C}$ and we are to find current at this temperature. However from the given data, utilising the formula in the text,

$$\begin{aligned} R_{2020} &= R_{20}[1 + \alpha_{20}(t_2 - t_1)] \\ &= R_{20}[1 + 0.005(2020 - 20)] \\ &= R_{20} \times 11. \end{aligned}$$

$$\therefore R_{20} = \frac{R_{2020}}{11}$$

$$\text{However, } R_{2020} = \frac{V}{I \text{ (at steady state)}} = \frac{V}{(W/V)}$$

$$= \frac{220^2}{60} = 807 \, \Omega$$

$$\therefore R_{20} = \frac{807}{11} = 73.36 \, \Omega.$$

Thus current at the moment of switching, i.e. at 20°C would be

$$I_{sw} = \frac{V}{R_{20}} = \frac{220}{73.36} = 3 \, \text{A}.$$

1.36 Two materials, A and B, have resistance temperature coefficient of 0.004 and 0.0004 respectively at a particular temperature. In what proportion must A and B be joined in series to produce a circuit having a temperature coefficient of 0.001?

Solution

Let us assume that at the lower temperature let the resistance of A be $1 \, \Omega$ and that of B be $r \, \text{ohm}$. As the temperature is raised by $t^\circ\text{C}$, the resistance of the combination becomes $[(1+r)(1+0.001 \times t)]$.

However, individual resistance of element A at $t^\circ\text{C}$ is $[1(1+0.004t)]$ and that of B is $[r(1+0.0004t)]$.

Since both the elements A and B are in series.

$$[1(1+0.004t)] + [r(1+0.0004t)] = [(1+r)(1+0.001 \times t)]$$

$$\text{or } 1 + 0.004t + r + 0.0004tr = 1 + 0.001t + r + 0.001t \times r$$

$$\text{or } 0.004 + 0.0004r = 0.001 + 0.001r$$

$$\therefore r = 5.$$

Thus the required proportion A and B that must be joined in series is A : B = 1 : 5.

1.37 In Fig. 1.8(a), assume all the resistances are equal to r . A battery with $V = 2$ volts and internal resistance of $0.1 \, \Omega$ is connected across the given circuit. Calculate the value of r for which the heat generated is maximum.

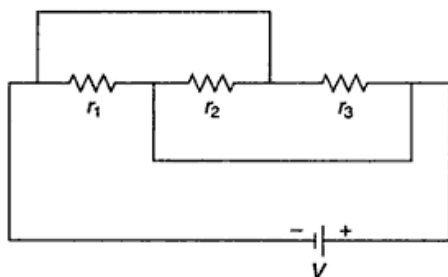


Fig. 1.8(a) Circuit of Ex. 1.37

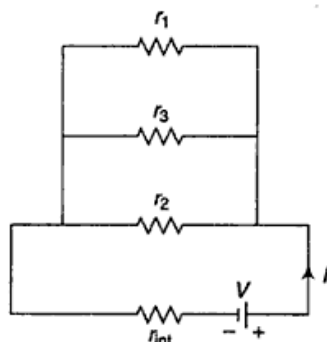


Fig. 1.8(b) Simplified circuit of Fig. 1.8.1

Solution

Let us simplify the circuit as shown in Fig. 1.8(b)

$$\therefore R_{eq} = \text{parallel of } r_1, r_2 \text{ and } r_3$$

Since

$$r_1 = r_2 = r_3 = r$$

$$R_{eq} = r/3$$

Current from the battery is $I = \frac{V}{R_{eq} + r_{int}} = \frac{V}{\frac{r}{3} + r_{int}} = \frac{3V}{r + 3r_{int}}$.

The rate at which heat is generated in the circuit is given by

$$W = I^2 R_{eq} = \left(\frac{3V}{r + 3r_{int}} \right)^2 \times \frac{r}{3} = \frac{3V^2 r}{(r + 3r_{int})^2}$$

Heat will be maximum when

$$\frac{dW}{dr} = 0.$$

i.e., $\frac{dW}{dr} = \frac{3V^2}{(r + 3r_{int})^2} - \frac{6V^2 r}{(r + 3r_{int})^3} = 0$

or $\frac{3V^2}{(r + 3r_{int})^2} \left[1 - \frac{2r}{r + 3r_{int}} \right] = 0$

$\therefore 2r = r + 3r_{int}$

or $r = 3r_{int} = 3 \times 0.1 = 0.3 \Omega$

Thus, at $r_1 = r_2 = r_3 = r = 0.3 \Omega$, the heat generated will be maximum.

.....

■ EXERCISES ■

1. Name the fundamental units in SI system. Why is the SI system preferred?
2. What are derived units in SI system? Name a few used in electrical engineering.
3. What is per unit (p.u.) system of measurement? What is its convenience? How do you convert a p.u. quantity from one base to another base?
4. How does electric current flow? How do you use sign notation for voltages?
5. How do you distinguish between source and load in electrical engineering?
6. State Ohm's law and define resistance. How do you express Ohm's law in terms of conductance? Can we apply Ohm's law in any electrical circuit?
7. What is resistivity? How is it expressed? What is its unit in SI system?
8. Write the expression of electric power and energy in terms of current and resistance. How is voltage related to electric power expression? What do you mean by negative power?
9. (a) Define temperature coefficient of resistance. If α_t be the temperature coefficient of resistance at $t^\circ\text{C}$, α_0 be its value at 0°C for any metal, show that we can represent α_t as

$$\alpha_t = \frac{1}{\frac{1}{\alpha_0} + t}$$

- (b) When can temperature coefficient of resistance be negative?

10. Find the power consumed by the combination of resistances when connected to a voltage source of 100 V at terminals P - Q (Fig. 1.9).

(Ans: 3.125 kW)

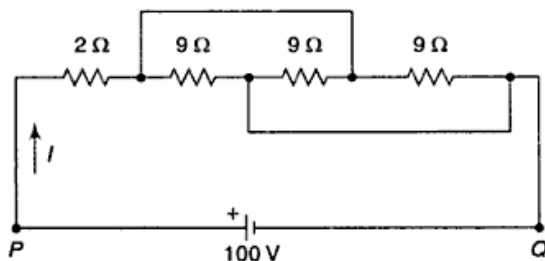


Fig. 1.9

[Hint: Fig. 1.9 can be reduced as shown below:

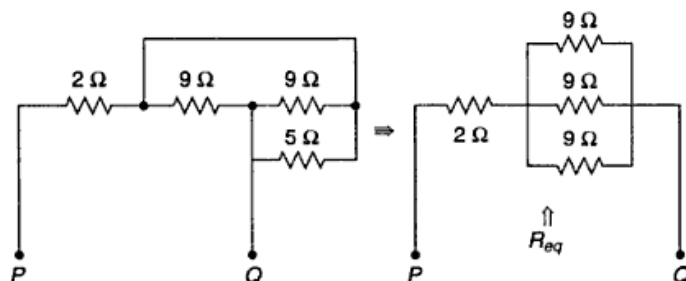


Fig. 1.10

$$R_{eq} = 2 + \frac{9}{3} = 5 \Omega$$

$$\therefore I = \frac{100}{5} = 25 \text{ A}; P_{\text{loss}} = I^2 R = 25^2 \times 5 = 3.125 \text{ kW.}]$$

11. A circular wire of resistance 5Ω is stretched to twice its original length. What will be the resistance of the wire now?

(Ans: 20Ω)

[Hint: Suffix 1 represents the parameters of the original wire while suffix 2 represents the parameters in the stretched condition. The mass (m) of the wire remains the same.

$$\therefore m = \pi r_1^2 l_1 \times d = \pi r_2^2 l_2 \times d \quad [\because m = \text{volume} \times \text{density}]$$

$$\text{or} \quad r_1^2 l_1 = r_2^2 l_2$$

$$\text{Since} \quad l_2 = 2l_1, \quad r_2^2 = r_1^2 / 2.$$

If R_1 is the resistance of the original wire, R_2 that of the stretched wire, we have

$$R_1 = \rho \frac{l_1}{\pi r_1^2}; \quad R_2 = \rho \frac{l_2}{\pi r_2^2}$$

$$\therefore \frac{R_2}{R_1} = \frac{l_2 r_1^2}{l_1 r_2^2} = 2 \times 2 = 4.$$

Then $R_1 = 4R_2$; Here $R_2 = 4 \times 5 = 20 \Omega$

12. A heater wire length 50 cm and 1 mm^2 in cross-section carries a current of 2A when connected across a 2 V battery. What is the resistivity of the wire? (Ans: $2 \times 10^{-10} \Omega \text{m}$)

$$[\text{Hint: } \rho = R \frac{a}{l} = \frac{V}{I} \times \frac{a}{l} = \frac{2}{2} \times \frac{1 \times 10^{-6}}{50 \times 10^{-2}} = 2 \times 10^{-10} \Omega \text{m}]$$

13. A copper rod of length 20 cm and cross-sectional area 2 mm^2 is joined with an identical aluminium rod, as shown in Fig. 1.11. Find the resistance of the combination along its length and between the ends. Assume $\rho_{\text{cu}} = 1.7 \times 10^{-8} \Omega \text{m}$; $\rho_{\text{al}} = 2.6 \times 10^{-8} \Omega \cdot \text{m}$. (Ans: 1.0 m Ω)

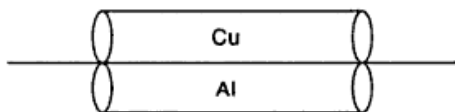


Fig. 1.11

$$[\text{Hint: } R_{\text{cu}} = \rho_{\text{cu}} \frac{l}{a} = \frac{1.7 \times 10^{-8} \times 20 \times 10^{-2}}{2 \times 10^{-6}} = 1.7 \times 10^{-3} \Omega$$

$$R_{\text{al}} = \rho_{\text{al}} \frac{l}{a} = \frac{2.6 \times 10^{-8} \times 20 \times 10^{-2}}{2 \times 10^{-6}} = 2.6 \times 10^{-3} \Omega$$

The rods are in parallel and hence

$$R = \frac{R_{\text{cu}} \times R_{\text{al}}}{R_{\text{cu}} + R_{\text{al}}} = \frac{1.7 \times 10^{-3} \times 2.6 \times 10^{-3}}{1.7 \times 10^{-3} + 2.6 \times 10^{-3}} = 1.0 \text{ m}\Omega.]$$

14. A wire of resistance 20Ω is bent to form a complete round loop. Find the amount of heat it will generate if a voltage of 10 V is applied at diametrical opposite points $m - n$ in the loop (Fig. 1.12). (Ans: 20 W)

[Hint: Let us assume two points p, q at the top and bottom of the circle and diametrically opposite. It is obvious that across 10 V source, current will enter at m and pass to n through two parallel paths mpn and mqn . Thus the equivalent

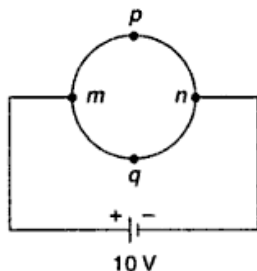


Fig. 1.12

resistance across mn is given by $R_{mn} = \frac{R_1 \times R_2}{R_1 + R_2}$; R_1 = resistance of mpn and R_2 = resistance of mqn .

$$= \frac{10 \times 10}{10 + 10} = 5 \Omega.$$

$$\therefore P_{\text{loss}} = \frac{V^2}{R_{mn}} = \frac{100}{5} = 20 \text{ W}.$$

15. Find the equivalent resistance between points a and b of the infinite ladder shown in Fig. 1.13.

$$(\text{Ans: } R_{\text{eq}(a-b)} = \frac{1 + \sqrt{5}}{2} \cdot R)$$

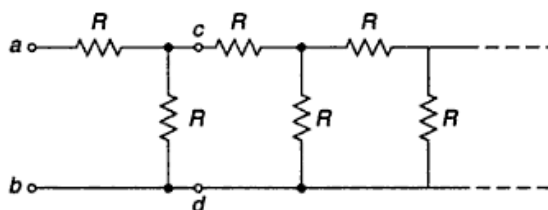


Fig. 1.13

[Hint: Let $R_{\text{eq}(a-b)}$ be the equivalent resistance between $a - b$. As the ladder is infinite, R_{eq} is also the equivalent resistance of the ladder to the right of c and d point. Thus, we can replace the part of right of cd by a resistance R_{eq} and reduce the given ladder network as shown in Fig. 1.14.

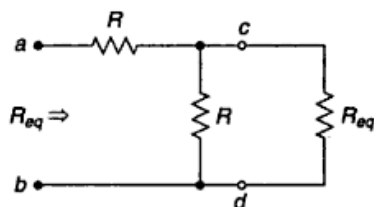


Fig. 1.14

$$R_{\text{eq}} = R + \frac{R_{\text{eq}} \times R}{R_{\text{eq}} + R}$$

$$\text{or } R_{\text{eq}}^2 - R R_{\text{eq}} - R^2 = 0$$

$$\therefore R_{\text{eq}} = \frac{R + \sqrt{R^2 + 4R^2}}{2} = \frac{1 + \sqrt{5}}{2} \cdot R$$

16. A copper wire of resistivity $1.7 \times 10^{-8} \text{ ohm} \cdot \text{m}$ and density 8900 kg/m^3 and an aluminium wire of resistivity $2.8 \times 10^{-8} \text{ ohm} \cdot \text{m}$ and density 2700 kg/m^3 here the same mass per unit length. What would be the ratio of resistances of aluminium and copper wire per unit length?

$$(\text{Ans: } \frac{R_{\text{al}}/\text{length}}{R_{\text{cu}}/\text{length}} = \frac{1}{2})$$

[Hint: Let ξ_1 and ξ_2 be the resistance per unit length of copper and aluminium.

$$\frac{\xi_1}{\xi_2} = \frac{R_1/l_1}{R_2/l_2} = \frac{\rho_1/a_1}{\rho_2/a_2} = \frac{\rho_1}{\rho_2} \times \frac{A_2}{A_1}$$

Also, mass = volume \times density. Here,

$$m_1 = (a_1 l_1) d_1; m_2 = (a_2 l_2) d_2$$

But as per question, $\frac{m_1}{l_1} = \frac{m_2}{l_2}$

$$\therefore a_1 d_1 = a_2 d_2 \quad \text{or} \quad \frac{a_2}{a_1} = \frac{d_1}{d_2}$$

$$\text{Hence} \quad \frac{\xi_1}{\xi_2} = \frac{\rho_1}{\rho_2} \times \frac{d_1}{d_2} = \frac{1.7 \times 10^{-8}}{2.8 \times 10^{-8}} \times \frac{8900}{2700} = 2$$

$$\text{Hence} \quad \frac{\xi_2}{\xi_1} = \frac{\text{resistance/length of aluminium}}{\text{resistance/length of copper}} = \frac{1}{2}$$

17. A 12 V, 24 W filament bulb is to be used against a battery of N number of cells. Each cell has emf of 1.5 V and internal resistance of 0.25 Ω . How many cells are to be used so that bulb runs at rated power?

(Ans: $N = 12$)

[Hint: $W = VI = 24$; $V = 12$ V; $I = 2$ A. As the bulb is connected to the battery in series, for each cell $V = E - Ir$; r being the internal resistance of each cell.

Or, $V = 1.5 - 2 \times 0.25 = 1$ V, assuming the cells are in series.

Thus 12 cells are required so that the voltage across the bulb is 12 V.]

18. Two wires made of the same materials and same cross-sectional area but the second wire has twice the mass than the first wire. If same current I flows through both the wires, what is the ratio of heat produced in the two wires? (Ans: In series $H_1 : H_2 = 1 : 2$, in parallel, $H_1 : H_2 = 2 : 1$)

[Hint: Let the first wire have mass m while the second wire have mass $(2m)$. Using the relation, $m = (a l) d$ (\because mass = volume \times density) we find

$$\frac{m}{2m} = \frac{a l_1 d}{a l_2 d} \quad \text{or,} \quad \frac{l_1}{l_2} = \frac{1}{2}$$

$$\text{But} \quad R = \rho \frac{l}{a}, \quad \therefore \frac{R_1}{R_2} = \frac{l_1}{l_2} = \frac{1}{2}$$

If they are connected in series, in the first one heat produced is $H_1 = I^2 R_1$, while in the second one heat produced is $H_2 = I^2 R_2$.

$$\therefore \frac{H_1}{H_2} = \frac{R_1}{R_2} = \frac{1}{2}$$

On the other hand, when they are in parallel, V across each of them remain same. This time $H_1 = \frac{V^2}{R_1}$, while $H_2 = \frac{V^2}{R_2}$.

$$\therefore \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{2}{1}]$$

19. Current flows through a copper bar of length 5 m long and 10 cm^2 cross-sectional area. If the resistivity of the bar at 0°C is $1.6 \times 10^{-8} \Omega\text{m}$, find the resistance of the bar at 0°C . If the strength of current is 5 kA, find the potential drop across the bar. If the bar is now stretched to form a thinner bar of 5 cm^2 cross-section, find the new resistance of the bar. If the same current is passed through the bar in original condition as well as in stretched condition, what is the ratio of heat produced in two conditions?

$$(\text{Ans: } R_0 = 8 \times 10^{-5} \Omega; V = 0.4 \text{ Volt}; R_{\text{stretched}} = 3.2 \times 10^{-4} \Omega;$$

Heat loss increases 4 times on stretching)

$$[\text{Hint: (i) } R_0 = \rho \frac{l}{a} = \frac{1.6 \times 10^{-8} \times 5}{10 \times 10^{-4}} = 8 \times 10^{-5} \Omega$$

$$(ii) V_{\text{drop}} = I \times R_0 = 5000 \times 8 \times 10^{-5} = 0.4 \text{ V}$$

(iii) After the bar is stretched,

$$l = \frac{\text{Volume}}{\text{New area}} = \frac{(5 \times 10 \times 10^{-4})}{5 \times 10^{-4}}$$

(\because volume remains same before and after stretching)

$$= 10 \text{ m.}$$

$$R_{\text{new}} = \rho \times \frac{l}{a} = \frac{1.6 \times 10^{-8} \times 10}{5 \times 10^{-4}} = 3.2 \times 10^{-4} \Omega.$$

(Note: resistance increases under stretched condition.) If H_1 and H_2 be the heat produced in two conditions,

$$H_1 = I^2 R_0 t; H_2 = I^2 R_{\text{new}} \times t$$

$$\therefore H_1 : H_2 = R_0 : R_{\text{new}} = 0.25.]$$

20. A battery of emf 6 V and internal resistance of 0.1Ω is charged by a dc charger (Fig. 1.15) with a constant current of 5 A. What is the p.d. across the terminals x-y? (Ans: 6.5 V)

[Hint: During charging current enters the battery through +ve terminal i.e., current passes from x - y. The battery is absorbing energy.

Here $V_x - V_y$ is p.d. across the battery. Since the battery emf is 6 V, we can write

$$V_x - 6 - \text{drop in } 0.1 \Omega \text{ internal resistance} - V_y = 0$$

$$\text{i.e. } V_x - 6 - 5 \times 0.1 - V_y = 0$$

$$\therefore V_x - V_y = 6.5 \text{ V.}]$$

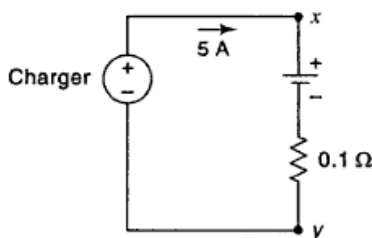


Fig. 1.15



ELECTROSTATICS

2.1 INTRODUCTION

In *electrostatics* we deal with static electricity (i.e., when charges are at rest). The knowledge of electrostatics is important in electrical engineering as we frequently come across the design process of electrical insulations and performance of various equipment, cables and overhead lines when subjected to electric stress. Natural phenomenon like lightning is very much related to electrostatic processes and laws. Electrostatics finds extensive applications in extra high voltage systems (ehv) in transmission engineering. *Capacitors* play a vital role in different spheres of electrical engineering as well as electronics engineering. The performance of a capacitor can be best analysed and it can be properly designed with knowledge in electrostatics.

2.2 COULOMB'S LAW AND CONCEPT OF PERMITTIVITY

Coulomb's first law states that like charges repel each other while opposite charges attract each other. *Coulomb's second law* states that the force of attraction between two opposite charges or force of repulsion between two like charges is

- directly proportional to the product of the charges, the distance between them being same;
- inversely proportional to the square of the straight distance between them, magnitude of the charges being constant.

If we assume the charges to be of magnitude (Q) and (q) separated by a straight distance x , then from Coulomb's second law we can write

$F \propto Q \cdot q/x^2$, (F) being the force of repulsion if both charges are alike or force of attraction if the charges have opposite polarity. The force (F) is measured in Newtons when the magnitude of the charges are expressed in Coulombs and the distance in meters.

$$\therefore F = K \frac{Q \cdot q}{x^2} \quad (2.1)$$

(K) being constant of variation and in SI unit (K) in vacuum is given by $1/4\pi\epsilon_0$; otherwise $K = 1/4\pi\epsilon$, when the charges are placed in any other medium other than vacuum or space.

$$\therefore F = \frac{Q \cdot q}{4\pi\epsilon x^2} \quad (2.2)$$

In electrical engineering we term this ϵ as permittivity of the medium in which charges are placed. It is known as absolute permittivity and is represented as

$$\epsilon = \epsilon_0 \times \epsilon_r \quad (2.3)$$

where (ϵ_0) is the *permittivity* of space while (ϵ_r) is the *relative permittivity* of the medium where the charges are placed.

In SI unit,

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ Farad/metre}$$

$$\therefore \frac{1}{4\pi\epsilon_0} = \frac{1}{4\pi \times 8.854 \times 10^{-12}} = 9 \times 10^9$$

Thus, Coulomb's law can be written as

$$F = 9 \times 10^9 \frac{Q \times q}{\epsilon_r x^2} \quad (2.4a)$$

When the charges are placed in vacuum (or space),

$$F = 9 \times 10^9 \frac{Q \cdot q}{x^2} \quad (2.4b)$$

If $Q = q = 1$ Coulomb and $x = 1$ metre, from Coulombs law, $F = 9 \times 10^9$ Newtons (in space). This gives rise to the definition of *unit charge* (i.e. 1 Coulomb) which means that it is such a charge which when placed at one metre apart from another similar charge experiences a force of 9×10^9 Newton in vacuum.

2.3 PERMITTIVITY

Permittivity of a medium is basically that property of the medium which permits electric flux to pass through it. If the permittivity is more it means that the medium allows more flux to pass through it and hence this medium is more susceptible to the electric field.

Absolute permittivity (ϵ) is the ratio of electric flux density in a dielectric medium to the corresponding electric field strength and is expressed as Farad/meter.

$$\text{i.e.} \quad \epsilon = \frac{\delta}{E} \text{ F/m} \quad (2.5)$$

where δ is electric flux density and E is the strength of the field.

Also, $\epsilon = \epsilon_0 \times \epsilon_r$, where ϵ_0 is the permittivity of free space (8.854×10^{-12} F/m) and (ϵ_r) is the relative permittivity of a dielectric medium. It is defined as the

ratio of flux densities of the dielectric medium to that in vacuum produced by the same electric field strength.

$$[\epsilon_r = \frac{\delta}{\delta_o} = \frac{(\epsilon E)}{(\epsilon_o E)} = \frac{\epsilon}{\epsilon_o}]$$

$$\therefore \epsilon = \epsilon_r \times \epsilon_o.$$

Relative permittivity of space is 1 while that of air is 1.0006. In practice, we assume ϵ_r of vacuum and air as 1. Commonly used dielectric medium have permittivity between 2 and 10.

2.4 ELECTRIC POTENTIAL AND POTENTIAL DIFFERENCE

The *electric potential* at any point in an electric field is defined as the work done in joules in moving a unit positive charge from infinity (i.e., from zero potential) to that point against the electric field.

$$\therefore \text{Electric potential} = \frac{\text{Work done}}{\text{Electric charge}}$$

$$\text{or} \quad V = \frac{W}{Q} \quad (2.6)$$

When W is expressed in joules, Q in coulombs, V is expressed in volts. Then the electric potential at a particular point in an electric field is one volt provided one joule of work is done in moving a unit positive charge from zero potential to that point against the field.

In electrical engineering we are more interested in measuring the potential difference between two points in a field than to know the absolute value of the electric potential at any point s in the field. The *potential difference (p.d.)* is the work done in joule in moving a unit positive charge from the point of lower potential to higher potential within the field.

The potential difference is obviously measured in volts and the p.d. of one volt means one joule of work is done in bringing a unit positive charge from the point of lower potential to the point of higher potential within the electric field.

2.5 EXPRESSION FOR POTENTIAL AT A POINT WITHIN AN ELECTRIC FIELD

Let us consider two positive charges, the first one having a charge of Q coulombs while the second one is a unit positive charge. Both the charges are assumed to be placed in space at a straight distance x metres between them. From Coulomb's law we can express the force of repulsion between these two charges as

$$F = \frac{Q \times 1}{(4\pi\epsilon_o)x^2}; \epsilon_o \text{ being the permittivity of space.}$$

The work done dW in moving the unit charge towards the charge Q for a small distance dx metre will be given as

$$dW = \left[\frac{Q}{(4\pi\epsilon_0)x^2} (-dx) \right] \text{ joule}$$

Work done is negative as the charge is moved against a repulsive force and against the direction of the field.

In order to find the total work done in moving the unit positive charge from infinity to any point d metres away from the charge Q against the field, we will integrate the expression of dW obtained within the limit of integral ∞ to d .

$$\therefore W = \int_{\infty}^d \frac{Q(-dx)}{(4\pi\epsilon_0)x^2} = \frac{-Q}{4\pi\epsilon_0} \left[-\frac{1}{x} \right]_{\infty}^d = \frac{Q}{(4\pi\epsilon_0) \cdot d} \text{ joules.}$$

Thus, from definition we can write the potential at a point d metres away from the

charge Q is simply $\left(\frac{Q}{4\pi\epsilon_0 \cdot d} \right)$ volts.

$$\therefore V = \frac{Q}{(4\pi\epsilon_0) \cdot d} \text{ volts} \quad (2.7a)$$

If the analysis be performed assuming the surrounding medium as a dielectric of negative permittivity ϵ_r , we can modify the expression for potential at distance d away from Q as

$$V = \frac{Q}{4\pi\epsilon_0 \epsilon_r \cdot d} \text{ volts} \quad (2.7b)$$

If we consider an isolated sphere of radius R placed in space and having +ve charge Q coulombs uniformly distributed over its surface, the potential at the surface of the sphere would be

$$V = \frac{Q}{4\pi\epsilon_0 R} \quad (2.8)$$

[the charge on the sphere would act as a concentrated charge at the centre O of the sphere.]

The potential will remain constant for the space between O and R in the sphere and will be same as the potential V at the surface of the sphere. The surface of the sphere would be termed as equipotential surface and electric lines of force always cross such a equipotential surface normally.

2.6 ELECTRIC FIELD INTENSITY

The *intensity of the electric field* at a point is defined as the mechanical force per unit charge placed at that point. The direction of the intensity is same as direction of the force exerted on a positive charge.

Thus, if F be the force experienced by a test charge q placed at a point in an electric field, the intensity E at that point is given by

$$E = \frac{F}{q} \quad (2.9)$$

E is expressed in newton per coulomb or in volt/metre (V/m). Frequently the term *electric field strength* is also used instead of the term electric field intensity.

Let us assume a positive point charge $+Q$ is placed at a point M and a test charge $+q$ is placed at point N , as shown in Fig. 2.1.

The force F experienced by q is given by

$$F = \frac{Qq}{4\pi\epsilon_0 x^2}$$

Since intensity E is given by F/q , we can write

$$E = \frac{Q}{4\pi\epsilon_0 x^2} \quad (2.10)$$

The direction of E is towards the point charge or away from it according as the charge is negative or positive.

[In vector form the intensity can be expressed as

$$\vec{E} = \frac{1}{4\pi\epsilon_0} \times \frac{Q}{r^2} \cdot \hat{r}$$

$$\text{or} \quad \vec{E} = \frac{1}{4\pi\epsilon_0} \times \frac{Q}{r^3} \cdot \vec{r} \quad (2.11)$$

where x is the distance between the charges Q and q ; \hat{r} is unit vector along \vec{r} and is given by

$$\hat{r} = \frac{\vec{r}}{|\vec{r}|} = \frac{\vec{r}}{r}$$

2.7 ELECTRIC FIELD INTENSITY AND POTENTIAL OF ISOLATED POINT CHARGE $(+q)$

Figure 2.2 represents an isolated point charge $+q$ placed in space. We are to find the field intensity and potential at point P .



Fig. 2.2 An isolated point charge $(+q)$ placed in space

To find intensity:

By definition of electric field intensity, the intensity at a point along the direction \vec{r} is given by (in vector form)

$$\vec{E} = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2} \hat{r} \quad (2.12a)$$

where q = positive point charge
 r = distance between $+q$ and point P and
 \hat{r} = unit vector along \vec{r} .

$$\therefore \vec{E} = \frac{1}{4\pi\epsilon_0} \left(\frac{q}{r^3} \right) \vec{r} \quad \left(\because \hat{r} = \frac{\vec{r}}{|\vec{r}|} = \frac{\vec{r}}{r} \right) \quad (2.12b)$$

From Eq. (2.10), we can also write field intensity as

$$E = \frac{1}{4\pi\epsilon_0} \times \frac{Q}{x^2} \quad (2.12c)$$

To find potential:

By definition of potential at a point P ,

$$V = - \int_{\infty}^r |\vec{E}| dr = - \int_{\infty}^r \frac{1}{4\pi\epsilon_0} \left(\frac{q}{r^2} \right) dr = - \left[-\frac{1}{4\pi\epsilon_0} \left(\frac{q}{r} \right) - 0 \right] = \frac{q}{4\pi\epsilon_0 r}$$

$$\therefore V = \frac{q}{4\pi\epsilon_0 r} \quad (2.12d)$$

2.8 ELECTRIC FIELD INTENSITY AND POTENTIAL GRADIENT

Electric field strength E due to a point charge at any point in the vicinity of the charge is defined as the force experienced by a unit positive charge placed at that point within the field. It is expressed in Newton/Coulomb (or volt/meter). If this force is stronger, the electric field strength is more. We also can state that the work done in moving a unit positive charge through a small distance dx meters in the direction of the field is given by

$$(dW) = \text{force} \times \text{displacement of the charge} \\ = E \times dx \text{ joules, where } E \text{ is expressed in}$$

Newton/Coulomb.

Obviously this work done would be equal to the "drop" or reduction in potential as this time the unit positive charge is moved along the direction of the field and the work done would consequently be positive.

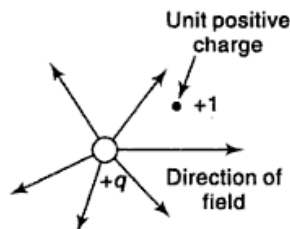


Fig. 2.3 A unit (+ve) charge in a field

Then we can write $dV = E \times dx$

$$\text{or} \quad E = \frac{dV}{dx} \quad (2.13)$$

(dV/dx) is known as the *potential gradient* and is thus the drop in potential per meter in the direction of the field. It is expressed as volt/meter. We thus find that the electric field strength and potential gradient being same, both are expressed in volt/meter.

2.9 ELECTRIC POTENTIAL ENERGY

Let us consider a system of two charges Q_1 and Q_2 . Suppose Q_1 is a fixed charge at a point M while the charge Q_2 is taken from a point N to a point P along the line MNP (Fig. 2.4).

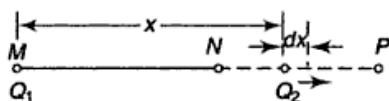


Fig. 2.4 A system of two charges

Let distance $MN = x_1$, while distance $MP = x_2$. We consider a small displacement of charge Q_2 . Its distance from M then changes to $(x + dx)$. The electric force on Q_2 is given by

$$F = \frac{Q_1 Q_2}{4\pi\epsilon_o x^2}, \text{ in direction } M \text{ to } N.$$

[We assume the medium in which the charges are placed in space and hence $\epsilon_r = 1$.]

The work done by the force in making small displacement dx by the charge is

$$dW = \frac{Q_1 Q_2}{4\pi\epsilon_o x^2} \cdot dx$$

[\therefore Work done = force \times displacement]

The total work done as Q_2 moves from N to P is thus

$$\begin{aligned} W &= \int_{x_1}^{x_2} \frac{Q_1 Q_2}{4\pi\epsilon_o x^2} \cdot dx \\ &= \frac{Q_1 Q_2}{4\pi\epsilon_o} \left[\frac{1}{x_1} - \frac{1}{x_2} \right] \text{ joule} \end{aligned} \quad (2.14)$$

[Charges are expressed in Coulomb and distance in metres]

[It may be noted here that no work is done by the electric force on the charge Q_1 as it remains fixed.]

The change in potential energy is thus

$$\begin{aligned} u(x_2) - u(x_1) &= -W = -\frac{Q_1 Q_2}{4\pi\epsilon_o} \left[\frac{1}{x_1} - \frac{1}{x_2} \right] \\ &= \frac{Q_1 Q_2}{4\pi\epsilon_o} \left[\frac{1}{x_2} - \frac{1}{x_1} \right] \end{aligned} \quad (2.15a)$$

[We define *change in electric potential energy* of the system as negative of work done by the electric force.]

If one charge is placed at infinity, its potential is zero and consequently $u(\infty) = 0$.

The potential energy, when the separation is x , can be obtained as

$$U(x) = u(x) - u(\infty) \\ = \frac{Q_1 Q_2}{4\pi\epsilon_0} \left(\frac{1}{x} - \frac{1}{\infty} \right) = \frac{Q_1 Q_2}{4\pi\epsilon_0 x} \quad (2.15b)$$

The equations derived here assume that one of the charges is fixed and the other is moving. However, the potential energy depends essentially on the separation between charges and is independent of the spatial location of the charged particles.

2.10 RELATION BETWEEN ELECTRIC FIELD STRENGTH AND POTENTIAL

Let us suppose the electric field at a point n due to a charge distribution is E , while the electric potential at the same point is V . Let us assume the point charge of strength q is moved slightly from the point x to $(x + dx)$. The force on the charge is $F = q \cdot E$, while the work done is

$$dW = F(-dx) = qE(-dx)$$

[In article 2.8, we have assumed dx in the direction of the field, i.e. from $+q$ towards infinity. If any charge is moved against the field, dx becomes $-ve$.] The change in potential energy due to this displacement is

$$du = +dW = -q \cdot E \cdot dx.$$

The change in potential is $dV = \frac{du}{q}$ i.e. $dV = -E dx$.

[If the test charge is moved along the field, $dV = E \times dx$ (as shown in article 2.8).]

Integrating between x_1 and x_2 , we get

$$V_2 - V_1 = - \int_{x_1}^{x_2} E dx, \text{ where } V_2 \text{ and } V_1 \text{ are the potentials at } x_2 \text{ and } x_1 \text{ respectively.}$$

If we select point x_1 as reference having zero potential, we can write $V(r)$

$$= - \int_{\infty}^x E \cdot dx, \text{ where } x \text{ is distance equal to } x_2.$$

2.11 ELECTRIC FIELD INSIDE A CONDUCTOR

When there is no electric field around a conductor the conduction electrons are almost uniformly distributed within the conductor. In any small volume of the conductor the number of electrons is equal to the number of proton in the nuclei

of each atom of the conductor. The net charge in the volume is then zero. Next we suppose that an electric field E is created in the direction left to right across the conductor. This field will exert a force on the free electrons in the atoms of the conductor from right to left. The free electron then move towards the left and consequently the number of electrons in the left will increase while the number of electrons in the right decreases. The left side of the conductor then becomes negatively charged while the right side is positively charged. The electron continue to drift towards the left. The result is the creation of an electric field of strength E' within the conductor in the direction opposite to the applied field. With passage of time a situation comes when the field E' inside the conductor is equal to the magnitude of the external field E . The net electric field inside the conductor is zero. Then a steady state is reached when some positive and negative charges appear at the surface of the conductor while there is no electric field inside the plate. Thus there is no electric field inside the conductor when it is subjected to an external electric field. The redistribution of electrons take place in such a way that charges remain at the surface of the conductor only.

It may be recalled here from the basic concepts of physics that in conductors there is always existence of free electrons while in insulators all atomic electrons are tightly bound to their respective nuclei. When insulators are placed in an electric field they may slightly shift their parent position but cannot drift from their parent atoms and hence cannot move long distance. These materials are then said to act as dielectrics. If the external field is strengthened further, a time will come when the bonding of the electron with their nuclei may break causing them to drift apart. We call this phenomenon as breakdown of dielectric medium.

2.12 GAUSS' LAW AND ITS DERIVATION

Statement of Gauss' Law: The flux of the net electric field through a closed surface is equal to the net charge enclosed by the surface divided by ϵ_0 .

$$\text{i.e.,} \quad \oint E \, ds = \frac{q_{\text{in}}}{\epsilon_0} \quad (2.16)$$

where $\oint E \, ds$ represents the flux ϕ through a closed surface and q_{in} is the net charge enclosed by the surface through which the flux passes.

Derivation of Gauss' Law from Coulomb's Law

Let us suppose that a charge q is placed at a point O inside a closed surface (Fig. 2.5). We assume a point P on the surface and consider a small area Δs on the surface around P .

Let $OP = x$.

The electric field at point P due to the charge q is given by, $E = q/4\pi\epsilon_0 \cdot x^2$, directed along the line OP .

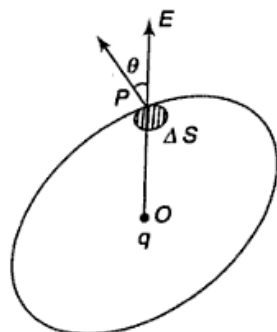


Fig. 2.5 A charge (q) placed inside a closed surface

Let us suppose this line OP makes an angle (θ) with the outward normal to the surface Δs . The flux of the electric field through Δs is given by

$$\begin{aligned}\Delta\phi &= E \Delta s \cos \theta \\ &= \frac{q}{4\pi\epsilon_0 x^2} \cdot \Delta s \cos \theta \\ &= \frac{q}{4\pi\epsilon_0} \cdot \Delta\sigma\end{aligned}$$

where $\Delta\sigma = \frac{\Delta s \cdot \cos \theta}{x^2}$ [Actually ($\Delta\sigma$) is the solid angle subtended by (Δs) at O]

$$\therefore \phi = \sum \frac{q}{4\pi\epsilon_0} \cdot \Delta\sigma = \frac{q}{4\pi\epsilon_0} \sum \Delta\sigma$$

We can see that [$\sum(\Delta\sigma)$] represents the sum that is actually the total solid angles subtended by a closed surface at O . Obviously this total solid angle is 4π .

\therefore The total flux of the electric field due to the internal charge q through the closed surface is

$$\phi = \frac{q}{4\pi\epsilon_0} \cdot 4\pi = \frac{q}{\epsilon_0}$$

$\therefore \phi \equiv \oint E ds$, hence we have

$$\oint E ds = \frac{q_{in}}{\epsilon_0} \text{ (proof of Gauss' law)}$$

where, $\frac{q_{in}}{\epsilon_0} = \sum \frac{q_i}{\epsilon_0}$ (i.e. the sum of all charges $q_1, q_2, \dots, q_i, \dots, q_n$ located in the

said closed surface: We do not consider external charges as the solid angle ($\Delta\sigma$) subtended by a closed surface at any external point is zero, then ϕ becomes zero.

2.13 ELECTRIC DIPOLE

Definition: Two equal and opposite charges separated by a finite distance (Fig. 2.6) is said to constitute an *electric dipole*. It is characterised by dipole moment vector \vec{P} .

Dipole moment vector \vec{P} is defined as

$$\vec{P} = q\vec{l}$$

and is aligned along the same line that join the two equal and opposite charges.

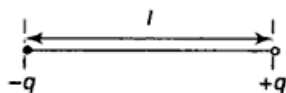


Fig. 2.6 Two equal and opposite charges separated by a finite distance

2.14 ELECTRIC FIELD AND POTENTIAL DUE TO A DIPOLE AT AN AXIAL POINT

Let the charges $(-q)$ and $(+q)$ be kept at $(-a, 0)$ and $(a, 0)$ (Fig. 2.7). The electric field at $P(x, 0)$ then

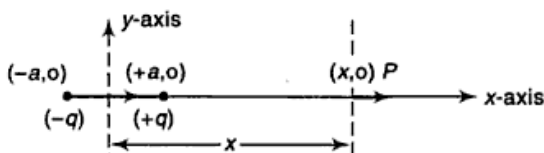


Fig. 2.7 Charges $(+q)$ and $(-q)$ placed at $(+a, 0)$ and $(-a, 0)$

$$\begin{aligned}
 \vec{E}_{\text{axial}} &= \vec{E}_{+q} + \vec{E}_{-q} \\
 &= \frac{kq}{(x-a)^2} \hat{i} - \frac{kq}{(x+a)^2} \hat{i}; \left(k = \frac{1}{4\pi\epsilon_0} \right) \\
 &= \frac{k(q \cdot 2a)2x}{(x^2 - a^2)^2} \hat{i} \\
 &= \frac{2K\vec{P}_x}{(x^2 - a^2)^2} \quad [\vec{P} = \text{dipole moment vector } (2aq)\hat{i}]
 \end{aligned}$$

Assuming $x \gg a$,

$$\vec{E}_{\text{axial}} = \frac{2K\vec{P}}{x^3} = \frac{\vec{P}}{2\pi\epsilon_0 x^3} \quad (2.17)$$

Also, potential $= V_{\text{axial}} = - \int_{\infty}^x |\vec{E}_{\text{axial}}| dx$

$$= \int_{\infty}^x \frac{P}{2\pi\epsilon_0 x^3} dx$$

$$\therefore V_{\text{axial}} = \frac{P}{4\pi\epsilon_0 x^2} \quad (2.18)$$

2.15 ELECTRIC FIELD AND POTENTIAL DUE TO DIPOLE ON EQUATORIAL LINE

At P (Fig. 2.8),

$$\vec{E}_{\text{eq}} = \vec{E}_{+q} + \vec{E}_{-q}$$

$$\begin{aligned}
 &= \left(\frac{Kq}{y^2 + a^2} \right) (-\cos \theta \hat{i} + \sin \theta \hat{j}) \\
 &+ \left(\frac{Kq}{y^2 + a^2} \right) (-\cos \theta \hat{i} - \sin \theta \hat{j}) \\
 &= \frac{-2Kq}{y^2 + a^2} \cos \theta \hat{i} = \frac{-KP}{(y^2 + a^2)^{3/2}} \\
 &= \frac{-\vec{P}}{4\pi\epsilon_0 (y^2 + a^2)^{3/2}} \quad \left[\because \vec{P} = 2aq\hat{i} \text{ and } \cos \theta = \frac{a}{(a^2 + y^2)^{1/2}} \right]
 \end{aligned}$$

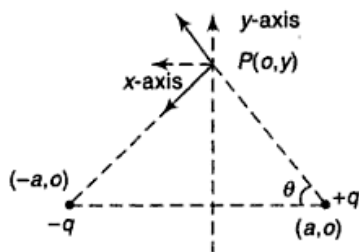


Fig. 2.8 Field and potential on equatorial line

Assuming $y \gg a$, $\vec{E}_{eq} = \frac{KP}{y^3} = \frac{\vec{P}}{4\pi\epsilon_0 y^3}$. (2.19)

Potential $V_{eq} = (\text{Potential at } P \text{ due to } -q) + (\text{Potential at } P \text{ due to } +q)$

$$= \frac{-Kq}{r} + \frac{Kq}{r}$$

$$= 0, \text{ where } K = \frac{1}{4\pi\epsilon_0} \text{ and } r = \sqrt{a^2 + y^2}.$$

Ex. 2.1 Three equal charges, each of magnitude $3.0 \times 10^{-6}\text{C}$, are placed at three corners of a right-angled triangle of sides 3 cm, 4 cm and 5 cm. Find the force on the charge at the right-angle corner.

Solution

Force on A due to B (Fig. 2.9)

$$\begin{aligned}
 (= F_1) &= \frac{(3.0 \times 10^{-6})(3.0 \times 10^{-6})}{4\pi\epsilon_0 (4 \times 10^{-2})^2} \\
 &= 9 \times 10^9 \times 9.0 \times 10^{-12} \times \frac{1}{16 \times 10^{-4}} \\
 &= 5.0625 \times 10^1 = 50.625 \text{ N.}
 \end{aligned}$$

This force acts along BA. Similarly, force on A due to C is, $F_2 = 90 \text{ N}$ in direction CA.

$$\begin{aligned}
 \therefore \text{Net electric force} = F &= \sqrt{F_1^2 + F_2^2} \\
 &= \sqrt{(50.625)^2 + (90)^2} \\
 &= 103.261 \text{ N.}
 \end{aligned}$$

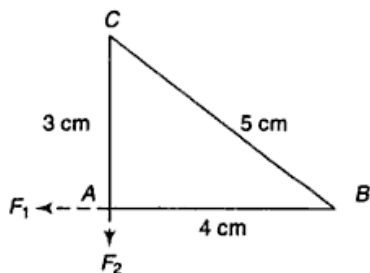


Fig. 2.9 Right angle triangle of Ex. 2.1

The resultant makes an angle of θ with BA where $\tan \theta = \frac{90}{50.625} = 1.778$

2.2 A charge Q is divided between two point charges. What should be the values of the charges on the objects so that the force between them is maximum?

Solution

Let charge on the objects be q and $(Q - q)$.

$$\therefore \text{force between them } (= F) = \frac{q(Q - q)}{4\pi\epsilon_0 d^2} \quad (i)$$

where d is the distance between them.

For maximum F , numerator of (i) is maximum. Let $q(Q - q) = y$.

$\therefore y$ should be maximum.

Differentiating y w.r.t. (q) we get

$$\frac{dy}{dq} = Q - 2q.$$

Equating to zero (to get the maxima of y), $Q - 2q = 0$ or $q = Q/2$.

Thus, the charge should be equally distributed between the objects.

2.3 Three concentric thin spherical shells A , B , C of radii r_1 , r_2 , r_3 are kept as shown in Fig. (2.10i). Shells A and C are given charges q and $-q$ respectively, shell B is earthed. Find charges appearing on the surfaces of B and C .

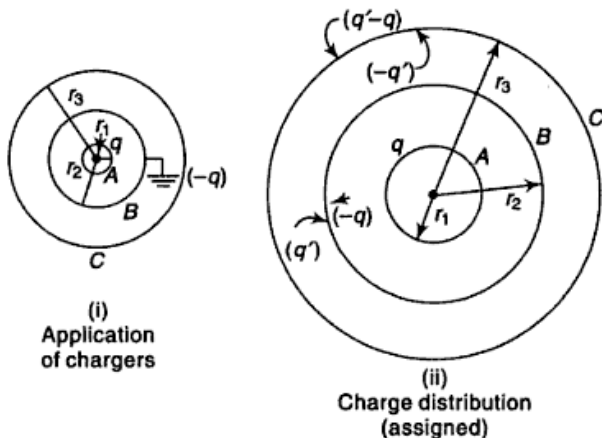


Fig. 2.10 Three concentric spherical shells (Ex. 2.3)

Solution

Inner surface of B (by Gauss's law) must have charge $-q$. Let the outer surface of B have charge q' . The inner surface of C must have charge $-q'$ from Gauss's law. As net charge on C must be $-q$, its outer surface should have a charge $(q' - q)$. The charge distribution is shown in Fig. (2.10ii)

$$\text{Potential at } B \text{ due to charge } q \text{ on } A = \frac{q}{4\pi\epsilon_0 r_2}$$

due to charge $-q$ on the inner surface of $B = \frac{-q}{4\pi\epsilon_0 r_2}$

due to charge q' on outer surface of $B = \frac{q'}{4\pi\epsilon_0 r_2}$

due to charge $-q'$ on inner surface of $C = \frac{-q'}{4\pi\epsilon_0 r_3}$

and due to charge $(q' - q)$ on outer surface of $C = \frac{q' - q}{4\pi\epsilon_0 r_3}$.

Net potential on B is obtained adding all the potentials at B . We then obtain

$$V_B = \frac{q'}{4\pi\epsilon_0 r_2} - \frac{q}{4\pi\epsilon_0 r_3}$$

But $V_B = 0$ as B is earthed.

$$\therefore q' = \frac{r_2}{r_3} q$$

The final charge distribution is shown in Fig. 2.11.

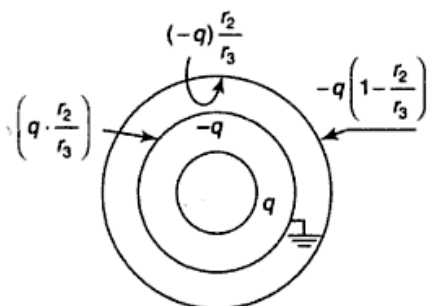


Fig. 2.11 Final charge distribution

2.4 A charge 8×10^{-8} C is distributed uniformly on the surface of a sphere of radius 1 cm. It is covered by a concentric, hollow conducting sphere of radius 5 cm.

- Find the electric field at a point 2 cm away from the centre.
- A charge 6×10^{-8} C is placed on the hollow sphere. Find surface charge density on the outer surface of the hollow sphere.

Solution

To find the field at P of Fig. 2.12(i). Let us consider a Gaussian surface through P .

$$\begin{aligned} \therefore \text{Flux through surface} &= \oint \vec{E} \cdot d\vec{s} \\ &= E \oint ds = 4\pi x^2 E \end{aligned}$$

where $x = 2 \times 10^{-2}$ m.

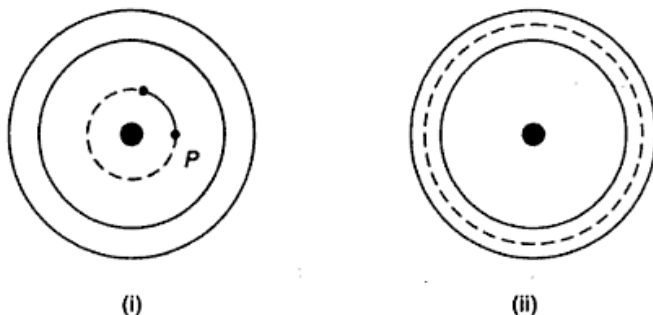


Fig. 2.12 Concentric spheres (Ex. 2.4)

From Gauss' law,

$$4\pi x^2 E = q/\epsilon_0$$

or

$$E = \frac{q}{4\pi x^2 \epsilon_0} = 9 \times 10^9 \times \frac{8 \times 10^{-8}}{4 \times 10^{-4}} = 18 \times 10^5 \text{ N/C.}$$

In Fig. (2.12ii) we take a Gaussian surface through the material of the hollow sphere.

As electric field in a conducting material is zero,

$$\therefore \oint \vec{E} \cdot d\vec{s} = 0 \text{ (through this Gaussian surface).}$$

Using Gauss' law, the total charge enclosed must be zero.

Hence charge on inner sphere of the hollow sphere is $(-8 \times 10^{-8} \text{ C})$. But the total charge given to this hollow sphere is $(6 \times 10^{-8} \text{ C})$.

\therefore Charge on the outer surface will be $(2 \times 10^{-8} \text{ C})$

2.5 There are two thin wire rings, each of radius R , whose axes coincide. The charges of the rings are $(+Q)$ and $(-Q)$. Find the potential difference between the centres of the rings separated by a distance a .

Solution

The arrangement of the rings are shown in Fig. 2.13. The potential at point 1 is given by V_1 = potential at 1 due to ring 1 + potential at 1 due to the ring 2;

$$\text{i.e., } V_1 = \frac{Q}{4\pi\epsilon_0 R} + \frac{-Q}{4\pi\epsilon_0 (R^2 + a^2)^{1/2}}$$

Similarly, the potential at point 2 is

$$V_2 = \frac{-Q}{4\pi\epsilon_0 R} + \frac{Q}{4\pi\epsilon_0 (R^2 + a^2)^{1/2}}$$

$$\begin{aligned} \therefore V &= V_1 - V_2 = \Delta V = 2 \left(\frac{Q}{4\pi\epsilon_0 R} + \frac{-Q}{4\pi\epsilon_0 (R^2 + a^2)^{1/2}} \right) \\ &= \frac{Q}{2\pi\epsilon_0 R} \left[1 - \frac{1}{\sqrt{1 + (a/R)^2}} \right] \end{aligned}$$

.....

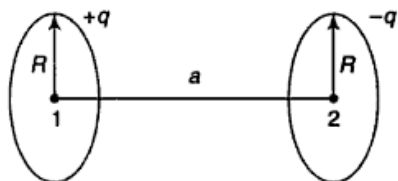


Fig. 2.13 Arrangement of rings in Ex. 2.5

2.6 Three point charges q , $2q$ and $8q$ are to be placed on a 9 cm long straight line. Find the position where the charges should be placed such that the potential energy of this system is minimum. In this situation, what is the electric field at the position of the charge q due to the other two charges?

Solution

Let charges q , $2q$ and $8q$ be placed along a straight line of length 9 cm or 0.09 m with distance between the charges q and $2q$ being x metres. Then distance between $2q$ and $8q$ would be $(0.09 - x)$ m. Thus the potential energy u of the system is given by

$$u = \frac{1}{4\pi\epsilon_0} \left[\frac{q \cdot 2q}{x} + \frac{2q \cdot 8q}{(0.09 - x)} + \frac{q \cdot 8q}{0.09} \right] = 9 \times 10^9 \times 2q^2 \left[\frac{1}{x} + \frac{8}{0.09 - x} + \frac{4}{0.09} \right]$$

u to be minimum,

$$\frac{du}{dx} = 0, \text{ i.e. } 0 = -\frac{1}{x^2} + \frac{8}{(0.09 - x^2)}$$

This, gives
$$x^2 = \frac{(0.09 - x^2)}{8}$$

or
$$2\sqrt{2}x = \pm(0.09 - x)$$

or
$$2\sqrt{2}x \pm x = \pm 0.09$$

$\therefore x(\text{minimum}) = \frac{0.09}{2\sqrt{2} + 1} = 0.0235 \text{ m.}$

Again with E_1 and E_2 as the electric fields at the position of charge q due to charge $2q$ and $8q$ respectively,

$$E_1 = \frac{1}{4\pi\epsilon_0} \times \frac{2q}{x^2} \quad \text{and} \quad E_2 = \frac{1}{4\pi\epsilon_0} \cdot \frac{8q}{(0.09)^2}$$

The electric field at q due to the other two charges is $(E_1 + E_2)$

$$\begin{aligned} \therefore E_1 + E_2 &= \frac{1}{4\pi\epsilon_0} \left[\frac{2q}{(0.0235)^2} + \frac{8q}{(0.09)^2} \right] \\ &= 9 \times 10^9 \times 2q \left[\frac{1}{(0.0235)^2} + \frac{4}{(0.09)^2} \right] \\ &= 4.15 \times 10^{13} \text{ q N/C.} \end{aligned}$$

2.7 An infinite number of charges each equal to Q coulomb are placed along the x -axis at $x = 1, x = 2, x = 8, \dots$ and so on. Find the potential and the electric field at the point ($x = 0$) due to these charges. What will be the potential and electric field if, in the above setup, the consecutive charges have opposite signs?

Solution

Referring to Fig. 2.14, the potential at $x = 0$ due to this set of charges is given by

$$\begin{aligned} V &= \frac{1}{4\pi\epsilon_0} \left(\frac{q}{1} + \frac{q}{2} + \frac{q}{4} + \frac{q}{8} + \dots \right) \\ &= \frac{q}{4\pi\epsilon_0} \left(1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots \right) \\ &= \frac{q}{4\pi\epsilon_0} \times \frac{1}{1 - 1/2} = \frac{2q}{4\pi\epsilon_0} \end{aligned}$$

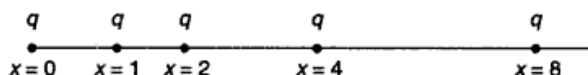


Fig. 2.14 Infinite number of charges placed along x -axis (Ex. 2.7)

Since the point charges are along the same straight line, the intensities at $x = 0$ are also along the x -axis.

$$\begin{aligned}
 E &= \frac{1}{4\pi\epsilon_0} \left[\frac{q}{1^2} + \frac{q}{2^2} + \frac{q}{4^2} + \frac{q}{8^2} + \dots \right] \\
 &= \frac{q}{4\pi\epsilon_0} \left[1 + \frac{1}{4} + \frac{1}{16} + \frac{1}{64} + \dots \right] \\
 &= \frac{1}{4\pi\epsilon_0} \left\{ \frac{q}{1 - 1/4} \right\} = \frac{1}{4\pi\epsilon_0} \times \frac{4q}{3} = \frac{q}{3\pi\epsilon_0}
 \end{aligned}$$

If the consecutive charges are of opposite sign, the potential at $x = 0$ is

$$\begin{aligned}
 V &= \frac{1}{4\pi\epsilon_0} \left(\frac{q}{1} - \frac{q}{2} + \frac{q}{4} - \frac{q}{8} + \frac{q}{16} - \frac{q}{32} + \dots \right) \\
 &= \frac{q}{4\pi\epsilon_0} \left\{ \left(1 + \frac{1}{4} + \frac{1}{16} + \dots \right) - \left(\frac{1}{2} + \frac{1}{8} + \frac{1}{32} + \dots \right) \right\} \\
 &= \frac{q}{4\pi\epsilon_0} \left\{ \frac{1}{1 - 1/4} - \frac{1}{2} \times \frac{1}{1 - 1/4} \right\} = \frac{q}{4\pi\epsilon_0} \left[\frac{4}{3} - \frac{2}{3} \right] \\
 &= \frac{q}{6\pi\epsilon_0}
 \end{aligned}$$

$$\therefore V = \frac{1}{4\pi\epsilon_0} \left(\frac{2q}{3} \right)$$

The electric field intensity at $x = 0$ is

$$\begin{aligned}
 E &= \frac{1}{4\pi\epsilon_0} \left\{ \frac{q}{(1)^2} - \frac{q}{(2)^2} + \frac{q}{(4)^2} - \frac{q}{(16)^2} \dots \right\} \\
 &= \frac{q}{4\pi\epsilon_0} \left\{ \left(1 + \frac{1}{16} + \frac{1}{256} + \dots \right) - \left(\frac{1}{4} + \frac{1}{64} + \frac{1}{1024} + \dots \right) \right\} \\
 &= \frac{q}{4\pi\epsilon_0} \left\{ \frac{1}{1 - 1/16} - \frac{1}{4} \times \frac{1}{1 - 1/16} \right\} \\
 &= \frac{q}{4\pi\epsilon_0} \left\{ \frac{16}{15} - \frac{1}{4} \times \frac{16}{15} \right\} \\
 &= \frac{1}{4\pi\epsilon_0} \left(\frac{4q}{5} \right)
 \end{aligned}$$

.....

2.8 Some equipotential surfaces are shown in Fig. 2.15a and 2.15b. What are the magnitudes and directions of the electric field intensity for these two figures?

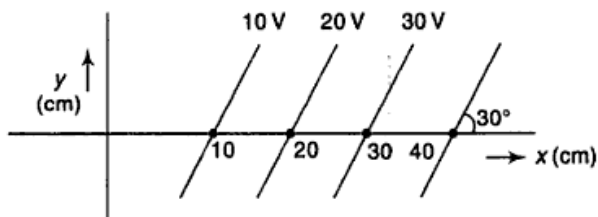


Fig. 2.15a Equipotential surfaces (linear)

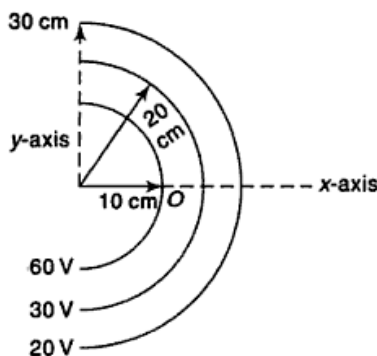


Fig. 2.15b Equipotential surfaces (circular)

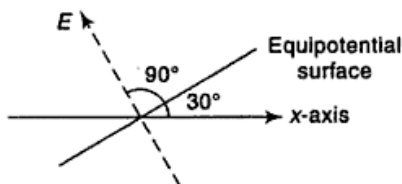


Fig. 2.15c Direction of field of equipotential surfaces shown in Fig. 2.15a

Solution

We know electric field is normal to the equipotential surface in the direction of the decreasing potential.

Thus for the equipotential surfaces of Fig. 2.15a, the field will be at an angle making an angle 120° to the x-axis (Fig. 2.15c)

Magnitude of the electric field in this case is

$$E \cos 120^\circ = -\frac{(20-10)}{(20-10)10^{-2}} \left[\because E = -\frac{dv}{dx} \right]$$

$$\text{or } E \times \left(-\frac{1}{2}\right) = -\frac{10}{0.10}$$

$$\therefore E = 200 \text{ V/m.}$$

In Fig. 2.15b, direction of electric field will be radially outward, similar to a point charge kept at centre,

i.e. $V = \frac{Kq}{r}$, (r) being the radius.

When $V = 60 \text{ V}$,

$$60 = \frac{Kq}{(0.1)}$$

$$\therefore Kq = 6.$$

Then, potential at any distance from the centre is

$$V(r) = \frac{6}{r} \left[\because V = \frac{Kq}{r} \right]$$

Hence

$$E = -\frac{dv}{dr} = \left(\frac{6}{r^2}\right) \text{ V/m}$$

2.9 A square frame of edge 20 cm is placed with its positive normal making an angle of 60° with a uniform electric field of 10 V/m. Find the flux of the electric field through the surface bounded by the frame.

Solution

The situation is displayed in Fig. 2.16. The surface considered is plane and the electric field is uniform. The flux is

$$\begin{aligned}\Delta\phi &= \vec{E} \times \Delta S \\ &= E \Delta S \cos 60^\circ \\ &= (10 \text{ V/m}) \left(20 \times 20 \times \frac{1}{2} \times 10^{-4} \text{ m}^2 \right) \\ &= 0.2 \text{ V.m.}\end{aligned}$$

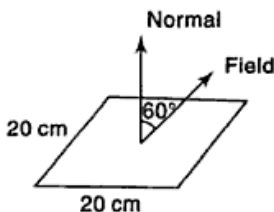


Fig. 2.16 Situation of the square of Ex. 2.9

2.10 A charge q is placed at the centre of a sphere (Fig. 2.17). Taking the outward normal as positive, find the flux of the electric field through the surface of the sphere due to the enclosed charge.

Solution

The electric field here is radially outward and has the magnitude $q/4\pi\epsilon_0 r^2$, (r) being the radius of the sphere. As the positive normal is outward, $Q = 0$ and the flux through this part is

$$\Delta\phi = \vec{E} \cdot \Delta S = \frac{q}{4\pi\epsilon_0 r^2} \times \Delta S.$$

Summing over all the parts of the spherical surface,

$$\begin{aligned}\phi &= \sum \Delta\phi = \frac{q}{4\pi\epsilon_0 r^2} \sum \Delta S = \frac{q}{4\pi\epsilon_0 r^2} \cdot 4\pi r^2 \\ &= \frac{q}{\epsilon_0}.\end{aligned}$$

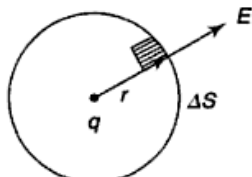


Fig. 2.17 (+q) charge is placed at the centre of a sphere (Ex. 2.10)

2.16 CAPACITOR AND CAPACITANCE

A combination of two conductors placed close to each other and separated by a dielectric medium forms a *capacitor*. One of the conductors is given a positive charge (+Q) while the other one is charged by the same amount of negative charge (-Q). The conductor with (+Q) charge is called the *positive plate* while that with (-Q) charge is known as the *negative plate*. The charge stored in the positive or in the negative plate is the charge on the capacitor [note that the total charge on the capacitor is (+Q + (-Q)) zero]. The potential difference (V) between the plates is called the *potential of the capacitor*. If the positive plate has a potential $V(+)$ while the negative plate has a potential $V(-)$, then $(V) = V(+) - V(-)$.

For any given capacitor, the charge Q on the capacitor is proportional to the p.d. (V) between the plates-

i.e. $Q \propto V$

or $Q = CV$. (2.20)

The constant of proportionality being C , it is called *capacitance* of the capacitor. It depends on the shape, size and geometrical spacing of the conductors as well as the medium between them.

In SI system capacitance is expressed in coulomb/volt and is termed as *Farad*. Since Farad is a large unit by magnitude, in electrical engineering frequently *microfarad* (10^{-6} F) or μF is used.

If $Q = 1$, $V = 1$, then $C = 1\text{F}$, i.e. the capacitor is one Farad if it requires a charge of one coulomb when the potential difference is one volt across its plates. It may be noted here that when the capacitor is fully 'charged' i.e., if it is full to its capacity of containing charges across a voltage source, then the p.d. across its plates is always equal to the magnitude of the voltage source.

2.17 SERIES AND PARALLEL CONNECTION OF CAPACITORS

(a) Capacitors in Series Let us assume three capacitors of capacitances (C_1), (C_2) and (C_3) are connected in series across a dc supply of potential difference (V) through a switch K (Fig. 2.18). On closing the switch, the capacitors get charged and at steady state the p.d. across (C_1), (C_2) and (C_3) are (V_1), (V_2) and (V_3) respectively while the charge in each capacitor is (Q) (since the capacitors are connected in series, same charging current would flow resulting in accumulation of charge (Q) in each capacitor).

Obviously,

$$V_1 = \frac{Q}{C_1}; \quad V_2 = \frac{Q}{C_2}; \quad V_3 = \frac{Q}{C_3}$$

Since $V = V_1 + V_2 + V_3$, we can write

$$\frac{Q}{C} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

or $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$ [(C) being the hypothetical capacitance equivalent to three capacitances (C_1), (C_2) and (C_3) in series].

\therefore For n number of capacitances in series,

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \quad (2.21)$$

Thus we can conclude that for series connection of capacitance across a voltage source, the charge on each capacitor being same while the voltages vary. Also,

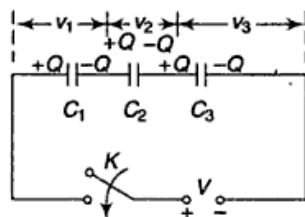


Fig. 2.18 Capacitors in series connection

the sum of individual voltage drops across each capacitor gives the total supply voltage. *The reciprocal of the equivalent capacitance of the series combination is equal to the sum of the reciprocals of the capacitances of the individual capacitors.*

(b) Capacitors in Parallel In this arrangement (Fig. 2.19) on closing K , charges Q_1 , Q_2 and Q_3 would accumulate in capacitances C_1 , C_2 and C_3 during steady state while the voltage will remain V across each capacitor in the parallel combination. Obviously,

$$Q = Q_1 + Q_2 + Q_3,$$

where Q is the total charge drained from the source.

or
$$CV = C_1V + C_2V + C_3V$$

[(C) is assumed to be the equivalent hypothetical capacitance of this parallel combination of capacitance]

i.e.
$$C = C_1 + C_2 + C_3 \quad (2.22)$$

Generalising for n number of capacitances

Thus, in case of parallel combination of capacitances (where voltage across each capacitance remain the same but the capacitors share the charge depending on the value of their capacitance), *the equivalent capacitance is equal to the sum of their individual capacitance.*

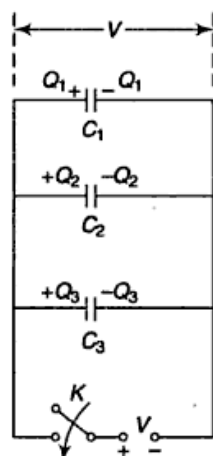


Fig. 2.19 Capacitors in parallel connection

2.18 CONCEPT OF DIELECTRIC STRENGTH

Dielectric strength is the potential gradient required to cause breakdown of a dielectric medium. It is usually expressed in megavolts/millimetre (MV/mm). Dielectric strength depends on the moisture content, carbon content or presence of other impurity and thickness of the medium. With pressure of moisture and other impurities, dielectric strength drops while with increase of thickness the dielectric strength increases.

2.19 TYPES OF CAPACITORS COMMONLY USED

Depending on the nature of dielectric medium the following types of capacitors are usually available:

- Air Capacitors** These have two sets of metal foils (aluminium or brass) and the inbetween medium is ordinary air. These capacitors are used in voltage ranges 100 V to 3000 V and the capacity varies up to 500 μF .
- Paper Capacitors** These have a pair of elongated foil of metal (aluminium or copper or tin) interrelated with oil impregnated paper. Multiple layers of foils with paper is available. They can be used in the range of 100 V to 100 KV and is applicable for both AC and DC circuits. The capacitances are small and is usually in the range of pF.

- (c) **Mica Capacitors** These consist of a series of aluminium or tin foils separated by very thin layers of mica sheets. Usually multiple sheets are used and alternate plates are connected to each other. These capacitors are used in the range of 100–500 V and the capacitances in the range of pF to μF . These capacitors can be used in AC circuits.
- (d) **Ceramic Capacitors** These capacitors are made of discs of ceramic material and the parallel facing surfaces are coated with silver. They have application in the range of a few volts to 3000 volts and the capacitances are from low values of pF to low values of μF . They are extensively used in AC and DC circuit.
- (e) **Electrolytic Capacitors** Usually aluminium foils or cylinders are used as electrodes while electrolytes like porous paper, plastic, aluminium oxide, tantalum powder, etc. are used as dielectric. These capacitors are used in DC circuits and applicable in the range of 1 V to 1 kV. The range of capacitances are usually from 1 pF to even Farad.

2.20 CAPACITANCE OF A PARALLEL-PLATE CAPACITOR

Let us consider two identical plates *A* and *B* are kept in close proximity and parallel to each other and separated by a dielectric medium of thickness (*x*) metre and relative permittivity (ϵ_r) (Fig. 2.20). Let us connect the parallel plates with a potential difference (*V*) volts and we assume (*Q*) coulombs of charge is accumulated by the parallel plate combination acting on a parallel plate capacitor. The electric flux is ψ between the plates having charge of (*Q*) coulombs and the area of each plate is considered to be (*A*) square metres.

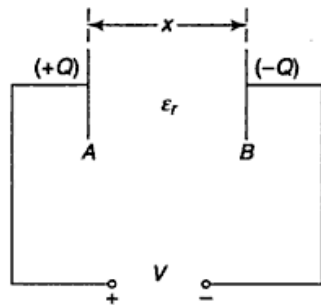


Fig. 2.20 Parallel plate capacitor

Since the charge *Q* is distributed uniformly over each plate, the electric field between the plates is nearly uniform. Let δ represent the electric flux density while *E* the intensity (or the potential gradient) and *C* the capacitance in Farads for this parallel plate capacitor.

Here

$$\delta = \frac{\psi}{A} = \frac{Q}{A} \text{ coulomb/square metre.}$$

But $E = \frac{V}{x}$, *V* being the potential;

also, $\frac{\delta}{E} = \epsilon$ [see equation (2.5)]

or $\frac{Q/A}{V/x} = \epsilon = \epsilon_0 \times \epsilon_r$

$$\therefore \frac{Q}{V} = C = \frac{\epsilon_0 \epsilon_r \times A}{x} \text{ Farad.} \quad (2.23a)$$

If the dielectric medium of the capacitance is vacuum, $\epsilon_r = 1$ and hence

$$C = \frac{\epsilon_0 A}{x} \quad (2.23b)$$

Hence we find capacitance C of a parallel plate capacitor becomes

- (i) proportional to the area of the plate,
- (ii) inversely proportional to the distance of separation (x) between plates, and
- (iii) directly proportional to the relative permittivity of the medium of separation of plates.

2.21 CAPACITANCE OF A MULTI-PLATE CAPACITOR

We just obtained the capacitance of a parallel plate capacitor having only two plates held in parallel. If there are n number of parallel plates, each being identical to the other and alternate plates being connected to the same polarity of the supply potential (Fig. 2.21). We can say that there are $(n - 1)$ space between n number of parallel plates. Thus the capacitor is equivalent to $(n - 1)$ number of parallel plate capacitor consisting of two parallel plates.

\therefore Total capacitance C of multiple parallel plate capacitor (containing n number of plates)

$$= (n - 1) \times \text{capacitance of one pair of plates}$$

$$= (n - 1) \times \frac{\epsilon_0 \epsilon_r A}{x} \text{ Farad} \quad (2.24)$$

where ϵ_0 = absolute permittivity of space,
 ϵ_r = relative permittivity of dielectric medium,
 x = thickness of dielectric medium between any two parallel plates in metres, and
 A = area of each plate in m^2 .

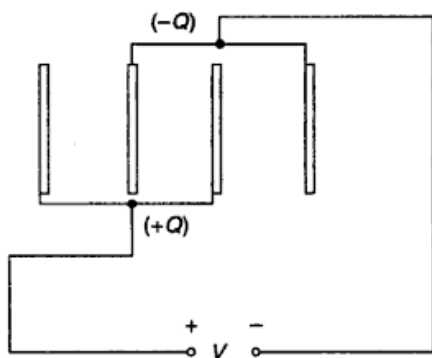


Fig. 2.21 Alternate plates of parallel plate capacitor being connected to same polarity

2.22 CAPACITANCE OF A PARALLEL-PLATE CAPACITOR WITH COMPOSITE DIELECTRICS

Let us assume a parallel plate capacitor with two different dielectrics having relative permittivities ϵ_{r1} and ϵ_{r2} . The separation of plates are x_1 and x_2 metres, as

shown in Fig. 2.22. The plates are of identical cross-sectional area (A) square metre and the charge accumulated in the capacitor is Q coulombs when a p.d. of (V) volts is applied across the capacitor terminals.

Electric flux density is given by

$$\delta = \frac{\psi}{A} = \frac{Q}{A} \text{ coulomb/m}^2.$$

Since $\epsilon = \frac{\delta}{E}$, E being the electric field intensity, we can write

$$\epsilon_1 = \frac{\delta}{E_1} \text{ and } \epsilon_2 = \frac{\delta}{E_2}$$

i.e.
$$E_1 = \frac{\delta}{\epsilon_1} = \frac{\delta}{\epsilon_0 \epsilon_{r_1}}$$

and
$$E_2 = \frac{\delta}{\epsilon_2} = \frac{\delta}{\epsilon_0 \epsilon_{r_2}}.$$

If V_1 and V_2 be the p.d. across the respective dielectrics, we can write

$$\begin{aligned} V &= V_1 + V_2 \\ &= E_1 x_1 + E_2 x_2 \left[\because \text{Intensity } E = \frac{\text{Potential (V)}}{\text{Distance (x)}} \right] \\ &= \frac{\delta}{\epsilon_0 \epsilon_{r_1}} \cdot x_1 + \frac{\delta}{\epsilon_0 \epsilon_{r_2}} \cdot x_2 \\ &= \frac{\delta}{\epsilon_0} \left[\frac{x_1}{\epsilon_{r_1}} + \frac{x_2}{\epsilon_{r_2}} \right] \\ &= \frac{Q}{\epsilon_0 A} \left[\frac{x_1}{\epsilon_{r_1}} + \frac{x_2}{\epsilon_{r_2}} \right] \end{aligned}$$

$$\therefore \text{Capacitance (C)} = \frac{Q}{V} = \frac{Q}{\frac{Q}{\epsilon_0 A} \left[\frac{x_1}{\epsilon_{r_1}} + \frac{x_2}{\epsilon_{r_2}} \right]}$$

$$\text{or } C = \frac{\epsilon_0 A}{\left[\frac{x_1}{\epsilon_{r_1}} + \frac{x_2}{\epsilon_{r_2}} \right]} \text{ Farad} \quad (2.25a)$$

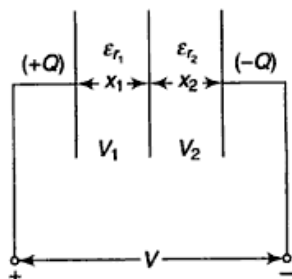


Fig. 2.22 Parallel plate capacitor with composite dielectric

i.e.
$$C = \frac{\epsilon_o A}{\sum \frac{x}{\epsilon_r}}, \text{ for more number of dielectrics.} \quad (2.25b)$$

2.23 CAPACITANCE OF AN ISOLATED SPHERE

We have seen earlier that in case of an isolated sphere, charged with Q coulombs of electricity, the potential at the surface is given by

$$V = \frac{Q}{4\pi\epsilon_o R},$$

R being the radius of the sphere. V being expressed in volts, we can find the capacitance of this sphere as

$$C = \frac{Q}{V} = 4\pi\epsilon_o \cdot R \text{ Farad.}$$

If the medium within the sphere is filled up with a dielectric medium of relative permittivity ϵ_r , we can modify this expression of capacitance as

$$C = 4\pi\epsilon_o \epsilon_r \cdot R \text{ Farad.} \quad (2.26)$$

2.24 CAPACITANCE OF CONCENTRIC SPHERES

A pair of concentric sphere S_1 and S_2 of radii r_1 and r_2 metres, separated by a dielectric medium of permittivity ϵ_r , forms a spherical capacitance. We will consider two cases of this spherical capacitor.

Case-A

S_2 (the outer sphere) is earthed:

Let the inner sphere S_1 be charged by $(+Q)$ coulomb of charge. It will induce $(-Q)$ coulomb charge at the inner surface of S_2 and $(+Q)$ coulomb charge at the outer surface of S_2 . But as the outer surface of S_2 is earthed, this $(+Q)$ charge at the outer surface of S_2 will escape (ϵ_1) to the earth (Fig. 2.23).

\therefore Surface potential of S_1 is given by

$$V_{S_1} = \frac{+Q}{4\pi\epsilon_o \epsilon_r R_1},$$

while surface potential at the inner surface of S_2 is given by $V_{S_2} = \frac{-Q}{4\pi\epsilon_o \epsilon_r R_2}$.

\therefore Potential difference between S_1 and S_2 is

$$\begin{aligned} V &= V_{S_1} - V_{S_2} \\ &= \frac{Q}{4\pi\epsilon_o \epsilon_r} \left[\frac{1}{R_1} - \frac{1}{R_2} \right] = \frac{Q}{4\pi\epsilon_o \epsilon_r} \times \frac{R_2 - R_1}{R_1 R_2} \end{aligned}$$

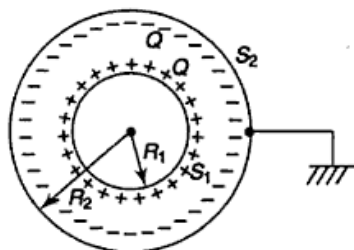


Fig. 2.23 Charge distribution of concentric spheres (outer sphere earthed)

Then,

$$C = \frac{Q}{V} = \frac{Q}{\frac{Q}{4\pi\epsilon_0\epsilon_r} \times \frac{R_2 - R_1}{R_2 R_1}} = 4\pi\epsilon_0\epsilon_r \left[\frac{R_2 - R_1}{R_2 R_1} \right] \text{ Farad} \quad (2.27)$$

Case-B

S_1 (the inner sphere) earthed: This time the outer sphere S_2 is given a charge of $(+Q)$ coulomb. This charge is uniformly distributed in the outer and inner surface of S_2 ; we assume $(+Q_2)$ charge remain at the outer surface while $(+Q_1)$ at the inner surface of S_2 . The charge $(+Q_1)$ at the inner surface of S_2 would induce a charge of $(-Q_1)$ coulomb on the outer surface of S_1 ; $(+Q_1)$ charge induced in the inner surface of S_1 would pass to the earth as the inner surface of S_1 is earthed (Fig. 2.24).

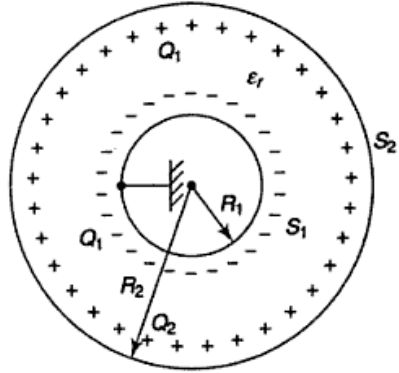


Fig. 2.24 Charge distribution of concentric spheres (inner sphere earthed)

The system is now composed of two subsystems of capacitors as described below:

- (i) Capacitor formed by inner surface of S_2 and outer surface of S_1 and is similar to the case we described in case A

$$\begin{aligned} \therefore \text{Its capacitance, } C_1 &= 4\pi\epsilon_0\epsilon_r \left[\frac{1}{R_2} - \frac{1}{R_1} \right] \\ &= 4\pi\epsilon_0\epsilon_r \left[\frac{R_1 - R_2}{R_2 R_1} \right] \end{aligned}$$

- (ii) Capacitor formed by the outer surface of outer sphere S_2 and earth with air as dielectric.

$$\therefore \text{Its capacitance, } C_2 = 4\pi\epsilon_0\epsilon_r R_2$$

Since these two subsystems of capacitors are electrically parallel, we can find the total capacitance (C) as

$$\begin{aligned} C &= C_1 + C_2 \\ &= 4\pi\epsilon_0\epsilon_r \left[\frac{R_1 - R_2}{R_1 + R_2} \right] + 4\pi\epsilon_0 R_2 \\ &= 4\pi\epsilon_0 \left[\epsilon_r \cdot \frac{R_1 - R_2}{R_1 + R_2} + R_2 \right] \text{ Farad} \end{aligned} \quad (2.28)$$

2.25 CAPACITANCE OF A PARALLEL PLATE CAPACITOR WHEN AN UNCHARGED METAL SLAB IS INTRODUCED BETWEEN PLATES

Let us consider each parallel plate has area of $A \text{ m}^2$ and the distance between them is $x \text{ m}$, the dielectric medium being air. If the charge retained by the capacitor is Q coulombs, the charge density δ is given by

$$\delta = \frac{Q}{A} \text{ C/m}^2.$$

Also
$$C = \frac{\epsilon_o A}{x} \text{ Farad}$$

And,
$$\epsilon = \frac{\delta}{E}, (E) \text{ being the field intensity}$$

$$\therefore E = \frac{\delta}{\epsilon_o} = \frac{Q}{\epsilon_o A}; \epsilon_o \text{ being the permittivity of air medium}$$

When an uncharged metal plate of thickness a ($a < b$) is inserted between the plates, equal and opposite charges are induced on the slab (Fig. 2.25) and the net charge on the slab is equal to zero. Thus the electric field inside the slab is zero. Then electric field would act in the distance $(x - a) \text{ m}$.

However, p.d. (V) = $E \times \text{Distance}$

In our case,
$$V = E \times (x - a) = \frac{Q}{\epsilon_o A} \times (x - a)$$

Thus, the new capacitance C' is given by

$$C' = \frac{Q}{V} = \frac{\epsilon_o A}{(x - a)} \text{ Farad} \quad (2.29)$$

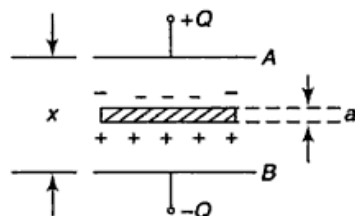


Fig. 2.25 Parallel plate capacitor with uncharged metal plate in between

2.11 Find the equivalent capacitance of the network shown in Fig. 2.26 connected across terminals a and b .

Solution

The capacitors of $3 \mu\text{F}$ and $6 \mu\text{F}$ are connected in series. Hence their equivalent capacitance

$$C_1 = \frac{1}{\frac{1}{3} + \frac{1}{6}} = \frac{6}{2+1} = 2 \mu\text{F}$$

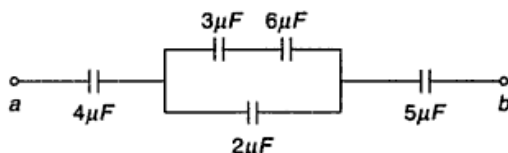


Fig. 2.26 Capacitance configuration of Ex. 2.11

However C_1 and $2\ \mu\text{F}$ are in parallel, therefore their equivalent capacitance $C_2 = C_1 + 2 = 2 + 2 = 4\ \mu\text{F}$.

Thus the network of capacitors reduces to that as shown in Fig. 2.26a.

If C_{eq} be the equivalent capacitance of the new network configuration then,

$$\frac{1}{C_{eq}} = \frac{1}{4} + \frac{1}{4} + \frac{1}{5} = \frac{5+5+4}{20} = \frac{14}{20}\ \mu\text{F}$$

Hence $C_{eq} = \frac{20}{14}\ \mu\text{F} = 1.43\ \mu\text{F}$.

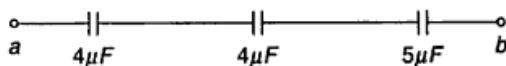


Fig. 2.26a Reduced network of capacitors

2.12 Find the equivalent capacitance of the system of capacitances shown in Fig. 2.27.

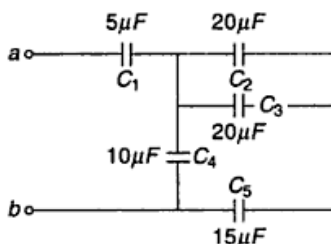


Fig. 2.27 Capacitor configuration of Ex. 2.12

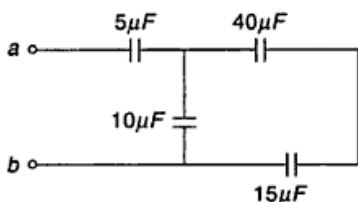


Fig. 2.27a Reduced network

Solution

The capacitors C_2 and C_3 ($20\ \mu\text{F}$ each) are connected in parallel. Hence their equivalent capacitance is $20 + 20 = 40\ \mu\text{F}$. The network is shown in Fig. 2.27a.

$40\ \mu\text{F}$ and $15\ \mu\text{F}$ are connected in series. Hence their equivalent capacitance is $\frac{40 \times 15}{40 + 15}$ i.e. $10.91\ \mu\text{F}$.

Thus, $10\ \mu\text{F}$ and $10.91\ \mu\text{F}$ are connected in parallel. Their equivalent capacitance is $10 + 10.91 = 20.91\ \mu\text{F}$. The corresponding network is shown in Fig. 2.27b.

Hence the equivalent capacitance of the system is

$$C_{eq} = \frac{5 \times 20.91}{5 + 20.91}\ \mu\text{F}, \text{ i.e. } 4.035\ \mu\text{F}$$

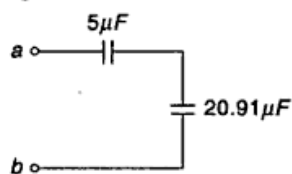


Fig. 2.27b Equivalent network of capacitances of Ex. 2.12

2.13 A $50\ \mu\text{F}$ capacitor is initially charged to accumulate $100\ \mu\text{C}$ of charge. One uncharged capacitor of $200\ \mu\text{F}$ is connected across it in parallel. How much charge will be transferred?

Solution

Let V be the voltage across the capacitors connected in parallel. We know that $V = Q/C$, where Q is the charge in coulomb and C is the capacitance in Farad.

Hence $Q_1/C_1 = Q_2/C_2$, where Q_1 is the charge of capacitor C_1 and Q_2 is the charge of capacitor C_2 . Voltage across the parallel combination of C_1 and C_2 remain the same.

Therefore,
$$\frac{Q_1}{Q_2} = \frac{C_1}{C_2} = \frac{50}{200} = \frac{1}{4} \quad (i)$$

Again, Total charge = Initial charge accumulated by C only = 100 μ Coulomb.

Hence $Q_1 + Q_2 = 100 \quad (ii)$

Solving equations (i) and (ii)

$$Q_1 + 4Q_1 = 100 \mu\text{C}$$

or $Q_1 = 20 \mu\text{C}$ and $Q_2 = 80 \mu\text{C}$

Therefore 80 μC charge will be transferred from C_1 to C_2

2.14 Find the equivalent capacitance across terminals x - y in Fig. 2.28. Also find the time to charge the capacitances by a direct current of 10A.

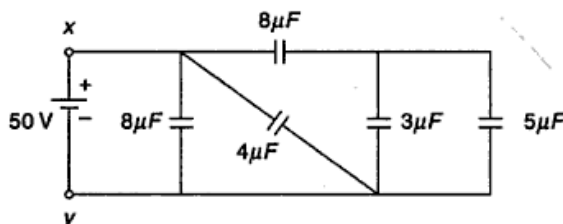


Fig. 2.28 Network of capacitances of Ex. 2.14

Solution

Equivalent capacitance of 3 μF and 5 μF is $(3 + 5)\mu\text{F}$, i.e. 8 μF

The equivalent capacitance of two 8 μF capacitors in series is $8 \times 8/8 + 8 \mu\text{F}$, i.e. 4 μF . The equivalent capacitance of two 4 μF capacitors in parallel is $(4 + 4) \mu\text{F}$, i.e. 8 μF . Here we find two 8 μF capacitors are in parallel with the voltage source.

Hence the equivalent capacitance of the circuit across terminals $(x - y)$ is $(8 + 8) \mu\text{F}$, i.e. 16 μF .

$$\begin{aligned} \text{Now, charge} &= 50 \times 16 \times 10^{-6} \text{ coulomb} \\ &= 800 \times 10^{-6} \text{ coulomb} \end{aligned}$$

If t be the charging time and i be the current then

$$i \times t = 800 \times 10^{-6} [\because Q = i \times t]$$

or
$$t = \frac{800 \times 10^{-6}}{10} \text{ s} = 80 \mu \text{ second.} \quad \dots\dots\dots$$

2.15 A voltage of 90V d.c is applied across two capacitors in series having capacitances of 50 μF and 25 μF . Find the voltage drop across each capacitor. What is the charge in coulomb in each capacitor?

Solution

Since the capacitors are in series, same charge Q is flowing across each of them.

Hence $Q = C_1 V_1 = C_2 V_2$, where C_1 and V_1 are the capacitance and voltage across one capacitor and C_2 and V_2 are the capacitance and voltage across the other.

Therefore, $50V_1 = 25V_2$ or, $V_2 = 2V_1 \quad (i)$

Again $V_1 + V_2 = 90$

Solving equations (i) and (ii), $V_1 + 2V_1 = 90$

or $V_1 = 30$ and $V_2 = 60$.

Hence voltage drop across the capacitors are 30 V and 60 V.

Since both the capacitors are in series

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \quad \text{or} \quad C = \frac{C_1 C_2}{C_1 + C_2} = \frac{50 \times 10^{-6} \times 25 \times 10^{-6}}{50 \times 10^{-6} + 25 \times 10^{-6}}$$

$$= 16.67 \mu\text{F}.$$

The charge supplied by the dc source is

$$Q = CV = 16.67 \times 10^{-6} \times 90 = 1500 \mu\text{C}.$$

In series combination, each capacitor has equal charge and this charge equals the charge supplied by the dc source.

\therefore each capacitor would retain a 1500 μC charge in fully charged condition.

2.16 Calculate the capacitance of a parallel plate capacitor having 20 cm \times 20 cm square plates separated by a distance of 1.0 mm. Assume the dielectric medium to be air with permittivity of 8.85×10^{-12} F/m.

Solution

$$C = \frac{\epsilon_0 A}{x}, \text{ for parallel plate capacitor}$$

$$= \frac{8.85 \times 10^{-12} \times 400 \times 10^{-4}}{1 \times 10^{-3}}$$

$$= 3.54 \times 10^{-10} \text{ F} = 354 \text{ pF}.$$

.....

2.17 In Fig. 2.29, a voltage source is connected across a combination of capacitances at terminals (x - y). Find the current supplied by the battery to charge this combination if the time taken to charge is 50 m sec.

$$[C_1 = C_2 = C_3 = 10 \mu\text{F}]$$

$$V = 100 \text{ V}]$$

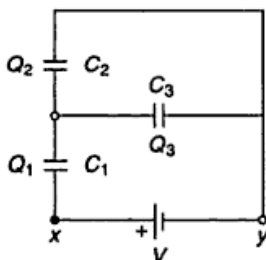


Fig. 2.29 Capacitance configuration
(Ex. 2.17)

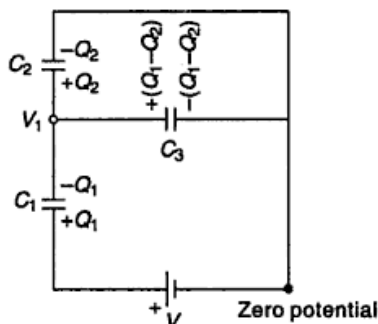


Fig. 2.29a Voltage-charge distribution

Solution

Let us redraw the diagram with voltage and charge distribution (Fig. 2.29a)

Here

$$Q_1 = C_1(V - V_1) \quad (i)$$

$$Q_2 = C_2 V_1 \quad (ii)$$

$$(Q_1 - Q_2) = C_3 V_1 \quad (iii)$$

From equations (ii) and (iii)

$$Q_1 = (C_2 + C_3) V_1$$

$$\text{i.e.} \quad V_1 = \frac{Q_1}{C_2 + C_3} \quad (iv)$$

$$\text{From (i), } \frac{Q_1}{C_1} = V - V_1 \quad (v)$$

Adding (iv) and (v)

$$V = \frac{Q_1}{C_2 + C_3} + \frac{Q_1}{C_1}$$

$$\text{or} \quad V = \frac{(C_1 + C_2 + C_3) Q_1}{C_1 (C_2 + C_3)}$$

$$\begin{aligned} \therefore C (\text{equivalent capacitance}) &= \frac{Q_1}{V} = \frac{C_1 (C_2 + C_3)}{C_1 + C_2 + C_3} \\ &= \frac{10 \times 10^{-6} (10 + 10) 10^{-6}}{(10 + 10 + 10) 10^{-6}} \\ &= 6.67 \times 10^{-6} \mu\text{F} \end{aligned}$$

$$\text{Hence, } Q = \text{charge drawn from source} \\ = CV = 6.67 \times 10^{-6} \times 100 = 6.67 \times 10^{-4} \text{ coulombs}$$

Also, Charge = Current \times Time

$$\therefore \text{Current } (I) = \frac{\text{Charge}}{\text{Time}} = \frac{6.67 \times 10^{-4}}{50 \times 10^{-3}} = 13.34 \text{ mA.}$$

.....

2.18 What is the capacitance across AD in Fig. 2.30?

.....

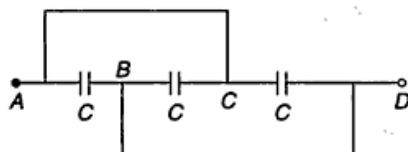


Fig. 2.30 Capacitance configuration (Ex. 2.18)

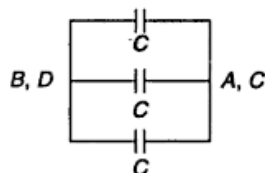


Fig. 2.30a Reduced network (Ex. 2.18)

Solution

Observation reveals that B and D are electrically same points while A and C are electrically same points. The given figure then reduces as shown in Fig. 2.30a. Thus the equivalent capacitance of this parallel combination becomes $3C$.

.....

2.19 If capacitance between adjacent parallel plates be C , find the total capacitance in the system shown in Fig. 2.31.

Solution

Let us redraw the circuit in a conventional form (Fig. 2.31a).

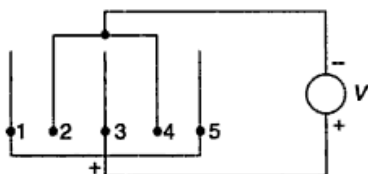


Fig. 2.31 Circuit of Ex. 2.19

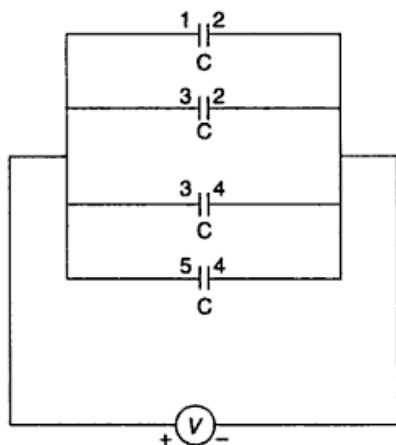


Fig. 2.31a Equivalent circuit of Fig. 2.31

Hence we find that the plate pairs are in parallel and hence the net capacitance is $4C$.

2.20 Find the value of the capacitance C if the equivalent capacitance between points X and Y is to be $1 \mu\text{F}$. All capacitances are in μF .

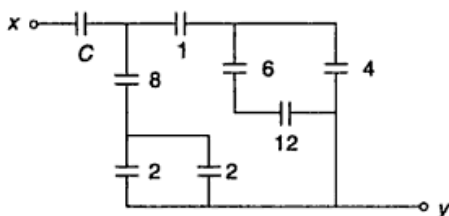


Fig. 2.32 Capacitance configuration (Ex. 2.20)

Solution

The series combination of capacitances 6 and 12 is $6 \times 12 / 6 + 12$ i.e. $4 \mu\text{F}$. The parallel combination of 2 and 2 is $(2 + 2)$, i.e. $4 \mu\text{F}$. Figure 2.32 is reduced to Fig. 2.32a. The parallel combination of 4 and 4 is $8 \mu\text{F}$ in Fig. 2.32a, while the series combination of 8 and 4 is $8 \times 4 / 8 + 4$, i.e. $8/3 \mu\text{F}$. We can reduce Fig. 2.32a further to Fig. 2.32b.

The series combination of 1 and 8 yield $1 \times 8 / 1 + 8$, i.e. $8/9 \mu\text{F}$ and this $8/9 \mu\text{F}$ is in parallel to $8/3 \mu\text{F}$ in Fig. 2.32b. The equivalent capacitance is then $(8/9 + 8/3)$ i.e., $32/9 \mu\text{F}$. Thus finally we reduce the network of Fig. 2.32b to Fig. 2.32c, where C is in series with $32/9 \mu\text{F}$. By the given question,

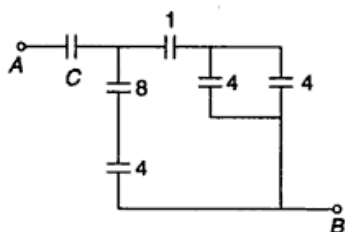


Fig. 2.32a Partly reduced network of Fig. 2.32

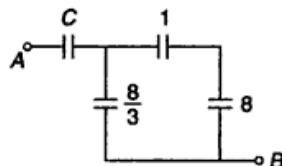


Fig. 2.32b Further network reduction of Fig. 2.32a

$$1 = \frac{1}{C} + \frac{9}{32}$$

$$\therefore C = \frac{32}{23} = 1.39 \mu\text{F}.$$

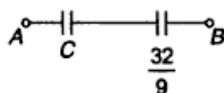


Fig. 2.32c Finally reduced network of Fig. 2.32b

2.21. In Fig. 2.33, $C = 9\text{F}$; $C_1 = 6\text{F}$. Find the equivalent capacitance across $(a - b)$.

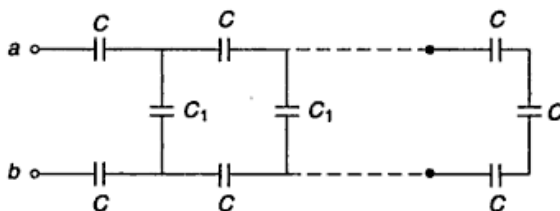


Fig. 2.33 Capacitance configuration (Ex. 2.21)

Solution

We may note that the last three capacitors are all C , i.e. all are 9F each. Since they are in series, the net capacitance of these three capacitors is 3F . This 3F equivalent capacitor is in parallel to C_1 of the previous loop (Fig. 2.33a). Thus parallel combination of $C_1(6\text{F})$ and $C_4(3\text{F})$ gives $C_{q1} = 9\text{F}$.

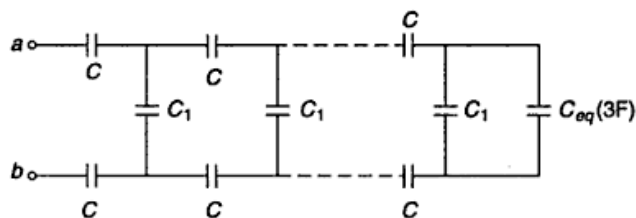


Fig. 2.33a Reduced network of Fig. 2.33

Thus in this loop, there are again two capacitors of C Farad (9F) each in series with C_{q1} . The net capacitance of this loop again becomes 3F . This process continues and finally we come to the first loop while the same result is obtained.

\therefore Equivalent capacitance across ab becomes 3F (Fig. 2.33b).

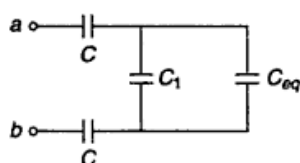


Fig. 2.33b Finally reduced network of Ex. 2.21

2.22 Find the equivalent capacitance across XY (Fig. 2.34).

Solution

Each vertical column is having equivalent capacitance of

$$C_1 = 1F$$

$$C_2 = \frac{1}{2}F$$

$$C_3 = \frac{1}{4}F$$

$$C_4 = \frac{1}{8}F$$

and so on.

It may be noticed that all these capacitors C_1, C_2, \dots are in parallel. (Fig. 2.34a)

$$\therefore C = C_1 + C_2 + C_3 + \dots$$

$$= 1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots$$

$$= 2 \left[\because \text{it is a geometric series whose sum is } 2 \right]$$

$$\therefore C = 2 F.$$

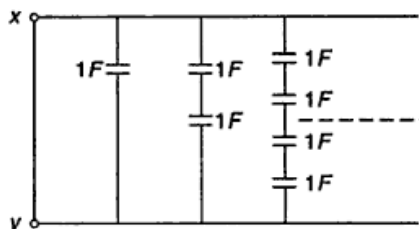


Fig. 2.34 Capacitance network of Ex. 2.22

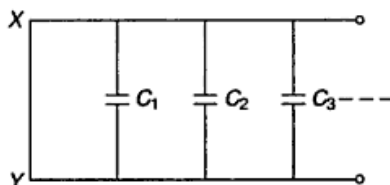


Fig. 2.34a Equivalent network of Fig. 2.34

2.23 In the network of Fig. 2.35, find the capacitance between points x and y. Also find the charges on the three capacitors. Assuming the potential of y to be zero, find the potential at z.

Solution

Equivalent capacitance of $12 \mu F$ and $6 \mu F$ capacitors (being joined in series) is $12 \times 6 / 12 + 6 = 4 \mu F$ (C_x), across XY.

This equivalent capacitance C_x is in parallel to the $2 \mu F$ capacitor. The final equivalent capacitance C is then

$$C = C_x + 2 = 6 \mu F.$$

C is the net capacitance between x and y points. The charge supplied by the battery is then

$$Q = CV = 6 \mu F \times 24 V \\ = 144 \mu C$$

$$[\because \text{Voltage across the equivalent capacitance } C \text{ is } 24 V]$$

Since the p.d. across the $2 \mu F$ capacitor is $24 V$ hence charge on the $2 \mu F$ capacitor is

$$2 \mu F \times 24 V = 48 \mu C.$$

The charge on each of the 12 and $6 \mu F$ capacitors is then $(144 \mu C - 48 \mu C)$, i.e. $96 \mu C$. \therefore Drop across the $6 \mu F$ capacitor is obtained as $96 \mu C / 6 \mu F = 16$ Volts. Observation reveals that this $16 V$ drop is actually the potential V_{zy} (i.e. $V_z - V_y$). Since V_y is zero, hence $V_{zy} = V_z = 16 V$. Then potential at z with respect to y is $16 V$.

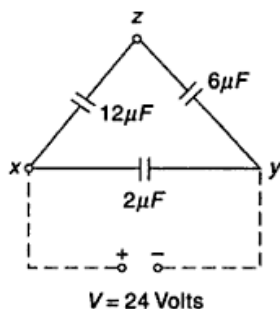


Fig. 2.35 Circuit of Ex. 2.23

2.24 The plates of a parallel plate air capacitor of a capacitance C consists of two circular plates, each of 10 cm radius and placed 0.2 cm apart. The capacitor is charged to $100 V$ and connected across an electrostatic voltmeter. The space between the plates is

then filled up by a dielectric medium so that the capacitance of the parallel plate capacitor becomes $4.5C$ and the voltmeter now reads 25 V. What is the capacitance of the electrostatic voltmeter?

Solution

Let V be the p.d. across the combination (condenser C in parallel to capacitance C' of voltmeter). Since C and C' are in parallel (Fig. 2.36),

$$Q = CV + C'V = (C + C')V$$

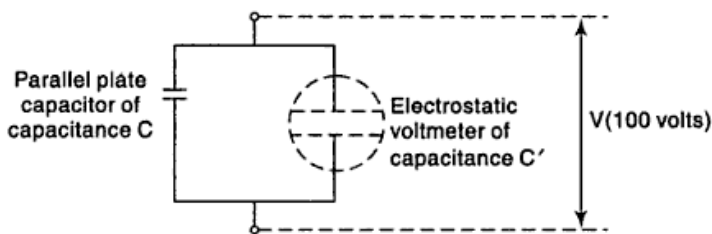


Fig. 2.36 Fig. of Ex. 2.24

Let us now replace the air medium of C and fill it by a dielectric medium such that the new capacitance is $4.5C$.

Total charge remaining the same we can now write

$$4.5C V_1 + C'V_1 = Q = (C + C') V$$

[V_1 is the new voltage across the capacitor]

or $(4.5C + C') V_1 = (C + C') V$

$$\therefore \frac{4.5C + C'}{C + C'} = \frac{V}{V_1} = \frac{100}{25} = 4$$

$$\therefore C' = \frac{C}{6} \text{ (on simplification).}$$

Now $C = \frac{\epsilon_0 A}{x}$, where $A = \pi r^2$

Here,
$$C = \frac{8.85 \times 10^{-12} \times \pi \times (10 \times 10^{-2})^2}{0.2 \times 10^{-2}}$$

$$= \frac{8.85 \times \pi \times 10^{-14}}{0.2 \times 10^{-2}}$$

$$= 1.39 \times 10^{-10} \text{ F}$$

Hence $C' = \frac{C}{6} = 2.32 \times 10^{-11} \text{ F}$.

.....

2.25 In Fig. 2.37, find the p.d. between (x-y) and (x-z) in steady state. Figures shown against capacitances are in μF .

Solution

At steady state all the capacitors are fully charged and no current passes through the circuit. Thus points y and z are at some potential as points a and b respectively.

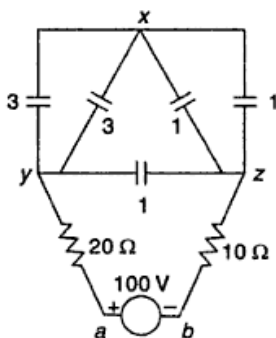


Fig. 2.37 Network of Ex. 2.25

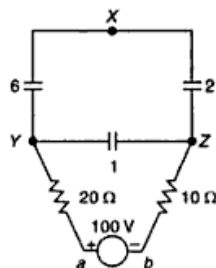


Fig. 2.37a Reduced network of Fig. 2.37

Figure 2.37a shows the reduced network where both $3 \mu\text{F}$ capacitors at the left hand side are replaced by their equivalent capacitance as well as two $1 \mu\text{F}$ capacitors at the right hand side of Fig. 2.37 are also replaced by their equivalent capacitance.

Further reduction of the network (shown in Fig. 2.37a) is possible (Fig. 2.37b).

We thus find the $\frac{3}{2} \mu\text{F}$ equivalent capacitor is placed in parallel to the $1 \mu\text{F}$ capacitor. The charge retained by each of them will be different. We find that charge retained by the $\frac{3}{2} \mu\text{F}$ equivalent capacitance is

$$Q = CV = \frac{3}{2} \times 10^{-6} \times 100 = 150 \mu\text{C}.$$

If we go back to the capacitor configuration of Fig. 2.37a, we find this $150 \mu\text{C}$ charge will be retained by capacitors $6 \mu\text{F}$ and $2 \mu\text{F}$. Thus, the p.d. between x and y is actually the drop across the $6 \mu\text{F}$ capacitor.

$$\therefore V_{x-y} = \frac{Q}{C} = \frac{150 \times 10^{-6}}{6 \times 10^{-6}} = 25 \text{ V}.$$

Similarly, p.d. at $x - z$ will be the drop across the $2 \mu\text{F}$ capacitor

$$\text{i.e. } V_{x-z} = \frac{150 \times 10^{-6}}{2 \times 10^{-6}} = 75 \text{ V}.$$

[Check that, $V_{x-y} + V_{x-z} = V$.]

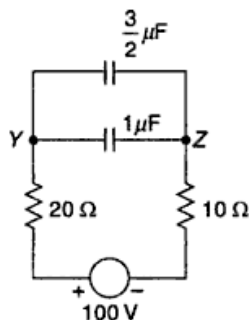


Fig. 2.37b Final reduced network of Fig. 2.37a

2.26 Show that if a dielectric of thickness t and with the same area as the plates of parallel plate capacitor is introduced, the capacitor would then have the capacitance

$$C = \frac{\epsilon_0 A}{\left[d - t + \frac{t}{\epsilon_r} \right]}$$

Solution

Let us suppose that we have a parallel plate capacitor with air as the dielectric medium and capacitance C . Obviously, $C = \epsilon_0 A/d$, (d) being the separation between the plates.

Next we imagine that the capacitor is filled up by another dielectric of dielectric strength ϵ_r replacing the air medium (Fig. 2.38). Let C' be the new capacitance.

$$C' = \frac{\epsilon_0 \epsilon_r A}{d} = \frac{\epsilon_0 A}{d/\epsilon_r}$$

Now, if the two capacitances are supposed to be equal then we find that d/ϵ_r replaces d in the original expression when air was the dielectric medium.

Thus d distance between the plates with air as the dielectric medium is equivalent to distance d/ϵ_r in air medium.

Therefore, if a dielectric of thickness t is introduced then it being equivalent to t/ϵ_r of air medium, the effective air distance between the plate is $(d - t + t/\epsilon_r)$.

$$\therefore C = \frac{\epsilon_0 A}{d - t + (t/\epsilon_r)}$$

[Also, the problem may be solved in another way:

C_1 is the capacitance with ϵ_0 .

$$\therefore C_1 = \frac{\epsilon_0 A}{d - t}$$

C_2 is the capacitance with ϵ_r .

$$\therefore C_2 = \frac{\epsilon_r \epsilon_0 A}{t}$$

Since C_1 and C_2 are in series

$$\begin{aligned} C &= \frac{C_1 C_2}{C_1 + C_2} = \frac{\epsilon_0 A/d - t \times \epsilon_r \epsilon_0 A/t}{\epsilon_0 A/d - t + \epsilon_r \epsilon_0 A/t} \\ &= \frac{\epsilon_0^2 \epsilon_r A^2}{\epsilon_0 A(t + d\epsilon_r - t\epsilon_r)} = \frac{\epsilon_0 A}{\left(d - t + \frac{t}{\epsilon_r}\right)} \end{aligned}$$

We have obtained same result using the previous method.]

2.27 Three plates are held parallel to a common plate (Fig. 2.39). A is the area in m^2 for each of the three parallel plates, while d metre is the distance between each pair of plates. What is the equivalent capacitance?

Solution

Each of the three plates form a parallel plate capacitance with the common plate (the bottom most plate). Also by virtue of their placement and configuration, these capacitances are parallel.

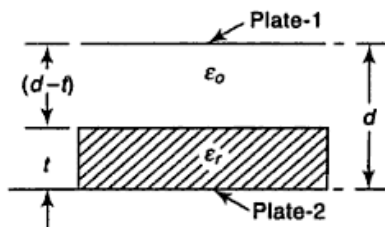


Fig. 2.38 Parallel plate capacitor with two dielectric medium

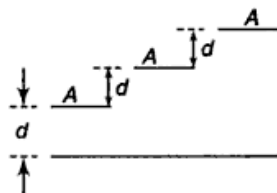


Fig. 2.39 Three plates parallel to a common plate

∴ Equivalent capacitance

$$\begin{aligned}
 C &= C_1 + C_2 + C_3 \\
 &= \frac{\epsilon_0 A}{d} + \frac{\epsilon_0 A}{2d} + \frac{\epsilon_0 A}{3d} \\
 &= \frac{\epsilon_0 A}{d} \left[1 + \frac{1}{2} + \frac{1}{3} \right] = \frac{11}{6} \times \frac{\epsilon_0 A}{d}
 \end{aligned}$$

Hence, equivalent capacitance is $\frac{11}{6} \frac{\epsilon_0 A}{d}$.

2.28 Figure 2.40 shows a set of capacitor configurations. Find charges on the three capacitors.

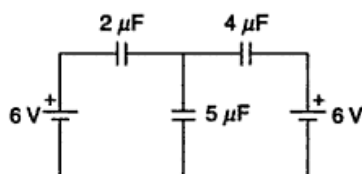


Fig. 2.40 Capacitor configuration in Ex. 2.28

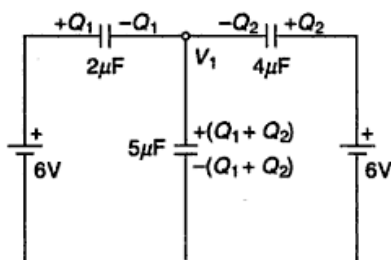


Fig. 2.40a Charge distribution (Ex. 2.28)

Solution

Let us redraw the given figure with charge distribution diagram (Fig. 2.40a)

Since $Q = CV$, we can write

$$Q_1 = 2 \times 10^{-6} (6 - V_1) \quad (i)$$

$$Q_2 = 4 \times 10^{-6} (6 - V_1) \quad (ii)$$

$$(Q_1 + Q_2) = 5 \times 10^{-6} (V_1 - 0) \quad (iii)$$

$$Q_2 = 2Q_1 \quad (iv)$$

Solving for (ii) and (iii) we get

$$5Q_2 + 4(Q_1 + Q_2) = 20 \times 10^{-6} \times 6$$

$$4Q_1 + 9Q_2 = 120 \times 10^{-6}$$

or $4Q_1 + 18Q_1 = 120 \times 10^{-6}$

∴ $Q_1 = 5.45 \mu\text{C}$

Thus $Q_2 = 10.9 \mu\text{C}$.

2.29 Figure 2.41 represents a capacitive ladder network. Obtain equivalent capacitance across $(x - y)$.

Solution

As the capacitive ladder network is infinitely long, the capacitance of the ladder to the right of points M and N is the same as that of the ladder to the right of the points $(x - y)$.

Let the equivalent capacitance of the network to the right of $M - N$ be C_1 . We must draw the reduced network (Fig. 2.41a).

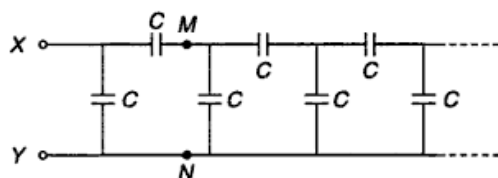


Fig. 2.41 A capacitive ladder network

The equivalent capacitance between $x - y$ is

$$C_{x-y} = C + \frac{CC_1}{C + C_1}$$

However, the ladder is symmetric and hence all the loops are identical to the adjacent loop. Hence the equivalent capacitance of the ladder is also C_1 , i.e. $C_{x-y} = C_1$.

$$\therefore C_1 = C + \frac{CC_1}{C + C_1}$$

$$\text{or } C_1^2 - CC_1 - C^2 = 0$$

$$\therefore C_1 = \frac{C + \sqrt{C^2 + 4C^2}}{2} = \frac{1 + \sqrt{5}}{2} C$$

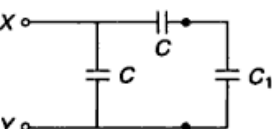


Fig. 2.41a Reduced network of Fig. 2.41

[negative sign is neglected]

2.30 The space between two plates of a parallel plate capacitor C is filled up with three different dielectric slabs of identical size as shown in Fig. 2.42. If the dielectric constants of the three slabs be ϵ_1 , ϵ_2 , and ϵ_3 , find the new value of the capacitance. The plate cross-sectional area is A and the separation is d .

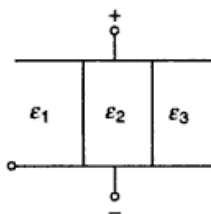


Fig. 2.42 Capacitor of Ex. 2.30

Solution

Let us consider each $1/3$ assembly as separate capacitors C_1 , C_2 and C_3 .

$$C_1 = \frac{\epsilon_1 (A/3)}{d}; \quad C_2 = \frac{\epsilon_2 (A/3)}{d}; \quad C_3 = \frac{\epsilon_3 (A/3)}{d}$$

As the three capacitors are in parallel (the +ve plates are joined together for all capacitors as well as the negative plates are also connected together),

$$C_{eq} = C_1 + C_2 + C_3 = \frac{A}{3d} (\epsilon_1 + \epsilon_2 + \epsilon_3).$$

2.26 EXPRESSION OF INSTANTANEOUS CURRENT AND VOLTAGE IN A CAPACITOR

The instantaneous current in a capacitor is given by

$$i = \frac{dq}{dt} = \frac{d}{dt}(Cv) = C \frac{dv}{dt} \quad (2.30a)$$

Thus, the voltage across the capacitor being constant, current through it is zero. This means, on application of dc voltage across the capacitor and with no initial charge the capacitor first acts as short circuit but as soon as it accumulates full charge, it behaves like an open circuit.

Also, from above

$$dv = \frac{1}{C} \cdot i \cdot dt$$

$$\text{or} \quad \int_{v_o}^{v_f} dv = \frac{1}{C} \int_0^t i \cdot dt \quad [v_o = \text{initial voltage in the capacitor, if any and } v_f = \text{the final voltage in the capacitor}]$$

$$\text{or} \quad v_f - v_o = \frac{1}{C} \int_0^t i \cdot dt$$

$$\therefore \quad v_f = \frac{1}{C} \int_0^t i \cdot dt + v_o \quad (2.30b)$$

[Normally, $v_o = 0$ and hence $v_f = v_C = \frac{1}{C} \int_0^t i \cdot dt$]

2.27 CHARGING AND DISCHARGING OF CAPACITANCE

(a) Charging

Let a dc voltage V be applied (at $t = 0$) by closing a switch S in a series RC circuit (Fig. 2.43). The capacitor being charged, at $t > 0$, the charging current becomes i . We can write

$$Ri + \frac{1}{C} \int_0^t i \cdot dt = V \quad (2.31)$$

[\because drop across the resistor $= Ri$ and the drop across (C) is obtained from the instantaneous current (i) given by

$$i = C \frac{dv}{dt}$$

$$\text{i.e.} \quad v = \frac{1}{C} \int i \cdot dt]$$

It may be noted here that as the charging gets started, upper plate of (C) will start accumulating +ve charges while the lower plate accumulates -ve charge.

Differentiation of equation 2.31 results

$$R \frac{di}{dt} + \frac{i}{C} = 0 \quad (2.31a)$$

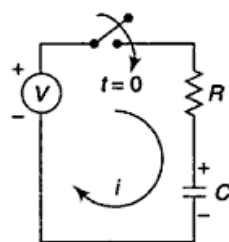


Fig. 2.43 Charging and discharging of capacitor

or
$$\frac{di}{i} = -\frac{1}{RC} dt$$

Integrating both sides

$$\log_e i = -\frac{t}{RC} + K_1, \text{ where } K_1 \text{ is a constant}$$

or
$$\log_e \frac{i}{K_2} = \log_e e^{-t/RC} \quad (\text{where } K_1 = \log_e K_2)$$

or
$$i = K_2 e^{-t/RC} \quad (2.32)$$

With application of voltage and assuming no initial charge across the capacitor, the capacitor will not produce any voltage across it but acts as a short circuit causing the circuit current to be (V/R) .

i.e. at $t = 0^+, i(0^+) = \frac{V}{R}$

Hence from equation (2.32) at $t = 0^+$

$$\frac{V}{R} = K$$

Finally we then obtain,
$$i = \frac{V}{R} e^{-t/RC} \quad (2.33)$$

It may be observed that the charging current is a decaying function, the plot being shown in Fig. 2.44a. As the capacitor is getting charged, the charging current dies out.

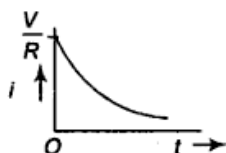


Fig. 2.44a Profile of current in RC charging circuit

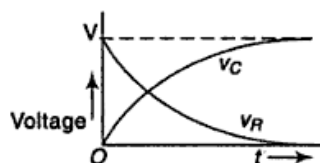


Fig. 2.44b Profiles of v_R and v_C in RC charging circuit

The corresponding voltage drops across the resistor and capacitor can be obtained as follows:

$$v_R = iR = V e^{-t/RC} \quad (2.34)$$

and
$$v_C = \frac{1}{C} \int i dt = \frac{1}{C} \int_0^t \frac{V}{R} e^{-t/RC} dt$$

$$= V (1 - e^{-t/RC}) \quad (2.35)$$

Observing equations (2.34) and (2.35) it reveals that (v_R) is a decaying function while (v_C) is an exponentially rising function [profiles of (v_R) and (v_C) are shown in Fig. 2.44b]. The steady state voltage across capacitor is V volts.

The constant is obtained by substituting $t = RC$ which gives $v_C = V(1 - 0.368) = 0.632V$, i.e. the item by which the capacitor attains 63.2% of steady state voltage. The instantaneous powers are given by

$$p_R = iv_R = \frac{V^2}{R} e^{-2t/RC}$$

and
$$p_C = iv_C = \frac{V^2}{R} (e^{-t/RC} - e^{-2t/RC})$$

(b) Discharging

Let us now study the discharging case when the switch S is thrown to a contact S' such that the R - C circuit is shorted and the voltage source is withdrawn (Fig. 2.45). Here we can write

$$Ri + \frac{1}{C} \int i dt = 0 \quad (2.36)$$

Differentiating equation (2.36) we get

$$R \frac{di}{dt} + \frac{i}{C} = 0 \quad (2.37)$$

Solution of equation (2.37) is

$$i = K' e^{-t/RC} \quad (2.38)$$

where K' is a constant.

However at $t = 0^+$, the voltage across the capacitor will start discharging current through the resistor in opposite direction to the original current (shown by i_{dis} in Fig. 2.45). Hence the direction of i during discharge is negative and its magnitude is given by (V/R) .

Hence from equation (2.38) we get

$$-\frac{V}{R} = K' \text{ (at } t = 0^+)$$

The complete solution is then

$$i = -\frac{V}{R} e^{-t/RC} \quad (2.39)$$

The decay transient is plotted in Fig. 2.46.

The corresponding transient voltages are given by

$$v_R \text{ (voltage drop across } R) = iR = -Ve^{-t/RC} \quad (2.40a)$$

and
$$v_C \text{ (voltage drop across } C) = \frac{1}{C} \int i dt = Ve^{-t/RC} \quad (2.40b)$$

Obviously, $v_R + v_C = 0$

Figure 2.47 represents the profiles of v_R and v_C with t . In the discharging circuit, the time constant is given by the product of R and C such that $v_C = Ve^{-t/RC}$

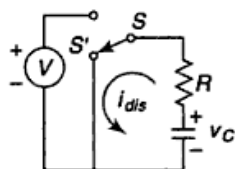


Fig. 2.45 Discharging in RC series circuit

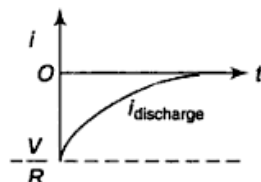


Fig. 2.46 Current decay transient in RC discharging circuit

0.369V = 0.37V, i.e. the time by which the capacitor discharges to 37% of its initial voltage.

The instantaneous powers are given by

$$p_R = v_R i = \frac{V^2}{R} e^{-2t/RC} \quad (2.41a)$$

and
$$p_C = v_C i = -\frac{V^2}{R} e^{-2t/RC} \quad (2.41b)$$

[The charge stored in the capacitor during charging is

given by $q = Cv_C = CV (1 - e^{-t/RC})$ or $q =$

$Q(1 - e^{-t/RC})$ while that during discharging is given by $q = Cv_C = CVe^{-t/RC}$ coulombs or, $q = Qe^{-t/RC}$].

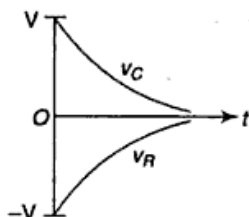


Fig. 2.47 v_R and v_C in RC discharging circuit

2.31 Calculate the time taken by the capacitor of 1 μF and in series with a 1 $\mu\Omega$ resistance to be charged upto 80% of the final value.

Solution

The time constant T is given by

$$T = RC = 1 \times 10^6 \times 10^{-6} = 1 \text{ sec.}$$

The charging of capacitor is expressed by the following equation

$$q = Q_0 (1 - e^{-t/RC}).$$

Here $q = 0.8 Q_0$; $R = 1 \text{ sec.}$

$$\therefore 0.8 = 1 - e^{-t} \quad \text{or, } e^{-t} = 0.2$$

Hence $t = 1.61 \text{ sec.}$

.....

2.32 A dc constant voltage source feeds a resistance of 2000 $\text{k}\Omega$ in series with a 5 μF capacitor. Find the time taken for the capacitor when the charge retained will be decayed to 50% of the initial value, the voltage source being short circuited.

Solution

Time constant $T = RC = 2 \times 10^6 \times 5 \times 10^{-6} = 10 \text{ sec.}$

The decaying condition is represented by the following expression

$$q = Q_0 e^{-t/T}$$

However,

$$q = 0.5 Q_0,$$

$$\therefore 0.5 Q_0 = Q_0 e^{-t/T}$$

$$\text{or } 0.5 = e^{-t/T} = e^{-t/10}$$

$$\text{or } -t/10 = \log_e (0.5)$$

$$\text{or } t = 6.938$$

.....

2.33 In Fig. 2.48 the switch K is closed. Find the time when the current from the battery reaches to 500 mA.

$[R_x = 50 \Omega; R_y = 70 \Omega; C = 100 \mu\text{F}]$

Solution

Let current through R_x be I_x and through C be I_y after switch K is closed.

$$I_x = \frac{10}{50} = 0.2 \text{ A} = 200 \text{ mA}$$

However

$$I = I_x + I_y$$

[I being the current from the supply]

or $500 = 200 + I_y$ [\because supply current is 500 mA]

$$I_y = 300 \text{ mA}$$

But

$$I_y = \frac{V}{R_y} e^{-t/T} \quad [T = RC = 70 \times 100 \times 10^{-6} = 0.007 \text{ sec}]$$

or

$$0.3 = \frac{10}{70} e^{-t/0.007}$$

or

$$\frac{t}{0.007} = \log_e (2.1)$$

$$t = 5.2 \text{ m-sec.}$$

This is the time required when the d.c. source current flow will be 500 mA.

2.34 A $10 \mu\text{F}$ capacitor is initially charged to 100 volts dc. It is then discharged through a resistance of (R) ohms for 20 seconds when the p.d. across the capacitor is 50 V. Calculate the value of (R).

Solution

In the discharging condition of the capacitor,

$$q = Q_0 e^{-t/RC} \quad \text{or} \quad v = V_0 e^{-t/RC}$$

As per the question capacitor p.d. gets discharged to 50 V from the initial p.d. of 100 V.

$$\therefore v = 0.5 V_0$$

Hence we obtain, $0.5 = e^{-t/R \times 10 \times 10^{-6}}$

$$\text{or} \quad \log_e 0.5 = -\frac{t}{R \times 10^{-5}} = -\frac{20}{R \times 10^{-5}}$$

$$\text{or} \quad -0.7 = -\frac{20}{R \times 10^{-5}}$$

$$\therefore R = 28.86 \times 10^5 \Omega = 2.86 \text{ M}\Omega.$$

2.35 A resistance R and $5 \mu\text{F}$ capacitor are connected in series across a 100 V d.c. supply. Calculate the value of R such that the voltage across the capacitor becomes 50 V in 5 sec after the circuit is switched on.

Solution

In case of charging

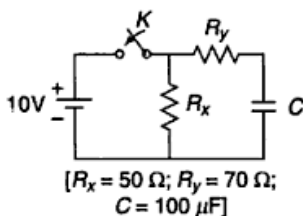


Fig. 2.48 Circuit of Ex. 2.33

$$q = Q_0(1 - e^{-t/T}) \quad [T = RC = (5 \times 10^{-6} R) \text{ sec.}]$$

$$\text{or} \quad v = V_0(1 - e^{-t/T})$$

As per the question, the p.d. across the capacitor is 50 V within 5 sec.

$$\therefore v = 0.5 V_0 \quad [V_0 = \text{final p.d. in steady state} = 100 \text{ V}]$$

$$\text{and} \quad t = 5 \text{ sec.}$$

$$\therefore 0.5 = 1 - e^{(-5)/(5 \times 10^{-6})R} \quad \text{or, } -0.5 = -e^{-10^6/R}$$

$$R = 1.45 \text{ M}\Omega$$

.....

2.36 A $5 \mu\text{F}$ capacitor is initially charged with $500 \mu\text{C}$. At $t = 0$, the switch K is closed (Fig. 2.49). Determine the voltage drop across the resistor at $t < T$ and $t = \infty$.

Solution

The equivalent capacitance of bank of parallel capacitances is $5 \mu\text{F}$. As soon as K is closed, the equivalent $5 \mu\text{F}$ capacitor is in series with C_0 and the net capacitance becomes $2.5 \mu\text{F}$.

$$\therefore T(\text{time constant}) = R C_{\text{net}} = 10 \times 2.5 \times 10^{-6} = 25 \mu \text{ sec.}$$

The initial voltage V_0 across capacitor C_0 is given by

$$V_0 = \frac{Q_0}{C_0} = \frac{500 \mu\text{C}}{5 \times 10^{-6}} = 100 \text{ V}$$

With closing of K , capacitor C_0 will start discharging, however at $t = 0^+$, there will be no voltage across C_1 , C_2 or C_3 .

Thus the entire voltage drop will be across R only (v_R) at $t = 0^+$ time.

i.e.

$$v_R = V_0 \text{ (decaying)}$$

$$= V_0 e^{-t/RC} = 100 e^{-t/25 \times 10^{-6}}$$

$$= 100 e^{-4 \times 10^4 t} \text{ V}$$

At $t = \infty$, v_R becomes zero.

[It is also evident that in steady state ($t = \infty$), the charge of C_0 will be distributed through C_1 , C_2 and C_3 and no current will flow through the circuit. Hence $i = 0$, $v_R = i_R = 0$].

.....

2.37 In Fig. 2.50, a capacitor of capacitance C is charged to a voltage V_0 (dc) and is allowed to discharge through a resistance R while charging another capacitor of capacitance αC . Determine the final voltage at terminals $(a - b)$ under steady state condition.

Solution

Let V_f be the final voltage appearing across $(a - b)$ after discharging of C charging αC through R .

Equating the charge of the two capacitors

$$V_f(\alpha C) = V_0 C - V_f C$$

or

$$V_f(1 + \alpha) = V_0$$

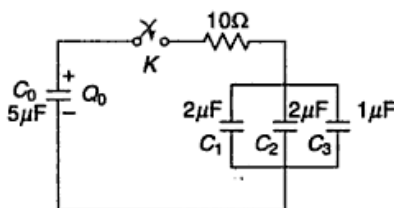


Fig. 2.49 Circuit of Ex. 2.36

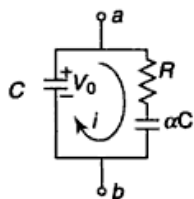


Fig. 2.50 Circuit of Ex. 2.37

$$\therefore V_f = \frac{V_o}{1+\alpha}$$

[It may be noted that the final voltage across $(a-b)$ is independent of R].

2.38 In Example 2.37 what fraction of the energy originally stored is lost?

Solution

Initial energy = $\frac{1}{2}CV_o^2$ [the proof is furnished in Article 2.28]

Final energy = $\frac{1}{2}(\alpha C)V_f^2 + \frac{1}{2}CV_f^2 = \frac{1}{2}CV_f^2(1+\alpha)$

$$= \frac{1}{2}(1+\alpha)C\left(\frac{V_o}{1+\alpha}\right)^2 = \frac{1}{2}\frac{V_o^2 C}{(1+\alpha)} \quad [\because V_f = \frac{V_o}{1+\alpha}, \text{ as described in Ex. 2.37}]$$

Hence, loss in energy = initial energy - final energy

$$\begin{aligned} &= \frac{1}{2}CV_o^2 - \frac{1}{2}CV_o^2 \cdot \frac{1}{\alpha+1} \\ &= \frac{1}{2}CV_o^2 \left[1 - \frac{1}{\alpha+1}\right] = \frac{1}{2}CV_o^2 \cdot \frac{\alpha}{\alpha+1} \end{aligned}$$

[It may be noted that this loss of energy is due to presence of resistance R . However, the energy loss expression is independent of R].

2.39 The $10 \mu\text{F}$ capacitor in RC circuit of Fig. 2.51 has initial charge of $100 \mu\text{C}$ with polarities as shown in Fig. 2.51. At $t = 0$, the switch being closed, a dc voltage of 100 V is applied. Find the expression for the current.

Solution

In the charging case

$$100 = 500 \times i + \frac{1}{10 \times 10^{-6}} \int i dt$$

$$\text{or} \quad 0 = 500 \frac{di}{dt} + \frac{i}{C}$$

$$\text{or} \quad \frac{di}{i} = -\frac{1}{500C} dt$$

$$\text{or} \quad i = Ke^{-200t}, \text{ where } K \text{ is constant.}$$

However, due to initial charge of $100 \mu\text{C}$ in the polarity shown, the equivalent voltage becomes

$$V_o = \frac{q_o}{C} = \frac{100 \times 10^{-6}}{10 \times 10^{-6}} = 10 \text{ V}$$

This 10 V also sends current in the direction of i .

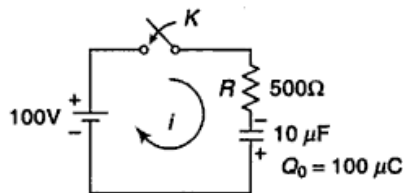


Fig. 2.51 Circuit of Ex. 2.39

Hence at $t = 0$

$$i_0 = (V + V_o)/R = \frac{110}{500} = 0.22 \text{ A}$$

Thus at $t = 0$, $0.22 = Ke^{-200 \times 0}$

or $K = 0.22$

Thus the expression for current becomes

$$i = 0.22 e^{-200t} \text{ A.}$$

.....

2.28 ENERGY STORED IN CAPACITOR

A capacitor never dissipates energy and only stores it when the capacitor is assumed to be ideal. It can store finite amount of energy, even if the steady state current through it is zero. A capacitor discharges its energy when connected in a circuit having resistances.

The power absorbed by the capacitor is given by

$$p = v \cdot i = v \cdot C \cdot \frac{dv}{dt}$$

\therefore Energy stored by the capacitor is

$$\begin{aligned} W &= \int_0^t p dt = \int_0^t v \cdot C \cdot \frac{dv}{dt} \cdot dt \\ &= \frac{1}{2} C v^2 \end{aligned} \quad (2.39)$$

The energy stored by the capacitor is then $1/2 C v^2$ Joules.

$$\left[\text{Also, } W = \frac{1}{2} C v^2 = \frac{1}{2} C \cdot \frac{Q^2}{C^2} = \frac{Q^2}{2C} \right] \quad (2.40)$$

W is always expressed in joules.

2.40 A 10F capacitance is charged to 5 V and is isolated. It is then connected in parallel to a 40 F capacitor. What is the decrease in total energy of the system?

Solution

$$Q_1 = C_1 V_1 = 10 \times 5 = 50 \text{ C}$$

$$W_1 = \frac{1}{2} C_1 V_1^2 = \frac{1}{2} \times 10 \times (5)^2 = 125 \text{ J}$$

Next, with parallel combination of 10 F and 40 F, the equivalent capacitance of the system becomes 50 F.

$\therefore W_2$ (final energy when both the capacitors are connected in parallel)

$$= \frac{1}{2} C V^2 = \frac{1}{2} \cdot \frac{Q^2}{C} = \frac{1}{2} \times (50)^2 \times \frac{1}{50} = 25 \text{ J}$$

Thus, the decrease in total energy of the system is $(125 \text{ J} - 25 \text{ J})$, i.e. 100 J.

.....

2.41 A parallel plate capacitor of plate area A and plate separation d is charged to a potential difference V and then the battery is disconnected. A slab of dielectric constant ϵ is then inserted between the plates so as to fill the space between the plates. If Q , E and W denote respectively, the magnitude of charge on each plate, the electric field between the plates (after the slab is inserted), and the work done on the system, show that in the process of inserting the slab the work done is given by

$$W = \frac{\epsilon_0 AV^2}{2d} \left(1 - \frac{1}{\epsilon} \right)$$

Solution

Let us assume that the capacitor retain charge Q when charged to voltage V at the initial condition. This charge will remain same even when the slab is inserted; however, the electric field intensity will reduce by a factor ϵ .

$$\therefore Q = CV = \epsilon_0 \frac{AV}{d}; E \text{ (field intensity)} = \frac{V}{\epsilon d}$$

Energy of the system before dielectric ϵ is inserted,

$$\begin{aligned} W_1 &= \frac{1}{2} \frac{Q^2}{C} = \frac{\epsilon_0^2 A^2 V^2}{2d^2} \times \frac{d}{\epsilon_0 A} & \left[\because \text{from above } C = \frac{\epsilon_0 A}{d} \right] \\ &= \frac{\epsilon_0 AV^2}{2d} \end{aligned}$$

After insertion of dielectric

$$\begin{aligned} W_2 &= \frac{1}{2} \frac{Q^2}{C}, \text{ where } C_1 = \epsilon_0 \frac{\epsilon A}{d} \\ &= \frac{1}{2} \frac{\epsilon_0^2 A^2 V^2}{2d^2} \times \frac{d}{\epsilon_0 \epsilon A} = \frac{\epsilon_0 AV^2}{2\epsilon d} \end{aligned}$$

$$\therefore W_1 - W_2 = \frac{\epsilon_0 AV^2}{2d} \left(1 - \frac{1}{\epsilon} \right).$$

2.42 A capacitor of capacitance C is fully charged by a 220 V supply. It is then discharged through a small resistance embedded in a thermally insulated block of specific heat $2.5 \times 10^2 \text{ J kg}^{-1} \text{ K}^{-1}$ and of mass 0.2 kg. If the temperature of the block rises by 1°K , find the value of C .

Solution

Energy stored in the capacitor is

$$W = \frac{1}{2} CV^2 = \frac{1}{2} \times C \times (220)^2 \text{ Joule}$$

Energy supplied as heat in the block is obtained as

$$H = m s t$$

where

H = heat,

m = mass,

s = specific heat, and

t = temperature rise.

Here $H = 0.2 \times 2.5 \times 10^2 \times 1 \text{ Joule} = 50 \text{ Joule}$

In a thermally insulated system

$$W = H$$

$$\therefore \frac{1}{2} \times C \times (220)^2 = 50$$

$$\therefore C = \frac{50}{(220)^2} \times 2 = 2066 \mu\text{F}.$$

.....

2.43. An uncharged capacitor is connected to a battery. Show that half the energy supplied by the battery is lost as heat while charging the capacitor.

Solution

The charge required by the capacitor is $Q = CV$ while the work done by the battery is

$$W = Q \cdot V$$

The capacitor would store energy of $\frac{1}{2}CV^2$.

$$\text{However, } \frac{1}{2}CV^2 \equiv \frac{1}{2}QV.$$

Then the remaining energy is $\left(QV - \frac{1}{2}QV\right)$

i.e. $\frac{1}{2}QV$ is lost as heat. Then half the energy supplied by the battery is lost as heat.

.....

■ ADDITIONAL EXAMPLES ■

2.44. A ring of radius r contains a charge Q distributed uniformly over its length. Find the electric field at a point on the axis of the ring at a distance x from the centre.

Solution

Let us consider a small element of the ring at point A having a charge dQ . The field at P due to this element is

$$dE = \frac{dQ}{4\pi\epsilon_0 (AP)^2}$$

The component of dE along x -axis is

$$\begin{aligned} dE \cos \theta &= \frac{dQ}{4\pi\epsilon_0 (AP)^2} \times \frac{QP}{AP} \\ &= \frac{x \cdot dQ}{4\pi\epsilon_0 (r^2 + x^2)^{3/2}} \end{aligned}$$

\therefore The net field at P is

$$\begin{aligned} E &= \int dE \cos \theta = \int \frac{x dQ}{4\pi\epsilon_0 (r^2 + x^2)^{3/2}} \\ &= \frac{x}{4\pi\epsilon_0 (r^2 + x^2)^{3/2}} \int dQ = \frac{xQ}{4\pi\epsilon_0 (r^2 + x^2)^{3/2}} \text{ V/m} \end{aligned}$$

.....

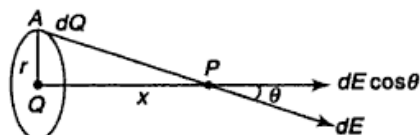


Fig. 2.52 A ring of radius r containing a charge Q

2.45 Three charges, each equal to q , are placed at three corners of a square of side s . Find the electric field at the fourth corner.

Solution

Let the charges be placed along A, B, C (Fig. 2.53).

Now, the electric field at D , $\vec{E}_D = \vec{E}_1 + \vec{E}_2 + \vec{E}_3$

[where \vec{E}_1 = field at D due to A ,
 \vec{E}_2 = field at D due to C , and
 \vec{E}_3 = field at D due to B]

$$= \frac{kq}{s^2} \hat{i} + \frac{kq}{s^2} \hat{j} + \frac{kq}{(\sqrt{2}s)^2} (\hat{i} + \hat{j})$$

$$= \frac{kq}{s^2} \left(1 + \frac{1}{2}\right) \hat{i} + \frac{kq}{s^2} \left(1 + \frac{1}{2}\right) \hat{j}$$

$$= \frac{3kq}{2s^2} (\hat{i} + \hat{j})$$

$$\therefore |\vec{E}_D| = \frac{3}{2} \frac{kq}{s^2} \sqrt{1^2 + 1^2} = \frac{3\sqrt{2}}{2} \frac{kq}{s^2}, \text{ where } K = \frac{1}{4\pi\epsilon_0}$$

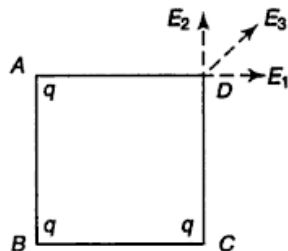


Fig. 2.53 A square of side s having charges q at three corners

2.46 Six similar charges, each of value q are placed at the corners of a regular hexagonal pyramid of side l . Find the resultant electric field strength at the apex due to charges if the diagonal of the base equals slant edge of the pyramid.

Solution

With reference to Fig. 2.54, side of base = l ; slant edge = $2l$.

As charge is same for all points and slant edge is also same hence magnitude of electric field due to each charge is equal to $kq/(2l)^2$ though the directions are different. Solving them into components, we find horizontal components will cancel among themselves.

Resultant electric field = $6 E \cos \theta$

$$= 6 \times \frac{1}{4\pi\epsilon_0} \times \frac{q}{(2l)^2} \times \frac{\sqrt{3}}{2} \quad [\because \theta = 30^\circ]$$

$$= \frac{1}{4\pi\epsilon_0} \times \frac{3\sqrt{3}}{4} \times \frac{q}{l^2}$$

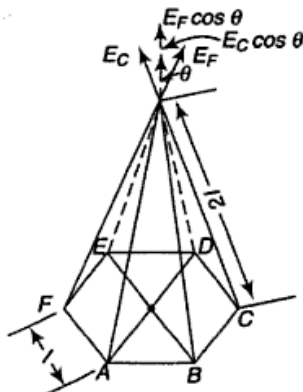


Fig. 2.54 Charges placed at the corners of a hexagonal pyramid

2.47 A $1.0 \mu\text{F}$ parallel plate capacitor with air in dielectric medium is charged to 200 V at steady state. Assuming the distance between the two parallel plates to be 1.0 cm , find

- the electric stress on dielectric
- the electric stress on plate surface and electric flux density

- (iii) the charges on the plate.
 (iv) if the dielectric medium of air is replaced by another dielectric medium of permittivity 4, recalculate the answers for (i), (ii) and (iii).

Solution

(i) $E = \frac{V}{x}$ V/m [E = electric stress on dielectric i.e. field intensity]

$$= \frac{200}{1 \times 10^{-2}} = 20 \text{ kV/m}$$

- (ii) Electric stress on plate surface will also be 20 kV/m while the flux density is given by

$$\begin{aligned}\delta &= \epsilon_0 \times E = 8.854 \times 10^{-12} \times 20 \times 10^3 \\ &= 1.771 \times 10^{-7} \text{ C/sq. m.}\end{aligned}$$

- (iii) $Q = CV$; Q is the charge on the plate
 $= 1 \times 10^{-6} \times 200 = 200 \text{ } \mu\text{C}.$

- (iv) If the air medium is replaced by another medium of permittivity 4, we can obtain the new values of E , δ and Q as follows:

$$\begin{aligned}C_{\text{new}} &= \frac{\epsilon_0 \epsilon_r A}{x} \\ &= \epsilon_r \times \frac{\epsilon_0 A}{x} = \epsilon_r \times 1 \times 10^{-6}\end{aligned}$$

[\because original capacitance of the given capacitor with air on dielectric medium is given as 1 μF .]

$$\therefore C_{\text{new}} = 4 \times 1 \times 10^{-6} = 4 \text{ } \mu\text{F}$$

Also, $E_{\text{new}} = \frac{V}{x} = \frac{200}{1 \times 10^{-2}} = 20 \text{ kV/m}$ [distance x remains same]

$$\begin{aligned}\delta_{\text{new}} &= \epsilon_0 \epsilon_r E = 8.854 \times 10^{-12} \times 4 \times 20 \times 10^3 \\ &= 7.1 \times 10^{-7} \text{ C/m}^2\end{aligned}$$

The new charge accumulation is

$$\begin{aligned}Q_{\text{new}} &= C_{\text{new}} \times V = 4 \times 10^{-6} \times 200 \\ &= 8 \times 10^{-4} \text{ Coulomb.}\end{aligned}$$

.....

2.48 Two capacitors C_1 and C_2 are placed in (i) Series and (ii) Parallel. If $C_1 = 100 \text{ } \mu\text{F}$; $C_2 = 50 \text{ } \mu\text{F}$, find the maximum energy stored when a 220 dc supply is applied across the combination.

Solution

If C is the equivalent capacitance, for series connection of C_1 and C_2 ,

$$C = \frac{C_1 C_2}{C_1 + C_2} = \frac{100 \times 50}{100 + 50} = 33.33 \text{ } \mu\text{F}.$$

\therefore Maximum energy stored is $\frac{1}{2} CV^2$, i.e. $\frac{1}{2} \times 33.333 \times 10^{-6} \times (220)^2$ i.e. 0.807 J.

When the capacitors are in parallel, $C = C_1 + C_2 = 150 \text{ } \mu\text{F}$

∴ Maximum energy stored is

$$\frac{1}{2} \times 150 \times 10^{-6} \times (220)^2 \text{ i.e. } 3.63 \text{ J.}$$

[It may be observed here that capacitor conserves maximum energy when they are in parallel configuration.]

2.49 Find the equivalent capacitance between A and B in Fig. 2.55. Assume the capacitances are equal to each other and having a value of $2 \mu\text{F}$ each.

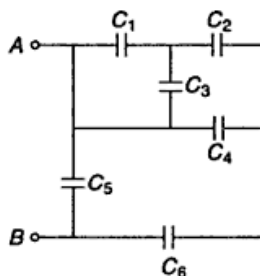


Fig. 2.55 Capacitance configuration of Ex. 2.49

Solution

We can reduce the given circuit as shown in Fig. 2.55(a).

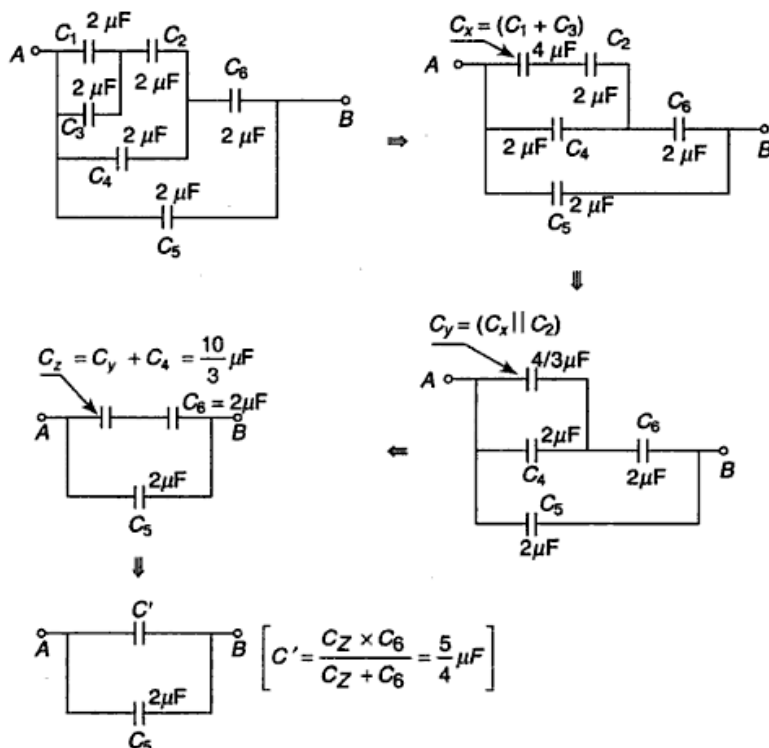


Fig. 2.55a Circuit reduction for Ex. 2.49

Finally we obtain

$$C = C' \parallel C_3 = C' + C_3 = \frac{5}{4} + 2 = \frac{13}{4} \mu\text{F}$$

2.50 In Fig. 2.56, if $C_1 = C_2 = C_3 = C_4 = \dots = C_{12} = 1 \text{ F}$, and $V = 10 \text{ V}$, find the charge supplied by the battery. If the charging current drawn from the battery is 10 A , how much time would the battery take to charge the capacitor cube? What is the energy stored in the capacitances of the cube?

Solution

Let us assume Q be the charge entering terminal x from the battery to the cube. Obviously, capacitance C_1 , C_2 and C_3 would store charges $Q/3$, $Q/3$ and $Q/3$. Since charge (Q) leaves out terminal y hence charge on capacitors C_{10} , C_{11}

and C_{12} must also be $\left(\frac{Q}{3}\right)$ each. On the other

hand since C_3 is connected to C_4 and C_5 at terminal z , hence C_4 and C_5 should have a total charge equal to that stored in C_3 . Hence

we can say since C_3 stores $\left(\frac{Q}{3}\right)$, hence C_4 and C_5 would individually have $\left(\frac{Q}{6}\right)$ each.

Following charging current path in the cube from x to y we find

$$\begin{aligned} V_{xy} &= V_x - V_y = (V_x - V_z) + (V_z - V_p) + (V_p - V_y) \\ &= V_{xz} + V_{zp} + V_{py} = \frac{Q/3}{C} + \frac{Q/6}{C} + \frac{Q/3}{C} \\ &= \frac{5Q}{6C} \quad [\because C_1 = C_2 = C_3 = \dots = C_{12} = C] \end{aligned}$$

or
$$\frac{Q}{C_{eq}} = \frac{5Q}{6C}$$

$$C_{eq} = \frac{6}{5}C = \frac{6}{5}\text{F} \quad [\because C = 1 \text{ F}]$$

Hence charge stored in the cube is

$$Q = C_{eq} \cdot V = \frac{6}{5} \times 10 = 12 \text{ coulomb.}$$

The battery supplies 12 coulomb of electricity. Also $Q = \text{Charging current} \times \text{Time}$.

$$\therefore \text{Time} = \frac{Q}{I_{ch}} = \frac{12}{10} = 1.2 \text{ sec.}$$

Energy stored in the capacitor cube

$$= \frac{1}{2} \frac{Q^2}{C_{eq}} = \frac{(12)^2}{2 \times 6/5} = 60 \text{ J.}$$

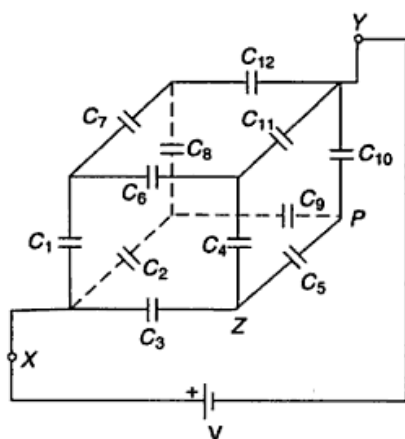


Fig. 2.56 Cube of Ex. 2.50

2.51 Find the amount of heat generated in the circuit shown in Fig. 2.57 after the switch is shifted from position 1 to position 2.

Solution

When the switch is in position 1, the combination has C and C_0 in parallel and C in series for which the equivalent capacitance is

$$C_{eq} = \frac{(C_0 + C)C}{C_0 + 2C}$$

The total charge on the combination is

$$Q = V \times C_{eq} = \frac{VC(C + C_0)}{2C + C_0}$$

The total charge in the three capacitors can be obtained as

$$Q_3 = VC_{eq} = \frac{VC(C + C_0)}{2C + C_0}$$

$$Q_2 = \frac{VC(C + C_0)C_0}{(2C + C_0)(C + C_0)} = \frac{VC C_0}{2C + C_0}$$

$$Q_1 = \frac{VC(C + C_0)C}{(2C + C_0)(C + C_0)} = \frac{VC^2}{2C + C_0}$$

When the switch is in position 2, the charge distinguishes on the three capacitors is

$$Q_3' = \frac{VC^2}{2C + C_0}; Q_2' = Q_2 \text{ and } Q_1' = \frac{VC(C + C_0)}{2C + C_0}$$

Heat produced = loss in stored electrical energy + extra energy drawn from the battery. Since the equivalent capacitance C_{eq} remain unchanged in both the positions of the key, the loss in stored energy is zero.

Hence,

Heat produced = Energy drawn from the battery

$$= V(Q_1' - Q_1)$$

$$= V(Q_3 - Q_3')$$

$$= V \left[\frac{VC(C + C_0)}{2C + C_0} - \frac{VC^2}{2C + C_0} \right]$$

$$= \frac{V^2 C C_0}{2C + C_0}$$

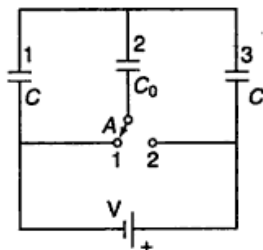


Fig. 2.57 Circuit of Ex. 2.51

2.52 A parallel plate capacitor has plate area of 0.1 m^2 and plate separation 0.015 cm . The dielectric medium between the plates has relative permittivity 3. The capacitors retain a charge of $1.0 \mu\text{C}$ when placed across a dc voltage source. Find the flux density, electric field strength and voltage across the plates. Assume ϵ_0 , the permittivity space as $8.854 \times 10^{-12} \text{ F/m}$.

Solution

Given:

$$A = 0.1 \text{ m}^2; x = 0.015 \text{ cm} = 0.015 \times 10^{-2} \text{ m}$$

$$\epsilon_r = 3; Q = 1.0 \text{ } \mu\text{C}.$$

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

 \therefore for the given parallel plate capacitor,

$$C = \frac{\epsilon_0 \epsilon_r A}{x} = \frac{8.854 \times 10^{-12} \times 3 \times 0.1}{0.015 \times 10^{-2}} \\ = 0.01771 \text{ } \mu\text{F}.$$

Flux density is obtained identical to charge density.

$$\therefore \delta = \frac{Q}{A} = \frac{1.0 \times 10^{-6}}{0.1} = 10 \text{ } \mu\text{C/m}^2.$$

Field strength (E) is obtained as

$$E = \frac{\delta}{\epsilon_0 \epsilon_r} = \frac{10 \times 10^{-6}}{8.854 \times 10^{-12} \times 3} \\ = 37.65 \times 10^4 \text{ V/m}.$$

The p.d. across plates is formed as

$$V = \frac{Q}{C} = \frac{1 \times 10^{-6}}{0.01771 \times 10^{-6}} = 56.47 \text{ V}.$$

.....

2.53 Find the charge that will flow through the battery B when switch S is closed (Fig. 2.58).

SolutionFirst we consider S is open. Equivalent capacitance across $X - Y$ is

$$C_{X-Y} = \frac{C \times 2C}{C + 2C} = \frac{2}{3} C$$

Hence Q_1 (charge retained by C_{X-Y} when S is open)


$$= C_{X-Y} \cdot V = \frac{2}{3} C \cdot V \text{ coulomb}$$

Next we consider S is closed. Equivalent capacitance C'_{X-Y} across XY is

$$C'_{X-Y} = 2C$$

 $\therefore Q_2$ (charge retained by C'_{X-Y} when S is closed)

$$= C'_{X-Y} \times V = 2CV.$$

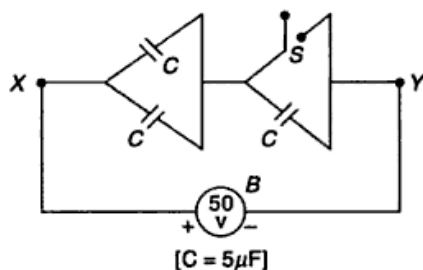Hence we can find charge flowing through battery as $|Q_1 - Q_2|$ **Fig. 2.58** Circuit of Ex. 2.53

This becomes $|Q_1 - Q_2| = \frac{2C}{3} \cdot V = 2CV$

$$= \frac{4}{3} CV = \frac{4}{3} \times 5 \times 10^{-6} \times 50 = 333.33 \mu\text{C}.$$

Thus 333.33 μC of charge would pass through the battery upon switching S.

2.54 A $20\mu\text{F}$ capacitor is charged to 100 V and then discharged through a resistor of $10\text{ k}\Omega$. Find (i) initial value of current, (ii) value of current when $t =$ time constant, and (iii) rate at which current begins to decrease.

Solution

- (i) As soon as the capacitor is switched to the discharging charging circuit having a series resistance $10\text{ k}\Omega$, the initial value of discharging current would be

$$I = \frac{100}{10^4} = 0.01\text{ A}$$

- (ii) While discharging

$$i = Ie^{-t/RC};$$

at $t =$ time constant (RC),

$$i = Ie^{-t/t} = I \times \frac{1}{e}.$$

Here, $i = 0.01 \times \frac{1}{e} = 0.00368\text{ A}$

- (iii) Normally the time constant is RC in the discharging circuit and hence $RC = 10^4 \times 20 \times 10^{-6} = 0.2\text{ sec}.$

$$i = I \times e^{-t/RC} = 0.01 \times e^{-\frac{t}{0.2}} \\ = 0.01 e^{-5t}$$

$$\therefore \frac{di}{dt} \text{ (= rate of discharging)} \\ = 0.01(-5)e^{-5t} = -0.05e^{-5t}\text{ A/s.}$$

2.55 Two metal plates form a parallel plate capacitor with an in-between metal plate of the same material. There are two dielectric medium K_1 and K_2 having relative permittivity ϵ_1 and ϵ_2 respectively as shown in figure (Fig. 2.59). If the metal plate is removed find the work done in slowly removing the plate when a p.d. of (V) volts is applied across the capacitors.

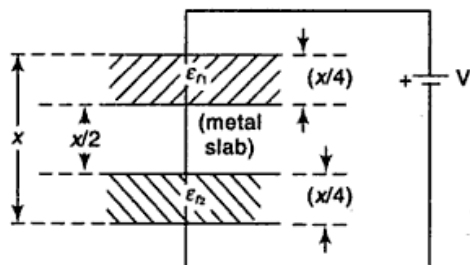


Fig. 2.59 A parallel plate capacitor (Ex. 2.55)

Solution

From the given (Fig. 2.59) it is evident that the capacitor consists of two series capacitors C_1 and C_2 when C_1 is formed with ϵ_1 while C_2 is formed with ϵ_2 .

$$\therefore C_1 = \frac{\epsilon_0 \epsilon_1 A}{(x/4)}; \quad C_2 = \frac{\epsilon_0 \epsilon_2 A}{(x/4)}$$

$$\begin{aligned} \text{and } C_{eq} &= \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = \left(\frac{x}{4\epsilon_0 \epsilon_1 A} + \frac{x}{4\epsilon_0 \epsilon_2 A} \right)^{-1} \\ &= \frac{4\epsilon_0 A}{x} \left[\frac{\epsilon_1 \times \epsilon_2}{\epsilon_1 + \epsilon_2} \right] \end{aligned}$$

$$\therefore \text{Energy stored } (E_1) = \frac{1}{2} C_{eq} V^2 = \frac{1}{2} \times \frac{4\epsilon_0 A}{x} \left[\frac{\epsilon_1 \times \epsilon_2}{\epsilon_1 + \epsilon_2} \right] V^2$$

When the metal slab is removed, there are now three capacitors formed, the first one is C_1 as it was, the second one is with dielectric medium air C_A (as the metal slab is removed, the space between ϵ_1 and ϵ_2 is now air) and the third one is C_2 as it was and now, $C_A =$

$$\frac{\epsilon_0 A}{x/2} = \frac{2\epsilon_0 A}{x}$$

$$\begin{aligned} \therefore C'_{eq} &= \left(\frac{1}{C_1} + \frac{1}{C_A} + \frac{1}{C_2} \right)^{-1} \text{ i.e., } \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_A} \right)^{-1} \\ &= \left(\frac{x}{4\epsilon_0 \epsilon_1 A} + \frac{x}{4\epsilon_0 \epsilon_2 A} + \frac{x}{2\epsilon_0 A} \right)^{-1} \\ &= \frac{4\epsilon_0 A}{x} \left[\frac{1}{\epsilon_1} + \frac{1}{\epsilon_2} + 2 \right]^{-1} \\ &= \frac{4\epsilon_0 A}{x} \left[\frac{\epsilon_1 + \epsilon_2 + 2\epsilon_1 \epsilon_2}{\epsilon_1 \epsilon_2} \right]^{-1} \\ &= \frac{4\epsilon_0 A}{x} \left[\frac{\epsilon_1 \epsilon_2}{\epsilon_1 + \epsilon_2 + 2\epsilon_1 \epsilon_2} \right]^{-1} \end{aligned}$$

$$\begin{aligned} \therefore \text{Energy stored } (E_2) &= \frac{1}{2} C'_{eq} V^2 \\ &= \frac{1}{2} \times \frac{4\epsilon_0 A}{x} \left[\frac{\epsilon_1 \epsilon_2}{\epsilon_1 + \epsilon_2 + 2\epsilon_1 \epsilon_2} \right] V^2 \end{aligned}$$

Since work done (ΔE) is given by ($\Delta E = E_1 - E_2$), it represents the work done to remove the metal slab.

$$\begin{aligned} \therefore \Delta E &= E_1 - E_2 = \frac{1}{2} V^2 \times \frac{4\epsilon_0 A}{x} \left[\frac{\epsilon_1 \epsilon_2}{\epsilon_1 + \epsilon_2} - \frac{\epsilon_1 \epsilon_2}{\epsilon_1 + \epsilon_2 + 2\epsilon_1 \epsilon_2} \right] \\ &= V^2 \times \frac{2\epsilon_0 A \epsilon_1 \epsilon_2}{x} \left[\frac{1}{\epsilon_1 + \epsilon_2} - \frac{1}{\epsilon_1 + \epsilon_2 + 2\epsilon_1 \epsilon_2} \right] \end{aligned}$$

$$\begin{aligned}
 &= V^2 \times \frac{2 \epsilon_0 A \epsilon_1 \epsilon_2}{x} \left[\frac{2 \epsilon_1 \epsilon_2}{(\epsilon_1 + \epsilon_2)(\epsilon_1 + \epsilon_2 + 2 \epsilon_1 \epsilon_2)} \right] \\
 &= \frac{4 \epsilon_0 A V^2 \epsilon_1^2 \epsilon_2^2}{x (\epsilon_1 + \epsilon_2)(\epsilon_1 + \epsilon_2 + 2 \epsilon_1 \epsilon_2)} \text{ Joules.}
 \end{aligned}$$

This is the work done in removing the metal slab from the capacitor.

2.56. Three delta connected capacitors are set to form a unit as shown in Fig. 2.60. It is required to transform the delta unit to equivalent star. Find these star capacitances for equal capacitances between similar terminals in both the connections.

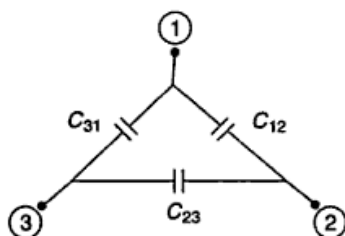


Fig. 2.60 Delta connected capacitors (Ex. 2.56)

\Rightarrow

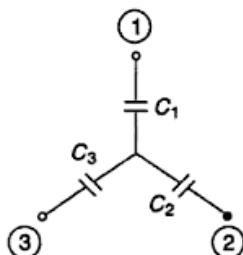


Fig. 2.60a Equivalent star connection of delta connected capacitors in Ex. 2.56

Solution

Figure 2.60a represent the equivalent star capacitances provided net capacitances between terminals ① - ②, ② - ③, ③ - ① remain same for both the configurations. Capacitances

between ① and ② in star connection is $\left(\frac{C_1 C_2}{C_1 + C_2} \right)$ while that between ① and ② in delta

connection is $\left(C_{12} + \frac{C_{23} C_{31}}{C_{23} + C_{31}} \right)$.

For equal capacitance between similar terminals,

$$\frac{C_1 C_2}{C_1 + C_2} = \frac{C_{23} C_{31}}{C_{23} + C_{31}} + C_{12} = \frac{C_{23} C_{31} + C_{12} C_{23} + C_{31} C_{12}}{C_{23} + C_{31}}$$

$$\text{or} \quad \frac{C_1 + C_2}{C_1 C_2} = \frac{C_{23} + C_{31}}{C_{23} C_{31} + C_{12} C_{23} + C_{31} C_{12}} = \frac{C_{23} + C_{31}}{\Delta} \quad (i)$$

where $\Delta = C_{12} C_{31} + C_{23} C_{31} + C_{12} C_{23}$

Similarly, capacitance between ② and ③ in star connection is $\left(\frac{C_2 C_3}{C_2 + C_3} \right)$ while that in delta connection is

$$\frac{C_{31} C_{12}}{C_{31} + C_{12}} + C_{23}$$

By the same reasoning,

$$\frac{C_2 C_3}{C_2 + C_3} = C_{23} + \frac{C_{31} C_{12}}{C_{31} + C_{12}}$$

$$\text{or} \quad \frac{C_2 + C_3}{C_2 C_3} = \frac{C_{31} + C_{12}}{\Delta} \quad (\text{ii})$$

Also, capacitance between ③ and ① in star connection is $\frac{C_3 C_1}{C_3 + C_1}$ and that between ③

and ① in delta connection is $\frac{C_{12} C_{23}}{C_{12} + C_{23}} + C_{31}$.

$$\therefore \frac{C_3 C_1}{C_3 + C_1} = \frac{C_{12} C_{23}}{C_{12} + C_{23}} + C_{31}, \text{ we can write}$$

$$\frac{C_3 + C_1}{C_3 C_1} = \frac{C_{12} + C_{23}}{\Delta} \quad (\text{iii})$$

Adding (i) and (ii) we have

$$\frac{C_1 + C_2}{C_1 C_2} + \frac{C_2 + C_3}{C_2 C_3} = \frac{C_{23} + C_{31}}{\Delta} + \frac{C_{31} + C_{12}}{\Delta}$$

$$\text{or,} \quad \frac{C_1 C_3 + C_2 C_3 + C_1 C_2 + C_1 C_3}{C_1 C_2 C_3} = \frac{C_{23} + C_{31} + C_{31} + C_{12}}{\Delta} \quad (\text{iv})$$

Subtracting (iii) from (iv) we have

$$\frac{C_1 C_3 + C_2 C_3 + C_1 C_2 + C_1 C_3 - C_2 C_3 - C_2 C_1}{C_1 C_2 C_3}$$

$$= \frac{C_{23} + C_{31} + C_{31} + C_{12} - C_{12} - C_{23}}{\Delta}$$

$$\text{or} \quad \frac{2 C_1 C_3}{C_1 C_2 C_3} = \frac{2 C_{31}}{\Delta}$$

$$\text{or} \quad \frac{1}{C_2} = \frac{C_{31}}{\Delta}, \quad C_2 = \frac{\Delta}{C_{31}}$$

$$\therefore C_2 = \frac{C_{12} C_{31} + C_{23} C_{12} + C_{31} C_{23}}{C_{31}} \quad (\text{iva})$$

$$= C_{12} + C_{23} + \frac{C_{23} C_{12}}{C_{31}} \quad (\text{ivb})$$

Similarly,

$$C_1 = C_{31} + C_{12} + \frac{C_{31} C_{12}}{C_{23}} \quad (\text{ivc})$$

$$\text{and} \quad C_3 = C_{23} + C_{31} + \frac{C_{23} C_{31}}{C_{12}} \quad (\text{ivd})$$

2.57. Three star connected capacitances C_1 , C_2 and C_3 are to be transformed to delta. Show that for equal capacitances between similar terminals in both connections,

$$C_{12} = \frac{C_1 C_2}{C_1 + C_2 + C_3}$$

$$C_{23} = \frac{C_2 C_3}{C_1 + C_2 + C_3}$$

$$C_{31} = \frac{C_3 C_1}{C_1 + C_2 + C_3}$$

Solution

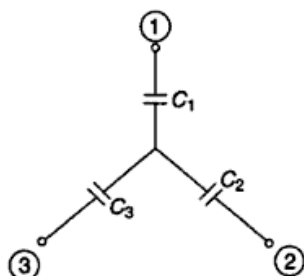


Fig. 2.61 Star connected capacitors (Ex. 2.57)

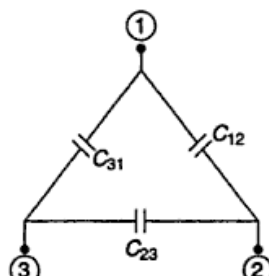


Fig. 2.61a Equivalent delta connected capacitors of Ex. 2.57

With reference to Fig. 2.61 and Fig. 2.61a we have found out in the previous example that for capacitance between identical terminals being same for both star and delta, delta capacitances can be successfully converted to star where

$$\begin{aligned} C_1 &= C_{12} + C_{31} + \frac{C_{12} C_{31}}{C_{23}} = \frac{C_{12} C_{23} + C_{23} C_{31} + C_{31} C_{12}}{C_{23}} \\ &= \frac{\Delta}{C_{23}} \end{aligned} \quad \text{(i)}$$

$$C_2 = C_{23} + C_{12} + \frac{C_{23} C_{12}}{C_{31}} = \frac{\Delta}{C_{31}} \quad \text{(ii)}$$

$$C_3 = C_{31} + C_{23} + \frac{C_{31} C_{23}}{C_{12}} = \frac{\Delta}{C_{12}} \quad \text{(iii)}$$

Multiplying equations (i) and (ii), (iii) and (iv) and (v) and (vi), we have

$$C_1 C_2 = \frac{\Delta^2}{C_{23} C_{31}} \quad \text{(iv)}$$

$$C_2 C_3 = \frac{\Delta^2}{C_{31} C_{12}} \quad \text{(v)}$$

$$C_3 C_1 = \frac{\Delta^2}{C_{12} C_{23}} \quad \text{(vi)}$$

Inverting and adding equations (iv), (v) and (vi),

$$\frac{1}{C_1 C_2} + \frac{1}{C_2 C_3} + \frac{1}{C_3 C_1} = \frac{C_{12} C_{23} + C_{31} C_{12} + C_{23} C_{31}}{\Delta^2}$$

or
$$\frac{C_3 + C_1 + C_2}{C_1 C_2 C_3} = \frac{\Delta}{\Delta^2} = \frac{1}{\Delta}$$

or
$$\frac{C_1 C_2 C_3}{C_1 + C_2 + C_3} = \Delta$$

or
$$\frac{\Delta}{C_3} = \frac{C_1 C_2}{C_1 + C_2 + C_3} \quad (\text{vii})$$

However, we have proved earlier in the preceding example

$$\begin{aligned} C_3 &= C_{23} + C_{31} + \frac{C_{23} C_{31}}{C_{12}} = \frac{C_{23} C_{12} + C_{31} C_{12} + C_{23} C_{31}}{C_{12}} \\ &= \frac{\Delta}{C_{12}} \end{aligned}$$

∴ From equation (iii), using $C_3 = \frac{\Delta}{C_{12}}$, we can write

$$\frac{\Delta}{C_3} = C_{12} = \frac{C_1 C_2}{C_1 + C_2 + C_3}$$

Similarly,
$$C_{23} = \frac{C_2 C_3}{C_1 + C_2 + C_3}$$

and
$$C_{31} = \frac{C_3 C_1}{C_1 + C_2 + C_3}$$

2.58 In the circuit of Fig. 2.62, switch S is switched on at $t = 0$ and kept at on position for long time. At steady state, the switch is suddenly opened. Instantaneously, the dielectric mediums of the capacitors are replaced by another dielectric medium having dielectric constant of 0.5. Find the ratio of total electrostatic energy in both the capacitors before and after opening of the switch at steady state.

Solution

Condition 1: Switch closed, steady state prevails. Both the capacitors C_1 and C_2 are at same potential and the total electrostatic energy of both C_1 and C_2 are given by

$$W_1 = \frac{1}{2} CV^2 + \frac{1}{2} CV^2 = CV^2.$$

Condition 2: Switch opened and dielectric medium replaced.

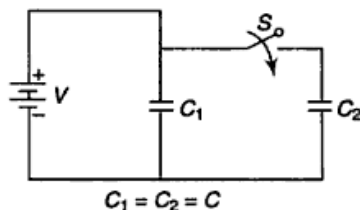


Fig. 2.62 Circuit of Ex. 2.58

This time the capacitance of each of the capacitors becomes $0.5C$. Let v be the new potential of C_2 and C_2 is isolated as the switch is already opened. However it will retain the same charge before and after switching and hence we can write

$$\begin{aligned} CV & \text{ (charge before } S \text{ is opened)} \\ &= 0.5 CV' \text{ (charge after } S \text{ is opened)} \end{aligned}$$

$$\text{i.e.,} \quad V' = 2V$$

The new electrostatic energy of the system is now the summation of electrostatic energies of each of the capacitors.

$$\begin{aligned} \therefore W' &= \frac{1}{2} \cdot (0.5C) \cdot V^2 + \frac{1}{2} \cdot (0.5C) \cdot V'^2 \\ &= \frac{1}{2} \times 0.5C \times V^2 + \frac{1}{2} \times 0.5C \times (2V)^2 \\ &= 1.25 CV^2 \end{aligned}$$

$$\therefore \frac{W}{W'} = \frac{CV^2}{1.25 CV^2} = \frac{1}{1.25}$$

Hence the required ratio is 1 : 1.25.

2.59 A $8 \mu\text{F}$ capacitor is connected in series with a $0.5 \text{ M}\Omega$ resistor across a 200 V dc supply. Calculate (i) the time constant during charging of the capacitor, (ii) the initial charging current, (iii) the time taken for the p.d. across the capacitor to grow to 160 V and (iv) the current and the p.d. across the capacitor in 4 sec after it is connected to the supply.

Solution

$$(i) \text{ Time constant} = RC = 0.5 \times 10^6 \times 8 \times 10^{-6} = 4.0 \text{ sec.}$$

$$(ii) I = \frac{V}{R} = \frac{200}{0.5 \times 10^6} = 0.4 \text{ mA}$$

[capacitor acts as short circuit as soon as voltage is applied and hence initial charging current is (V/R)]

$$(iii) \therefore v_C = V(1 - e^{-t/RC}), \quad [\text{refer text}]$$

$$\text{Here,} \quad 160 = 200(1 - e^{-t/4})$$

$$\text{i.e.,} \quad \frac{160}{200} = 1 - e^{-t/4} \quad \text{or,} \quad 0.2 = e^{-t/4}$$

$$\text{or,} \quad \log_{10} 0.2 = -\frac{t}{4} \cdot \log_{10} e$$

$$\therefore t = 6.42 \text{ sec.}$$

$$\begin{aligned} (iv) \quad i &= Ie^{-t/RC} \\ &= (0.4 \times 10^{-3})e^{-t/4} \\ &= (0.4 \times 10^{-3})2.718 \\ &= 0.147 \text{ mA} \\ v &= V(1 - e^{-t/RC}) \\ &= 200(1 - e^{-4/4}) \\ &= 126.40 \text{ V.} \end{aligned}$$

■ EXERCISES ■

1. State and explain Coulomb's law in Electrostatics and hence define "Coulomb", the unit for electric charge.
2. What is permittivity? What do you mean by relative permittivity of a medium? Why it does not have any unit?
3. Define electric potential and potential difference with their units. Find an expression for potential at a point within an electric field. What is equipotential surface?
4. What is meant by electric field intensity? Discuss the various factors upon which it depends.
5. Find the expression of electric field intensity and electric potential of an isolated point charge in vector form.
6. Define potential gradient. What is its unit? Why do we say electric field intensity and potential gradient both are expressed in volt/m?
7. Derive an expression of potential energy in an electric field.
8. Find a relationship between electric field strength and electric potential.
9. State Gauss' Law and derive from Coulomb's law.
10. What do you mean by electric dipole? Obtain an expression of electric field and potential due to a dipole at an axial point.
11. (a) Define electric capacitance and derive an expression for the capacitance of a parallel plate capacitor.
(b) Discuss the various factors upon which the value of capacitance of parallel plate capacitor depends.
12. State the factors on which the capacitance of a condenser would depend.
13. Derive expression for the equivalent capacitance for a number of capacitors connected in (i) series (ii) parallel.
14. Derive the expression of capacitance of a parallel plate capacitor with (i) uniform dielectric medium (ii) compound dielectric medium.
15. How would you find capacitance of multiplate capacitors?
16. Find the capacitors of an isolated sphere.
17. Derive the expression to find capacitance of concentric spheres.
18. How do you find the capacitance of a parallel plate capacitor if a metal plate (uncharged) is introduced within the parallel plates?
19. Derive an expression for the energy stored in a condenser charged to a potential.
20. Explain charging and discharging of a capacitor alongwith necessary derivation when the capacitor is connected across a dc voltage source and when discharging from steady state with resistance in series in both the cases.
21. What is the potential at $x = 0$ due to these charges? $x =$ distance in m.

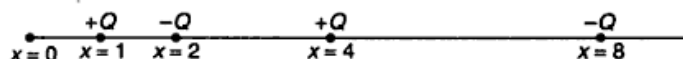


Fig. 2.63

$$\left(\text{Ans: } V = \frac{Q}{6\pi\epsilon_0} \right)$$

[Hint: Potential V_1 at $x = 0$ due to +ve charges is given by

$$\begin{aligned} V_1 &= \frac{Q}{4\pi\epsilon_0(1)} + \frac{Q}{4\pi\epsilon_0(4)} + \frac{Q}{4\pi\epsilon_0(16)} + \dots \\ &= \frac{Q}{4\pi\epsilon_0} \left(1 + \frac{1}{4} + \frac{1}{16} + \dots \right) = \frac{Q}{4\pi\epsilon_0} \left[\frac{1}{1 - 1/4} \right] \\ &= \frac{Q}{3\pi\epsilon_0} \end{aligned}$$

Potential V_2 at $x = 0$ due to -ve charges is given by

$$\begin{aligned} V_2 &= \frac{-Q}{4\pi\epsilon_0(2)} + \frac{-Q}{4\pi\epsilon_0(8)} + \frac{-Q}{4\pi\epsilon_0(32)} + \dots \\ &= \frac{-Q}{4\pi\epsilon_0} \left[1 + \frac{1}{4} + \frac{1}{16} + \dots \right] = \frac{-Q}{6\pi\epsilon_0} \end{aligned}$$

$$\therefore V = V_1 - V_2 = \frac{Q}{6\pi\epsilon_0}$$

22. Find the potential and field intensity at $x = 0$ due to these set of charges; x represents the distance from origin in x -axis. Q is magnitude of charge.

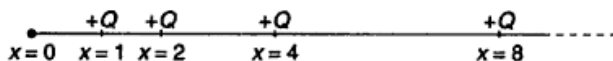


Fig. 2.64

$$\left(\text{Ans: } V = \frac{Q}{2\pi\epsilon_0}; \frac{Q}{3\pi\epsilon_0} \right)$$

[Hint:

$$V = \frac{Q}{4\pi\epsilon_0} \left[1 + \frac{1}{2} + \frac{1}{4} + \dots \right] = \frac{Q}{4\pi\epsilon_0} \times 2 = \frac{Q}{2\pi\epsilon_0}$$

$$E = \frac{Q}{4\pi\epsilon_0 x^2} = \frac{Q}{4\pi\epsilon_0} \left[1 + \frac{1}{2^2} + \frac{1}{4^2} + \dots \right]$$

$$= \frac{Q}{4\pi\epsilon_0} \left(1 + \frac{1}{4} + \frac{1}{16} + \dots \right) = \frac{4Q}{3} \times \frac{1}{4\pi\epsilon_0} = \frac{Q}{3\pi\epsilon_0}$$

23. Three point charges $4q$, Q and q are placed in a straight line of length l at point of distance 0 , $l/2$ and l from origin respectively. The net force on charge q is zero. What is the value of Q ?

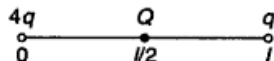


Fig. 2.65

$$[\text{Ans: } Q = -q]$$

[Hint: With ref. to Fig. 2.65, the net force on Q is zero when

$$\frac{4q \times q}{4\pi\epsilon_0 \times (l)^2} + \frac{Q \times q}{4\pi\epsilon_0 (l/2)^2} = 0$$

i.e. $4q^2 + 4Qq = 0$

i.e. $Q = -q]$

24. Eight charged drops of a fluid carry a charge of $10^{-4} \mu\text{C}$ each. Each drop has a diameter of 2 mm. If they merge together to form a single drop, find the potential of the merged big drop. (Ans: 3.6 kV)

[Hint: Total charge of 8 drops = $8 \times 10^{-4} \mu\text{C}$ ($=q$)

Potential due to a charge ' q ' is given by.

$$V = \frac{1}{4\pi\epsilon_0} \times \frac{q}{R}, \text{ where } R \text{ is the radius of the big drop and } q \text{ is its charge.}$$

Since the single big drop is equivalent to eight drops, assuming all drops to be perfect spheres,

$$8 \times \frac{4}{3} \pi r^3 \times \rho = \frac{4}{3} \pi R^3 \times \rho,$$

ρ being the density of the fluid and $\frac{4}{3} \pi r^3$ is the volume of each small drop.

$$\therefore \text{ We have } 8r^3 = R^3$$

$$\text{or } R = 2r.$$

$$\therefore V = \frac{1}{4\pi \times 8.854 \times 10^{-12}} \times \frac{8 \times 10^{-4} \times 10^{-6}}{2 \times 10^{-3}} = 3600 \text{ V}$$

25. Show that when a dielectric slab of thickness t and permittivity ϵ_r is inserted between two fixed charges Q_1 and Q_2 , the force of repulsion between them is given by

$$F = \frac{1}{4\pi\epsilon_0} \cdot \frac{Q_1 Q_2}{(d - t + \sqrt{\epsilon_r t})^2}$$

and hence find the dielectric constant of the slab, if on interposing another slab of same material of thickness $(d/2)$ the force of repulsion reduces in the ratio $(9/4)$. Assume the distance between the fixed charges to be d .

(Ans: $\epsilon_r = 4$)

$$[\text{Hint: } F = \frac{1}{4\pi\epsilon_0 \epsilon_r} \times \frac{Q_1 Q_2}{d^2}]$$

Let us assume that when the same two charges are placed d' apart in air, same force of repulsion arises between them.

$$\therefore F = \frac{1}{4\pi\epsilon_0} \times \frac{Q_1 Q_2}{d'^2}$$

Then, $\epsilon_r d^2 = d'^2$ i.e., $d' = \sqrt{\epsilon_r} \cdot d$

Then, d of medium is equivalent to d' of air

i.e., $\sqrt{\epsilon_r} \cdot d$ in air.

\therefore Effective air separation is $(d - t + \sqrt{\epsilon_r} \cdot t)$

$$F = \frac{1}{4\pi\epsilon_o} \times \frac{Q_1 Q_2}{(d - t + \sqrt{\epsilon_r} \cdot t)^2}$$

$$\text{Substituting } t = d/2, F' = \frac{1}{4\pi\epsilon_o} \times \frac{Q_1 Q_2}{\left(d - \frac{d}{2} + \sqrt{\epsilon_r} \cdot \frac{d}{2}\right)^2}$$

$$= \frac{1}{4\pi\epsilon_o} \times \frac{4Q_1 Q_2}{(1 + \sqrt{\epsilon_r})^2 d^2}$$

$$\text{Force in air is } F = \frac{1}{4\pi\epsilon_o} \times \frac{Q_1 Q_2}{d^2}$$

$$\therefore \quad F'/F = \frac{4}{(1 + \sqrt{\epsilon_r})^2} \quad \text{But it is given } F'/F = 4/9$$

$$\therefore \quad \frac{4}{(1 + \sqrt{\epsilon_r})^2} = \frac{4}{9} \therefore \sqrt{\epsilon_r} = 2$$

26. If the capacitance between two successive plates is $0.5C$ (Fig. 2.66), find the capacitance of the equivalent system between points P and Q .

(Ans: $1.5C$)

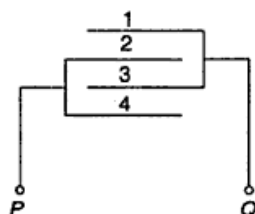


Fig. 2.66

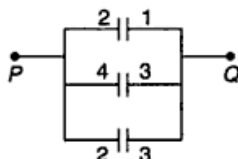


Fig. 2.66a

[Hint: The four plates form three capacitors (Fig. 2.66a)]

$$\therefore \quad C_{eq} = 0.5C + 0.5C + 0.5C = 1.5C$$

27. Two capacitors are once connected in parallel and then in series. If the equivalent capacitance in the two cases be $10F$ and $5F$ respectively, find the capacitance of each of the capacitors.

$$[\text{Hint: } C_1 + C_2 = 10; \frac{C_1 C_2}{C_1 + C_2} = 2.1]$$

Solving, $C_1 = 7F$, $C_2 = 3F$

28. Two dielectrics of equal size are introduced inside a parallel plate capacitor as shown in Fig. 2.67. How does the effective capacitance change?

(Ans: Increase by $\frac{\epsilon_1 + \epsilon_2}{2}$)

[Hint: With introduction of two dielectrics two parallel capacitors are formed.]

$$C_{eq} = \frac{\epsilon_o \epsilon_1 (A/2)}{d} + \frac{\epsilon_o \epsilon_2 (A/2)}{d} = \frac{\epsilon_o A}{d} \left(\frac{\epsilon_1 + \epsilon_2}{2} \right)$$

while without these dielectrics it was $\frac{\epsilon_o A}{d}$, assuming the area of plates to be A .

$$\therefore \text{Ratio} = \frac{\frac{\epsilon_o A}{d} \left(\frac{\epsilon_1 + \epsilon_2}{2} \right)}{\frac{\epsilon_o A}{d}} = \frac{\epsilon_1 + \epsilon_2}{2}$$

$\therefore \epsilon_1$ and ϵ_2 are both more than 1, hence the new capacitance is increased by $\frac{\epsilon_1 + \epsilon_2}{2}$ times].

29. Find the charge drawn from the battery at steady state when K is closed. Assume $C_1 = C_2 = C$.

(Fig. 2.68) (Ans: $\frac{1}{2} CV$)

[Hint: K open:

$$Q = C_{eq} \cdot V = \frac{C}{2} \cdot V$$

Next K closed; C_2 gets shorted. Charge is now drawn by C_1 only.

$$Q' = CV$$

$$Q' - Q = \frac{1}{2} CV$$

This is the amount of charge drawn with K closed].

30. If each of the capacitances is C , find the equivalent capacitance between A and B (Fig. 2.69).

(Ans: $2C$)

[Hint: The given circuit can be redrawn as shown below:

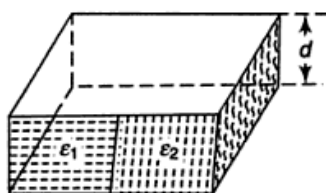


Fig. 2.67

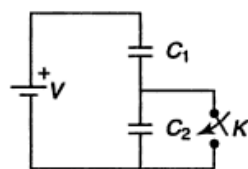


Fig. 2.68

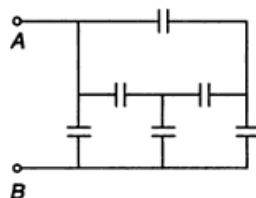


Fig. 2.69

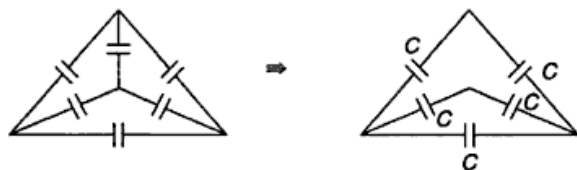


Fig. 2.69a

One capacitor may be deleted from star as no charge will flow through it since p.d. will be same across it. This simplifies the figure and we find net capacitance $2C$. The problem can also be solved using ($Y - \Delta$) conversion].

31. A capacitor is formed by two parallel metal plates of area 5 cm^2 separated by a distance of 1.5 cm in air medium. It is then connected to a 1000 V dc supply. A flat sheet of a dielectric material is now introduced in the capacitor and pasted to the +ve plate. The sheet has a permittivity of 3 and thickness of 0.5 cm . What is the new capacitance? What is the electric stress developed in air? (Ans: $37.84 \times 10^{-14} \text{ F}$; 85.5 V/m)

[Hint: Ref. Fig. 2.70]

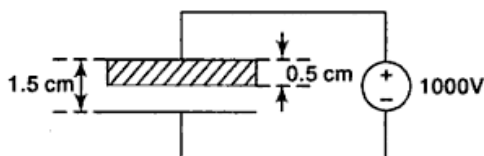


Fig. 2.70

$$\begin{aligned}
 C_{\text{new}} &= \frac{\epsilon_o A}{\frac{d_1}{\epsilon_1} + \frac{d_2}{\epsilon_2}} \text{ Farad} \\
 &= \frac{\epsilon_o \times 5 \times 10^{-4}}{\frac{0.5 \times 10^{-2}}{3} + \frac{1 \times 10^{-2}}{1}} \\
 &= \epsilon_o \times 4.274 \times 10^{-2} \\
 &= 37.84 \times 10^{-14} \text{ F}
 \end{aligned}$$

\therefore

$$Q = CV, \text{ here}$$

$$Q = 37.84 \times 10^{-14} \times 1000 = 37.84 \times 10^{-11} \text{ C}$$

$$\delta = \frac{Q}{A} = \frac{37.84 \times 10^{-11}}{5 \times 10^{-4}} = 7.57 \times 10^{-7} \text{ C/m}^2$$

\therefore

$$E = \frac{\delta}{\epsilon_o} = \frac{7.57 \times 10^{-7}}{8.854 \times 10^{-12}} = 85.5 \text{ V/m}.$$

32. Two plates of a capacitor of capacitance C are given charges q_1 and q_2 . The capacitor is connected across a resistance r (Fig. 2.71). Find the charges on the plate after time t .

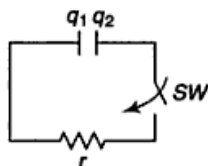


Fig. 2.71

$$\left(\text{Ans: } Q(\text{left plate}) = \frac{q_1 + q_2}{2} + \left(\frac{q_1 - q_2}{2} \right) \cdot e^{-t/RC} \right.$$

$$\left. Q(\text{right plate}) = \frac{q_1 + q_2}{2} - \left(\frac{q_1 - q_2}{2} \right) \cdot e^{-t/RC} \right)$$

[Hint: Ref. Fig. 2.71a for charge distribution diagram before closing of switch.]

Initially the p.d. is $\frac{q_1 - q_2}{2C}$. During discharging, the charges on the outer surfaces would not change as the p.d. is independent of charges in the outer system. Charge on the inner

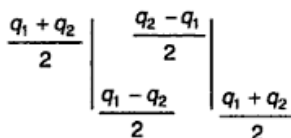


Fig. 2.71a

surface decreases as $Q = \left(\frac{q_1 - q_2}{2} \right) \cdot e^{-t/RC}$

$$\begin{aligned} \therefore Q(\text{left plate}) &= C \cdot \frac{q_1 - q_2}{2C} + \frac{q_1 - q_2}{2} \cdot e^{-t/RC} \\ &= \frac{q_1 - q_2}{2} + \frac{q_1 - q_2}{2} \cdot e^{-t/RC} \end{aligned}$$

Similarly for right plate it is $\frac{q_1 + q_2}{2} - \frac{q_1 - q_2}{2} \cdot e^{-t/RC}$

33. A dc voltage of 100 V is connected to a capacitor of 0.1F. The source is removed when steady state is reached and the charged capacitor is connected to a second uncharged capacitor. If the charge is equally distributed on these two capacitors, find the total energy stored in these two capacitors. Find the ratio of final to initial energy. (Ans: 250 J; 1 : 2)

[Hint: Initial stored energy $E = \frac{1}{2} \times 0.1 \times 100^2 = 500$ J. Removing the voltage source this capacitor is connected to another 0.01F and charge distribution is same for both. Hence final voltage is 100/2, i.e. 50 V.]

$$\begin{aligned} \text{Final stored energy} &= \frac{1}{2} \times 0.1 \times 50^2 + \frac{1}{2} \times 0.1 \times 50^2 \\ &= 250 \text{ J.} \end{aligned}$$

\therefore Ratio of energy = 1 : 2.]

34. A 6 μF capacitor is charged to 100 V and another 10 μF capacitor is charged to 200 V. They are then connected across each other. Find the p.d. across them and calculate the heat produced. (Ans: 162.5 V; 0.0188 J)

[Hint: $q_1 = C_1 V_1 = 6 \times 10^{-6} \times 100 = 600 \mu\text{C}$

$q_2 = C_2 V_2 = 10 \times 10^{-6} \times 200 = 2000 \mu\text{C}$

After connecting one across the other, the common p.d. is V across them.

$\therefore V = \frac{q_1 + q_2}{C_1 + C_2} = \frac{q'_1 + q'_2}{C_1 + C_2} = \frac{q'_1}{C_1} = \frac{q'_2}{C_2}$; q'_1 and q'_2 are new charge distributions

i.e. $V = \frac{600 + 2000}{6 + 10} = 162.5 \text{ V}$

$$W_1 = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 = \frac{1}{2} \times 6 \times 10^{-6} \times 100^2 + \frac{1}{2} \times 10 \times 10^{-6} \times 200^2 = 23 \times 10^{-2} \text{ J}$$

$$W_2 = \frac{1}{2} (C_1 + C_2) V^2 = \frac{1}{2} (16) \times 10^{-6} \times 162.5^2 = 21.12 \times 10^{-2} \text{ J}$$

35. A parallel plate capacitor has 30 plates each of 0.1 m^2 area, the separation between them being 0.2 cm . If the dielectric constant is 3, find the capacitance and the capacitive energy stored if the capacitance stores $10 \mu\text{C}$.

(Ans: $385.15 \times 10^{-10} \text{ F}$; 0.1298 J)

[Hint: $C = \frac{(n-1)\epsilon_0\epsilon_r A}{d}$

$$= \frac{(30-1) \times 8.854 \times 10^{-12} \times 0.1 \times 3}{0.2 \times 10^{-2}} = 385.15 \times 10^{-10} \text{ F}$$

$$\text{Energy stored} = \frac{Q^2}{2C} = \frac{(10 \times 10^{-6})^2}{2 \times 385.15 \times 10^{-10}} = 0.1298 \text{ J}$$

36. A $1 \mu\text{F}$ and a $2 \mu\text{F}$ capacitors are connected in series across a 1200 V supply.

- find the charge on each capacitor and voltage across each capacitor,
- the charged capacitors are disconnected from the supply and are now connected in parallel with terminals of like sign together. Find the final charge on each capacitor and the voltage across each.

(Ans: $800 \mu\text{C}$; 800 V across $1 \mu\text{F}$ and 400 V across $2 \mu\text{F}$;

In parallel, charges are $\frac{1600}{3} \mu\text{C}$ across $1 \mu\text{F}$ and

$\frac{3200}{3} \mu\text{C}$ across $2 \mu\text{F}$. Final voltage = $(1600/3) \text{ Volts}$)

[Hint: $Q = \frac{2}{2+1} \times 1200 \times 10^{-6} = 800 \mu\text{C}$

$V \text{ (across } 1 \mu\text{F)} = \frac{800}{1} = 800 \text{ V}$

$$V \text{ (across } 2 \mu\text{F)} = \frac{800}{2} = 400 \text{ V}$$

$$\text{When in parallel, } V = \frac{\text{net charge}}{\text{net capacitance}} = \frac{1600 \times 10^{-6}}{3 \times 10^{-6}} = \frac{1600}{3} \text{ V}$$

$$\therefore Q_f \text{ (across } 1 \mu\text{F)} = 1 \mu\text{F} \times \frac{1600}{3} = \frac{1600}{3} \mu\text{C}$$

$$Q_f \text{ (across } 2 \mu\text{F)} = 2 \mu\text{F} \times \frac{1600}{3} = \frac{3200}{3} \mu\text{C}$$

37. A $100 \mu\text{F}$ capacitor is charged to a p.d. of 100 V . It is then connected to an uncharged capacitor of $20 \mu\text{F}$. What will be the new p.d. across the $100 \mu\text{F}$ capacitor? (Ans: 83.33 V)

$$[\text{Hint: } Q = CV = 100 \times 10^{-6} \times 100 = 10^{-2} \text{ C}]$$

$$V' = \frac{Q}{C_{\text{eq}}} = \frac{10^{-2}}{(100 + 20)10^{-6}} = 83.33 \text{ V}$$

38. A circuit is displayed in Fig. 2.72. Find
(i) the charge across each capacitor,
(ii) the potential difference across each capacitor,
(iii) the stored energy of each capacitor.

$$(\text{Ans: } Q_{C_1} = 333.33 \mu\text{C} = Q_{C_2}, \\ Q_{C_3} = 400 \mu\text{C})$$

$$V_{C_1} = 33.33 \text{ V}; V_{C_2} = 66.66 \text{ V}; V_{C_3} = 100 \text{ V}$$

$$W_{C_1} = 5.5 \times 10^{-3} \text{ J}; W_{C_2} = 10.9 \times 10^{-3} \text{ J}$$

$$W_{C_3} = 2 \times 10^{-2} \text{ J}.$$

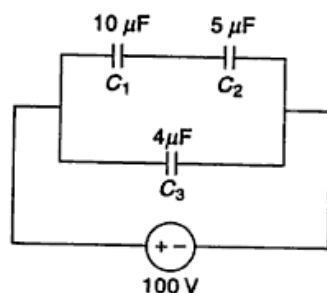


Fig. 2.72

$$[\text{Hint: } C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2} + C_3 = \frac{22}{3} \mu\text{F}]$$

$$Q_{C_1} = \frac{C_1 C_2}{C_1 + C_2} \times 100 = \frac{1000}{3} \mu\text{C}$$

$$Q_{C_2} = \frac{C_1 C_2}{C_1 + C_2} \times 100 = \frac{1000}{3} \mu\text{C}$$

$$Q_{C_3} = 4 \times 100 = 400 \mu\text{C}$$

(all capacitances are expressed in μF)

$$V_{C_3} = 100 \text{ V}; V_{C_1} = \frac{1000/3}{10} = 33.33 \text{ V}$$

$$V_{C_2} = \frac{1000/3}{5} = 66.66 \text{ V}$$

$$W_{C_1} = \frac{1}{2} C_1 \times \left(\frac{100}{3}\right)^2 = 5.5 \times 10^{-3} \text{ J}$$

$$W_{C_2} = \frac{1}{2} C_2 \times (66.66)^2 = 10.9 \times 10^{-3} \text{ J}$$

$$W_{C_3} = \frac{1}{2} \times C_3 \times 100^2 = 2 \times 10^{-2} \text{ J}$$

39. A 40 μF capacitor is charged to a potential difference of 400 V and then discharged through a 100 k Ω resistor. Derive an expression representing the discharge current. How much energy will be dissipated in the resistor over a period of 4s following the initiation of discharge. [Ans: 2.767 J]

[Hint: $\lambda = RC = 100 \times 10^3 \times 40 \times 10^{-6} = 4$

$$v_c = 400 e^{-t/4}$$

$$i_c = C \frac{dv_c}{dt} = 40 \times 10^{-6} \times 400 \left(-\frac{1}{4}\right) e^{-t/4} \\ = 0.004 e^{-t/4}$$

$$\text{Initial stored energy} = \frac{1}{2} \times 40 \times 10^{-6} \times (400)^2 \text{ J} = 3.2 \text{ J}$$

$$\text{After 4s } v_c = 400 e^{-4/4} = 147.15 \text{ V}$$

$$\text{Stored energy} = \frac{1}{2} \times 40 \times 10^{-6} (147.15)^2 \text{ J} = 0.433 \text{ J}$$

$$\text{Energy dissipated} = 3.2 - 0.433 = 2.767 \text{ J}$$

40. A capacitor is constructed from two square metal plates each of side 120 mm. The plates are separated by a dielectric of thickness 2 mm and relative permittivity 5. Calculate the capacitance. If the electric field strength in the dielectric is 12.5 kV/mm calculate the total charge on each plate.

[Ans: $C = 318.7 \mu\text{F}$ $Q = 7.968 \text{ C}$]

[Hint: $C = \frac{\epsilon_0 \epsilon_r A}{d} = \frac{8.854 \times 10^{-12} \times 5 \times 0.12 \times 0.12}{2 \times 10^{-3}} \text{ F}$

$$= 0.3187 \times 10^{-9} \text{ F} = 318.7 \mu\text{F}$$

$$Q = CV = CE d = 318.7 \times 10^{-6} \times 12.5 \times 10^3 \times 2 \\ = 7.9675 \text{ C}]$$

41. A parallel plate capacitor is formed using three dielectric substances having permittivities ϵ_1 , ϵ_2 and ϵ_3 (Fig. 2.73). If the plate area is 'a', find the equivalent capacitance between A and B.

$$\left(\text{Ans: } \frac{2\epsilon_0 \epsilon_3 A}{d} \left(\frac{\epsilon_1 + \epsilon_2}{\epsilon_1 + \epsilon_2 + 2\epsilon_3} \right) \right)$$

[Hint: Ref. equivalent circuit Fig. 2.73.

$$C_3 = \frac{\epsilon_0 \epsilon_3 A}{d/2}; C_2 = \frac{\epsilon_0 \epsilon_2 (A/2)}{d/2} = \frac{\epsilon_0 \epsilon_2 A}{d}$$

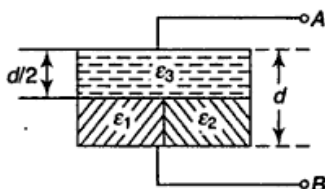


Fig. 2.73

Similarly $C_1 = \frac{\epsilon_o \epsilon_1 A}{d}$.

Since C_1 and C_2 are in parallel contribution and this is in series with C_3 we can write

$$C = \frac{(C_1 + C_2) \times C_3}{C_1 + C_2 + C_3} = \frac{\frac{\epsilon_o A}{d} (\epsilon_1 + \epsilon_2) \times \frac{2\epsilon_o \epsilon_3 A}{d}}{\frac{\epsilon_o A}{d} (\epsilon_1 + \epsilon_2 + 2\epsilon_3)}$$

$$= \frac{2\epsilon_o \epsilon_3 A}{d} \left[\frac{\epsilon_1 + \epsilon_2}{\epsilon_1 + \epsilon_2 + 2\epsilon_3} \right]$$

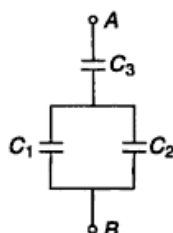


Fig. 2.73a

42. Find the capacitance of an isolated spherical conductor of radius r_1 surrounded by a concentric layer of dielectric of outer radius r_2 and relative permittivity ϵ_r .

$$\left(\text{Ans: } \frac{4\pi\epsilon_o \epsilon_r r_1 r_2}{r_2 + (\epsilon_r - 1)r_1} \right)$$

$$\left[\text{Hint: } C_1 = \frac{4\pi\epsilon_o \epsilon_r r_1 r_2}{r_1 - r_2}; C_2 = 4\pi\epsilon_o r_2 \right]$$

$$C = \frac{C_1 C_2}{C_1 + C_2} = \frac{4\pi\epsilon_o \epsilon_r r_1 r_2}{r_2 + (\epsilon_r - 1)r_1}$$



ELECTRO- MAGNETISM AND MAGNETIC CIRCUITS

3.1 INTRODUCTION

The fascinating properties of magnets have been known since ancient times. The word 'magnet' comes from the ancient Greek city of Magnesia (The modern town Manisa in Western Turkey), where the natural magnets called lodestones were found.

The fundamental nature of magnetism is the interaction of moving electric charges. Unlike electric forces which act on electric charges whether they are moving or not, magnetic forces act only on moving charges and current-carrying conductors.

The power of a magnet by which it attracts certain substances is called *magnetism* and the materials which are attracted by a magnet are called *magnetic materials*.

Few important characteristics of magnets are:

- (a) Magnets can exist only in dipole and the pole strength of its two poles is the same.
- (b) Magnets always attract iron and its alloys.
- (c) A magnetic field is established by a permanent magnet, by an electric current or by other moving charges.
- (d) Between magnets, like poles repel and unlike poles attract (Coulomb's first law of magnetism).
- (e) A magnetic substance becomes a magnet, when it is placed near a magnet. This phenomenon is known as *magnetic induction*.
- (f) Magnetic field, in turn, exerts forces on other moving charges and current carrying conductors.
- (g) The two poles of a magnet cannot be isolated (i.e., separated out) Magnetics monopole does not exist.
- (h) It can be magnetically saturated.
- (i) It can be demagnetized by beating, mechanical jerks, heating and with lapse of time.

- (j) It produces magnetism in other materials by induction.
- (k) On bending a magnet its pole strength remains unchanged but its magnetic moment changes.
- (l) The magnetism of materials is mainly due to the spin motion of its electrons.

Electromagnetism was discovered by H.C. Oersted in 1820. He found that electric current in a conductor can produce a magnetic field around it. This discovery by Oersted provided the interaction between electricity and magnetism. The strength of this magnetic field can be increased by increasing the current in the conductor. The strength can also be increased by forming the wire into a coil of many turns as only by providing an iron core. The magnetic force has been conventionally assumed to act along a curved line from the N-pole to the S-pole.

Properties of Lines of Force

- (a) They are always in the closed curves existing from a N-pole and terminating on a S-pole.
- (b) They never cross one another
- (c) Parallel lines of forces acting in the same direction repel one another.
- (d) They always take the path of least opposition.
- (e) They never have an origin nor an end.

Coulomb's Law

The mechanical force produced between two magnetic poles is produced to the product of their pole strengths, and inversely proportional to the square of the distance between them.

$$F \propto \frac{m_1 m_2}{d^2}$$

In SI system, the law is given by

$$F = \frac{m_1 m_2}{\mu_o \cdot \mu_r \cdot d^2} \quad (3.1)$$

where F is the force between the poles (in Newtons), m_1 and m_2 are pole strengths, d is the distance between the poles in meters, μ_r is the relative permeability of the medium in which the poles are situated, and μ_o is the permeability of free space (in air). μ = Absolute permeability of air (or vacuum) \times relative permeability $= \mu_o \cdot \mu_r = 4\pi \times 10^{-7} \times \mu_r$ wb/AT.

Gauss's Law of Magnetism

If there were such a thing as a single magnetic charge (magnetic monopole), the total magnetic flux through a closed surface would be proportional to the total magnetic charge enclosed. But as no magnetic monopole has ever been observed, we can conclude that the total magnetic flux through a closed surface is zero.

$$\oint \vec{B} \cdot d\vec{s} = 0 \quad (3.2)$$

i.e. the total magnetic flux entering a closed surface equals the total magnetic flux leaving.

Intensity of Magnetism

When a material is placed in a magnetic field, it acquires magnetic moment M . The intensity of magnetization is defined as the magnetic moment per unit volume. Its unit is Ampere/meter. The magnetic susceptibility is defined as the intensity of magnetisation per unit magnetizing field. It has no unit and is dimensionless.

Lorentz Force

If a charge q moves in a region where both electric field \vec{E} and a magnetic field \vec{B} are present the resultant force acting on it is

$$\vec{F} = q(\vec{E} + \vec{v} \times \vec{B}) \quad (3.3)$$

This is called the *Lorentz force*.

The phenomenon of magnetizing an unmagnetized substance by the process magnetic induction is called *magnetization*.

The process of protecting any apparatus from the effect of earth's magnetic field is known as *magnetic shielding*.

The phenomenon of decreasing or spoiling magnetic strength of a material is known as *demagnetization*.

The state of a material after which the increase in its magnetic strength stops is known as *magnetic saturation*.

Curie Law

The magnetic susceptibility of paramagnetic substances is inversely proportional to its absolute temperature, i.e. magnetic susceptibility (x) $\propto 1/T$

$$x = \frac{C}{T}$$

where C = Curies constant and T = absolute temperature.

On increasing the temperature, the magnetic susceptibility of paramagnet materials decreases and vice versa. The magnetic susceptibility of ferro-magnetic substances does not change according to Curie law.

Curie Temperature

The temperature above which a ferromagnetic materials behaves like a paramagnetic material is defined as the Curie temperature.

For Ni, $T_c = 358^\circ\text{C}$

For Fe, $T_c = 770^\circ\text{C}$

For Co, $T_c = 1120^\circ\text{C}$

At this temperature the ferro magnetism of the substance suddenly vanishes.


Curie-Weiss Law

At temperatures above the Curie temperature the magnetic susceptibility (x) of ferromagnetic material is inversely proportional to $(T - T_c)$, i.e.

$$x \propto \frac{1}{T - T_c}, \quad x = \frac{C}{T - T_c} \quad (3.4)$$

where T_c = curie-temperature, C = variation constant (Curie constant).

$x - T$ curve is shown in Fig. 3.1.

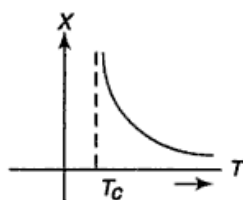Fig. 3.1 $\chi - T$ characteristic

3.2 MAGNETIC FIELD AROUND A CURRENT-CARRYING CONDUCTOR

If electric current passes through a conductor, a magnetic field immediately builds up due to the motion of electrons. When a magnetic field is applied to a conductor, the electrons come in motion. This is the converse phenomenon of the previous one.

When a conductor carries current downwards, i.e. away from the observer, the flux distribution is shown in Fig. 3.2(a) when it carried current upwards, i.e. towards observer, flux distribution is shown in Fig. 3.2(b).

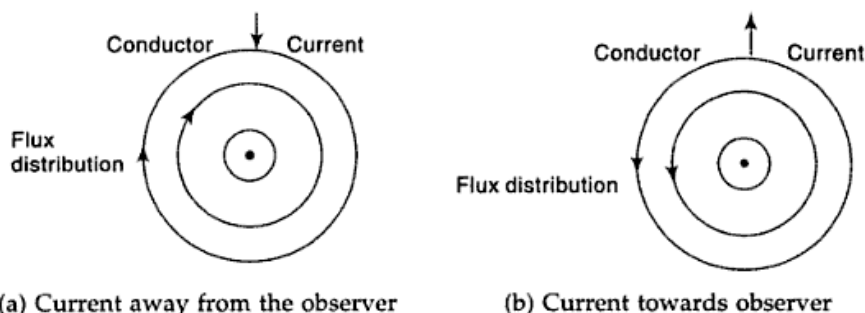


Fig. 3.2 Magnetic field distribution around a current carrying conductor

The dot and cross symbol may be thought of as viewing an arrow in the direction of current flow and in the direction away from the current flow. Direction of the field (flux) can be determined by using Ampere's right-hand rule for a conductor, which states that when the conductor is being held by the right hand in such a way that the thumb outstretched parallel to the conductor and pointing the direction of current flow, the closed fingers then give the direction of flux around the conductor. (It can be obtained from right hand *cork screw rule*.)

3.2.1 Fleming's Left hand Rule

This rule is used to determine the direction of force acting on a current carrying conductor placed in a magnetic field. According to this rule, if the middle finger, forefinger and the thumb of the left hand are at right angles to one another and if

* Remember: Flux is a scalar quantity. Its SI unit is Weber (Wb), CGS unit is Maxwell, $1 \text{ Wb} = 10^8 \text{ Maxwell}$.

the middle finger and forefinger represent the direction of current and magnetic field respectively, then the thumb will indicate the direction of force acting on the conductor (Fig. 3.3) This rule is used to determine the direction of motion of a conductor (rotor) in the magnetic field produced by the stator for a motor.

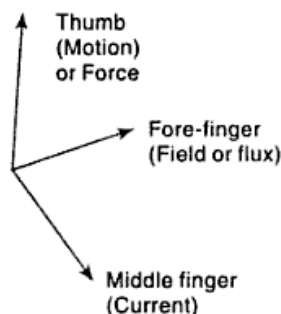


Fig. 3.3 Diagrammatic explanation of Fleming's left hand rule

3.3 FORCE ON A CURRENT-CARRYING CONDUCTOR IN A MAGNETIC FIELD

It has been found that when a current carrying conductor is placed in a right angles to the direction of magnetic field, the conductor experiences a mechanical force, which is right angles to both the direction of magnetic field as well as flow of current. This force experienced is directly proportional to:

- (a) Current (I) flowing through the conductor
- (b) Flux density (B) and
- (c) The length (l) of the conductor.

\therefore Force acting on conductor,

$$F = BIl \text{ N (Newtons).} \quad (3.5a)$$

Now, say the conductor is not placed at the right angles to the field, but instead placed at an angle (θ), then from natural reasoning,

$$F = BIl \sin \theta \text{ N} \quad (3.5b)$$

The direction of the mechanical force (F) is found by Fleming's left hand rule (described in previous section).

3.4 FORCE BETWEEN TWO PARALLEL CURRENT-CARRYING CONDUCTORS

Figure 3.4 shows two conductors, kept in parallel, and carrying currents I_1 and I_2 , each has a length of l meters and placed at distance d meters from each other in air. When these two parallel conductors are carrying currents in the same direction [Fig. 3.5a], lines of force in circle each other in the same direction and as a result, resultant field tends to attract the conductor together towards each other. On the other hand, when two parallel conductors are carrying currents in the opposite direction [Fig. 3.5b] then lines of force in the same direction are crowded

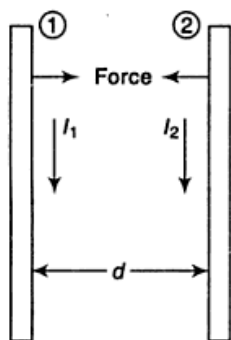


Fig. 3.4 Force between two parallel current-carrying conductors

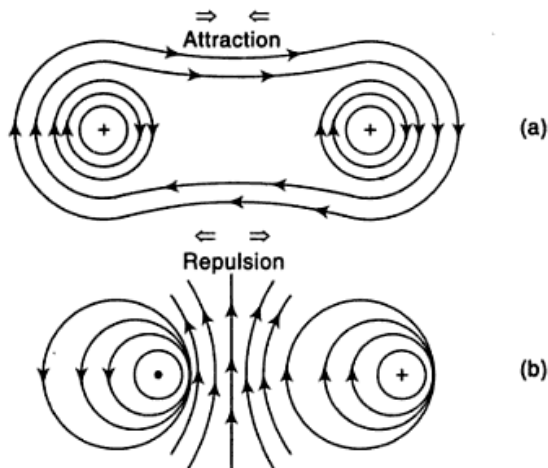


Fig. 3.5 Direction of lines of force between two parallel current carrying conductors

between the two conductors, and thereby experience a mutual repulsive force. In fact, a mechanical force is developed between these two conductors.

In order to determine the magnitude of force between two parallel current-carrying conductors, one of the two conductors (say conductor 1) is considered placed in a magnetic field due to the other (i.e. due to conductor 2).

Magnetic field due to conductor 2 is given by

$$H = \frac{I_2}{2\pi d} \quad (3.6)$$

\therefore Force acting on conductor 1 is $F = BI_1l$, where B is the flux density of the field due to conductor 2.

$$\therefore F = \mu_o \mu_r H I_1 l \quad (3.7a)$$

where $B = \mu_o \mu_r H$

$[\mu_r$ is the relative permeability of the medium in which both the conductors are placed]

Substituting the value of (H) in equation (3.7a), we have

$$\begin{aligned} F &= \frac{\mu_o \mu_r I_1 I_2 l}{2\pi d} \cdot N \\ &= \frac{\mu_o I_1 I_2 l}{2\pi d} \text{ N (in air } \mu_r = 1) \\ &= \frac{4\pi \times 10^{-7} \times I_1 I_2 l}{2\pi d} \text{ N} \\ &= \frac{2I_1 I_2 l \times 10^{-7}}{d} \text{ N} \end{aligned} \quad (3.7b)$$

In differential form, we can write

$$\frac{dF}{dl} = \frac{2 \times 10^{-7} \times I_1 I_2}{d} \text{ N} \quad (3.8)$$

From the above expression it can be concluded that *the larger the currents carried by the conductor, and less is the distance between the conductors, greater is the force between them.*

3.1 In uniform field of 1 Wb/m^2 , a direct current of 70 A is passed through a straight wire of 1.5 m placed perpendicular to the field. Calculate:

- The magnitude of the mechanical force produced in the wire.
- The prime mover power (i.e. the mechanical power) in watts to displace the conductor against the force at a uniform velocity of 5 m/sec .
- The emf generated in the current carrying wire.

How do you show that the electrical power produced is same as the mechanical power in creating the motion?

Solution

$$\begin{aligned} \text{(a) Force} &= BIl \sin \theta \\ &= 1.0 \times 70 \times 1.5 \sin 90^\circ \quad [\text{here } \theta = 90^\circ] \\ &= 105 \text{ N} \end{aligned}$$

$$\begin{aligned} \text{(b) Prime-mover, i.e. mechanical power} \\ &= F \times v \\ &= 105 \times 5 = 525 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{(c) Emf generated} &= Blv \\ &= 1 \times 1.5 \times 5 = 7.5 \text{ V.} \end{aligned}$$

The electrical power $= eI = 7.5 \times 70 = 525 \text{ W. (= mechanical power)}$

3.2 Calculate the force developed per meter length between two current-carrying conductors 10 cm apart and carrying 1000 A and 1500 A currents respectively.

Solution

Given $I_1 = 1000 \text{ A}$, $I_2 = 1500 \text{ A}$, $d = 10 \text{ cm} = 0.10 \text{ m}$

$$\begin{aligned} \text{Force per meter length} &= \frac{2 \times 10^{-7} I_1 I_2}{d} \\ &= \frac{2 \times 10^{-7} \times 1000 \times 1500}{0.10} \\ &= 3 \text{ N} \end{aligned} \quad \dots\dots\dots$$

3.3 Two long straight conductors each carrying an electric current of 5.0 A , are kept parallel to each other at a separation of 2.5 cm . Calculate the magnitude of magnetic force experienced by 10 cm of a conductor.

Solution

The field at the side of one conductor due to the other is

$$B = \frac{\mu_0 \cdot I}{2\pi d} = \frac{2 \times 10^{-7} \times 5}{2.5 \times 10^{-2}} = 4.0 \times 10^{-5} \text{ T}$$

∴ The force experienced by 10 cm of the conductor due to the other is

$$\begin{aligned} F &= I l B \\ &= 5.0 \times 10 \times 10^{-2} \times 4.0 \times 10^{-5} \\ &= 2 \times 10^{-5} \text{ N.} \end{aligned}$$

3.4 Two long straight parallel wires situated in air at a distance of 2.5 cm having a current of 100 A in each wire in the same direction. Determine the magnetic force on each wire. Justify whether the force is of the repulsion or attraction type.

Solution

Given, $d = 2.5 \text{ cm} = 2.5 \times 10^{-2} \text{ m}$
 $I_1 = I_2 = 100 \text{ A.}$

∴ Force on each wire per meter length

$$F = \frac{4 \times 10^{-7} \times I_1 \cdot I_2}{2d} = \frac{2 \times 10^{-7} \times 100 \times 100}{2.5 \times 10^{-2}} = 0.08 \text{ N}$$

Force is attraction type since currents in both the wires are flowing in same direction.

3.5 Two infinite parallel conductors carrying parallel currents of 50 A each. Find the magnitude and direction of the force between the conductors per meter length if the gap between them is 25 cm.

Solution

We know $F = \mu_0 \cdot \frac{I_1 I_2 d}{2\pi d}$

$$\begin{aligned} &= \frac{2 \times 10^{-7} \times 50 \times 50 \times 1}{25 \times 10^{-2}} \text{ N} \\ &= 10^2 \times 10^2 \times 10^{-7} \times 2 \\ &= 2 \times 10^{-3} \text{ N.} \end{aligned}$$

The direction of force will depend on whether the two currents are flowing in the same direction or not. For same direction, it will be force of attraction and for opposite direction it will be force of repulsion.

3.6 A wire of 1 m length long is bend to form a square. The plane of the square is right angled to a uniform field having a flux density of 2 m Wb/mm². Determine the work done if the wire carries a current of 20 Amps through it, is changed to a circular shape.

Solution

Side of the square = $\frac{1}{4} \text{ m} = 0.25 \text{ m}$

$A_1 = \text{area of square} = (0.25)^2 = 0.0625 \text{ m}^2$

Circumference of a circle is 1 m = $2\pi r$

∴ $r = \frac{1}{2\pi} = 0.15909 \text{ m}$

∴ $A_2 = \text{area of the circle} = \pi r^2$

$$\begin{aligned} &= \frac{22}{7} \times (0.15909)^2 \\ &= 0.0795 \text{ m}^2 \end{aligned}$$

$$\begin{aligned}
 \therefore \text{Work done} &= \text{difference between the torques} = BIA_2 - BIA_1 \\
 &= 2 \times 10^{-3} \times 20 (0.0795 - 0.0625) \\
 &= 0.00068 \text{ J}
 \end{aligned}$$

3.5 BIOT SAVART'S (OR LAPLACE'S) LAW

If a current carrying conductor is placed at an angle (θ) to the direction of a magnetic field, the effective length being ($l \sin \theta$), the force on the conductor (Fig. 3.6) will be $F = BIl \sin \theta$. (The effective length is the length of the conductor lying within the magnetic field).

In magnetics, there are basically two methods of calculating magnetic field at some point. One is Bio-Savart Law (or Laplace's Law) which gives the magnetic field due to an infinitesimally small current-carrying conductor (wire) at some point and another is Ampere's law.

Let dH be the magnetic field at a point P associated with length element dl carrying a steady current of I amperes. Imagine a unit N-pole is present at point P (Fig. 3.6(c)). Then flux density B due to the pole strength of 1 wb is given by

$$B = \frac{1}{4\pi r^2} \text{ wb/m}^2$$

\therefore Mechanical force acting at the element (dl)

$$dF = BI(dl) \sin \theta = \frac{I \cdot dl \cdot \sin \theta}{4\pi r^2} \text{ N} \quad (3.9)$$

(Since action and reaction are equal and opposite)

Now, as per Newton's third law the magnetic field produced by the current element (dl) on the unit pole at point P , is given by

$$dH = \frac{I \cdot dl \cdot \sin \theta}{4\pi r^2} \text{ AT/m} \quad (3.10)$$

with the direction of (dH) and perpendicular to both (dl) and the unit vector r directed from (dl) to P .

This equation is known as Biot-Savart's Law (or Laplace's law).

The following point is worth noting regarding the Biot-Savart law.

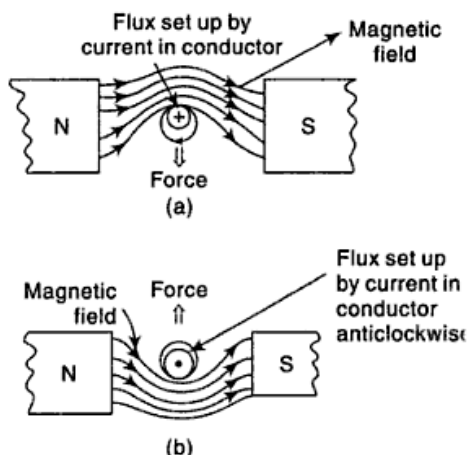


Fig. 3.6 (a, b) Force on a current-carrying conductor lying in a magnetic field

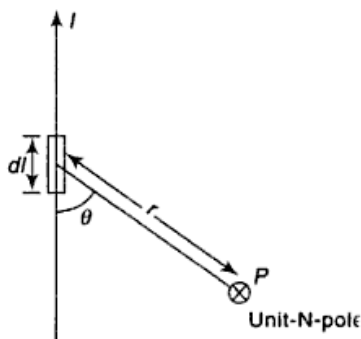


Fig. 3.6(c) A current carrying conductor in a magnetic field

The magnitude of dH is given by

$$|dH| = \frac{I \cdot dl \cdot \sin \theta}{4\pi r^2}$$

$|dH|$ is zero at $\theta = 0^\circ$ or 180°
and maximum at $\theta = 90^\circ$.

This law is employed for calculating the field strength near any system of conductors.

3.6 APPLICATION OF BIOT-SAVART LAWS

3.6.1 Determination of Magnetic Field Surrounding a Straight Long Conductor of Finite Size

Consider XY (Fig. 3.7) be a straight long finite conductor carrying a current I in the direction for X to Y , and P be a point at which the magnetic field H is required. Let us draw a perpendicular from P which meets the conductor at Q . Let $PQ = R$.

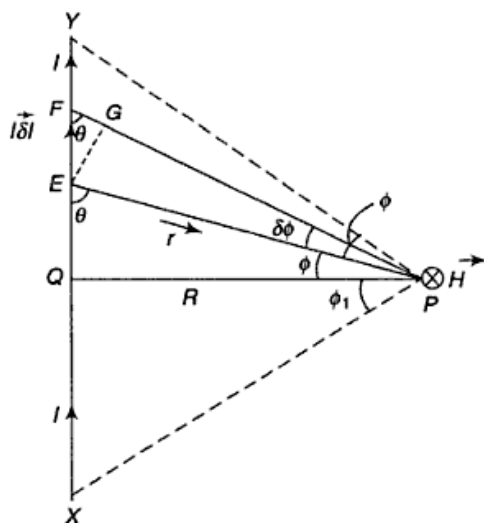


Fig. 3.7 Application of Biot-Savarts Law for a straight conductor

Let us consider the conductor to be divided into many small current elements and let $(i \cdot d\vec{l})$ be one such (vector) element, where length $EF (= \delta l)$. Let (\vec{r}) be the position vector from the element to the point P . Let $\angle EPQ = \phi$, $\angle FPE = \delta\phi$ and $\angle EFP = \theta$. Since the length $EF (= \delta l)$ is very small, $\angle QEP = \theta$. Let EG be a perpendicular from E to FP .

By Biot-Savart law, the magnetic field at P due to the current-element $(i \cdot d\vec{l})$ is given by

$$\delta\vec{H} = \frac{\mu_0}{4\pi} \cdot \frac{i\delta\vec{l} \times \vec{r}}{r^3}$$

The angle between vectors $(i\vec{dl})$ and (\vec{r}) is $(180 - \theta)$ and so the magnitude of the field at P is

$$\delta H = \frac{\mu_o}{4\pi} \cdot \frac{i\delta l \sin(180 - \theta)}{r^2} = \frac{\mu_o}{4\pi} \frac{i\delta l \sin \theta}{r^2} \quad (3.11)$$

By right-hand screw rule of vector product, the field $(\delta\vec{H})$ at point P is perpendicular to the page directed 'downwards'.

Now from the similar triangles $\triangle EFG$ and $\triangle PEG$, we have

$$EG = EF \sin \theta = \delta l \sin \theta$$

and $EG = EP \sin \delta\phi = r \sin \delta\phi = r \cdot \delta\phi$ ($\delta\phi$ being very small)

$$\therefore \delta l \sin \theta = r \cdot \delta\phi \quad (3.12)$$

Making this substitution in equation (3.11) we have

$$\delta H = \frac{\mu_o}{4\pi} \frac{i \cdot \delta\phi}{r}$$

From right-angled triangle EQP , we have

$$r = \frac{R}{\cos \phi}$$

$$\therefore \delta H = \frac{\mu_o}{4\pi} \cdot \frac{i \cos \phi \delta\phi}{R} \quad (3.13)$$

Let us join PX and PY . Let $\angle QPX = \phi_1$ (anticlockwise) and $\angle QPY = \phi_2$ (clockwise). Then the magnitude of the magnetic field \vec{H} at point P due to the whole conductor is

$$\begin{aligned} H &= \int_{-\phi_1}^{\phi_2} \frac{\mu_o}{4\pi} \cdot \frac{i}{R} \cos \phi \, d\phi = \frac{\mu_o}{4\pi} \cdot \frac{i}{R} [\sin \phi]_{-\phi_1}^{\phi_2} \\ &= \frac{\mu_o \cdot I}{4\pi R} [\sin \phi_2 - \sin (-\phi_1)] \\ &= \frac{\mu_o \cdot I}{4\pi R} [\sin \phi_1 + \sin \phi_2] \end{aligned} \quad (3.14)$$

For a conductor of infinite length, we have $\phi_1 = \phi_2 = 90^\circ$

$$\begin{aligned} H &= \frac{\mu_o}{4\pi} \cdot \frac{I}{R} (\sin 90^\circ + \sin 90^\circ) = \frac{\mu_o \cdot 2 \cdot I}{4\pi \cdot R} \\ &= \frac{\mu_o \cdot I}{2\pi R} \end{aligned} \quad (3.15a)$$

For a semi-infinite conductor the field is

$$H = \frac{\mu_o \cdot I}{4\pi r} (1 + \sin \phi) \quad (3.15b)$$

3.6.2 Field Strength Due to Circular Loop

Consider a circular coil of length l meters and radius r meters having N turns, and carrying a current of I amperes as shown in Fig. 3.8. Let a unit N-pole be placed on the axis of the coil at P at a distance x meters from the centre of the coil; then force dH experienced on unit N-pole, due to small arc length dl , is given by (from Biot-Savart's law)

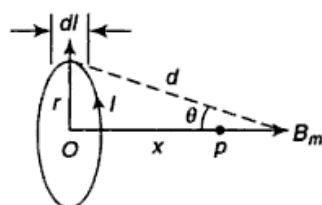


Fig. 3.8 A circular coil

$$\delta H = \frac{NI dl}{4\pi d^2}$$

Axial component of (δH) is thus obtained as $\left(\frac{NI dl}{4\pi d^2} \sin \theta \right)$

\therefore Total force experienced on unit N-pole placed at P due to entire coil is given by

$$\begin{aligned} H &= \frac{NI \sin \theta}{4\pi d^2} \int_0^l dl = \frac{NI \sin \theta}{4\pi d^2} \cdot l \\ &= \frac{NI \sin \theta}{4\pi d^2} \times 2\pi r = \frac{Nlr \sin \theta}{2d^2} \\ &= \frac{Nlr^2}{2(r^2 + x^2)^{3/2}} \left[\because \frac{r}{\sin \theta} = (r^2 + x^2)^{1/2} \right] \end{aligned} \quad (3.16)$$

Now if we want to calculate the field strength at the centre of the loop, x becomes zero.

H (Force experienced on a unit N-pole placed at that point) is given by = $\frac{NI}{2r}$ AT/m.

In the above expression if we want to calculate the field strength far away from the centre of the circular loop, i.e. if $x \gg r$, $r^2 + x^2 \approx x^2$,

then,
$$H = \frac{1}{4\pi} \cdot \frac{2M}{x^3}$$

where $M = \text{magnetic moment of the loop} = NIA = NI\pi r^2$.

3.6.3 Field in a Solenoid

A solenoid is a helical coil and is a very effective method of producing a magnetic field. Figure 3.9 shows a solenoid of length l carrying a steady current of I amperes. Let the number of turns be N and the radius of the coil be R . Since the spacing between the turns is very small, the wire (conductor) can be considered

as current sheet of width $\left(\frac{l}{N}\right)$ and negligible spacing between turns. Then the current in the solenoid causes a cylindrical current sheet having a linear current density K .

i.e., $K = \frac{NI}{l}$ ampere turns/meter.

For an element (dx), shown in Fig. 3.10,

The current density = $Kdx = NI\left(\frac{dx}{l}\right)$

Using the equation

$H = \frac{NIR^2}{2(R^2 + x^2)^{3/2}}$, the flux density

(dB) at the centre of the solenoid, due to element (dx) is

$$dB = \frac{\mu NIR^2}{2l(R^2 + x^2)^{3/2}} dx \quad (3.17)$$

The total flux density can be formed by integrating (dB) over the length of the solenoid, i.e. from $x = -\frac{l}{2}$ to $x = +\frac{l}{2}$. Thus

$$\begin{aligned} B &= \frac{\mu NIR^2}{2l} \int_{-l/2}^{l/2} \frac{dx}{(R^2 + x^2)^{3/2}} \\ &= \frac{\mu NI}{4(R^2 + l^2)^{1/2}} \end{aligned} \quad (3.18)$$

If the length is much larger than the radius, i.e. if $l \gg R$, we have

$$B = \frac{\mu NI}{l} = \mu \cdot K$$

The obtained equations give B at the centre of the solenoid. If the limit of integration is changed from 0 to l , we get B at one end of the solenoid. This value is

$$B = \frac{\mu NI}{2(R^2 + l^2)^{1/2}} \quad (3.19)$$

If $l \gg R$, this flux density at one end is

$$B = \frac{\mu NI}{2l} = 0.5 \mu K \quad \left[\because K = \frac{NI}{l} \right]$$

A comparison of the above equations shows that flux density at one end of the coil is half of that at the centre.

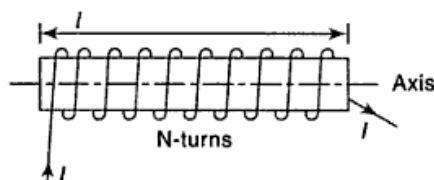


Fig. 3.9 Solenoid of length l

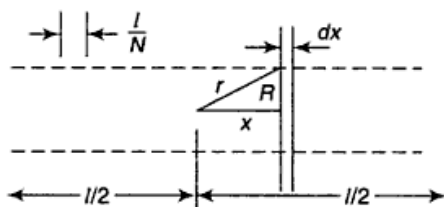


Fig. 3.10 Field in an elemental portion in the solenoid

3.7 A circular current-carrying coil has a radius R . Show that the distance from the centre of the coil, on the axis, where B will be $\left(\frac{1}{8}\right)$ of its value at the centre of the coil is $(\sqrt{3}r)$.

Solution

$$B_{\text{axis}} = \frac{1}{8} B_{\text{centre}} \quad (\text{given})$$

$$\therefore \frac{\mu_o \cdot NI r^2}{2(r^2 + x^2)^{3/2}} = \frac{1}{8} \left(\frac{\mu_o \cdot NI}{2 \cdot r} \right)$$

$$\text{or} \quad 8r^3 = (r^2 + x^2)^{3/2}$$

$$\text{or} \quad (2r)^3 = \left\{ \left(\sqrt{r^2 + x^2} \right) \right\}^3$$

$$\text{or} \quad \sqrt{r^2 + x^2} = 2r$$

$$\text{or} \quad r^2 + x^2 = 4r^2$$

$$\text{or} \quad x = \sqrt{3} r.$$

3.8 A current of 10 A is flowing in a flexible conductor of length 1.5 m. A force of 15 N acts on it when it is placed in a uniform field of 2 T. Calculate the angle between the magnetic field and the direction of the current.

Solution

$$\begin{aligned} \text{We know} \quad F &= BIl \sin \theta \\ 15 &= 2 \times 10 (1.5) \sin \theta \end{aligned}$$

$$\therefore \sin \theta = \frac{15}{30} = \frac{1}{2} = \sin^{-1} (30^\circ)$$

$$\therefore \theta = 30^\circ$$

3.9 A straight conductor is carrying 2000 A and a point P is situated in such that $\phi_1 = 60^\circ$ and $\phi_2 = 30^\circ$. Calculate the field strength at P if its perpendicular distance from the conductor is 0.2 meter.

Solution

$$H = \frac{\mu_o \cdot I}{4\pi r} (\sin \phi_1 + \sin \phi_2)$$

$$\begin{aligned} \text{Given} \quad \phi_1 &= 60^\circ, \phi_2 = 30^\circ, r = 0.2 \text{ meter} \\ I &= 2000 \text{ Amps and } \mu_o = 1 \text{ [in air]} \end{aligned}$$

$$\begin{aligned} \therefore H &= \frac{2000}{4 \times \pi \times 0.2} [\sin 60^\circ + \sin 30^\circ] \\ &= 1087.05 \text{ A/m.} \end{aligned}$$

3.10 A solenoid of 400 turns is wound on a continuous ring of iron, the mean diameter of the ring being 10 cm. The relative permeability is 1250. What current is required in order that the flux density (B) in the iron shall be 12,000 maxwells/cm².

Solution

given $l = \text{mean circumference of ring} = 10 \times \pi \text{ cm}$
 $= 0.10 \pi \text{ meter}$

and $B = 12,000 \text{ maxwells/cm}^2$
 $= 12,000 \times 10^{-8} \times 10^4 = 1.2 \text{ wb/m}^2$

We know $B = \mu_r \cdot \mu_o \frac{NI}{l}$

$$\therefore I = \frac{B \cdot l}{\mu_r \mu_o \cdot N} = \frac{1.2 \times 0.10 \pi}{1.25 \times 10^3 \times 4\pi \times 10^{-7} \times 400}$$

$$= \frac{0.12}{2000 \times 10^{-4}} = \frac{0.12}{2 \times 10^{-1}} = \frac{1.2}{2} = 0.6 \text{ A}$$

.....

3.11 Prove that the magnetic field due to a current-carrying coil on the axis at a large distance x from the centre of the coil varies approximately as x^{-3} .

Solution

We know $B_{\text{axis}} = \frac{\mu_o \cdot N I r^2}{2(r^2 + x^2)^{3/2}}$

For $x \gg r$

$$B_{\text{axis}} \equiv \frac{\mu_o \cdot N I r^2}{2 \cdot x^3}$$

$$\therefore B_{\text{axis}} \propto \frac{1}{x^3} \text{ and hence proved.}$$

.....

3.7 ELECTROMAGNETIC INDUCTION

Whenever magnetic flux is linked with a circuit changes, an emf is induced in the circuit. If the circuit is closed, a current is also induced in it. The emf and current so produced lasts as long as the flux linked with the circuit changes (in direction and or in magnitude). This phenomenon is called *electromagnetic induction (EMI)*. The magnetic force can be considered as magnetic induction and its SI unit is tesla (T).

3.7.1 Laws of Electromagnetic Induction

In 1831, Michael Faraday, after performing a number of experiments, summarised a phenomenon of electromagnetic induction, which are stated as follows:

Faraday's first law states that "*whenever magnetic flux linked with a close coil changes, an induced emf is set up in the coil and the induced emf lasts as long as the change in magnetic flux continues.*"

Faraday's second law states that *the magnitude of the induced emf is proportional to the rate of change of magnetic lines of force.*

If ϕ is the magnetic flux linked with the current [coil of (N) turns] at any instant t , then the induced emf's expression in differential form is

$$|e| = \frac{d(N\phi)}{dt} = N \cdot \frac{d\phi}{dt} \text{ V.}$$

Since the induced emf (e) sets up a current in a direction that opposes the very cause of producing magnetic field, so a minus sign is given to the induced emf.

Therefore,
$$e = -N \frac{d\phi}{dt} \text{ V} \quad (3.20)$$

3.7.2 Lenz's Law

Even though Faraday's laws give no idea regarding the direction of induced emf, the direction of induced emf is, however, given by Lenz's law which is based on the law of conservation of energy and it states that "*The direction of the induced current (or emf) is such that it opposes the very cause producing this current (or emf), i.e. it opposes the change in magnetic flux.*"

In view of Lenz's law, the induced emf equation takes the form $e = -N \cdot \frac{d\phi}{dt}$.

In 1834, Heinrich Lenz, a German Physicist, enunciated a simple rule, now known as Lenz's law. In fact, this law basically interpreted the law of conservation of energy which can be justified as follows.

When the north pole of a magnet is moved towards the coil, the induced current flows in a direction so as to oppose the motion of the magnet towards the coil. This is only possible when the nearer face of the coil acts as a magnetic north pole which makes an anticlockwise current to flow in the coil. Then the repulsion between the two similar poles opposes the motion of the magnet towards the coil.

Similarly, when the magnet is moved away from the coil, the direction of induced current is such as to make the nearer face of the coil as a south pole which makes a clockwise induced current to flow in the coil. Then the attraction between the opposite poles opposes the motion of the magnet away from the coil. In either case, therefore, work has to be done in moving the magnet. It is this mechanical work which appears as electrical energy in the coil. Hence the production of induced emf or induced current in the coil as in accordance with the law of conservation of energy.

3.7.3 Fleming's* Right Hand Rule

The direction of the induced emf (and hence the induced current) is given by Fleming's Right Hand Rule which states that "stretch the fore finger, middle finger and the thumb of right hand in such a way that all three are mutually perpendicular to each other. If fore finger points in the direction of field, thumb points in the direction of motion of conductor, then middle finger will point along the direction of induced conventional current", as shown in Fig. 3.11.

* John Ambrose Fleming (1849-1945) was professor of Electrical Engineering at University College, London.

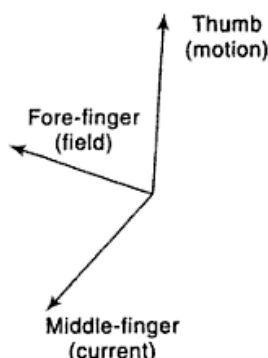


Fig. 3.11 Fleming's right hand rule.

3.8 CONCEPT OF SELF-INDUCTANCE AND MUTUAL INDUCTANCE

Self-Inductance

When a coil carries a current it establishes a magnetic flux (Fig. 3.12). When the current in the coil changes, the magnetic flux linking with the coil also changes. It is observed that this change in the value of current or flux in the coil is opposed by the instantaneous induction of opposing emf. This property of the coil by which it opposes the change in value of current or flux through it due to the production of self induced emf is called *self-inductance*. It is measured in terms of co-efficient of self-inductance L . It obeys Faraday's law of electromagnetic induction like any other induced emf.

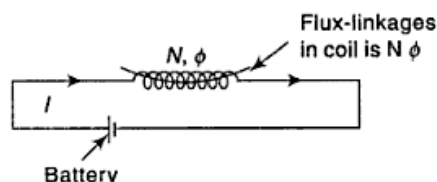


Fig. 3.12 Diagrammatic explanation of self-inductance

For a given coil (provided no magnetic material such as iron is nearby) the magnetic flux linked with it will be proportional to the current, i.e.

$$\phi \propto I \text{ or } \phi = LI \quad (3.21a)$$

where L is called the self-inductance (or simply inductance) of the coil.

The induced emf is given by

$$E = -\frac{d\phi}{dt} = -L \frac{dI}{dt} \quad (3.21b)$$

The S.I. unit of inductance is henry (symbol H). Henry is a big unit of inductance. Smaller units millihenry (mH) and microhenry (μH) are used

$$1 \text{ mH} = 10^{-3} \text{ H and } 1 \mu\text{H} = 10^{-6} \text{ H}$$

Thus, the self-inductance of a coil is 1 H if an induced emf of 1 volt is set up when the current in the coil changes at the rate of one ampere per second. Also, $1 \text{ H} = 1 \text{ Wb A}^{-1}$. This is also termed as *co-efficient of self-induction* or simply *self-induction*.

The role of self-inductance in an electrical circuit is the same as that of the inertia in mechanical motion. Thus the self-inductance of a coil is a measure of its ability to oppose the change in current through it and hence is also called *electrical inertia*.

Mutual Inductance

Whenever a change in current occurs in a coil, an induced emf is set up in the neighbouring coil. This process is called *mutual induction*. The coil in which the emf is induced is called the *secondary coil*. If a current I_1 flows in the primary coil, the magnetic flux linked with the secondary coil (Fig 3.13) will be

$$\phi_2 = M \cdot I_1 \quad (3.22a)$$

where M is called the mutual inductance between the two coils or circuits.

The emf induced in the secondary coil is given by

$$E_2 = \frac{d\phi_2}{dt} = -M \frac{dI_1}{dt} \quad (3.22b)$$

Thus the mutual inductance of a pair of circuits is 1 H if a rate of change of current of one ampere per second induces an emf of 1 V in the other circuit.

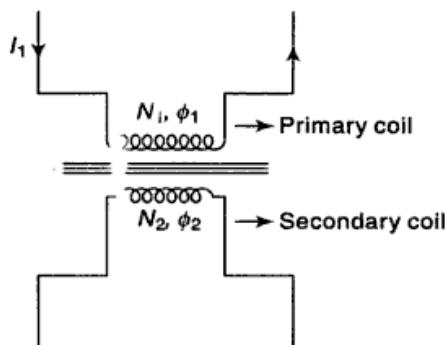


Fig. 3.13 Explanation of mutual inductance

3.9 CONCEPT OF MAGNETIC COUPLING

The coils are said to be *magnetically coupled* if either or part of the magnetic flux produced by one links that of the other. If L_1 = self-inductance of coil 1 and L_2 be the self-inductance of coil 2 and M be the mutual inductance of two coils, then $M = K\sqrt{L_1 L_2}$ where K is co-efficient of coupling. If the total flux produced by coil 1 links with the flux produced by coil 2, then $K = 1$ and $M = \sqrt{L_1 L_2}$.

On the other hand, if there is no common flux between the two coils, then they are said to be magnetically isolated. Therefore, co-efficient of coupling K between the coils =

$$\text{between the coils} = \frac{\text{'actual' mutual inductance}}{\text{maximum possible value}}$$

When the two coils are closely coupled magnetically through an iron core, K is close to unity. On the other hand, when the two coils are loosely coupled magnetically, K is equal to 0.5 or even less. In the magnetically isolated case, $K = 0$, i.e. $M = 0$.

3.12 A magnetic flux of $400 \mu \text{ Wb}$ passing through a coil of 1500 turns is reversed in 0.1 s. Determine the average value of the emf induced in the coil.

Solution

The magnetic flux has to decrease from $400 \mu \text{ Wb}$ to zero and then increase to $400 \mu \text{ Wb}$ in the reverse direction, hence the increase of flux in the original direction is $800 \mu \text{ Wb}$.

We know, average emf induced in the coil is

$$\begin{aligned}
 e &= \frac{N\phi}{t} \\
 &= \frac{1500 \times (800 \times 10^{-6})}{0.1} \\
 &= 12 \text{ V.}
 \end{aligned}$$

3.13 A coil has a self-inductance of 40 milli-henry. Determine the emf in the coil when the current in the coil

- (a) increase at the rate of 300 A
 (b) raises from 0 to 10 A in 0.05 sec.

Solution

Given (a) Self-inductance $L = 40 \times 10^{-3} \text{ H}$

$$\begin{aligned}
 E &= L \cdot \frac{dI}{dt} \quad (\text{only magnitude}) \\
 &= 40 \times 10^{-3} \times 300 = 12 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b) } L &= 40 \times 10^{-3} \text{ H} \\
 dI &= 10 - 0 = 10 \text{ A} \\
 dt &= 0.05 \text{ sec}
 \end{aligned}$$

$$\begin{aligned}
 \therefore e &= L \frac{dI}{dt} \\
 &= \frac{40 \times 10^{-3} \times 10}{0.05} = 8 \text{ V}
 \end{aligned}$$

3.14 Determine the emf induced in a coil of 4.19×10^{-4} Henry when a current of 5 A is reversed in 60 milliseconds.

Solution

Given $L = 4.19 \times 10^{-4} \text{ H}$

Also given $dI = 5 - (-5) = 10 \text{ A}$

$dt = 60 \text{ milliseconds} = 60 \times 10^{-3} \text{ sec.}$

$$\therefore \text{emf induced} = L \frac{dI}{dt} \quad (\text{only magnitude})$$

$$\begin{aligned}
 &= \frac{4.19 \times 10^{-4}}{60 \times 10^{-3}} \times 10 \\
 &= \frac{4.19}{60} \\
 &= 0.0698 \text{ V.}
 \end{aligned}$$

3.15 Two identical coils X and Y each having 1000 turns lie in parallel planes such that 60% of the flux produced by one coil links with the other. A current of 10 A in coil X produces in it a flux of 10^{-4} wb . If the current in the coil X changes from +15 A to -15 A in 0.03 seconds, what would be the magnitude of the emf induced in the coil Y?

Solution

Given $N_1 = N_2 = 1000$ turns

$$I_x = 10 \text{ A}$$

$$\phi_x = 10^{-4} \text{ Wb.}$$

The amount of flux linking with second coil $= 0.6 \times 10^{-4} \text{ Wb.}$

$$\therefore \frac{dI_x}{dt} = \frac{[15 - (-15)]}{0.03} = \frac{30}{0.03} = 1000 \text{ A/sec.}$$

We have

$$e_{My} = M \cdot \frac{dI_1}{dt} \text{ volts (ignoring -ve sign)}$$

$$\text{where } M = \frac{N_2 (\text{Amount of } \phi_1 \text{ linking with the coil } Y)}{I_1}$$

$$= \frac{1000 \times (0.6 \times 10^{-4})}{10}$$

$$= 0.6 \times 10^{-2} \text{ H}$$

$$\therefore e_{My} = 0.6 \times 10^{-2} \times 1000$$

$$= 6 \text{ volts.}$$

3.16 A square coil of 10 cm side and with 120 turns is rotated at a uniform speed of 1000 rpm about an axis at right angles to a uniform magnetic field having a flux density of 0.5 Wb/m^2 . Determine the instantaneous value of the electromotive force have the plane of the coil

- at right angles to the field
- at 30° to the field
- in the plane of the field.

Solution

We know

$$\phi = B \cdot A = 0.5 \times (10 \times 10^{-2})^2 = 5 \text{ milli-Wb}$$

$$\psi = \phi \cdot N = 5 \times 10^{-3} \times 120 = 0.6$$

$$\omega = \frac{2\pi n}{60} = \frac{2 \times \pi \times 1000}{60} = 104.719 \text{ radian/sec}$$

$$\therefore \psi = \psi_m \cos \omega t = 0.6 \cos 104.719t$$

$$\therefore e = -\frac{d\psi}{dt} = +0.6 \times 104.719 \sin 104.719t$$

$$= 62.83 \sin 104.719t \text{ volt.}$$

$$\text{(a) When } \theta = 0^\circ$$

$$e = 62.83 \sin 0^\circ = 0 \text{ V}$$

$$\text{(b) When } \theta = 90^\circ - 30^\circ = 60^\circ$$

$$e = 62.83 \sin 60^\circ = 62.83 \times \frac{\sqrt{3}}{2} = 54.412 \text{ V.}$$

$$\text{(c) When } \theta = 90^\circ$$

$$e = 62.83 \text{ V.}$$

3.10 CALCULATION OF SELF-INDUCTANCE

3.10.1 For a Circular Coil

Consider a circular coil of radius r and number of turns N . If current I passes in the coil, then magnitude field at centre of coil

$$B = \frac{\mu_0 NI}{2r}$$

the effective magnetic flux linked with this coil,

$$\phi = NBA = \frac{N(\mu_0 NI)A}{2r}$$

Since, by definition, $L = \frac{\phi}{I}$

$$\therefore L = \frac{\mu_0 N^2 A}{2r} = \frac{\mu_0 N^2 \pi r^2}{2r} \quad [\because A = \pi r^2 \text{ for a circular coil}]$$

$$\text{or,} \quad L = \frac{\mu_0 N^2 \pi r}{2} \quad (3.23)$$

3.10.2 For a Solenoid

Consider a solenoid with n number of turns per meter. Let current I flow in the windings of solenoid, then the magnetic field inside solenoid is given by

$$B = \mu_0 n I$$

the magnetic flux linked with its length l is $\phi = NBA$, where N is the total number of turns in length l of solenoid.

$$\phi = (nl)BA = (nl)(\mu_0 \cdot n \cdot I)A \quad (\because N = nl)$$

$$\text{Since,} \quad L = \frac{\phi}{I}$$

$$\therefore L = \mu_0 n^2 A l \quad (3.24)$$

$$\text{Since} \quad n = \frac{N}{l}$$

$$\therefore \text{ Self-inductance, } L = \frac{\mu_0 N^2 A}{l} \quad (3.25)$$

3.11 ENERGY STORED IN INDUCTOR

When the current in a circuit of a coil of inductance L henry increases from zero to its maximum steady value of I amperes, work has to be done against the opposing induced emf.

Let dw be the infinitesimal work done in time dt , then
 $dw = VI dt$, where V is voltage across an inductor.

Since $V = L \frac{di}{dt}$

$$\therefore dw = \left(L \frac{di}{dt} \right) \cdot I \cdot dt = LI di$$

$$\text{or } w = \int_0^I LI di = \frac{1}{2} LI^2 \text{ J.} \quad (3.26)$$

This work done is stored in the form of energy of the magnetic field in an inductor.

Also we can write $L = \frac{2w}{I^2}$ if $I = 1$ Amp, $L = 2w$, using equation (3.26)

Thus the self-inductance of a circuit is numerically equal to twice the work done against the inductance emf in establishing a circuit of 1 A in the coil. Again, from the definition of self-inductance (Ref. equation number 3.25)

$$L = \frac{\mu_o \mu_r A \cdot N^2}{l}$$

$$\text{And stored energy} = \frac{1}{2} LI^2 = \frac{1}{2} \frac{\mu_o \cdot \mu_r \cdot A \cdot N^2 \cdot I^2}{l} \text{ J}$$

$$\text{But magnetic field intensity, } H = \frac{NI}{l}$$

$$\therefore \text{Stored energy} = \frac{1}{2} \mu_o \cdot \mu_r \cdot A \cdot l \cdot \frac{N^2 I^2}{l^2} = \frac{1}{2} \mu_o \mu_r A \cdot l \cdot H^2 \text{ J}$$

Now, Al = volume of the magnetic field in m^3

$$\text{Energy stored/m}^3 = \frac{1}{2} \mu_o \cdot \mu_r \cdot H^2 \text{ J}$$

$$= \frac{1}{2} BH \text{ J} = \frac{1}{2} \cdot B \cdot \frac{B}{\mu_o \cdot \mu_r} \text{ J} [\because B = \mu_o \mu_r H]$$

$$= \frac{B^2}{2\mu_o} \quad [\because \mu_r = 1 \text{ in air}]. \quad (3.27)$$

3.12 MAGNETIC ENERGY DENSITY (U_M)

Since, $W = \frac{1}{2} LI^2$, for a solenoid

$$L = \mu_o n^2 Al \text{ and } B = \mu_o nI$$

$$\begin{aligned}\therefore W &= \frac{1}{2} (\mu_o \cdot n^2 A l) \left(\frac{B}{\mu_o n} \right)^2 \\ &= \frac{B^2}{2\mu_o} (A l)\end{aligned}\quad (3.28)$$

Again we know $\frac{W}{A l} = \frac{\text{Energy}}{\text{Volume}} = \text{Magnetic energy density (say } U_M)$

$$\therefore U_M = \frac{B^2}{2\mu_o} \text{ J.} \quad (3.29)$$

Thus we can conclude that the energy stored in magnetic field in terms of per unit volume of the magnetic material used is called the *magnetic energy density*.

3.13 COMBINATION OF INDUCTANCES

3.13.1 Dot Covention

The emf induced due to mutual inductance may either aid or oppose the emf induced due to self-inductance in a magnetic coupling circuit. It depends on the relative direction of currents, the relative modes of windings of the coils as well as the physical location, i.e. either far away or very close with respect to the other. Figure 3.14 clearly explains the sign of mutually induced emf.

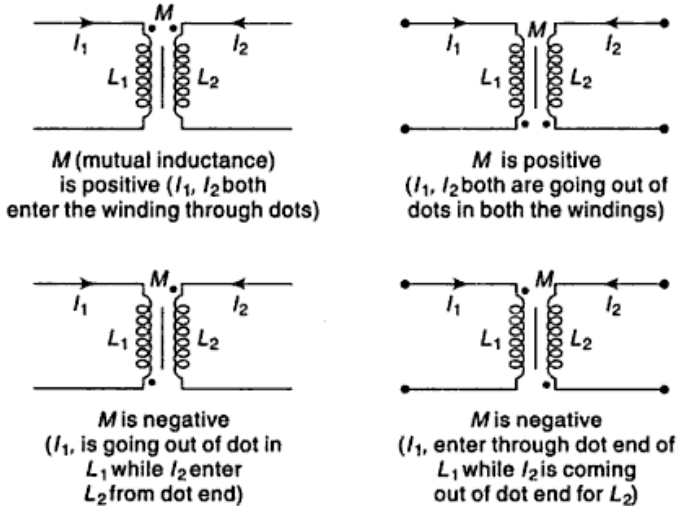


Fig. 3.14 Dot convention to determine sign of M (A dot represents the +ve polarity of the winding at any instant).

3.13.2 Inductances in Series and Parallel

Series Connection

When two inductors are coupled in series, a mutual inductance exists between them.

Figure 3.15(a) shows the connection of two inductive coils in series aiding. The flux produced by the two coils are additive in nature as per dot convention. Let L_1 be the self-inductance of the coil 1 and L_2 is the self-inductance of coil 2 and M is the mutual inductance between coil 1 and coil 2.

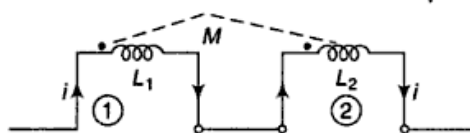


Fig. 3.15(a) Inductance in series (Cumulative coupling) (flux-aiding)

For coil 1, the self-induced emf $e_1 = -L_1 \frac{di}{dt}$ and the mutual induced emf $= -M \frac{di}{dt}$ due to change of current in coil 2.

For coil 2, self-induced emf $e_2 = -L_2 \frac{di}{dt}$ and mutually induced emf $= -M \frac{di}{dt}$ due to change of current in coil 1.

Therefore the total induced emf of the above connection can be written as

$$\begin{aligned} e &= -L_1 \frac{di}{dt} - L_2 \frac{di}{dt} - 2M \frac{di}{dt} \\ &= -(L_1 + L_2 + 2M) \frac{di}{dt} \end{aligned}$$

If (L_s) is the equivalent inductance of the coil in series then it can be expressed as

$$e = -L_s \frac{di}{dt}$$

Now comparing the above two equations, we have

$$\therefore -L_s \frac{di}{dt} = -(L_1 + L_2 + 2M) \frac{di}{dt}$$

$$\therefore L_s = L_1 + L_2 + 2M \quad \left[\because \frac{di}{dt} \neq 0 \right] \quad (3.30a)$$

Similarly, for the series opposing, from the Fig. 3.15(b) we can write

$$L_s = L_1 + L_2 - 2M \quad (3.30b)$$

If the two coils of self-inductances L_1 and L_2 having mutual inductance M are in series and are far away from each other, so that the mutual inductance between them is negligible, then the net self-inductance is

$$L_s = L_1 + L_2 \quad [\because M = 0]$$

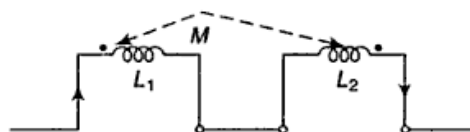


Fig. 3.15(b) Inductance in series (flux opposing) (Differential coupling)

Parallel Connection

When two coils are coupled in parallel and mutual inductance M exists, the equivalent inductance can be calculated as follows:

For Parallel Aiding The Fig. 3.16 shows the connection of parallel connection of two coils where the flux is additive as per dot convention. Using Kirchhoff's voltage law, we have

$$V = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad (3.31a)$$

also,
$$V = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \quad (3.31b)$$

From the above two equations, we can write

$$L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

Here $i = i_1 + i_2 \quad \therefore \quad i_2 = i - i_1$

Thus,
$$L_1 \frac{di_1}{dt} + M \frac{d}{dt}(i - i_1) = L_2 \frac{d}{dt}(i - i_1) + M \frac{di_1}{dt}$$

or
$$L_1 \frac{di_1}{dt} + M \frac{di}{dt} - M \frac{di_1}{dt} = L_2 \frac{di}{dt} - L_2 \frac{di_1}{dt} + M \frac{di_1}{dt}$$

i.e.
$$(L_1 + L_2 - 2M) \frac{di_1}{dt} = (L_2 - M) \frac{di}{dt}$$

$$\therefore \frac{di_1}{dt} = \frac{L_2 - M}{L_1 + L_2 - 2M} \cdot \frac{di}{dt} \quad (3.32a)$$

Similarly
$$\frac{di_2}{dt} = \frac{L_1 - M}{L_1 + L_2 - 2M} \cdot \frac{di}{dt} \quad (3.32b)$$

Using equations (3.32a) and (3.32b), we can write,

$$\begin{aligned} V &= L_1 \left(\frac{L_2 - M}{L_1 + L_2 - 2M} \right) \frac{di}{dt} + M \left(\frac{L_1 - M}{L_1 + L_2 - 2M} \right) \frac{di}{dt} \\ &= \frac{L_1 L_2 - L_1 M + L_1 M - M^2}{L_1 + L_2 - 2M} \cdot \frac{di}{dt} \\ &= \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \cdot \frac{di}{dt} \end{aligned} \quad (3.32c)$$

If L_P be the equivalent inductance of the parallel combination, it can be written as

$$V = L_P \frac{di}{dt} \quad (3.32d)$$

Comparing equation (3.32c) and (3.32d) we have

$$\begin{aligned} L_P \frac{di}{dt} &= \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \left(\frac{di}{dt} \right) \\ \therefore L_P &= \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \end{aligned} \quad (3.33a)$$

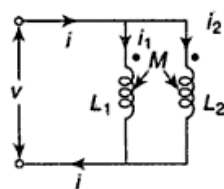


Fig. 3.16 Inductances in parallel flux aiding

Equation (3.33a) gives the required equivalent inductance for parallel connections when inductances are in the flux aiding mode.

Similarly, for inductances in parallel opposing, we can write

$$L_P = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} \quad (3.33b)$$

This is the required equivalent inductance in parallel for the flux opposing mode.

Again, if the two coils are far away from each other, $M \cong 0$ and hence

$$L_P = \frac{L_1 L_2}{L_1 + L_2} \quad (3.33c)$$

Therefore by combining parallel aiding and parallel opposing, the final expression for the equivalent inductance is

$$L_P = \frac{L_1 L_2 - M^2}{L_1 + L_2 \pm 2M} \quad (3.33d)$$

3.17 Two coils are connected in parallel as shown in Fig. 3.17. Calculate the net inductance of the connection.

Solution

The net inductance in the given circuit

$$\begin{aligned} &= \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} \\ &= \frac{0.2 \times 0.3 - (0.1)^2}{0.2 + 0.3 + 2 \times 0.1} \\ &= \frac{0.06 - 0.01}{0.7} = \frac{0.05}{0.7} = 0.0714 \text{ H.} \end{aligned}$$

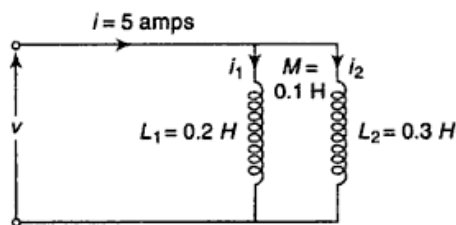


Fig. 3.17

3.18 The combined inductance of the two coils connected in series is 0.60 H and 0.40 H, depending on the relative directions of currents in the coils. If one of the coils, when isolated, has a self-inductance of 0.15 H, then find: (a) the mutual inductance, and (b) the co-efficient of coupling K .

Solution

$$\begin{aligned} L_{\text{additive}} &= L_1 + L_2 + 2M \\ 0.60 &= 0.15 + L_2 + 2M \end{aligned} \quad (i)$$

$$\begin{aligned} L_{\text{subtractive}} &= L_1 + L_2 - 2M \\ 0.40 &= 0.15 + L_2 - 2M \end{aligned} \quad (ii)$$

adding equations (i) and (ii), we have

$$1.0 = 0.3 + 2L_2$$

$$\therefore L_2 = \frac{(1.0 - 0.3)}{2} = 0.35 \text{ H}$$

Substituting this value of L_2 in equation (i),

$$0.60 = 0.15 + 0.35 + 2M$$

or

$$M = 0.05 \text{ H}$$

$$\begin{aligned}
 \text{(b) Co-efficient of coupling, } K &= \frac{M}{\sqrt{L_1 L_2}} \\
 &= \frac{0.05}{\sqrt{0.15 \times 0.35}} = 0.218 = 0.22.
 \end{aligned}$$

3.19 Pure inductors each of inductance 3 H are connected as shown in Fig. 3.18. Find the equivalent inductance of the circuit.

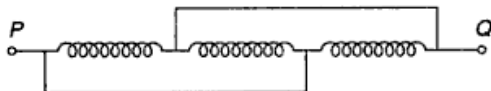


Fig. 3.18 The equivalent inductance of the circuit

Solution

Since all three are in parallel. Hence the equivalent inductance is $L/3 = 3/3 = 1$ H.

3.20 A current of 10 A when flowing through a coil of 2000 turns establishes a flux of 0.6 milliwebers. Calculate the inductance L of the coil.

Solution

Given $I = 10$ A
 $N = 2000$ turns
 $\phi = 0.6 \times 10^{-3}$ wb
 $L =$ to be calculated.

$$\begin{aligned}
 \text{We have } L &= \frac{N\phi}{I} = \frac{2000 \times 0.6 \times 10^{-3}}{10} \\
 &= 0.12 \text{ H.}
 \end{aligned}$$

3.21 Determine the inductance L of a coil of 500 turns wound on an air cored toroidal ring having a mean diameter of 300 mm. The ring has a circular cross section of diameter 50 mm.

Solution

Given $N = 500$ turns
 Mean diameter, $D = 300 \text{ mm} = 300 \times 10^{-3} \text{ m}$
 $l = \pi D = \pi \times 300 \times 10^{-3} \text{ m}$
 $= 0.942 \text{ m}$
 Cross-sectional diameter $d = 50 \text{ mm}$
 $= 50 \times 10^{-3} \text{ m}$

$$\begin{aligned}
 A &= \frac{\pi d^2}{4} = \frac{\pi \times (50 \times 10^{-3})^2}{4} \\
 &= 1.963 \times 10^{-3} \text{ m}^2.
 \end{aligned}$$

For air cored toroidal ring, $\mu_r = 1$ and $L =$ is to be calculated.

$$\text{We have, inductance } L = \frac{N^2}{\text{Reluctance}}$$

$$L = \frac{\mu_o \mu_r AN^2}{l}$$

$$= \frac{N^2}{l/\mu_o \mu_r A} = \frac{N^2}{\text{Reluctance}}$$

$$\text{where Reluctance} = \frac{l}{\mu_o \cdot \mu_r \cdot A}$$

(The concept of reluctance is explained in article 3.18 and 3.24)

Here Reluctance = $\frac{\pi \times 300 \times 10^{-3}}{4\pi \times 10^{-7} \times 1 \times 1.963 \times 10^{-4}}$

$$= 3.818 \times 10^8 \text{ AT/Wb}$$

$$\therefore L = \frac{N^2}{\text{Reluctance}} = \frac{500 \times 500}{3.818 \times 10^8}$$

$$= 0.000654 \text{ H}$$

$$= 6.54 \times 10^{-4} \text{ H.}$$

3.22 Two coils having 80 and 350 turns respectively are wound side by side on a closed iron circuit of mean length 2.5 m with a cross-sectional area of 200 cm². Calculate the mutual inductance between the coils. Consider relative permeability of iron as 2700.

Solution

Given $N_1 = 80$ turns
 $N_2 = 350$ turns
 $l = 2.5$ m
 $A = 200 \text{ cm}^2 = 200 \times 10^{-4} \text{ m}^2$
 $\mu_r = 2700$
 $\mu_o = 4\pi \times 10^{-7} \text{ H/m}$
 $M = \text{to be calculated.}$

We have $M = \frac{N_1 \cdot N_2}{\text{Reluctance}}$ [for two coils of turns N_1 and N_2]

where reluctance = $\frac{l}{\mu_o \cdot \mu_r \cdot A}$ (Ref. article 3.18)

$$= \frac{2.5}{4\pi \times 10^{-7} \times 2700 \times 200 \times 10^{-4}}$$

$$= 36860 \text{ AT/Wb}$$

$$\therefore \text{Mutual inductance } (M) = \frac{80 \times 350}{36860}$$

$$= 0.760 \text{ H.}$$

3.23 A solenoid 60 cm long and 24 cm in radius is wound with 1500 turns. Calculate:

- the inductance
- the energy stored in the magnetic field when a current of 5 A flows in the solenoid.

Solution

Given: $l = 60 \text{ cm} = 0.6 \text{ m}$, $N = 1500 \text{ turns}$, $A = \pi (0.24)^2 \text{ m}^2$
 $\mu = \mu_0 \mu_r = 4\pi \times 10^{-7} \times 1$, $I = 5 \text{ A}$.

(a) Inductance:

$$\begin{aligned} \text{We know } L &= \frac{\mu \cdot N^2 \cdot A}{l} \\ &= \frac{4\pi \times 10^{-7} \times (1500)^2 \times \pi (0.24)^2}{0.6} \\ &= 0.8534 \text{ H} \end{aligned}$$

(b) Energy stored:

$$\begin{aligned} \text{We have } W &= \frac{1}{2} LI^2 \\ &= \frac{1}{2} (0.8534) (5)^2 = 10.67 \text{ J}. \end{aligned}$$

3.24 Two coils of inductance 8 H and 10 H are connected in parallel. If their mutual inductance is 4 H, determine the equivalent inductance of the combination if (a) mutual inductance assists the self-inductance, (b) mutual inductance opposes the self-inductance.

Solution

It is given that

$$L_1 = 8 \text{ H}, L_2 = 10 \text{ H}, M = 4 \text{ H}$$

$$(a) L = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = \frac{8 \times 10 - 4^2}{8 + 10 - 2 \times 4} = \frac{80 - 16}{18 - 8} = 6.4 \text{ H}.$$

$$(b) L = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} = \frac{8 \times 10 - 4^2}{8 + 10 + 2 \times 4} = \frac{80 - 16}{26} = 2.46 \text{ H}.$$

3.25 Three coils are connected in series. Their self-inductances are L_1 , L_2 and L_3 . Each coil has a mutual inductance M with respect to the other coil. Determine the equivalent inductance of the connection. If $L_1 = L_2 = L_3 = 0.3 \text{ H}$ and $M = 0.1 \text{ H}$, calculate the equivalent inductance. Consider that the fluxes of the coil are additive in nature.

Solution

Let the current i and v_1 , v_2 , v_3 be the voltage across the three coils.

$$\therefore v_1 = L_1 \frac{di}{dt} + M \frac{di}{dt} + M \frac{di}{dt}$$

$$v_2 = L_2 \frac{di}{dt} + M \frac{di}{dt} + M \frac{di}{dt}$$

$$v_3 = L_3 \frac{di}{dt} + M \frac{di}{dt} + M \frac{di}{dt}$$

$$v = v_1 + v_2 + v_3 = (L_1 + L_2 + L_3 + 6M) \frac{di}{dt}$$

∴ Equivalent inductance = $L_1 + L_2 + L_3 + 6M$.

Now putting the values of L_1 , L_2 , L_3 and M , we have

$$\begin{aligned}\text{Equivalent inductance} &= 0.3 + 0.3 + 0.3 + 6 \times 0.1 \\ &= 0.9 + 0.6 \\ &= 1.5 \text{ H.}\end{aligned}$$

3.26 In a telephone receiver, the cross-section of the two poles is $10 \text{ cm} \times 0.2 \text{ cm}$. The flux between the poles and the diaphragm is $6 \times 10^{-6} \text{ wb}$. With what force is the diaphragm attracted to the poles? Assume $\mu_0 = 4\pi \times 10^{-7}$.

Solution

Here

$$\phi = 6 \times 10^{-6} \text{ wb}$$

$$A = 1.0 \text{ cm} \times 0.2 \text{ cm} = 0.2 \text{ cm}^2 = 2 \times 10^{-5} \text{ m}^2$$

$$B = \frac{\phi}{A} = \frac{6 \times 10^{-6}}{2 \times 10^{-5}} = 0.3 \text{ wb/m}^2.$$

∴ Force acting on the diaphragm

$$\begin{aligned}F &= \frac{B^2 A}{2\mu_0} \text{ N} \\ &= \frac{(0.3)^2 \times 2 \times 10^{-5}}{2 \times 4\pi \times 10^{-7}} = 0.7159 \text{ N.}\end{aligned}$$

3.27 Determine the force in kg necessary to separate two surfaces with 200 cm^2 of contact area, when the flux density perpendicular to the surfaces is 1.2 wb/m^2 .

Solution

Given

$$A = 200 \text{ cm}^2 = 2 \times 10^{-2} \text{ m}^2$$

and

$$B = 1.2 \text{ wb/m}^2$$

$$\begin{aligned}\therefore F &= \frac{B^2 A}{2\mu_0 \times 9.81} \text{ kg} = \frac{(1.2)^2 \times 2 \times 10^{-2}}{2 \times 4\pi \times 10^{-7} \times 9.81} \\ &= 1167.64 \text{ kg.}\end{aligned}$$

3.14 LIFTING POWER OF A MAGNET

Magnetic force is utilised in lifting magnets, operation of brakes, relays, circuit breakers, etc. All such devices have electromagnets and a steel armature. An air gap exists between the forces of the electromagnet and the armature and energy is stored in the air gap.

Let us consider two poles, north and south, as shown in Fig. 3.19.

Here, A = Area of cross-section (in m^2) of each pole

F = Force in Newtons between the poles.

Suppose one of the poles (say N-pole) is pulled apart against this attractive force through a small distance of dx meters. Then, work done in moving the S-pole against the force of attraction is $F dx$ joules. However in moving the N-pole through a small distance dx , the volume of the path is increased to $(A dx)\text{m}^3$.

Also, energy stored E in the magnetic field (air) is given by $E = \frac{B^2}{2\mu_0}$ joules/m³

i.e., Increase in stored energy = $\frac{B^2}{2\mu_0} \cdot A \cdot dx$ joules.

As we know, the increase in stored energy = work done, hence we can write $\frac{B^2}{2\mu_0} A \cdot dx = F \cdot dx$, when F is the force of attraction or lifting power of the magnet.

$$\therefore F = \frac{B^2}{2\mu_0} \text{ Newtons} = \frac{B^2 A}{2\mu_0 \times 9.81} \text{ kg}$$

and lifting power per unit area = $\frac{B^2}{2\mu_0}$ Newton/meter²

where B is the flux density in wb/m².

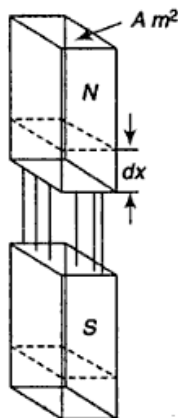


Fig. 3.19 Lifting power of magnet

3.15 CONCEPT OF MAGNETIC CIRCUIT

The path of a magnetic flux is known as magnetic circuit. Similarly, the flow of magnetic flux is almost analogous to the flow of electric current in an electric circuit. In fact, the laws of magnetic circuit are almost similar (but not exactly same) to those electric circuits. It is known to us that to carry electric current in an electric circuit, usually aluminium or copper wires are used because the resistance of these materials is comparatively much lower than other materials. Similarly, to carry magnetic flux, iron or soft steel circuits are used as "opposition" of these materials to flux is low in comparison with other materials.

The study of magnetic circuit concepts is essential in the design analysis and application of electromagnetic devices like transformers, electromagnetic relays, electrical machines, etc.

3.16 CONCEPT OF MAGNETO-MOTIVE FORCE (MMF)

It is the amount of work done (in joules) required to carry a unit magnetic pole once through the entire magnetic field. In fact it is a kind of magnetic flux through a magnetic circuit and is called the *magneto motive force*. It's unit being ampere-turns (AT), it is actually measured by the product of number of turns N in the coil of a magnetic circuit, and the current I in amperes required to produce the magneto motive force.

Thus, $F(\text{MMF}) = NI$ AT/m

Where N = number of turns in the coil and I = current through the coil (in Amps). It should be noted that through the unit of MMF is ampere turn (AT), it's dimension is taken as ampere since N is dimensionless.

3.17 MAGNETIC FIELD INTENSITY

The MMF for unit length (along the path of magnetic flux) is defined as the *magnetic field intensity* and it is designated by the symbol H . The magnetic field intensity thus can be expressed as

$$H = \frac{\text{Magneto motive force}}{\text{Mean length of the magnetic path}}$$

$$\text{i.e.} \quad H = \frac{F}{l} = \frac{NI}{l} \text{ AT/m.} \quad (3.34)$$

where l is the *mean length* of the magnetic circuit in meters. Magnetic field intensity is also termed as *magnetising force* or *magnetic field strength*.

3.18 CONCEPT OF RELUCTANCE

It is designated by the symbol " S " and is analogous to resistance of an electric circuit. Flux in a magnetic circuit is limited by *reluctance*. Thus, reluctance S is a measure of the opposition offered by a magnetic circuit to the establishment of magnetic flux.

It is directly proportional to the length and inversely proportional to the area of cross section of the magnetic path.

$$S \propto \frac{l}{a}$$

$$\therefore S = \frac{l}{\mu_o \cdot \mu_r \cdot a} \quad (3.35)$$

The unit of reluctance is AT/Wb.

For air, vacuum and non-magnetic materials $\mu_r = 1$

$$\therefore S = \frac{l}{\mu_o \cdot a} \quad (3.36)$$

the reciprocal of reluctance is called the "permeance". It is designated by the symbol A .

$$\therefore \text{Permeance (= } A) = \frac{1}{S} \text{ wb/A [or henry (H)]} \quad (3.37)$$

Concept of magnetic reluctance is based on the following assumptions:

- B-H curve of the magnetic core is linear
- Leakage flux is of negligible order.

3.19 PERMEABILITY AND RELATIVE PERMEABILITY

Permeability of a material μ is defined as *its conducting power for magnetic lines of force*. It is the ratio of the flux density B produced in a material to the magnetic field strength H , i.e. $\mu = \frac{B}{H}$.

Permeability of free space or vacuum is minimum and its value in SI units is $4\pi \times 10^{-7}$ henry/meter.

It may be noted here that flux density (B) is usually expressed as flux (Wb) per unit area (sq. m) and its unit in SI system is Tesla (T).

$$\therefore 1 \text{ T} = 1 \text{ Wb/m}^2$$

Relative Permeability

When the magneto motive force is applied to a ferromagnetic material, the flux produced is very large compared with that in air, free space (vacuum) or a non-magnetic material. *The ratio of the flux density produced in material to the flux density produced in air or a non-negative material by the same magnetic field intensity is called the relative permeability of that material.* It is designated by the symbol μ_r . The relative permeability of vacuum is taken as unity.

Thus, permeability of any medium,

$$\begin{aligned}\mu &= \text{Absolute permeability of air} \times \text{Relative permeability} \\ &= \mu_o \cdot \mu_r = 4\pi \times 10^{-7} \times \mu_r \text{ Wb/AT.}\end{aligned}$$

(with special nickel-iron alloys the value of μ_r may be as high as 2×10^5 whereas for most commonly used magnetic materials the values of μ_r is much smaller).

3.28 A coil of 600 turns and of resistance of 20Ω is wound uniformly over a steel ring of mean circumference 30 cm and cross-sectional area 9 cm^2 . It is connected to a supply of 20 V (DC). If the relative permeability of the ring is 1,600 find (a) the reluctance, (b) the magnetic field intensity, (c) the mmf, and (d) the flux.

Solution

Here $N = 600$ turns, resistance of the coil is 20Ω , $l = 30 \text{ cm} = 0.3 \text{ m}$, $A = 9 \text{ cm}^2 = 9 \times 10^{-4} \text{ m}^2$, relative permeability $\mu_r = 1600$ and $\mu_o = 4\pi \times 10^{-7}$.

$$\begin{aligned}\text{(a) Reluctance } S &= \frac{l}{\mu_o \cdot \mu_r \cdot a} = \frac{0.3}{4\pi \times 10^{-7} \times 1600 \times 9 \times 10^{-4}} \\ &= 1.657 \times 10^5 \text{ At/wb}\end{aligned}$$

(b) The magnetic field intensity

$$H = \left(\frac{NI}{l} \right) = \frac{600 \times 1}{0.3} = 2000 \text{ AT}$$

$$\left(\text{where } I = \frac{V}{\text{resistance of the coil}} = \frac{20}{20} = 1 \text{ Amp} \right)$$

$$\text{(c) MMF} = (NI) = 600 \times 1 = 600 \text{ AT}$$

$$\begin{aligned}\text{(d) Flux}(\phi) &= \frac{\text{mmf}}{\text{reluctance}} = \frac{NI}{S} = \frac{600 \times 1}{1.657 \times 10^5} = \frac{600}{1.65 \times 10^5} \\ &= 3.62 \times 10^{-3} \text{ wb} = 3.62 \text{ m Wb.}\end{aligned}$$

.....

3.29 What is the value of the net mmf acting in the magnetic circuit shown in Fig. 3.20.

Solution

Net mmf acting in the magnetic circuit = mmf of all the three coils = $N_1 I_1 + N_2 I_2 + N_3 I_3$
 $= (10 \times 2 + 50 \times 1 + 300 \times 1) \text{ AT} = 370 \text{ AT}.$

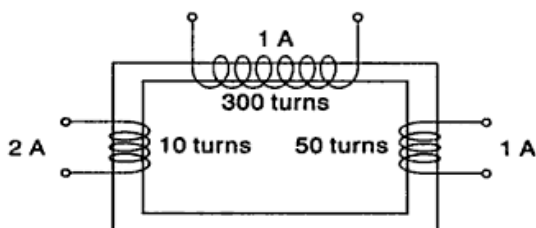


Fig. 3.20

[It may be observed here that since the flux in all the coils are additive within the core, hence AT's are additive.]

3.30 A mild-steel ring having a cross-sectional area of 400 mm^2 and a mean circumference of 400 mm has a coil of 200 turns wound uniformly around it. [given $\mu_r = 300$].

Determine:

- the reluctance S of the ring,
- the current required to produce a flux of $800 \mu \text{ Wb}$ in the ring.

Solution

(a) Flux density B in the ring is $\frac{800 \times 10^{-6}}{400 \times 10^{-6}} = 2 \text{ Wb/m}^2$.

\therefore The reluctance S of the ring is $\frac{0.4}{300 \times 4\pi \times 10^{-7} \times 0.4 \times 10^{-3}} = 2.65 \times 10^6 \text{ A/Wb}$

Again we know $\phi = \frac{\text{mmf}}{\text{Reluctance}}$

$800 \times 10^{-6} = \frac{\text{mmf}}{\text{Reluctance}}$

$\therefore \text{mmf} = 800 \times 10^{-6} \times 2.65 \times 10^6$
 $= 2.122 \times 10^3 \text{ AT}$

and magnetizing current is $\frac{\text{mmf}}{\text{No. of turns}} = \frac{2.122 \times 10^3}{200}$
 $= 10.6 \text{ A.}$

3.31 A magnetic circuit having 150 turns coils and the cross-sectional area and length of the magnetic circuit are $5 \times 10^{-4} \text{ m}^2$ and $25 \times 10^{-2} \text{ m}$ respectively. Determine H and the relative permeability μ_r of the core when the current is 2 A and the total flux is $0.3 \times 10^{-3} \text{ Wb}$.

Solution

When

$I = 2 \text{ A}$

$\text{mmf} = NI = 150 \times 2 = 300 \text{ A/T}$

$\therefore H = \frac{NI}{l} = \frac{300}{25 \times 10^{-2}} = 1200 \text{ A/m}$

$B = \frac{\text{flux } (\phi)}{\text{area } (a)} = \frac{0.3 \times 10^{-3}}{5 \times 10^{-4}} = 0.6 \text{ T}$

$$\mu = \frac{B}{H} = \frac{0.6}{1200} = 500.00 \times 10^{-6} \text{ H/m}$$

$$\mu_r = \frac{\mu}{\mu_o} = \frac{500.00 \times 10^{-6}}{4\pi \times 10^{-7}} = 3.9788 \times 10^2 = 397.88.$$

.....

3.32 An air cored coil has 500 turns. The mean length of magnetic flux path is 50 cm and the area of cross-section is $5 \times 10^{-4} \text{ m}^2$. If the exciting current is 5 A, determine (a) H (b) the flux density and (c) the flux (ϕ).

Solution

$$\text{mmf} = NI = 500 \times 5 = 2500 \text{ A}$$

Given, $l = 50 \text{ cm} = 0.5 \text{ m}$
 $a = 5 \times 10^{-4} \text{ m}^2$

$$(a) \therefore H = \frac{NI}{l} = \frac{2500}{0.5} = 5000.00 \text{ A/m.}$$

$$(b) B = \text{flux density} = \mu \cdot H = \mu_r \cdot \mu_o \cdot H$$

$$= \mu_o \cdot H \quad [\because \mu_r = 1]$$

$$= 4\pi \times 10^{-7} \times 5000.00$$

$$= 6.283 \times 10^{-3} \text{ T.}$$

$$(c) \text{Flux } (\phi) = B \times a = 6.283 \times 10^{-3} \times 5 \times 10^{-4}$$

$$= 3.1415 \times 10^{-6} \text{ Wb.}$$

.....

3.33 Two identical co-axial circular loops carry a current I each circulating in the same direction. If the loops approach each other, the current in each decreases. Justify the statement.

Solution

When the loops approach each other, the field becomes strong, which should not be allowed in accordance with Lenz's law. So, the current in both should be in such a way that the field decreases and hence I decreases.

.....

3.34 An iron ring 10 cm mean circumference is made from a round iron of cross-section 10^{-3} m^2 . Its relative permeability is 500. If it is wound with 250 turns, what current will be required to produce a flux of $2 \times 10^{-3} \text{ Wb}$?

Solution

The lines of magnetic flux follow the circular path of the iron so that

$$l = 100 \text{ cm} = 1 \text{ m}$$

$$a(\text{area}) = 10^{-3} \text{ m}^2$$

$$\therefore \text{Reluctance } S = \frac{1}{\mu_r \mu_o a} = \frac{1}{(500 \times 4\pi \times 10^{-7} \times 10^{-3})}$$

$$= 1.59 \times 10^6 \text{ A/Wb.}$$

Given Flux (ϕ) = $2 \times 10^{-3} \text{ Wb}$

$$\therefore H = \phi \cdot S = 2 \times 10^{-3} \times 1.59 \times 10^6$$

$$= 3.1847 \times 10^3 \text{ AT.}$$

As we know

$$H = NI$$

$$\begin{aligned}\therefore I &= \frac{H}{N} = \frac{3.1847 \times 10^3}{250} \\ &= 12.738 \text{ A.}\end{aligned}$$

3.35 An air gap 1.1 mm long and 40 sq. cm in cross-section exists in a magnetic circuit. Determine (a) Reluctance S of the air-gap, and (b) mmf required to create a flux of 10×10^{-4} Wb in the air gap.

Solution

$$\begin{aligned}\text{(a) Reluctance } (S) &= \frac{l}{\mu_r \cdot \mu_o a} = \frac{l}{m_o \cdot a} \quad [\because \mu_r = 1] \\ &= \frac{1.1 \times 10^{-3}}{4\pi \times 10^{-7} \times 40 \times 10^{-4}} = 2.1885 \times 10^5 \text{ A/m}\end{aligned}$$

$$\begin{aligned}\text{(b) Since } \phi &= 10 \times 10^{-4} \text{ Wb (given)} \\ \therefore \text{mmf} &= \text{flux} \times \text{reluctance} \\ &= 10 \times 10^{-4} \times 2.1885 \times 10^5 \\ &= 218.85 \text{ AT.}\end{aligned}$$

3.36 An iron ring of mean length 110 cm with an air gap of 1.5 mm has a winding of 600 turns. The relative permeability of iron is 600. When a current of 4 A flows in the winding, calculate the flux density B . Do not consider fringing.

Solution

$$\begin{aligned}\text{Given that } l_i &= 110 \text{ cm} - 0.15 \text{ cm} \\ &= 109.85 \text{ cm} \\ &= 1.0985 \text{ m} \\ l_g &= 1.5 \text{ mm} = 1.5 \times 10^{-3} \text{ m.} \\ N &= 600 \text{ turns, } \mu_r = 600 \text{ (given)} \\ I &= 4 \text{ A}\end{aligned}$$

$$\begin{aligned}\therefore \text{Flux density } B &= \frac{\mu_o \cdot NI \cdot \mu_r}{l_i} + \frac{m_o NI \cdot 1}{l_g} \\ &= \mu_o NI \left(\frac{\mu_r}{l_i} + \frac{1}{l_g} \right) \\ &= 4\pi \times 10^{-7} \times 600 \times 4 \times \left[\frac{600}{1.0985} + \frac{1}{1.5 \times 10^{-3}} \right] \text{ Wb/m}^2 \\ &= 3.0159 \times 10^{-3} \times (5.46 \times 10^2 + 6.666 \times 10^2) \\ &= 3.657 \text{ Wb/m}^2.\end{aligned}$$

3.20 DEFINITION OF AMPERE

Consider two parallel wires separated by 1 m in space carrying a current of 1 A each, then $I_1 = I_2 = 1$ A and $d = 1$ m. From the expression of magneto motive

force developed between two parallel conductors, we have $dF/dl = 2 \times 10^{-7}$ Newton per meter.

This is used to formally define the unit 'ampere' of electric current.

Therefore, ampere is defined as the current, which when flowing in each of the two infinitely long parallel wires (conductors) of negligible cross-section and placed 1 meter apart in vacuum produces on each wire a force of 2×10^{-7} Newton per meter length.

3.21 B-H CHARACTERISTICS

The graph between the flux density B and field intensity H of a magnetic material is called B - H or familiar magnetization curve. Figure 3.21 shows a typical B - H curve for an iron specimen. As seen from the curve it can be divided into four distinct regions OA , AB_1 , B_1C and the region beyond C .

The slope of the B - H curve for iron (Fig. 3.21) can be explained as follows:

- In the region OA (in step region), magnetic field strength H (another name is magnetizing force) is too weak to cause any appreciable alignment of domains (or elementary magnets). Consequently, the increase in flux density B is small. In the neighbourhood of the origin the graph is a straight line through the origin, and the slope gives the initial permeability.
- In the region AB_1 , more and more domains get aligned as H increases, consequently, B increases almost linearly with H .
- In the region B_1C only a few domains are left unaligned, consequently, the increase in B with H is very small.
- Beyond C , i.e. beyond the knee zone, no more domains are left unaligned and the iron material is said to be magnetically saturated. This upper portion of the curve is represented with fair accuracy by Frohlich's equation

$$B_S = B - \mu_0 H = \frac{H}{a + bH}$$

$$\therefore \frac{1}{B_S} = \frac{a + bH}{H} = \frac{a}{H} + b$$

where (a) is a hardness constant while $\left(b = \frac{1}{B_S}\right)$. Here B_S is the saturation flux density.

A magnetic material is said to be magnetically saturated when it fails to attain a still higher degree of magnetization, even when the magnetizing power is increased enormously. The slope of the curve beyond C shows that the increase in

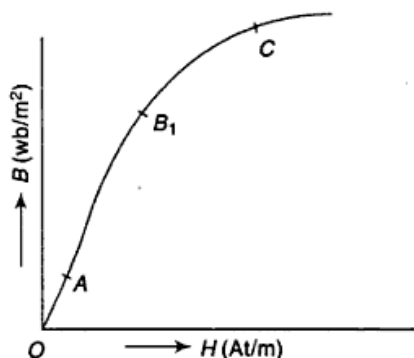


Fig. 3.21 B - H Curve for an iron sample

B with increase in H is nominal. This point C is called the *point of saturation* for the material.

The slope of the B - H curve at any point E is given by $\tan \theta = B/H$, again $B = \mu_r \mu_0 H$;

$$\mu_r H; \mu_r = 1/\mu_0 \cdot \tan \theta \left[\text{since } \frac{B}{H} = \tan \theta \right]$$

Thus, (μ_r) is proportional to the slope of the B - H curve at any point. Starting from a definite value at the origin, the slope increases as B increases until it becomes a maximum. It then gradually decreases as B increases further. The slope becomes almost zero in the saturation region when the curve becomes almost horizontal. The B - H curve shows that the permeability μ_r of a magnetic material changes with the flux density B . It is important to note that the lesser the impurities like carbon, sulphur and phosphorus in iron (the magnetic material) higher is its permeability.

Importance of B - H curve

- It helps in selecting the magnetic material for a specific application.
- It helps in making practical magnetic calculations in the design or analysis of the magnetic circuits.

3.22 FERROMAGNETIC MATERIALS

Ferromagnetism, characterised by the strong attraction or repulsion of one magnetised body by another. In fact, in some materials, the permanent atomic magnetic moments have a strong tendency to align themselves even without any external field. These materials are called *ferromagnetic materials* and permanent magnets are made from them. The force between the neighbouring atoms, responsible for their alignment, and it can only be explained on the basis of Bohr's theory of atomic structure.

According to this theory, the electrons revolve around the nucleus in fixed orbits. Since these electrons are in motion they constitute electric currents. These currents produce magnetic fields called *orbital magnetic fields*. In addition to this, each electron spins on its axis as it revolves in an orbit. (the spin of an electron is similar to the spin of the earth). A spinning electron has a charge in motion and, therefore, constitutes an electric current. This current produces a magnetic field called the *spin magnetic field*.

For an individual atom these fields are very weak. Strong magnetic fields can be produced if the atoms are grouped in a material in such a way that their orbital and spin fields reinforce one another. In ferromagnetic materials there is an appreciable interaction between neighbouring atoms. Atoms do not act singly but in groups called *domains*. Each domain contains between 10^9 and 10^{20} atoms. If a magnetic field is applied, the domains which are aligned along the direction of the field grow in size and those opposite to it get reduced. Also, domains may orient themselves in favour of the applied field. Consequently the resultant magnetic flux density inside the material is much greater than the flux density of the applied field. Examples of ferromagnetic materials are iron, cobalt and nickel but there are many ferromagnetic alloys, some of which do not even possess iron as one of their components. The ferromagnetic materials are all solids.

3.23 TYPES OF MAGNETIC MATERIALS

From an engineering point of view, magnetic materials can be broadly classified into two groups, namely:

(a) **Soft Magnetic Materials** i.e. soft iron (3.5 to 4.5% silicon content) and are used in transformers, electric machines and taperecorder tapes. Their magnetization can be changed rapidly. Its susceptibility, permeability and retentivity are greater while coercivity and hysteresis loss per cycle are smaller than those of steel. These possess a uniform structure (i.e. well-aligned crystal grains).

(b) **Hard Magnetic Materials** like steel or alloy alnico (Al + Ni + Co) are used for permanent magnets, coercivity and curie temperature for these materials are high and their retentivity is low. Their hysteresis loops are generally characterized by a broad hysteresis loop of large area compared to soft magnetic materials. Its demagnetization takes place with difficulty.

3.24 MAGNETIC CIRCUIT LAWS

The path of the magnetic flux is called the magnetic circuit. Just as the flow of electric current in an electric circuit necessitates the presence of an emf, so the establishment of a magnetic flux requires the presence of a mmf. In fact there is a close mathematical analogy between magnetic and d.c. resistive circuits. For a d.c. resistive circuits, Ohm's law relationship is

$$I = \frac{\text{e.m.f.}}{\text{resistance}} = \frac{V}{R}, \quad \text{also} \quad R = \rho \cdot \frac{l}{a}; \quad \rho \cdot \frac{1}{\sigma}$$

where σ is the conductivity.

For a magnetic circuit, magnetic flux ϕ is equal to mmf divided by reluctance,

$$\text{i.e. } \phi = \frac{\text{mmf}}{\text{reluctance}} = \frac{F}{S} \quad (\text{in symbols}) \quad (3.38)$$

Again we know for electric circuits $R = \rho \cdot \frac{l}{a}$ and for magnetic circuits

$$S = \frac{1}{\mu_o \cdot \mu_r} \cdot \frac{l}{a}$$

Therefore the definition of reluctance S is obtained from the above analogy. Reluctivity is *specific reluctance* and is comparable to resistivity ρ which is *specific resistance*.

Again ϕ can be written as from the equation 3.38

$$\text{Flux} = \phi = \frac{\text{mmf}}{\text{reluctance}} = \frac{AT}{\frac{1}{\mu_o \cdot \mu_r} \cdot \frac{l}{a}}$$

$$\therefore AT = \frac{\phi}{a} \cdot \frac{l}{\mu_o \cdot \mu_r} = \frac{B \cdot l}{\mu_o \cdot \mu_r} = H \times l \quad (3.39)$$

= field strength of the particular magnetic path \times length
of this particular magnetic path.

Therefore by analogy, σ the conductivity of the conductor is equal to the $(\mu_o \cdot \mu_r)$ in the magnetic circuit.

No name is in common use for the unit of reluctance; it is evidently measured in ampere-turns per weber of magnetic flux in the circuit.

By analogy, the laws of resistance in series and parallel also hold good for reluctances in a composite magnetic circuit.

In case of a composite electric circuit we have for series connected conductors

$$R_{\text{Total}} = R_1 + R_2 + R_3 + \dots + R_n$$

Similarly, with a composite magnetic circuit, we have to substitute S for R .

$$\text{i.e. } S_{\text{Total}} = S_1 + S_2 + S_3 + \dots + S_n \quad (3.40)$$

Again in case of parallel magnetic circuit, the same mmf is applied to each of the parallel paths and the total flux divides between paths in inverse proportion to their reluctances.

$$\phi = \phi_1 + \phi_2 + \phi_3 + \dots + \phi_n$$

The total reluctance S_{Total} of a number of reluctances in parallel is given by

$$\frac{1}{S_{\text{Total}}} = \frac{1}{S_1} + \frac{1}{S_2} + \frac{1}{S_3} + \dots + \frac{1}{S_n} \quad (3.41)$$

Similarly, *permeances* (reciprocal of reluctances) in series and parallel obey the same rules as electrical conductances.

3.25 COMPARISON BETWEEN ELECTRIC AND MAGNETIC CIRCUITS

1.

Basic Model

The toroidal copper ring (Fig. 3.22) is assumed open by an infinitesimal amount with the ends connected to a battery.

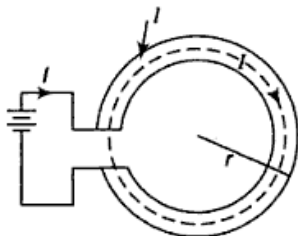


Fig. 3.22 (a)

The toroidal iron ring is assumed wound with N turns of wire with a current i flowing through it. The magneto motive force creates the flux ϕ .

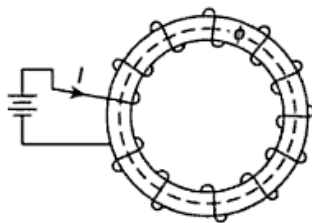




Fig. 3.22 (b)

2.

Driving Forces

Applied battery voltage is E or V

Applied Ampere turns is AT or NI

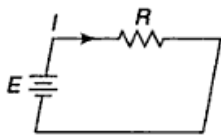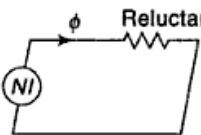3. Response	
<p>Current = $\frac{\text{Driving force}}{\text{Electric resistance}}$</p> <p>$\therefore I = \frac{E}{R}$</p>	<p>Flux = $\frac{\text{Driving force}}{\text{Magnetic resistance}}$</p> <p>$= \frac{AT}{R}$</p> <p>where $R = \frac{l}{a \cdot \mu_o \cdot \mu_r} \text{ AT/Wb}$</p> <p>where a = area of magnetic path</p>
4. Impedance	
<p>Resistance $R = \rho \times \frac{l}{a}$, here $l = 2\pi r$ = mean length of turn of the toroid and a is the toroidal cross-section</p>	<p>Reluctance ($= R$) = $\frac{l}{\mu_o \mu_r a} = \frac{l}{\mu \cdot a}$</p> <p>where $l = 2\pi r$ = mean length of turn of the toroid and a is the toroidal cross-sectional area.</p>
5. Equivalent Circuit	
<p>Here electromotive force E is the driving force and electric current flows through the circuit.</p>  <p>Electrical circuit</p> <p>$E = I.R$</p> <p>Fig. 3.23 (a)</p>	<p>Here electromotive force is the driving force and magnetic flux does not flow and it only links with the coil.</p>  <p>Magnetic circuit</p> <p>$AT = NI = \phi \cdot \text{reluctance}$</p> <p>Fig. 3.23 (b)</p>
6. Field Intensity	
<p>Electric field intensity: with the application of the voltage E to the homogeneous copper toroid, an electric potential gradient ϵ produced within the material and is given by</p> $\epsilon = \frac{E}{l} = \frac{E}{2\pi n} \text{ V/m}$ <p>This electric field must occur in a closed loop path if it is to be maintained. If then follows the closed line integral of ϵ is equal to the battery voltage E. Thus</p> $\oint \epsilon \times dl = E$	<p>Magnetic field intensity: when a magnetomotive force is applied to the homogeneous iron toroid, there is produced within the material a magnetic potential gradient given by</p> $H = \frac{NI}{l} = \frac{NI}{2\pi r} \text{ AT/m}$ <p>As already pointed out in connection with Ampere's circuited law, the closed line integral of H equals the enclosed magnetomotive force. Thus</p> $\oint H \times dl = NI$

7. Voltage drop	mmf drop
Voltage drop is given $V = I \times R$ where R is the resistance of the copper toroid between the two points.	$NI = \phi$. Reluctance where R is the reluctance of the iron toroid between the points.
8. Current density	Flux density
Current density is the amount of ampere per unit area = $\frac{\text{Amp.}}{m^2} = \frac{I}{a}$	Flux density is expressed as webers per unit area i.e. $\frac{Wb}{m^2} = \frac{\phi}{a}$.

3.26 DISTINCTION BETWEEN MAGNETIC AND ELECTRIC CIRCUITS

1. In an electric circuit current does not flow in air, unless the dielectric strength between the current-carrying conductor and nearest earth fails but flux in a magnetic circuit can flow in air.
2. Current flows (actual flow of electrons) in an electric circuit but flux does not flow because magnetic flux lines are imaginary.
3. Based on property, some materials act as insulators and some as conductors but there is no such material as 'insulators' to magnetic circuits.
4. The resistance in electric circuit changes with temperature but at constant ampere turns (AT), reluctance does not change with temperature.
5. The electric current can be confined to flow in an accurately defined path but there is no good magnetic insulator to confine all the magnetic flux to one prescribed path in a magnetic circuit. There is always some leakage flux.

3.37 An iron ring has a mean circumference of 80 cm and having cross-sectional area of 5 cm^2 and having coil of 150 turns. Using the following data, calculate the existing current for a flux of $6.4 \times 10^{-4} \text{ Wb}$. Also calculate the relative permeability (μ_r).

$B \text{ (Wb/m}^2\text{)}$: 0.9	1.1	1.2	1.3
$H \text{ (A/m)}$: 260	450	600	820

Solution

It is given that $\phi = 6.4 \times 10^{-4} \text{ Wb}$

$$\therefore \text{flux density } B = \frac{\phi}{\text{area}} = \frac{6.4 \times 10^{-4}}{5 \times 10^{-4}} = 1.28 \text{ Wb/m}^2$$

Assuming B-H curve to be linear in the range from 1.2 to 1.3 Wb/m^2 ,

$$H = 600 + \frac{820 - 600}{1.3 - 1.2} \times (1.28 - 1.2)$$

$$= 776 \text{ A/m.}$$

$$\therefore \text{mmf} = 776 \times \frac{80}{100} = 620.8 \text{ A}$$

$$\therefore I = \frac{620.8}{150.0} = 4.138 \text{ A}$$

We know $B = \mu \cdot H = \mu_o \cdot \mu_r \cdot H$

$$\therefore \mu_r = \frac{B}{\mu_o \cdot H} = \frac{1.28}{4\pi \times 10^{-7} \times 776} = 1312.089$$

.....

3.38 In the magnetic circuit shown in Fig. 3.24, the cross-sectional area of limbs Q and R are 0.01 m^2 and 0.02 m^2 respectively and the lengths of air-gap are 1.1 mm and 2.1 mm respectively, are cut in the limbs Q and R . If the magnetic medium can be assumed to have infinite permeability and the flux in the limb is 1.5 Wb , calculate the flux in the limb P .

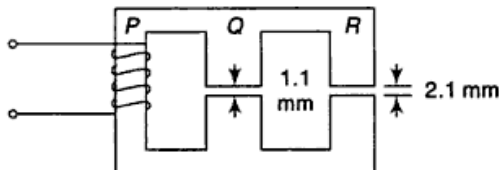


Fig. 3.24 Magnetic circuit of Ex. 3.38

Solution

It is given that

Area of cross-section of limb $Q = 0.01 \text{ m}^2$

Area of cross-section of limb $R = 0.02 \text{ m}^2$

Length of air-gap = 1.1 mm for limb Q and 2.1 mm for limb R

Flux in limb $Q = 1.5 \text{ Wb}$

As because the permeability of the magnetic medium is infinity, reluctance of the given iron path is zero. The electrical equivalent is shown in Fig. 3.25.

Now if we assume S_1 is the reluctance of air-gap of limb Q and S_2 is the reluctance of the air-gap of limb R respectively. Let ϕ_1 is the flux across the air-gap of limb Q and ϕ_2 is the flux across the air-gap of limb R .

$$\therefore S_1 \times \phi_1 = S_2 \times \phi_2$$

$$\frac{l_1}{\mu_o \times a_1} \times \phi_1 = \frac{l_2}{\mu_o \times a_2} \times \phi_2$$

$$\begin{aligned} \therefore \phi_2 &= \frac{a_2}{a_1} \times \frac{l_1}{l_2} \times \phi_1 \\ &= \frac{0.02}{0.01} \times \frac{1.1}{2.1} \times 1.5 \\ &= 1.5714 \text{ Wb.} \end{aligned}$$

$$\begin{aligned} \therefore \text{Flux in the limb } P &= \phi_1 + \phi_2 \\ &= 1.5 + 1.5714 = 3.0714 \text{ Wb.} \end{aligned}$$

.....

3.39 A ring, made of steel has a rectangular cross-sectional area. The outer diameter of the ring is 25 cm while the inner diameter is 20 cm , the thickness being 2 cm . The ring has a winding of 500 turns and when carrying a current of 3 A , produces a flux density of 1.2 T in the air gap produced when the ring is cut to have an air gap of 1 mm length (Fig. 3.26). Find (a) the magnetic field intensity of the steel ring and in the air gap,

(b) relative permeability of the magnetic material, (c) total reluctance of the magnetic circuit, (d) inductance of the coil and (e) emf induced in the coil when the coil carries a current of $i_{(ac)} = 5 \sin 314 t$.

Solution

$$NI = 500 \times 3 = 1500 \text{ AT}$$

$$B_{\text{steel}} = B_{\text{gap}} = 1.2 \text{ T}$$

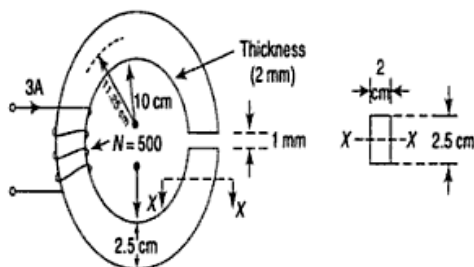


Fig. 3.26

$$(a) \therefore H_{\text{gap}} = \frac{1.2}{4\pi \times 10^{-7}} = 9.55 \times 10^5 \text{ AT/m}$$

$$\text{Since } NI = H_{\text{gap}} \times l_g + H_{\text{core}} \times l_{\text{core}},$$

$$\text{where } l_{\text{gap}} (\text{mean length of gap}) = 1 \text{ mm} = 1 \times 10^{-3} \text{ m},$$

$$\begin{aligned} l_{\text{core}} &= 2\pi \times \left(10 + \frac{2.5}{2}\right) = (2\pi \times 11.25) \text{ cm} \\ &= 2\pi \times 11.25 \times 10^{-2} \text{ m}. \end{aligned}$$

We can write,

$$1500 = 9.55 \times 10^5 \times 10^{-3} + H_{\text{core}} \times 2\pi \times 11.25 \times 10^{-2}$$

$$\text{i.e. } H_{\text{core}} = 771.20 \text{ AT/m}.$$

$$(b) \text{ Also, } H_{\text{core}} = \frac{B_{\text{core}}}{\mu_0 \mu_r}; \therefore \mu_r = \frac{1.2}{4\pi \times 10^{-7} \times 771.20} = 1238.2$$

$$\begin{aligned} (c) S &= S_1 + S_2 = \frac{1 \times 10^{-3}}{4\pi \times 10^{-7} \times 2 \times 2.5 \times 10^{-4}} \\ &\quad + \frac{2\pi \times 11.25 \times 10^{-2}}{4\pi \times 10^{-7} \times 1238.2 \times 2 \times 2.5 \times 10^{-4}} \\ &= 2.5 \times 10^6 \text{ AT/Wb} \end{aligned}$$

$$(d) L = \frac{N\phi}{I} = \frac{500 \times (B \times a)}{3} = \frac{500 \times (1.2 \times 2.5 \times 2 \times 10^{-4})}{3} = 0.1 \text{ H}$$

$$\begin{aligned} (e) E &= L \frac{di}{dt} = 0.1 \times \frac{d}{dt} (5 \sin 314 t) = 0.5 \frac{d}{dt} \sin(314 t) \\ &= 157 \cos 314 t. \end{aligned}$$

.....

3.40 An iron ring of circular cross-section of $5 \times 10^{-4} \text{ m}^2$ has a mean circumference of 2 m. It has a saw-cut of $2 \times 10^{-3} \text{ m}$ length and is wound with 800 turns of wire. Determine the exciting current when the flux in the air gap is $0.5 \times 10^{-3} \text{ Wb}$. [given: μ_r of iron = 600 and leakage factor is 1.2] Assume areas of air gap and iron are same.

Solution

The flux linking with the iron ring is

$$\begin{aligned} \phi_{\text{iron}} &= \phi_{\text{air-gap}} \times \text{Leakage factor} \\ &= 0.5 \times 10^{-3} \times 1.2 \\ &= 0.6 \times 10^{-3} \text{ Wb}. \end{aligned}$$

[As the leakage factor is given as 1.2]

Again we know,

Ampere turns required = NI

$$= \left[\frac{\phi_{\text{iron}} \times l_{\text{iron}}}{\mu_r \times \mu_o \text{ of iron} \times \text{area}} + \frac{\phi_{\text{air-gap}} \times l_{\text{air}}}{\mu_o \text{ of air} \times \text{area}} \right] \quad [\because \mu_r \text{ for air} = 1]$$

$$\therefore I = \frac{1}{800} \left[\frac{0.6 \times 10^{-3} \times 2}{4 \times \pi \times 10^{-7} \times 600 \times 5 \times 10^{-4}} + \frac{0.5 \times 10^{-3} \times 2 \times 10^{-3}}{4\pi \times 10^{-7} \times 5 \times 10^{-4}} \right]$$

$$= 5.95 \text{ A.}$$

3.41 An iron ring of 100 cm mean circumference is made from round iron of cross-section 10 cm^2 . Its relative permeability is 500. Now a saw-cut of 2 mm wide has been made on it. It is wound with 200 turns. Determine the new current required to produce a flux of $0.12 \times 10^{-2} \text{ Wb}$ in the air-gap, given that the leakage factor x is 1.24, and that the relative permeability of the iron under the new condition is 350.

Solution

Given:

$$\begin{aligned}\phi_{\text{air-gap}} &= 1.2 \times 10^{-3} \text{ Wb} \\ l_{\text{air-gap}} &= 0.2 \times 10^{-2} = 2 \times 10^{-3} \text{ m} \\ a_{\text{air-gap}} &= 10^{-3} \text{ m}^2 \\ \mu_{\text{air}} &= 1.\end{aligned}$$

\therefore Reluctance in the air-gap is

$$\frac{2 \times 10^{-3}}{(4\pi \times 10^{-7} \times 1 \times 1.2 \times 10^{-3})} = 1.325 \times 10^6 \text{ AT/Wb}$$

$$\begin{aligned}\phi_{\text{iron-path}} &= 1.25 \times 1.2 \times 10^{-3} \text{ Wb} \\ &= 1.5 \times 10^{-3} \text{ Wb}\end{aligned}$$

$$l_{\text{iron-path}} = 0.998 \text{ m}$$

$$a_{\text{iron-path}} = 10^{-3} \text{ m}^2$$

$$\mu_{\text{iron-path (new)}} = 350.$$

$$\begin{aligned}\therefore \text{Reluctance in the iron-path} &= \frac{998 \times 10^{-3}}{(350 \times 4\pi \times 10^{-7} \times 1.2 \times 10^{-3})} \\ &= 1890912.3 \text{ AT/Wb} = 1.89 \times 10^6 \text{ AT/Wb}.\end{aligned}$$

As we cannot add up the values of air-gap reluctance and iron-path reluctance to get the total reluctance, we therefore calculate in this way.

$$\begin{aligned}H &= H_{\text{air-gap}} + H_{\text{iron-path}} \\ &= (\text{Reluctance of air-gap} \times \text{Flux in this path}) \\ &\quad + (\text{Reluctance of iron-path} \times \text{Flux in this path}) \\ &= (1.325 \times 10^6 \times 1.2 \times 10^{-3}) + (1.89 \times 10^6 \times 1.5 \times 10^{-3}) \\ &= 4.425 \times 10^3 = 4425\end{aligned}$$

$$\therefore \text{Current } (= I) = \frac{4,425}{200} = 22.125 \text{ A.}$$

3.42 A magnetic circuit shown in Fig. 3.27 is constructed of wrought iron:

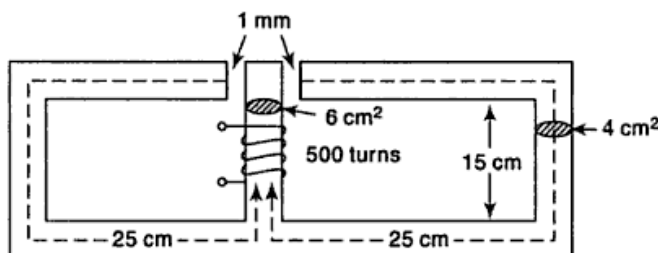


Fig. 3.27 Magnetic circuit of Ex. 3.42

The cross-section of the central limb is 6 cm^2 , and each outer limb is 4 cm^2 . If the coil is wound with 500 turns, determine the exciting current required to set up a flux of 1.0 m Wb in the central limb.

B-H curve of wrought iron are:

$B \text{ (Wb/m}^2\text{)}$	1.25	1.67
$H \text{ (AT/m)}$	600	2,100

Solution

Given that Flux (ϕ_1) in the central limb $= 1.0 \times 10^{-3} \text{ Wb}$
 Area (a_1) of the central limb $= 6 \times 10^{-4} \text{ m}^2$
 $l_1 = 15 \text{ cm} = 0.15 \text{ m}$

$$B_1 = \frac{\phi_1}{a_1} = \frac{1.0 \times 10^{-3}}{6.0 \times 10^{-4}} = 1.667 \text{ Wb/m}^2$$

$$\therefore \text{AT required} = H_1 l_1 = 2100 \times 0.15 = 315 \text{ AT}$$

$$\text{For outer limb flux } (\phi_2) = \frac{1}{2} \times 1.0 \times 10^{-3} \text{ Wb}$$

$$\text{Area } (a_2) = 4 \times 10^{-4} \text{ m}^2, \\ \text{Length } l_2 = 25 \text{ cm} = 0.25 \text{ m}$$

$$\therefore B_2 = \frac{1/2 \times 1.0 \times 10^{-3}}{4 \times 10^{-4}} = 1.25 \text{ Wb/m}^2$$

From B-H curve, $H_2 = 600 \text{ AT/m}$

$$\therefore \text{AT required} = H_2 l_2 = 600 \times 0.25 = 150 \text{ AT}$$

$$\text{Air-gap } A_g = B_g = 1.25 \text{ Wb/m}^2 \\ l_g = 1 \times 10^{-3} \text{ m}$$

$$\therefore \text{AT required} = \frac{B_g \cdot l_g}{\mu_o} = \frac{1.25 \times 1 \times 10^{-3}}{4\pi \times 10^{-3}} = 994.45 \text{ AT}$$

$$\therefore \text{Total AT required} \\ = 315 + 150 + 994.45 \\ = 1,459.45 \text{ AT.}$$

∴ The exciting current I

$$= \frac{NI}{N} = \frac{1459.45}{500} = 2.92 \text{ A}$$

3.43 An iron ring made up of three parts, $l_1 = 12 \text{ cm}$, $a_1 = 6 \text{ cm}^2$; $l_2 = 10 \text{ cm}$, $a_2 = 5 \text{ cm}^2$, $l_3 = 8 \text{ cm}$ and $a_3 = 4 \text{ cm}^2$. It is surrounded by a coil of 200 turns. Determine the exciting current required to create a flux of 0.5 m wb in the iron ring. [Given $\mu_1 = 2670$, $\mu_2 = 1055$, $\mu_3 = 680$.]

Solution

Total reluctance $S = S_1 + S_2 + S_3$

$$= \sum_{\mu_r a}^3 \frac{l}{\mu_o \mu_r a} = \frac{l_1}{\mu_o \mu_r a_1} + \frac{l_2}{\mu_o \mu_r a_2} + \frac{l_3}{\mu_o \mu_r a_3}$$

premier12

$$= \frac{1}{4\pi \times 10^{-7}} \left[\frac{0.12}{2670 \times 6 \times 10^{-4}} + \frac{0.1}{1055 \times 5 \times 10^{-4}} + \frac{0.08}{680 \times 4 \times 10^{-4}} \right]$$

$$= \frac{1}{4\pi \times 10^{-7}} [0.074906 + .189573 + 0.294117]$$

$$= 4.445 \times 10^5 \text{ AT/Wb.}$$

$$\therefore \text{Flux } (\phi) = \frac{\text{mmf}}{\text{reluctance}} = \frac{NI}{4.445 \times 10^5}$$

$$\therefore I = \frac{\text{flux} \times 4.45 \times 10^5}{N}$$

$$= \frac{0.5 \times 10^{-3} \times 4.45 \times 10^5}{200}$$

$$= 1.11125 \text{ A}$$

$$= 1111.25 \times 10^{-3} \text{ Amps} = 1111.25 \text{ mA.}$$

3.27 LEAKAGE FLUX IN MAGNETIC CIRCUIT AND FRINGING AND STAKING

In a magnetic circuit, it is never possible to confine all the fluxes in the direction of designated path, since a portion of the total flux will follow different paths from the intended path (generally through air). The shapes of these paths, and the amount of flux in them, depend on the geometry of the magnetic circuit and also in the value of the relative permeability μ_r . Therefore the part of the magnetic flux that has its path within the magnetic circuit is known as the useful flux or main flux and that taking other paths is called *leakage flux*. This phenomenon of wastage of some flux is called *magnetic leakage*. Sum of the two parts is called the *total flux produced*.

The ratio of the total flux produced by the magnet to the main flux is called *leakage co-efficient* or *leakage factor*.

$$\text{Mathematically, leakage factor} = \frac{\phi_T}{\phi_m} = \frac{\text{Total useful flux}}{\text{Main flux}} = \frac{\phi_l + \phi_m}{\phi_m}$$

where ϕ_l = leakage flux
 ϕ_m = main flux and
 ϕ_T = Total flux.

This leakage co-efficient is generally designated by λ and its value ranges from 1.12 to 1.25, i.e. is always greater than unity.

Magnetic leakage in magnets is undesirable since it increases their weight as well as cost of manufacturer.

Fringing

Figure 3.28 shows a ring provided with an air gap. The flux lines crossing this air-gap tend to repel each other and therefore buldge out across the edges of the air gap. This phenomenon is known as *fringing*. Due to this fringing, the effective gap area is larger than that of the ring. Longer the air-gap, greater is the fringing. Generally, the increase in cross-sectional area of air-gap due to fringing is assumed to be about 9 to 10%.

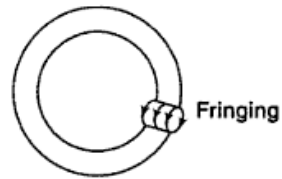


Fig. 3.28 Concept of fringing

Stacking

Magnetic circuits are generally laminated to reduce eddy current loss. These laminations are coated with insulating varnish. Therefore, a small space is present between the successive laminations. So the effective magnetic cross-sectional area is less than the overall area of the stack. *Stacking factor* is defined as the ratio of the effective area to the total area. This factor plays an important role during calculation of flux densities in magnetic parts. This factor is usually less than unity.

3.28 MAGNETIC HYSTERESIS

When a bar of ferromagnet material is magnetised by a varying magnetic field and the intensity of magnetization B is measured for different values of magnetizing field H , the graph of B versus H is shown in Fig. 3.29 and it is called B - H curve or magnetization curve. From graph, it is observed that

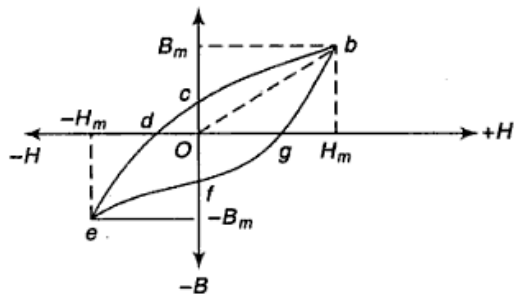


Fig. 3.29 Magnetic hysteresis

- (a) When the magnetizing field is increased from 0, the intensity of magnetization (H) increases and becomes maximum. This maximum value is called the saturation value.

The state of magnetic material in which the value of H becomes maximum and does not increase further on increasing the value of H is called the *state of magnetic saturation*.

- (b) When H is reduced, B reduces but is not zero when $H = 0$. The remainder value OC of magnetization, when $H = 0$, is called the *residual magnetism* or *retentivity*. The property by virtue of which the magnetism B remains in material even on the removal of magnetizing field is called *retentivity* or *residual magnetism* or *remnant magnetism*.
- (c) When magnetic field H is reversed, the magnetization decreases and for a particular value of H , denoted by H_C , it becomes zero, i.e. $H_C = od$ when $I = 0$. This value of H is called *coercivity*.

So, the process of demagnetizing a material completely by applying magnetizing field in a negative direction is defined as coercivity. Coercivity assesses the softness or hardness of a magnetic material. If the coercivity of a magnetic material is low then it is magnetically soft and when its value is high then the material is magnetically hard.

- (d) When the field H is further increased in reverse direction the intensity of magnetization attains saturation value in reverse direction (i.e., point e).
- (e) When H is decreased to zero and changed direction in steps, we get the part $efgb$.

Thus complete cycle of magnetization and demagnetization is represented by $bcdefgb$. In the complete cycle the intensity of magnetization H is lagging behind the applied magnetizing field. This is called *hysteresis* and the closed loop $bcdefgb$ is called *hysteresis cycle*.

The energy loss in magnetizing and demagnetizing a specimen is proportional to the area of hysteresis loop.

The selection of a material for a specific purpose depends on its hysteresis loop. When the magnet is to operate on ac voltage it undergoes a large number of reversals every second. The material for such application should have a low hysteresis loss and therefore, the hysteresis loop should enclose a small area. Soft iron is one such example.

In recent times some development has been made in Ni-Fe alloys. They are called *square loop* materials produced by maintaining the alloy for a time in a magnetic field at a temperature of 400°C to 590°C . The ultimate of this development is to make the knee point of magnetizing curve very sharp, the coercive force becomes small and the permeability is very high. The hysteresis curve showing variation of B with H of in "square loop" material is shown in Fig. 3.30. In fact these properties are essential in devices like magnetic storage of information like in computers.

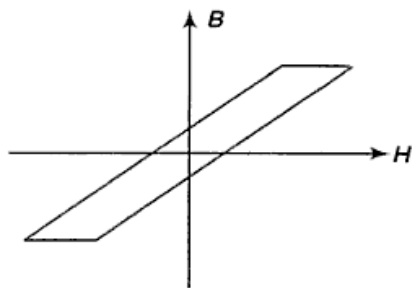


Fig. 3.30 B - H curve for square loop material

3.29 HYSTERESIS LOSS

This loss occurs due to the B - H magnetization curve which swings to positive and negative maximum B_m before returning to zero. Ideally the energy absorbed during the positive swing should be returned to the source during reversal of the magnetizing cycle. But in actuality there is only a partial return to source, the rest being dissipated as heat.

Figure 3.31 represents the hysteresis loop obtained of a steel ring of mean circumference (l) meters and cross-sectional area (a) square meters. Let (N) be the number of turns on the magnetizing coil.

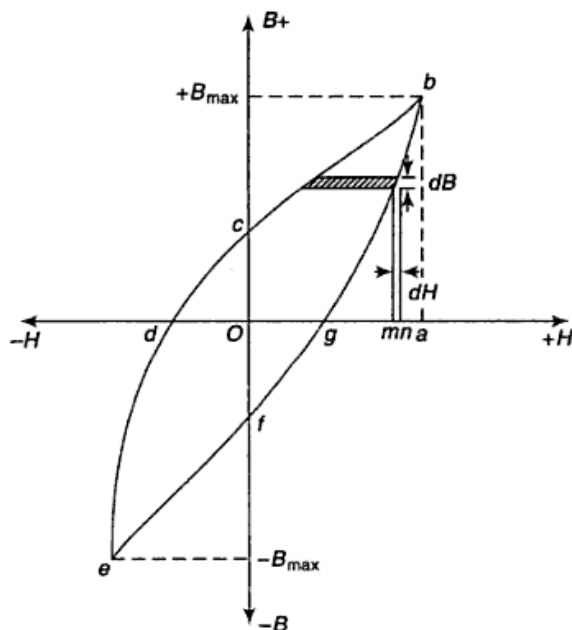


Fig. 3.31 Hysteresis loop for steel ring

Let (dB) = increase of flux density when the magnetic field intensity is increased by a very small amount dH (say) in dt seconds, and i = current in amperes corresponding to om , i.e., $om = \frac{Ni}{l}$.

Instantaneous emf induced in the winding is $a \times dB \times \frac{N}{dt}$ V.
and component of applied voltage to neutralize this emf equals

$$\left(an \times \frac{dB}{dt} \right) \text{ V.}$$

Therefore instantaneous power supplied to the magnetic field is

$$\left(i \times an \times \frac{dB}{dt} \right) \text{ W.}$$

and energy supplied to the magnetic field in time dt second is

$$(i \times an \times dB) \text{ J}$$

Since, $om = \frac{Ni}{l}$

$$i = l \times \frac{om}{N}$$

hence energy supplied to magnetic field in time dt is

$$l \times \frac{om}{N} \times an \times dB \text{ J} = (om \times dB \times lA) \text{ J}$$

$$= \text{area of shaded strip, J/m}^3.$$

Thus energy supplied to the magnetic field when H is increased from zero to oa is equal to area $f g b B_m f \text{ J/m}^3$. Similarly, energy returned from the magnetic field when H is reduced from oa to zero is area $b B_m cb \text{ J/m}^3$. Then net energy absorbed by the magnetic field is

$$\text{Area } f g b B_m f \text{ J/m}^3.$$

Hence, hysteresis loss for a complete cycle is

$$\text{area of } e f b c e \text{ jouled per m}^3.$$

If we define hysteresis loss as P_n ,

$$\therefore P_n = v.f. (K_H \cdot B_m^n) \text{ W} \quad (3.42)$$

where v is volume of core material and f is the frequency of variation of H in Hz.

The value of n is between 1.5 and 2.5 ($1.5 \leq n \leq 2.5$) but mostly it is 1.6.

B_m is the maximum flux density in Tesla and K_H is a constant and n is the exponent which depends on the material.

The constant K_H (depending on the chemical properties of the material and the heat treatment and mechanical treatment the material has been subjected to) may have value as low as 5×10^{-7} for permalloys and as high as 6×10^{-5} for cast iron. However K_H for electrical sheet steel is generally 4×10^{-5} .

The exponent n has been found by Steinmetz as 1.6 and does not have any theoretical basis. This value suits most material at flux densities generally not exceeding 1 wb/m^2 . However, for higher value of flux densities, the value may be as great as 2.5.

3.30 EDDY CURRENTS (OR FOUCAULT'S CURRENTS) AND EDDY CURRENT LOSS

When a metallic body is moved in a magnetic field in such a way that the flux through it changes or is placed in a changing magnetic field, induced currents circulate throughout the volume of the body. These are called *eddy currents*. If the resistance of the said conductor is small, then the magnitudes of the eddy currents are large and the metal gets heated up. This heating effect is a source of power loss in iron-cored devices such as dynamos, motors and transformers,

The eddy current loss is given by

$$P_e = K_e \cdot f \cdot B_m^2 t^2 v^2 \text{ W} \quad (3.43)$$

where K_e is a constant, f is frequency, B_m is the maximum flux density, t is the thickness of the core material and v is the total volume of the core material.

If the core is made of laminations insulated from one another, the eddy currents are confined to their respective sheets, the eddy current loss is thereby reduced. Thus, if the core is split up into five laminations, the emf per lamination is only a fifth of that generated in the solid core. Also, the cross-sectional area per path is reduced to about a fifth, so that the resistance per path is roughly five times that of the solid core. Consequently the current per path is about one-twenty-fifth of that in the solid core. Hence:

$$\frac{I^2 R \text{ loss per lamination}}{I^2 R \text{ loss in solid core}} = \left(\frac{1}{25}\right)^2 \times 5 = \frac{1}{125} \quad (\text{approx.})$$

Since there are five laminations,

$$\frac{\text{Total eddy current loss per laminated core}}{\text{Total eddy current loss in solid core}} = \frac{1}{125} \left(\frac{1}{5}\right)^2$$

It follows that the eddy current loss is approximately proportional to the square of the thickness of the laminations.

Hence the eddy current loss can be reduced to any desired value, but if the thickness of the laminations is made less than about 0.4 mm, the reduction in the loss does not justify the extra cost of construction.

Since the emfs induced in the core are proportional to the frequency and the flux, therefore the eddy current loss is proportional to $(\text{frequency} \times \text{flux})^2$.

Eddy current loss can also be reduced considerably by the use of silicon-iron alloy and employing conducting material of high resistivity.

The hysteresis and eddy current losses are together known as *core losses* or *iron losses*. For any particular material B_m and f are also nearly constant and does not vary with current. Therefore the core losses are also known as *constant losses* and is independent of the load current.

3.31 RISE AND DECAY OF CURRENT IN INDUCTIVE CIRCUIT

Let us consider a circuit (Fig. 3.32) consisting of a battery of emf E , a coil of self-inductance L and a resistor R . The resistor R may be a separate circuit element or it may be the resistance of the inductor windings. Growth of current by closing switch S_1 , we connect R and L in series with constant emf E . Let i be the current at some time t after switch S_1

is closed and $\left(\frac{di}{dt}\right)$ be its rate of change at that

time. Applying Kirchoff's law starting at the negative terminal and proceeding counter clockwise around the loop,

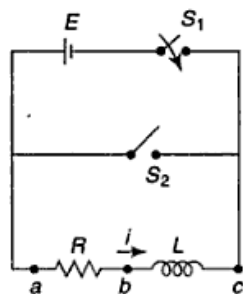


Fig. 3.32 Charging and discharging in inductive circuit

$$\begin{aligned}
 & E - V_{ab} - V_{bc} = 0 \\
 \therefore & E - iR - L \frac{di}{dt} = 0 \\
 \text{or} & E - iR = L \frac{di}{dt} \\
 \text{or} & \int_0^t \frac{dt}{L} = \int_0^i \frac{di}{E - iR} \\
 \text{or} & I = \frac{E}{R} \left(1 - e^{-\frac{R}{L}t} \right) \quad (3.44a)
 \end{aligned}$$

By letting $\frac{E}{R} = i_0$ and $\frac{L}{R} = \tau$, the above expression reduces to

$$i = i_0 \left(1 - e^{-\frac{t}{\tau}} \right) \quad (3.44b)$$

and $\tau = L/R$ is called the *time constant* of the L-R circuit.

If $t \rightarrow \infty$, then the current $i = i_0 = E/R$. It is also called the *steady state current* or the *maximum current* in the circuit.

At a time equal to one time constant the current has risen to $(1 - e^{-1})$ or about 63% of its final value i_0 .

The i - t graph is as shown in Fig. 3.33.

Note that the final current i_0 does not depend on the inductance L , it is the same as it would be if the resistance R alone were connected to the source with emf E . Let us have an insight into the behaviour of an L-R circuit from energy considerations.

The instantaneous rate at which the source delivers energy to the current $P = Ei$ is equal to the instantaneous rate at which energy is dissipated in the resistor ($=i^2R$) plus the rate at which energy is stored in the inductor

$$\therefore \frac{d}{dt} \left(\frac{1}{2} Li^2 \right) = Li \frac{di}{dt} \quad (3.45)$$

$$\text{Thus} \quad E \cdot i = i^2 R + Li \frac{di}{dt} \quad (3.46)$$

Decay of Current

Now, let us suppose switch S_1 in the circuit shown in Fig. 3.34 has been closed for a long time and that the current has reached its steady state value i_0 . Resetting

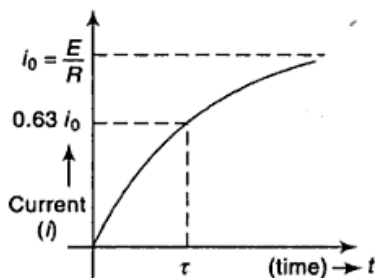


Fig. 3.33 i - t charging characteristic

our stopwatch to reduce the initial value the close switch S_2 at time $t = 0$ and at the same time we should open the switch S_1 to by-pass the battery. The current through L and R does not instantaneously go to zero but decays exponentially. Applying Kirchhoff's law to find current in the circuit (Fig. 3.34) at time t , we can write.

$$(V_a - V_b) + (V_b - V_c) = 0$$

$$\text{or} \quad i \cdot R + L \left(\frac{di}{dt} \right) = 0 \quad [\text{as } V_a = V_c]$$

$$\frac{di}{i} = -\frac{R}{L} dt$$

$$\text{or} \quad \int_0^i \frac{di}{i} = -\frac{R}{L} \int_0^t dt$$

$$\text{or} \quad i = i_0 e^{-\frac{t}{\Upsilon}} \quad (3.47)$$

where $\Upsilon \left(= \frac{L}{R} \right)$ is the time for current to decrease to $\left(\frac{1}{e} \right)$ or about 37% of its original value.

The current (i)—time (t) graph for the decaying condition is as shown in Fig. 3.35

The energy that is needed to maintain the current during this decay is provided by the energy stored in the magnetic field. Thus, the rate at which energy is dissipated in the resistor is equal to the rate at which the stored energy decreases in the magnetic field of the inductor.

$$\therefore i^2 R = -\frac{d}{dt} \left(\frac{1}{2} Li^2 \right) = Li \left(-\frac{di}{dt} \right)$$

$$\text{or} \quad i^2 R + Li \frac{di}{dt} = 0$$

or $iR + L \frac{di}{dt} = 0$, which confirms when R - L circuit is short-circuited the current does not cease to flow immediately (i.e. at $t = 0$) but reduced to zero gradually.

3.44 The hysteresis loop of a specimen of $5 \times 10^{-4} \text{ m}^3$ of iron is 12 cm^2 . The scale is $1 \text{ cm} = 0.4 \text{ Wb/m}^2$ and $1 \text{ cm} = 400 \text{ AT/m}$. Find out the hysteresis loss, when subjected to an alternating flux density of 50 c/sec.

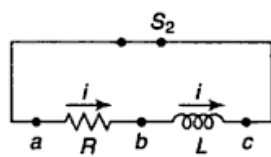


Fig. 3.34 L-R circuit

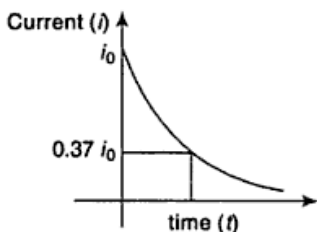


Fig. 3.35 Current decay in an inductive circuit

Solution

$$\begin{aligned}
 \text{Hysteresis loss} &= 12 \text{ cm}^2 \times (400 \text{ AT/m}) \text{ cm}^{-1} \times (0.4 \text{ Wb/m}^2) \text{ cm}^{-1} \\
 &= 1.92 \times 10^3 \text{ Wb/m}^3 \\
 &= 1.92 \times 10^3 \times 50 \text{ J/m}^3/\text{sec} \\
 &= 9.6 \times 10^4 \text{ J/m}^3/\text{sec}.
 \end{aligned}$$

It given that volume of the specimen is $5 \times 10^{-4} \text{ m}^3$.

$$\begin{aligned}
 \therefore \text{Hysteresis loss} &= 9.6 \times 10^4 \times 5 \times 10^{-4} \text{ J/sec.} \\
 &= 48 \text{ J/s} = 48 \text{ W.}
 \end{aligned}$$

3.45 The flux in a magnetic core is varying sinusoidally at a frequency of 600 c/s. The maximum flux density B_{\max} is 0.6 Wb/m^2 . The eddy current loss then is 16 W. Find the eddy current loss in this core, when the frequency is 800 c/sec, and the flux density is 0.5 Wb/m^2 (Tesla).

Solution

We know, eddy current loss $\propto B_{\max}^2 \times f$

$$\text{at } 600 \text{ c/sec: } P_{e_1} \propto (0.6)^2 \times 600 \quad (\text{i})$$

$$\text{at } 800 \text{ c/sec: } P_{e_2} (\text{say}) \propto (0.5)^2 \times 800 \quad (\text{ii})$$

Dividing equation (ii) by equation (i) gives:

$$\begin{aligned}
 \frac{P_{e_2}}{16} &= \frac{(0.5)^2 \times 800}{(0.6)^2 \times 600} \quad [\because P_{e_1} \text{ is } 16 \text{ W}] \\
 &= 9.259 \times 10^{-1}
 \end{aligned}$$

$$\begin{aligned}
 \therefore P_{e_2} &= 16 \times 9.259 \times 10^{-1} \text{ W} \\
 &= 14.8148 \text{ W.}
 \end{aligned}$$

3.46 A coil having a resistance of 10Ω and inductance of 15 H is connected across a d.c. voltage of 150 V . Calculate: (i) The value of current at 0.4 sec after switching on the supply. (ii) With the current having reached the final value the time it would take for the current to reach a value of 9 A after switching off the supply.

Solution

It is given that

$$\begin{aligned}
 V(d.c.) &= 150 \text{ V} \\
 R &= 10 \Omega \\
 L &= 15 \text{ H}
 \end{aligned}$$

(i) \therefore The value of the current

$$\begin{aligned}
 i &= \frac{V}{R} \left(1 - e^{-\frac{R}{L}t} \right) = \frac{150}{10} \left(1 - e^{-\frac{10}{15} \times 0.4} \right) \\
 &= 15 \left(1 - e^{-\frac{4}{15}} \right) \\
 &= 3.51 \text{ A}
 \end{aligned}$$

(ii) Let us assume that at $t = t_1$, $i = 9$ A

$$\therefore 9 = 15 \times e^{-\frac{t_1}{1.5}}$$

(for decaying)

$$e^{-\frac{t_1}{1.5}} = \frac{9}{15}$$

taking \log_e in both sides,

$$-\frac{t_1}{1.5} = \log_e \frac{9}{15}$$

$$\therefore t_1 = 0.7662 \text{ sec.}$$

.....

3.47 For the network shown in Fig. 3.36

- Find the mathematical expression for the variation of the current in the inductor following the closure of the switch at $t = 0$ on to position 'a';
- The switch is closed on to position 'b' when $t = 100$ m/sec, calculate the new expression for the inductor current and also for the voltage across R ;
- Plot the current waveforms for $t = 0$ to $t = 200$ m/sec.

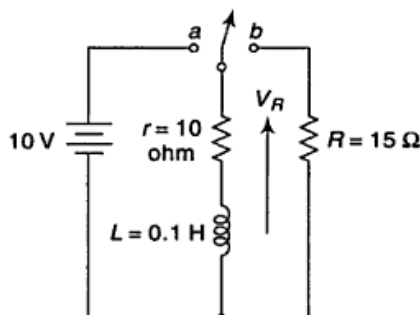


Fig. 3.36 Network of Ex. 3.47

Solution

(a) For the switch in position 'a', the time constant is

$$\tau_a = \frac{L}{r} = \frac{0.1}{10} = 10 \text{ milli-sec(ms)}$$

$$\therefore i_a = \frac{V}{r} \left(1 - e^{-\frac{t}{\tau_a}} \right) = \frac{10}{10} \left(1 - e^{-\frac{t}{10 \times 10^{-3}}} \right)$$

$$= \left(1 - e^{-\frac{t}{10^{-2}}} \right) \text{ A.}$$

(b) For the switch in position 'b' the time constant

$$\tau_b = \frac{L}{R+r} = \frac{0.1}{15+10} = 4 \text{ ms}$$

$$\therefore i_b = \frac{V}{R} e^{-\frac{t}{\tau_b}} \quad (\text{for decaying})$$

$$= \frac{10}{15} e^{-\frac{t}{4 \times 10^{-3}}} = e^{-\frac{t}{4 \times 10^{-3}}} \text{ A.}$$

The current continues to flow in the same direction as before, therefore the voltage drop across R is negative to the direction of the arrow shown in Fig. 3.36. $v_R = i_b \cdot R = -15 \times e^{-t/4 \times 10^{-3}} \text{ V.}$

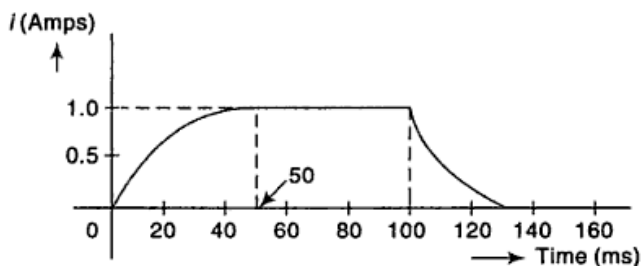


Fig. 3.37 Current profile

It will be noted that in the first switched period, five times the time constant is 50 m/sec. The transient has virtually finished at the end of this time and it would not have mattered whether the second switching took place then or later. During the second period the transient took only 25 m/sec.

(c) The profile current waveform has been plotted in Fig. 3.37.

3.48 For the network shown in Fig. 3.36 (Ex. No. 3.47) the switch is closed on the position 'a'. Next, it is closed on to position 'b' when $\tau = 10$ ms. Again, find the expression of current and hence draw the current wave forms.

Solution

For the switch in position 'a', the time constant τ is 10 m/sec as in Ex. No. 3.47, and the current expression as is before. However, the switch is moved to position 'b' while the transient is proceeding. When $t = 10$ m/sec.

$$i = \left(1 - e^{-\frac{t}{10 \times 10^{-3}}} \right) = \left(1.0 - e^{-\frac{10 \times 10^{-3}}{10 \times 10^{-3}}} \right)$$

$$= (1 - e^{-1}) = 0.632 \text{ A.}$$

i.e., the second transient commences with an initial current in R of 0.632 A.

\therefore The current decay is, $i_b = 0.632 \times$

$\frac{t}{4 \times 10^{-3}}$ A. which is shown in Fig. 3.38.

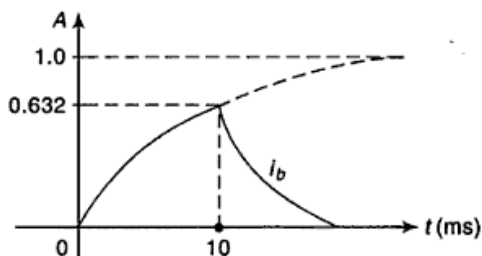


Fig. 3.38

3.49 A d.c. voltage of 150 V is applied to a coil whose resistance is 10Ω and inductance is 15 H. Find: (i) the value of the current 0.3 sec after switching on the supply; (ii) with the current having reached the final value, how much time it would take for the current to reach a value of 6 A after switching off the supply.

Solution

(a) It is given that

$$V = 150 \text{ V, } R = 10 \Omega, L = 15 \text{ H}$$

\therefore The value of the current 0.3 sec after switching on is

$$i = \frac{150}{10} \left(1 - e^{-\frac{10}{15} \times 0.3} \right) = 2.72 \text{ A.}$$

- (b) After switching off the supply, the current will be decaying and is given by

$$i = \frac{V}{R} e^{-\frac{R}{L}t} \quad \therefore 6 = \frac{150}{10} e^{-\frac{10}{15} \times t}$$

$$\therefore t = 1.375 \text{ sec.}$$

3.50 A coil of resistance 24Ω and having inductor 36 H is suddenly connected to a d.c. of 60 V supply. Determine

- the initial rate of change of current $\left(\frac{di}{dt}\right)$
- the time-constant
- the current after 3 sec.
- the energy stored in the magnetic field at $t = 3 \text{ sec.}$
- the energy lost as heat energy at $t = 3 \text{ sec.}$

Solution

It is given that: $V = 60 \text{ V}$, $R = 24 \Omega$, $L = 36 \text{ H}$

- (a) Initial rate of change of current:

$$i = \frac{V}{R} \left(1 - e^{-\frac{R}{L}t}\right)$$

$$\begin{aligned} \therefore \frac{di}{dt} &= -\frac{V}{R} \cdot \left(-\frac{R}{L}\right) \cdot e^{-\frac{R}{L}t} \\ &= \frac{V}{L} e^{-\frac{R}{L}t}; \end{aligned}$$

When $t = 0$,

$$\frac{di}{dt} = \frac{V}{L} \cdot e^0 = \frac{V}{L} = \frac{60}{36} = 1.67 \text{ A/sec.}$$

- (b) Time constant (τ):

$$\tau = \frac{L}{R} = \frac{36}{24} = 1.5 \text{ sec.}$$

- (c) Current; the current at $t = 3 \text{ sec}$ is

$$i = \frac{V}{R} \left(1 - e^{-\frac{R}{L}t}\right) = \frac{60}{24} \left(1 - e^{-\frac{24}{36} \times 3}\right) = 2.16 \text{ A.}$$

- (d) Energy stored:

$$\begin{aligned} \text{at } t = 3 \text{ sec, the energy stored in the magnetic field is } &\frac{1}{2} Li^2 \\ &= \frac{1}{2} \times 36 \times (2.16)^2 = 84 \text{ J.} \end{aligned}$$

- (e) Energy lost as heat energy:

at $t = 3 \text{ sec}$, the energy lost as heat energy is

$$i^2 \times R = (2.16)^2 \times 24 \approx 112 \text{ J.}$$

3.32 AMPERE'S CIRCUITAL LAW

We know the integral of static (time independent electric field around a closed path is zero but what about the integral of the magnetic field around a closed path? Actually, the quantity (Hdl) does not represent some physical quantity, and certainly not work. Although the static magnetic force does no work on a moving charge, we cannot conclude that the path integral of the magnetic field around a closed path is zero.

The line integral ($\oint B \cdot dl$) of the resultant magnetic field along a closed plane curve is equal to μ_0 times the total current crossing the area bounded by the closed curve provided the electric field inside the loop remains constant.

Thus
$$\oint B \cdot dl = \mu_0 \cdot I$$

This is known as *Ampere's circuital law*. The above equation can be simplified as $B \cdot l = \mu_0 \cdot I$

But this equation can be used only under the following condition.

- At every point of the closed path B is parallel to dl .
- Magnetic field has the same magnitude B at all places on the closed path.

If this is not the case, then the above equation can be written as

$$B_1 dl_1 \cos \theta_1 + B_2 dl_2 \cos \theta_2 + \dots = \mu_0 \cdot I$$

■ ADDITIONAL EXAMPLES ■

3.51 If the vertical component of the earth's magnetic field be $4.0 \times 10^{-5} \text{ Wb m}^{-2}$, then what will be the induced potential difference produced between the rails of a meter-gauge running north-south when a train is running on them with a speed of 36 km h^{-1} ?

Solution

When a train is on the rails, it cuts the magnetic flux lines of the vertical component of the earth's magnetic field. Hence, a potential difference is induced between the ends of its axle.

Distance between the rails = 1 m; speed of train (v) = $36 \text{ km/hr} = 10 \text{ m/sec}$. Magnetic field $B_v = 4.0 \times 10^{-5} \text{ Wb/m}$. \therefore The induced potential difference in $e = Bvl = (4.0 \times 10^{-5}) \times 10 \times 1 = 4.0 \times 10^{-9} \text{ V}$

3.52 The current in the coil of a large electromagnet falls from 6 A to 2 A in 10 ms. The induced emf across the coil is 100 V. Find the self-inductance of the coil.

Solution

The self-induced emf is given by

$$e = -L \frac{di}{dt}$$

Here $di = 2 - 6 = -4 \text{ A}$
 $dt = 10 \text{ ms} = 10^{-2} \text{ sec}$

and $e = 100 \text{ V}$

$$\therefore L = -e \frac{dt}{di} = -100 \times \frac{10^{-2}}{-4} = 0.25 \text{ H}.$$

.....

3.53 The current (in ampere) in an inductor is given by $i = 5 + 16t$, where t is in seconds. The self-induced emf in it is 10 mV. Find (a) the self-inductance, and (b) the energy stored in the inductor and the power supplied to it at $t = 1$.

Solution

The induced emf in the inductor due to current change is

$$|e| = L \frac{di}{dt}$$

$$\therefore L = \frac{|e|}{di/dt}$$

Hence $i = 5 + 16t$, from this, we have

$$\frac{di}{dt} = 0 + 16 = 16 \text{ A sec}^{-1}, \text{ and } e = 10 \text{ mV} = 10 \times 10^{-3} \text{ V}$$

$$\therefore L = \frac{10 \times 10^{-3} \text{ V}}{16 \text{ A sec}^{-1}} = 0.666 \times 10^{-3} \text{ H} = 0.666 \text{ mH}$$

(b) The current at $t = 1$ sec is

$$i = 5 + 16t = 5 + 16 \times 1 \\ = 21 \text{ A}$$

\therefore Energy stored in the inductor is

$$\frac{1}{2} Li^2 = \frac{1}{2} \times (0.666 \times 10^{-3}) \times (21)^2 \\ = 137.8 \times 10^{-3} = 137.8 \text{ mJ}$$

Power supplied to the inductor at $t = 1$ sec is

$$P = li = (10 \times 10^{-3} \text{ V}) \times 21 = 0.21 \text{ W.}$$

.....

3.54 Calculate the self-inductance of an air-cored solenoid, 40 cm long, having an area of cross-section 20 cm^2 and 800 turns.

Hints:
$$L = \frac{\mu_0 \cdot N^2 \cdot A}{l}$$

[here we assume $\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$].

$$\therefore L = \frac{4\pi \times 10^{-7} \times 800^2 \times 20 \times 10^{-4}}{40 \times 10^{-2}} = 4.022 \times 10^{-3} \text{ H}$$

.....

3.55 A solenoid of inductance L and resistance R is connected to a battery. Prove that the time taken for the magnetic energy to reach $1/4$ of its maximum value is $L/R \log_e(2)$.

Solution

The growth of current in an LR circuit is given by

$$I = I_0 \left(1 - e^{-\frac{R}{L} \cdot t} \right) \quad (i)$$

where I_0 is the maximum current. The energy stored at time t is

$$u = \frac{1}{2} LI^2$$

We are required to find the time at which the energy stored is $1/4$ the maximum value,

i.e., when $u = \frac{u_o}{4}$ where $u_o = \frac{1}{2} L I_0^2$.

$$\text{i.e.,} \quad \frac{1}{2} L I^2 = \frac{1}{4} \left(\frac{1}{2} L I_0^2 \right) \quad \text{or} \quad I = \frac{I_0}{2}$$

\therefore Using the equation 1, we have

$$\frac{I_0}{2} = I_0 \left(1 - e^{-\frac{R}{L}t} \right)$$

$$\frac{1}{2} = 1 - e^{-\frac{R}{L}t}$$

$$\text{or} \quad e^{-\frac{R}{L}t} = \frac{1}{2}$$

$$\text{or} \quad -\frac{R}{L}t = \log_e \left(\frac{1}{2} \right) = -\log_e(2)$$

$$\therefore \quad t = \frac{L}{R} \log_e(2)$$

3.56. An aeroplane with a 20 m wingspread is flying at 250 m/s parallel to the earth's surface at a plane where the horizontal component of the earth's magnetic field is 2×10^{-5} Tesla and angle of dip 60° . Calculate the magnitude of the induced emf between the tips of the wings.

Solution

As the aeroplane is flying horizontally parallel to the earth's surface the flux linked with it will be due to the vertical component B_V on the earth's field.

$$\therefore \quad B_V = B_H \tan \theta = 2 \times 10^{-5} \times \tan 60^\circ$$

$$= 2\sqrt{3} \times 10^{-5} \text{ Wb/m}^2.$$

$$\therefore \text{ Induced emf is } |e| = B_V l v \sin \theta$$

$$= 2\sqrt{3} \times 10^{-5} \times 20 \times 250 \times \sin 90^\circ$$

$$\text{or} \quad |e| = \frac{\sqrt{3}}{10} \text{ V} = 0.173 \text{ V}.$$

3.57. A rectangular loop of sides 25 cm \times 10 cm carries a current of 15 A. It is placed with its longer side parallel to a long straight conductor 2.0 cm apart and carrying a current at 25 A. Find the net force on the loop. What will be the difference in force if the current in the loop be reversed?

Solution

Let ABCD be the loop (length l , width b and current i_1), with its longer side AB placed parallel and at a distance d from a long conductor XY, carrying current i_2 as shown in Fig. 3.39.

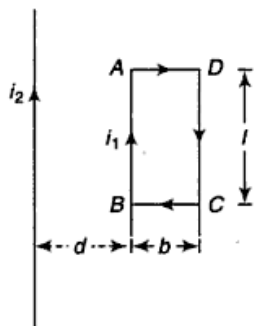


Fig. 3.39 Rectangular loop

The attractive force on the side AB of the loop, due to current i_2 , is

$$F_1 = \frac{\mu_0}{2\pi} \cdot \frac{i_1 \cdot i_2 \cdot l}{d} \text{ towards } XY$$

Similarly, the (repulsive) force in the side CD of the loop is

$$F_2 = \frac{\mu_0}{2\pi} \cdot \frac{i_1 \cdot i_2 \cdot l}{(d+b)} \text{ away from } XY$$

\therefore The forces on the sides AD and BC of the loop; being equal, opposite and collinear, cancel each other.

\therefore Net force on the loop is

$$\begin{aligned} F_1 - F_2 &= \frac{\mu_0}{2\pi} i_1 \cdot i_2 \cdot l \left[\frac{1}{d} - \frac{1}{(d+b)} \right] \\ &= \frac{\mu_0}{2\pi} \cdot \frac{i_1 \cdot i_2 \cdot l \cdot b}{d(d+b)} \text{ towards } XY. \end{aligned}$$

Substituting the values:

$$i_1 = 15 \text{ A}, i_2 = 25 \text{ A}$$

$$l = 0.25, b = 0.10 \text{ m}$$

$$d = 0.02 \text{ m}, d + b = 0.12 \text{ m}$$

and $\frac{\mu_0}{2\pi} = 2 \times 10^{-7} \text{ NA}^{-2}$, we get

$$\begin{aligned} F_1 - F_2 &= (2 \times 10^{-7}) \times \frac{15 \times 25 \times 0.25 \times 0.10}{0.02 \times 0.12} \\ &= 7.8 \times 10^{-4} \text{ N}. \end{aligned}$$

The net force is directed towards the long conductor. If the current in the loop, or in the long conductor, be reversed, the net force will remain same in magnitude but will then be directed away from the long conductor.

3.58 Show that the time for attaining half the value of the final steady current in an L - R series circuit is $0.6931L/R$.

Solution

The instantaneous current during its growth in an L - R series circuit is given by $i =$

$$i_0 \left(1 - e^{-\frac{R}{L}t} \right)$$

where i_0 = final steady current for $i/i_0 = 1/2$, we have

$$\frac{1}{2} = 1 - e^{-\frac{R}{L}t}$$

$$\therefore e^{-\frac{R}{L}t} = 1 - \frac{1}{2} = \frac{1}{2}$$

$$\therefore e^{\frac{R}{L}t} = 2$$

$$\frac{R}{L} \cdot t = \log_e 2 = 0.6931$$

$$\therefore t = 0.6931 \times \frac{L}{R}$$

3.59 The resistors of 100Ω and 200Ω and an ideal inductance of 10 H are connected to a 3-V battery through a key K , as shown in the Fig. 3.40.

If K is closed at $t = 0$, calculate

- the initial current drawn from the battery
- the initial potential drop across the inductance
- the final current drawn from the battery
- the final current through 100Ω resistance.

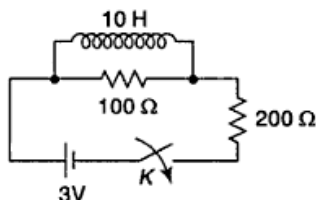


Fig. 3.40 Circuit of Ex. 3.59

Solution

- (a) 'Immediately' after closing K , there is almost no current in the inductance due to self-induction, the current is only in resistance. Thus, the initial current is

$$i = \frac{3\text{V}}{(100+200)\Omega} = 0.01 \text{ A}$$

- (b) The p.d. across the inductor is same as across the 100Ω resistance, that is $0.01 \times 100 = 1 \text{ V}$.
- (c) When the current has become steady the opposing emf in the inductance is zero and it short circuits the 100Ω resistance. The resistance of the circuit is now only 200Ω and so the current drawn from the cell is $3\text{V}/200 \Omega = 0.015 \text{ A}$. This is the final current in the 200Ω resistance.
- (d) The final current through the 100Ω is zero.

3.60 A horizontal power-line carries a current of 90 A from east to west. Compute the magnetic field generation at a point 1.5 meter below the line.

Solution

The magnitude of the magnetic field \vec{B} due to a long current carrying conductor at a distance R is given by

$$B = \frac{\mu_0}{2\pi} \cdot \frac{i}{R}$$

where $\frac{\mu_0}{2\pi} = 2 \times 10^{-7} \text{ Tm A}^{-1}$.

Putting, $i = 90 \text{ A}$, $R = 1.5 \text{ m}$, we have

$$B = (2 \times 10^{-7}) \times \frac{90}{1.5} = 1.2 \times 10^{-5} \text{ T}.$$

Applying Right Hand Rule, we find \vec{B} is directed towards the south.

3.61 Two coils with terminals T_1, T_2 and T_3, T_4 respectively are placed side by side. Measured separately, the inductance of the first is $1200 \mu\text{H}$ and that of the second coil is $800 \mu\text{H}$. With T_2 joined with T_3 (Fig. 3.41), the total inductance between the two coils is

2500 μH . What is the mutual inductance? If T_2 is joined with T_4 instead of T_3 , what would be the value of equivalent inductance of the two coils?

Solution

Given $L_1 = 1200 \mu\text{H}$, $L_2 = 800 \mu\text{H}$, $T_{14} = 2500 \mu\text{H}$.

Let the mutual inductance between the two coils be M , then total inductance $L_1 + L_2 + 2M$. In the first case (refer (Fig. 3.41)

$$T_{14} = L_1 + L_2 + 2M$$

$$2500 = 1200 + 800 + 2M$$

$$\therefore M = \frac{500}{2} = 250 \mu\text{H}.$$

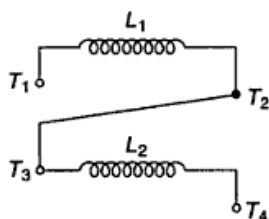


Fig. 3.41 Connection of two coils, 1st case

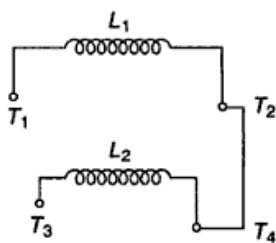


Fig. 3.42 Connection of two coils, 2nd case

If T_{13} is the total inductance in the second case, then

$$T_{13} = L_1 + L_2 - 2M$$

$$= 1200 + 800 - 2 \times 250$$

$$= 1500 \mu\text{H}.$$

(See Fig. 3.42)

3.62 A coil has a resistance of 5Ω and an inductance of 1 H . At $t = 0$ it is connected to a 2 V battery. Find (a) the rate of rise of current at $t = 0$; (b) the rate of rise of current when $i = 0.2 \text{ A}$ and (c) the stored energy when $i = 0$ and $i = 0.3 \text{ A}$.

Solution

$$\tau = \frac{L}{R} = \frac{1}{5} = 0.2 \text{ sec}.$$

$$(a) \frac{di}{dt} = \frac{E}{L} e^{-\frac{t}{\tau}} = 2e^{-5t}$$

$$\text{at } t = 0, \quad \frac{di}{dt} = 2 \text{ A/sec}.$$

$$(b) i = \frac{E}{R} (1 - e^{-5t})$$

$$= 0.4(1 - e^{-5t})$$

time t_1 when $i = 0.2 \text{ A}$ is

$$0.2 = 0.4(1 - e^{-5t_1})$$

$$\text{or } t_1 = 0.1386 \text{ sec}.$$

$$\frac{di}{dt} = 2e^{-5(0.1386)}$$

$$= 1 \text{ A/sec}$$

- (c) At $i = 0$, stored energy = 0
 when $i = 0.3$ A, stored energy

$$= \frac{1}{2} Li^2 = \frac{1}{2} \times 1 \times (0.3)^2 = 0.045 \text{ J.}$$

3.63 A small flat coil of area $2.0 \times 10^{-4} \text{ m}^2$ with 25 closely wound turns is placed with its plane perpendicular to a magnetic field. When the coil is suddenly withdrawn from the field, a charge of 7.5 mc flows through the coil. The resistance of the coil is 0.50Ω . Estimate the strength of the magnetic field.

Solution

The magnetic flux passing through each turn of coil of area A , perpendicular to a magnetic field B is given by

$$\phi_B = BA$$

when the coil is withdrawn from the field, the flux through it vanishes. Therefore, the change in flux is $d\phi_B = 0 - BA = -BA$.

By Faraday's law, the emf induced in the coil is

$$e = -N \cdot \frac{d\phi_B}{dt} = \frac{NBA}{dt}$$

where dt is the time taken in withdrawal. The induced current in the coil of resistance (say R) is

$$i = \frac{e}{R}$$

This current persists only during the time interval dt . Hence the charge flowed through the

coil is $q = i \times dt = \frac{e}{R} \cdot dt = \frac{NBA}{R}$.

$$\therefore B = \frac{qR}{NA}$$

Substituting the given values, we have

$$B = \frac{(7.5 \times 10^{-3}) \times 0.50}{25 \times (2.0 \times 10^{-4})} = 0.75 \text{ Wb/m}^2.$$

3.64 A copper rod of length 1.0 m is revolving with a frequency of 50 rev/sec. around one of its ends, perpendicular to a uniform magnetic field of 1.0 Wb/m^2 . Find the emf developed between the two ends of the revolving rod.

Solution

The magnetic flux linked with an area of perpendicular to a uniform magnetic field of magnitude B is given by $\phi_B = BA$.

Suppose the copper rod of length l (say) revolving about its one end O is completing n revolutions per unit time is shown in Fig. 3.43, then, the rate of change of magnetic flux linked with the revolving rod is given by

$$\begin{aligned} \frac{d\phi_B}{dt} &= B \cdot \frac{dA}{dt} = B \times (\text{area swept by the rod} \\ &\quad \text{per unit time}) \\ &= B \times (\pi l^2) \cdot n \end{aligned}$$



Fig. 3.43 Revolving copper rod

By Faraday's law of electromagnetic induction, the emf induced across the rod is given by

$$|e| = \frac{d\phi_B}{dt} = B \pi l^2 \cdot n$$

Substituting the given values, we have

$$\begin{aligned} |e| &= 1.0 \times 3.14 \times (1.0)^2 \times 50 \\ &= 157 \text{ Wb/sec} = 157 \text{ V} \end{aligned}$$

3.65 A rectangular iron-core is shown below in Fig. 3.44. It has a mean length of magnetic path of 100 cm, cross-section of (2 cm × 2 cm), relative permeability of 1400 and an air-gap of 5 mm is cut in the core. The three coils carried by the core have number of turns $N_1 = 335$, $N_2 = 600$ and $N_3 = 600$, and the respective currents are $I_1 = 1.6 \text{ A}$, $I_2 = 4.0 \text{ A}$ and $I_3 = 3.0 \text{ A}$. The directions of the currents are as shown. Calculate the flux in the air-gap.

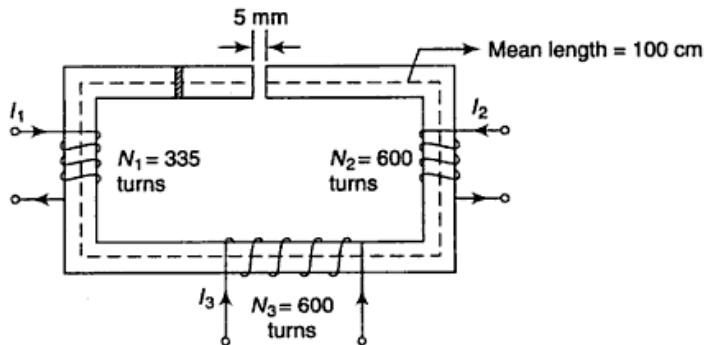


Fig. 3.44 A rectangular iron-core (Ex. 3.65)

Solution

The mmf acting in the magnetic circuit (current considering in the clockwise direction)

$$= \Sigma NI = -335 \times 1.6 + 600 \times 4 - 600 \times 3 = 64 \text{ AT}$$

$$\therefore 64 \text{ AT} = \frac{\phi}{\mu_o A} \left[\frac{l_i}{\mu_r} + l_g \right],$$

where l_i = mean length, μ_r = relative permeability and l_g = air-gap cut length.

$$\begin{aligned} \therefore 64 &= \frac{\phi}{4\pi \times 10^{-7} \times (2 \times 2) \times 10^{-4}} \left[\frac{1}{1400} + 5 \times 10^{-3} \right] \\ &= 1.136 \times 10^7 \phi \end{aligned}$$

$$\begin{aligned} \therefore \text{Flux, } \phi &= \frac{64}{1.136 \times 10^7} = 5.63 \times 10^{-6} \text{ Wb} \\ &= 5.63 \mu \text{ Wb} \end{aligned}$$

■ EXERCISES ■

1. Define mmf, reluctance and permeability. Deduce an expression for the force between two parallel conductors. Explain the significance of reluctance in a magnetic circuit.
2. Compare magnetic and electric circuits.
3. What are the different types of magnetic losses? What is the eddy-current loss? What are the considerable effects of eddy currents? How can they be minimised? Mention some application of eddy currents. How is the different types of losses to be minimised?
4. Explain the terms: magnetic leakage and flux fringing. Derive an expression for the weight which can be lifted by a horse-shoe magnet.
5. Why do magnetic circuits usually have air-gaps? How does the presence of air-gaps affect the magnetic circuit calculations which has higher reluctance an air-gap or an iron path? And why? Prove that $B = \mu H$.
6. Draw and explain the B - H curves for air and a magnetic material.
7. Explain with the aid of a typical B - H curve the meaning of the following terms:
Relative permeability, coercivity, and remanence.
What information can be derived from the B - H loop?
What is meant by magnetic hysteresis?
8. Explain briefly under what conditions it is advantageous to use in a magnetic circuit:
(a) a granulated iron core
(b) a laminated iron core.
9. An air-cooled solenoid has a diameter of 30 cm and a length of 5070 cm and is wound with 3000 turns. If a current of 6 A flow in the solenoid find the energy stored in its magnetic field.

[Hints: Calculate $A = \frac{\pi D^2}{4} = \frac{\pi \times 9 \times 10^{-4}}{9}$

and $L = \frac{\mu_o \cdot \mu_r \cdot N^2 A}{l}$,

have $\mu_o = 4\pi \times 10^{-7} \mu_r = 1$

\therefore Energy stored = $E = \frac{1}{2} LI^2$ J.] [Ans: 2875 J]

10. An air cored torodial coil has 450 turns and a mean diameter of 300 mm and a cross-sectional area of 300 mm². Determine the self-inductance of the coil and the average voltage induced in it when a current of 2 A is reversed in 40 m/sec. [Ans: 8.1 mH; 8.1 mV]

[Hint: $L = \frac{\mu_o \mu_r AN^2}{l} = \frac{4\pi \times 10^{-7} \times 1 \times 300 \times 10^{-6} \times (450)^2}{\pi \times 300 \times 10^{-3}}$ H
= 0.81×10^{-4} H.

emf = $L \frac{di}{dt} = 0.81 \times 10^{-4} \times \frac{2+2}{40 \times 10^{-3}} = 0.0081$ V.]

11. Two identical coils, having 1000 turns each, lie in parallel planes such that 90% flux produced by one coil links with the other. If a current of 4 A flowing in one coil produces a flux of 0.05 m Wb in it, find the magnitude of mutual inductance between the two coils. [Ans: 9 mH]
12. A solenoid of length 1 meter, and diameter 10 cm has 5000 turns. Calculate: (i) the approximate inductance, and (ii) the energy stored in a magnetic field when a current of 2 A flows in the solenoid.

[Ans: $L = 0.247$ H; Energy stored = 0.494 J]

13. The coils having 150 and 200 turns respectively are wound side by side on a closed magnetic circuit of cross-section $1.5 \times 10^{-2} \text{ m}^2$ and mean length 3 m. The relative permeability of the magnetic circuit is 2000. Calculate (a) the mutual inductance between the coils; (b) the voltage induced in the second coil if the current changes from 0 to 10 A in the first coils is 20 m/sec.

[Hints: $N_1 = 150, N_2 = 200$

$$a = 1.5 \times 10^{-2}, l = 3 \text{ m}, \mu_r = 2000$$

$$(a) M = \mu_o \cdot \mu_r \cdot N_1 \cdot N_2 \cdot \frac{a}{l} = 0.377 \text{ H}$$

$$(b) di_1 = 10 - 0 = 10 \text{ A.}$$

$$dt = 20 \text{ ms} = 20 \times 10^{-3} \text{ sec.}$$

$$\therefore e_2 = M \cdot \frac{di_1}{dt} = 188.5 \text{ V}]$$

14. Two coils of negligible resistance and of self-inductances 0.2 H and 0.1 H, are connected in series. If the mutual inductance is 0.1 H, calculate the effective inductance of the combination. [Ans: 0.5 H or 0.1 H]
15. Two coils A and B, each with 100 turns, are mounted so that part of the flux set up by one links the other. When the current through coil A is changed from +2A to -2A in 0.5 second, an emf of 8 mV is induced in coil B, calculate: (i) the mutual inductance between the coils, and (ii) the flux produced in coil B to 2A in coil A. [Ans: $M = 1$ mH; $\phi = 200$ m wb]

[Hints: $N_A = N_B = 100$ turns

$$I_A = 2\text{A}, dI_A = 2 - (-2) = 4 \text{ A}$$

$$dt = 0.5 \text{ sec}, e_M = 8 \times 10^{-3} \text{ V}$$

$$(i) \text{ Now } e_M = M \cdot \frac{di_A}{dt}, M = 1 \times 10^{-3} \text{ H}$$

$$(ii) \text{ Flux induced in B} = \phi_B = \frac{MI_A}{N_B} = 2 \times 10^{-5} \text{ Wb.}$$

16. A coil has 100 turns of wire, and a flux of 5 m Wb linkage with this coil changes to zero in 0.05 second. Determine the self-induced emf in the coil. [Ans: 10 V]
17. Two long single-layer solenoids have the same length and the same number of turns but are placed coaxially one within the other. The diameter of

the inner coil is 60 mm and that of the outer coil is 75 mm. Determine the co-efficient of coupling between the coils. [Ans: 0.8]

18. A coil has a self-inductance of 1 H. If a current of 25 mA is reduced to zero in a time of 12 m/sec, find the average value of the induced voltage across the terminals of the coil. [Ans: 25 V]

19. A conductor of length 300 cm moves at an angle of 30° to the direction of uniform magnetic field of strength 2.0 Wb/m^2 with a velocity of 100 m/sec. Calculate the emf induced. What will be the emf induced if the conductor moves at right angles to the field?

[Hints: (i) $e = Blv \sin 30^\circ = 300 \text{ V}$;

(ii) $e = Blv \sin 90^\circ = 600 \text{ V}$.]

20. A conductor having a length of 80 cm is placed in a uniform magnetic field of 2 Wb/m^2 (Tesla). If the conductor moves with a velocity of 50 m/sec, find the induced emf when it is (i) at right angle (ii) at an angle of 30° and (iii) parallel to the magnetic field. [Ans: 80 V, 40 V and 0 V]

[Hint: $B = 2 \text{ Wb/m}^2$, $l = 0.8 \text{ m}$, $v = 50 \text{ m/sec}$.

(i) $e = Blv = 2 \times 0.8 \times 50 = 80 \text{ V}$

[$\therefore \sin \theta = \sin 90^\circ = 1$]

(ii) $e = 80 \sin 30^\circ = 40 \text{ V}$;

(iii) $e = 80 \sin 0^\circ = 0$.]

21. Calculate the mmf required to produce a flux of 0.01 Wb across an air-gap of 2 mm. of length having an effective area of 200 cm^2 of a wrought iron ring of mean iron path of 0.5 m and cross-sectional area of 125 cm^2 . Assume a leakage co-efficient of 1.25. The magnetization curve of the wrought iron is given below:

$B(\text{Wb/m}^2)$:	0.6	0.8	1	1.2	1.4
$H(\text{AT/m})$:	75	125	250	500	1000

[Ans: 921.18 AT]

[Hint: $\phi = 0.01 \text{ Wb}$

$$\text{Air-gap: } H = \frac{B}{\mu_o} = \frac{\phi}{A \cdot \mu_o} = \frac{0.01}{200 \times 10^{-4} \times 4\pi \times 10^{-7}} \text{ AT/m}$$

$$= 3.98 \times 10^5 \text{ AT/m.}$$

$$\text{Total AT required} = 3.98 \times 10^5 \times 2 \times 10^{-3} = 796.178$$

$$\text{Iron path: } B = \frac{0.01 \times 1.25}{125 \times 10^{-4}} \text{ Wb/m}^2 = 1 \text{ Wb/m}^2$$

$$\therefore H = 250 \text{ AT/m}$$

$$\text{Total AT required} = 250 \times 0.5 = 125$$

$$\text{Total mmf} = 796.178 + 125 = 921.178]$$

22. (a) An iron ring, having a mean diameter of 75 cm and a cross-sectional area of 5 cm^2 is wound with a magnetizing coil of 120 turns. Using the following data, calculate the current required to set-up a magnetic flux of $630 \mu \text{ Wb}$ in the ring.

Flux density (T)	0.9	1.1	1.2	1.3
A/m	260	450	600	820

- (b) The air gap in a magnetic circuit is 1.1 m long and 20 cm² in cross-section. Calculate (i) the reluctance of the air-gap and (ii) the ampere turns required to send a flux of 700 μ Wb across the air-gap.
[Ans: a = 4.5 A. (b) 4.375×10^5 A/Wb, 306 A]
23. A mild steel having a cross-sectional area of 10 cm² and a mean circumference of 60 cm has a coil of 300 turns wound around it. Determine
- reluctance of the steel ring,
 - current required to produce a flux of 1 mole in the ring. Relative permeability of the given steel is 400 at the flux density developed in the core.
 - if a slit of 1 mm. is cut in the ring, what will be the new value of current? Assume no fringing effect.
- [Ans: 119.43×10^4 A/Wb; 3.98 A; 6.635 A]

$$[\text{Hint: (i) Reluctance} = \frac{l}{\mu_o \mu_r a}]$$

$$= \frac{0.6}{4\pi \times 10^{-7} \times 400 \times 10 \times 10^{-4}} \text{ A/Wb}$$

$$= 119.426 \times 10^4 \text{ A/Wb}$$

$$\text{(ii) } AT = 1 \times 10^{-3} \times 119.426 \times 10^4 = 1194.26$$

$$I = \frac{1194.26}{300} \text{ A} = 3.98 \text{ A}$$

$$\text{(iii) Reluctance of iron path} = \frac{1 \times 10^{-3}}{4\pi \times 10^{-7} \times 10 \times 10^{-4}} \text{ A/Wb}$$

$$= 79.62 \times 10^4 \text{ A/Wb}$$

$$AT \text{ for air gap} = 79.62 \times 100 \times 1 \times 10^{-3} = 796.2.$$

$$\therefore I = \frac{1194.26 + 796.2}{300} = 6.635 \text{ A.}]$$

24. A magnetic circuit has an area of 10 cm² and length of 0.2 m. If $\mu_r = 2000$, find the reluctance. [Ans: 0.79×10^5 A/Wb]
25. Find out the inductance and energy stored in the magnetic field of an air-cored solenoid of 100 cm long, 10 cm in diameter and some wound with 900 turns and a current of 7.5 A is passing through the solenoid.
[Ans: $L = 8$ mH; $E = 0.225$ J]

[Hints: Inductance of solenoid

$$L = \frac{N^2 \cdot A \cdot \mu_o \cdot \mu_r}{l} = 0.008 \text{ H}$$

$$\text{and energy stored} = E = \frac{1}{2} LI^2 = 0.225 \text{ J}]$$

26. A circuit has 2000 turns enclosing a magnetic circuit of 30 cm² sectional area. When with 5A, the flux density is 1.2 Wb/m² and 10³ A it is

1.7 Wb/m², find the mean value of the inductance between these current limits and the induced emf if the current falls from 10 A to 4 A in 0.08 sec.

$$[Hints: \quad L = N \cdot \frac{d\phi}{dt} = N \cdot \frac{d(BA)}{dt} = NA \frac{dB}{dt}]$$

$$\text{here} \quad dB = 1.7 - 1.2 \text{ and } dt = 10 - 5$$

$$\therefore \quad L = 0.6 \text{ H}$$

$$\text{again} \quad dI = 10 - 4 = 6 \text{ A and } dt = 0.08$$

$$\therefore \quad e_L = L \cdot \frac{dI}{dt} = 45 \text{ V}]$$

27. An iron ring of mean length 200 cm and circular cross-section of area 15 cm² has an air gap of 6 mm and a winding of 200 turns. Calculate the inductance of the coil. μ_r for iron is given as 800. [Ans: 200 V]

28. A conductor 1.5 m long carries a current of 50 A at right angles to a magnetic field of density 1.2 T. Calculate the force on the conductor.

$$[Ans: F = 90 \text{ N}]$$

$$[Hints: F = BIl \sin \theta]$$

29. A horseshoe electromagnet is required to lift a 200 kg weight. Find the exciting current required if the electromagnet is wound with 500 turns. The magnetic length of the electromagnet is 60 cm and is of permeability 500. The reluctance of the load can be neglected. The pole face has a cross-section 20 sq. cm. [Ans: 2.35 A]

$$[Hint: \quad F = 2 \times \frac{B^2 A}{2\mu_0} = \frac{B^2 A}{\mu_0}]$$


$$\therefore \quad B^2 = \frac{\mu_0 F}{A} = \frac{4\pi \times 10^{-7} \times 200 \times 9.81}{20 \times 10^{-4}}$$

$$\text{or} \quad B = 1.232 \text{ Wb/m}^2$$

$$H = \frac{B}{\mu_0 \mu_r} = \frac{1.232}{4\pi \times 10^{-7} \times 500} = 1961.78 \text{ AT/m}$$

$$\text{Total AT} = 1961.78 \times 0.6 = 1177$$
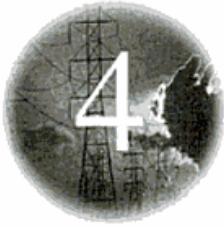
$$I = \frac{1177}{500} = 2.35 \text{ A.}]$$



DC NETWORK ANALYSIS

.....

4.1 INTRODUCTION

When a number of network elements* are connected together to form a system that consists of set(s) of interconnected elements performing specific or assigned functions, it is called a “network”. An electrically closed network is a “circuit”. An electrical network is a combination of numerous electric elements (e.g., resistance R , inductance L , capacitance C , etc.).

Some important definitions related to an electrical network are as follows:

Node: It is the junction in a circuit where two or more network elements are connected together.

Branch: It is that part of the circuit which lies between two junctions in a circuit.

Loop: It is a closed path in a circuit in which no element or node is encountered more than once.

Mesh: It is such a loop that contains no other loop within it.

4.2 CHARACTERISTICS OF NETWORK ELEMENTS

4.2.1 Linear and Non-linear Elements

A *linear element* shows linear characteristics of voltage vs current. Thus the parameters of linear elements remain constant (i.e., the parameters do not change with voltage or current applied to that element). Resistors, inductors and capacitors are linear elements.

On the other hand, for a *non-linear element*, the current passing through it does not change linearly with the linear change in applied voltage across it, at a particular temperature and frequency. In a non-linear element the parameters change with applied voltage and current changes. Semiconductor devices like diodes, transistors, thyristors, etc. are typical examples of non-linear elements. Ohm's law is not valid for non-linear elements.

*A network element is a component of a circuit having different characteristics like linear, non-linear, active or passive etc. and will be defined shortly.

4.2.2 Active and Passive Elements

If a circuit element has the capability of enhancing the energy level of an electric signal passing through it, it is called an *active element*, viz., a battery, a transformer, semiconductor devices, etc. Otherwise the element that simply allows the passage of the signal through it without enhancement is called *passive element* (viz., resistors, inductors, thermistors and capacitors). Passive elements do not have any intrinsic property of boosting an electric signal.

4.2.3 Unilateral and Bilateral Elements

If the magnitude of the current passing through an element is affected due to change in polarity of the applied voltage, the element is called a *unilateral element*. On the other hand if the current magnitude remains the same even if the polarity of the applied voltage is reversed, it is called a *bilateral element*. Unilateral elements offer varying impedances with variation in the magnitude or direction of flow of the current while bilateral elements offer same impedance irrespective of the magnitude or direction of flow of current. A resistor, an inductance and a capacitor, all are bilateral elements while diodes, transistors, etc. are unilateral elements.

4.3 SERIES RESISTIVE CIRCUITS

Resistors are said to be in *series* when they are connected in such a way that there is only one path through which current can flow. Therefore the current in a series circuit is the same at all parts in the circuit. The voltage drop across each component in a series circuit depends on the current levels and the component resistance (or impedance).

4.3.1 Currents and Voltages in a Series Circuits

The circuit diagram for three series connected resistors and a d.c. voltage source is shown in Fig. 4.1.

The total resistance connected across the voltage source is $R = R_1 + R_2 + R_3$. (R is called the *equivalent resistance* in ohms for the given circuit.)

For a series circuit with n resistors, the equivalent resistance R is thus

$$R = R_1 + R_2 + R_3 + \cdots + R_n \quad (4.1)$$

The equivalent circuit for the series resistance circuit is shown in Fig. 4.2.

The equivalent circuit consists of the voltage source E and the equivalent resistance R . The current I flows from the positive terminal of the voltage source. Using Ohm's law the current through the series circuit in ampere is obtained as

$$I = \frac{E}{R} = \frac{E}{R_1 + R_2 + R_3 + \cdots + R_n} \quad (4.2)$$

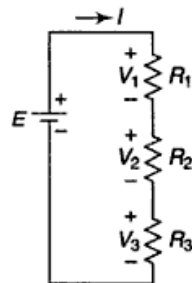


Fig. 4.1 A simple series resistive circuit

There is only one path for current flow in a series circuit.

The current flow causes a voltage drop V or *potential difference* across each resistor in the circuit of Fig. 4.1. Using Ohm's law, the voltage drops across each resistor in volts are obtained as

$$V_1 = IR_1, V_2 = IR_2 \text{ and } V_3 = IR_3.$$

Since the sum of the resistive voltage drops is equal to the applied emf, for any series circuit,

$$E = V_1 + V_2 + V_3 + \dots + V_n$$

$$\text{or } E = I(R_1 + R_2 + R_3 + \dots + R_n).$$

Next we consider series connection of voltage sources instead of series connection of resistors.

If three voltage sources are connected in series as shown in Fig. 4.3, the resultant voltage in volt is

$$E = E_1 + E_2 + E_3.$$

In Fig. 4.4 the lowermost voltage source E_3 has its negative terminal connected to the negative terminal of the middle cell. The resultant voltage in this case is

$$E = E_1 + E_2 - E_3$$

In Fig. 4.3 the voltage sources assist one another to produce the circuit current, so they are said to be "series aiding". In Fig. 4.4 the bottommost voltage source will attempt to produce current in the opposite direction to that formed by the other two. Therefore this bottommost source is connected in "series opposing" with the top two cells.

4.3.2 Voltage Divider

In Fig. 4.5 two series connected resistors are used as a *voltage divider* or *potential divider*.

Here,

$$V_1 = IR_1 = \frac{E}{R_1 + R_2} \cdot R_1$$

$$\left[\because I = \frac{E}{R_1 + R_2} \right]$$

Also

$$V_2 = IR_2 = \frac{E}{R_1 + R_2} \cdot R_2$$

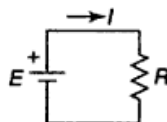


Fig. 4.2 Equivalent of a simple series resistive circuit

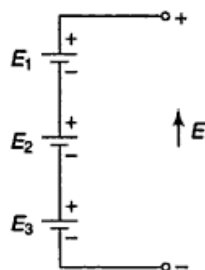


Fig. 4.3 Series connection of three-voltage sources

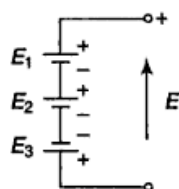


Fig. 4.4 Series connections of three voltage sources with the polarity of one source reversed

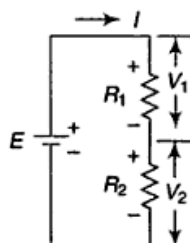


Fig. 4.5 Voltage divider (or potential divider) circuit

If $R_1 = R_2$ then $V_1 = V_2 = \frac{E}{2}$.

When n number of resistors are connected in series then voltage drop (V_i) across any resistance (R_i) is given by

$$V_i = E \times \frac{R_i}{R_1 + R_2 + R_3 + \dots + R_n} \quad (4.4)$$

V_i and E are expressed in volt and resistors are given in ohms.

Voltage Divider Theorem

In a series circuit, the portion of applied emf developed across each resistor is the ratio of that resistor's value to the total series resistance in the circuit.

4.3.3 Potentiometer

The circuit diagram of a variable resistor employed as a *potentiometer* is shown in Fig. 4.6. The *potentiometer* is essentially a single resistor with terminals at each end and a movable contact that can be set to any point on the resistor. Terminals A and B are the end terminals and terminals C is the adjustable contact (Fig. 4.6).

The output voltage (V_o), in volt, is given as

$$V_o = E \times \frac{R_2}{R_1 + R_2} \quad (4.5)$$

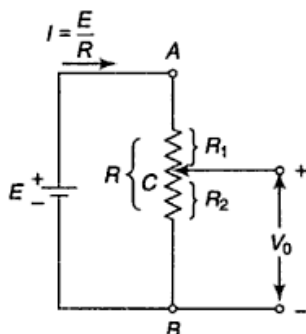


Fig. 4.6 A simple potentiometric circuit

If the moving contact is half way between the two end terminals then

$$R_1 = R_2 = \frac{R}{2}$$

or
$$V_o = E \times \frac{1}{2}$$

When $R_2 = R$, $V_o = E$

and when $R_2 = 0$, $V_o = 0$

Thus it is seen that the potentiometer can be adjusted to give an output voltage ranging linearly from 0 to E.

4.3.4 Power in a Series Circuit

In Fig. 4.5, the power (VA) dissipated in R_1 is given by

$$P_1 = V_1 I = \frac{V_1^2}{R_1} = I^2 R_1$$

\therefore For any series circuit containing n number of resistors the power dissipated is

$$\begin{aligned} P &= P_1 + P_2 + P_3 + \dots + P_n \\ &= V_1 I + V_2 I + V_3 I + \dots + V_n I \\ &= I(V_1 + V_2 + V_3 + \dots + V_n) \\ &= IE \end{aligned}$$

$$\therefore P = \frac{E^2}{R_1 + R_2 + R_3 + \dots + R_n} \quad (4.6)$$

In dc circuit volt-ampere power (VA) is same as power expressed in watts. Thus P is usually expressed in watts in dc circuits.

4.3.5 Current-limiting Resistor

Sometimes a resistor is included in series with an electrical circuit or electronic device to drop the supply voltage down to a desired level. This resistor can be treated as a *current-limiting resistor*.

In Fig. 4.7, R_s provides a voltage drop to the series connected lamps L_1 and L_2 . The lamps operate to a voltage level lower than the source voltage even in series connection. Also the resistor R_s limits the current I to the level required by the lamps.

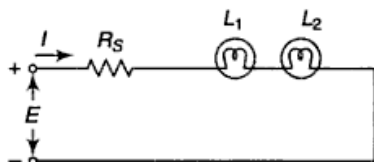


Fig. 4.7 Application of current-limiting resistor R_s

Here circuit current in ampere is obtained as

$$I = \frac{E}{R_s + (\text{sum of resistances of lamps})}$$

$$\text{or } R_s = (E/I) - (\text{sum of resistances of lamps}) \quad (4.7)$$

4.3.6 Open Circuits and Short Circuits in a Series Circuit

An *open circuit* occurs in a series resistance circuit when one of the resistors (or any series network element) becomes disconnected from the adjacent one. Open circuit can also occur when one of the resistors (or an element) has been destroyed by excessive power dissipation.

In the circuit shown in Fig. 4.8, the open circuit can be thought of another resistance in series with

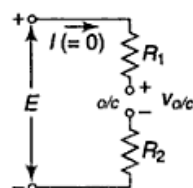


Fig. 4.8 An open circuit

value "infinity". Therefore the current, $I = \frac{E}{R_1 + R_2 + \infty} = 0$.

The voltage drop across the open circuit ($V_{O/C}$) in volts is obtained as

$$V_{O/C} = E - IR_1 = E - 0 = E$$

Figure 4.9 shows a series resistance R_3 short circuited in the series circuit. Here the resistance between the terminals of R_3 becomes zero after short circuit. Therefore, the circuit current I in ampere is given by

$$I = \frac{E}{R_1 + R_2 + 0} = \frac{E}{R_1 + R_2}$$

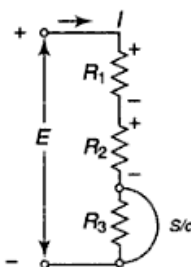


Fig. 4.9 Deactivation of a resistance (R_3) in a series circuit by shorting terminals of R_3

4.1 Find the current that flows through the resistors $10\ \Omega$, $20\ \Omega$, and $30\ \Omega$ connected in series across a 240 V supply.

Solution

$$\text{Current } I = \frac{V}{10 + 20 + 30} \text{ A} = \frac{240}{10 + 20 + 30} = 4\text{ A}$$

4.2 Determine the voltage drops across each resistor of the circuit shown in Fig. 4.10.

Solution

The current flowing through each resistor is given as

$$I = \frac{100}{5 + 2 + 3} \text{ A} = 10\text{ A}$$

Voltage drop across the $5\ \Omega$ resistor $= 10 \times 5 = 50\text{ V}$

Voltage drop across the $2\ \Omega$ resistor $= 10 \times 2 = 20\text{ V}$

Voltage drop across the $3\ \Omega$ resistor $= 10 \times 3 = 30\text{ V}$

Polarities are marked in Fig. 4.10(a). Check that total voltage drop is 100 V , same as the supply voltage.

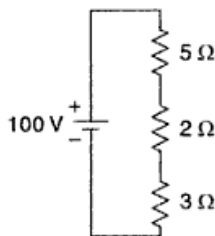


Fig. 4.10 Circuit of Ex. 4.2

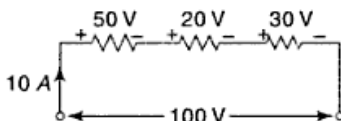


Fig. 4.10(a) Voltage drops for the series circuit shown in Fig. 4.10

4.3 In the circuit shown in Fig. 4.11, if $E_1 = 10\text{ V}$ and $E_2 = 7\text{ V}$, find the current through the resistors.

Solution

The current through the resistors

$$I = \frac{E_1 + E_2}{R_1 + R_2 + R_3} = \frac{10 + 7}{2 + 7 + 3} \text{ A} = 1.4167\text{ A}$$

(Note that E_1 and E_2 are in series aiding connection.)

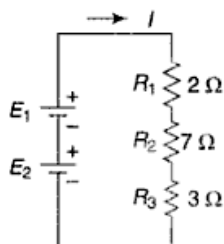


Fig. 4.11 Circuit of Ex. 4.3

4.4 Determine the current through the resistors in the circuit shown in Fig. 4.11 when the polarity of E_2 is reversed.

Solution

$$\text{Current } I = \frac{E_1 - E_2}{R_1 + R_2 + R_3} = \frac{10 - 7}{2 + 7 + 3} \text{ A} = 0.25\text{ A}$$

(this time E_1 and E_2 are in series opposition.)

4.5 Calculate the minimum and maximum values of V_o that can be obtained from the circuit shown in Fig. 4.12. P is the moving contact and can slide linearly along a $300\ \Omega$ resistor.

Solution

By inspection it is evident that, if P is at the bottommost point of $300\ \Omega$ resistor, V_o is minimum.

$$\therefore V_{o(\min)} = 240 \times \frac{800}{800 + 300 + 500} = 120\text{ V.}$$

On the other hand, if P is at the topmost point of $300\ \Omega$ resistor, V_o is maximum.

$$V_{o(\max)} = 240 \times \frac{800 + 300}{800 + 300 + 500} = 165\text{ V.}$$

It is possible to obtain values of (V_o) between 120 V and 165 V by sliding P suitably across the $300\ \Omega$ resistor.

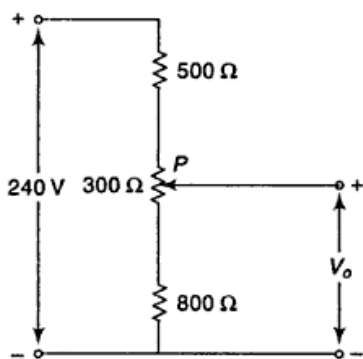


Fig. 4.12 Circuit of Ex. 4.5

4.6 Determine the power dissipated in each resistor of Fig. 4.11 and also find the total power.

Solution

Power dissipated across the $2\ \Omega$ resistor in Fig. 4.11 is $I^2 \times 2$, i.e., $(1.4167)^2 \times 2$, i.e., 4.014 W. (The value of circuit current has been obtained in Ex 4.3 as 1.4167 A.)

Power dissipated across the $7\ \Omega$ resistor is $I^2 \times 7$, i.e., $(1.4167)^2 \times 7$ or 14.05 W.

Similarly, power dissipated in the $3\ \Omega$ resistor is $(1.4167)^2 \times 3$, i.e., 6.02 W.

Total power is $(E \times I)$, i.e., $(E_1 + E_2) \times I$.

This gives $(10 + 7) \times 1.4167$, i.e., 24.084 W.

[Check: Total power is $I^2(2 + 7 + 3)$, i.e., $(1.4167)^2 \times 12$ or 24.085 W.]

4.7 In the circuit shown in Fig. 4.13 find the value of the resistor R so that the lamps L_1 and L_2 operate at rated conditions. The rating of each of the lamps is 12 V, 9 W. If L_2 becomes short circuited find the current through the circuit and the power dissipated in each of the lamps.

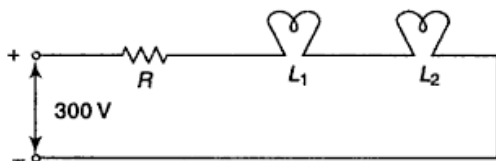


Fig. 4.13 Circuit of Ex. 4.7

Solution

Voltage rating of the lamps is 12 V each, while power rating of each of the lamps is 9 W.

If I be the rated current through the lamps then

$$VI = P$$

$$\text{or } I = \frac{P}{V} = \frac{9}{12} = 0.75\text{ A}$$

If R_L be the resistance of each lamp,

$$I^2 R_L = 9 \text{ or, } R_L = \frac{9}{(0.75)^2} \Omega$$

$$= 16\ \Omega.$$

Supply voltage = 300 V (given)

∴ Voltage across resistor (R) is $(300 - 2 \times 12)$ i.e., 276 V

Also, current through R is 0.75 A

$$\therefore R = \frac{276}{0.75} \Omega = 368 \Omega.$$

If L becomes short circuited, resistance across terminals of L_2 is 0.

If the current now is I' , we can write

$$300 = I'(R + R_L) = I'(368 + 16)$$

or $I' = 0.78$ A.

Power dissipated in L_1 is now $(0.78)^2 \times 16 = 9.73$ W (L_1 will glow brighter)

Power dissipated in L_2 is obviously 0.

4.4 PARALLEL RESISTANCE CIRCUITS

Resistors are said to be connected in parallel when equal voltages appear across each resistor (or network element). The total current taken from the supply is the sum of all the individual resistor or network elements' currents.

4.4.1 Currents and Voltages in Parallel Circuits

Resistors are said to be connected in parallel when the circuit has two terminals which are common to each resistor. Figure 4.14 represents a circuit having three resistors connected in parallel.

The voltage across each resistor is E volts and the current through R_1 is I_1 , through R_2 is I_2 and through R_3 is I_3 .

$$\therefore I_1 = \frac{E}{R_1}, I_2 = \frac{E}{R_2} \quad \text{and} \quad I_3 = \frac{E}{R_3}$$

The current supplied by the battery in ampere is $(I) = I_1 + I_2 + I_3$

If R be the equivalent resistance (in ohms) of the circuit in Fig. 4.14,

$$I = \frac{E}{R} = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3}$$

$$\text{or} \quad \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\text{or} \quad R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}. \quad (4.8)$$

The equivalent circuit is shown in Fig. 4.15.

If n resistors are connected in parallel then we have

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n} \quad (4.9)$$

where R is the equivalent resistance.

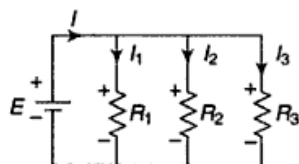


Fig. 4.14 The resistors in parallel connection

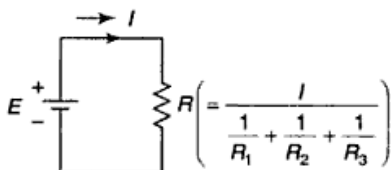


Fig. 4.15 Equivalent circuit of three resistances in a parallel circuit

Therefore, the reciprocal of the equivalent resistance of resistors in parallel connection is equal to the sum of the reciprocals of the individual resistances.

4.4.2 Conductances in Parallel

In dc circuits *conductance* is the reciprocal of resistance and its unit is "Siemens" (S) in SI units or "mho" in cgs units. If $G_1, G_2, G_3, \dots, G_n$ be the conductances of the resistors connected in parallel then the equivalent conductance (G) in Siemens is given by

$$G = G_1 + G_2 + G_3 + \dots + G_n \quad (4.10)$$

According to Ohm's law, $I = \frac{V}{R} = VG$, where V is the applied voltage, G is the equivalent conductance of a parallel circuit, and I is the source current.

4.4.3 Current Divider

Parallel resistance circuits are often called *current divider circuits* because the supply current is divided among the parallel branches.

The circuit in Fig. 4.16 can be called as a current divider circuit. Here

$$I_1 = \frac{E}{R_1} \quad \text{and} \quad I_2 = \frac{E}{R_2}$$

Again,

$$\begin{aligned} I &= I_1 + I_2 \\ &= \frac{E}{R_1} + \frac{E}{R_2} = E \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \end{aligned}$$

or

$$I = E \frac{R_1 + R_2}{R_1 \times R_2}$$

or

$$E = I \times \frac{R_1 R_2}{R_1 + R_2} = IR.$$

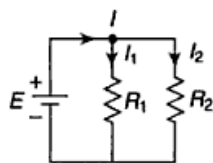


Fig. 4.16 Concept of current division

$$\left[\text{If } (R) \text{ be the equivalent resistance then, } R = \frac{R_1 R_2}{R_1 + R_2} \right]$$

$$\text{Now,} \quad I_1 = \frac{E}{R_1} = \frac{1}{R_1} (I) \times \frac{R_1 R_2}{R_1 + R_2} = I \frac{R_2}{R_1 + R_2} \quad (4.11)$$

$$\text{Similarly} \quad I_2 = I \frac{R_1}{R_1 + R_2} \quad (4.12)$$

I_1 and I_2 are the currents in the branches of this current divider circuit in amperes.

These two equations (4.11 and 4.12) can be used to determine how a known supply current is divided into two individual currents through parallelly connected resistors or network elements.

If G_1 and G_2 be the conductances of the resistors R_1 and R_2 ,

$$I_1 = I \frac{\frac{1}{G_2}}{\frac{1}{G_1} + \frac{1}{G_2}} = \frac{G_1}{G_1 + G_2} \cdot I \quad (4.13)$$

and

$$I_2 = I \frac{\frac{1}{G_1}}{\frac{1}{G_1} + \frac{1}{G_2}} = \frac{G_2}{G_1 + G_2} \cdot I. \quad (4.14)$$

If there are n number of resistors with conductances G_1, G_2, \dots, G_n connected in parallel across a voltage source then current in any resistor with conductance G_i is

$$I_i = \frac{G_i}{G_1 + G_2 + G_3 + \dots + G_n} \cdot I \quad (4.15)$$

[I being the supply current in ampere while I_i is the current through G_i].

4.4.4 Power in Parallel Circuits

For the circuit in Fig. 4.14, the power (in VA) across resistor R_1 is given by

$$P_1 = EI_1 = \frac{E^2}{R_1} = I_1^2 R_1$$

Total power $P = E(I_1 + I_2 + I_3)$

$$= E^2 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = I_1^2 R_1 + I_2^2 R_2 + I_3^2 R_3$$

$$= P_1 + P_2$$

When n resistors are connected in parallel

$$P = P_1 + P_2 + P_3 + \dots + P_n \quad (4.16)$$

(P) can be expressed in VA or in Watts in dc circuits.

4.4.5 Open Circuits and Short Circuits in Parallel Circuits

When one of the components in a parallel resistive circuit is open circuited, as shown in Fig. 4.17, no current flows through that branch. The other branch currents are not affected by the open circuit as they still have the normal supply voltage applied across each of them. In Fig. 4.17, $I_1 = 0$. Supply current $I = I_2 + I_3$. All currents are expressed in amperes.

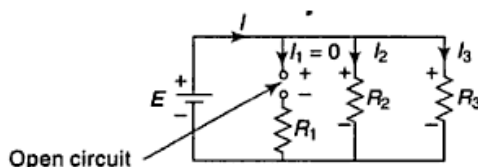


Fig. 4.17 Open circuit in a branch in a parallel resistive circuit

Figure 4.18 shows a short circuit across resistor (R_3).

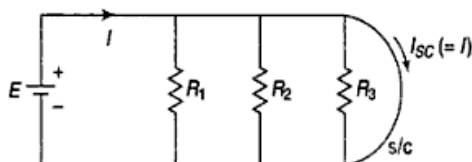


Fig. 4.18 Short circuit in a branch in a parallel circuit

As there is a short circuited path across R_3 , i.e., across one of the resistors in the parallel circuit, no current will flow through resistors R_1 , R_2 and R_3 . Total current will flow from the battery through the short circuited path and the current ($I_{SC} = I = E/0 = \infty$). However, in practice this current is limited by the internal resistance of the battery and lead resistances of the wires. If the internal resistance of the battery be taken only and is equal to R_i , then current $I = E/R_i$ which is also very high (as the internal resistance of a battery is very small).

4.8 Calculate the total current supplied by the battery in Fig. 4.19.

Solution

$$I_1 = \frac{24}{2} \text{ A} = 12 \text{ A}, I_2 = \frac{24}{3} \text{ A} = 8 \text{ A} \text{ and}$$

$$I_3 = \frac{24}{6} \text{ A} = 4 \text{ A}$$

\therefore The total current $I = I_1 + I_2 + I_3 = (12 + 8 + 4) \text{ A} = 24 \text{ A}$

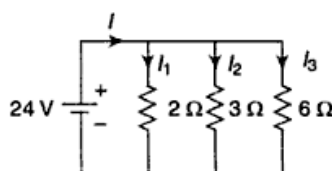


Fig. 4.19 Circuit of Ex. 4.8

4.9 Determine the equivalent resistance of the four resistances connected in parallel across a 240 V supply. Also find the total current. The resistances are of 10 Ω , 15 Ω , 25 Ω and 40 Ω .

Solution

The equivalent resistance

$$R = \frac{1}{\frac{1}{10} + \frac{1}{15} + \frac{1}{25} + \frac{1}{40}} = \frac{1}{0.1 + 0.067 + 0.04 + 0.025} = 4.31 \Omega$$

$$\text{Total current } I = \frac{E}{R} = \frac{240}{4.31} \text{ A} = 55.68 \text{ A.}$$

4.10 Three resistors of conductances 0.1 Siemens, 0.2 Siemens and 0.5 Siemens are connected in parallel. Calculate the equivalent resistance of the circuit.

Solution

$$\begin{aligned} \text{Equivalent conductance } (G) &= G_1 + G_2 + G_3 \\ &= 0.1 + 0.2 + 0.5 = 0.8 \text{ Siemens} \end{aligned}$$

$$\text{Equivalent resistance } R = \frac{1}{G} = \frac{1}{0.8} \Omega = 1.25 \Omega.$$

4.11 Using the current divider rule find the current in the resistors R_1 and R_2 connected in parallel across a voltage source. The supply current is 50 A, $R_1 = 10 \Omega$ and $R_2 = 20 \Omega$.

Solution

Total current $I = 50$ A

$$\begin{aligned}\text{Current through resistor } R_1 \text{ is } (I_1) &= I \times \frac{R_2}{R_1 + R_2} \\ &= 50 \times \frac{20}{20 + 10} \\ &= 33.33 \text{ A}\end{aligned}$$

$$\begin{aligned}\text{Current through resistor } R_2 \text{ is } (I_2) &= I \times \frac{R_1}{R_1 + R_2} \\ &= 50 \times \frac{10}{10 + 20} \\ &= 16.67 \text{ A}\end{aligned}$$

4.12 In the circuit shown in Fig. 4.19 find the power dissipated across each resistor and the total power.

Solution

$$\begin{aligned}\text{Power dissipated across } 2 \Omega \text{ resistor } (P_1) &= I_1^2 \times 2 = (12)^2 \times 2 \\ &= 288 \text{ W.}\end{aligned}$$

$$\begin{aligned}\text{Power dissipated across } 3 \Omega \text{ resistor } (P_2) &= I_2^2 \times 3 = (8)^2 \times 3 \\ &= 192 \text{ W.}\end{aligned}$$

$$\begin{aligned}\text{Power dissipated across } 6 \Omega \text{ resistor } (P_3) &= I_3^2 \times 6 = (4)^2 \times 6 \\ &= 96 \text{ W.}\end{aligned}$$

$$\begin{aligned}\text{Total power } (P) &= P_1 + P_2 + P_3 \\ &= 288 + 192 + 96 = 576 \text{ W.}\end{aligned}$$

[The values of I_1 , I_2 , and I_3 have been obtained as 12 A, 8 A and 4 A in Ex 4.8]. Also, $(P) = EI = 24 \text{ V} \times 24 \text{ A} = 576 \text{ W}$ (check).

4.5 SERIES-PARALLEL CIRCUITS

Series-parallel resistive circuits consist of combinations of series connected and parallel connected resistors (or other passive network elements). Figure 4.20 represents a simple series-parallel resistive circuit. In this circuit R_2 and R_3 are connected in parallel. The parallel combination of R_2 and R_3 is $R_2 R_3 / (R_2 + R_3)$ ($= R_{eq}$).

The equivalent circuit is shown in Fig. 4.21.

Since R_1 and R_{eq} are connected in series, therefore the equivalent resistance of the whole circuit is $[(R_1 + R_{eq}) \Omega]$.

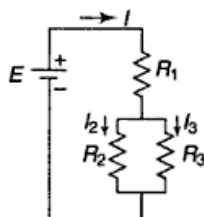


Fig. 4.20 A series parallel circuit

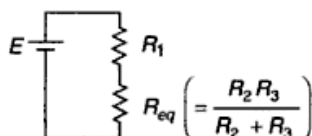


Fig. 4.21 Equivalent of series-parallel circuit

4.5.1 Currents and Voltages in Series-parallel Circuits

In Fig. 4.20 the supply current I flows through resistance R_1 . Then I splits into I_2 and I_3 flowing through R_2 and R_3 respectively.

Obviously, $I = I_2 + I_3$, I being expressed in amps

The currents I_2 and I_3 can easily be calculated using the current divider rule.

The voltage across resistor R_1 is given by $V_1 = IR_1$

The voltage across resistors R_2 and R_3 are equal as they are connected in parallel. Here

$$V_2 = V_3 = I_2 R_2 = I_3 R_3$$

Also, $E = V_1 + V_2 = V_1 + V_3$.

Once the branch currents are known, the voltages across each resistor can easily be calculated.

4.5.2 Open Circuits and Short Circuits in a Series Parallel Circuit

The effect of open circuit in a series-parallel circuit is shown in Fig. 4.22(a) and Fig. 4.22(b).

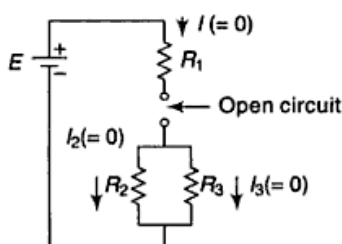


Fig. 4.22(a) Open circuit in series-parallel circuit

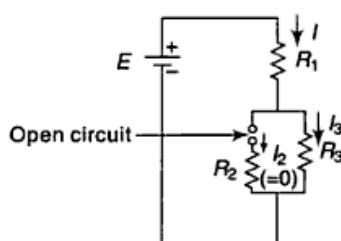


Fig. 4.22(b) Open circuit in a branch of series-parallel circuit

In Fig. 4.22(a), open circuit occurs at one terminal of R_1 . This has the same effect as an open circuit in the supply line, so that the main current flowing in any part of the circuit is zero. Also as the main current is zero there is no voltage drop across the resistors and the supply voltage E appears across the open circuit.

When open circuit occurs at one end of one of the parallel resistors, as shown in Fig. 4.2(b), the current through that resistor only is zero. Here, $I_2 = 0$.

Also, R_1 and R_3 can be assumed to be connected in series.

Hence
$$I = I_3 = \frac{E}{R_1 + R_3}$$

As there is no current through R_2 so there is no voltage drop across it and the voltage across the open circuit is equal to the voltage across R_3 , i.e. V_3 .

When short circuit occurs across the terminals of R_1 as shown in Fig. 4.23(a), the resistance across the terminals of R_1 is 0.

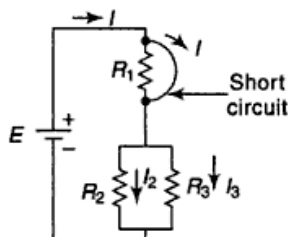


Fig. 4.23(a) Short circuit in series part of series-parallel circuit

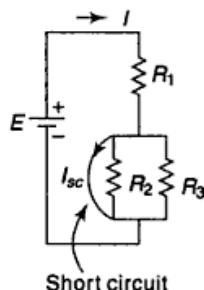


Fig. 4.23(b) Short circuit in a parallel branch of a series-parallel circuit

The total current is obtained as, $I = \frac{E}{R_2 \parallel R_3} = \frac{E}{R_2 R_3 / (R_2 + R_3)}$

$$I_2 = I \cdot \frac{R_3}{R_2 + R_3} \quad \text{and} \quad I_3 = I \cdot \frac{R_2}{R_2 + R_3}$$

When short circuit occurs across the terminals of R_2 , as shown in Fig. 4.23(b), the resistance across the terminals of R_2 is 0. Therefore no current will pass through R_3 as there is a short circuited path in parallel with it.

Hence
$$I = \frac{E}{R_1};$$

also,
$$I_3 = 0 = I_2$$

If I_{sc} be the current in amps through the short circuited path then $(I_{sc}) (= I) = \frac{E}{R_1}$.

4.5.3 Analysis of a Series Parallel Circuit

The following are the steps for solving series-parallel circuits.

1. Draw a circuit diagram identifying all components by number and showing all currents and resistor voltage drops.
2. Convert all series branches of two or more resistors into a single equivalent resistance.
3. Convert all parallel combinations of two or more resistors into a single equivalent resistance.
4. Repeat procedures 2 and 3 until the desired level of simplification is achieved.

The final circuit should be simple series or parallel circuit. Once the current through each equivalent resistance or the voltage across it is known, the original circuit can be used to determine individual resistor currents and voltages.

4.13 Find the supply current and the currents in the parallel branches in the circuit shown in Fig. 4.24.

Solution

In the circuit shown in Fig. 4.24, $10\ \Omega$ and $20\ \Omega$ are in parallel. The equivalent resistance of the parallel combination is $\frac{10 \times 20}{10 + 20} = \frac{200}{30}\ \Omega = 6.67\ \Omega$. $5\ \Omega$ and $6.67\ \Omega$ are now in series as shown in Fig. 4.24(a)

The supply current is $I = \frac{100}{5 + 6.67}\ \text{A} = 8.57\ \text{A}$

From Fig. 4.24,

$$I_1 = 8.57 \times \frac{20}{10 + 20} = 5.71\ \text{A}$$

$$I_2 = 8.57 \times \frac{10}{10 + 20} = 2.857\ \text{A}$$

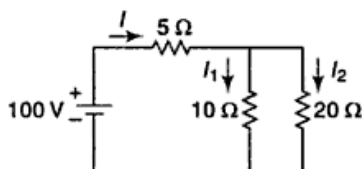


Fig. 4.24 Circuit of Ex. 4.13

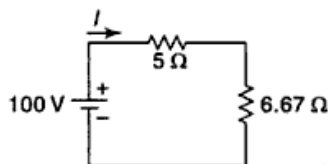


Fig. 4.24(a) Equivalent circuit of the series-parallel circuit of Fig. 4.24

4.14 Find all resistor currents and voltages in the circuit shown in Fig. 4.25.

Solution

The parallel combination of $1\ \Omega$ and $2\ \Omega$ is $\frac{1 \times 2}{1 + 2} = \frac{2}{3}\ \Omega$.

The parallel combination of $5\ \Omega$ and $10\ \Omega$ is $\frac{5 \times 10}{5 + 10}$

$$= \frac{50}{15}\ \Omega = \frac{10}{3}\ \Omega.$$

Also, $\frac{2}{3}\ \Omega$ and $\frac{10}{3}\ \Omega$ are in series as shown in Fig. 4.25(a)

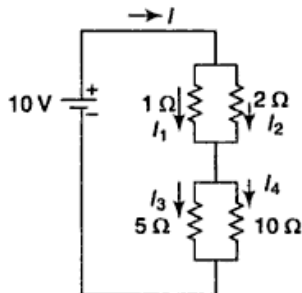


Fig. 4.25 Circuit of Ex. 4.14

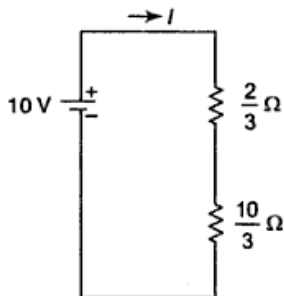


Fig. 4.25(a) Simplified equivalent of circuit of Fig. 4.25

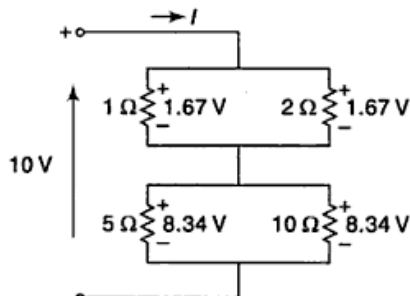


Fig. 4.25(b) Polarity of voltage drops of the circuit of Fig. 4.25

Figure 4.25(a) represents a simple series circuit. The supply current is given by

$$I = \frac{10}{\frac{2}{3} + \frac{10}{3}} \text{ A} = \frac{10 \times 3}{12} \text{ A} = 2.5 \text{ A}$$

From Fig. 4.25,

$$\text{Current through } 1 \Omega \text{ resistor } I_1 = 2.5 \times \frac{2}{1+2} \text{ A} = 1.67 \text{ A}$$

$$\text{Current through } 2 \Omega \text{ resistor } I_2 = 2.5 \times \frac{1}{1+2} \text{ A} = 0.83 \text{ A}$$

$$\text{Current through } 5 \Omega \text{ resistor } I_3 = 2.5 \times \frac{10}{10+5} \text{ A} = 1.676 \text{ A}$$

$$\text{Current through } 10 \Omega \text{ resistor } I_4 = 2.5 \times \frac{5}{10+5} \text{ A} = 0.834 \text{ A}$$

Therefore

$$\text{Voltage across } 1 \Omega \text{ resistor is } 1.67 \times 1 = 1.67 \text{ V}$$

$$\text{Voltage across } 2 \Omega \text{ resistor is } 0.833 \times 2 = 1.67 \text{ V}$$

$$\text{Voltage across } 5 \Omega \text{ resistor is } 1.676 \times 5 = 8.34 \text{ V}$$

$$\text{Voltage across } 10 \Omega \text{ resistor is } 0.834 \times 10 = 8.34 \text{ V}$$

[Polarities of voltage drops are shown in Fig. 4.25(b)].

4.15 Find the current through 5Ω resistor in Fig. 4.26 when the terminals across a 10Ω resistor is (i) open circuited and (ii) short circuited. Also find the current through the short circuited path.

Solution

(i) When terminals across 10Ω resistor is open circuited as shown in Fig. 4.26(a), 15Ω and 5Ω are in series. Hence current I flows through both 15Ω and 5Ω . The current through the 10Ω resistor is obtained as

$$I = \frac{50}{15+5} \text{ A} = \frac{50}{20} \text{ A} = 2.5 \text{ A}$$

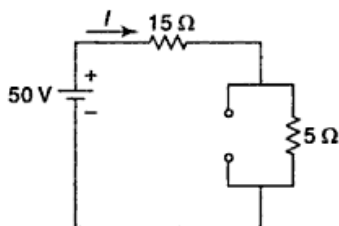


Fig. 4.26(a) One resistor in circuit of Fig. 4.26 open

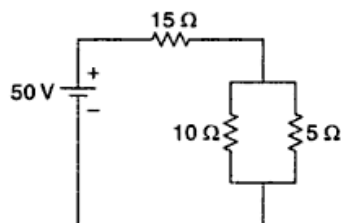


Fig. 4.26 Circuit of Ex. 4.15

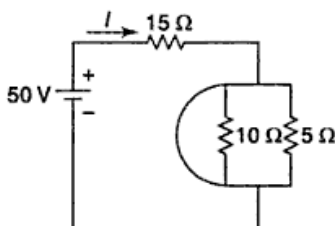


Fig. 4.26(b) 10Ω resistor is shorted in circuit of Fig. 4.26

(ii) When terminals across $10\ \Omega$ resistor is short circuited as shown in Fig. 4.26(b), no current will pass through the $5\ \Omega$ resistor as there is a short-circuited path in parallel with it. Therefore current through the $5\ \Omega$ resistor is 0.

The supply current I will pass through $15\ \Omega$ and through the short circuited path. Hence the current through the short circuited path is $50/15\ \text{A} = 10/3\ \text{A} = 3.33\ \text{A}$.

4.6 KIRCHHOFF'S LAWS

A German physicist Gustav Kirchhoff developed two laws enabling easier analysis of circuits containing interconnected impedances. The first law deals with flow of current and is popularly known as *Kirchhoff's current law* (KCL) while the second one deals with voltage drop in a closed circuit and is known as *Kirchhoff's voltage laws* (KVL).

4.6.1 Kirchhoff's Current Law (KCL)

It states that in any electrical network the algebraic sum of currents meeting at any node of a circuit is zero.

In Fig. 4.27, i_1 and i_2 are the inward currents towards the junction 0 and are assumed as negative currents. Currents i_3 , i_4 and i_5 are outward currents and taken as positive. As per KCL,

$$-i_1 - i_2 + i_3 + i_4 + i_5 = 0$$

$$\text{i.e., } i_1 + i_2 = i_3 + i_4 + i_5 \quad (4.18)$$

i.e., the algebraic sum of currents entering a node must be equal to the algebraic sum of currents leaving that node.

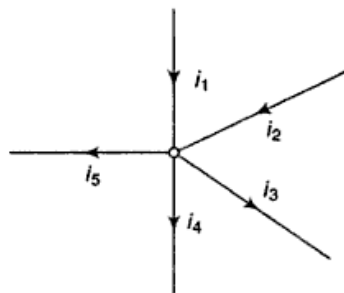


Fig. 4.27 Explanation of KCL

4.6.2 Kirchhoff's Voltage Law (KVL)

It states that the algebraic sum of voltages (or voltage drops) in any closed path, in a network, traversed in a single direction is zero.

In Fig. 4.28, if we travel clockwise in the network along the direction of the current, application of KVL yields

$$-V_1 + iR_1 + V_2 + iR_2 + iR_3 = 0$$

$$\text{or } V_1 = i(R_1 + R_2 + R_3) + V_2 \quad (4.19)$$

[We can also write equation (4.19) as follows:

$$V_1 - V_2 = i(R_1 + R_2 + R_3)$$

$$\text{or } i = \frac{V_1 - V_2}{R_1 + R_2 + R_3} \quad (4.20)]$$

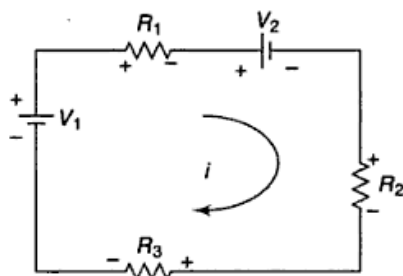


Fig. 4.28 Explanation of KVL

We consider the voltage drop as positive when current flows from positive to negative potential. Hence V_1 is negative while V_2 is positive in the first step of equation (4.19).

4.6.3 Network Analysis Procedure using Kirchhoff's Laws

1. Convert all current sources to voltage sources.
2. Letter or number all junctions on the network as A, B, C or $1, 2, 3$ etc.
3. Identify current directions and voltage polarities and number them according to the resistor involved.
4. Identify each current path according to the lettered junctions and applying Kirchhoff's voltage law, write the voltage equations for the paths.
5. Applying Kirchhoff's current law, write the equations for the currents entering and leaving all junctions where more than one current is involved.
6. Solve the equations by substitution to find the unknown currents and or voltages.

4.16 Find the magnitude and direction of the unknown currents in Fig. 4.29. Given $i_1 = 20$ A, $i_2 = 12$ A and $i_5 = 8$ A.

Solution

Applying KCL at node 'a'

$$-i_1 + i_2 + i_4 = 0 \dots (x)$$

or $i_4 = i_1 - i_2 = 20 - 12 = 8$ A

Applying KCL at node 'b'

$$-i_2 - i_3 + i_5 = 0 \dots (y)$$

or $i_3 = i_5 - i_2 = 8 - 12 = -4$ A

Applying KCL at node 'd'

$$-i_4 + i_3 - i_6 = 0 \dots (z)$$

or $i_6 = i_3 - i_4 = -4 - 8 = -12$ A

The actual currents are now marked in Fig. 4.29(a).

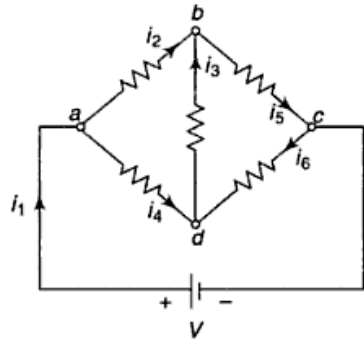


Fig. 4.29 Circuit of Ex. 4.16

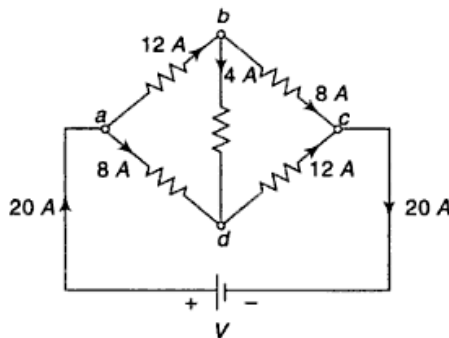


Fig. 4.29(a) Actual current flows in circuit of Fig. 4.29

We can interpret as follows:

$$i_3 = -4 \text{ A (from } d \text{ to } b)$$

i.e. $i_3 = 4 \text{ A (from } b \text{ to } d)$

$$i_4 = 8 \text{ A (from } a \text{ to } d)$$

$$i_6 = -12 \text{ A (from } c \text{ to } d)$$

or $i_6 = 12 \text{ A (from } d \text{ to } c)$

.....

4.17 In Fig. 4.30, find v . Also find the magnitudes and direction of the unknown currents through 10Ω , 2Ω and 5Ω resistors.

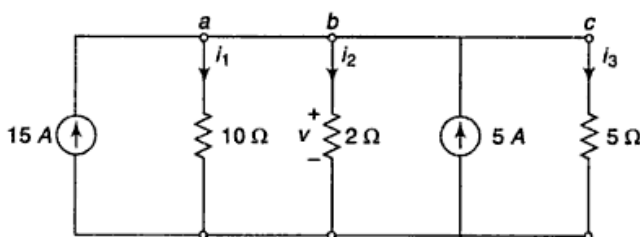


Fig. 4.30 Circuit of Ex. 4.17

Solution

Applying KCL at node 'a', (Fig. 4.30),

$$-15 + i_1 + i_2 - 5 + i_3 = 0$$

or $i_1 + i_2 + i_3 = 20$ (i)

From Ohm's Law, $i_2 = \frac{v}{2}$; $i_1 = \frac{v}{10}$ and $i_3 = \frac{v}{5}$.

Then from equation (i), we have

$$\frac{v}{10} + \frac{v}{2} + \frac{v}{5} = 20$$

or $v + 5v + 2v = 200$

$\therefore v = 25 \text{ V.}$

Hence $i_1 = \frac{v}{10} = \frac{25}{10} = 2.5 \text{ A}$

$$i_2 = \frac{25}{2} = 12.5 \text{ A}$$

$$i_3 = \frac{25}{5} = 5 \text{ A.}$$

.....

4.18 In the part of the electrical network, shown in Fig. 4.31, find v_1 . Assume $i_2 = (10e^{-3t}) \text{ A}$, $i_4 = 6(\sin t) \text{ A}$ and $v_3 = (8e^{-3t}) \text{ V}$.

Solution

Applying KCL at the node '0' in Fig. 4.31,

$$-i_1 - i_2 - i_3 + i_4 = 0$$

$$\begin{aligned}
 \text{or} \quad & i_1 + 10e^{-3t} + c \frac{dv_3}{dt} - 6 \sin t = 0 \\
 \text{or} \quad & i_1 + 10e^{-3t} + 2 \times \frac{d}{dt} (8e^{-3t}) - 6 \sin t = 0 \\
 \text{or} \quad & i_1 + 10e^{-3t} - 48e^{-3t} - 6 \sin t = 0 \\
 \therefore \quad & i_1 = 38e^{-3t} + 6 \sin t \\
 \text{Now,} \quad & v_1 = L \frac{di}{dt} = 4 \times \frac{d}{dt} (38e^{-3t} + 6 \sin t) \\
 & = 4 \{-114e^{-3t} + 6 \cos t\} \\
 \therefore \quad & v_1 = (24 \cos t - 456 e^{-3t}) \text{ V}
 \end{aligned}$$

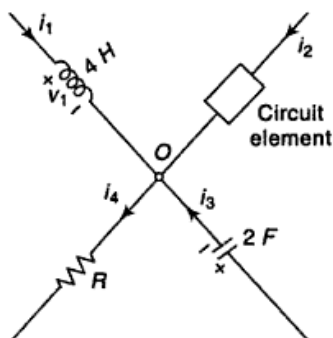


Fig. 4.31 Circuit of Ex. 4.18

4.19 Find branch currents in the bridge circuit shown in Fig. 4.32.

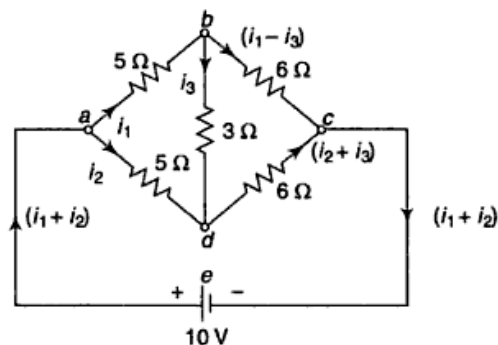


Fig. 4.32 Circuit of Ex. 4.19

Solution

We assume currents i_1 , i_2 and i_3 in the directions as shown in Fig. 4.32.

Applying KVL in loop 'abda', we find

$$5i_1 + 3i_3 - 5i_2 = 0. \quad (i)$$

Applying KVL in loop 'bcdb', we find

$$6(i_1 - i_3) - 6(i_2 + i_3) - 3i_3 = 0 \quad (ii)$$

or

$$6i_1 - 6i_2 - 15i_3 = 0. \quad (iii)$$

Applying KVL in loop 'adcea', we find

$$5i_2 + 6(i_2 + i_3) - 10 = 0 \quad (iv)$$

or

$$11i_2 + 6i_3 - 10 = 0. \quad (v)$$

Solving equations (i), (ii) and (iii) we get

$$i_1 = i_2 = 0.91 \text{ A}; i_3 = 0.$$

.....

4.20 In the network of Fig. 4.33, find v_1 and v_2 using KVL.

Solution

In loop 'abca', from KVL we can write,

$$1 + v_2 - v_1 = 0$$

or

$$v_1 - v_2 = 1. \quad (i)$$

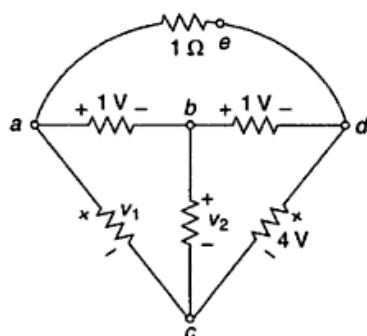


Fig. 4.33 Circuit of Ex. 4.20

In loop 'bcdcb', using KVL we find,

$$-v_2 + 1 + 4 = 0$$

or

$$v_2 = 5 \text{ V.}$$

Substituting the value of v_2 in equation (i) we get

$$v_1 = 6 \text{ V.}$$

4.21 Find current i in the circuit shown in Fig. 4.34.

Solution

The assumed and given currents in various branches of the circuit shown in Fig. 4.34 are drawn in Fig. 4.34(a).

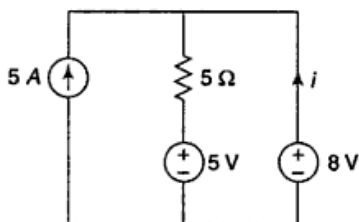


Fig. 4.34 Circuit of Ex. 4.21

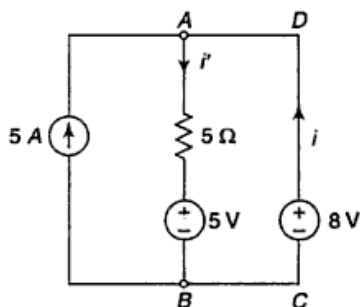


Fig. 4.34(a) Circuit of Ex. 4.21

Using KCL at node 'A',

$$-5 + i' - i = 0$$

or

$$i' - i = 5.$$

(i)

Applying KVL in loop 'ABCD',

$$5i' + 5 - 8 = 0$$

i.e.

$$i' = \frac{3}{5} = 0.6 \text{ A.}$$

Substituting the value of i' in (i), we have $i = 0.6 - 5 = -4.4 \text{ A.}$

Thus $i(4.4 \text{ A})$ flows from node D to node C in the actual circuit.

4.7 NODAL ANALYSIS

Nodal analysis is based on Kirchhoff's current law. This method has the advantage that a minimum number of equations are needed to determine the unknown quantities. Moreover, it is particularly suited for networks having many parallel branches and also when there are current sources in the network.

For the application of this method one of the nodes in the network is regarded as the *reference* or *datum* node or *zero potential* node. The number of simultaneous equations to be solved becomes $(n - 1)$, where n is the number of independent nodes.

Illustration

Referring Fig. 4.35, we find that nodes 'A' and 'B' are independent nodes. Let node 'B' be considered as reference node and the voltages at nodes 'A' and 'B' be (V_A) and (V_B) respectively. Obviously, $V_B = 0$.

Using Ohm's Law,

$$I_1 = \frac{E_1 - V_A}{R_1};$$

$$I_2 = \frac{E_2 - V_A}{R_2}$$

$$I_3 = \frac{V_A - V_B}{R_3} = \frac{V_A}{R_3}.$$

Applying KCL at node A,

$$-I_1 - I_2 + I_3 = 0$$

$$\text{i.e.,} \quad -\frac{E_1 - V_A}{R_1} - \frac{E_2 - V_A}{R_2} + \frac{V_A}{R_3} = 0. \quad (4.20)$$

This equation represents the *nodal* form of KCL. In nodal analysis we usually assume inward currents as negative while outward currents as positive.

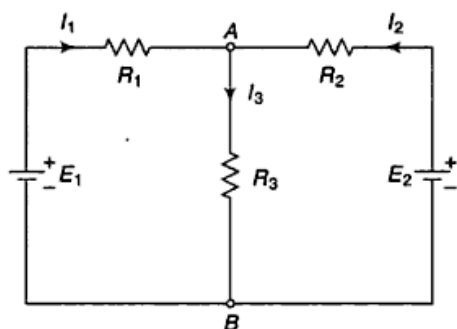


Fig. 4.35 Illustration for nodal method

4.7.1 Nodal Analysis Procedure

1. Convert all voltage sources to current sources and redraw the circuit diagram.
2. Identify all nodes and choose a reference node. (Usually, the common node is the reference node.)
3. Write the equation for the currents flowing into and out of each node, with the exception of the reference node.
4. Solve the equation to determine the node voltage and the required branch currents.

4.22 Find the voltage v in the circuit shown in Fig. 4.36.

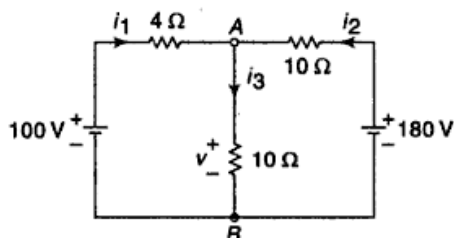


Fig. 4.36 Circuit of Ex. 4.22

Solution

Considering 'B' as reference node, $V_B = 0$. Let V_A be the potential at node 'A'.

Obviously, $V_A - V_B = v$, i.e., $V_A = v$.

Using nodal analysis at node 'A', we get

$$\frac{V_A - 100}{4} + \frac{V_A}{10} + \frac{V_A - 180}{10} = 0$$

$$\text{or } \frac{v - 100}{4} + \frac{v}{10} + \frac{v - 180}{10} = 0$$

$$\text{or } v \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{4} \right) = 43$$

$$\therefore v = \frac{43 \times 10}{4.5} = 95.55 \text{ V.}$$

4.23 Find the currents in different branches of the network shown in Fig. 4.37 using nodal analysis.

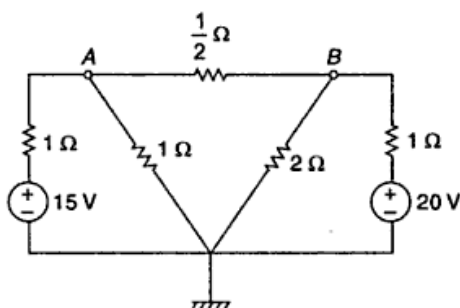


Fig. 4.37 Circuit of Ex. 4.23

Let V_A and V_B be the nodal voltages at nodes 'A' and 'B' in the given figure. The ground node is the reference node. Using nodal analysis, at node 'A' we can write

$$\frac{V_A - 15}{1} + \frac{V_A}{1} + \frac{V_A - V_B}{1/2} = 0$$

$$\text{or } 4V_A - 2V_B = 15.$$

(i)

At node 'B' we can write

$$\frac{V_B - V_A}{1/2} + \frac{V_B}{2} + \frac{V_B - 20}{1} = 0$$

or $3.5 V_B - 2 V_A = 20$

(ii)

Solving equations (i) and (ii), we get

$$V_B = 11 \text{ V}; V_A = 9.25 \text{ V}.$$

Hence, current through the respective resistors can be calculated as follows:

$$I_1 = \frac{V_A - 15}{1} = -5.75 \text{ A}$$

$$I_2 = \frac{V_A}{1} = 9.25 \text{ A}$$

$$I_3 = \frac{V_A - V_B}{1/2} = -3.5 \text{ A}$$

$$I_4 = \frac{V_B}{2} = 5.5 \text{ A}$$

$$I_5 = \frac{V_B - 20}{1} = -9 \text{ A}.$$

Figure 4.37(a) represents the circuit along with associated currents.

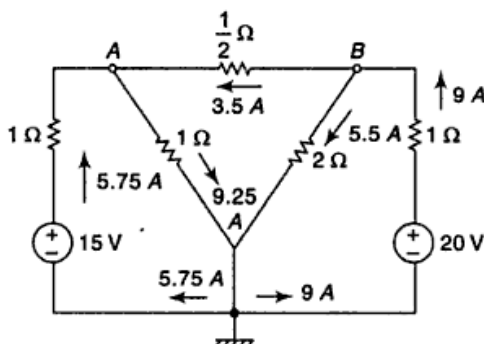


Fig. 4.37(a) Current values in branches of Fig. 4.37

4.24 Find the node voltages (V_x) and (V_y) using nodal analysis (Fig. 4.38).

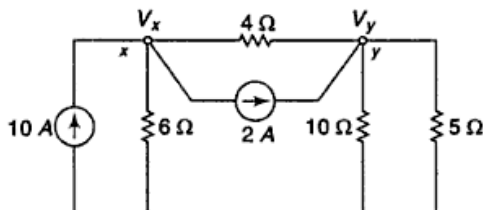


Fig. 4.38 Circuit of Ex. 4.24

Solution

At node 'x', we have

$$-10 + \frac{V_x}{6} + 2 + \frac{V_x - V_y}{4} = 0$$

$$\text{or} \quad V_x \left(\frac{1}{4} + \frac{1}{6} \right) - \frac{V_y}{4} = 8$$

$$\text{or} \quad 5V_x - 3V_y = 96. \quad (\text{i})$$

Applying nodal analysis at 'y', we get

$$-2 + \frac{V_y - V_x}{4} + \frac{V_y}{10} + \frac{V_y}{5} = 0$$

$$\text{or} \quad -\frac{V_x}{4} + V_y \left(\frac{1}{4} + \frac{1}{5} + \frac{1}{10} \right) = 2$$

$$\text{or} \quad 5V_x - 11V_y = -40. \quad (\text{ii})$$

Solving equations (i) and (ii), we get

$$V_x = 29.4 \text{ V}; V_y = 17 \text{ V}.$$

.....

4.25 Find current in the 15Ω resistor using nodal method (Fig. 4.39).

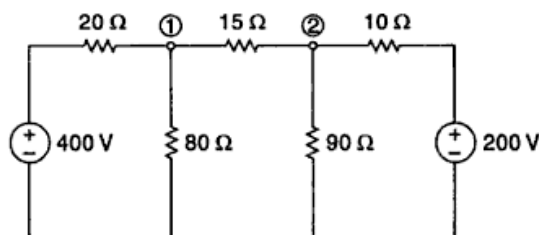


Fig. 4.39 Circuit of Ex. 4.25

Solution

Let us first designate the nodes '1' and '2' in Fig. 4.39 and assume nodal voltages to be (V_1) and (V_2) respectively

At node '1',

$$\frac{V_1 - 400}{20} + \frac{V_1}{80} + \frac{V_1 - V_2}{15} = 0$$

$$\text{or} \quad V_1 \left(\frac{1}{20} + \frac{1}{80} + \frac{1}{15} \right) - \frac{V_2}{15} = 20$$

$$\text{or} \quad \frac{31}{240} \cdot V_1 - \frac{1}{15} \cdot V_2 = 20 \quad (\text{i})$$

Similarly, using nodal analysis at node '2',

$$\frac{V_2 - 200}{10} + \frac{V_2}{90} + \frac{V_2 - V_1}{15} = 0$$

$$\text{or} \quad -\frac{V_1}{15} + V_2 \left(\frac{1}{10} + \frac{1}{15} + \frac{1}{90} \right) V_2 = 20$$

$$\text{or} \quad -\frac{1}{15} \cdot V_1 + \frac{16}{90} \cdot V_2 = 20 \quad (\text{ii})$$

Solving equations (i) and (ii) we get

$$V_1 = 264.88 \text{ V}; \quad V_2 = 211.33 \text{ V}$$

Hence, current in the 15Ω resistor is obtained as

$$I_{15} = \frac{V_1 - V_2}{15} = \frac{264.88 - 211.33}{15} = 3.57 \text{ A}$$

This current is directed from node '1' and node '2'.

4.26 In Fig. 4.40, find " v " in the given circuit using nodal analysis.

Solution

Let us mark the junction of two resistors (1Ω and 2Ω) as node 'A' and assume the voltage at this node to be (V_A). Applying nodal analysis at 'A' we get

$$\frac{V_A}{2} + \frac{V_A + 5}{1 + 1} + \frac{V_A + 10}{1} = 0$$

$$\text{or} \quad V_A \left(\frac{1}{2} + \frac{1}{2} + 1 \right) + \frac{5}{2} + 10 = 0$$

$$\text{or} \quad V_A = -6.25 \text{ V.}$$

We now find the currents passing through both side resistors of the node 'A'. We redraw Fig. 4.40 as Fig. 4.40(a) and mark the corresponding resistors as r_1 and r_2 . The current through r_1 is given by $i_{r_1} = V_A + 10/1 = 3.75 \text{ A}$, directed outwards of node 'A'. Similarly, current through r_2 is given by $i_{r_2} = \frac{V_A + 5}{1 + 1} = -0.625 \text{ A}$, directed towards the node 'A'.

\therefore Voltage drop across r_1 is (3.75×1) i.e., 3.75 V while that across r_2 is (-0.625×1) i.e., -0.625 V . The corresponding polarities have been marked in Fig. 4.40(a).

Finally, in loop ' $mnApq$ ' we can write, from KVL,

$$-v - 2 - 3.75 + 0.625 = 0$$

$$\text{i.e.} \quad v = -5.125 \text{ V.}$$

(It means, polarity of 'm' is actually negative while polarity of 'q' is actually positive in Fig. 4.40(a)).

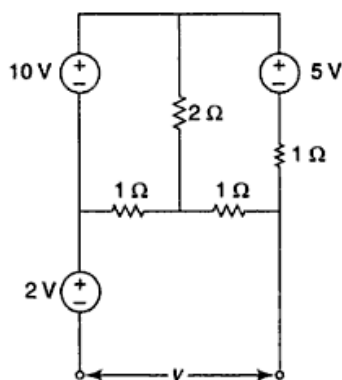


Fig. 4.40 Circuit of Ex. 4.26

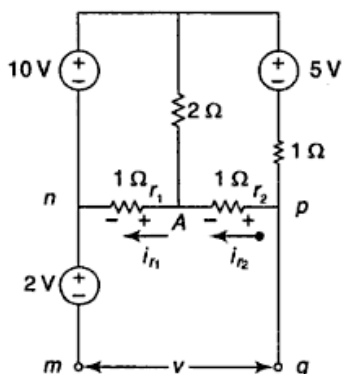


Fig. 4.40(a) Figure 4.40, redrawn, for analysis

4.27 Obtain the current through the $1\ \Omega$ resistor using node voltage method for the circuit shown in Fig. 4.41.

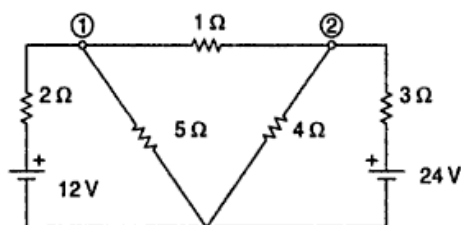


Fig. 4.41 Circuit of Ex. 4.27

Solution

Let us first mark the nodes '1' and '2' in Fig. 4.41 and assume corresponding nodal voltages to be V_1 and V_2 .

At node '1', we have

$$\frac{V_1 - 12}{2} + \frac{V_1}{5} + \frac{V_1 - V_2}{1} = 0$$

or $V_1 \left(\frac{1}{5} + \frac{1}{2} + 1 \right) - V_2 = 6$

or $17V_1 - 10V_2 = 60.$

(i)

At node '2', we have

$$\frac{V_2 - 24}{3} + \frac{V_2}{4} + \frac{V_2 - V_1}{1} = 0$$

or $-V_1 + V_2 \left(\frac{1}{3} + \frac{1}{4} + 1 \right) = 8$

or $-V_1 + \frac{19}{12}V_2 = 8$

or $-12V_1 + 19V_2 = 96.$

(ii)

Solving (i) and (ii) we get, $V_1 = 10.35\text{ V}$; $V_2 = 11.6\text{ V}$

Hence the current through $1\ \Omega$ resistor is

$$I_1 = \frac{V_2 - V_1}{1} = \frac{11.6 - 10.35}{1}.$$

$$= 1.25\text{ V, directed from node '2' and to node '1'.$$

.....

4.28

.....

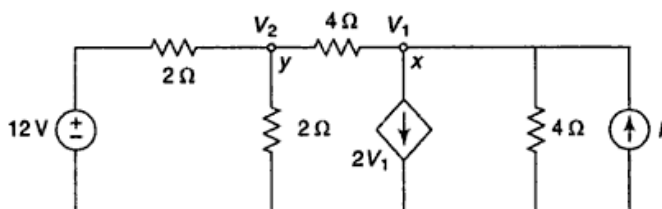


Fig. 4.42 Circuit of Ex. 4.28

In Fig. 4.42, find I so that $V_1 = 0$.

Solution

At node 'x' we can write, using nodal analysis,

$$\frac{V_1 - V_2}{4} + 2V_1 + \frac{V_1}{4} - I = 0$$

$$\text{or} \quad 2.5 V_1 - 0.25 V_2 = I \quad (i)$$

At node 'y', using nodal analysis, we write

$$\frac{V_2 - V_1}{4} + \frac{V_2}{2} + \frac{V_2 - 12}{2} = 0$$

$$\text{or} \quad 1.25 V_2 - 0.25 V_1 = 6 \quad (ii)$$

But as per question, $V_1 = 0$.

$$\therefore \text{from (ii), } V_2 = \frac{6}{1.25} = 4.8 \text{ V.}$$

Also, from (i), $I = -4.8 \times 0.25 = -1.2 \text{ A}$

Thus the current source I pushing current in the reverse direction and of magnitude 1.2 A will make $V_1 = 0$

4.29 Obtain the value of V_R in the network shown in Fig. 4.43.

Solution

In the network of Fig. 4.43 let us assume that the node voltage at node 'x' be ' V_x '. Thus at node 'x' we can write,

$$-1 + \frac{V_x - 2}{2} + \frac{V_x - 8V_R}{10} = 0$$

$$\text{or} \quad \frac{V_x}{2} + \frac{V_x}{10} - 1 - \frac{4}{5} V_R = 1$$

$$\text{or} \quad V_R = \left(\frac{3}{4} V_x - \frac{5}{2} \right) \text{ V} \quad (i)$$

Also, in branch 'xy', $V_x - 2 = V_R$

$$\text{i.e.} \quad V_x = (V_R + 2) \text{ V} \quad (ii)$$

Substituting the value of V_x from equation (ii) in equation (i), we get

$$V_R = \frac{3}{4} (V_R + 2) - \frac{5}{2} = \frac{3}{4} V_R - 1$$

$$\therefore V_R = -4 \text{ V.} \quad \dots\dots\dots$$

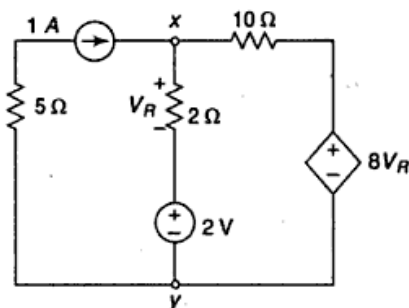


Fig. 4.43 Circuit of Ex. 4.29

4.8 MESH ANALYSIS (OR LOOP ANALYSIS)

The *mesh* or *loop analysis* is based on Kirchhoff's voltage law. Here the currents in different meshes are assigned continuous paths so that they do not split at a junction into branch currents. In this method loop voltage equations are written by KVL in terms of unknown loop currents. Circuits with voltage sources are comparatively easier to be solved by this method.

Illustration

Figure 4.44 shows that two batteries having emf E_1 and E_2 are connected in a network containing five resistors. There are two loops and the respective loop currents are I_1 and I_2 . Applying KVL in loop 1, we have

$$-E_1 + I_1 R_1 + (I_1 - I_2) R_2 + I_1 R_4 = 0$$

$$\text{or } E_1 = I_1(R_1 + R_2 + R_4) - I_2 R_2 \quad (i)$$

Applying KVL in loop 2, we get

$$E_2 + I_2 R_3 + (I_2 - I_1) R_2 + I_2 R_5 = 0$$

$$\text{or } E_2 = I_1 R_2 - (R_2 + R_3 + R_5) I_2 \quad (ii)$$

Solving equations (i) and (ii), we can find the values of I_1 and I_2 and subsequently branch currents can be evaluated.

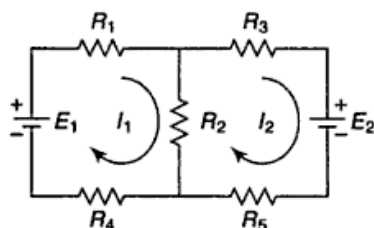


Fig. 4.44 Illustration of mesh analysis

4.8.1 DC Circuit Analysis Procedure using Loop Equations

1. Convert all current sources to voltage sources.
2. Draw all loop currents in a clockwise direction and identify them.
3. Identify all resistor voltage drops as + to - in the direction of the loop current and assume these drops to be positive.
4. Identify all voltage sources according to their correct polarity.
5. Write the equations for the voltage drops around each loop in turn, by equating the sum of the voltage drops to zero.
6. Solve the equations to find the unknown currents and/or voltage drops.

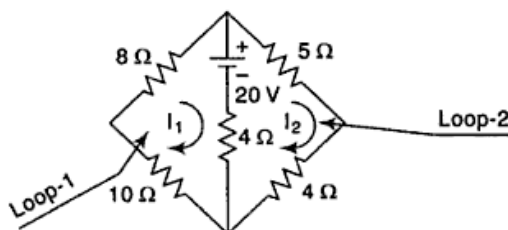


Fig. 4.45 Circuit of Ex. 4.30

4.30 Calculate the current supplied by the battery in Fig. 4.45 using loop current method.

Applying KVL in loop-1

$$8I_1 + 20 + (I_1 - I_2) 4 + 10I_1 = 0$$

$$\text{or } 22I_1 - 4I_2 = -20$$

$$\text{or } 11I_1 - 2I_2 = -10$$

$$\text{or} \quad I_2 = \frac{11I_1 + 10}{2} \quad (\text{i})$$

Applying KVL in loop-2,

$$5I_2 + 4I_2 + (I_2 - I_1) 4 - 20 = 0$$

$$\text{or} \quad -4I_1 + 13I_2 = 20 \quad (\text{ii})$$

Substituting the value of I_2 from equation (i) in equation (ii), we get

$$-4I_1 + 13 \times \frac{10 + 11I_1}{2} - 20 = 0$$

$$\text{or} \quad I_1 = -0.667 \text{ A}$$

$$\text{Also,} \quad I_2 = \frac{10 + 11(-0.667)}{2} = 1.33 \text{ A.}$$

Hence the current supplied by the battery is obtained as $(I_2 - I_1)$, i.e. $1.33 + 0.667 = 1.997 \text{ A}$

4.31 Find the currents in 2Ω , 3Ω , 4Ω , 5Ω and 10Ω resistances in the circuit shown in Fig. 4.46 using loop method.

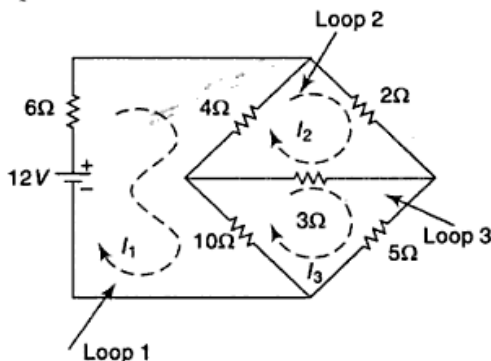


Fig. 4.46 Circuit of Ex. 4.31

Solution

Let us first mark the loop current in Fig. 4.46 as shown by dotted arrows.

For loop 1 we can write,

$$-12 + 6I_1 + (I_1 - I_2) 4 + (I_1 - I_3) 10 = 0$$

$$\text{or} \quad 10I_1 - 2I_2 - 5I_3 = 6. \quad (\text{i})$$

Applying mesh method in loop 2, we have

$$2I_2 + (I_2 - I_3) 3 + (I_2 - I_1) 4 = 0$$

$$\text{or} \quad 4I_1 - 9I_2 + 3I_3 = 0. \quad (\text{ii})$$

Applying mesh method in loop 3, we have

$$5I_3 + (I_3 - I_1) 10 + (I_3 - I_2) 3 = 0$$

$$\text{or} \quad 10I_1 + 3I_2 - 18I_3 = 0. \quad (\text{iii})$$

Comparing equations (i) and (iii), we get

$$5I_2 - 13I_3 = -6$$

$$\therefore \quad I_2 = \frac{13I_3 - 6}{5} \quad (\text{iv})$$

Again, from equation (ii) we can write

$$I_1 = \frac{9I_2 - 3I_3}{4}$$

Substituting this value of I_1 in equation (i), we get

$$10 \times \frac{9I_2 - 3I_3}{4} - 2I_2 - 5I_3 = 6.$$

Simplifying,

$$I_2 = \left(6 + \frac{50}{4} I_3\right) \frac{4}{82}. \quad (v)$$

From equations (iv) and (v), we have

$$\frac{13I_3 - 6}{5} = \frac{4}{82} \left(6 + \frac{50}{4} I_3\right)$$

$$\text{or } 82(13I_3 - 6) = 20 \left(6 + \frac{50}{4} \times I_3\right)$$

$$\text{or } I_3 = \frac{612}{816} = 0.75 \text{ A.}$$

\therefore From equation (iv) we now can write

$$I_2 = \frac{13 \times 0.75 - 6}{5} = 0.75 \text{ A}$$

Also from equation (i), we can write

$$10I_1 = 2 \times 0.75 + 5 \times 0.75 + 6 = 11.25$$

$$\therefore I_1 = 1.125 \text{ A.}$$

Thus current in the 2Ω and 5Ω resistors is 0.75 A each;

current in the 4Ω resistor is $(I_1 - I_2)$ i.e., 0.375 A ,

current in the 10Ω resistor is $(I_1 - I_3)$ i.e., 0.375 A ,

and current in the 3Ω resistor is $(I_2 - I_3)$ i.e., 0 A .

4.32 From the mesh analysis find the current flow through a 50 V source in Fig. 4.47.

Solution

Let us designate the loop currents by dotted arrows in the network of Fig. 4.47.

In loop 1 we have

$$-50 + 5i_1 + (i_1 - i_2) 2 + 20 = 0$$

$$\text{or } 7i_1 - 2i_2 - 30 = 0 \quad (i)$$

In loop 2 we can write,

$$3i_2 + 10 - 20 + (i_2 - i_1) 2 = 0$$

$$\text{or } i_1 = \frac{5}{2} i_2 - 5 \quad (ii)$$

Substituting the value of i_1 from equation (ii) to equation (i), we get

$$7 \left(\frac{5}{2} i_2 - 5 \right) - 2i_2 - 30 = 0$$

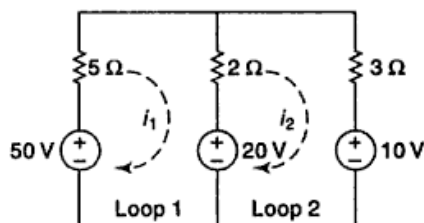


Fig. 4.47 Circuit of Ex. 4.32

Simplification yields,

$$i_2 = 4.19 \text{ A}$$

Thus from equation (ii) we get

$$i_1 = \frac{5}{2} \times 4.19 - 5 = 5.475 \text{ A.}$$

The current through the 50 V source is thus 5.475 A.

4.33 Find the voltage drop between terminals (y) and (d) in the network of Fig. 4.48.

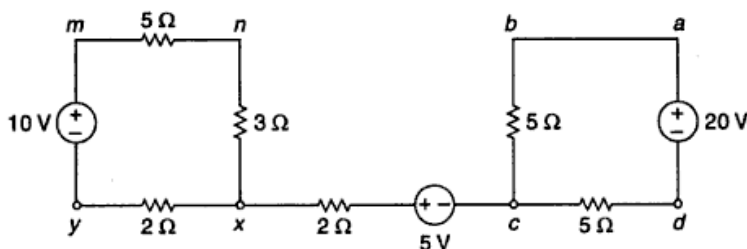


Fig. 4.48 Circuit of Ex. 4.33

Solution

The current supplied by the 10 V source in the loop-mnxy is obtained as

$$i_1 = \frac{10}{5+3+2} = 1 \text{ A.}$$

The current supplied by the 20 V source in the loop-badc is given by

$$i_2 = \frac{20}{5+5} = 2 \text{ A.}$$

The corresponding drops with polarities are shown in Fig. 4.48(a).

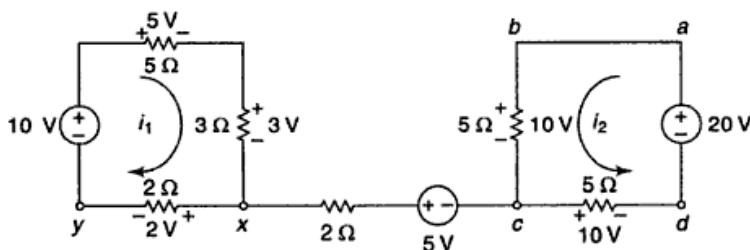


Fig. 4.48(a) Currents and voltages for the circuit of Ex. 4.33

$$\therefore V_{yd} = -V_{yx} + 5V + V_{cd} = -2 + 5 + 10 = 13 \text{ V.}$$

The drop across terminal (y) and (d) is 13 V.

4.34 Find the current through the resistors using mesh method for the network shown in Fig. 4.49.

Solution

Let us first draw the loop currents in the network of Fig. 4.49. The loop currents are shown by dotted arrows. It may be noted that due to presence of current source of 3 A, the corresponding loop current I_3 is 3 A.

In the loop containing 12 V source, we have

$$-12 + (I_1 + 3)5 + (I_1 - I_2)2 = 0$$

$$\text{or } 7I_1 - 2I_2 + 3 = 0. \quad (\text{i})$$

Applying mesh analysis in the loop containing 6V source, we get

$$I_2 1 + (I_2 - I_1) 2 + (I_2 + 3) 6 + 6 = 0$$

$$\text{or } I_1 = \frac{9}{2} I_2 + 12. \quad (\text{ii})$$

Substituting the value of I_1 from equation (ii) in (i), we get

$$7\left(\frac{9}{2} I_2 + 12\right) - 2I_2 + 3 = 0$$

$$\text{or } I_2 = -2.95 \text{ A}$$

Thus from equation (ii), we get

$$I_1 = \frac{9}{2} \times (-2.95) + 12 = -1.275 \text{ A}$$

We now can find currents in respective resistors:

Current through 5 Ω resistor ($= I_1 + I_3$) = $-1.275 + 3 = 1.725 \text{ A}$.

[It may be noted that the current obtained through the 5 Ω resistor is directed from a to b].

Current through the 6 Ω resistor ($= I_2 + I_3$) = $-2.95 + 3 = 0.05 \text{ A}$.

[This current is directed from b to c].

Current through the 2 Ω resistor ($= I_1 + I_2$) = $-1.275 + 2.95 = 1.675 \text{ A}$.

[The current through the 2 Ω resistor is directed from b to d].

Finally, the current through the 1 Ω resistor (I_2) is (-2.95 A) and is directed from d to c .

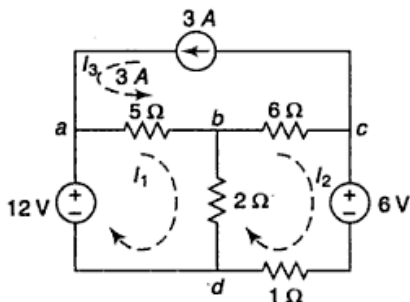


Fig. 4.49 Circuit of Ex. 4.34

4.35 In the bridge network shown in Fig. 4.50 find the current through the galvanometer having 20 Ω internal resistance. Use mesh analysis.

Solution

We first assign loops as *loop 1*, *loop 2* and *loop 3* with circulating currents I_1 , I_2 and I_3 through these loops (Fig. 4.50).

In loop 1 we have

$$6 I_1 + (I_1 - I_2) 20 + (I_1 - I_3) 3 = 0$$

$$\text{or } 29 I_1 - 20 I_2 - 3 I_3 = 0. \quad (\text{i})$$

In loop 2 we have

$$12 I_2 + (I_2 - I_3) 10 + (I_2 - I_1) 20 = 0$$

$$\text{or } -20 I_1 + 42 I_2 - 10 I_3 = 0. \quad (\text{ii})$$

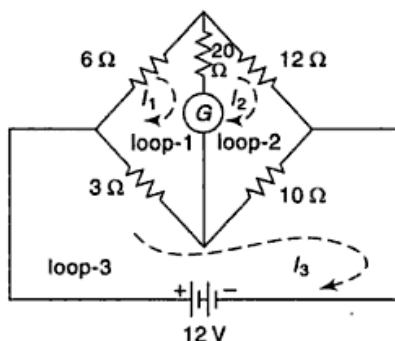


Fig. 4.50 Circuit of Ex. 4.35

Similarly, in loop 3 we can write

$$-12 + (I_3 - I_1) 3 + (I_3 - I_2) 10 = 0$$

$$\text{or} \quad -3 I_1 - 10 I_2 + 13 I_3 - 12 = 0. \quad (\text{iii})$$

Let us now solve these three simultaneous equations.

$$\text{From equation (i), } I_1 = \frac{20 I_2 + 3 I_3}{29} \quad (\text{iv})$$

$$\text{and from equation (ii), } I_1 = \frac{42 I_2 - 10 I_3}{20} \quad (\text{v})$$

Comparing equation (iv) and (v) we get

$$\frac{20 I_2 + 3 I_3}{29} = \frac{42 I_2 - 10 I_3}{20}$$

$$\text{or} \quad 818 I_2 - 350 I_3 = 0 \quad (\text{vi})$$

Again, from equation (iii) we find

$$I_1 = \frac{-10 I_2 + 13 I_3 - 12}{3} \quad (\text{vii})$$

Comparing equation (v) with equation (vii) we get

$$\frac{-10 I_2 + 13 I_3 - 12}{3} = \frac{42 I_2 - 10 I_3}{20}$$

$$\text{or} \quad 326 I_2 - 290 I_3 = -240 \quad (\text{viii})$$

From equation (vi) we find $I_2 = (350 I_3 / 818)$; substitution of value of I_2 in equation (viii) yields

$$326 \times \frac{350}{818} \cdot I_3 - 290 I_3 = -240$$

$$\text{or} \quad I_3 = 1.59 \text{ A.}$$

From (vi), I_2 can be found as $I_2 = (350 / 818) \times 1.59$

$$\text{i.e.,} \quad I_2 = 0.68 \text{ A}$$

From (vii) we can find the value of I_1 ;

$$I_1 = \frac{-10 \times 0.68 + 13 \times 1.59 - 12}{3} = 0.633 \text{ A.}$$

The current $(I_2 - I_1)$ through the galvanometer is then obtained. Obviously,

$$(I_2 - I_1) = I_G = 0.68 - 0.633 = 0.047 \text{ A (directed upwards).} \quad \dots\dots$$

4.36 Find current in all branches of the network shown in Fig. 4.51.

Solution

Let the current in the arm AF be I amps, as shown by dotted arrow. Using the concept of KCL, the currents at each of the branches have been identified in Fig. 4.51 in terms of the assumed current I . Next we apply the mesh analysis at the hexagonal network $AFEDCBA$. We have

$$\begin{aligned} &0.02(I) + 0.01(I - 60) + 0.03(I) + 0.01(I - 120) \\ &+ 0.01(I - 50) + 0.02(I - 80) = 0. \end{aligned}$$

Solving for I , we get $I = 39 \text{ A.}$

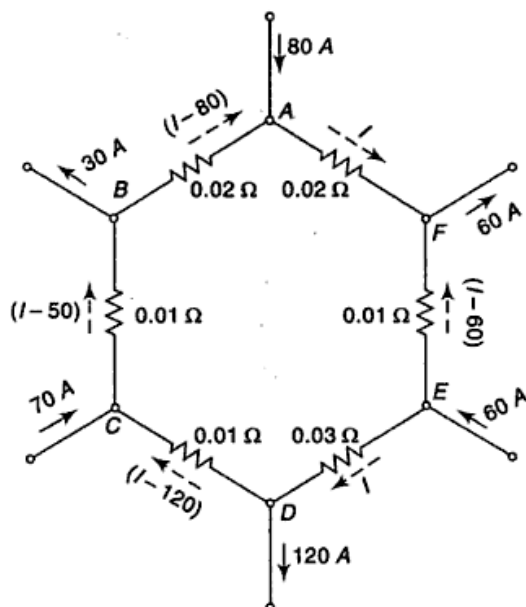


Fig. 4.51 Circuit of Ex. 4.36

Thus we can identify the branch currents as

$$\text{current in } AF = I_{AF} = 39 \text{ A } (=I)$$

$$\text{current in } FE = (I - 60) = -21 \text{ A}$$

$$\text{current in } ED = I_{ED} = I = 39 \text{ A}$$

$$\text{current in } DC = I_{DC} = (I - 120) = -81 \text{ A}$$

$$\text{current in } CB = I_{CB} = (I - 50) = -11 \text{ A}$$

$$\text{current in } BA = I_{BA} = (I - 80) = -41 \text{ A}.$$

.....

4.8.2 Mesh Analysis Using Matrix Form

Let us consider the network shown in Fig. 4.52; it contains three meshes. The three mesh currents are I_1 , I_2 and I_3 and they are assumed to flow in a clockwise direction.

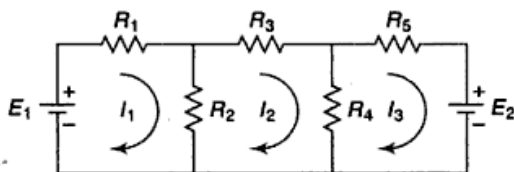


Fig. 4.52 Concept of mesh analysis in matrix form

Applying KVL to mesh 1

$$-E_1 + (I_1 - I_2)R_2 + I_1R_1 = 0$$

$$\text{or } I_1R_1 + (I_1 - I_2)R_2 = E_1$$

$$\text{or } I_1(R_1 + R_2) - I_2R_2 = E_1$$

$$\text{or } I_1(R_1 + R_2) + I_2(-R_2) = E_1.$$

(4.21)

Applying KVL to mesh 2

$$(I_2 - I_1)R_2 + I_2R_3 + (I_2 - I_3)R_4 = 0$$

$$\text{or } -I_1R_2 + I_2(R_2 + R_3 + R_4) - I_3R_4 = 0$$

$$\text{or } I_1(-R_2) + I_2(R_2 + R_3 + R_4) + I_3(-R_4) = 0 \quad (4.22)$$

Applying KVL to mesh 3

$$E_2 + I_3R_5 + (I_3 - I_2)R_4 = 0$$

$$\text{or } -I_2R_4 + I_3(R_4 + R_5) = -E_2. \quad (4.23)$$

It should be noted that the signs of resistances in the above equations have been so arranged as to make the items containing self-resistances positive. The matrix equivalent of the above three equations is

$$\begin{bmatrix} R_1 + R_2 & -R_2 & 0 \\ -R_2 & R_2 + R_3 + R_4 & -R_4 \\ 0 & -R_4 & R_4 + R_5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} E_1 \\ 0 \\ -E_2 \end{bmatrix}$$

In general the resistance matrix $[R]$ can be written as

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix}$$

where R_{11} = self-resistance of mesh 1 = $R_1 + R_2$

R_{22} = self-resistance of mesh 2 = $R_2 + R_3 + R_4$

R_{33} = self-resistance of mesh 3 = $R_4 + R_5$

$R_{12} = R_{21}$

= - [sum of all the resistances common to meshes 1 and 2]

= $-R_2$

$R_{23} = R_{32}$

= - [sum of all the resistances common to meshes 2 and 3]

= $-R_4$

$R_{13} = R_{31}$

= - [sum of all the resistances common to meshes 3 and 1]

= 0 (here).

$[R_{11}, R_{22}, R_{33} \dots]$ are called *diagonal elements* of the resistance matrix while $R_{12}, R_{13}, R_{21}, R_{23}, \dots$ are called *off-diagonal elements*.

4.37 Find the mesh currents in Fig. 4.53 using mesh current method.

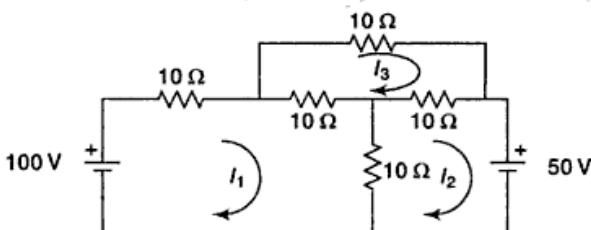


Fig. 4.53 Circuit of Ex. 4.37

Solution

Applying KVL in loop 1

$$-100 + 10(I_1 - I_2) + 10(I_1 - I_3) + 10I_1 = 0$$

$$\text{or } I_1(10 + 10 + 10) - 10I_2 - 10I_3 = 100$$

Applying KVL in loop 2

$$50 + 10(I_2 - I_3) + 10(I_2 - I_1) = 0$$

$$\text{or } -10I_1 + I_2(10 + 10) - 10I_3 = -50$$

Applying KVL in loop 3

$$10I_3 + 10(I_3 - I_1) + 10(I_3 - I_2) = 0$$

$$\text{or } -10I_1 - 10I_2 + I_3(10 + 10 + 10) = 0$$

The above equations in matrix form can be written as

$$\begin{bmatrix} 30 & -10 & -10 \\ -10 & 20 & -10 \\ -10 & -10 & 30 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 100 \\ -50 \\ 0 \end{bmatrix}$$

Hence

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 30 & -10 & -10 \\ -10 & 20 & -10 \\ -10 & -10 & 30 \end{bmatrix}^{-1} \begin{bmatrix} 100 \\ -50 \\ 0 \end{bmatrix}$$

or

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \frac{1}{8000} \begin{bmatrix} 500 & 400 & 300 \\ 400 & 800 & 400 \\ 300 & 400 & 500 \end{bmatrix} \begin{bmatrix} 100 \\ -50 \\ 0 \end{bmatrix}$$

Therefore,

$$I_1 = \frac{500 \times 100 - 400 \times 50}{8000} \text{ A} = 3.75 \text{ A}$$

$$I_2 = \frac{400 \times 100 - 50 \times 800}{8000} \text{ A} = 0 \text{ A}$$

and

$$I_3 = \frac{300 \times 100 - 400 \times 50}{8000} \text{ A} = 1.25 \text{ A}$$

.....

4.38 Find the ammeter current in Fig. 4.54 using mesh analysis.

Solution

Applying mesh method in mesh 1

$$4 + 10I_1 + 2(I_1 - I_2) = 0$$

$$\text{or } 12I_1 - 2I_2 = -4.$$

Applying mesh method in mesh 2

$$2 + 2(I_2 - I_1) + 10I_2 = 0$$

$$-2I_1 + 12I_2 = -2.$$

In the matrix form the above equations can be written as

$$\begin{bmatrix} 12 & -2 \\ -2 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -4 \\ -2 \end{bmatrix}$$

or

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 & -2 \\ -2 & 12 \end{bmatrix}^{-1} \begin{bmatrix} -4 \\ -2 \end{bmatrix} = \frac{1}{144 - 4} \begin{bmatrix} 12 & 2 \\ 2 & 12 \end{bmatrix} \begin{bmatrix} -4 \\ -2 \end{bmatrix}$$

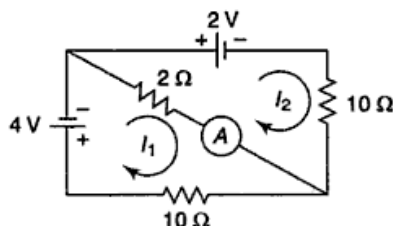


Fig. 4.54 Circuit of Ex. 4.38

or

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \frac{1}{140} \begin{bmatrix} -52 \\ -32 \end{bmatrix}$$

Hence $I_1 = \frac{-52}{140} \text{ A}$ and $I_2 = -\frac{32}{140} \text{ A}$.

Therefore, the current through ammeter is

$$I_2 - I_1 = \frac{52}{140} - \frac{32}{140} = \frac{1}{7} \text{ A [in the direction of } (I_2) \text{ as shown in Fig. 4.54].}$$

4.9 STAR DELTA CONVERSION

Like series and parallel connections the resistances may be connected in *star* (Y) or *delta* (Δ) connection as shown in Fig. 4.55(a) and Fig. 4.55(b).

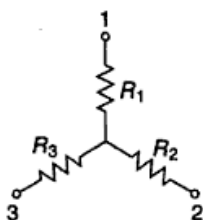


Fig. 4.55(a) A star (or T) connection

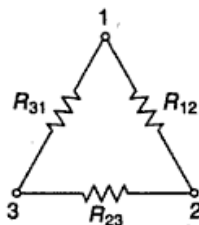


Fig. 4.55(b) A delta (or mesh) connection

Circuits shown in Fig. 4.55(a) and Fig. 4.55(b) are identical provided their respective resistances from terminals (12), (23) and (32) are equal.

In star connection,

Resistance between terminals 1 & 2 is $(R_1 + R_2)$

Resistance between terminals 2 & 3 is $(R_2 + R_3)$

Resistance between terminals 3 & 1 is $(R_3 + R_1)$.

Similarly in delta connection,

Resistance between terminals 1 & 2 is $[R_{12} \parallel (R_{23} + R_{31})]$

$$= \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

Resistance between terminals 2 & 3 is $[R_{23} \parallel (R_{31} + R_{12})]$

$$= \frac{R_{23}(R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}}$$

Resistance between terminals 3 & 1 is $[R_{31} \parallel (R_{12} + R_{23})]$

$$= \frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}}$$

Now, we equate the resistances in star and delta across appropriate terminals.

i.e. $R_1 + R_2 = \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad (4.24)$

$$R_2 + R_3 = \frac{R_{23}(R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} \quad (4.25)$$

$$R_3 + R_1 = \frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \quad (4.26)$$

Subtracting equation (4.25) from equation (4.24) we get

$$\begin{aligned} R_1 - R_3 &= \frac{R_{12}(R_{23} + R_{31}) - R_{23}(R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} \\ &= \frac{R_{12}R_{31} - R_{23}R_{31}}{R_{12} + R_{23} + R_{31}} \end{aligned} \quad (4.27)$$

Adding equations (4.26) and (4.27)

$$2R_1 = \frac{2R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$

or
$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$

In a similar way, $R_2 = \frac{R_{12}R_{23}}{R_{12} + R_{23} + R_{31}}$ and

$$R_3 = \frac{R_{31}R_{23}}{R_{12} + R_{23} + R_{31}}$$

Thus we see that if the resistances in delta connected resistance network are known, we can find the equivalent star network where

$$R_1 = \frac{R_{31}R_{12}}{R_{12} + R_{23} + R_{31}} \quad 4.28(a)$$

$$R_2 = \frac{R_{12}R_{23}}{R_{12} + R_{23} + R_{31}} \quad 4.28(b)$$

$$R_3 = \frac{R_{23}R_{31}}{R_{12} + R_{23} + R_{31}} \quad 4.28(c)$$

R_1 , R_2 and R_3 being equivalent resistances in the star network and R_{12} , R_{23} and R_{31} the resistances in the delta network.

Next, multiplying each equation [4.28(a), 4.28(b) and 4.28(c)] with another and adding

$$R_1R_2 + R_2R_3 + R_3R_1 = \frac{R_{31}R_{12}^2R_{23} + R_{12}R_{23}^2R_{31} + R_{23}R_{31}^2R_{12}}{(R_{12} + R_{23} + R_{31})^2} \quad (4.29)$$

Dividing equation (4.29) by (R_1) , we get

$$R_2 + \frac{R_2 R_3}{R_1} + R_3 = \frac{R_{12} R_{23} R_{31} (R_{12} + R_{23} + R_{31})}{R_1 (R_{12} + R_{23} + R_{31})^2}$$

$$= \frac{R_{12} R_{23} R_{31}}{R_1 (R_{12} + R_{23} + R_{31})} \quad (4.30)$$

Substituting the value of R_1 from equation (4.28(a)) in equation (4.30) we get

$$R_2 + R_3 + \frac{R_2 R_3}{R_1} = \frac{R_{12} R_{23} R_{31} (R_{12} + R_{23} + R_{31})}{R_{31} R_{12} (R_{12} + R_{23} + R_{31})}$$

$$= \frac{R_{12} R_{23} R_{31}}{R_{31} R_{12}} = R_{23}$$

i.e.,
$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

Similarly, dividing equation (4.29) by R_2 we get

$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

and dividing equation (4.29) by (R_3) we get

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Thus we find R_{12} , R_{23} and R_{31} , i.e. the equivalent delta network provided R_1 , R_2 and R_3 of the star network are given.

The equations are

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \quad [4.31(a)]$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \quad [4.31(b)]$$

$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \quad [4.31(c)]$$

4.9.1 Delta-Star (Δ -Y) and Star-Delta (Y- Δ) Transformation Procedures

1. When starting with a Δ network, draw a Y network; when starting with a Y network, draw a Δ network.
2. Identify the three corresponding terminals on each network as 1, 2 and 3.
3. Identify the resistors on the Δ network as follows:
 Resistor between terminals 1 and 2 as (R_{12})
 Resistor between terminals 1 and 3 as (R_{13})
 Resistor between terminals 2 and 3 as (R_{23}) .

4. Identify the resistors on the Y network as follows:

Resistor connected to terminal 1 as (R_1)

Resistor connected to terminal 2 as (R_2)

Resistor connected to terminal 3 as (R_3).

5. For Δ to Y transformation, substitute the Δ network resistor values into equations 4.28(a), 4.28(b) and 4.28(c) to obtain the Y network resistor values.
6. For Y to Δ transformation, substitute the Y network resistor values into equations 4.31(a), 4.31(b) and 4.31(c) to obtain the Δ network resistor values.

[A Y network is also called as T (Te) network while a Δ network may be called as a mesh or π (pi) network].

- 4.39** Convert the π network shown in Fig. 4.56 into equivalent T network.

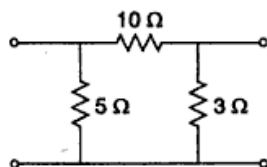


Fig. 4.56 Circuit of Ex. 4.39

Solution

The network in Fig. 4.56 can be redrawn as shown in Fig. 4.56(a). Here R_1 , R_2 and R_3 in star combination represent the equivalent of the given delta network.

$$R_1 = \frac{R_{12} \times R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{10 \times 5}{10 + 3 + 5} = 2.78 \, \Omega$$

$$R_2 = \frac{R_{23} \times R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{3 \times 10}{10 + 3 + 5} = 1.67 \, \Omega$$

$$R_3 = \frac{R_{31} \times R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{3 \times 5}{10 + 3 + 5} = 0.83 \, \Omega$$

Thus we have obtained the equivalent star (or T) resistances given by

$$R_1 = 2.78 \, \Omega; R_2 = 1.67 \, \Omega; R_3 = 0.83 \, \Omega.$$

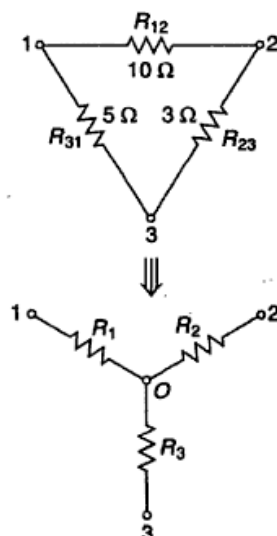


Fig. 4.56(a) Δ - Y conversion of the given network

- 4.40** Find the input resistance (R) of the network shown in Fig. 4.57.

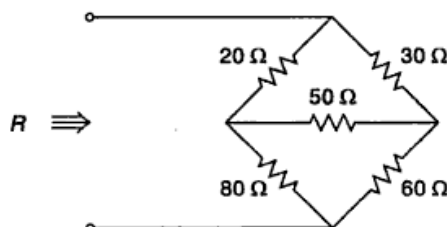


Fig. 4.57 Circuit of Ex. 4.40

Solution

Converting the upper delta network of Fig. 4.57 into a star network [Fig. 4.57(a)] we obtain the arm impedances of the equivalent star network as

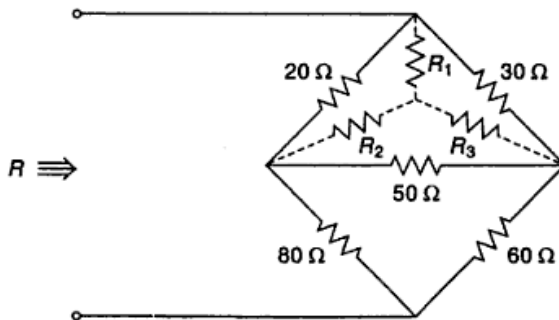


Fig. 4.57(a) Conversion of upper delta network to equivalent star for the network of Ex. 4.40

$$R_1 = \frac{20 \times 30}{20 + 30 + 50} = 6 \, \Omega$$

$$R_2 = \frac{20 \times 50}{20 + 30 + 50} = 10 \, \Omega$$

$$R_3 = \frac{30 \times 50}{20 + 30 + 50} = 15 \, \Omega.$$

Next we further reorient the network as shown in Fig. 4.57(b).

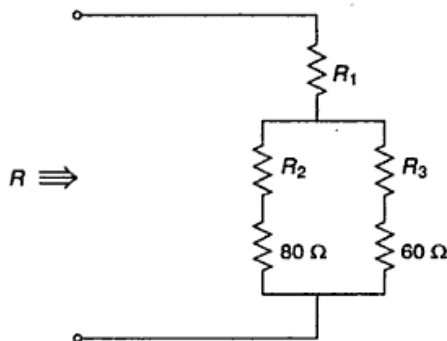


Fig. 4.57(b) Simplified equivalent of network of Fig. 4.57(a)

Here,

$$\begin{aligned}
 R &= 6 + \frac{(10 + 80) \times (15 + 60)}{(10 + 80) + (15 + 60)} \\
 &= 6 + \frac{90 \times 75}{90 + 75} \\
 &= 46.9 \, \Omega.
 \end{aligned}$$

Thus, the equivalent resistance of the network given in Fig. 4.57 is 46.9 Ω .

4.41. Using star-delta conversion, find the equivalent resistance between terminals *A* and *B* in the network shown in Fig. 4.58.

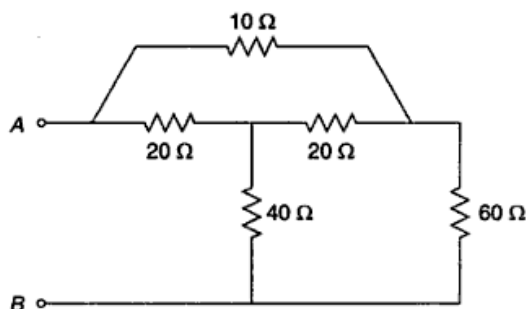


Fig. 4.58 Circuit of Ex. 4.41

Solution

Let us first convert the star connected network using 20 Ω , 20 Ω and 40 Ω resistors to an equivalent delta network [Ref. Fig. 4.58(a)].

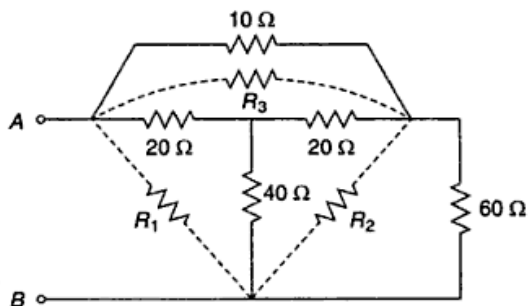


Fig. 4.58(a) Equivalent Δ network of a part of circuit of Fig. 4.58

Here,

$$R_1 = \frac{20 \times 40 + 20 \times 40 + 20 \times 20}{20} = 100 \Omega$$

$$R_2 = \frac{20 \times 40 + 20 \times 40 + 20 \times 20}{20} = 100 \Omega$$

$$R_3 = \frac{20 \times 40 + 20 \times 40 + 20 \times 20}{40} = 50 \Omega.$$

Figure 4.58(b) is the final form of the given network as reduced in Fig. 4.58(a).

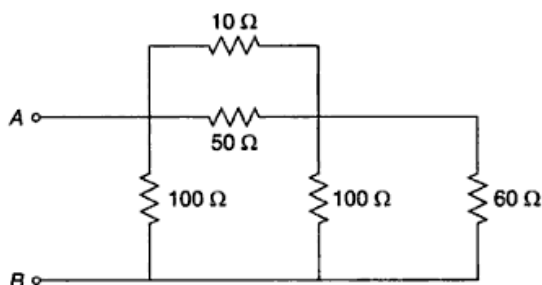


Fig. 4.58(b) Simplified equivalent of network of Ex. 4.41

Thus the equivalent resistance between terminals A and B is obtained as

$$\begin{aligned} R_{eq} &= 100 \parallel \left[\frac{50 \times 10}{50 + 10} + \frac{100 \times 60}{100 + 60} \right] \\ &= 100 \parallel \left(\frac{50}{6} + \frac{600}{16} \right) \\ &= 100 \parallel 45.83 \\ &= \frac{100 \times 45.83}{100 + 45.83} = 31.43 \, \Omega. \end{aligned}$$

The equivalent resistance across terminals A and B is thus $31.43 \, \Omega$

4.42 Find the resistance across terminals AB for the circuit shown in Fig. 4.59.

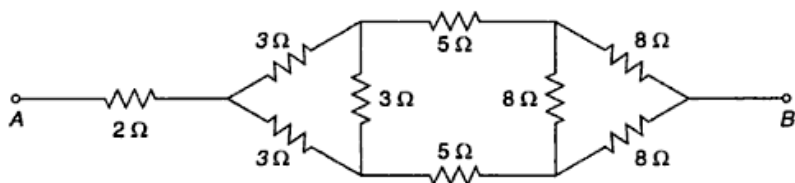


Fig. 4.59 Circuit of Ex. 4.42

Solution

We convert the two delta networks formed in the given circuit to equivalent star networks as shown in Fig. 4.59(a).

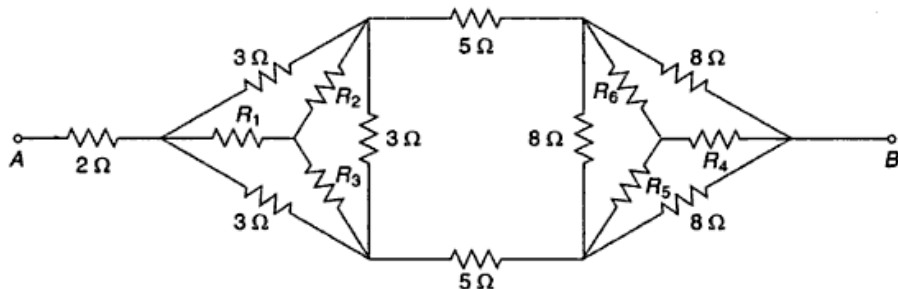


Fig. 4.59(a) Formation of equivalent stars for the given network in Ex. 4.42

We find, $R_1 = R_2 = R_3 = \frac{3 \times 3}{3 + 3 + 3} = 1 \, \Omega$

and $R_4 = R_5 = R_6 = \frac{8 \times 8}{8 + 8 + 8} = 2.67 \, \Omega$.

The equivalent resistance between terminals CD (Fig. 4.59(b)) can be obtained by redrawing Fig. 4.59(a) as Fig. 4.59(b).

$$\begin{aligned} R_{CD} &= (R_2 + 5 + R_6) \parallel (R_3 + 5 + R_5) \\ &= (1 + 5 + 2.67) \parallel (1 + 5 + 2.67) = 4.335 \, \Omega \end{aligned}$$

Hence the resistance between terminals AB of the given network is

$$\begin{aligned} R &= 2 + R_1 + 4.335 + R_4 = 2 + 1 + 4.335 + 2.67 \\ &= 10 \, \Omega. \end{aligned}$$

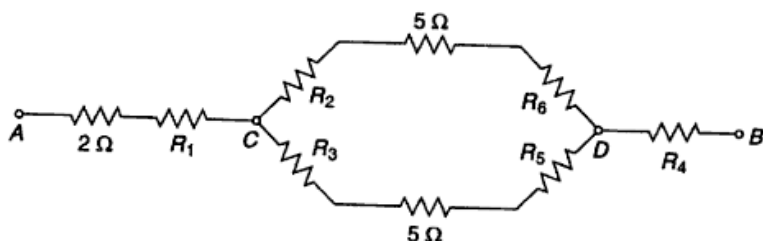


Fig. 4.59(b) Equivalent network of the circuit shown in Fig. 4.59(a)

4.43 Determine the resistance between points A and B in the network shown in Fig. 4.60.

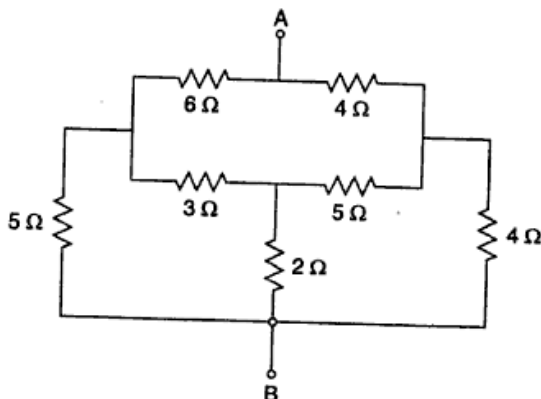


Fig. 4.60 Circuit of Ex. 4.43

Solution

Figure 4.60(a) is drawn to represent a star equivalent to the part of the given network containing resistances 3 Ω, 2 Ω and 5 Ω.

In Fig. 4.60(a),

$$R_1 = \frac{3 \times 2}{3 + 2 + 5} = 0.6 \, \Omega$$

$$R_2 = \frac{2 \times 5}{5 + 2 + 3} = 1 \, \Omega$$

$$R_3 = \frac{3 \times 5}{3 + 5 + 2} = 1.5 \, \Omega.$$

We redraw Fig. 4.60(a) as Fig. 4.60(b) and the circuit is further reduced to Fig. 4.60(c). We draw a star equivalent for the delta connected resistances 5.6 Ω, 4 Ω and 1 Ω in Fig. 4.60(c).

Here, $R_4 = \frac{1 \times 4}{1 + 4 + 5.6} = 0.377 \, \Omega$

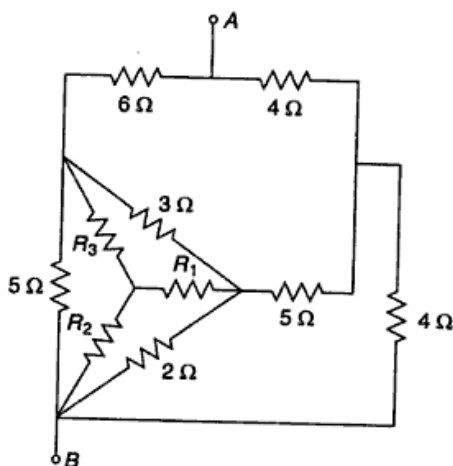


Fig. 4.60(a) Formation of star equivalent for a portion of network shown in Fig. 4.60

$$R_5 = \frac{1 \times 5.6}{1 + 4 + 5.6} = 0.528 \, \Omega$$

$$R_6 = \frac{4 \times 5.6}{1 + 4 + 5.6} = 2.11 \, \Omega$$

The final configuration of the given network is shown in Fig. 4.60(d). The resistance between terminals AB is then obtained as

$$\begin{aligned} R_{AB} &= \{(7.5 + 0.528) \parallel (4 + 2.11)\} + 0.377 \\ &= \frac{8.028 \times 6.11}{8.028 + 6.11} + 0.377 = 3.84 \, \Omega. \end{aligned}$$

The equivalent resistance across AB is then 3.84 Ω .

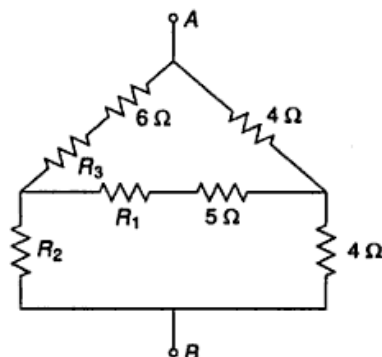


Fig. 4.60(b) Reduction of circuit shown in Fig. 4.60(a)

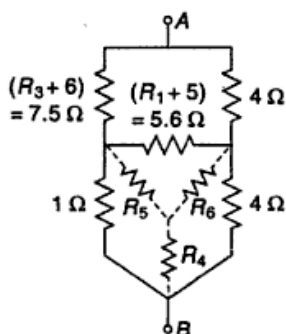


Fig. 4.60(c) Further simplification of circuit shown in Fig. 4.60(c)

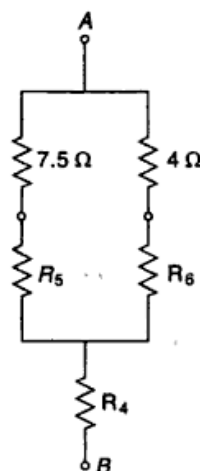


Fig. 4.60(d) Final simplified equivalent circuit of Ex. 4.43

4.10 VOLTAGE SOURCES AND CURRENT SOURCES

A network can sometimes be simplified by converting *voltage sources* to *current sources* and vice versa.

Voltage sources can be represented by an ideal voltage cell in series with the internal resistance of the cell or battery. The ideal cell is assumed to be a constant voltage source and the output current produces a voltage drop across the internal resistance. Figure 4.61 shows such a constant voltage source, with voltage E , source resistance R_s and an external load resistance R_L . Using the voltage divider rule in Art. 4.3.2 the output voltage developed across R_L can be determined.

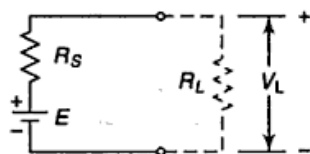


Fig. 4.61 A constant voltage source with a load resistor

$$V_L = E \frac{R_L}{R_S + R_L} \quad (4.32)$$

If $R_S \ll R_L$, then $V_L \cong E$

When the load resistance is very much larger than the source resistance, the constant voltage source is assumed to have zero source resistance and all of the source voltage is assumed to be applied to the load.

Certain electronic devices can produce a current that tends to remain constant regardless of how the load resistance varies. Hence it is possible to have a constant current source. The circuit of constant current source is shown in Fig. 4.62 with its source resistance R_S and a load resistance R_L .

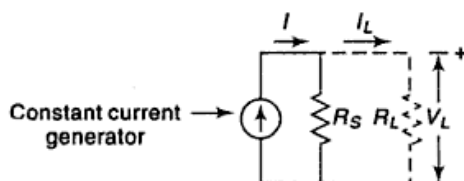


Fig. 4.62 A constant current source with a load resistor

Here R_S is in parallel with the current source. Hence some current flows through R_S and remaining through R_L . Using the current divider rule as shown in Art 4.4.3, the output current (or load current) from a constant current source can be determined in terms of R_L and R_S :

$$I_L = I \frac{R_S}{R_S + R_L} \quad (4.33)$$

If $R_S \gg R_L$ then $I_L \cong I$.

Figure 4.63(a) and Fig. 4.63(b) show how a voltage source can be converted into an equivalent current source that will produce the same current level in a given load resistor.

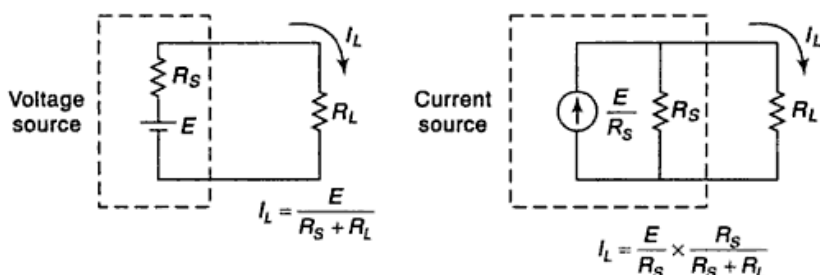


Fig. 4.63(a) & (b) Conversion of a constant voltage source to an equivalent constant current source

When the load resistance is very much smaller than the source resistance, a constant current source is assumed to have an infinite source resistance, and all of the source current is assumed to flow through the load.

4.10.1 Source Conversion

According to source conversion technique a given voltage source with a series resistance can be converted into an equivalent current source with a parallel resistance (as explained in Art. 4.10). Similarly, a current source with a parallel resistance can be converted into a voltage source with a series resistance.

Here we explain again the conversion of the constant voltage source shown in Fig. 4.64 into an equivalent constant current source.

The current supplied by the constant voltage source when a short circuit is placed across terminals 1 & 2 is $I = V/R$.

A constant current source supplying this current I and having the same resistance R connected in parallel with it represents the equivalent current source as shown in Fig. 4.65.

Similarly, a constant current source of I and a parallel resistance R can be converted into a constant voltage source of voltage $V (= IR)$ and a resistance R in series with it.

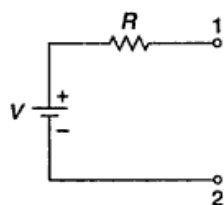


Fig. 4.64 A constant voltage source with series resistor

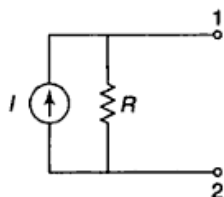


Fig. 4.65 Equivalent constant current source of the voltage source (V)

4.44 Convert the constant voltage source shown in Fig. 4.66 into equivalent current

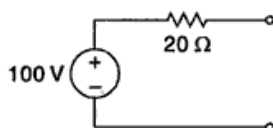


Fig. 4.66 Circuit of Ex. 4.44

source.

Solution

The current supplied by the 100 V source when a short circuit is placed across the output terminals is $I = 100/20 = 5$ A. So the value of the equivalent constant current source is 5 A; the equivalent circuit with current source is shown in Fig. 4.67.

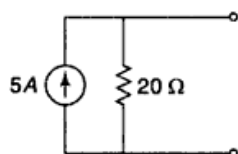


Fig. 4.67 Equivalent current source of the 100 V voltage source

4.45 Convert the constant current source of Fig. 4.68 into equivalent voltage source.

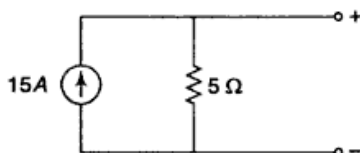


Fig. 4.68 Circuit of Ex. 4.45

Solution

The value of the equivalent constant voltage source is given as $V (= IR) = 15 \times 5 = 75 \text{ V}$. The equivalent network with the voltage source is shown in Fig. 4.68(a).

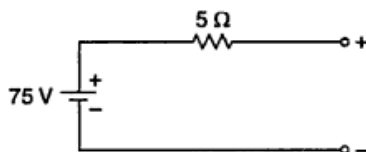


Fig. 4.68(a) Equivalent voltage source of 15 A current source

4.46 Use source transformation technique to find the current through the 2Ω resistor in Fig. 4.69.

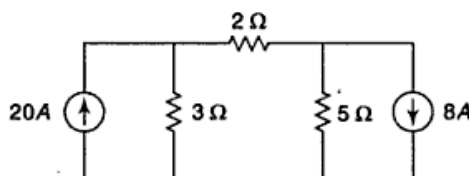


Fig. 4.69 Circuit of Ex. 4.46

Solution

Converting the two sources into equivalent voltage source, the network shown in Fig. 4.70 is obtained.

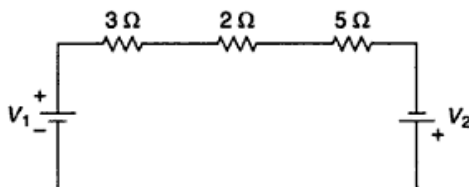


Fig. 4.70 Current sources of Fig. 4.69 converted to voltage sources

The values of V_1 and V_2 are $20 \times 3 = 60 \text{ V}$ and $8 \times 5 = 40 \text{ V}$ respectively.

As the voltage sources are series connected hence they deliver current in the same direction. Hence the current through 2Ω resistor is

$$\frac{60 + 40}{3 + 2 + 5} = 10 \text{ A.}$$

.....

4.47 By using source conversion technique find the value of voltage across R_L where $R_L = 4 \Omega$ in Fig. 4.71.

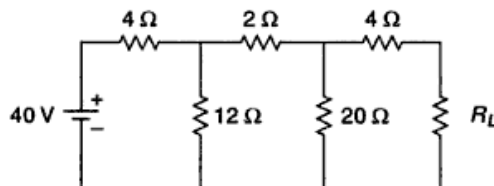


Fig. 4.71 Circuit of Ex. 4.47

Solution

Converting 40 V source into equivalent current source, in Fig. 4.71(a) the value of the current source is $40/4 = 10$ A.

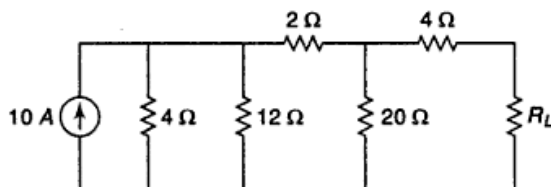


Fig. 4.71(a) Conversion of 40 V voltage source to equivalent current source

The combination of the parallel resistances of 4 Ω and 12 Ω is $(12 \times 4)/(12 + 4) = 3$ Ω (the network is shown in Fig. 4.71(b)).

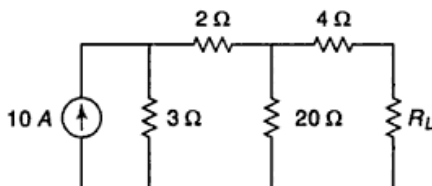


Fig. 4.71(b) Reduction of network shown in Fig. 4.71(a)

Converting 10 A current source into equivalent voltage source, the value of the voltage source is $10 \times 3 = 30$ V, the equivalent circuit is shown in Fig. 4.71(c).

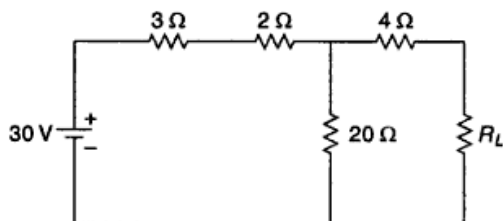


Fig. 4.71(c) Conversion of 10 A current source to equivalent voltage source

Again converting the voltage source into current source, the network in Fig. 4.71(d) is obtained where the parallel combination of 5 Ω and 20 Ω is $\frac{5 \times 20}{5 + 20} = 4$ Ω.

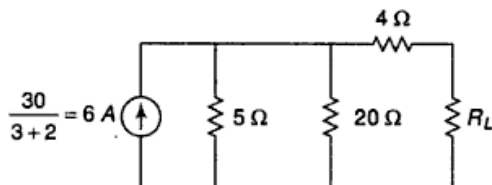


Fig. 4.71(d) Conversion of 30 V voltage source to an equivalent current source

Further converting the current source into voltage source (Fig. 4.71 (e)) we get current through R_L as $\frac{24}{4+4+4} = 2 \text{ A}$ and the voltage across R_L is $4 \times 2 = 8 \text{ V}$.

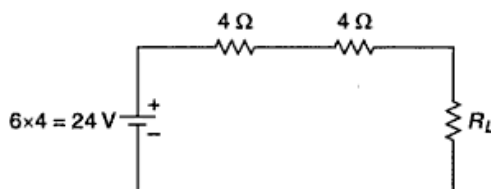


Fig. 4.71(e) Conversion of 6 A current source to equivalent voltage source

4.48 Using source conversion technique find the current I in Fig. 4.72.

Solution

The current source is connected in parallel with a 2Ω resistor; so the value of the equivalent voltage source is obtained as, $V = 10 \times 2 = 20 \text{ V}$ (as shown in Fig. 4.73)

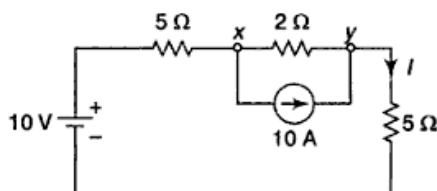


Fig. 4.72 Circuit of Ex. 4.48

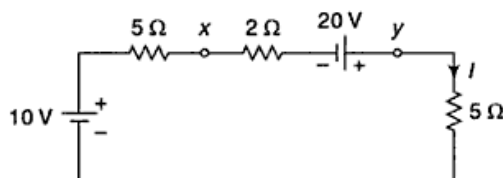


Fig. 4.73 Conversion of 10 A current source to equivalent voltage source

The current delivered by a 10 A source would flow from y to x in 20Ω resistor. The polarity of the 20 V source is shown in Fig. 4.73.

Therefore,
$$I = \frac{20 + 10}{5 + 2 + 5} = 2.5 \text{ A}.$$

4.49 Convert the circuit of Fig. 4.74 into a single voltage source in series with a single resistor.

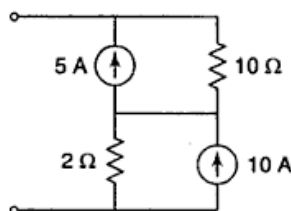


Fig. 4.74 Circuit of Ex. 4.49

Solution

Figure 4.74(a) represents the conversion of 5 A source into equivalent voltage source.

Fig. 4.74(b) represents conversion of 10 A current source into equivalent voltage source.

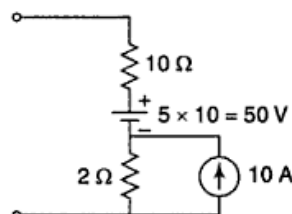


Fig. 4.74(a) Conversion of 5 A current source to equivalent voltage source

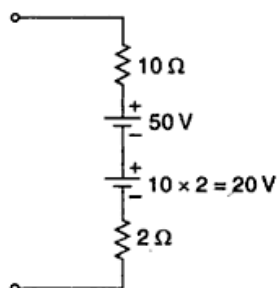


Fig. 4.74(b) Conversion of 10 A current source to equivalent voltage source

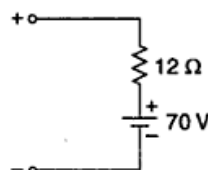


Fig. 4.74(c) Equivalent circuit of network shown in Fig. 4.74

The net voltage of the single voltage source is thus $(50 + 20) \text{ V} = 70 \text{ V}$ and the net resistance is $(10 + 2) \Omega = 12 \Omega$.

The equivalent circuit is shown in Fig. 4.74(c).

4.10.2 Independent and Dependent Sources

The voltage or current sources which do not depend on any other quantity in the circuit (i.e. the strength of voltage or current in the sources), and do not change for any change in the connected network, are called *independent sources*. Independent sources are represented by circles. An independent voltage source and an independent current source is shown in Fig. 4.74.1(a) and 4.74.1(b)

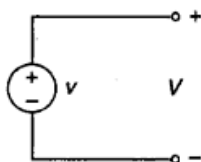


Fig. 4.74-1(a) Independent voltage source

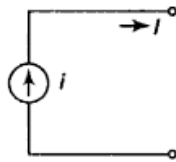


Fig. 4.74-1(b) Independent current source

A *dependent voltage or current source* is one which depends on some other quantity in the circuit (may be either voltage or current) i.e. the strength of voltage or current changes in the source for any change in the connected network. Dependent sources are represented by diamond-shaped symbol. There are four possible dependent sources:

Voltage dependent voltage source, as shown in Fig. 4.74.1(c).

Voltage dependent current source, as shown in Fig. 4.74.1(d).

Current dependent current source, as shown in Fig. 4.74.1(e).

Current dependent voltage source as shown in Fig. 4.74.1(f).

In the above figures a , b , c and d are the constants of proportionality a and c has no units, unit of b is siemens and unit of d is ohms.

Some examples of independent sources are battery, dc (or ac) generator. Dependent sources are parts of models which are used to represent electrical properties of electronic devices such as operational amplifiers and transistors etc.

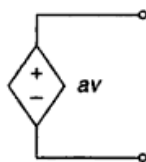


Fig. 4.74-1(c) Voltage dependent voltage source

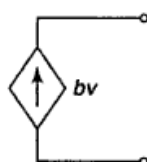


Fig. 4.74-1(d) Voltage dependent current source

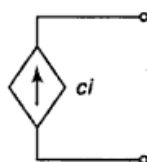


Fig. 4.74-1(e) Current dependent current source

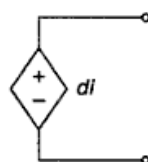


Fig. 4.74-1(f) Current dependent voltage source

4.11 SUPERPOSITION THEOREM

Statement: In a linear bilateral network containing several sources, the current through or voltage across any branch in the network equals the algebraic sum of the currents or voltages of each individual source considered separately with all other sources made inoperative, i.e., replaced by resistances equal to their internal resistances.

It may be noted here that while removing the voltage source it should be replaced by its internal resistance (if any) or by a short circuit and while removing the current source it should be replaced by an open circuit. Superposition theorem is applicable only to linear networks (both ac and dc) where current is linearly related to voltage as per Ohm's law.

..... Illustration

Let us find the current I as shown in Fig. 4.75 applying superposition theorem.

Considering the voltage source E_1 acting alone and removing the other voltage source E_2 after replacing it by its internal resistance (if any) otherwise short circuiting the source, the current through R_1 is [Fig. 4.75(a)]

$$I_1' = \frac{E_1}{R_1 + \frac{R R_2}{R + R_2}} \quad (4.34)$$

Hence current through R is

$$I' = I_1' \times \frac{R_2}{R + R_2} = \frac{E_1 R_2}{R R_1 + R_1 R_2 + R_2 R} \quad (4.35)$$

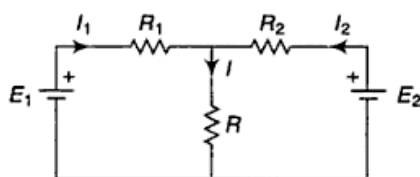
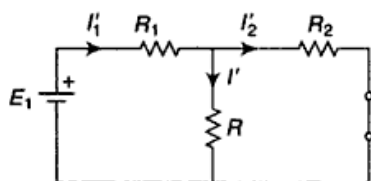
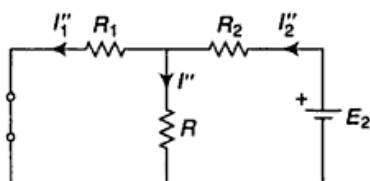


Fig. 4.75 A simple resistive network with two voltage sources

Fig. 4.75(a) Source E_1 retained, E_2 deactivatedFig. 4.75(b) Source E_2 retained, E_1 deactivated

Similarly considering the voltage source E_2 acting alone removing the source E_1 and replacing it by a short circuit [Fig. 4.75(b)], the current through R_1 , R_2 and R being I_1'' , I_2'' and I'' respectively, we find for E_2 acting alone

$$I_2'' = \frac{E_2}{R_2 + \frac{RR_1}{R + R_1}} \quad (4.36)$$

and
$$I'' = I_2'' \times \frac{R_1}{R + R_1} = \frac{E_2 R_1}{RR_2 + R_2 R_1 + RR_1} \quad (4.37)$$

Therefore, if there are two sources connected through a network, the resultant current flowing through R is

$$I = I' + I'' = \frac{E_1 R_2 + E_2 R_1}{RR_2 + R_2 R_1 + RR_1} \quad (4.38)$$

4.11.1 Procedure for Applying Superposition Theorem

1. Select one source and replace all other sources by their internal impedances.
2. Determine the level and direction of the current that flows through the desired branch as a result of the single source acting alone.
3. Repeat steps 1 and 2 using each source in turn until the branch current components have been calculated for all sources.
4. Algebraically sum the component currents to obtain the actual branch current(s).

4.50 Compute the current in the $10\ \Omega$ resistor as shown in Fig. 4.76 using Superposition theorem.

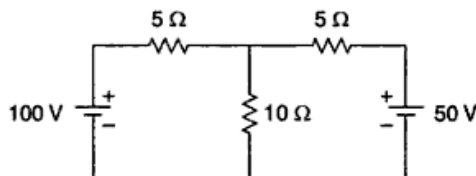


Fig. 4.76 Circuit of Ex. 4.50

Solution

Considering the 100 V source acting alone, the direction of currents supplied by the source has been shown in Fig. 4.76(a).

Here
$$I_1 = \frac{100}{5 + \frac{10 \times 5}{10 + 5}} = \frac{1500}{125} \text{ A}$$

Hence current through 10Ω resistor $I' = I_1 \times \frac{5}{5 + 10} = 4 \text{ A}$

Considering a 50 V source acting alone the direction of currents supplied by the source are shown in Fig. 4.76(b).

Here,
$$I_2 = \frac{50}{5 + \frac{10 \times 5}{10 + 5}} = \frac{750}{125} \text{ A}$$

Hence current through the 10Ω resistor is

$$I'' = I_2 \times \frac{5}{5 + 10} = 2 \text{ A}$$

When both the sources are acting simultaneously, the current through 10Ω resistor (according to Superposition theorem) is given by $(I' + I'')$ i.e., $(4 \text{ A} + 2 \text{ A} = 6 \text{ A})$.

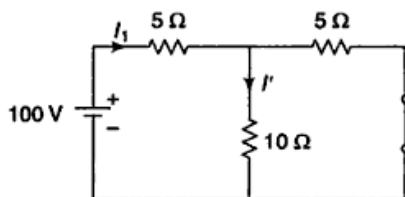


Fig. 4.76(a) Source 100 V only considered

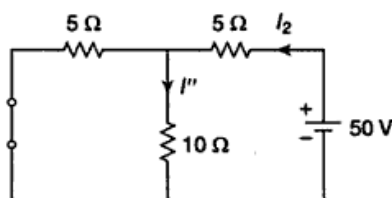


Fig. 4.76(b) Source 50 V only considered

4.51 Find the current in the 50Ω resistor in Fig. 4.77 using Superposition theorem.

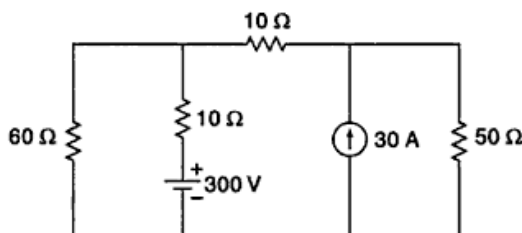


Fig. 4.77 Circuit of Ex. 4.51

Solution

Considering the voltage source acting alone and removing the current source (the corresponding figure being shown in Fig. 4.77(a)) the total current supplied by the voltage source is

$$I_1 = \frac{300}{10 + \frac{60(10 + 50)}{60 + (10 + 50)}} = \frac{15}{2} \text{ A}$$

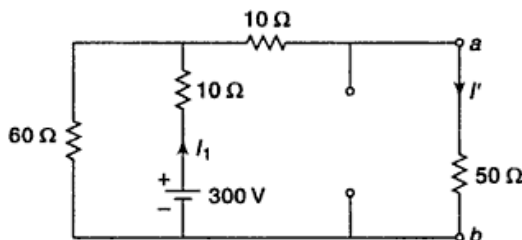


Fig. 4.77(a) Voltage source is acting only

Hence the current through the $50\ \Omega$ resistor due to the voltage source acting alone is

$$I' = \frac{15}{2} \times \frac{60}{60+10+50} = \frac{15}{4}\text{ A} = 3.75\text{ A (from } a \text{ to } b)$$

Next, removing the voltage source and considering the current source acting alone (the corresponding networks being shown in Fig. 4.77(b) and Fig. 4.77(c)), the current through the $50\ \Omega$ resistor is

$$I'' = 30 \times \frac{10+60/7}{50+10+60/7} = 8.124\text{ A (from } a \text{ to } b)$$

[The combined resistance of the $60\ \Omega$ and $10\ \Omega$ in parallel is $\frac{60 \times 10}{60+10} = \frac{60}{7}\ \Omega$]

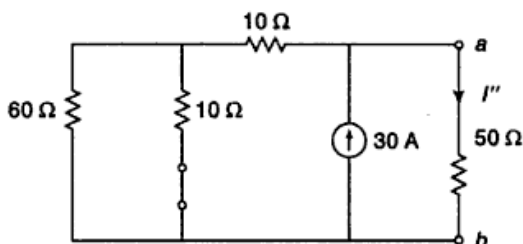


Fig. 4.77(b) Current source is acting only

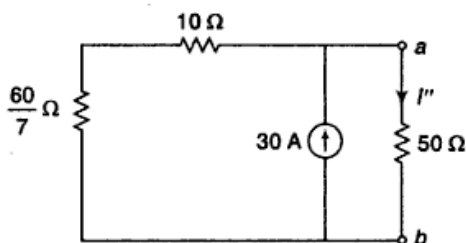


Fig. 4.77(c) Simplified circuit of network shown in Fig. 4.77(b)

According to the Superposition theorem when both the sources are acting simultaneously, the current through the $50\ \Omega$ resistor is

$$I' + I'' = (3.75 + 8.124)\text{ A} = 11.874\text{ A (from } a \text{ to } b)$$

4.52 Obtain I using the Superposition theorem for the network shown in Fig. 4.78.

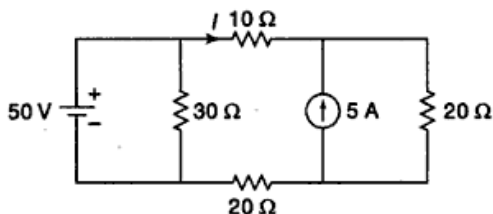


Fig. 4.78 Circuit of Ex. 4.52

Solution

Considering the voltage source acting alone [Fig. 4.78(a)] the current supplied by the source is

$$I_1 = \frac{50}{\frac{30(10+20+20)}{30+(10+20+20)}} = \frac{8}{3} \text{ A}$$

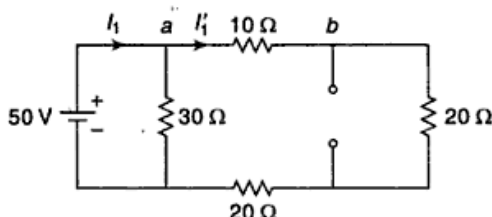


Fig. 4.78(a) Voltage source is acting alone

Hence the current through the 10 Ω resistor is

$$I'_1 = \frac{8}{3} \times \frac{30}{30+10+20+20} = 1 \text{ A (from } a \text{ to } b)$$

Removing the voltage source and considering the current source acting alone [Fig. 4.78(b)] the current through the 30 Ω resistor is zero as there is a short circuit path in parallel with it. Hence the network of Fig. 4.78(b) reduces to that in Fig. 4.78(c). The current through the 10 Ω resistor is then given by

$$I'' = 5 \times \frac{20}{20+20+10} = 2 \text{ A (from } b \text{ to } a) \text{ (or } -2 \text{ A from } a \text{ to } b)$$

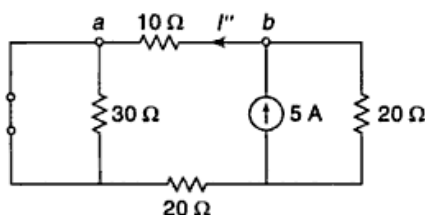


Fig. 4.78(b) Current source is acting alone

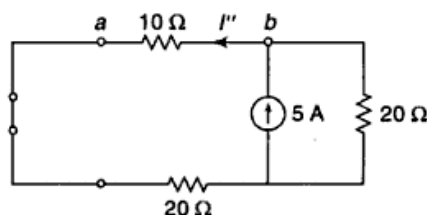


Fig. 4.78(c) Simplified circuit of Fig. 4.78(b)

Therefore according to the Superposition theorem when both the sources are acting simultaneously the current

$$I = I' + I'' = 1 - 2 = -1 \text{ A (from } a \text{ to } b)$$

.....

4.53 Find the voltage across 20 Ω resistor using the Superposition theorem in Fig. 4.79.

Solution

When 1 A current source is acting alone (the corresponding figure being shown in Fig. 4.79(a), the current through the 20 Ω resistor under this condition is obtained as $1 \times$

$$\frac{4+5}{20+4+5} = \frac{9}{29} \text{ A (from } a \text{ to } b)$$

Hence voltage across 20 Ω resistor is $\frac{9}{29} \times 20 = \frac{180}{29} \text{ V } (= V'_{ab})$

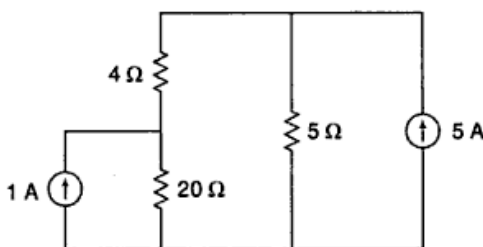


Fig. 4.79 Circuit of Ex. 4.53

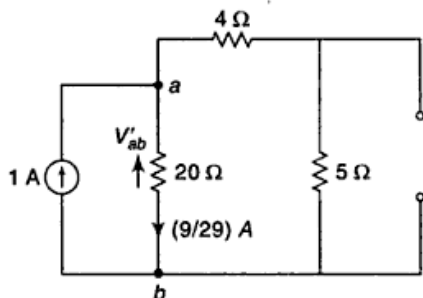


Fig. 4.79(a) Current source (1 A) acting alone

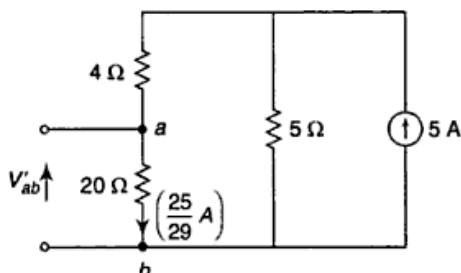


Fig. 4.79(b) Current source (5 A) is acting alone

Fig. 4.79(b) shows the network when 1 A source is deactivated and 5 A source acts alone. The current through 20 Ω resistor under this condition is

$$5 \times \frac{5}{5 + 4 + 20} \text{ A} = \frac{5 \times 5}{29} \text{ A} = \frac{25}{29} \text{ A (from } a \text{ to } b)$$

The voltage across the 20 Ω resistor is then $V_{ab}'' = \frac{25}{29} \times 20 \text{ V} = \frac{500}{29} \text{ V}$

According to the Superposition theorem the voltage across 20 Ω resistor (V_{ab}) when both sources are acting simultaneously is

$$V_{ab} = V_{ab}' + V_{ab}'' = \frac{180}{29} + \frac{500}{29} = \frac{680}{29} \text{ V} = 23.45 \text{ V}$$

.....

4.54 Find the current through 40 Ω resistor using Superposition theorem in Fig. 4.80.

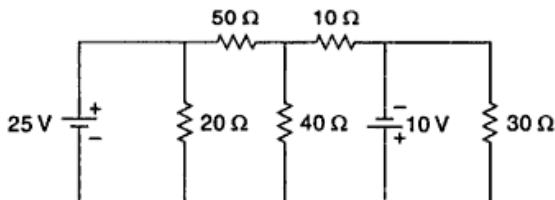


Fig. 4.80 Circuit of Ex. 4.54

Solution

Let us consider that the 25 V source is acting alone and the other source is deactivated. The corresponding figures are shown in Fig. 4.80(a) and Fig. 4.80(b).

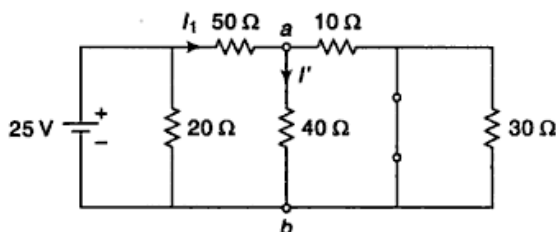


Fig. 4.80(a) 25 V source is acting alone

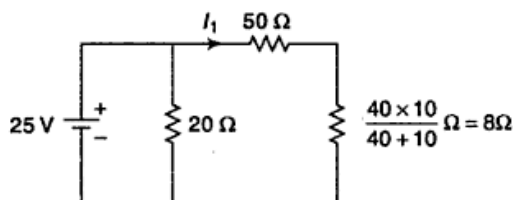


Fig. 4.80(b) Simplified circuit of Fig. 4.80(a)

The current through 50 Ω resistor is

$$I_1 = \frac{25}{\frac{20 \times 58}{20 + 58}} \times \frac{20}{20 + 50 + 8} = 0.431 \text{ A}$$

Hence the current through 40 Ω resistor due to 25 V source alone is

$$I' = 0.431 \times \frac{10}{40 + 10} \text{ A} = 0.0862 \text{ A} \quad (\text{from } a \text{ to } b \text{ in Fig. 4.80(a)})$$

Next consider the 10 V source acting alone deactivating the 25 V source.

The current through the 10 Ω resistor [Fig. 4.80(c) and Fig. 4.80(d)] is

$$I_2 = \frac{10}{\frac{30 \times (200/9 + 10)}{30 + 200/9 + 10}} \times \frac{30}{30 + 200/9 + 10} = 0.31 \text{ A}$$

Hence the current through the 40 Ω resistor is

$$I'' = 0.31 \times \frac{50}{50 + 40} = 0.172 \text{ A (from } b \text{ to } a)$$

Using the Superposition theorem the current through the 40 Ω resistor is

$$I'' - I' = 0.172 - 0.086 = 0.086 \text{ A (from } b \text{ to } a)$$

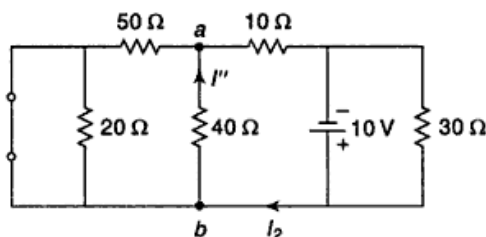


Fig. 4.80(c) 10 V source is acting alone

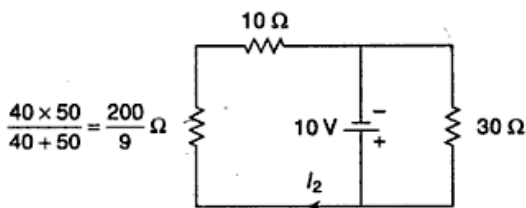


Fig. 4.80(d) Simplified circuit of Fig. 4.80(c)

4.55 Utilising the Superposition theorem find the current through the $20\ \Omega$ resistor for the network shown in Fig. 4.81.

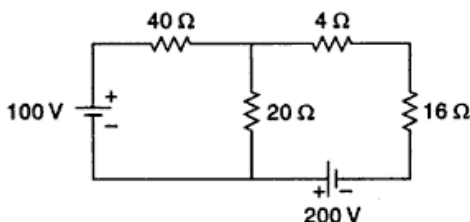




Fig. 4.81 Circuit of Ex. 4.55

Solution

Considering the 10 V source acting alone [Fig. 4.81(a)] the current through the $20\ \Omega$ resistor is

$$I_1 = \frac{100}{40 + \frac{20 \times (4 + 16)}{20 + 4 + 16}} \times \frac{4 + 16}{4 + 16 + 20} \text{ A}$$

$$= 1 \text{ A (from } a \text{ to } b)$$

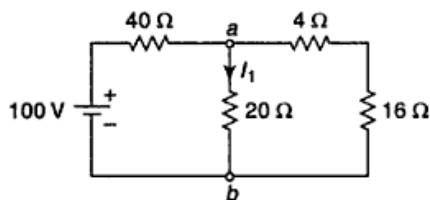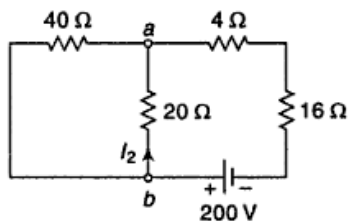Fig. 4.81(a) 100 V source is acting aloneFig. 4.81(b) 200 V source is acting alone

Considering the 200 V source acting alone [Fig. 4.81(b)] the current through the $20\ \Omega$ resistor is

$$I_2 = \frac{200}{16 + 4 + (40 \times 20)/(40 + 20)} \times \frac{40}{40 + 20} = 4 \text{ A (from } b \text{ to } a)$$

Then, according to the Superposition theorem, the current through $20\ \Omega$ resistor is $(I_2 - I_1) = 4 - 1 = 3 \text{ A (from } b \text{ to } a)$.

4.56 Find the current through $1\ \Omega$ resistor applying the Superposition theorem in Fig. 4.82.

Solution

Consider 10 V source acting alone (the corresponding figures are shown in Fig. 4.82(a) and Fig. 4.82(b)).

$$I_1 = \frac{10}{5 + \frac{4 \times (8 + (5/6))}{4 + 8 + (5/6)}} \times \frac{4}{4 + 8 + (5/6)}$$

$$= 0.4\text{ A}$$

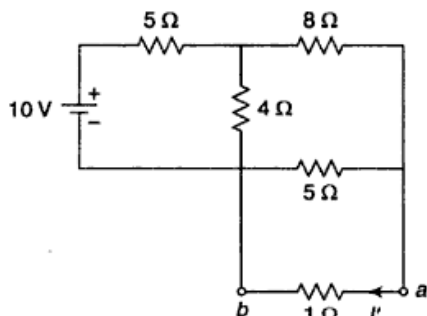


Fig. 4.82(a) 10 V source is acting alone

Therefore current through the $1\ \Omega$ resistor is

$$I' = 0.4 \times \frac{5}{5 + 1} = 0.33 \text{ (from } a \text{ to } b)$$

Next considering the 5 V source acting alone (corresponding figures are shown in Fig. 4.82(c) and Fig. 4.82(d)).

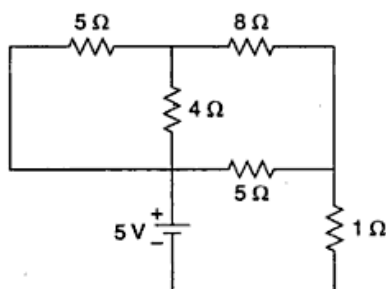


Fig. 4.82(c) 5 V source is acting alone

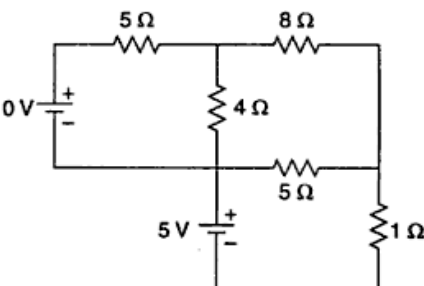


Fig. 4.82 Circuit of Ex. 4.56

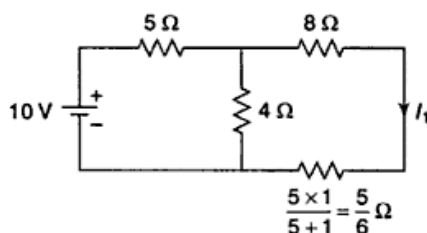


Fig. 4.82(b) Simplified circuit of Fig. 4.82(a)

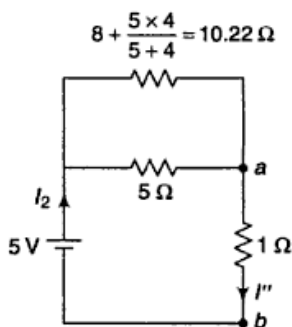


Fig. 4.82(d) Simplified circuit of Fig. 4.82(c)

The current supplied by 5 V source is

$$I_2 = \frac{5}{5 + \frac{5 \times 10.22}{1 + \frac{5}{5 + 10.22}}} \text{ A} = 1.147\text{ A}$$

The current through the $1\ \Omega$ resistor due to the 5 V source acting alone is then

$$I'' = I_2 = 1.147 \text{ (from } a \text{ to } b)$$

Hence according to Superposition theorem the current through the $1\ \Omega$ resistor is obtained as

$$I' + I'' = 0.333 + 1.147 = 1.48\text{ A}$$

4.57. Find the current through resistance (R_L) for the network shown in Fig. 4.83 using the Superposition theorem

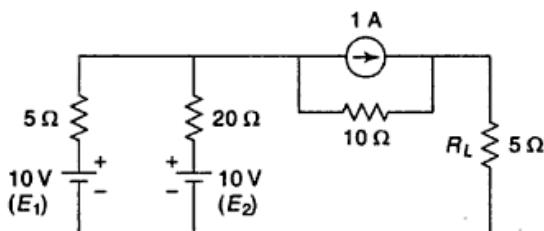


Fig. 4.83 Circuit of Ex. 4.57

Solution

Considering the 10 V source (E_1) acting alone the current through R_L [Fig. 4.83(a)] is

$$I_1 = \frac{10}{5 + \frac{20 \times 15}{20 + 15}} \times \frac{20}{20 + 15} = 0.42\text{ A (from } a \text{ to } b)$$

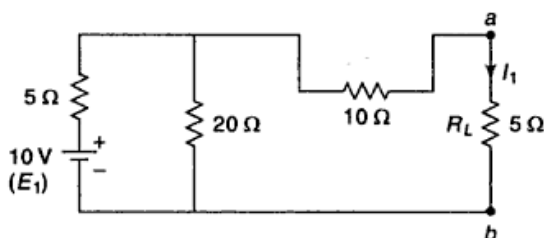


Fig. 4.83(a) 10 V source (E_1) is acting alone

Next, considering the other 10 V source (E_2) acting alone the current through R_L [Fig. 4.83(b)] is

$$I_2 = \frac{10}{20 + \frac{5 \times 15}{5 + 15}} \times \frac{5}{5 + 15} = 0.105\text{ A (from } a \text{ to } b)$$

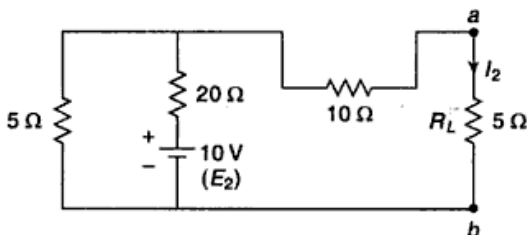


Fig. 4.83(b) Another 10 V source (E_2) is acting alone

Considering the current source (1A) acting alone the current through R_L [Fig 4.83(c) and Fig. 4.83(d)] is

$$I_3 = 1 \times \frac{10}{10+5+4} = \frac{10}{19} \text{ A} = 0.5263 \text{ A (from } a \text{ to } b).$$

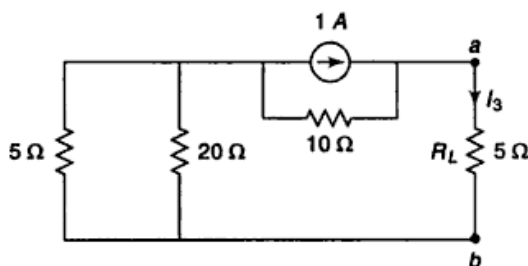


Fig. 4.83(c) 1 A current source is acting alone

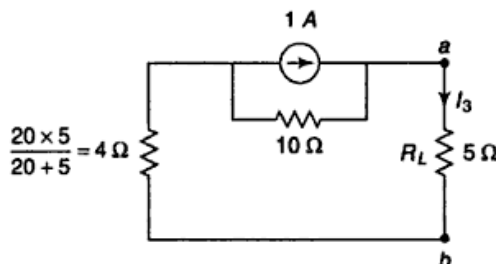


Fig. 4.83(d) Simplified circuit of Fig. 4.83(c)

Hence, according to the Superposition theorem the current through R_L , when all the sources are acting simultaneously, is obtained as $I_1 + I_2 + I_3 = 1.0513 \text{ A}$

4.12 THEVENIN'S THEOREM

Statement: The current flowing through a load resistance R_L connected across any two terminals A and B of a linear, bilateral network is given by $\frac{V_{oc}}{R_i + R_L}$, where

V_{oc} is the open circuit voltage (i.e. voltage across terminals AB when R_L is removed) and R_i is the internal resistance of the network as viewed back into the open circuited network from terminals AB deactivating all the independent sources. The following are the limitations of this theorem:

- Thevenin's theorem can not be applied to a network which contains non-linear impedances.
- This theorem can not calculate the power consumed internally in the circuit or the efficiency of the circuit.

Thevenin's theorem can be explained with the help of the following simple example. The steps are as follows:

Step I

R_L is to be removed from the circuit terminals a and b for the network shown in Fig. 4.84.

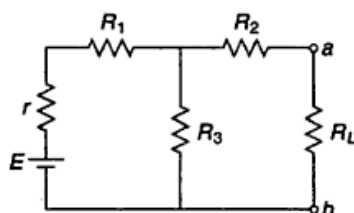
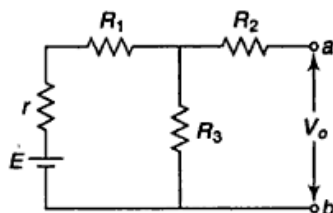


Fig. 4.84 Circuit to explain Thevenin's theorem

Fig. 4.84(a) R_L removed from circuit of Fig. 4.84**Step II**

The open circuit voltage (V_{oc}) which appears across terminals a and b in Fig. 4.84(a) is calculated as

$$V_{oc} (= \text{Voltage across } R_3) = \frac{E}{r + R_1 + R_3} \times R_3$$

V_{oc} is called the "Thevenin's voltage" (V_{Th})

Hence,
$$V_{Th} = \frac{ER_3}{r + R_1 + R_3} \quad (4.39)$$

Step III

Removing the battery from the circuit leaving the internal resistance (r) of the battery behind it [Fig. 4.84(b)] when viewed from terminals a and b , the internal resistance of the circuit is given by

$$R_i = R_2 + \frac{R_3 (R_1 + r)}{R_3 + R_1 + r}$$

This resistance R_i is called *Thevenin's equivalent resistance* (R_{Th})

$\therefore R_i = R_{Th} = R_2 + \frac{R_3 (R_1 + r)}{R_3 + R_1 + r} \quad (4.40)$

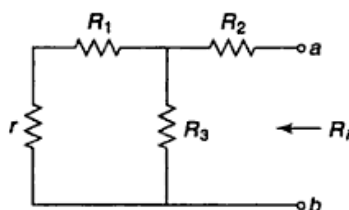
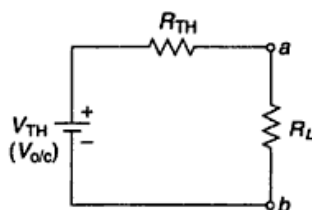
Fig. 4.84(b) Internal resistance R_i of the given network

Fig. 4.84(c) Thevenin's equivalent circuit

Step IV

Thevenin's equivalent circuit is drawn as shown in Fig. 4.84(c) and R_L is reconnected across terminals a and b . The current through R_L is

$$I_{Th} = \frac{V_{Th}}{R_{Th} + R_L}$$

Different methods of finding R_{Th}

- (a) *For independent sources:* Deactivate the sources, i.e. for independent current source deactivate it by open circuiting its terminals and for voltage source deactivate it by shorting it. Then find the internal resistance of the network looking through the load terminals kept open circuited. In case these independent sources are non-ideal, the internal resistance will remain connected across the deactivated source terminals.
- (b) *For dependent sources in addition or in absence of independent source:*

First Method

- (i) Find open circuit voltage V_{oc} across the open circuited load terminals. Next short circuit the load terminals and find the short circuit current (I_{sc}) through the shorted terminals. The Thevenin's equivalent resistance is then obtained as

$$R_{Th} = \frac{V_{oc}}{I_{sc}}$$

Second Method

- (ii) Remove the load resistance and apply a dc voltage V_{dc} at the open circuited load terminals. keep the other independent sources deactivated. A dc current I_{dc} will flow in the circuit from the load terminals. The Thevenin's equivalent resistance is then

$$R_{Th} = \frac{V_{dc}}{I_{dc}}$$

4.12.1 Thevenizing Procedure

1. Calculate the open circuit voltage (V_{Th}) across the network terminals.
2. Redraw the network with each independent source replaced by its internal resistance. This is called "deactivation of the sources".
3. Calculate the resistance (R_{Th}) of the redrawn network as seen from the output terminals.

4.58 Using Thevenin's theorem find the current through the $15\ \Omega$ resistor in Fig. 4.85.

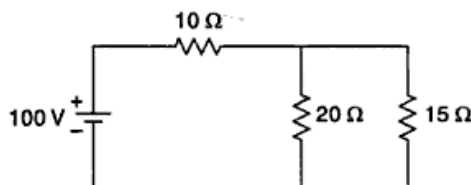


Fig. 4.85 Circuit of Ex. 4.58

Solution

Removing the $15\ \Omega$ resistor the open circuit voltage across a and b [Fig. 4.85(a)] is $V_{oc} =$

$$\frac{100}{10 + 20} \times 20\text{ V} = \frac{200}{3}\text{ V.}$$

The Thevenin's equivalent voltage is

$$V_{Th} (= V_{oc}) = \frac{200}{3} \text{ V}$$

Next removing the source, the internal resistance of the network as viewed from the open circuited terminals [Fig. 4.85(b)]

is $R_i = \frac{10 \times 20}{20 + 10}$ i.e. Thevenin's equivalent

resistance is $R_{Th} = R_i = (20/3) \Omega$. Thevenin's equivalent circuit is shown in Fig. 4.85 (c). The current through the 15Ω resistor (according to Thevenin's theorem) is then given by

$$I_{15} = \frac{(200/3)}{(20/3) + 15} \text{ A} = \frac{200}{65} \text{ A} = 3.077 \text{ A}$$

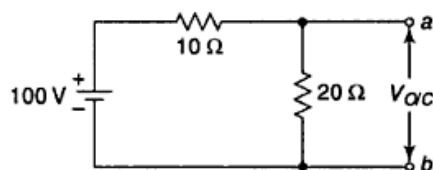


Fig. 4.85(a) Finding (V_{olc})

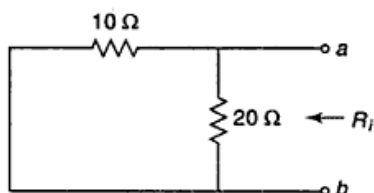


Fig. 4.85(b) Finding of R_i (R_{th})

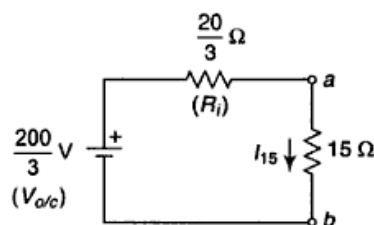


Fig. 4.85(c) Thevenin's equivalent circuit (Ex. 4.58)

4.59 Find the current through the 2Ω resistor using Thevenin's theorem [Fig. 4.86].

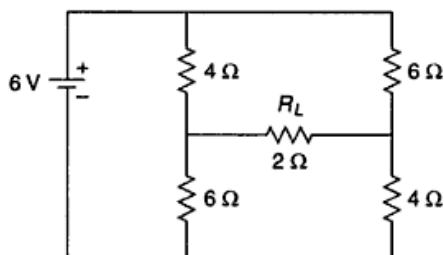


Fig. 4.86 Circuit of Ex. 4.59

Solution

The circuit is redrawn in Fig. 4.86(a) with terminals of R_L open circuited.

Thevenin's equivalent voltage is

$$\begin{aligned} V_{Th} &= V_{bd} = V_{cd} - V_{ab} \\ &= 6 \times \frac{6}{6+4} - 6 \times \frac{4}{6+4} \\ &= 3.6 - 2.4 \\ &= 1.2 \text{ V } [V_b \text{ is higher potential}]. \end{aligned}$$

Deactivating the voltage source, Thevenin's equivalent resistance is shown in Fig. 4.86(b) and Fig. 4.86(c).

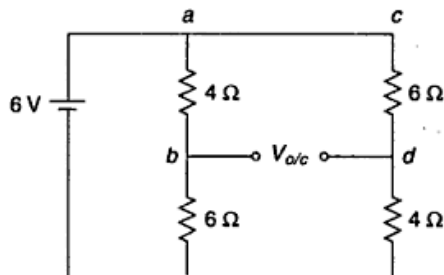
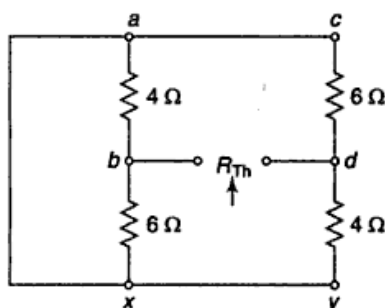
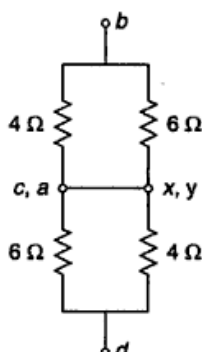


Fig. 4.86(a) Finding of (V_{olc})

Fig. 4.86(b) Finding of (R_{th})Fig. 4.86(c) Reduced equivalent network to find R_{th}

$$R_{Th} = (4 \parallel 6) + (6 \parallel 4) = 2 \times \frac{4 \times 6}{4 + 6} \Omega = 4.8 \Omega$$

Thevenin's equivalent circuit is shown in Fig. 4.86(d)

The current through (R_L) is then $I_L = \frac{1.2}{4.8 + 2} A$

$$= \frac{1.2}{6.8} = 0.176 A$$

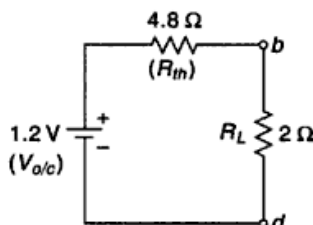


Fig. 4.86(d) Thevenin's equivalent circuit of Ex. 4.59

4.60 Find the current through 10 Ω resistor in Fig. 4.87 using Thevenin's theorem.

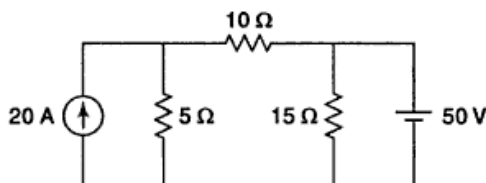
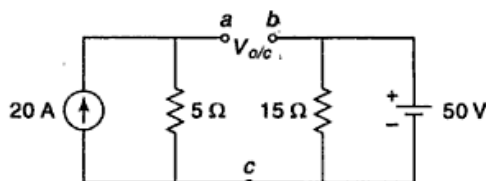


Fig. 4.87 Circuit of Ex. 4.60

Solution

Removing the load resistance of 10 Ω from its terminals, the open circuit voltage across terminals a and b (as shown in Fig. 4.87(a)) can be found out.

Fig. 4.87(a) Finding of $V_{o/c}$

The voltage across the 15 Ω resistor is due to the current supplied by the voltage source only.

∴ Voltage across the $15\ \Omega$ resistor is 50 V .

Hence $V_{bc} = 50\text{ V}$; Also, $V_{ac} = 20\text{ A} \times 5\ \Omega = 100\text{ V}$.

Therefore voltage across open circuit terminals a and b is

$$V_{oc} = V_{ab} = V_{ac} - V_{bc} = (100 - 50)\text{ V} = 50\text{ V}$$

i.e. $V_{Th} = 50\text{ V}$ ($= V_{oc}$).

Deactivating all the sources as shown in Fig. 4.87(b), the internal resistance of the network as viewed from the open circuited terminals is,

$R_{Th} = 5\ \Omega$ (as $15\ \Omega$ resistor is short circuited)

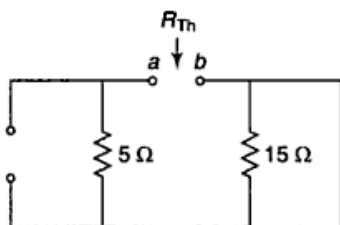


Fig. 4.87(b) Finding of R_{Th}

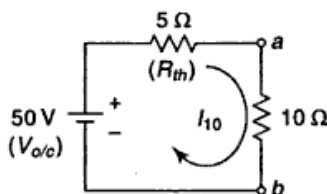


Fig. 4.87(c) Thevenin's equivalent circuit of Ex. 4.60

Thevenin's equivalent circuit is shown in Fig. 4.87(c). The current through $10\ \Omega$

$$\text{resistor is } I_{10} = \frac{V_{Th}}{R_{Th} + R_L} = \frac{50}{5 + 10}\text{ A} = 3.33\text{ A}.$$

.....

4.61 Find the current through $15\ \Omega$ resistor for the network shown in Fig. 4.88 using Thevenin's theorem.

Solution

Removing $15\ \Omega$ resistor the open circuit voltage across its terminals is found out in the network of Fig. 4.88(a).

The current through $10\ \Omega$ resistor is obtained as

$$\frac{200}{10 + 5}\text{ A} = \frac{200}{15}\text{ A}.$$

Voltage across the $10\ \Omega$ resistor is given by $V_{xa} =$

$$10 \times \frac{200}{15} = \frac{2000}{15}.$$

Current through the $12\ \Omega$ resistor is found as

$$\frac{200}{12 + 16}\text{ A} = \frac{200}{28}\text{ A}.$$

Voltage across the $12\ \Omega$ resistor is obtained as

$$V_{xb} = 12 \times \frac{200}{28}\text{ V} = \frac{2400}{28}\text{ V}.$$

$$\begin{aligned} V_{ab} &= V_{xb} - V_{xa} \\ &= \frac{2400}{28} - \frac{2000}{15} = 85.71\text{ V} - 133.33\text{ V} \\ &= -47.62\text{ V}. \end{aligned}$$

Hence b is at higher potential with respect to a .

Therefore $V_{Th} = V_{ba} = 47.62\text{ V}$.

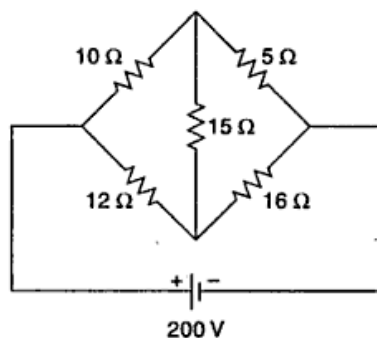


Fig. 4.88 Circuit of Ex. 4.61

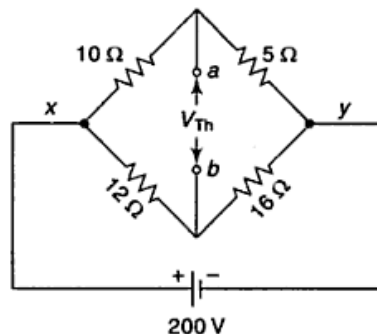
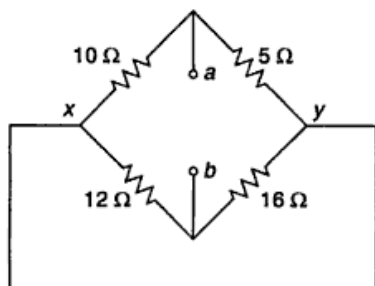
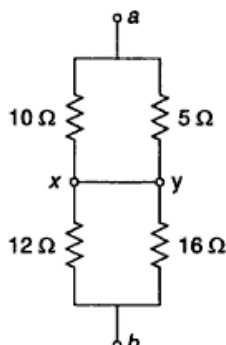


Fig. 4.88(a) Finding of V_{Th}

Deactivating the voltage source, Thevenin's equivalent resistance can be obtained as shown in Fig. 4.88(b) and Fig. 4.88(c).

Fig. 4.88(b) Finding of R_t Fig. 4.88(c) Reduced network to find R_t

The resistance between a and b is then found as

$$\begin{aligned} R_{Th} &= (10 \parallel 12) + (5 \parallel 16) \\ &= \frac{10 \times 12}{10 + 12} + \frac{5 \times 16}{5 + 16} \\ &= 10.19 \, \Omega (= R_t) \end{aligned}$$

\therefore Current through $15 \, \Omega$ resistor [Fig. 4.58d] is

$$I_{15} = \frac{V_{Th}}{R_{Th} + R_L} = \frac{47.62}{10.19 + 15} = 1.89 \, \text{A}$$

[flowing from terminal b to terminal a]

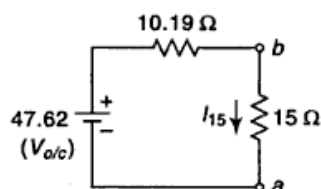


Fig. 4.88(d) Thevenin's equivalent circuit of Ex. 4.61

4.62 Find Thevenin's equivalent circuit of the network (shown in Fig. 4.89) across terminals x - y .

Solution

The voltage across the open circuited terminals is same as the voltage across the $6 \, \Omega$ resistor.

$\therefore V_{Th} = \text{Voltage across the } 6 \, \Omega \text{ resistor}$

$$= \frac{50}{5+6} \times 6 = \frac{300}{11} = 27.27 \, \text{V.}$$

Removing the source, Thevenin's equivalent resistance R_{Th} (Fig. 4.89(a)) is $10 + \frac{5 \times 6}{5+6} = 10 + \frac{30}{11} = 12.72 \, \Omega$.

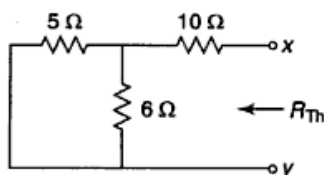
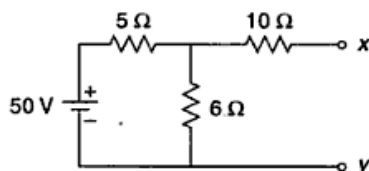
Fig. 4.89(a) Finding of (R_{Th}) 

Fig. 4.89 Circuit of Ex. 4.62

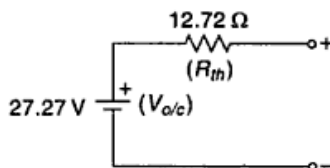


Fig. 4.89(b) Thevenin's equivalent circuit of Ex. 4.62

Thevenin's equivalent circuit is shown in Fig. 4.89(b).

4.63 Find Thevenin's equivalent circuit of the network shown in Fig. 4.90 across terminals a - b .

Solution

Removing the $3\ \Omega$ resistor, the circuit is redrawn as shown in Fig. 4.90(a). From Fig. 4.90(a) the circulating current is,

$$I = \frac{30+10}{2+1}\text{ A} = 13.33\text{ A.}$$

Applying KVL in loop $abxy$,

$$V_{ab} = -13.33 \times 2 + 30 = 3.34\text{ V}$$

$$\therefore V_{oc} (= V_{Th}) = 3.34\text{ V.}$$

Next deactivating the sources, Thevenin's equivalent resistance [Fig. 4.90(b)] is given by

$$R_{Th} = \frac{2 \times 1}{2+1} = 0.667\ \Omega.$$

Thevenin's equivalent circuit is then drawn in Fig. 4.90(c).

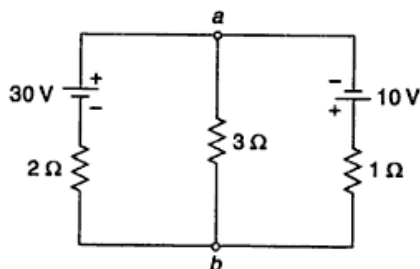


Fig. 4.90 Circuit of Ex. 4.63

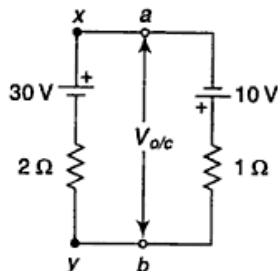


Fig. 4.90(a) Finding of (V_{oc})

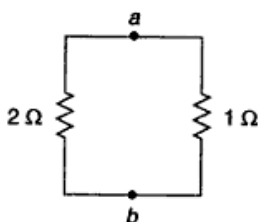


Fig. 4.90(b) Finding of R_{Th}

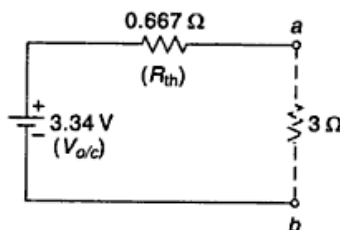


Fig. 4.90(c) Thevenin's equivalent circuit of Ex. 4.63

4.64 Find the current through the $5\ \Omega$ resistor using Thevenin's theorem in Fig. 4.91.

Solution

Removing the $5\ \Omega$ resistor [Fig. 4.91(a)] the current circulating in the loop $abxy$ is

$$I = \frac{20+10}{3+6}\text{ A} = \frac{10}{3}\text{ A}$$

(in the clockwise direction)

Let V_{Th} = voltage across branch xy = voltage across branch ab

$$\text{Here, } V_{xy} = -10 + 6 \times \frac{10}{3} = 10\text{ V} = V_{Th}.$$

$$\left[\text{Otherwise } V_{ab} = 20 - 3 \times \frac{10}{3} = 10\text{ V} = V_{Th}. \right]$$

$$\text{Deactivating all the sources, } R_{Th} = 3 + (6 \parallel 3) = 3 + \frac{6 \times 3}{6+3} = 5\ \Omega.$$

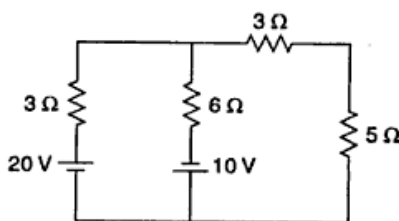


Fig. 4.91 Circuit of Ex. 4.64

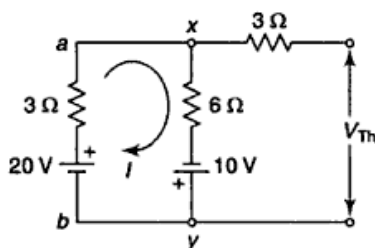
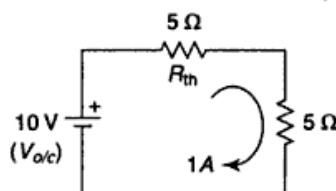
Fig. 4.91(a) Finding of (V_{Th})

Fig. 4.91(b) Thevenin's equivalent circuit of Ex. 4.64

From Fig. 4.91(b) the current through $5\ \Omega$ resistor is $\frac{10}{5+5} = 1\text{ A}$

.....

4.65 Find the Thevenin's equivalent circuit of Fig. 4.92, across R_L .

Solution

R_L is removed and the terminals are open circuited as shown in Fig. 4.92(a). The current supplied by the 24 V source circulates through the $3\ \Omega$ and $6\ \Omega$ resistor only while the current due to the current source circulated through the $4\ \Omega$ only when the circuit is open circuited at a and b .

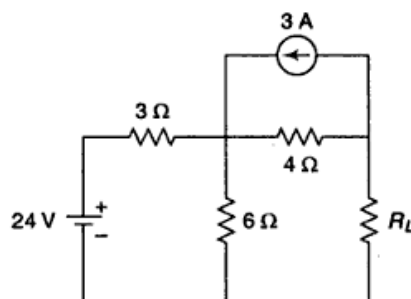
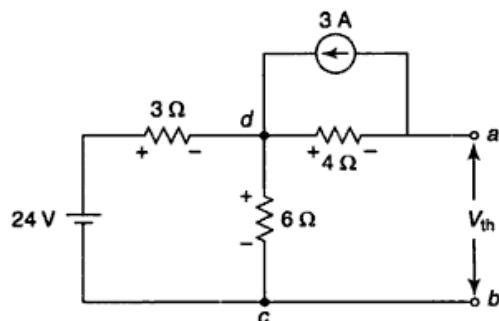


Fig. 4.92 Circuit of Ex. 4.65

Fig. 4.92(a) Finding of (V_{Th})

Voltage across dc is

$$V_{dc} = \frac{24 \times 6}{3+6} \text{ V} = 16 \text{ V}$$

Voltage across da is $V_{da} = 3 \times 4 \text{ V} = 12 \text{ V}$.

Applying KVL in the loop $abcd$

$$V_{ab} = 16 - 12 = 4 \text{ V i.e. } V_{Th} = 4 \text{ V}$$

Next, all the sources in the network is deactivated [Fig. 4.92(b)].

$$\therefore R_{Th} = 4 + \frac{3 \times 6}{3+6} = 6 \ \Omega$$

Thevenin's equivalent circuit is shown in Fig. 4.92c.

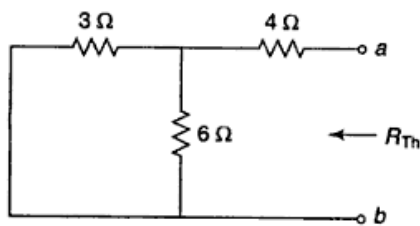
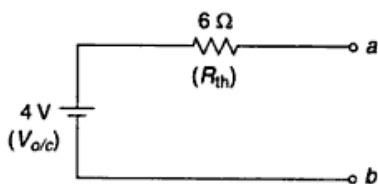
Fig. 4.92(b) Finding of (R_{Th}) 

Fig. 4.92(c) Thevenin's equivalent circuit of Ex. 4.65

4.66 Find the current in the ammeter of the $2\ \Omega$ resistance as shown in Fig. 4.93 using Thevenin's theorem.

Solution

The ammeter is removed and the circuit is shown in Fig. 4.93(a).

The total current delivered by 10 V source is

$$I = \frac{10}{1 + \frac{(10+6) \times (10+5)}{(10+6) + (10+5)}} = \frac{10}{1 + \frac{16 \times 15}{31}} = 1.144\text{ A}$$

$$\therefore I_1 = 1.144 \times \frac{10+5}{15+16} = 0.55\text{ A}$$

$$\text{and } I_2 = 1.144 \times \frac{10+6}{15+16} = 0.59\text{ A.}$$

Voltage across open circuited terminals a and b is

$$V_{Th} = V_{ab} = V_{cb} - V_{ca} = 0.59 \times 10 - 0.55 \times 10 = 0.4\text{ V.}$$

Deactivating the voltage source, the corresponding figure is drawn in Fig. 4.93(b). In this figure using delta star conversion values of R_1 , R_2 and R_3 can be found out.

$$R_1 = \frac{10 \times 6}{10 + 6 + 1} \Omega = \frac{60}{17} \Omega$$

$$R_2 = \frac{6 \times 1}{10 + 6 + 1} \Omega = \frac{6}{17} \Omega$$

$$R_3 = \frac{1 \times 10}{10 + 6 + 1} = \frac{10}{17} \Omega.$$

Resistance between a and b as shown in Fig. 4.93(c) is given by

$$\begin{aligned} R_{Th} &= \frac{60}{17} + \left[\left(\frac{10}{17} + 10 \right) \left(\frac{6}{17} + 5 \right) \right] \\ &= 3.53 + \frac{10.59 \times 5.35}{10.59 + 5.35} \\ &= 7.084\ \Omega \end{aligned}$$

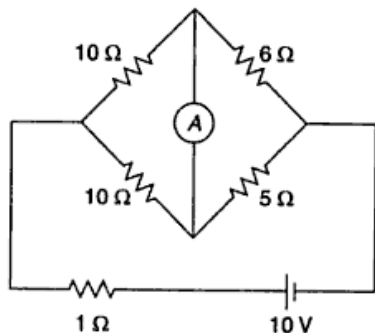
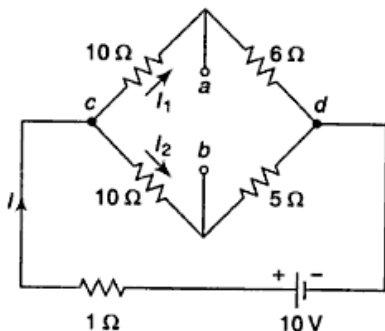
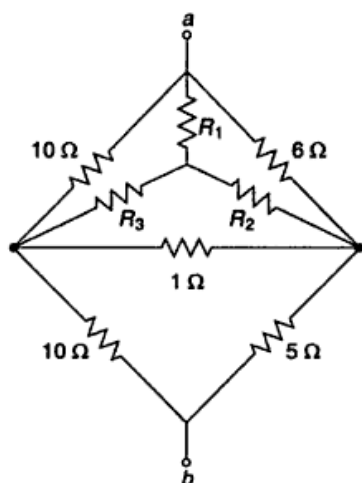
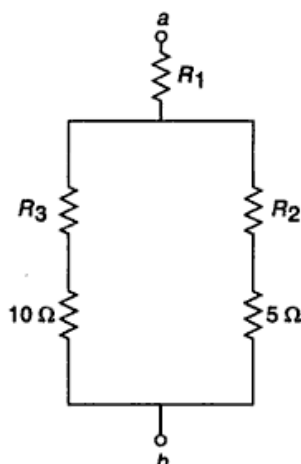


Fig. 4.93 Circuit of Ex. 4.66

Fig. 4.93(a) Finding of (V_{Th})

Fig. 4.93(b) Network reduction to find (R_{Th}) Fig. 4.93(c) Final network reduction to find (R_{Th})

The current through the 2Ω resistor is

$$I_{2\Omega} = \frac{V_{Th}}{R_{Th} + 2} = \frac{0.4}{7.0841 + 2} = 0.044 \text{ A (directed from } a \text{ to } b)$$

.....

4.67 Find the current through the 5Ω resistor in the network of Fig. 4.94 using Thevenin's theorem.

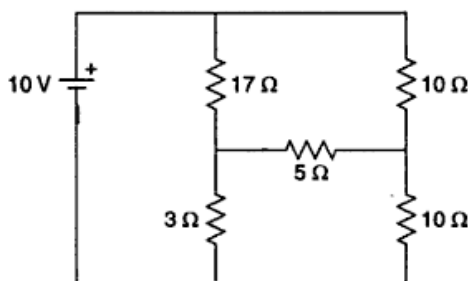


Fig. 4.94 Circuit of Ex. 4.67

Solution

The 5Ω resistor is first removed. The circuit configuration is shown in Fig. 4.94(a).

The current through 17Ω resistor is $\frac{10}{17+3} \text{ A} = 0.5 \text{ A}$.

The current through pair of 10Ω resistors is $\frac{10}{10+10} \text{ A} = 0.5 \text{ A}$.

Voltage across 17Ω resistor is $V_{ca} = 17 \times 0.5 = 8.5 \text{ V}$

Voltage across 10Ω resistor is $V_{cb} = 10 \times 0.5 = 5 \text{ V}$

Hence $V_{ab} = V_{cb} - V_{ca} = 5 - 8.5 = -3.5 \text{ V}$

or $V_{ba} = 3.5 \text{ V}$ (i.e. b is positive terminal)

i.e. $V_{Th} = 3.5 \text{ V}$

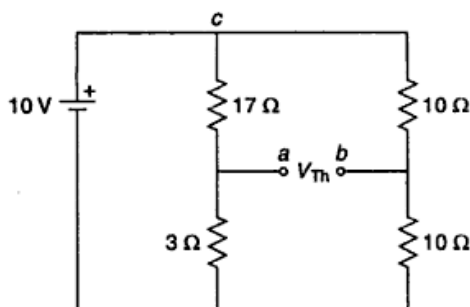


Fig. 4.94(a) Finding of V_{Th}

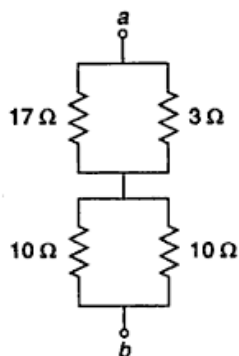


Fig. 4.94(b) Finding of R_{Th}

For finding R_{Th} , the circuit is redrawn in Fig. 4.94(b) deactivating the source;

$$R_{Th} = \frac{17 \times 3}{17 + 3} + \frac{10 \times 10}{10 + 10} = 7.55 \Omega$$

Current through the 5Ω resistor [Fig. 4.94(c)] is obtained as

$$I_{5\Omega} = \frac{V_{Th}}{R_{Th} + 5} = \frac{3.5}{7.55 + 5} \text{ A} = 0.279 \text{ A}$$

(flowing from b to a).

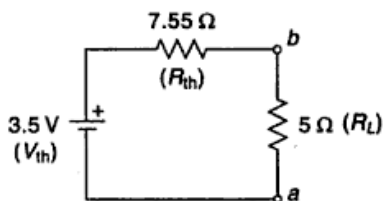


Fig. 4.94(c)

4.68 Find the current in the 5Ω resistor (using Thevenin's theorem) in Fig. 4.95.

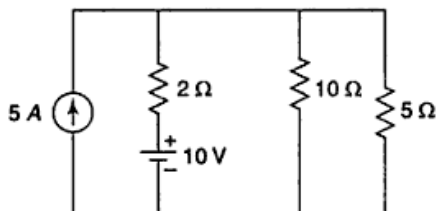


Fig. 4.95 Circuit of Ex. 4.68

Solution

Let us first remove the 5Ω resistor. The circuit configuration is shown in Fig. 4.95(a).

Applying the Superposition theorem, we consider one source at a time. Considering $5A$ source alone and removing the voltage source, the current through the 10Ω resistor is

$$5 \times \frac{2}{2 + 10} = \frac{10}{12} \text{ A.}$$

Considering the voltage source acting alone and removing the current source, the current through the 10Ω resistor is

$$\frac{10}{2 + 10} = \frac{10}{12} \text{ A.}$$

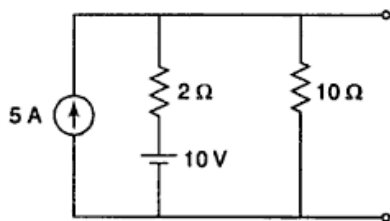


Fig. 4.95(a) Finding of V_{Th} V_{0IC}

Both the currents are directed in the same direction through $10\ \Omega$ resistor. So net current through $10\ \Omega$ resistor is $\frac{10}{12} + \frac{10}{12} = \frac{20}{12}\text{ A}$ and voltage across $10\ \Omega$ resistor is $\frac{20}{12} \times 10 = \frac{200}{12}\text{ V}$.

As $10\ \Omega$ is connected in parallel with the open circuited terminals hence,

V_{Th} = Voltage across $10\ \Omega$ resistor

$$= \frac{200}{12} = \frac{50}{3} = 16.67\text{ V}.$$

Removing all the sources, R_{Th} is found out and is shown in Fig. 4.95(b).

$$R_{Th} = \frac{10 \times 2}{10 + 2} = \frac{20}{12} = \frac{5}{3} = 1.67\ \Omega$$

So the current through the $5\ \Omega$ resistor is obtained as

$$I_{5\Omega} = \frac{V_{Th}}{R_{Th} + R_L} = \frac{16.67}{1.67 + 5} = 2.5\text{ A}$$

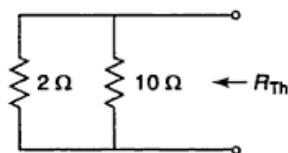


Fig. 4.95(b) Finding of R_{Th}

4.69 Find the power loss in $10\ \Omega$ resistor using Thevenin's theorem (Fig. 4.96).

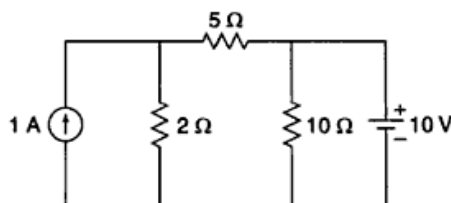


Fig. 4.96 Circuit of Ex. 4.69

Solution

Removing $10\ \Omega$ resistor the circuit configuration is shown in Fig. 4.96(a).

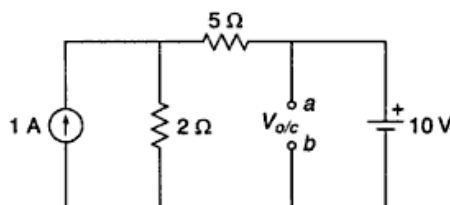


Fig. 4.96(a) Finding of V_{OLC}

As the open circuit voltage (V_{OLC}) across terminals a and b is in parallel with the 10 V source hence the open circuit voltage is becoming 10 V (or $V_{OLC} = V_{Th} = 10\text{ V}$)

Removing all the sources R_{Th} is found out from Fig. 4.96(b). However there is a short circuit path across ab , so $R_{Th} = 0\ \Omega$.

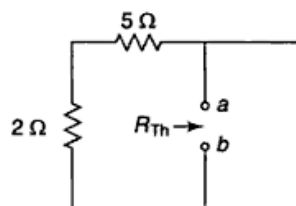


Fig. 4.96(b) Finding of R_{Th}

Current through the $10\ \Omega$ resistor according to Thevenin's theorem is

$$\frac{V_{Th}}{R_{Th} + R_L} = \frac{10}{0 + 10} \text{ A} = 1 \text{ A}$$

Therefore power loss in $10\ \Omega$ resistor is

$$\begin{aligned} I^2 R &= 1^2 \times 10 \text{ W} \\ &= 10 \text{ W.} \end{aligned}$$

.....

4.70 Find Thevenin's equivalent circuit of the network across R_L in Fig. 4.97.

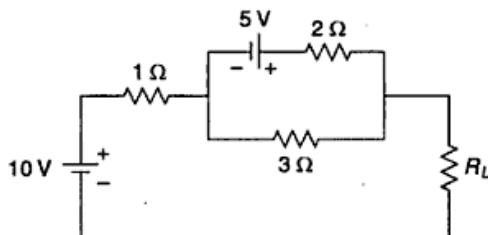


Fig. 4.97 Circuit of Ex. 4.70

Solution

R_L is removed first and the corresponding figure is shown in Fig. 4.97(a). Under this condition 10 V source can not deliver any current. Current due to 5 V source circulates through $2\ \Omega$ and $3\ \Omega$ resistor

$$\therefore I = \frac{5}{2+3} \text{ A} = 1 \text{ A}$$

Voltage across $3\ \Omega$ resistor is $3 \times 1 \text{ V} = 3 \text{ V}$

Applying KVL in loop $a b c d e f a$ of Fig. 4.97(a)

$$V_{ab} = 10 + 3 = 13 \text{ V}$$

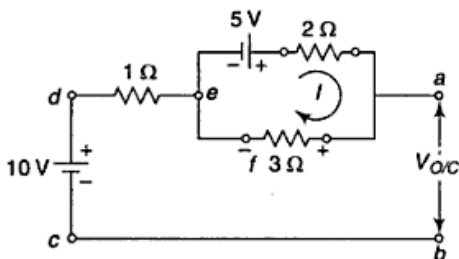


Fig. 4.97(a) Finding of V_{OC}

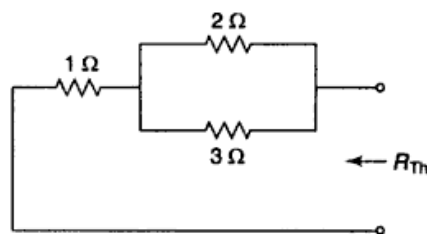


Fig. 4.97(b) Finding of R_{Th}

Deactivating the sources R_{Th} is found out [Fig. 4.97(b)].

$$\begin{aligned} \therefore R_{Th} &= 1 + \frac{3 \times 2}{3+2} \\ &= 2.2\ \Omega \end{aligned}$$

Thevenin's equivalent circuit is shown in Fig. 4.97(c).

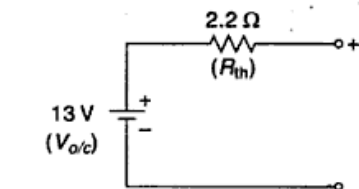


Fig. 4.97(c) Thevenin's equivalent circuit of Ex. 4.70

.....

4.13 NORTON'S THEOREM

According to this theorem, any two-terminal active network containing voltage sources and resistances when viewed from its output terminals is equivalent to a constant current source and an internal (parallel) resistance. The constant current source (known as Norton's equivalent current source) is of the magnitude of the short circuit current at the terminals. The internal resistance is the equivalent resistance of the network looking back into the terminals with all the sources replaced by their internal resistances.

A network is shown in Fig. 4.98 to explain Norton's theorem. Let us find out the current through R_L using Norton's theorem. The steps are as follows:

Step I

Remove (R_L) and short circuit the terminals a and b [Fig. 4.98(a)]. The current through the short circuited path is $I_{sc} = E/R_1 (= I_N)$, where I_N is the Norton's equivalent current.

Step II

For finding internal resistance R_i of the network, terminals a and b is open circuited and the source is deactivated [Fig. 4.98(b)].

$R_i = \frac{R_1 R_2}{R_1 + R_2} (= R_N)$, where R_N is called the Norton's equivalent resistance.

Step III

Norton's equivalent circuit is shown in Fig. 4.98(c). It contains Norton's current source I_N and a parallel resistance equal to internal resistance of the circuit R_i .

Step IV

Connect R_L across terminals a and b and find current I_L through R_L

$$I_L = I_N \times \frac{R_N}{R_N + R_L} \quad (4.41)$$

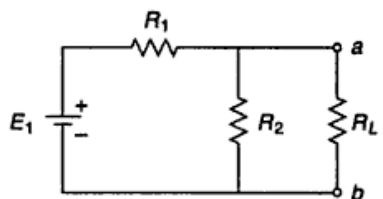


Fig. 4.98 Circuit to explain Norton's theorem

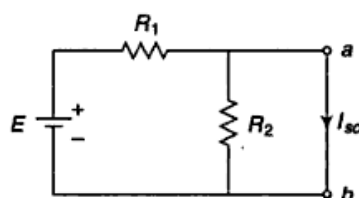


Fig. 4.98(a) Developing Norton's current source

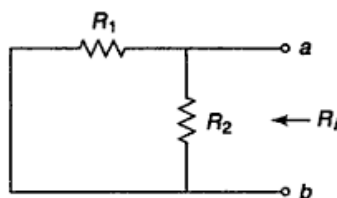


Fig. 4.98(b) Finding of internal resistance

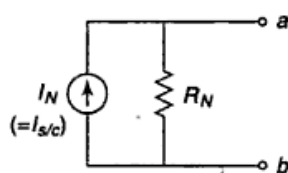


Fig. 4.98(c) Norton's equivalent circuit

4.13.1 Nortonizing Procedure

1. Calculate the short-circuit current I_N at the network terminals.
2. Redraw the network with each source replaced by its internal resistance.

- Calculate the resistance R_N of the redrawn network as seen from the output terminals.
- Draw Norton's equivalent circuit.

4.71 Find the current through R_L in Fig. 4.99 using Norton's theorem.

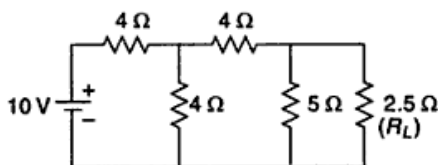


Fig. 4.99 Circuit of Ex. 4.71

Solution

R_L is removed and the terminals are short circuited as shown in Fig. 4.99(a). The short circuit current is

$$I_{sc} = \frac{10}{4 + \frac{4 \times 4}{4 + 4}} = \frac{10}{4 + 2} = 1.67 \text{ A}$$

\therefore Norton's equivalent current $I_N = 1.67 \text{ A}$

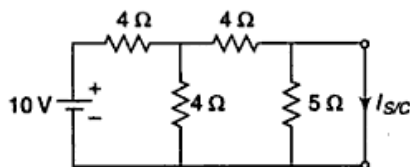


Fig. 4.99(a) Finding of I_{sc}

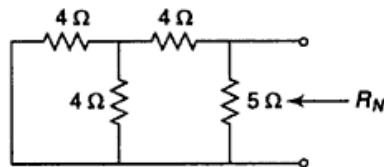


Fig. 4.99(b) Finding of internal resistance R_N

Norton's equivalent resistance R_N is found from Fig. 4.99(b).

$$R_N = \left(\frac{4 \times 4}{4 + 4} + 4 \right) \parallel 5 = \frac{6 \times 5}{6 + 5} = 2.73 \Omega.$$

Norton's equivalent circuit is drawn in Fig. 4.99(c).

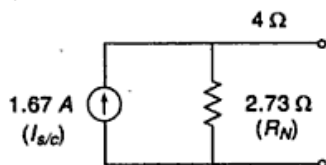


Fig. 4.99(c) Norton's equivalent circuit

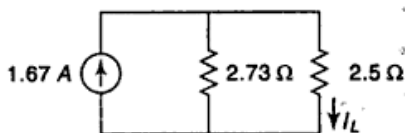


Fig. 4.99(d) Finding of I_L

Replacing R_L across the open circuited terminals as shown in Fig. 4.99(d), the current through R_L is

$$I_L = 1.67 \times \frac{2.73}{2.73 + 2.5} = 0.87 \text{ A}$$

4.72 Find the current through $10\ \Omega$ resistor in Fig. 4.100 using Norton's theorem.

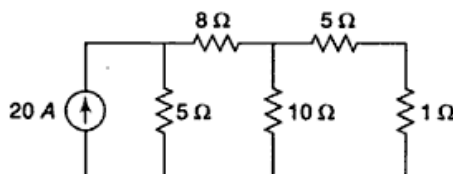


Fig. 4.100 Circuit of Ex. 4.100

Solution

The $10\ \Omega$ resistor is removed and the terminals are short circuited as shown in Fig. 4.100(a).

The current through the short circuited path is

$$I_{sc} = 20 \times \frac{5}{5+8} \text{ A} = 7.69 \text{ A}$$

Hence Norton's equivalent current $I_N = 7.69 \text{ A}$

Norton's equivalent resistance as seen from the open circuited terminals of the network (Fig. 4.100(b)), is obtained as

$$R_N = (8+5) \parallel (5+1) = \frac{13 \times 6}{13+6} \ \Omega = 4.1 \ \Omega$$

Norton's equivalent circuit is shown in Fig. 4.100(c).

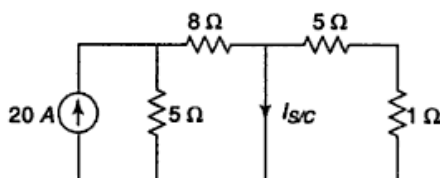


Fig. 4.100(a) Finding of I_{sc}

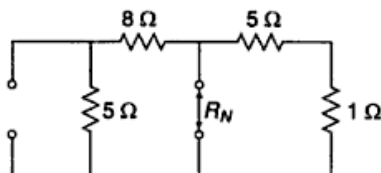


Fig. 4.100(b) Finding of R_N

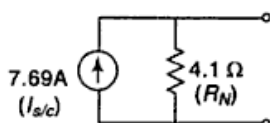


Fig. 4.100(c) Norton's equivalent circuit of Ex. 4.72

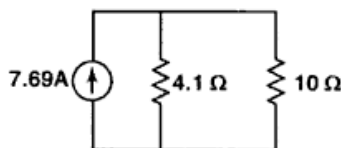


Fig. 4.100(d) Current I_L through the $10\ \Omega$ resistor

Therefore the current through the $10\ \Omega$ resistor is [Fig. 4.100(d)]

$$I_L = 7.69 \times \frac{4.1}{4.1+10} \text{ A} = 2.236 \text{ A}$$

.....

4.73 Find current in $6\ \Omega$ resistor using Norton's theorem for the network shown in Fig. 4.101.

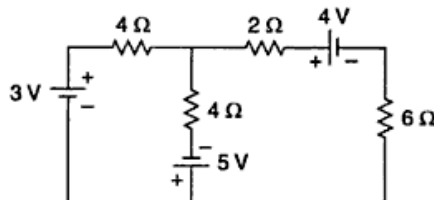


Fig. 4.101 Circuit of Ex. 4.73

Solution

The load resistance $6\ \Omega$ is short-circuited as shown in Fig. 4.101(a).

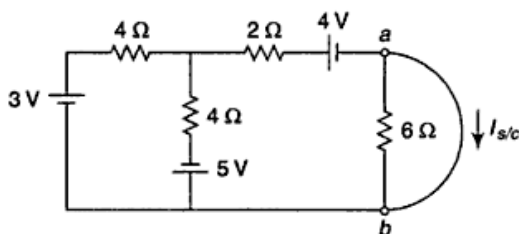


Fig. 4.101(a) Determination of I_{sc}

The current through the short circuited path ab due to the 3 V source acting alone is

$$I_{sc_1} = \frac{3}{4 + \frac{2 \times 4}{2 + 4}} \times \frac{4}{4 + 2} = 0.375\text{ A (from a to b)}.$$

The current through the short circuited path ab due to the 5 V source acting alone is

$$I_{sc_2} = \frac{5}{4 + \frac{4 \times 2}{2 + 4}} \times \frac{4}{4 + 2} = \frac{5 \times 4}{24 + 8} = 0.625\text{ A (from b to a)}.$$

The current through the short circuited path ab due to the 4 V source acting alone is

$$I_{sc_3} = \frac{4}{2 + \frac{4 \times 4}{4 + 4}} = 1\text{ A (from b to a)}.$$

Applying the superposition theorem when all the sources are acting simultaneously the short circuit current is obtained as

$$I_{sc} = (1 + 0.625 - 0.375)\text{ A} = 1.25\text{ A (from b to a)}$$

Hence Norton's equivalent current is $I_N = 1.25\text{ A}$.

Norton's equivalent resistance [Fig. 4.101(b)] is obtained as

$$R_N = 2 + \frac{4 \times 4}{4 + 4} = 4\ \Omega$$

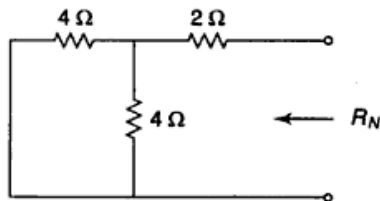


Fig. 4.101(b) Finding of R_N

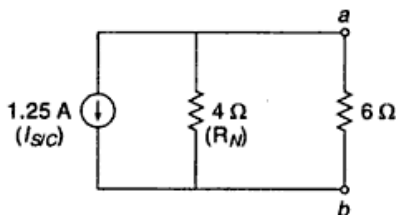


Fig. 4.101(c) Norton's equivalent circuit

The current through $6\ \Omega$ resistor is $I = 1.25 \times \frac{4}{4 + 6} = 0.5\text{ A (from b to a)}$.

.....

4.74 Find current through $5\ \Omega$ resistor in the circuit of Fig 4.102 using Norton's theorem.

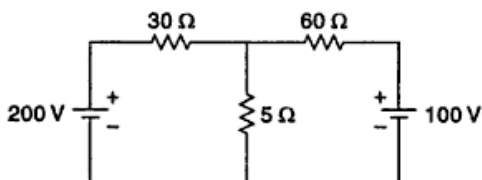


Fig. 4.102 Circuit of Ex. 4.74

Solution

$5\ \Omega$ resistor is short circuited as shown in Fig. 4.102(a). The current through the short-

circuited path $I_{sc} = \frac{200}{30} + \frac{100}{60} = 8.33\text{ A}$ from a to b .

Hence $I_N = 8.33\text{ A}$

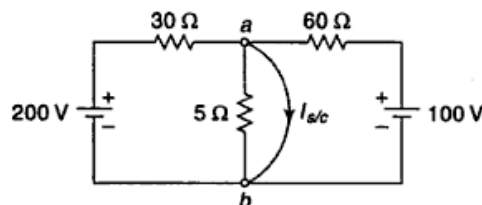


Fig. 4.102(a) Determination of (I_{sc})

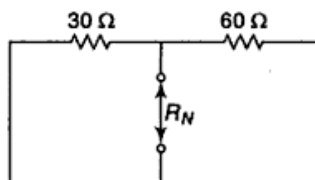


Fig. 4.102(b) Determination of (R_N)

The Norton's equivalent resistance is obtained by removing all sources and looking from open circuited terminals a and b in Fig. 4.102(b) as

$$R_N = \frac{30 \times 60}{30 + 60} = 20\ \Omega$$

Therefore, current through the $5\ \Omega$ resistor [Fig. 4.102(c)] is $I = 8.33 \times \frac{20}{20 + 5} = 6.664\text{ A}$ from a to b .

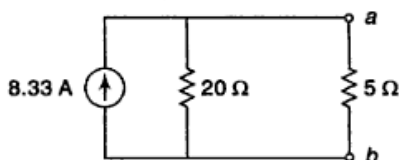


Fig. 4.102(c) Norton's equivalent circuit of Ex. 4.74

4.75 Find the current through R_L in Fig. 4.103 using Norton's theorem.

Solution

Removing R_L and short circuiting its terminals the network is redrawn in Fig. 4.103(a).

The current through the short circuited path is obtained as

$$\begin{aligned} I_{sc} &= \frac{1}{2} - \frac{2}{1} - \frac{1}{1} = 0.5 - 2 - 1 \\ &= -2.5\text{ A from } a \text{ to } b \text{ or } 2.5\text{ A} \\ &\quad \text{from } b \text{ to } a \end{aligned}$$

i.e. $I_N = 2.5\text{ A}$.

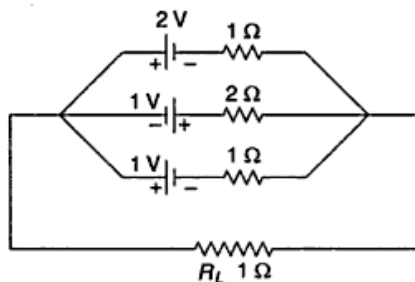
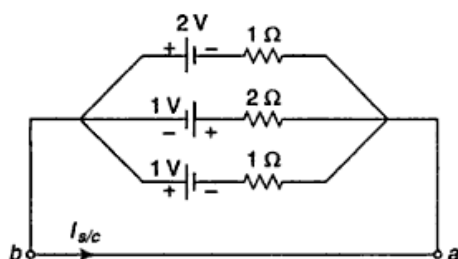


Fig. 4.103 Circuit of Ex. 4.75

Fig. 4.103(a) Determination of I_{SC}

Removing the sources and open circuiting the short circuited path [as shown in Fig. 4.103(b)], we get

$$R_N = \frac{1 \times 2 \times 1}{1 \times 2 + 2 \times 1 + 1 \times 1} \Omega = 0.4 \Omega$$

The current through R_L [Fig 4.103(c)] is (I)

$$= 2.5 \times \frac{0.4}{1 + 0.4} \text{ A} = 0.714 \text{ A from } b \text{ to } a.$$

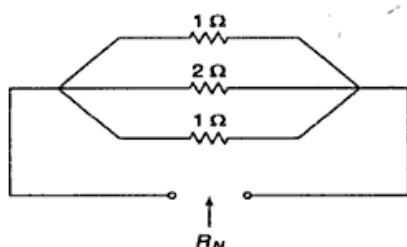
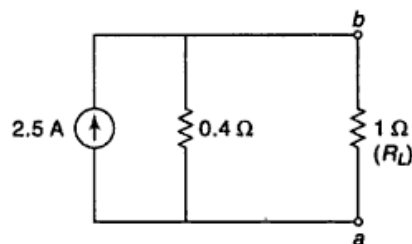
Fig. 4.103(b) Determination of R_N 

Fig. 4.103(c) Norton's equivalent circuit of Ex. 4.75

4.76 Find current through the 20Ω resistor in Fig. 4.104 using Norton's theorem.

Solution

Short circuiting 20Ω resistor [Fig. 4.104(a)] the current through the short circuited path due to 20 A source acting alone is $I_{sc1} = 20 \text{ A}$ from a to b .

Considering the 40 V source acting alone the current through the short circuited path is

$$I_{sc2} = \frac{40}{10} \text{ A} = 4 \text{ A (from } a \text{ to } b).$$

Considering the 80 V source acting alone the current through the short circuited path $I_{sc3} = \frac{80}{10} \text{ A}$

$$= 8 \text{ A (from } b \text{ to } a).$$

Applying the Superposition theorem the net current through the short circuited path $I_{sc} = (20 + 4 - 8) \text{ A} = 16 \text{ A (from } a \text{ to } b).$

Thus, Norton's equivalent current is $I_N = 16 \text{ A}$. Next, removing all the sources, R_N is found out from Fig. 4.104(b) as $R_N = 10 \Omega$.

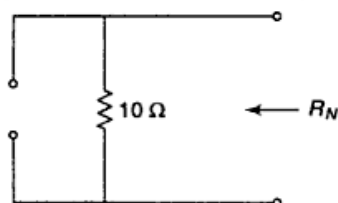
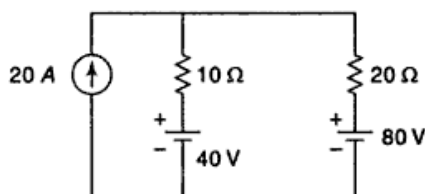
Fig. 4.104(b) Determination of (R_N)

Fig. 4.104 Circuit of Ex. 4.76

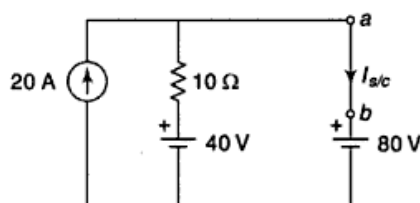
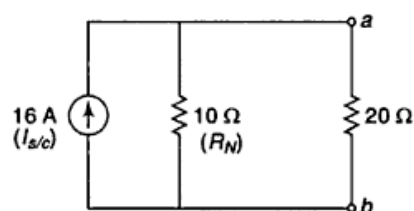
Fig. 4.104(a) Determination of (I_{SC})

Fig. 4.104(c) Norton's equivalent circuit of Ex. 4.76

From Fig. 4.104(c) the current through the $20\ \Omega$ resistor can be found out as

$$I = 16 \times \frac{10}{10 + 20} \text{ A} = 5.33 \text{ A (from } a \text{ to } b).$$

4.77 Find the current through the $2\ \Omega$ resistor in Fig. 4.105 using Norton's theorem.

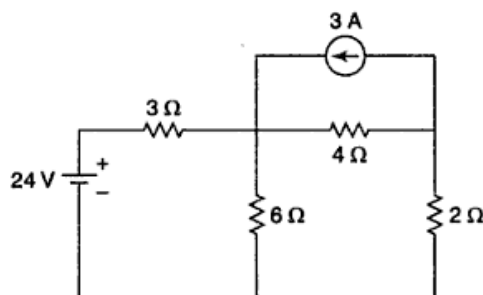


Fig. 4.105 Circuit of Ex. 4.77

Solution

Short circuiting the $2\ \Omega$ resistor [as shown in Fig. 4.105(a)], and with 25 V source acting

alone, the short circuit current through ab is $I_{sc1} = \frac{24}{3 + \frac{6 \times 4}{6 + 4}} \times \frac{6}{6 + 4} = 2.67 \text{ A from } a \text{ to } b.$

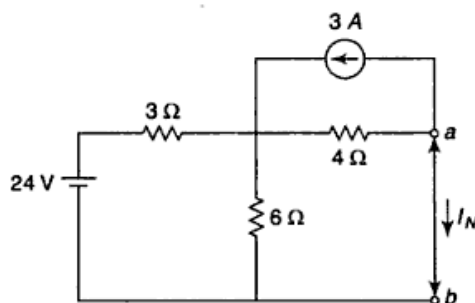


Fig. 4.105(a) Determination of I_N

Next with 3 A source acting alone, the current through ab is $I_{sc2} = 3 \times \frac{4}{4 + \frac{3 \times 6}{3 + 6}} = 2 \text{ A}$

from b to a .

\therefore the current through ab is

$$I_N = I_{sc1} - I_{sc2} = 2.67 \text{ A} - 2 \text{ A} = 0.67 \text{ A from } a \text{ to } b.$$

Norton's equivalent resistance [Fig. 4.105(b)] is

$$R_N = 4 + \frac{3 \times 6}{3 + 6} = 6\ \Omega$$

The current through the $2\ \Omega$ resistor [Fig. 4.105(c)] is $I = 0.67 \times \frac{6}{6 + 2} = 0.5 \text{ A from } a \text{ to } b.$

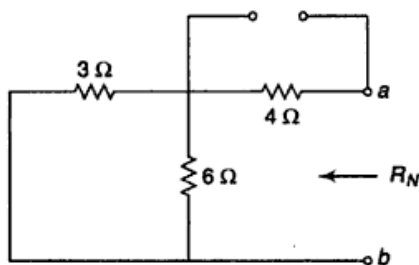
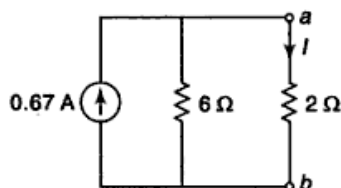
Fig. 4.105(b) Determination of R_N 

Fig. 4.105(c) Norton's equivalent circuit

4.78 Find Norton's equivalent circuit for the network shown in Fig. 4.106.

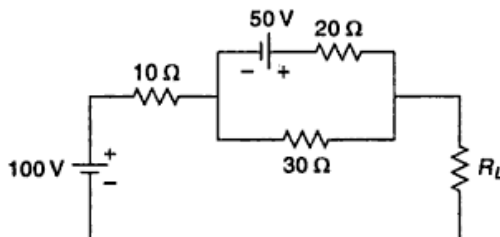
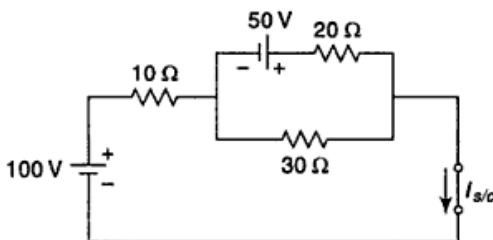


Fig. 4.106 Circuit of Ex. 4.78

Solution

Remove R_L and short circuit the terminals [as shown in Fig. 4.106(a)].

Fig. 4.106(a) Determination of I_{sc}

The short circuit current is

$$\begin{aligned}
 I_{sc} &= \frac{100}{10 + \frac{20 \times 30}{20 + 30}} + \frac{50}{20 + \frac{30 \times 10}{30 + 10}} \times \frac{30}{30 + 10} \\
 &= \frac{100}{10 + 12} + \frac{50 \times 30}{800 + 300} \\
 &= 5.9 \text{ A from } a \text{ to } b \text{ i.e. } I_N = 5.9 \text{ A.}
 \end{aligned}$$

Norton's equivalent resistance looking back from the open circuited terminals

[Fig. 4.106(b)] is $(R_N) = 10 + \frac{20 \times 30}{20 + 30} = 22 \Omega$.

Norton's equivalent circuit is shown in Fig. 4.106(c).

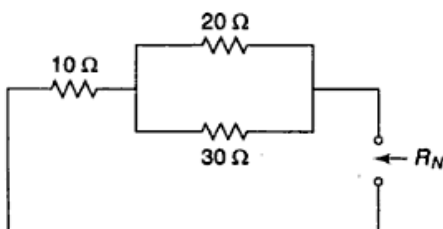
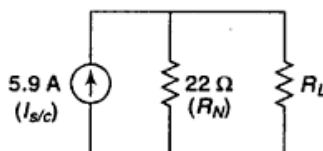
Fig. 4.106(b) Finding of R_N 

Fig. 4.106(c) Norton's equivalent circuit of Ex. 4.78

4.79 Find the current through the $1\ \Omega$ resistor in the network shown in Fig. 4.107 using Norton's theorem.

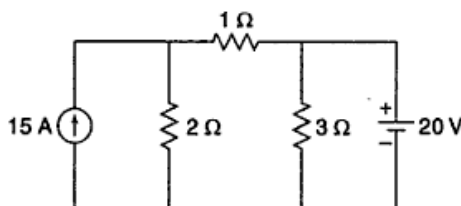
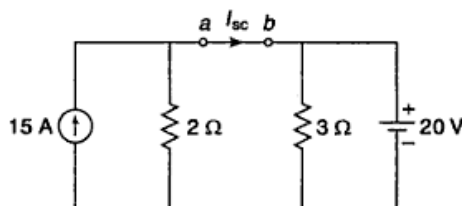


Fig. 4.107 Circuit of Ex. 4.79

Solution

$1\ \Omega$ resistor is removed and terminals are short circuited as shown in Fig. 4.107(a). The current through the short circuited path is

$$\begin{aligned}
 I_{sc} &= 15 - \frac{20}{\frac{2 \times 3}{2+3}} \times \frac{3}{3+2} \\
 &= 15 - \frac{20 \times 3}{6} \\
 &= 5\text{ A (from } a \text{ to } b)
 \end{aligned}$$

Fig. 4.107(a) Determination of I_{sc}

Removing all the sources and open circuiting terminals a and b [Fig. 4.107(b)], $R_N = 2\ \Omega$

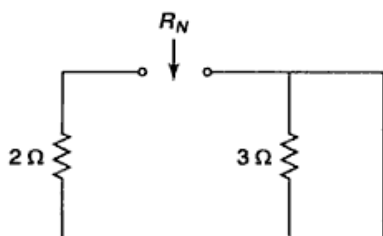
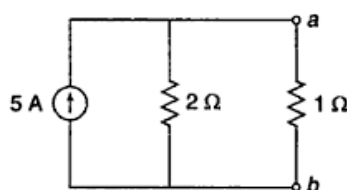
Fig. 4.107(b) Determination of R_N 

Fig. 4.107(c) Norton's equivalent circuit

Thus the current through $1\ \Omega$ resistor [Fig. 4.107(c)] is

$$I = 5 \times \frac{2}{2+1}\text{ A} = 3.33\text{ A}$$

4.80 Find the current through $8\ \Omega$ resistor using Norton's theorem in the network of Fig 4.108.

Solution

Short circuiting the $8\ \Omega$ resistor as shown in Fig. 4.108(a), the current through the short circuited path is $I_N = \frac{100}{20} - \frac{30}{10} = 2\text{ A}$ (from a to b).

Open circuiting ab and removing the sources the Norton's equivalent resistance [Fig. 4.108(b)] is

$$R_N = \frac{20 \times 10}{20 + 10} \Omega = 6.67\ \Omega$$

The current through the $8\ \Omega$ resistor [from Fig. 4.108(c)] is $(I) = 2 \times \frac{6.67}{6.67 + 8} = 0.9\text{ A}$.

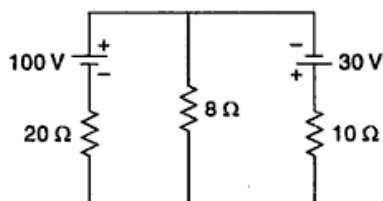


Fig. 4.108 Circuit of Ex. 4.80

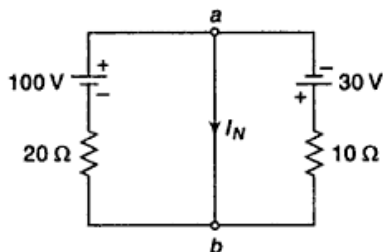


Fig. 4.108(a) Determination of I_N

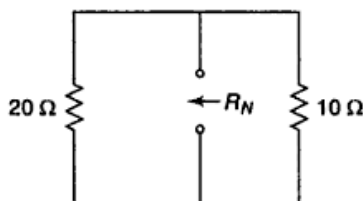


Fig. 4.108(b) Determination of R_N

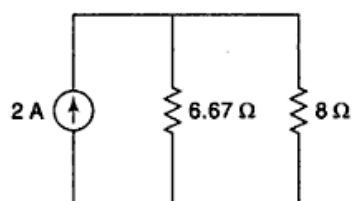


Fig. 4.108(c) Norton's equivalent circuit of Ex. 4.80

4.81 Find the current through the $20\ \Omega$ resistor in Fig. 4.109 using Norton's theorem.

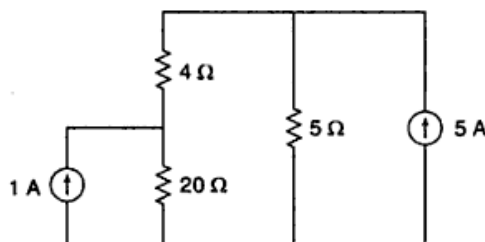




Fig. 4.109 Circuit of Ex. 4.81

Solution

The $20\ \Omega$ resistor is short circuited and the circuit is redrawn in Fig. 4.109(a). The current through the short-circuited path due to 1 A current source only is $I_{sc1} = 1\text{ A}$ (from a to b).

The current through the short-circuited path due to 5 A source only is $I_{sc2} = 5 \times \frac{5}{5+4}\text{ A} = \frac{25}{9}\text{ A}$ (from a to b). Norton's equivalent current is then

$$I_N (= I_{sc}) = I_{sc1} + I_{sc2} = 1 + \frac{25}{9} = 3.78\text{ A}.$$

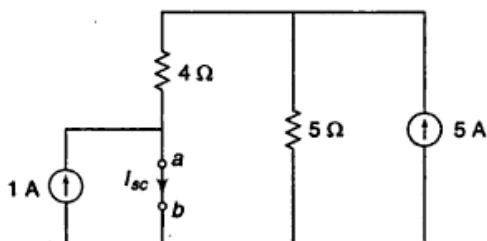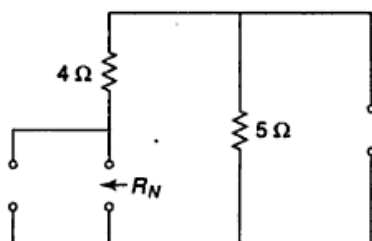Fig. 4.109(a) Determination of I_{sc} Fig. 4.109(b) Finding of R_N

Next, removing the sources and open-circuiting terminals a and b [as shown in Fig. 4.109 (b)] R_N is obtained as $(R_N) = 4 + 5 = 9 \Omega$.

The current I through the 20 Ω resistor is obtained from Fig. 4.109(c), where

$$I = 3.78 \times \frac{9}{9 + 20} = 1.173 \text{ A (from } a \text{ to } b)$$

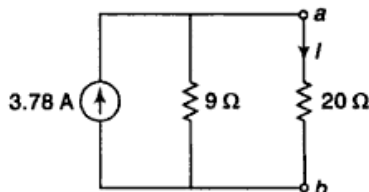


Fig. 4.109(c) Norton's equivalent circuit of Ex. 4.81

4.14 EQUIVALENCE OF THEVENIN'S AND NORTON'S THEOREMS

Figure 4.110 shows the equivalency of Thevenin's and Norton's theorems. It can be proved that the equivalent circuits given by Thevenin's and Norton's theorem yield exactly the same current and same voltage in the load impedance and they are effectively identical to one another. In any particular problem, either theorem can therefore be used. In most cases Thevenin's theorem is the easier to apply, although when the network impedance is high compared with the load impedance, the Norton's theorem concept may simplify calculations.

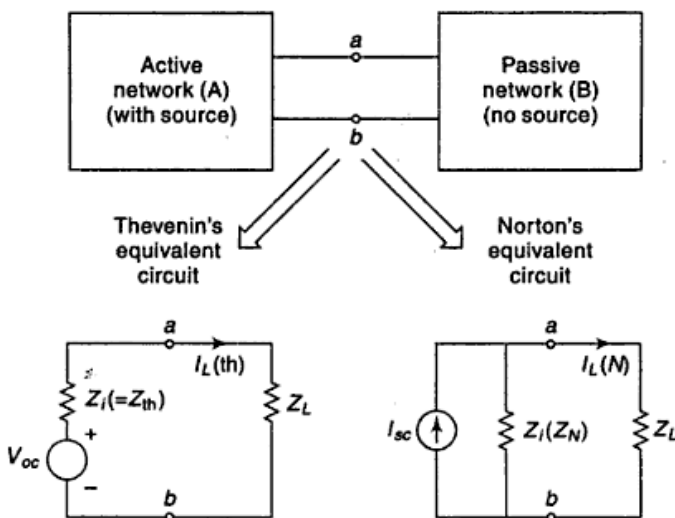


Fig. 4.110 Equivalence of Thevenin's and Norton's circuits

From Fig. 4.110 by applying Thevenin's theorem the load current is given by

$$I_{L(Th)} = \frac{V_{oc}}{Z_i + Z_L} \quad (4.42)$$

where V_{oc} = Open circuit voltage (Thevenin's equivalent voltage source)

Z_i = Thevenin's equivalent impedance (or resistance for dc circuit), and

Z_L = Load impedance of the load network.

On short circuiting the terminals a and b of the Thevenin's equivalent,

$$I_{sc} = \frac{V_{oc}}{Z_i} \quad (4.43)$$

$$\text{or } V_{oc} = I_{sc} \times Z_i \quad (4.44)$$

However from Norton's equivalent circuit [Fig. 4.110(b)], the load current is given by

$$I_{L(N)} = \frac{I_{sc} \times Z_i}{Z_i + Z_L} \quad (4.45)$$

Substituting the equation (4.44) in equation (4.45),

$$I_{L(N)} = \frac{V_{oc}}{Z_i + Z_L} \quad (4.46)$$

Comparing equation (4.42) and equation (4.46)

$$I_{L(Th)} = I_{L(N)} \quad (4.47)$$

Thus for any passive network, being connected to an active network, one can have equivalent representation of Norton's equivalent or Thevenin's equivalent circuit (i.e. both the theorems are equivalent to each other). For easy understanding, a simple example is shown in the circuit of Fig. 4.111(a).

From Fig. 4.111(b) the load current is

$$I_{L(Th)} = \frac{\frac{ER_2}{R_1 + R_2}}{\frac{R_1 R_2}{R_1 + R_2} + R_L} = \frac{ER_2}{R_1 R_2 + R_1 R_L + R_2 R_L} \quad (4.48)$$

\therefore In Fig. 4.111(a), removing R_L the equivalent resistance R_i looking back to the network from $a - b$, is

$$\left\{ \frac{R_1 R_2}{R_1 + R_2} \right\} \text{ and } V_{oc} \text{ is then } \left\{ \left(\frac{E}{R_1 + R_2} \right) \times R_2 \right\}.$$

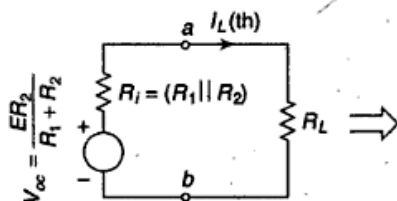


Fig. 4.111(b) Thevenin's equivalent circuit

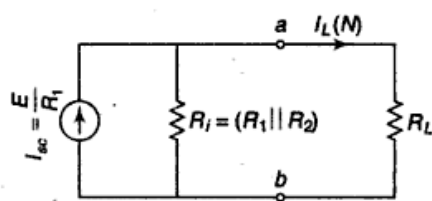


Fig. 4.111(c) Norton's equivalent circuit

On the other hand, from Fig. [4.111(c)] the load current is given by

$$I_{L(N)} = \frac{\frac{E}{R_1} \times \frac{R_1 R_2}{R_1 + R_2}}{\frac{R_1 R_2}{R_1 + R_2} + R_L} = \frac{\frac{ER_2}{R_1 + R_2}}{\frac{R_1 R_2 + R_1 R_L + R_2 R_L}{R_1 + R_2}}$$

$$= \frac{ER_2}{R_1 R_2 + R_1 R_L + R_2 R_L}$$

[\because Removing R_2 from $a-b$ terminal and applying short circuit at $a-b$, current through the terminals $a-b$ is (I_{sc}) i.e. $\left(\frac{E}{R_1}\right)$ while the internal resistance of the

network is $\left\{R_i = \frac{R_1 R_2}{R_1 + R_2}\right\}$]

$$\therefore I_{L(Th)} = I_{L(N)} = \frac{ER_2}{R_1 R_2 + R_1 R_L + R_2 R_L} \quad (4.49)$$

4.15 MAXIMUM POWER TRANSFER THEOREM

As applied to dc networks this theorem may be stated as follows: *A resistive load abstracts maximum power from a network when the load resistance equals the internal resistance of the network as viewed from the output terminals, with all energy sources removed, leaving behind their internal resistances.*

This theorem is applicable to all branches of electrical engineering including analysis of communication networks. However the overall efficiency of a network supplying maximum power to any branch is only 50%; hence application of this theorem to power transmission and distribution networks is limited because in that case, the final target is high efficiency and not maximum power transfer. But in electronics and communication network as the purpose is to receive or transmit maximum power, even at low efficiency, the problem of maximum power transfer is of crucial importance in the operation of communication lines and antennas.

Illustration

Figure 4.112 shows a simple resistive network in which a load resistance R_L is connected across terminals a and b of the network. The network consists of a generator emf(E) and internal resistance r along with a series resistance R . The internal resistance of the network as viewed from the terminals a and b is (R_i) = $r + R$.

According to maximum power transfer theorem R_L will abstract maximum power from the network when

$$R_i = R_L \text{ or } R_L = (r + R).$$

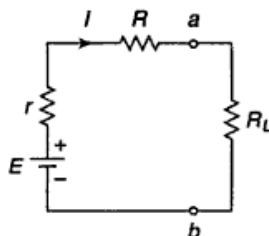


Fig. 4.112 Circuit for illustrating maximum power transfer theorem

4.15.1 Proof of Maximum Power Transfer Theorem

Let us assume that current I flows through R_L in the circuit shown in Fig. 4.112.

Obviously, $I = \frac{E}{R_i + R_L}$.

$$\text{Power across the load } (P_L) = I^2 R_L = \frac{E^2}{(R_i + R_L)^2} \cdot R_L = \frac{E^2 R_L}{(R_i + R_L)^2} \quad (4.50)$$

For P_L to be maximum,

$$\frac{dP_L}{dR_L} = 0$$

Differentiating Eq. (4.50),

$$\frac{dP_L}{dR_L} = E^2 \left[\frac{(R_i + R_L)^2 - 2R_L(R_i + R_L)}{(R_i + R_L)^4} \right] = 0$$

$$\text{or } R_i + R_L = 2R_L$$

$$\text{or } R_L = R_i = r + R$$

Thus for maximum power transfer, $R_L = R_i$.

$$\text{The maximum power is } (P_{L\max}) = I^2 R_L = \frac{E^2}{(R_L + R_L)^2} \times R_L = \frac{E^2}{4R_L}$$

$$\text{The power delivered by the source is } (EI) = \frac{E^2}{(R_L + R_L)} = \frac{E^2}{2R_L}.$$

So the efficiency under maximum power transfer condition is $\frac{E^2 / 4 R_L}{E^2 / 2 R_L} = \frac{1}{2}$

(or 50%).

4.82 Calculate the value of R_L which will abstract maximum power from the circuit shown in Fig. 4.113 Also find the maximum power.

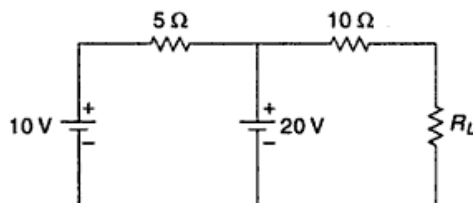


Fig. 4.113 Circuit of Ex. 4.82

Solution

Removing all the sources and open circuiting the terminals of R_L [Fig 4.113(a)] the internal resistance R_i of the network is found out as 10Ω .

$$\text{i.e., } R_i = 10 \Omega$$

\therefore For maximum power transfer

$$R_L = R_i = 10 \Omega$$

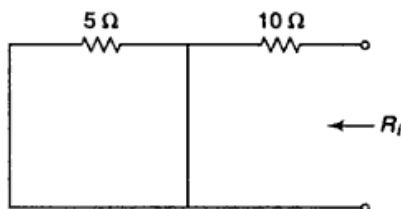


Fig. 4.113(a) Determination of (R_i)

Again for $R_L = 10 \Omega$, the total current through R_L due to both sources is given by

$$I = \frac{20}{\frac{5 \times (10+10)}{5+10+10}} \times \frac{5}{5+10+10} = 1 \text{ A}$$

[The current due to 10 V source circulates through 5Ω resistor and 20 V source only]

The maximum power across load is

$$I^2 R_L = (1)^2 \times 10 = 10 \text{ W}$$

4.83 Calculate the value of R_L which will absorb maximum power from the circuit shown in Fig. 4.114. Also calculate the value of this maximum power.

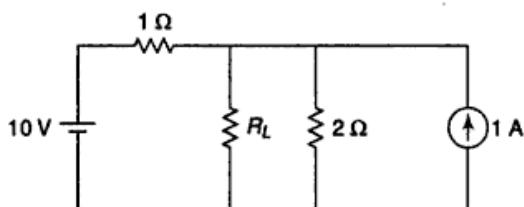


Fig. 4.114 Circuit of Ex. 4.83

Solution

Let R be removed and internal resistance of the network is calculated looking from the open circuited terminals after removing all the sources as shown in Fig. 4.114(a).

Here
$$R_i = \frac{1 \times 2}{1+2} \Omega = \frac{2}{3} \Omega$$

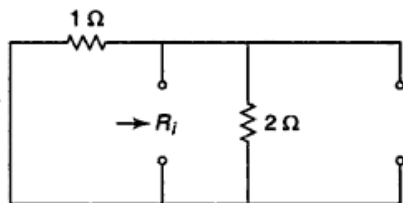


Fig. 4.114(a) Determination of (R_i)

i.e.
$$R = R_i = \frac{2}{3} \Omega = 0.667 \Omega \text{ [for maximum power transfer]}$$

The current through R due to both the sources acting simultaneously is given by

$$I = \frac{10}{1 + \frac{0.667 \times 2}{0.667 + 2}} \times \frac{2}{2 + 0.667} + 1 \times \frac{\frac{2 \times 1}{2+1}}{0.667 + \frac{2 \times 1}{2+1}}$$

$$= 4.998 + 0.5 = 5.5 \text{ A}$$

The value of the maximum power is $(5.5)^2 \times 0.667 \text{ W} = 20 \text{ W}$.

4.84 Obtain the maximum power transferred to R_L in the circuit of Fig. 4.115 and also the value of R_L .

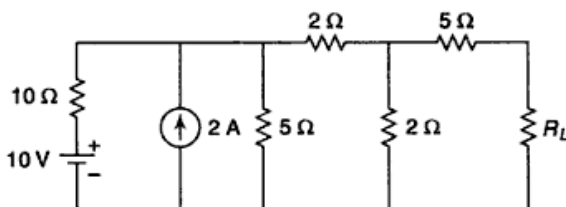



Fig. 4.115 Circuit of Ex. 4.84

Solution

R_L is removed and its terminals are open circuited. Deactivating the sources the internal resistance R_i of the network can be found out from Fig. 4.115(a).


$$R_i = \left[\left(\frac{10 \times 5}{10 + 5} + 2 \right) \parallel 2 \right] + 5 = 6.45 \, \Omega$$

Thus, according to the maximum power transfer theorem the value of R_L is $6.45 \, \Omega$ for maximum power transfer.

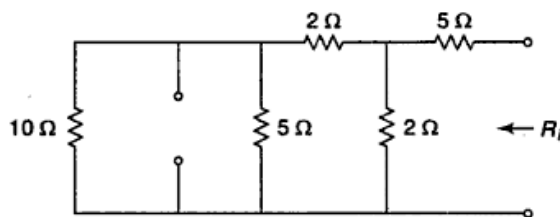Fig. 4.115(a) Finding of (R_i)

Next, considering the 10 V source acting alone in the network the total current supplied by the 10 V source [Fig. 4.115(b)] is

$$I = \frac{10}{10 + \frac{5 \times 3.7}{5 + 3.7}} = 0.82 \, \text{A.}$$

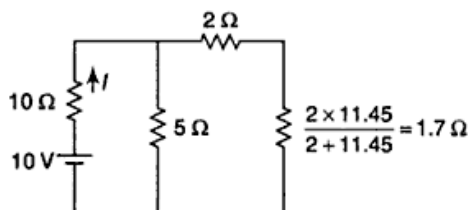
Fig. 4.115(b) Current (I) for 10 V source only

\therefore Current through R_L due to the 10 V source only is

$$I_1 = 0.82 \times \frac{5}{5 + 2 + 1.7} \times \frac{2}{2 + 5 + 6.45} = 0.07 \, \text{A.}$$

Again considering the 2 A source acting alone, the current through the $2 \, \Omega$ resistor is

$$I' = 2 \times \frac{10}{10 + \frac{5 \times 3.7}{5 + 3.7}} \times \frac{5}{5 + 2 + 1.7} \, \text{A} = 0.4739 \, \text{A}$$

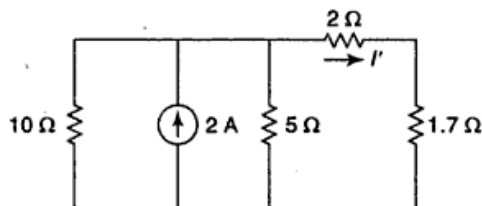Fig. 4.115(c) Determination of current through $2 \, \Omega$ resistor for 2 A source only

Hence the current due to the 2 A current source through R_L is

$$I_2 = 0.4739 \times \frac{2}{2+5+6.45} \text{ A} = 0.07 \text{ A}$$

Applying the superposition theorem current through R_L (when both the sources are acting simultaneously) is

$$I = I_1 + I_2 = 0.07 + 0.07 = 0.14 \text{ A}$$

∴ Maximum power transferred across R_L is

$$P^2 R_L = (0.14)^2 \times 6.45 = 0.126 \text{ W.}$$

.....

4.85 Find the value of R in the circuit of Fig. 4.116 such that maximum power transfer takes place. What is the amount of this power?

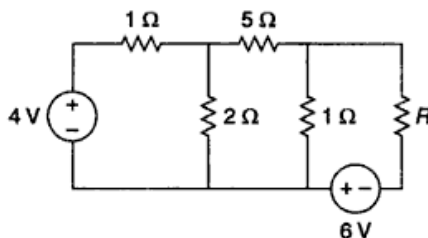


Fig. 4.116 Circuit of Ex. 4.85

Solution

Deactivating all the sources, internal resistance R_i of the network is found out as shown in Fig. 4.116(a).

$$\begin{aligned} R_i &= \left(\frac{2 \times 1}{2+1} + 5 \right) \parallel 1 \\ &= \frac{5.67 \times 1}{5.67+1} = 0.85 \Omega \end{aligned}$$

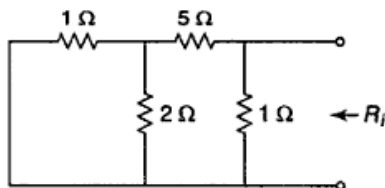


Fig. 4.116(a) Determination of (R_i)

According to the maximum power transfer theorem the maximum power takes place across R when $R = R_i = 0.85 \Omega$.

The current through R due to the 4 V source acting alone is

$$\begin{aligned} I_1 &= \frac{4}{\left[\left(\frac{0.85 \times 1}{0.85+1} + 5 \right) \parallel 2 \right] + 1} \times \frac{2}{2+5+\frac{1 \times 0.85}{1+0.85}} \times \frac{1}{1+0.85} \\ &= \frac{4}{\frac{5.46 \times 2}{5.46+2} + 1} \times \frac{2}{13.8} = 0.235 \text{ A} \end{aligned}$$

The current through (R) due to 6 V source acting alone is

$$I_2 = \frac{6}{\left[\left(\frac{1 \times 2}{1+2} + 5 \right) \parallel 1 \right] + 0.85} = \frac{6}{\frac{5.67 \times 1}{5.67+1} + 0.85} = 3.53 \text{ A}$$

According to superposition, the current through R when both the sources are acting simultaneously is

$$I = I_1 + I_2 = 0.235 + 3.53 = 3.765 \text{ A.}$$

Thus the maximum power is $P^2 R = (3.765)^2 \times 0.85 = 12 \text{ W.}$

.....

4.86 Assuming maximum power transfer from the source to R find the value of this power in the circuit of Fig. 4.117.

Solution

Deactivating the source the internal resistance R_i of the network is found from Fig. 4.117(a);

$$R_i = 5 + \frac{4(1+2+3)}{4+(1+2+3)}$$

$$= 5 + \frac{4 \times 6}{10} = 5 + 2.4 = 7.4 \, \Omega$$

According to the maximum power transfer theorem, the maximum power transfer from the source to R occurs when

$$R = R_i = 7.4 \, \Omega.$$

The current through R due to 10 V source is

$$I = \frac{10}{1+2+3 + \frac{4 \times (5+7.4)}{4+(5+7.4)}} \text{ A} = 1.108 \text{ A}$$

Hence the maximum power transfer from source to R is

$$I^2 R = (1.108)^2 \times 7.4 = 9.08 \text{ W.}$$

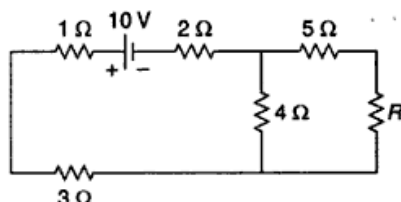


Fig. 4.117 Circuit of Ex. 4.86

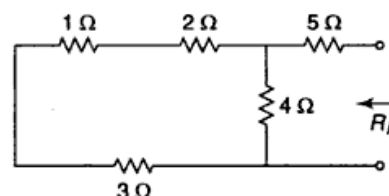


Fig. 4.117(a) Determination of (R_i)

4.87 Find the value of R_L for which the power transfer across R_L is maximum and find the value of this maximum power [Fig. 4.118].

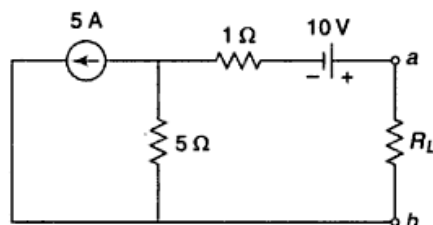


Fig. 4.118 Circuit of Ex. 4.87

Solution

Deactivating the sources the internal resistance of the network is found out looking back from the open circuited terminals of R_L [as shown Fig. 4.118(a)].

$$\therefore R_i = 1 + 5 = 6 \, \Omega.$$

Power transfer across R_L is maximum when

$$R_i = R_L = 6 \, \Omega.$$

The current through (R_L) is

$$I = \frac{10}{6+5+1} - 5 \times \frac{5}{5+1+6} \text{ (from a to b)}$$

$$= -1.25 \text{ A (from a to b) or } 1.25 \text{ A from (b to a)}$$

The value of the maximum power is obtained as

$$I^2 R_L = (1.25)^2 \times 6 = 9.375 \text{ W.}$$

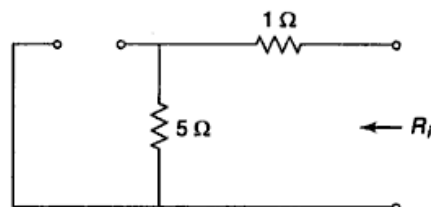


Fig. 4.118(a) Determination of (R_i)

■ **ADDITIONAL EXAMPLES** ■

4.88 In the network shown in Fig. 4.119 determine all branch currents and the voltage across the $5\ \Omega$ resistor by loop current analysis.

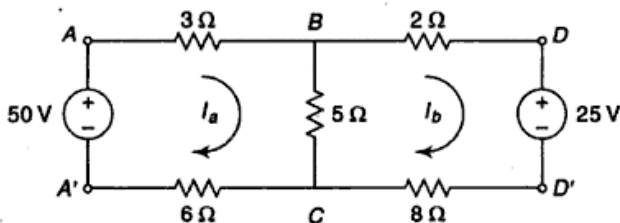


Fig. 4.119 Circuit of Ex. 4.88

Solution

Let I_a and I_b be the loop currents. Applying KVL to loop ABCA'A

$$3I_a + 5(I_a - I_b) + 6I_a = 50$$

or

$$14I_a - 5I_b = 50.$$

(i)

Applying KVL to loop BDD'CB

$$2I_b + 25 + 8I_b + 5(I_b - I_a) = 0$$

or

$$-5I_a + 15I_b = -25.$$

(ii)

Solution of equations (i) and (ii) yields

$$I_a = 3.3784\text{ A and } I_b = -0.541\text{ A}$$

The current through $3\ \Omega$ and $6\ \Omega$ resistors is thus 3.3784 A from A to B and C to A' respectively. The current through $2\ \Omega$ and $8\ \Omega$ resistors is 0.541 A from D to B and C to D' respectively, while the current through $5\ \Omega$ resistor is

$$I_a - I_b = 3.9194\text{ A from } B \text{ to } C.$$

Voltage across $5\ \Omega$ resistor is $5 \times 3.9194 = 19.597\text{ V}$.

.....

4.89 In the circuit shown in Fig. 4.120 find current I_a .

....

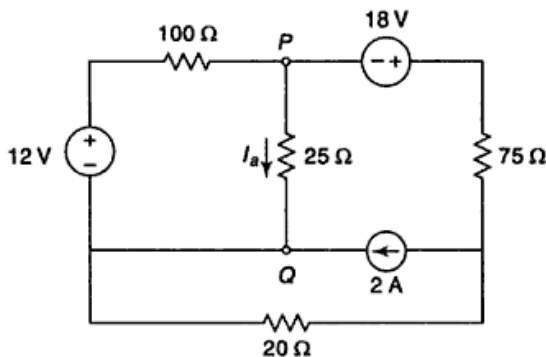


Fig. 4.120 Circuit of Ex. 4.89

Solution

The circuit is redrawn as shown in Fig. 4.120(a).

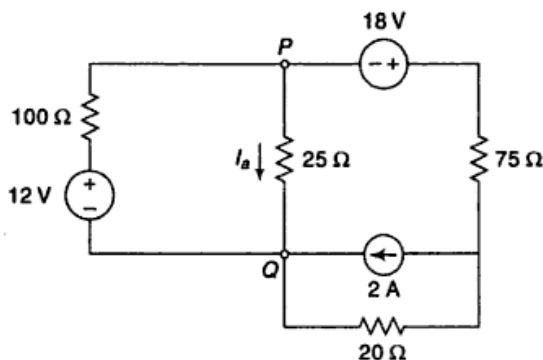


Fig. 4.120(a) Circuit of Ex. 4.89 redrawn

The 2 A current source can be replaced by an equivalent voltage source of $20 \times 2 = 40$ V in series with a $20\ \Omega$ resistance and the modified circuit is shown in Fig. 4.120(b).

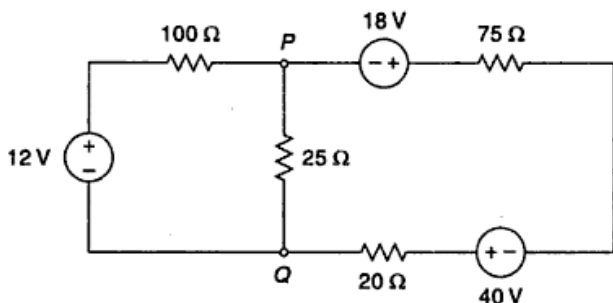


Fig. 4.120(b) Modified circuit

The two-voltage sources in series can be combined into a single source as shown in Fig. 4.120(c).

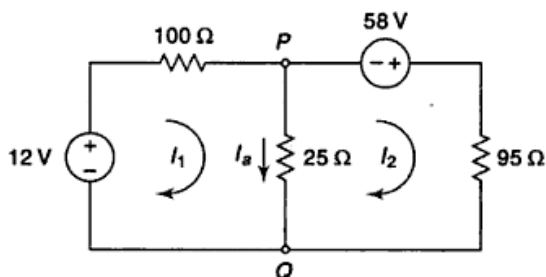


Fig. 4.120(c) Finally reduced circuit of Ex. 4.89

Let I_1 and I_2 be the loop currents applying KVL in these two loops

$$100 I_1 + 25(I_1 - I_2) = 12 \quad (\text{i})$$

$$\text{and} \quad 95 I_2 + 25(I_2 - I_1) = 58 \quad (\text{ii})$$

Solving the two equations (i) and (ii).

$$I_1 = 0.201\text{ A and } I_2 = 0.525\text{ A}$$

$$\therefore I_a (= I_1 - I_2) = -0.3242\text{ A (from P to Q)}$$

$$\text{or, } I_a = 0.3242\text{ A (from Q to P).}$$

4.90 From the circuit shown in Fig. 4.121, use loop analysis to determine the loop currents I_1 , I_2 , I_3 .

Solution

From Fig. 4.121 the current source of 1 A is equivalent to $(I_2 - I_1)$, i.e. $I_2 - I_1 = 1$ A. (i)

From loop ABCPA

$$2(I_3 - I_1) + 1(I_3 - I_2) + I_3 \times 1 = 0$$

$$\text{or } -2I_1 - I_2 + 4I_3 = 0 \quad (\text{ii})$$

From loop ABCFEDA

$$2(I_1 - I_3) + 1(I_2 - I_3) + 2I_2 - 2 = 0$$

$$\text{or } 2I_1 + 3I_2 - 3I_3 = 2 \quad (\text{iii})$$

Solving the three equations (i), (ii), (iii) we obtain

$$I_1 = -\frac{1}{11} \text{ A}, \quad I_2 = \frac{10}{11} \text{ A} \quad \text{and} \quad I_3 = \frac{2}{11} \text{ A}.$$

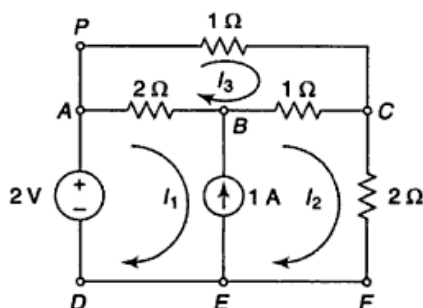


Fig. 4.121 Circuit of Ex. 4.90

4.91 In the circuit shown in Fig. 4.122 determine the voltages at nodes 1 and 2 with respect to the reference point.

Solution

Applying nodal analysis at node (1),

$$\frac{V_1}{4} + \frac{V_1 - V_2}{5} - 2 = 0$$

$$\text{or } 9V_1 - 4V_2 = 40 \quad (\text{i})$$

Applying nodal analysis at node (2),

$$\frac{V_2 - V_1}{5} + \frac{V_2}{6} - 3 = 0$$

$$\text{or } -6V_1 + 11V_2 = 90 \quad (\text{ii})$$

Solving equations (i) and (ii)

$$V_1 = 10.667 \text{ V and } V_2 = 14 \text{ V}.$$

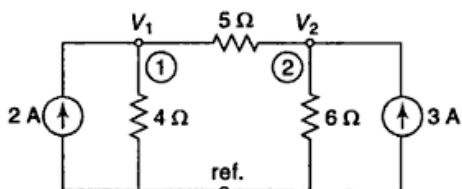


Fig. 4.122 Circuit of Ex. 4.91

4.92 In the circuit shown in Fig. 4.123 find voltage at node A.

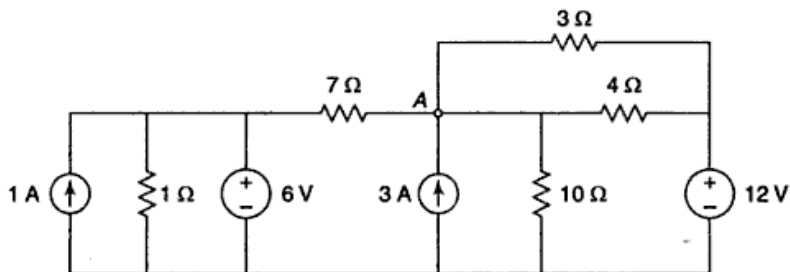


Fig. 4.123 Circuit of Ex. 4.92

Solution

Since the 3 A current source is in parallel with the 10 Ω resistor, hence converting the current source into the equivalent voltage source and replacing the parallel combination of 3 Ω and 4 Ω by a single resistance [Fig. 4.123(a)] we can write nodal equation at node A as

$$\frac{V_A - 30}{10} + \frac{V_A - 6}{7} + \frac{V_A - 12}{\frac{12}{7}} = 0$$

$$\text{or } V_A \left(\frac{1}{10} + \frac{1}{7} + \frac{7}{12} \right) - 3 - \frac{6}{7} - 7 = 0$$

$$\text{or } V_A = 13.14 \text{ V}$$

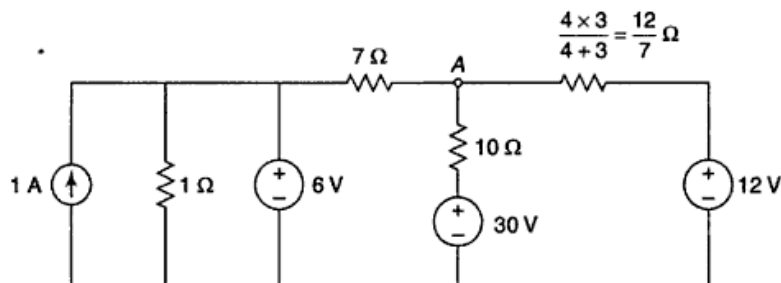


Fig. 4.123(a) Network reduction of the circuit shown in Fig. 4.123

4.93 Using mesh analysis obtain the values of all mesh currents of the network shown in Fig. 4.124.

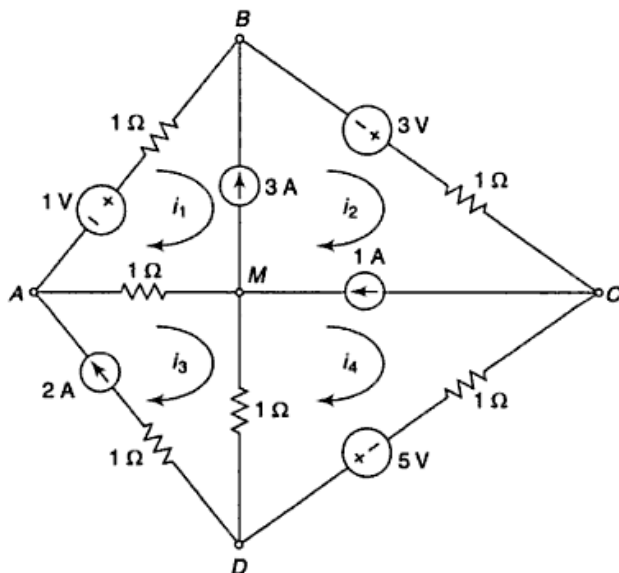


Fig. 4.124 Circuit of Ex. 4.93

Solution

From Fig. 4.124 it can easily be observed that

$$i_3 = 2 \text{ A}$$

$$i_2 - i_1 = 3 \text{ A}$$

and

$$i_2 - i_4 = 1 \text{ A}$$

By applying KVL to a closed loop which does not have any current source (loop *ABCDMA*) we obtain

$$-1 + i_1 - 3 + i_2 + i_4 - 5 + (i_4 - i_3) + (i_1 - i_3) = 0$$

$$\text{or } 2i_1 + i_2 + 2i_4 = 13$$

As $i_1 = (i_2 - 3)$ and $i_4 = (i_2 - 1)$, hence from above we can write,

$$2(i_2 - 3) + i_2 + 2(i_2 - 1) = 13$$

$$\text{or } i_2 = 4.2 \text{ A}$$

$$\text{Hence, } i_1 = 4.2 - 3 = 1.2 \text{ A and } i_4 = 4.2 - 1 = 3.2 \text{ A.}$$

$$\therefore i_1 = 1.2 \text{ A; } i_2 = 4.2 \text{ A; } i_3 = 2 \text{ A; } i_4 = 3.2 \text{ A.}$$

.....

4.94. Determine the current in the conductor of 2 Siemens of the network shown in Fig. 4.125 using node voltage analysis.

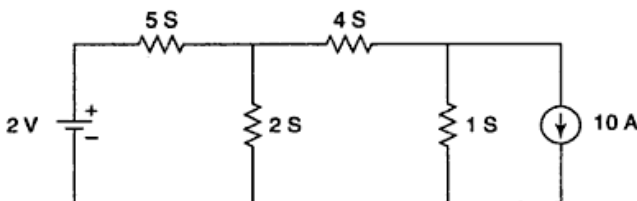


Fig. 4.125 Circuit of Ex. 4.93

Solution

Replacing the current source by an equivalent voltage source the new transformed circuit is shown in Fig. 4.125(a). Here there are two nodes (1) and (2). Let node (2) be taken as the reference node and let V be the potential at node (1).

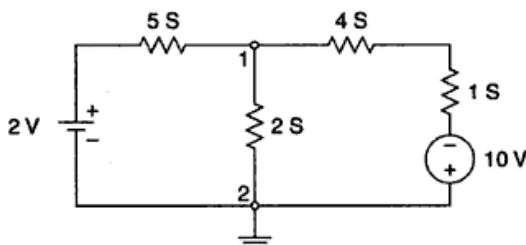


Fig. 4.125(a) Transformed circuit of Fig. 4.125

$$\text{Hence } (V - 2)5 + V \times 2 + (V + 10)(4 + 1) = 0$$

$$\text{or } V = -\frac{40}{12} = -3.333.$$

Hence current through conductance of 2 Siemens is $-3.333 \times 2 = -6.67 \text{ A}$. This current is directed from (2) to (1).

.....

4.95 Using loop equations obtain the current in the $12\ \Omega$ resistor of the network shown in Fig. 4.126.

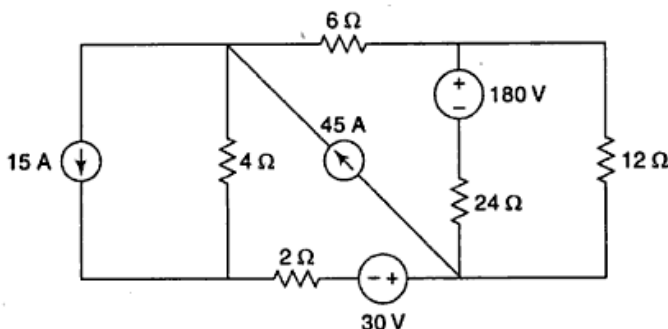


Fig. 4.126 Circuit of Ex. 4.95

Solution

Let us first replace 15 A current source by an equivalent voltage source; the corresponding figure is shown in Fig. 4.126(a).

Here $I_2 - I_1 = 45$ (i)

Applying KVL in loop ABCDA

$$6I_2 + 180 + 24(I_2 - I_3) + 30 + 6I_1 + 60 = 0$$

or $6I_1 + 30I_2 - 24I_3 = -270$

or $I_1 + 5I_2 - 4I_3 = -45$ (ii)

Applying KVL in loop BEFCB

$$12I_3 + 24(I_3 - I_2) - 180 = 0$$

or $-24I_2 + 36I_3 = 180$

or $-2I_2 + 3I_3 = 15$ (iii)

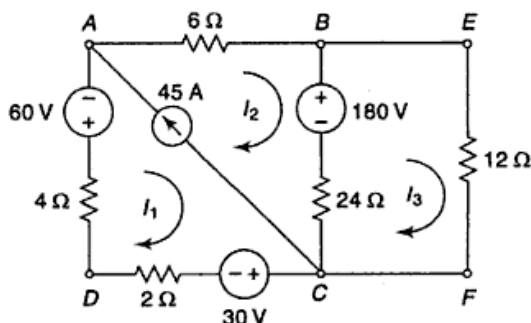


Fig. 4.126(a) Transformed circuit of Fig. 4.126

Solving equations (i), (ii) and (iii)

$$I_2 = 6\text{ A}, I_3 = 9\text{ A and } I_1 = -39\text{ A}$$

\therefore Current in the $12\ \Omega$ resistor is $I_3 = 9\text{ A}$.

4.96 Use node voltage analysis determine the power in the $2\ \Omega$ and $4\ \Omega$ resistor in the network of Fig. 4.127.

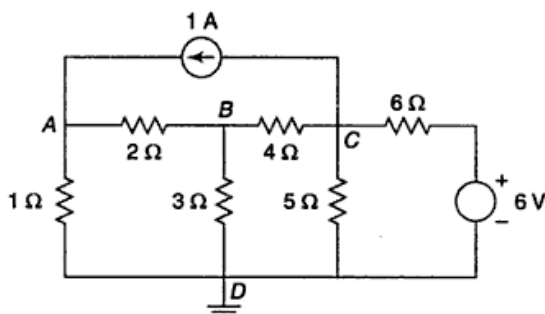


Fig. 4.127 Circuit of Ex. 4.96

Solution

There are four nodes in the network of which D is considered as the reference node.

At node A

$$\frac{V_A - V_B}{2} + V_A - 1 = 0$$

or

$$3V_A - V_B = 2 \quad (i)$$

At node B

$$-\frac{V_A - V_B}{2} + \frac{V_B - V_C}{4} + \frac{V_B}{3} = 0$$

or

$$6V_B - 6V_A + 3V_B - 3V_C + 4V_B = 0$$

or

$$-6V_A + 13V_B - 3V_C = 0 \quad (ii)$$

At node C

$$\frac{V_C - V_B}{4} + \frac{V_C}{5} + \frac{V_C - 6}{6} + 1 = 0$$

or

$$15V_C - 15V_B + 12V_C + 10V_C - 60 + 60 = 0$$

or

$$-15V_B + 37V_C = 0 \quad (iii)$$

Solving equations (i), (ii) and (iii)

$$V_A = 0.8031\text{ V}, V_B = 0.4088\text{ V and } V_C = 0.1658\text{ V}$$

$$\therefore \text{Power in the } 2\ \Omega \text{ resistor} = \frac{(V_A - V_B)^2}{2} = \frac{(0.8031 - 0.4088)^2}{2} = 0.078\text{ W}$$

$$\text{Power in } 4\ \Omega \text{ resistor} = \frac{(V_B - V_C)^2}{4} = \frac{(0.4088 - 0.1658)^2}{4} = 0.01476\text{ W.}$$

.....

4.97 Determine the Thevenin's equivalent circuit with respect to terminals A, B for the network shown in Fig. 4.128.

Solution

From Fig. 4.128 it is evident that open circuit voltage V_{oc} between A and B is the voltage across the $4\ \Omega$ resistor. The current through the $4\ \Omega$ resistor due to the 12 A

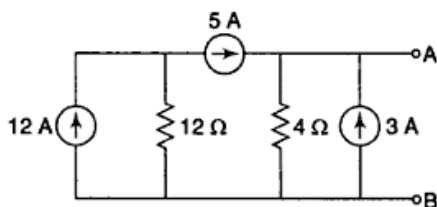


Fig. 4.128 Circuit of Ex. 4.97

source is zero due to the presence of 5 A current source. The other two current sources deliver 5 A and 3 A current in the same direction through the $4\ \Omega$ resistor. So voltage across the $4\ \Omega$ resistor V_{oc} is $[4 \times (5 + 3) = 32\text{ V}]$. Next, removing all the sources Thevenin's equivalent resistance can be obtained as shown in Fig. 4.128(a).

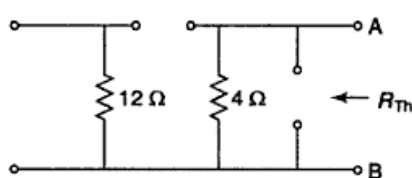


Fig. 4.128(a) Determination of Thevenin's equivalent resistance

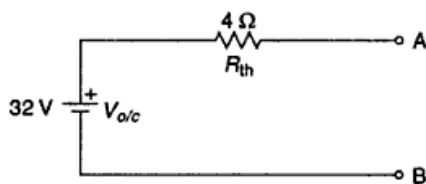


Fig. 4.128(b) Thevenin's equivalent network of Ex. 4.97

Here $R_{Th} = 4\ \Omega$

The Thevenin's equivalent circuit is shown in Fig. 4.128(b).

4.98 Find the Thevenin's equivalent circuit at terminals AB for the network shown in Fig. 4.129 and hence determine the power dissipated in a $5\ \Omega$ resistor connected between A and B.

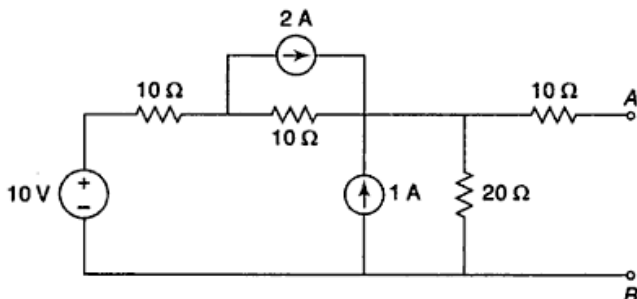


Fig. 4.129 Circuit of Ex. 4.98

Solution

Converting the current sources into equivalent voltage sources [Fig. 4.129(a)], current I through $20\ \Omega$ resistor is given as

$$I = \frac{20 + 10 - 20}{10 + 10 + 20} = 0.25\text{ A}$$

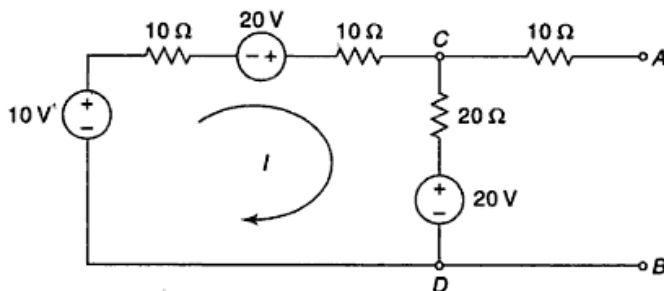


Fig. 4.129(a) Modified circuit

$$\begin{aligned} \therefore V_{Th} &= \text{Voltage across CD} \\ &= 20 + 20 \times 0.25 = 25 \text{ V} \end{aligned}$$

To find R_{Th} , deactivating all sources [Fig. 4.129(b)] we get

$$R_{Th} = 10 + \frac{20 \times (10 + 10)}{20 + (10 + 10)} = 20 \Omega$$

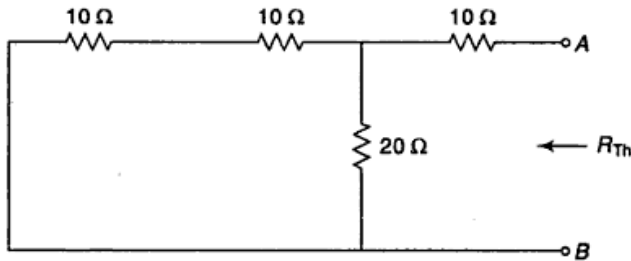


Fig. 4.129(b) Determination of R_{Th}

Thevenin's equivalent circuit is shown in Fig. 4.129(c).

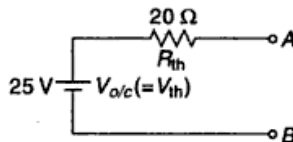


Fig. 4.129(c) Thevenin's equivalent circuit of Ex. 4.98

4.99 Obtain Thevenin's equivalent circuit with respect to terminals A and B of the network shown in Fig. 4.130.

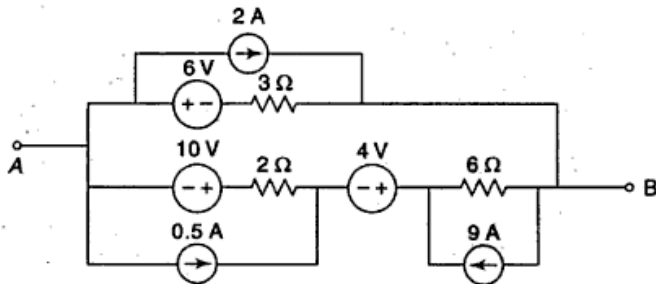


Fig. 4.130 Circuit of Ex. 4.99

Solution

Let us first convert 6 V and 10 V voltage sources into corresponding current sources and 9 A current source into voltage source [Fig. 4.130(a)]. Next, Fig. 4.130(a) is reduced to Fig. 4.130(b).

Next we convert 5.5 A current source into equivalent voltage source as shown in Fig. 4.130(c). Figure 4.130(d) shows further network reduction.

The current I through the loop in Fig. 4.130(d) is

$$I = \frac{39}{8+3} \text{ A} = 3.55 \text{ A}$$

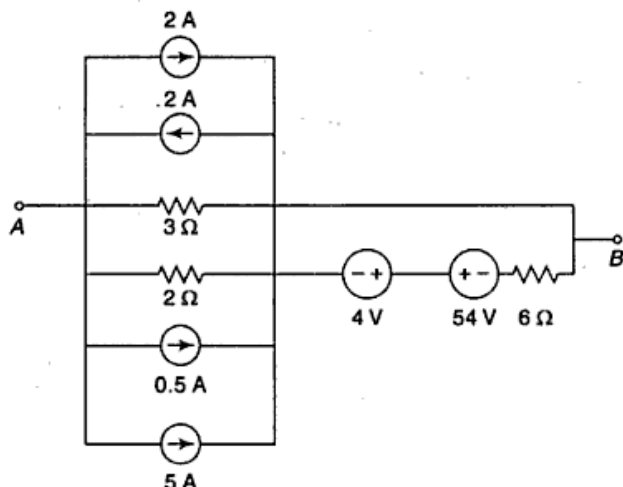


Fig. 4.130(a) Conversion of sources

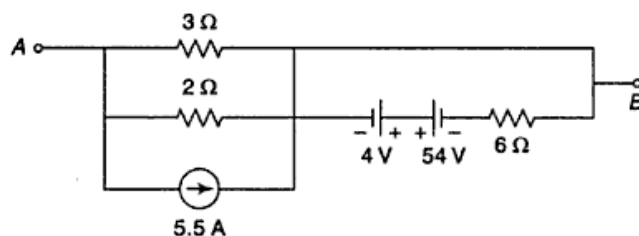


Fig. 4.130(b) Network reduction

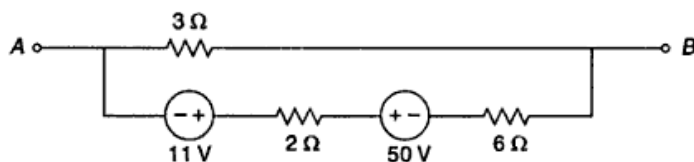


Fig. 4.130(c) Reduced network


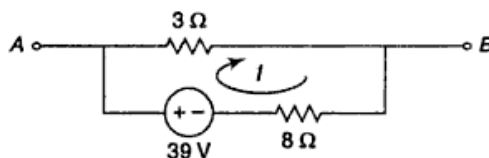


Fig. 4.130(d) Finally reduced network

$\therefore V_{Th} = \text{Voltage across the } 3 \Omega \text{ resistor}$
 $= 3 \times 3.55 \text{ V} = 10.65 \text{ V}.$

Thevenin's equivalent resistance $R_{Th} = \frac{8 \times 3}{3 + 8} \Omega$
 $= 2.18 \Omega.$

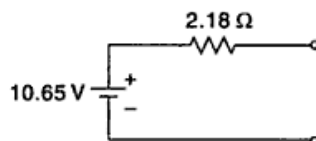Thevenin's equivalent circuit is shown in Fig. 4.130(e). Thevenin's equivalent network of Ex. 4.99



4.100 Determine the Thevenin's equivalent of the bridge network shown in Fig. 4.131 as seen from the galvanometer terminals B and D and hence determine the galvanometer current when $R_G = 50 \Omega$.

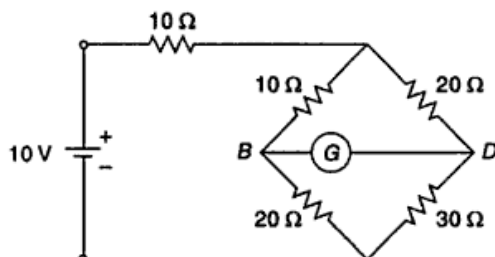


Fig. 4.131 Circuit of Ex. 4.100

Solution

To find the Thevenin's equivalent voltage across BD , the galvanometer is open-circuited and the corresponding figure is shown in Fig. 4.131(a). The circuit of Fig. 4.131(a) can then be reduced to that shown in Fig. 4.131(b).

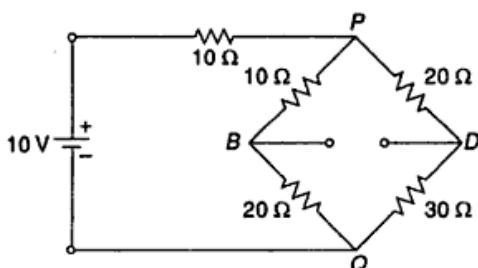


Fig. 4.131(a) Circuit configuration with galvanometer removed

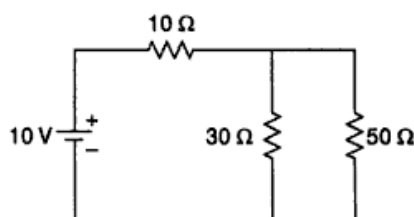


Fig. 4.131(b) Reduced network

$$\text{Current through the } 30 \Omega \text{ resistor} = \frac{10}{10 + \frac{30 \times 50}{30 + 50}} \times \frac{50}{50 + 30} = 0.217 \text{ A.}$$

$$\text{Current through the } 50 \Omega \text{ resistor} = \frac{10 \times 30}{2300} \text{ A} = 0.13 \text{ A.}$$

\therefore Currents through PB and PD in Fig. 4.131(a) are 0.217 A and 0.13 A respectively.

$$V_{th} = V_{BD} = V_{PD} - V_{PB} = 20 \times 0.13 - 0.217 \times 10 = 0.43 \text{ V}$$

To find Thevenin's equivalent resistance the voltage source is short circuited as shown in Fig. 4.131(c)

Converting delta network into equivalent star network Fig. 4.131(d) is obtained.

$$R_1 = \frac{10 \times 10}{10 + 20 + 10} = 2.5 \Omega$$

$$R_2 = \frac{10 \times 20}{40} = 5 \Omega$$

$$R_3 = \frac{20 \times 10}{40} = 5 \Omega$$

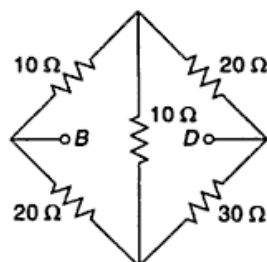


Fig. 4.131(c) Finding of R_{th}

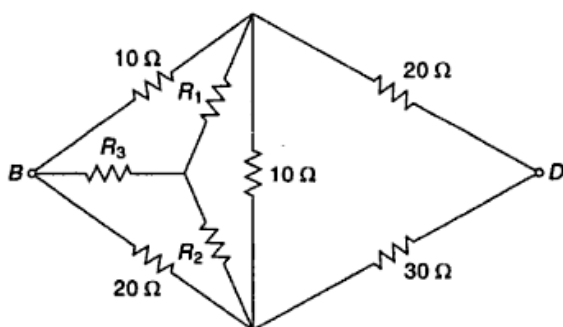


Fig. 4.131(d) Network reduction for network shown in Fig. 4.131(c)

The equivalent resistance across terminal BD can be found out from Fig. 4.31(e) as

$$R_{Th} = 5 + \frac{22.5 \times 35}{22.5 + 35} = 18.696 \, \Omega.$$

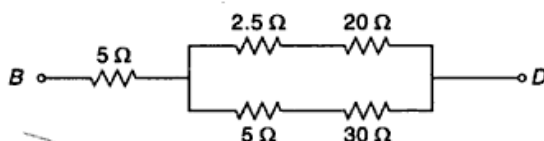


Fig. 4.131(e) Finally reduced network

Thevenin's equivalent of the bridge network is shown in Fig. 4.131(f).

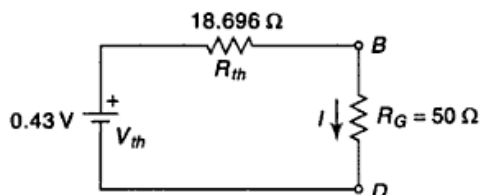


Fig. 4.131(f) Thevenin's equivalent of Ex. 4.100

The galvanometer current is given by

$$I = \frac{0.43}{18.696 + 50} \text{ A} = 0.0063 \text{ A} = 6.3 \text{ mA}$$

4.101 Find Norton's equivalent circuit at terminals A and B for the network shown in Fig. 4.132 and hence determine the power dissipated in a $5 \, \Omega$ resistor to be connected between terminals A and B .

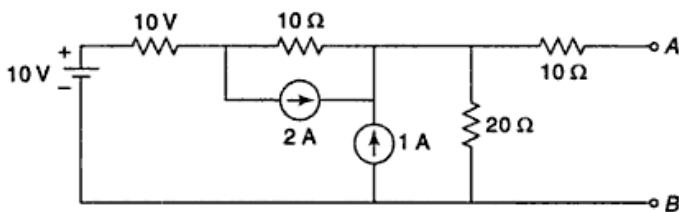


Fig. 4.132 Circuit of Ex. 4.101

Solution

First we convert the current sources into equivalent voltage sources and short circuit terminals AB [Fig. 4.132(a)].

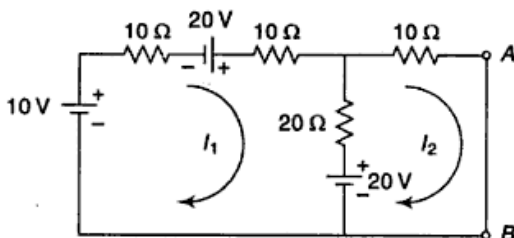


Fig. 4.132(a) Conversion of sources

If I_1 and I_2 be the loop currents then

$$-10 + (10 + 10) I_1 + 20(I_1 - I_2) = 0 \quad (i)$$

$$\text{and} \quad -20 + 20(I_2 - I_1) + 10I_2 = 0 \quad (ii)$$

Solving Eqs (i) and (ii) we get

$$I_2 = 1.25 \text{ A}$$

Now, Norton's equivalent current i.e., the current through short-circuited path AB is given by

$$\therefore I_N = 1.25 \text{ A}$$

To find Norton's equivalent resistance, AB is open circuited and the sources are removed as shown in Fig. 4.132(b).

$$R_N = 10 + \frac{20 \times 20}{20 + 20} = 20 \Omega$$

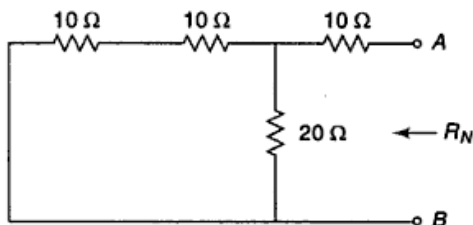


Fig. 4.132(b) Finding of R_N

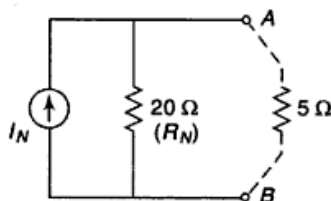


Fig. 4.132(c) Norton's equivalent circuit of Ex. 4.101

Norton's equivalent circuit is shown in Fig. 4.132(c).

So, the current I through 5Ω resistor connected between terminals A and B is

$$I = 1.25 \times \frac{20}{20 + 5} = 1 \text{ A}$$

Hence power dissipated through 5Ω resistor $= I^2 \times 5 = 5 \text{ W}$

4.102. In Fig. 4.133 the galvanometer G has a conductance of 10 S . Determine the current through the galvanometer using Thevenin's theorem.

Solution

Let us first see open-circuiting terminals AB [Fig. 4.133(a)]

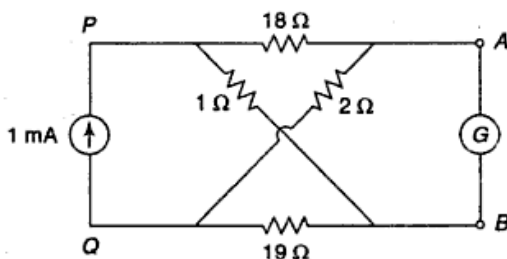


Fig. 4.133 Circuit of Ex. 4.102

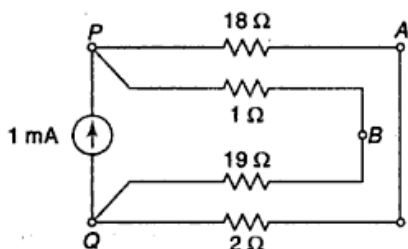


Fig. 4.133(a) Circuit with galvanometer removed

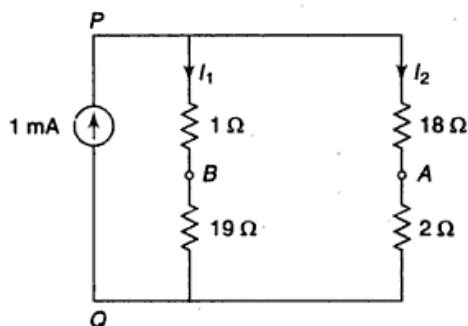


Fig. 4.133(b) Modified circuit of Fig. 4.133(a)

Figure 4.133(a) is redrawn as shown in Fig. 4.133(b).

From Fig. 4.133(b) current through the $1\ \Omega$ resistor is

$$I_1 = 1 \times \frac{20}{20 + 20} = 0.5\ \text{mA}$$

and current through $18\ \Omega$ resistor is also

$$I_2 = 1 \times \frac{20}{20 + 20} = 0.5\ \text{mA}$$

$$\begin{aligned} \text{Now } V_{AB} &= V_{PB} - V_{PA} \\ &= 1 \times 0.5 - 18 \times 0.5 = -8.5\ \text{mV} \end{aligned}$$

$$\therefore V_{Th} = V_{BA} = 8.5\ \text{mV}$$

[terminal B is at higher potential].

To find Thevenin's equivalent resistance current source is open-circuited and the network of Fig. 4.133(c) is obtained.

$$\text{Hence } R_{Th} = \frac{(18 + 1)(19 + 2)}{(18 + 1) + (19 + 2)} = 9.975\ \Omega$$

From Fig. 4.133(d) current through the galvanometer of $10\ \text{S}$, i.e. $1/10\ \Omega$ resistance is

$$\begin{aligned} \frac{8.5 \times 10^{-3}}{9.975 + \frac{1}{10}}\ \text{A} &= 0.844 \times 10^{-3}\ \text{A} \\ &= 0.844\ \text{mA} \end{aligned}$$

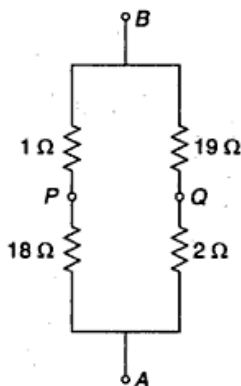
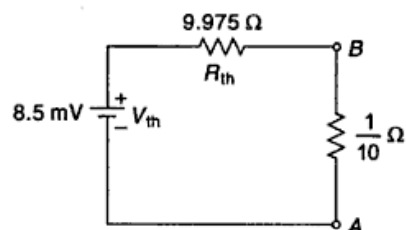
Fig. 4.133(c) Determination of R_{Th} 

Fig. 4.133(d) Thevenin's equivalent of Ex. 4.102

4.103 Determine the current through the $1\ \Omega$ resistor connected across A, B of the network shown in Fig. 4.134 using Norton's theorem.

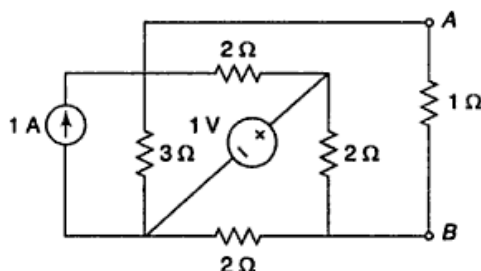


Fig. 4.134 Circuit of Ex. 4.134

Solution

Removing the $1\ \Omega$ resistor and short-circuiting the terminals AB the circuit is redrawn as shown in Fig. 4.134(a). The $1\ \text{A}$ current source has been transformed into voltage source. Applying KVL to the three loops we get the following three equations:

$$3I_1 + 2(I_1 - I_3) + 1 - 3 = 0$$

$$\text{or } 5I_1 - 2I_3 = 2 \quad (\text{i})$$

$$2I_2 - 1 + 2(I_2 - I_3) = 0$$

$$\text{or } 4I_2 - 2I_3 = 1 \quad (\text{ii})$$

$$\text{and } 2(I_3 - I_2) + 2(I_3 - I_1) = 0$$

$$\text{or } -2I_1 - 2I_2 + 4I_3 = 0 \quad (\text{iii})$$

Solving the three equations (i), (ii) and (iii) we get $I_3 = 0.59\ \text{A}$. Hence the current through the short circuited path AB is $I_3 = 0.59\ \text{A}$, i.e. $I_N = 0.59\ \text{A}$.

To find R_N , all the sources are deactivated and open circuiting terminals AB [Fig. 4.134(b)], we get

$$R_N = \frac{3 \times 2}{3 + 2} + \frac{2 \times 2}{2 + 2} = 2.2\ \Omega$$

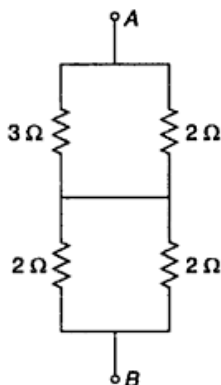


Fig. 4.134(b) Determination of (R_N)

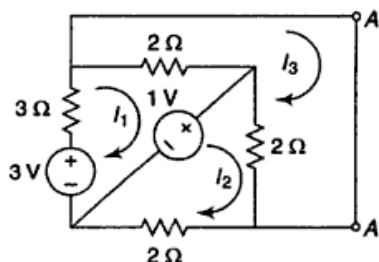


Fig. 4.134(a) Determination of (I_N)

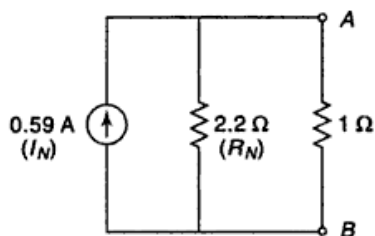


Fig. 4.134(c) Norton's equivalent circuit of Ex. 4.103

From Fig. 4.134(c) the current through the $1\ \Omega$ resistor is

$$0.59 \times \frac{2.2}{2.2 + 1} \text{ A} = 0.4056 \text{ A}.$$

4.104 Solve the above problem (Example 4.103) using the superposition theorem.

Solution

Considering a 1 A current source acting alone, the circuit shown in Fig. 4.134, transforms into the circuit shown in Fig. 4.135.

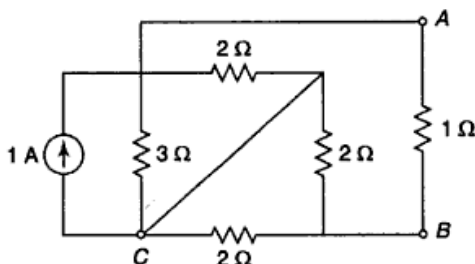


Fig. 4.135 1 A source is acting alone in circuit of Fig. 4.134

The circuit further reduces as shown in Fig. 4.135(a).

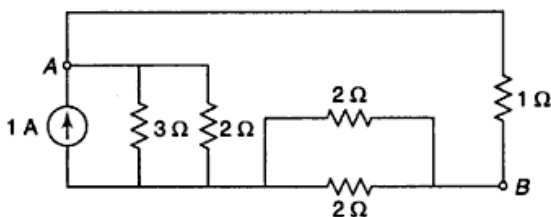


Fig. 4.135(a) Reduced circuit

Next, Fig. 4.135(a) is simplified into Fig. 4.135(b) and then into Fig. 4.135(c).

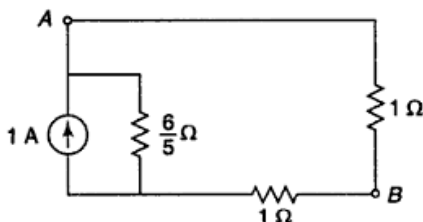


Fig. 4.135(b) Network reduction

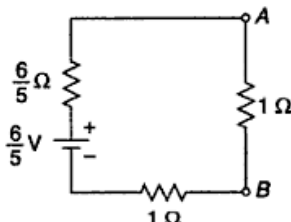


Fig. 4.135(c) Finally reduced circuit with 1 A source acting only

The current through the 1 Ω resistor when the current source acts alone is given by

$$\frac{\frac{6}{5}}{\frac{6}{5} + 1 + 1} \text{ A} = 0.375 \text{ A (from A to B)}$$

Next, considering the voltage source acting alone, the network in Fig. 4.134 transforms into Fig. 4.135(d).

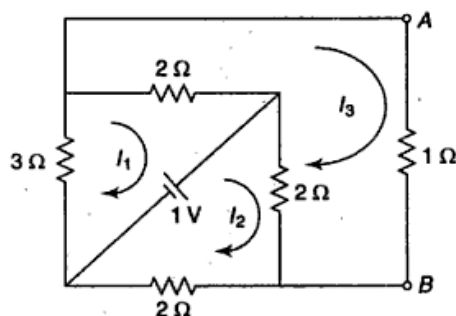


Fig. 4.135(d) Voltage source acting alone in circuit of Fig. 4.134

Applying KVL in the three loops the following three equations are obtained:

$$2(I_1 - I_3) + 1 + 3I_1 = 0 \quad (i)$$

$$2(I_2 - I_3) + 2I_2 - 1 = 0 \quad (ii)$$

$$\text{and } I_3 + 2(I_3 - I_2) + 2(I_3 - I_1) = 0 \quad (iii)$$

Solving these three equations, $I_3 = 0.03125$ A (from A to B).

Applying superposition theorem current through the $1\ \Omega$ resistor (when both the sources are acting simultaneously) is $0.375 + 0.03125 = 0.40625$ A (from A to B).

4.105 Using the superposition theorem find the voltage across the $20\ \Omega$ resistor of the circuit shown in Fig. 4.136.

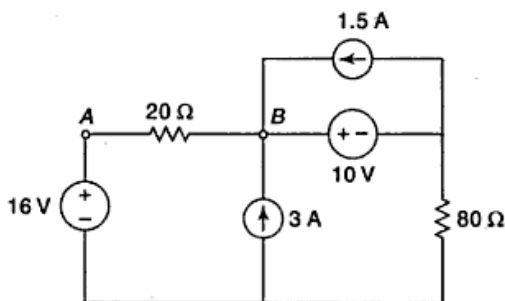


Fig. 4.136 Circuit of Ex. 4.105

Solution

Let us consider that the 16 V source acts alone; removing the other sources the circuit configuration is shown in Fig. 4.136(a). The current through the $20\ \Omega$ resistor is

$$I_1 = \frac{16}{20 + 80} \text{ A} = 0.16 \text{ A from A to B}$$

Considering 10 V source acting alone the circuit is redrawn as shown in Fig. 4.136(b).

$$\text{Current through the } 20\ \Omega \text{ is } I_2 = \frac{10}{20 + 80} \text{ A}$$

$= 0.1$ from B to A.

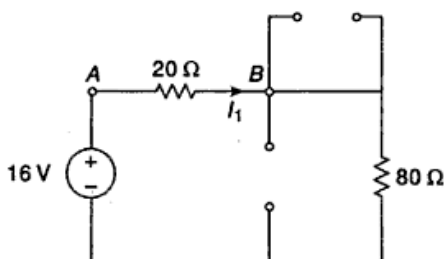


Fig. 4.136(a) 16 V source acting alone

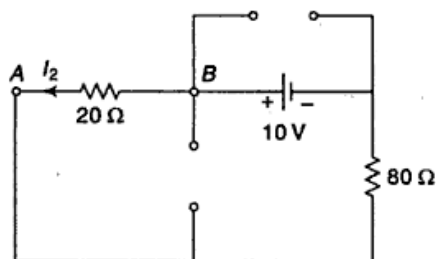


Fig. 4.136(b) 10 V source acting alone

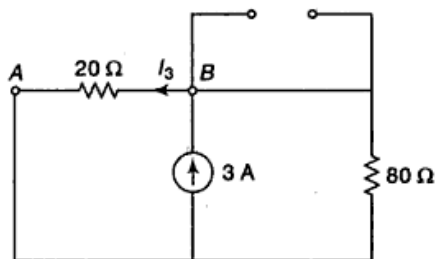


Fig. 4.136(c) 3 A source is acting alone

Next, considering 3 A source acting alone the corresponding circuit is shown in Fig. 4.136(c).

Current in the 20 Ω resistor is $I_3 = 3 \times \frac{80}{20+80}$ A = 2.4 A from B to A.

Considering the 1.5 A source acting alone the corresponding circuit is shown in Fig. 4.136(d).

As there is a short circuit path in parallel with 1.5 A current source, hence no current flows through 20 Ω resistor due to this source.

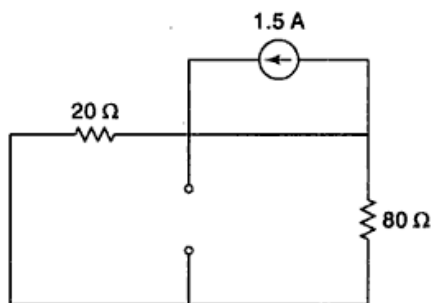


Fig. 4.136(d) 1.5 A source acting alone

Applying superposition theorem, when all the sources are acting simultaneously the current through the 20 Ω resistor is $(I_2 + I_3 - I_1) = (0.1 + 2.4 - 0.16) = 2.34$ A from B to A. or voltage across the 20 Ω resistor is $2.34 \times 20 = 46.8$ V.

4.106 Determine R_L in Fig. 4.137 for maximum power transfer to the load.

Solution

The two-delta networks, one formed by 3 numbers of 6 Ω resistors and another by 3 numbers of 21 Ω resistors, are first converted into equivalent star network.

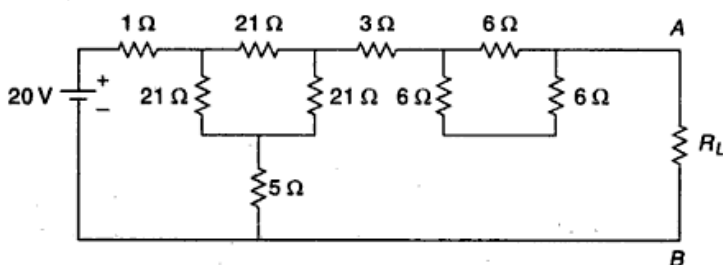


Fig. 4.137 Circuit of Ex. 4.106

Here

$$R_1 = \frac{21 \times 21}{21 + 21 + 21} \Omega = 7 \Omega$$

$$R_2 = \frac{6 \times 6}{6 + 6 + 6} \Omega = 2 \Omega$$

The corresponding network is shown in Fig. 4.137(a).

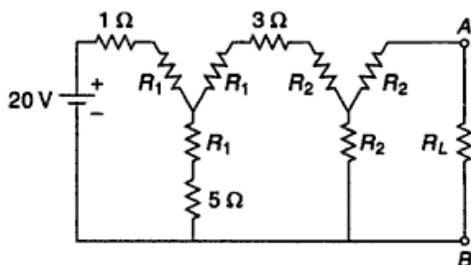


Fig. 4.137(a) Circuit reduction

The network shown in Fig. 4.137(a) can further be reduced to Fig. 4.137(b).

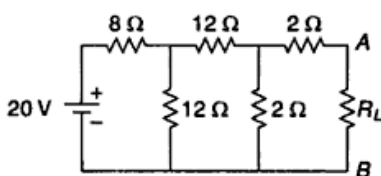


Fig. 4.137(b) Finally reduced circuit

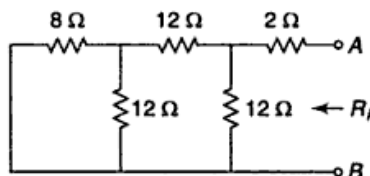


Fig. 4.137(c) Finding of (R_i)

For maximum power transfer to the load R_L the value R_L should be equal to R_i which is equal to the internal resistance of the network. R_i can be found from Fig. 4.137(c) removing the source and open circuiting terminals AB (Fig. 4.137 (c)).

$$R_L = R_i = \left\{ \left(\frac{8 \times 12}{8 + 12} + 12 \right) \parallel 12 \right\} + 2$$

$$= \frac{16.8 \times 12}{16.8 + 12} + 2 = 9 \Omega$$

.....

4.107 Using the superposition theorem, find the current through R_L in the circuit shown in Fig. 4.138.

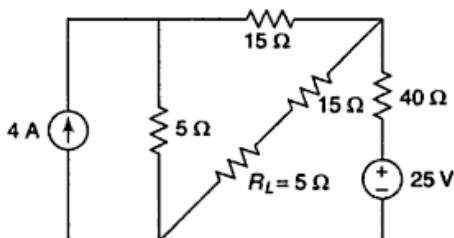


Fig. 4.138 Circuit of Ex. 4.107

Solution

Converting the current source into equivalent voltage source the transformed network is shown in Fig. 4.138(a)

Considering the 20 V source acting alone, the circuit is shown in Fig. 4.138(b).

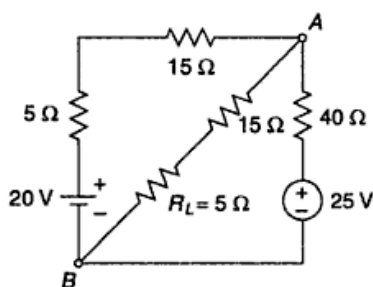


Fig. 4.138(a) Conversion of source

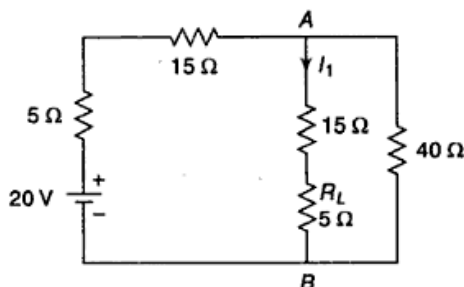


Fig. 4.138(b) 20 V source acting alone

The current through R_L is

$$I_1 = \frac{20}{20 + \frac{20 \times 40}{20 + 40}} \times \frac{40}{40 + 20}$$

$$= \frac{20 \times 40}{20 \times 60 + 20 \times 40} = \frac{800}{1200 + 800} = \frac{8}{20} = 0.4 \text{ A (from A to B)}$$

Considering the 25 V source acting alone from the circuit, is shown in Fig. 4.138(c), the current through (R_L) is

$$I_2 = \frac{25}{40 + \frac{20}{2}} \times \frac{1}{2} = \frac{25}{2 \times 50} = 0.25 \text{ A (from A to B).}$$

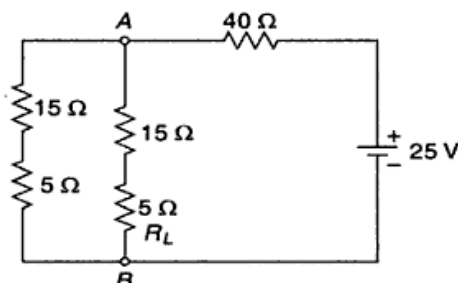


Fig. 4.138(c) 25 V source acting alone

Applying the superposition theorem when both the sources are acting simultaneously the current through R_L is

$$I_1 + I_2 = 0.4 + 0.25 = 0.65 \text{ A (from A to B)}$$

4.108 Find the current through the 2Ω resistor as shown in Fig. 4.139 using the Superposition theorem.

Solution

Considering the 2 A source acting alone, the corresponding circuit is shown in Fig. 4.139(a).

Fig. 4.139(a) is redrawn in Fig. 4.139(b).

Now the current through the 2Ω resistor is

$$I_1 = 2 \times \frac{1}{1 + 2 + \frac{4 \times 3}{4 + 3}} = \frac{2}{4.71} = 0.424 \text{ A (from P to A)}$$

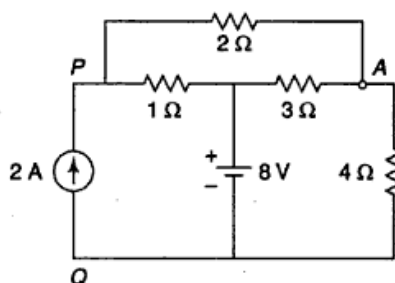


Fig. 4.139 Circuit of Ex. 4.108

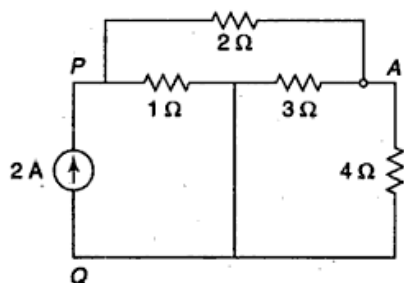


Fig. 4.139(a) 2 A source acting alone

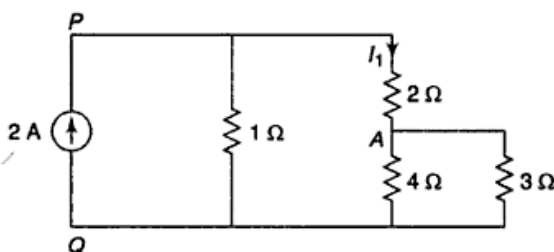


Fig. 4.139(b) Simplified circuit

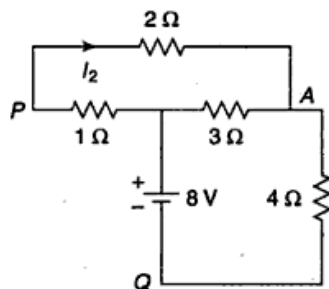


Fig. 4.139(c) 8 V Source acting alone

Considering the 8 V source acting alone, the corresponding circuit is shown in Fig. 4.139(c).

Current through the 2 Ω resistor is

$$I_2 = \frac{8}{4 + \frac{3}{2}} \times \frac{1}{2} = \frac{4}{5.5} = 0.727 \text{ A (from P to A)}$$

Using superposition theorem, net current through 2 Ω resistor is $I_1 + I_2 = 0.424 + 0.727 = 1.151 \text{ A}$.

4.109 Find the current through the 2 Ω resistor of Fig. 4.139 using Norton's theorem.

Solution

Let us short-circuit the terminals PA after removing the 2 Ω resistor. Now we consider the 2 A source acting alone the (corresponding circuit being shown in Fig. 4.140).

Figure 4.140 can be further reduced to the circuit shown in Fig. 4.140(a). The short circuit current due to the 2 A source acting alone is

$$I_{sc1} = 2 \times \frac{1}{\frac{4 \times 3}{1 + 4 + 3}} = \frac{2 \times 7}{19} = \frac{14}{19} \text{ A}$$

(from P to A).

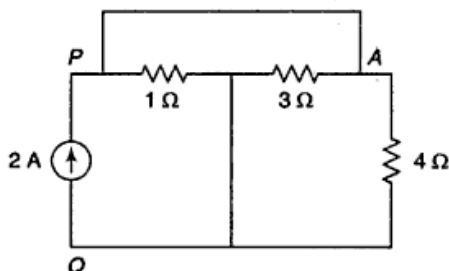


Fig. 4.140 Circuit of Ex. 4.109

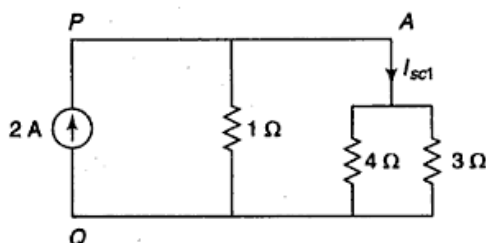


Fig. 4.140(a) Reduced network with 2 A source acting alone

Considering the 8 V source acting alone, the current through the short circuited path can be found from Fig. 4.140(b). Current through short circuited path due to the 8 V source acting alone is

$$I_{sc2} = \frac{8}{4 + \frac{3 \times 1}{3+1}} \times \frac{3}{3+1} = \frac{24}{19} \text{ (from P to A).}$$

Applying the superposition theorem the current through the short circuited path when both the sources are acting simultaneously is

$$I_{sc} = \left(\frac{14}{19} + \frac{24}{19} \right) = 2 \text{ A}$$

Hence, Norton's equivalent current $I_N = 2 \text{ A}$.

Now to find Norton's equivalent resistance R_N , all the sources are deactivated and open circuiting terminals PA the circuit configuration shown in Fig. 4.140(c) is obtained.

$$R_N = 1 + \frac{3 \times 4}{3+4} = 1 + \frac{12}{7} = \frac{19}{7} \Omega.$$

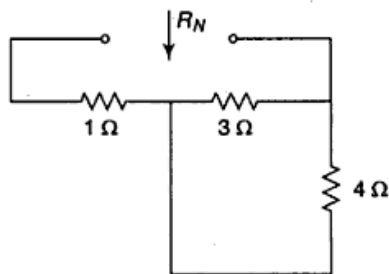
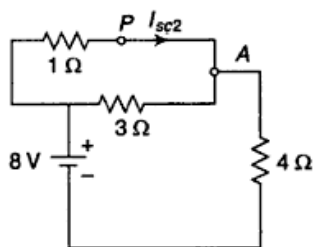
Fig. 4.140(c) Determination of (R_N)

Fig. 4.140(b) 8 V source acting alone

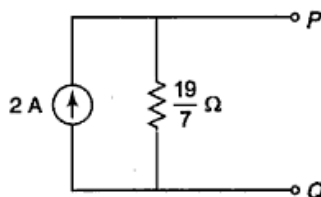


Fig. 4.140(d) Norton's equivalent circuit of Ex. 4.109

Norton's equivalent circuit is shown in Fig. 4.140(d).

The current through the 2 Ω resistor connected between terminals P&A using Norton's

theorem is $2 \times \frac{\frac{19}{7}}{2 + \frac{19}{7}} = \frac{2 \times 19}{33} \text{ A} = 1.151 \text{ A}.$

.....

4.110 Find the value of V_R in the circuit shown in Fig. 4.141.

Solution

Let V_a be the voltage at node a . Applying KCL at node a

$$\frac{V_a - 2}{2} + \frac{V_a - 8V_R}{10} - 2 = 0$$

or $5V_a - 10 + V_a - 8V_R = 20$

or $6V_a - 8V_R = 30$

Again $V_R = V_a - 2$ or, $V_a = V_R + 2$

Hence, $6(V_R + 2) - 8V_R = 30$

or $-2V_R = 18$

or $V_R = -9$ V [this means node "a" is of negative polarity.]

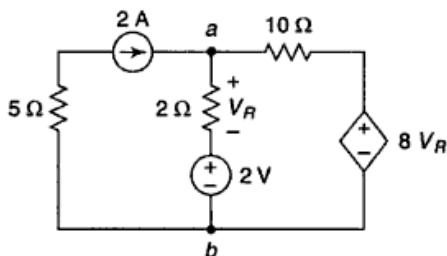


Fig. 4.141 Circuit of Ex. 4.110

4.111 Applying kirchhoff's voltage law find the values of current i and the voltages v_1 and v_2 in the circuit shown in Fig. 4.142.

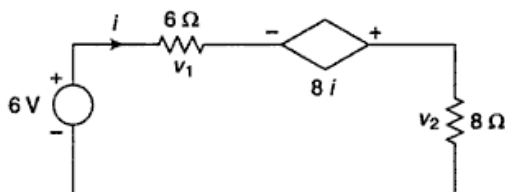


Fig. 4.142 Circuit of Ex. 4.111

Solution

Applying Kirchhoff's voltage law in Fig. 4.142

$$6 - v_1 + 8i - v_2 = 0$$

or $v_1 + v_2 = 6 + 8i$

Now $v_1 = 6i$ and $v_2 = 8i$

Hence $6i + 8i = 6 + 8i$

or $i = 1$

Therefore $v_1 = 6 \times 1 = 6$ Volts and $v_2 = 8 \times 1 = 8$ V.

4.112 Applying KCL find the value of current i in the circuit shown in Fig. 4.143.

Solution

Applying KCL at node (x),

$$i - i_1 + 2i_1 - i_2 = 0$$

or $i + i_1 - i_2 = 0$

$\therefore i_1 = \frac{50}{5} = 10$ A and $i_2 = \frac{50}{3}$ A,

$$i + 10 - \frac{50}{3} = 0$$

or, $i = \frac{50}{3} - 10 = \frac{20}{3} = 6.67$ A

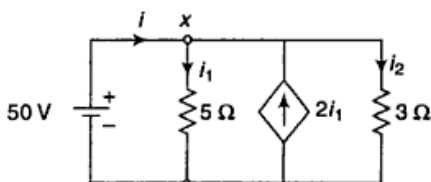


Fig. 4.143 Circuit of Ex. 4.112

4.113 Find i_1 , i_2 and i_3 in Fig. 4.144.

Solution

Let us consider mesh currents i_x and i_y in the two meshes as shown in Fig. 4.144(a).

Applying loop equations in the two meshes

$$6 \times 10^3(i_x - i_y) - 21 = 0$$

$$\text{and } 6 \times 10^3(i_y - i_x) + 12 \times 10^3 i_y + 28 = 0$$

$$\text{or } i_x = i_y + \frac{21}{6 \times 10^3} \quad (\text{i})$$

$$\text{and } 18 \times 10^3 i_y - 6 \times 10^3 i_x + 28 = 0 \quad (\text{ii})$$

Solving these two equations

$$i_y = -0.583 \text{ mA and } i_x = 2.917 \text{ mA}$$

From Fig. 4.144(a) it is evident that

$$0.5i_3 = 2.917 \text{ mA}$$

$$\text{or } i_3 = 5.834 \text{ mA.}$$

Applying KCL at node a

$$0.5i_3 + i_2 + i_3 = 0$$

$$\text{or } i_2 + 1.5i_3 = 0$$

$$\text{or } i_2 = -1.5 \times 5.834 \\ = -8.751 \text{ mA}$$

$$\text{Also, } i_1 = 0.5i_3 \\ = 0.5 \times 5.834 = 2.917 \text{ mA.}$$

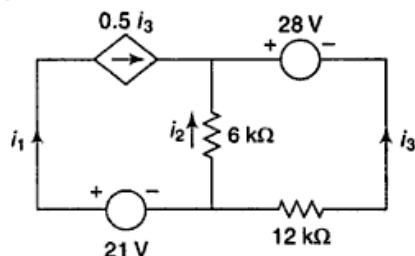


Fig. 4.144 Circuit of Ex. 4.113

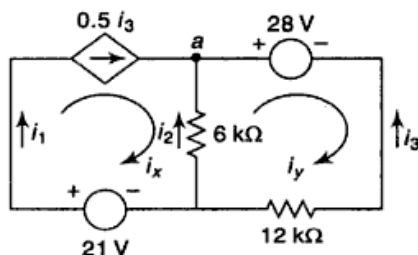


Fig. 4.144(a) Network of Fig. 4.144 with mesh currents

4.114 Find the power dissipated in the 100Ω resistor and find the voltage rating of the dependent source in Fig. 4.145.

Solution

Applying KVL in the given figure,

$$6 - 500i_o + 2 - 100i_o = 0$$

$$\text{or } i_o = \frac{8}{600} = 13.33 \text{ mA.}$$

Power dissipated in the 100Ω resistor = $(100) \times (0.0133)^2 = 17.7 \text{ m Watts}$. Hence voltage rating of the dependent source is $500 \times i_o = 500 \times 0.0133 = 6.65 \text{ V}$.

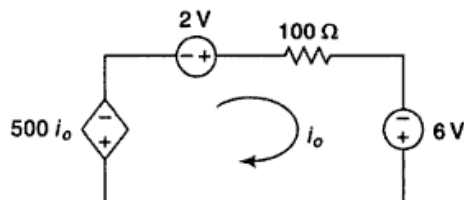


Fig. 4.145 Circuit of Ex. 4.114

4.115 Using node analysis find the value of α for the circuit shown in Fig. 4.146 when the power loss in the 1Ω resistor is 9 W .

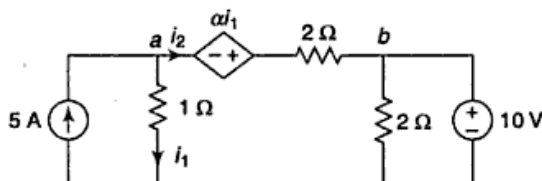


Fig. 4.146 Circuit of Ex. 4.115

Solution

Power loss in the $1\ \Omega$ resistor is

$$i_1^2 \times 1 = 9$$

or $i_1 = 3\text{ A}$

and $v_a = 3 \times 1 = 3\text{ V}$.

Applying KCL at node a

$$i_1 + i_2 = 5$$

or $i_2 = 5 - i_1 = 5 - 3 = 2\text{ A}$

Also $v_a + \alpha i_1 - 2i_2 = v_b$

or $3 + 3\alpha - 4 = v_b$

Since $v_b = 10\text{ V}$

hence $3\alpha = 10 + 1 = 11$

or $\alpha = 3.67$.

.....

4.116 Find i_1 and i_2 in the circuit shown in Fig. 4.147 using superposition theorem.

.....

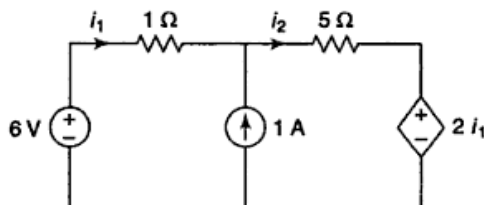


Fig. 4.147 Circuit of Ex. 4.116

Solution

Considering 6 V source acting alone and removing the current source (as shown in Fig. 4.147(a)), we get

$$6 - 2i_1 = (1 + 5)i_1 \quad \text{or} \quad i_1 = \frac{6}{8} = \frac{3}{4}\text{ A}$$

Also $i_2 = \frac{3}{4}\text{ A}$

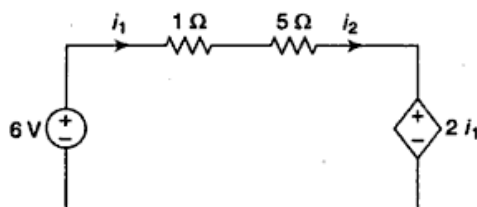


Fig. 4.147(a) 6 V source acting alone

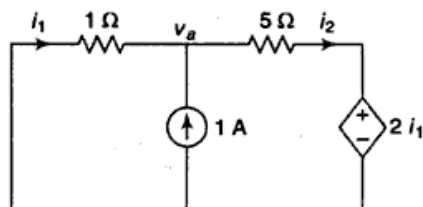


Fig. 4.147(b) 1 A source acting alone

Now, considering the 1 A current source acting alone and removing the others, from the corresponding circuit (shown in Fig. 4.147(b)), we have

$$1 + i_1 - \frac{v_a - 2i_1}{5} = 0$$

$$\text{or } 5 + 5i_1 - v_a + 2i_1 = 0$$

$$\text{or } 7i_1 - v_a + 5 = 0$$

$$\therefore \frac{v_a}{1} = -i_1,$$

$$\text{hence } 7i_1 + i_1 + 5 = 0$$

$$\text{or } i_1 = -\frac{5}{8} \text{ A}$$

$$\text{and } i_2 = \frac{v_a - 2i_1}{5} = \frac{-i_1 - 2i_1}{5} = \frac{3}{5} \times \frac{5}{8} = \frac{3}{8} \text{ A}$$

Applying superposition theorem when both the sources are acting simultaneously

$$i_1 = \frac{3}{4} - \frac{5}{8} = \frac{6-5}{8} = \frac{1}{8} = 0.125 \text{ A}$$

$$\text{and } i_2 = \frac{3}{4} + \frac{3}{8} = \frac{6+3}{8} = \frac{9}{8} = 1.125 \text{ A}$$

4.117 Find v in the circuit shown in Fig. 4.148 using superposition theorem.

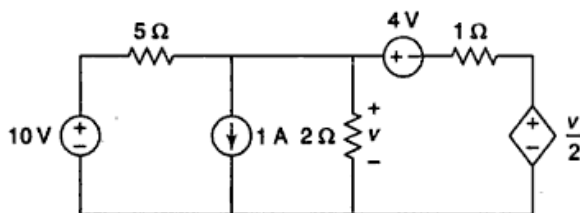


Fig. 4.148 Circuit of Ex. 4.117

Solution

Let us consider the 10 V source only removing the 1 A and 4 V source. The corresponding circuit is shown in Fig. 4.148(a). At node a ,

$$\frac{v-10}{5} + \frac{v-\frac{v}{2}}{2} + \frac{v}{2} = 0$$

$$\text{or } 2v - 20 + 10v - 5v + 5v = 0$$

$$\text{or } 12v = 20 \text{ or, } v = 1.67 \text{ V.}$$

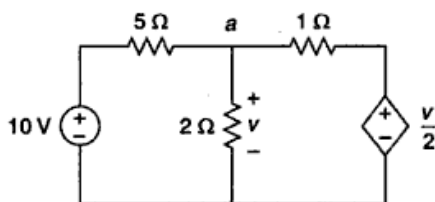


Fig. 4.148(a) 10 V source considered only

Now, let us consider 1 A source acting alone. The corresponding figure is shown in Fig. 4.148(b).

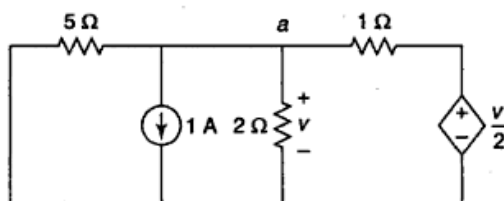


Fig. 4.148(b) 1 A source acting alone

At node a ,

$$\frac{v}{2} + \frac{v}{5} + 1 + \frac{v - \frac{v}{2}}{1} = 0$$

or $v + 5 + 5v = 0$

or $v = -\frac{5}{6} = -0.833 \text{ V}$

Finally let us consider 4 V source acting alone [as shown in Fig. 4.148(c)].

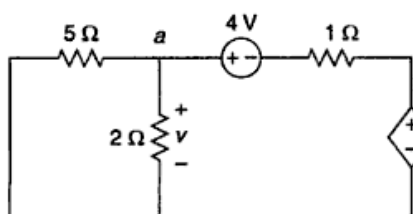


Fig. 4.148(c) 4 V source acting alone

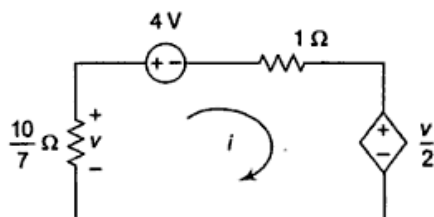


Fig. 4.148(d) Simplified network with 4 V source

Here 5 Ω and 2 Ω are in parallel. The transformed network is shown in Fig. 4.148(d).

In the circuit of Fig. 4.148(d),

$$v - 4 - 1 \times i - \frac{v}{2} = 0$$

or $\frac{v}{2} - i = 4$

Again, $v = -\frac{10}{7} \times i$

Hence $-\frac{10i}{2 \times 7} - i = 4$

or $i = -2.33$

$\therefore v = \frac{10}{7} \times 2.33 = 3.33 \text{ V}$

Using superposition theorem, when all the sources are acting simultaneously we have

$$v = 1.67 - 0.833 + 3.33 = 4.17 \text{ V.}$$

4.118 Find power loss in the 2 Ω resistor shown in Fig. 4.149 using superposition theorem.

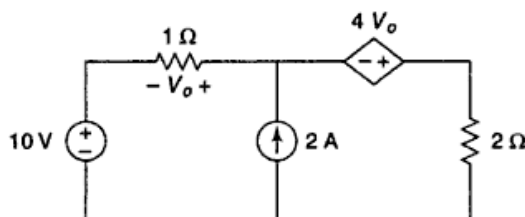


Fig. 4.149 Circuit of Ex. 4.118

Solution

Considering the 10 V source acting alone in the circuit [Fig. 4.149(a)] the loop equation

$$10 + V_o + 4V_o - 2i = 0$$

$$\text{or } 5V_o - 2i + 10 = 0$$

$$\text{Now } 1 \times i = -V_o$$

$$\text{Hence } 5(-i) - 2i + 10 = 0$$

$$\text{or } -7i + 10 = 0, \text{ i.e. } i = \frac{10}{7} \text{ A} = 1.43 \text{ A}$$

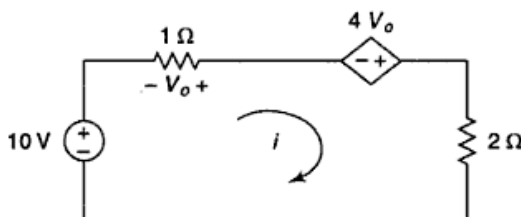


Fig. 4.149(a) 10 V source acting alone

Considering 2 A source acting alone [Fig. 4.149(b)] and applying KCL at node *a* we have

$$2 - \frac{v_a}{1} - \frac{v_a + 4V_o}{2} = 0$$

$$\text{or } 4 - 2v_a - v_a - 4V_o = 0$$

$$\text{or } 4 - 3v_a - 4V_o = 0$$

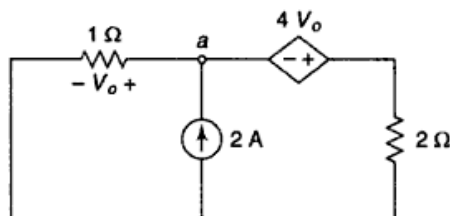


Fig. 4.149(b) 2 A source acting alone

Now, from the given figure, $v_a = V_o$

$$\text{Hence from (i) } 4 - 7V_o = 0 \text{ i.e. } V_o = \frac{4}{7} = 0.57 \text{ V}$$

Current through 2 Ω resistor is

$$\frac{v_a + 4V_o}{2} = \frac{V_o + 4V_o}{2} = \frac{5}{2} \times 0.57 = 1.425 \text{ A}$$

Applying superposition theorem the current through 2 Ω resistor is thus (1.43 + 1.425) A i.e. 2.855 A.

Hence power loss in 2 Ω resistor is $(2.855)^2 \times 2 = 16.31 \text{ W}$.


.....

4.119 Solve Example 4.118 using Thevenin's theorem.

Solution

Removing 2 Ω resistor as shown in Fig. 4.150, the open circuit voltage is obtained and


$$V_{oc} = 10 + V_o + 4V_o = 10 + 5V_o$$

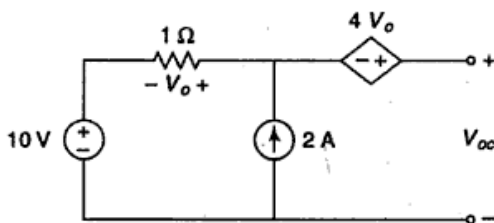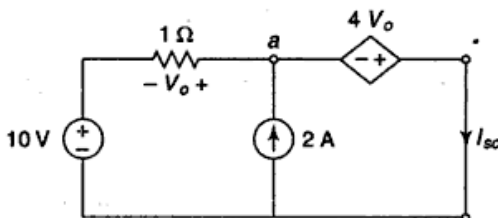Fig. 4.150 Determination of V_{oc}

However, V_o = voltage across the $1\ \Omega$ resistor
 $= 1 \times$ current through the $1\ \Omega$ resistor
 $= 1 \times 2 = 2\text{ V}$

Hence $V_{oc} = 10 + 5 \times 2 = 20\text{ V}$.

To find out R_{Th} , let us first short-circuit the output terminals as shown in Fig. 4.150(a).

Fig. 4.150(a) Determination of I_{sc} and R_{Th}

Applying KVL in the circuit,

$$10 + V_o + 4V_o = 0$$


or $V_o = -\frac{10}{5} = -2$

Applying nodal analysis at node a ,

$$2 - \frac{V_o}{1} - I_{sc} = 0$$

or $I_{sc} = 2 - \frac{-2}{1} = 4\text{ A}$

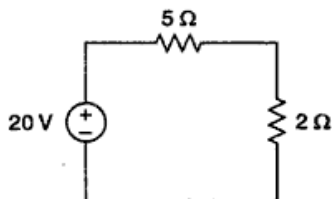Hence $R_{Th} = \frac{V_{oc}}{I_{sc}} = 5\ \Omega$.



The Thevenin's equivalent circuit is shown in Fig. 4.150(b) *Thevenin's equivalent circuit*

The current through $2\ \Omega$ resistor $= \frac{20}{7}\text{ A} = 2.857\text{ A}$.

Hence the power loss in the $2\ \Omega$ resistor is $(2.857)^2 \times 2 = 16.31\text{ W}$

.....

4.120 Obtain Thevenin's equivalent circuit across terminals $a-b$ in the Fig. 4.151.

Solution

The current through $1\text{ k}\Omega$ resistor is $\left(\frac{10}{1000} + \frac{V_o}{2000} \right)\text{ A}$

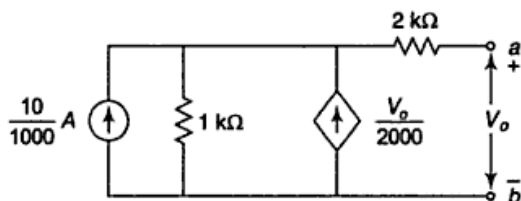



Fig. 4.151 Circuit of Ex. 4.120

Open circuit voltage across $a-b$ is the voltage across the $1\text{ k}\Omega$ resistor

Hence
$$V_o = \left(\frac{10}{1000} + \frac{V_o}{2000} \right) \times 1000 = 10 + 0.5 V_o$$

i.e.
$$V_o = 20\text{ V}$$

To find out Thevenin's equivalent resistance (R_{Th}) let us short circuit terminals ab as shown in Fig. 4.151(a).

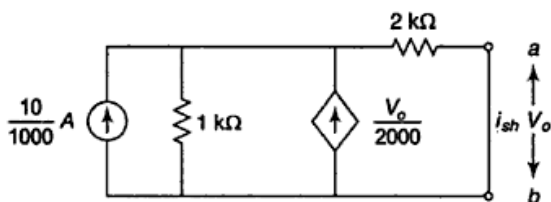Fig. 4.151(a) Determination of R_{Th}

As ab is short-circuited V_o is zero. The network reduces to that shown in Fig. 4.151(b).

Hence
$$i_{sh} = \frac{10}{1000} \times \frac{1}{1+2} = \frac{10}{3000}\text{ A}$$

Therefore,
$$R_{Th} = \frac{V_o}{i_{sh}} = \frac{20}{10/3000} = 6000\ \Omega$$

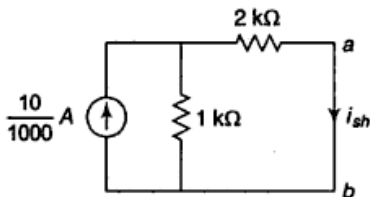


Fig. 4.151(b) Reduced network of the circuit shown in Fig. 4.151(a)

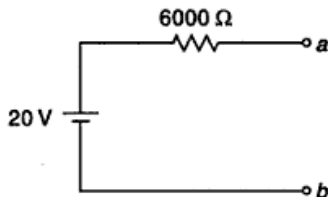


Fig. 4.151(c) Thevenin's equivalent circuit of Ex. 4.120

Thevenin's equivalent circuit is shown in Fig. 4.151(c).

4.121 Find the current in the $2\ \Omega$ resistor using Thevenin's theorem in the circuit shown in Fig. 4.152.

Solution

Let us remove the $2\ \Omega$ resistor. The corresponding figure is shown in Fig. 4.152(a).

Obviously the current supplied by the dependent current source $2i$ is zero.

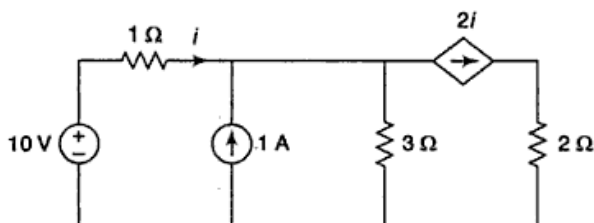
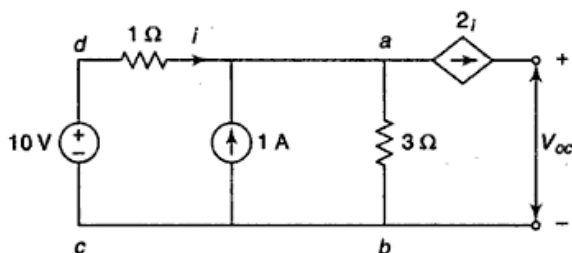


Fig. 4.152 Circuit of Ex. 4.121

Fig. 4.152(a) Determination of V_{OC}

Applying nodal method at node (a),

$$\frac{V_{oc}}{3} - 1 - i = 0$$

or

$$V_{oc} = 3(i + 1)$$

(i)

Applying KVL in loop $abcd$

$$10 - i - V_{oc} = 0 \quad \{V_{oc} = \text{voltage across the } 3\Omega \text{ resistor}\}$$

or

$$V_{oc} = 10 - i.$$

(ii)

Solving the two equations (i) and (ii),

$$3i + 3 = 10 - i$$


or

$$4i = 7 \text{ or, } i = 1.75 \text{ A}$$

and

$$V_{oc} = 10 - i = 8.25 \text{ A.}$$

To find out R_{Th} , terminals across the 2Ω resistor are shorted as shown in Fig. 4.152(b).

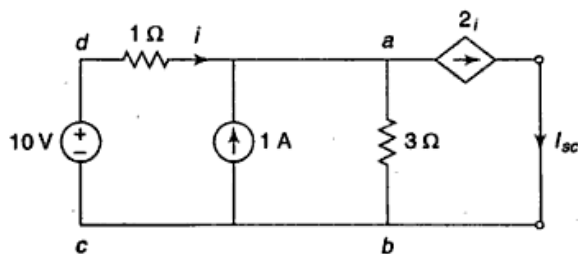Fig. 4.152(b) Determination of R_{Th}

$$I_{sc} = 2i$$

Applying the nodal method at node a ,

$$i + 1 = \frac{v_a}{3} + 2i$$

where v_a is the potential at node (a) w.r.t node (b)

Hence $3i + 3 = v_a + 6i$

or $3i = 3 - v_a$

(iii)

Applying KVL in loop $abcd$

$$10 - i - v_a = 0$$

i.e. $v_a = 10 - i$ (iv)

Solving the two equations (iii) and (iv),

$$3i = 3 - 10 + i$$

i.e. $2i = -7$ or, $i = -3.5$ A

Hence $I_{sc} = 2i = -7$

and $R_{Th} = \left| \frac{V_{oc}}{I_{sc}} \right| = \frac{8.25}{7} = 1.18 \Omega$

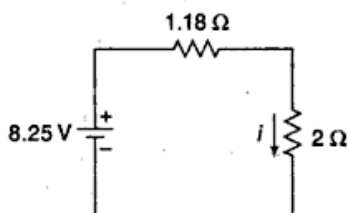


Fig. 4.152(c) Thevenin's equivalent circuit of Ex. 4.121

The Thevenin's equivalent circuit is shown in Fig. 4.152(c).

Hence current in the 2Ω resistor is $\frac{8.25}{2 + 1.18} = 2.59$ A.

4.122. Find the Norton's equivalent circuit for the transistor amplifier circuit shown in Fig. 4.153.

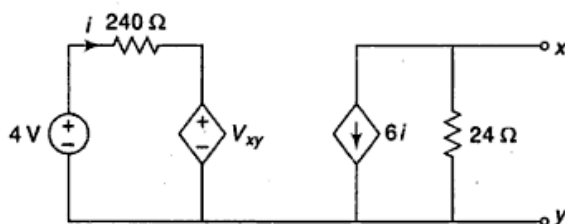


Fig. 4.153 Circuit of Ex. 4.122

Solution

To find the Norton's equivalent current source (i_N) let us short circuit xy . The corresponding figure is shown in Fig. 4.153(a).

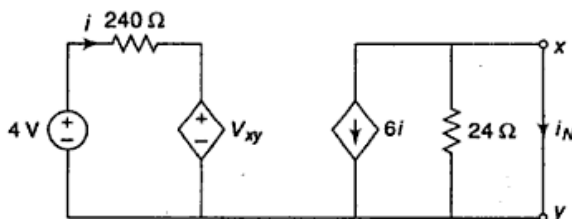


Fig. 4.153(a) x - y terminals shorted in the circuit of Fig. 4.153

The voltage across short-circuited terminals xy is zero, i.e. $V_{xy} = 0$.

Hence $i = \frac{4}{240}$ A = 0.0167 A

and $i_N = -6i = -6 \times 0.0167 = -0.1002$ A (from x to y)

or $i_N = 0.1002$ (from y to x)

To find the Norton's equivalent resistance R_N let us find the open circuit voltage V_{xy} from Fig. 4.153.

$$V_{xy} = \text{Voltage drop across the } 24 \Omega \text{ resistor} \\ = -6i \times 24 = -144i$$

$$\text{or} \quad i = -\frac{V_{xy}}{144}$$

Again applying KVL equation we find

$$4 - 240i - V_{xy} = 0$$

$$\text{or} \quad 4 - 240\left(-\frac{V_{xy}}{144}\right) - V_{xy} = 0$$

$$\text{or} \quad V_{xy} = -6$$

$$\text{Hence} \quad R_N = \frac{V_{xy}}{i_N} = \frac{6}{0.1002} = 60$$

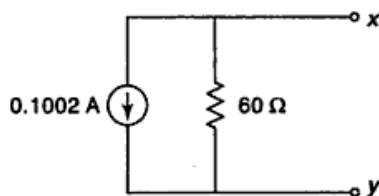


Fig. 4.153(b) Norton's equivalent circuit of Ex. 4.122

The Norton's equivalent circuit is shown in Fig. 4.153(b).

4.123 Find the current through R_L in the circuit shown in Fig. 4.154 using Norton's theorem.

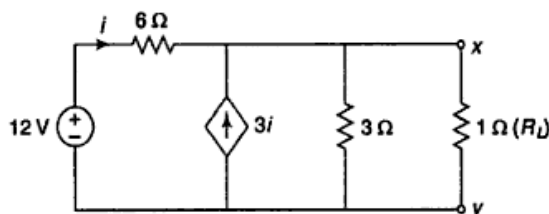


Fig. 4.154 Circuit of Ex. 4.123

Solution

Let us short-circuit the terminals xy to find out the Norton's equivalent current (Fig. 4.154(a)).

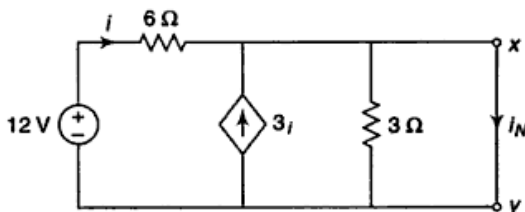



Fig. 4.154(a) Determination of i_N

$$i_N = i + 3i = 4i$$

$$\text{Now,} \quad i = \frac{12}{6} \text{ A} = 2 \text{ A}$$

$$\text{Hence} \quad i_N = 4 \times 2 = 8 \text{ A}$$

To find Norton's equivalent resistance R_N let us open circuit terminals xy . The corresponding circuit is shown in Fig. 4.154(b).

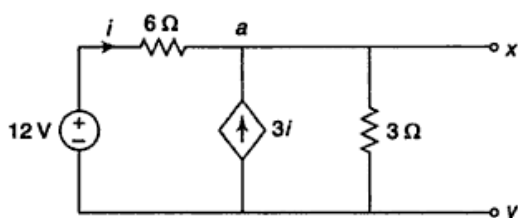Fig. 4.154(b) Determination of V_{xy}

At node a ,

$$i + 3i - \frac{V_{xy}}{3} = 0$$

$$V_{xy} = 12i$$

But,

$$i = \frac{12 - V_{xy}}{6}$$

Hence

$$V_{xy} = 12 \frac{12 - V_{xy}}{6} = 24 - 2V_{xy}$$

$$3V_{xy} = 24 \text{ i.e. } V_{xy} = 8 \text{ V.}$$

Therefore

$$R_N = \frac{8}{8} = 1 \Omega.$$

Norton's equivalent circuit is shown in Fig. 4.154(c).

Hence current through 1Ω resistor $= 8 \times \frac{1}{1+1} = 4 \text{ A.}$

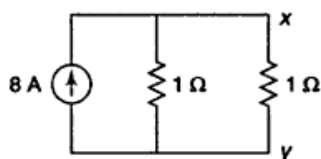


Fig. 4.154(c) Norton's equivalent circuit of Ex. 4.123

4.124 Using maximum power transfer theorem find the value of the load resistance R_L so that the maximum power is transferred across R_L in the circuit shown in Fig. 4.155.

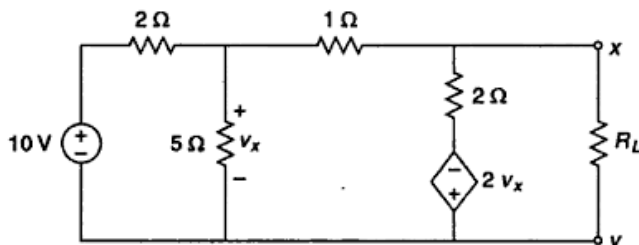


Fig. 4.155 Circuit of Ex. 4.124

Solution

Let us remove R_L and open circuit terminals xy to find out the internal resistance R_i of the circuit. According to maximum power transfer theorem the maximum power will be transferred through R_L when

$$R_L = R_i$$


From Fig. 4.155(a) applying KVL,

$$10 - 2i_1 - 5(i_1 - i_2) = 0$$

i.e.

$$7i_1 - 5i_2 = 10$$

(i)

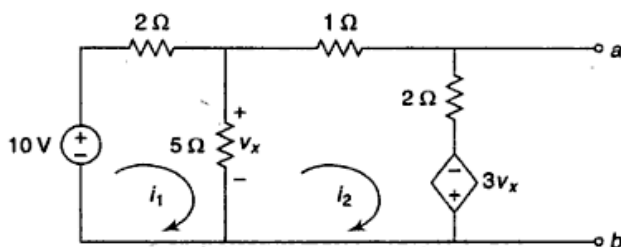Fig. 4.155(a) Determination of V_{ab}

and $3v_x - 5(i_2 - i_1) - i_2 \times 1 - 2i_2 = 0$

i.e. $3 \times 5(i_1 - i_2) - 5(i_2 - i_1) - 3i_2 = 0$ [$\because v_x = 5(i_1 - i_2)$]

or $20i_1 - 23i_2 = 0$ i.e., $i_1 = \frac{23}{20} i_2$

(ii)

Using equation (ii) in equation (i) we get

Hence $7 \times \frac{23}{20} i_2 - 5i_2 = 10$


or $i_2 = 3.28 \text{ A}$

and $i_1 = 3.772 \text{ A}$

$\therefore v_x = 5(3.772 - 3.28) = 2.46 \text{ V}$.

Now, $v_{ab} = -3v_x + 2i_2$
 $= -3 \times 2.46 + 2 \times 3.28$
 $= -0.82 \text{ V}$.

Let us now short circuit the terminals xy as shown in Fig. 4.155(b).

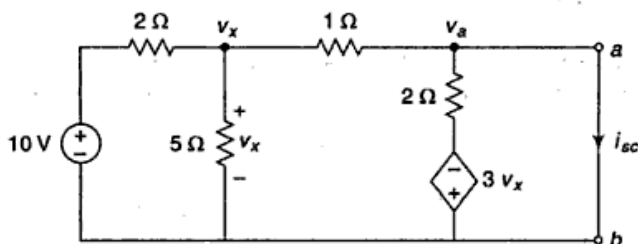Fig. 4.155(b) Determination of i_{sc}

At node a ,

$$\frac{v_a - v_x}{1} + \frac{v_a + 3v_x}{2} + i_{sc} = 0$$

As $a - b$ are shorted $v_a = 0$

Hence $-v_x + 1.5v_x + i_{sc} = 0$

i.e. $i_{sc} = -0.5v_x$

Now, v_x = Voltage across 5Ω resistor. Current through 5Ω resistor

$$I_{5\Omega} = \frac{10}{\frac{2 \times 5}{2+5+1}} \times \frac{1}{5+1} = \frac{60}{12+5} \times \frac{1}{6} = 0.588 \text{ A}$$

Hence $v_x = 5 \times 0.588 = 2.94 \text{ V}$

and $i_{sc} = -0.5 \times 2.94 = -1.47 \text{ A}$

Therefore, $R_L = R_i = \frac{-0.82}{-1.47} = 0.558 \Omega$.

.....

4.125 Determine the resistance connected across terminals $a-b$ which will transfer maximum power across it in the circuit shown in Fig. 4.156.

Solution

Applying KVL in the closed loop (Fig. 4.156), we have

$$15 - 10i + 5i - 5i = 0$$

or
$$i = \frac{15}{10} = 1.5 \text{ A}$$

Hence $V_{ab} = 1.5 \times 5 = 7.5 \text{ V}$

For finding out the internal resistance R_i of the circuit let us short circuit the path ab as shown in Fig. 4.156(a).

The mesh equations in the two loops are

$$-15 + 10i_1 - 5i + 5(i_1 - i_2) = 0$$

i.e., $-15i_1 + 5i_2 + 5i + 15 = 0$

and $20i_2 + 5(i_2 - i_1) = 0$

i.e. $5i_1 - 25i_2 = 0$

$\therefore i_1 = 5i_2$

Also $i = i_1 - i_2$

Hence $-15(5i_2) + 5i_2 + 5(i_1 - i_2) + 15 = 0$

With $i_1 = 5i_2$ we get

$$i_2 = 0.3 \text{ A } (= i_{sh})$$

$\therefore R_i = \frac{V_{ab}}{i_2} = \frac{7.5}{0.3} = 25 \Omega$

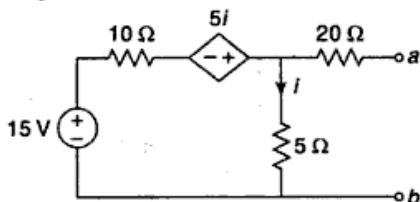


Fig. 4.156 Circuit of Ex. 4.125

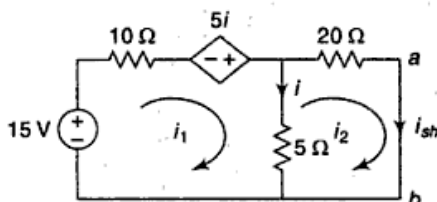


Fig. 4.156(a) Determination of R_i

According to the maximum power transfer theorem maximum power will be transferred across ab when the resistance connected across ab is equal to R_i i.e., 25Ω .

4.126

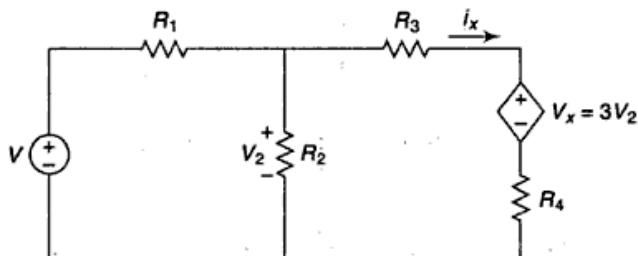


Fig. 4.157 Circuit of Ex. 4.126

[Given: $R_1 = 4 \Omega$, $R_2 = 6 \Omega$; $R_3 = 2 \Omega$; $R_4 = 10 \Omega$, $V = 9 \text{ V}$.]

In the circuit shown in Fig. 4.157, find i_x .

Solution

Let us first simplify the circuit by clubbing R_3 with R_4 to get $R (= R_3 + R_4)$ in the right loop (loop 2) in the given circuit. The simplified circuit is shown in Fig. 4.157(a).

In loop 2, $V_2 + V_x = i_x R = 12i_x$

or $V_2 + 3V_2 = 12i_x$

$\therefore V_2 = 3i_x$

(1)

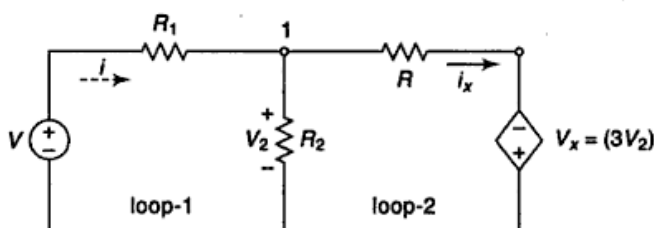


Fig. 4.157(a) Simplified circuit

Again at loop 1,

$$V - iR_1 = V_2 \quad [\text{assuming current 'i' passing through } R_1]$$

Using (1)

$$V - 4i = 3i_x \quad (2)$$

But

$$i = i_x + \frac{V_2}{6} \quad [\text{applying KCL at node 1}]$$

$$= i_x + \frac{3i_x}{6} \quad [\text{using (1)}]$$

$$= 1.5i_x$$

From (2) we then get

$$V - 4 \times 1.5i_x = 3i_x$$

or

$$V = 9i_x$$

$$\therefore i_x = \frac{V}{9} = \frac{9}{9} = 1 \text{ A.}$$

.....

4.127. In the circuit shown in Fig. 4.158, find i_o assuming $\beta = 8$. Use the superposition principle.

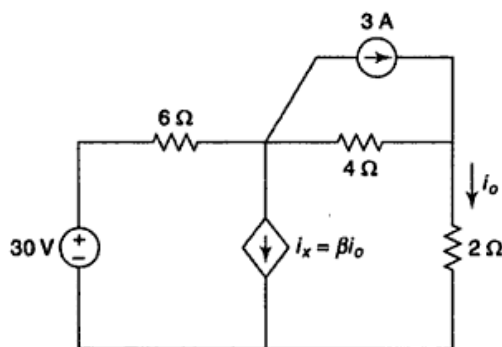


Fig. 4.158 Circuit of Ex. 4.127

Solution

First we take the 30 V source [Ref. Fig. 4.158(a)]

Here,

$$i_1 = i_x + i_{o1} = 9i_{o1}$$

In loop abcde, $-30 + 6 \times 9i_{o1} + (4 + 2) i_{o1} = 0$

$$\therefore i_{o1} = \frac{1}{2} \text{ A} = 0.5 \text{ A}$$

Next we consider the 3 A constant current source. [Ref. 4.158(b)].

(1)

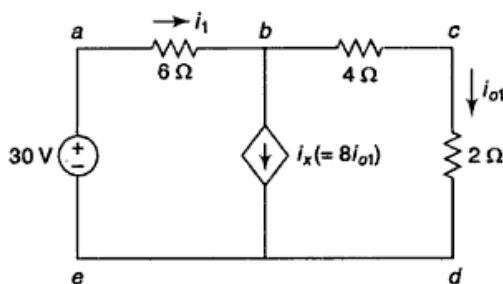


Fig. 4.158(a) 30 V source acting alone

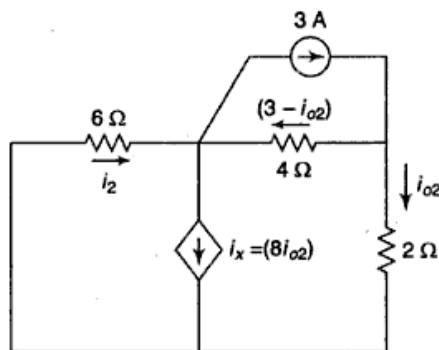


Fig. 4.158(b) 3 A source acting alone

Current through the $4\ \Omega$ resistor is $(3 - i_{o2})$ A, and current through the $6\ \Omega$ resistor is $i_2 = 9 i_{o2}$.

\therefore We can write from loop equation,

$$i_2 \times 6 - (3 - i_{o2}) \times 4 + i_{o2} \times 2 = 0$$

as $6 \times 9i_{o2} - 12 + 6i_{o2} = 0 \quad \therefore i_{o2} = (\text{since } i_2 = 9i_{o2}) \text{ A.}$

Then using superposition principle

$$i_0 = i_{o1} + i_{o2} = 0.5 + 0.2 = 0.7 \text{ A}$$

.....

4.128 In the circuit shown in Fig. 4.159, find I .

.....

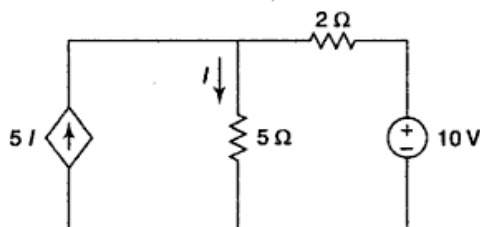


Fig. 4.159 Circuit of Ex. 4.128

Solution

We redraw the circuit with arbitrary current distribution and node number [Fig. 4.159(a)]

At node (x),

$$\begin{aligned} 5I &= I + I_2 \\ &= \frac{V}{5} + \frac{V - 10}{2} \end{aligned}$$

[Assuming voltage at node x to be (V)]

$$\therefore 5I = \frac{7V - 50}{10}$$

$$\text{or } 50I = 7V - 50 \quad (1)$$

$$\text{But } I = \frac{V}{5}$$

$$\therefore \text{From (1), } 10V = 7V - 50$$

$$\text{or } V = -\frac{50}{3} = -16.67 \text{ V}$$

$$\text{Thus } I = \frac{V}{5} = -\frac{16.67}{5} = -3.34 \text{ A}$$

The actual current I is directed upwards (i.e., towards x from y) in Fig. 4.159(a).

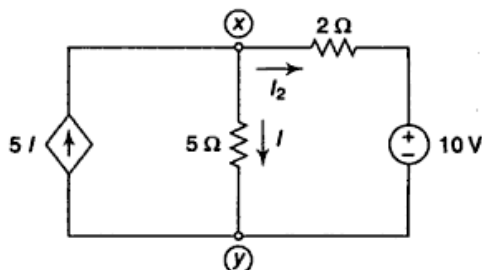


Fig. 4.159(a) Circuit of Ex. 4.128 redrawn with currents and nodes designated

4.129 In the network shown in Fig. 4.160, find the value of the dependent source using (i) nodal method and (ii) superposition theorem.

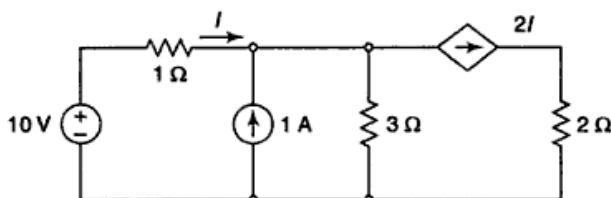


Fig. 4.160 Circuit of Ex. 4.129

Solution

Using nodal method: We first redraw the figure and assign a node (x) for application of nodal method (Fig. 4.160(a))

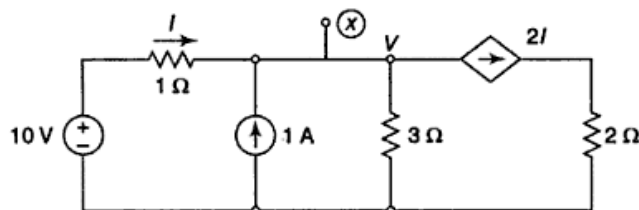


Fig. 4.160(a) Solution by nodal method

$$\text{At the node (x), we have, } \frac{10 - V}{1} + 1 = \frac{V}{3} + 2I$$

[(V) being the node voltage at (x)]

Since $I = \frac{10-V}{1}$, we can write, $\frac{10-V}{1} + 1 = \frac{V}{3} + 2\left(\frac{10-V}{1}\right)$

Simplification yields $V = 13.5$ V.

Thus, $I = \frac{10-13.5}{1} = -3.5$ and the dependent source would have value $2I$, i.e., $2 \times (-3.5)$ i.e., -7 A.

It may be noted here that the actual direction of the currents I and $2I$ would be just the reverse than given in the question.

Using Superposition Theorem

Let us first assume the 10 V source only (Fig. 4.160(b)).

At node (a), we find

$$\frac{10-V}{1} = \frac{V}{3} + 2\left(\frac{10-V}{1}\right)$$

Simplifying,

$$V = 15 \text{ Volts (at node } a)$$

$$\therefore I_1 = \frac{10-V}{1} = \frac{10-15}{1} = -5 \text{ A}$$

while

$$2I_1 = -10 \text{ A}$$

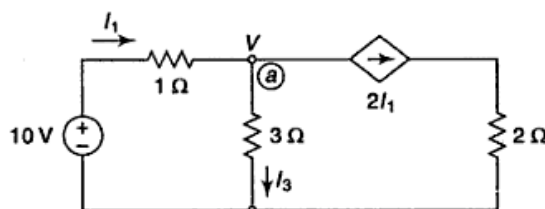


Fig. 4.160(b) Solution by superposition method (10 V source acting only)

Next we consider the constant current source 1 A only (Fig. 4.160(c)).

We select node (b) where we find

$$1 + I_2 = \frac{V}{3} + 2I_2$$

$$\text{or } \frac{V}{3} + I_2 = 1 \quad (i)$$

$$\text{But } I_2 = \frac{-V}{1} \quad (ii)$$

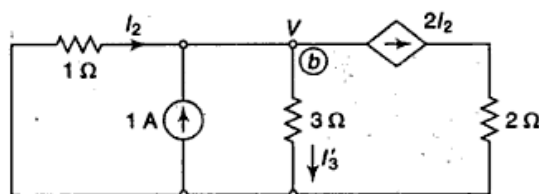


Fig. 4.160(c) 1 A source acting only

Using (ii) in (i), we get,

$$\frac{V}{3} - V = 1, \text{ i.e., } V = -1.5 \text{ V.}$$

$$\therefore I_2 = 1.5 \text{ A; } 2I_2 = 3 \text{ A.}$$

Finally, using the principle of superposition, we get

$$2I = 2I_1 + 2I_2 = -10 + 3 = -7 \text{ A}$$

(the same result that we obtained earlier).

4.130 Find Thevenin's equivalent for the given circuit in Fig. 4.161.

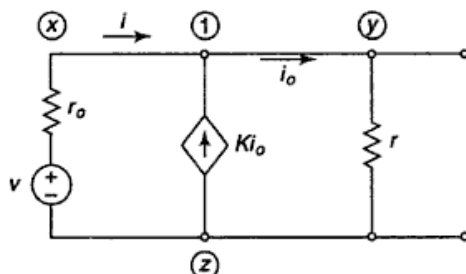


Fig. 4.161 Circuit of Ex. 4.130

Solution

At node $\frac{\infty}{7}$, we can write,

$$i + K i_o = i_o$$

$$i = i_o (1 - K)$$

Also, in loop $x - 1 - y - z$ we can write

$$-v + i r_o + i_o r = 0$$

$$\text{or } v = r_o i_o (1 - K) + i_o r \quad [\text{using } i = i_o (1 - K) \text{ for } i]$$

$$= i_o [r_o (1 - K) + r]$$

$$\therefore i_o = \frac{v}{r_o (1 - K) + r}$$

$$\text{Hence } V_{oc} = i_o \times r = \frac{v \times r}{r_o (1 - K) + r}$$

Let us now short the output terminals. Resistance r is bypassed [Fig. 4.161(a)]

$$\text{Here, } -v + i r_o = 0$$

$$\text{or } i = \frac{v}{r_o}$$

$$\text{However, } i = i_{sc} - K i_{sc}, \text{ at node } \frac{\infty}{7}$$

$$\text{or } \frac{v}{r_o} = i_{sc} (1 - K)$$

$$\therefore i_{sc} = \frac{v}{r_o (1 - K)}$$

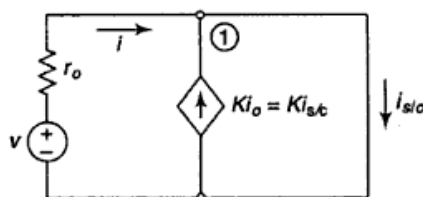


Fig. 4.161(a) Determination of i_{sc}

$$\therefore z_{Th} (\text{Thevenin equivalent impedance}) = \frac{V_{oc}}{i_{sc}}$$

$$\begin{aligned}
 &= \frac{v \times r}{r_o(1-K) + r} \bigg/ \frac{v}{r_o(1-K)} \\
 &= \frac{r \times r_o(1-K)}{r + r_o(1-K)}.
 \end{aligned}$$

Thus, for the given circuit,

$$V_{o/c} = \frac{v \times r}{r_o(1-K) + r}; Z_{th} = \frac{r \times r_o(1-K)}{r + r_o(1-K)}.$$

4.131 Obtain the values of I_1 , I_2 and I_3 in the circuit shown in Fig. 4.162.

Solution

In loop (X), the circulating current will be driven by 5 A constant current source and hence $I_3 = 5$ A.

In loop (Y), we write

$$(I_1 - I_3) 4 + 3I - 12 = 0 \quad (i)$$

But $I = I_2 - I_3$ (in loop (Z))

$$\therefore \text{From (i), } (I_1 - I_3) 4 + 3(I_2 - I_3) - 12 = 0$$

$$\text{or } 4I_1 + 3I_2 - 7I_3 = 12 \quad (ia)$$

Since $I_3 = 5$ A, equation (1a) gives

$$4I_1 + 3I_2 - 7 \times 5 = 12$$

$$\text{or } 4I_1 + 3I_2 = 47 \quad (ii)$$

For loop (Z), we write

$$1 \times I + 6 - 3I = 0 \quad \text{or, } I = 3 \text{ A}$$

Using $I = 3$ A, $I = I_2 - I_3$, we get

$$I_2 - I_3 = 3 \quad \text{or, } I_2 = I_3 + 3 = 8 \text{ A} \quad (\because I_3 = 5 \text{ A})$$

$$\text{Thus from (ii), } 4I_1 = 47 - 3I_2 = 23 \text{ A}$$

$$\text{or } I_1 = 5.75 \text{ A}$$

$$\text{Thus finally, } I_1 = 5.75 \text{ A, } I_2 = 8 \text{ A, } I_3 = 5 \text{ A.}$$

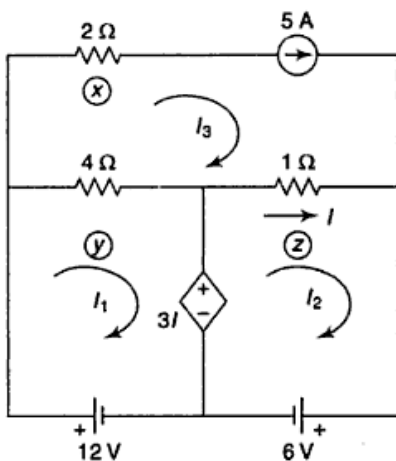


Fig. 4.162 Circuit of Ex. 4.131

4.132 Find v_a and v_b using the principle of superposition in Fig. 4.163.

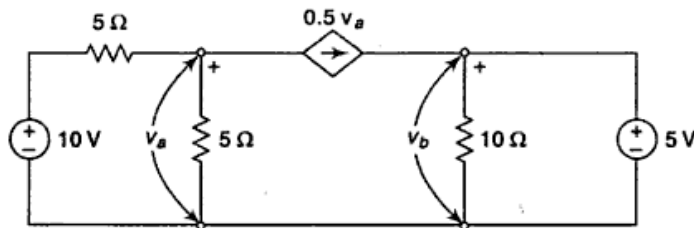


Fig. 4.163 Circuit of Ex. 4.132

Solution

Let us first take 10 V source (Fig. 4.163(a)). It may be observed that the 10 ohm resistor is shorted due to deactivation of the 5 V source.

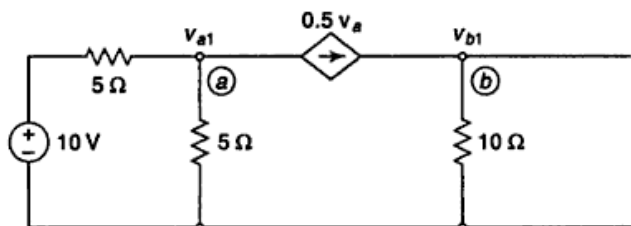


Fig. 4.163(a) 10 V source acting alone

At node (a), we have

$$\frac{10 - v_{a1}}{5} = \frac{v_{a1}}{5} + 0.5 v_{a1}$$

$$\text{or} \quad 2 - \frac{v_{a1}}{5} = \frac{v_{a1}}{5} + 0.5 v_{a1}$$

$$\text{or} \quad 0.9 v_{a1} = 2$$

$$\therefore v_{a1} = \frac{2}{0.9} = \frac{20}{9} \text{ V}$$

$$\text{Obviously} \quad v_{b1} = 0.$$

Next, we deactivate the 10 V source and activate the 5 V source. (Fig. 4.163(b))

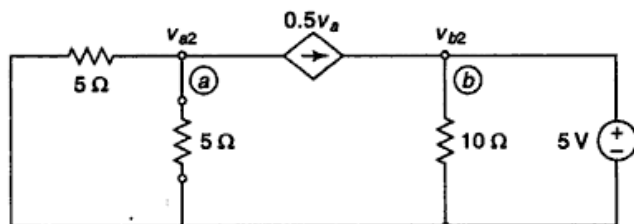


Fig. 4.163(b) 5 V source acting alone

At node (a), we have

$$\frac{v_{a2}}{5} + \frac{v_{a2}}{5} + 0.5 v_{a2} = 0$$

$$\therefore v_{a2} = 0.$$

v_{b2} is then 5 V.

Using superposition principle,

$$v_a = v_{a1} + v_{a2} = \frac{20}{9} = 2.22 \text{ V}$$

$$v_b = v_{b1} + v_{b2} = 5 \text{ V.}$$

.....

4.133 Obtain Thevenin equivalent across x-y in the network shown in Fig. 4.164.

Solution

$$V_{oc} = V_{xy} = 10(v - v_o) = v$$

$$\therefore 9v = 10v_o \quad \text{or} \quad v = \frac{10}{9}v_o$$

(i)

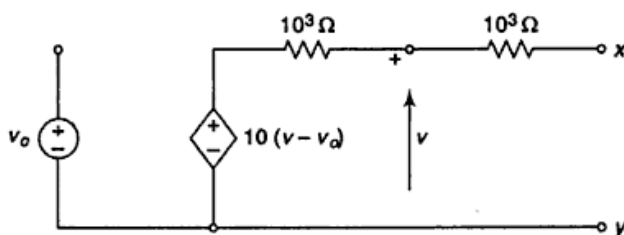


Fig. 4.164 Circuit of Ex. 4.133

Thus, $V_{oc} = V_{xy} = \frac{10}{9} v_o$

Next we short terminals x-y. (Fig. 4.164(a)).

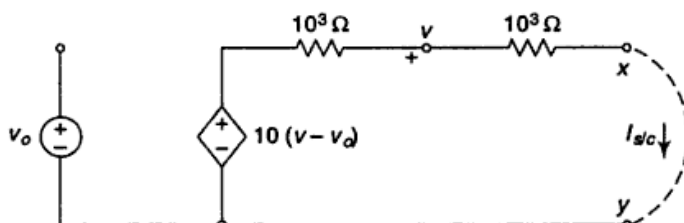


Fig. 4.164(a) Network of Fig. 4.164 with (x-y) shorted

Here,

$$10(v - v_o) = 10^3 \times 2 \times I_{sc}$$

$$\therefore I_{sc} = \frac{10(v - v_o)}{2 \times 10^3} = \frac{v - v_o}{200} \quad \text{(ii)}$$

$$\text{Also, } v = 10^3 \times I_{sc} = 1000 I_{sc} \quad \text{(iii)}$$

Using (iii) in (ii) we get

$$I_{sc} = \frac{1000 I_{sc} - v_o}{200} = 5 I_{sc} - \frac{v_o}{200}$$

$$\therefore 4 I_{sc} = \frac{v_o}{200}, \text{ i.e., } I_{sc} = \frac{v_o}{200} \times \frac{1}{4}$$

We now obtain the internal resistance of the circuit as

$$R_{int} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{10}{9} v_o}{\frac{v_o}{800}} = \frac{10}{9} \times 800 = 888.89 \, \Omega$$

The Thevenin's equivalent circuit is thus obtained as

$$V_{oc} = \frac{10}{9} v_o; R_{int} = 888.89 \, \Omega.$$

4.134 In the network shown in Fig. 4.165 find I using Thevenin theorem and verify the result using Norton's theorem.

Solution

Let us first remove $1 \, \Omega$ resistor from the given network. With reference to Fig. 5.165(a), we can write, $-10 + V_{oc} + V_1 = 0$

$$\therefore V_{oc} = 10 - V_1$$

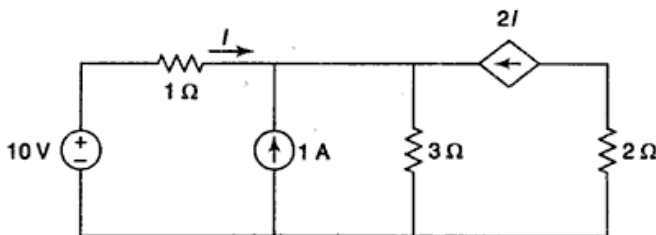
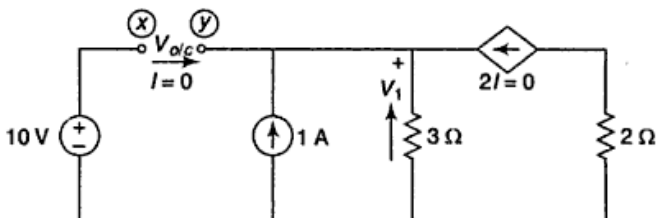


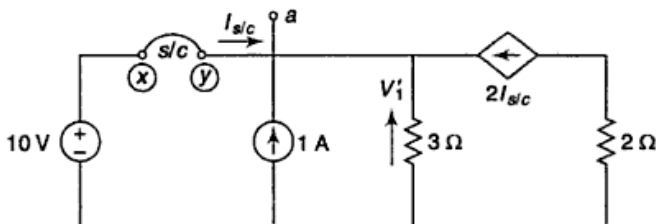
Fig. 4.165 Circuit of Ex. 4.165

Fig. 4.165(a) Determination of $V_{O/c}$

By inspection, $V_1 = 1 \text{ A} \times 3 \Omega = 3 \text{ V}$.

$\therefore V_{o/c} = 7 \text{ V}$.

Next, we short terminals (x)-(y) [Ref Fig. 4.165(b)]

Fig. 4.165(b) Determination of $I_{s/c}$

By inspection, $V_1' = 10 \text{ V}$.

At node a , we can write

$$I_{s/c} + 1 = \frac{10}{3} - 2 I_{s/c} \text{ i.e., } I_{s/c} = \frac{7}{9} \text{ A}$$

Thus, the internal resistance of the circuit is

$$R_{\text{int}} = \frac{V_{o/c}}{I_{s/c}} = \frac{7}{(7/9)} = 9 \Omega.$$

We now draw both Thevenin's and Norton's equivalent circuits. (Fig. 4.165(c) and 4.165(d) respectively).

In Fig. 4.165(c),

$$I = \frac{V_{o/c}}{R_{\text{int}} + 1} = \frac{7}{9 + 1} = 0.7 \text{ A}$$

Thus we have obtained current in 1Ω resistor by Thevenin's theorem which is 0.7 A .

4.136 In the network shown in Fig. 4.167, verify, using Thevenin theorem

$$V_{oc} = \frac{V r_1}{r_1 + r_2 + r_3}$$

$$I_{sc} = \frac{V}{r_2 - r_3 (\alpha - 1)}$$

$$z_{th} = \frac{r_1 [r_2 - r_3 (\alpha - 1)]}{r_1 + r_2 + r_3}$$

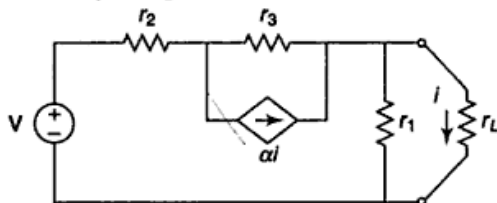


Fig. 4.167 Circuit of Ex. 4.136

Solution

With (r_L) opened, $i = 0$. This makes source $\alpha i = 0$.

$\therefore V_{oc}$ (i.e., voltage across open circuited output after removing r_L) is given by

$$V_{oc} = \frac{r_1 \times V}{r_1 + r_2 + r_3}$$

Next we apply short across the output so that (r_L) and r_1 are shorted [Fig. 4.167(a)].

\therefore Current through r_2 is i_{sc} ; current through r_3 is $(i_{sc} - \alpha i_{sc})$. Use of KVL in this loop gives

$$-V + i_{sc} r_2 + (i_{sc} - \alpha i_{sc}) r_3 = 0$$

$$\text{or } V = i_{sc} (r_2 + r_3 - \alpha r_3)$$

$$\therefore i_{sc} = \frac{V}{r_2 + r_3 - \alpha r_3} = \frac{V}{r_2 - r_3 (\alpha - 1)}$$

$$\text{and } z_{Th} = \frac{V_{oc}}{i_{sc}} = \frac{r_1 \times V}{r_1 + r_2 + r_3} \div \frac{V}{r_2 - r_3 (\alpha - 1)}$$

$$= \frac{r_1 [r_2 - r_3 (\alpha - 1)]}{(r_1 + r_2 + r_3)}$$

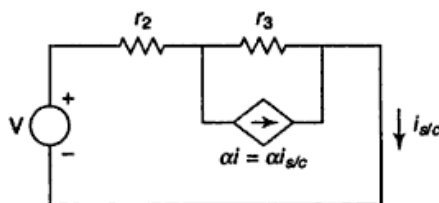


Fig. 4.167(a) Determination of (i_{sc}) and (Z_{Th})

4.137 In the network shown in Fig. 4.168, find the current through R_L . Assume $V = 5$ V.

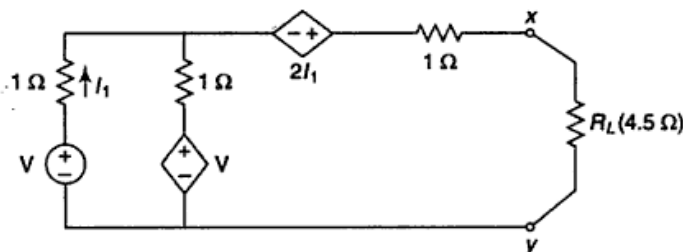


Fig. 4.168 Circuit of Ex. 4.137

Solution



Let us remove R_L from x-y terminals. In Fig. 4.168(a), in loop $abcd$,

$$-V + I_1 \times 1 + I_1 \times 1 + V = 0$$

$$\text{or } I_1 = 0.$$

$$\text{Also, } 2I_1 = 0.$$

$$\therefore V = V_{oc}$$

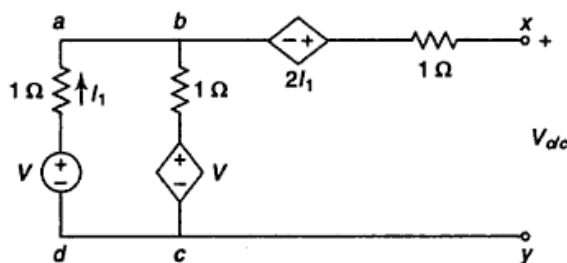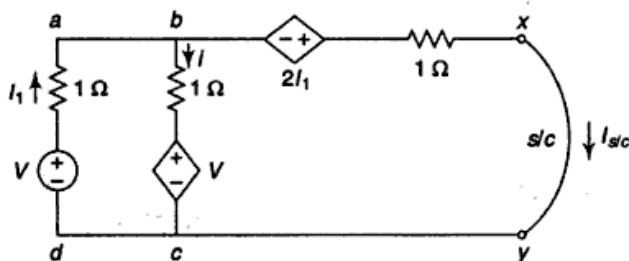Fig. 4.168(a) Determination of (V_{olc}) Fig. 4.168(b) Determination of I_{slc}

Next, we short terminal x-y (Fig. 4.168(b))

At node b,

$$I_1 = i + I_{slc}$$

$$i = I_1 - I_{slc}$$

Again in loop abxy cda we have

$$-V + 1 \times I_1 - 2I_1 + 1 \times I_{slc} = 0$$

$$\therefore I_{slc} = I_1 + V.$$

Also, in loop abcd

$$-V + 1 \times I_1 + 1 \times i + V = 0$$

$$\text{or } I_1 + (I_1 - I_{slc}) = 0$$

$$\text{or } 2I_1 - I_{slc} = 0$$


$$\therefore I_{slc} = 2I_1 = 2(I_{slc} - V) \quad [\because I_{slc} = I_1 + V]$$

$$\text{i.e., } I_{slc} = 2V.$$

Next, we find the internal resistance as

$$R_{int} = \frac{V_{olc}}{I_{slc}} = \frac{V}{2V} = \frac{1}{2} \Omega (= 0.5 \Omega)$$

The Thevenin's equivalent circuit can now be drawn as shown in Fig. 4.168(c).

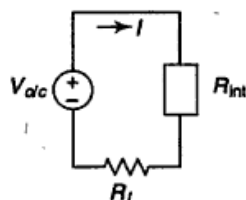Fig. 4.168(c) Determination of V_{olc}

$$\begin{aligned} \text{Here } I &= \frac{V_{olc}}{R_{int} + R_L} = \frac{5}{4.5 + 0.5} \\ &= 1 \text{ A.} \end{aligned}$$

Thus, the current through 4.5Ω resistor in the given circuit is 1 A.

.....

4.138 Find (I) using Thevenin's theorem and find the value of R_L to have maximum power transfer from source (Fig. 4.169). Also find the maximum value of power transfer.

Solution

Let V_x be the voltage at node $\frac{\infty}{7}$ when we remove R_L from the given circuit. The circuit is redrawn in Fig. 4.169 (a). Using node analysis at node $\frac{\infty}{7}$ we get

$$\frac{V_x - 10}{2} + 2 + 1 + \frac{V_x - V_{olc}}{1} = 0$$

or $1.5 V_x - V_{olc} = 2 \quad (1)$

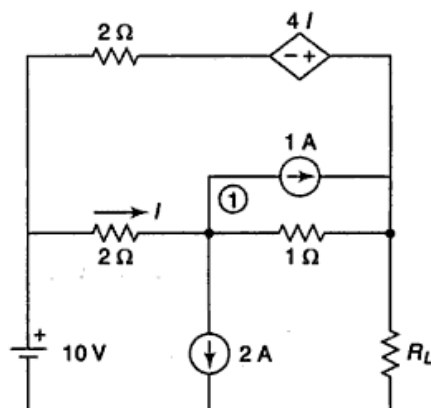


Fig. 4.169 Circuit of Ex. 4.138

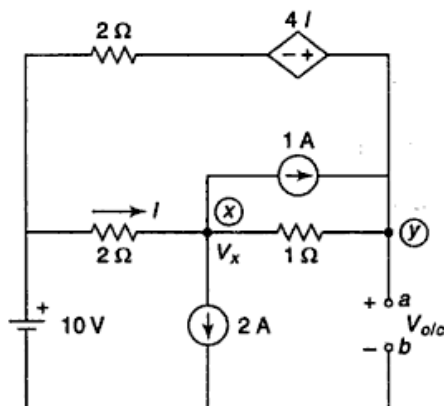


Fig. 4.169(a) Determination of V_{olc}

Again, using nodal analysis at node (y) we get

$$\frac{V_{olc} - V_x}{1} + \frac{V_{olc} - 4I - 10}{2} - 1 = 0$$

or $1.5 V_{olc} - V_x - 2I = 6;$

$$\text{But } I = \frac{10 - V_x}{2}.$$

Hence we can write

$$1.5 V_{olc} - V_x - 2 \cdot \frac{10 - V_x}{2} = 6$$


or $1.5 V_{olc} - V_x - 10 + V_x = 6$

or $V_{olc} = 10.67 \text{ V. and } V_x = 8.44 \text{ V.}$

Next we short the terminals $a-b$ in Fig. 4.169(b). Let the voltage at node $\frac{\infty}{7}$ be V . Using nodal method at node $\frac{\infty}{7}$ we can write,

$$\frac{V - 10}{2} + 1 + \frac{V}{1} + 2 = 0.$$

or $1.5 V = 2$ or, $V = 1.33 \text{ V.}$

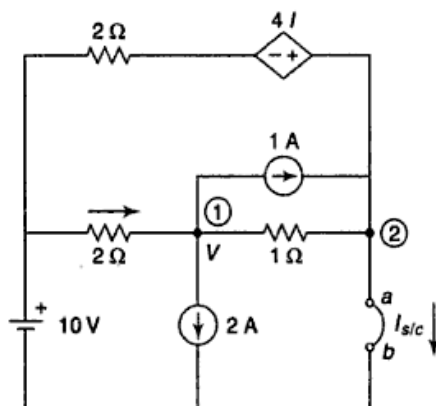Fig. 4.169(b) Determination of ($I_{s/c}$)

Next we use the nodal method at shorted node ②. Here we get

$$\frac{0-V}{1} + I_{s/c} + \frac{0-4I-10}{2} - 1 = 0$$

$$\text{or} \quad -V + I_{s/c} - 2I - 5 - 1 = 0$$

$$\therefore I_{s/c} = 6 + 2I + V$$

$$\text{But} \quad I = \frac{10-V}{2}$$

$$\therefore I_{s/c} = 6 + 2 \cdot \frac{10-V}{2} + V = 16 \text{ A}$$

$$\text{Hence} \quad R_{Th} = \frac{V_{o/c}}{I_{s/c}} = \frac{10.67}{16} \\ = 0.67 \Omega.$$

It is obvious that maximum power will flow to R_L provided $R_L = R_{Th}$. Thus R_L is to 0.67Ω to have maximum power flow for source to R_L .

$$\text{Also,} \quad P_{\max} = \frac{V_{o/c}^2}{4R} = \frac{(10.67)^2}{4 \times 0.67} = 42.48 \text{ W.}$$

.....

4.139 Determine the current I in the network of Fig. 4.170 using superposition theorem.

.....

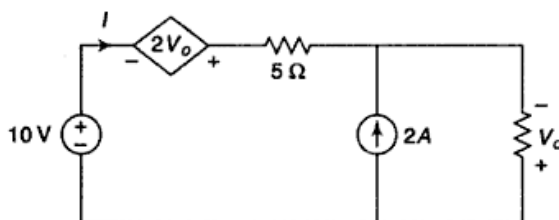


Fig. 4.170 Circuit of Ex. 4.139

Solution

Let us first assume the 10 V source only removing 2 A source as shown in Fig. 4.170(a).

Here we have

$$-10 - 2V_o + 5I' - V_o = 0 \quad (i)$$

$$\text{and } V_o = -2I' \quad (ii)$$

Using (ii) in (i), we get

$$-10 - 3(-2I') + 5I' = 0$$

$$\therefore I' = 0.91 \text{ A.}$$

Next, removing the 10 V source and connecting the 2 A current source as shown in Fig. 4.170(b), at node p ,

$$I'' + (-2) + I_{2\Omega} = 0$$

$$\text{or } \frac{-V_o - 2V_o}{5} - 2 - \frac{V_o}{2} = 0$$

$$\text{or } V_o = -\frac{20}{11} \text{ V}$$

$$\therefore I'' = \frac{-3V_o}{5} = 1.09 \text{ A}$$

$$\text{Hence, } I = I' - I'' = -0.18 \text{ A}$$

(the current flows opposite to given direction of (I) given in Fig. 4.170).

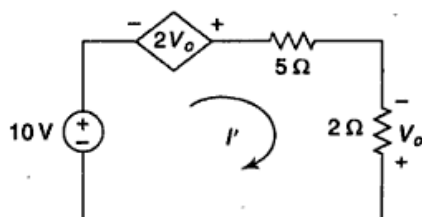


Fig. 4.170(a) 10 V source acting alone

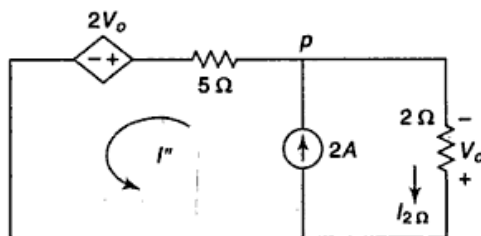


Fig. 4.170(b) 2 A current source acting alone

4.140 Find the current in the 14 Ω resistor using Thevenin's theorem in Fig. 4.171.

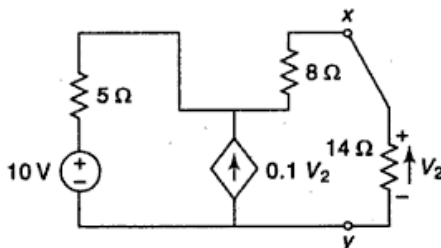


Fig. 4.171 Circuit of Ex. 4.140

Solution

Let us first open circuit x - y . See Fig. 4.171(a).


In loop $axyb$,

$$-10 - 5 \times 0.1 V_2 + V_{oc} = 0$$


$$\therefore V_{oc} = 10 + 0.5 V_2$$

$$= 10 + 0.5 V_{oc} \quad [\because V_{oc} \equiv V_2]$$

$$\therefore V_{oc} = 20 \text{ V.}$$

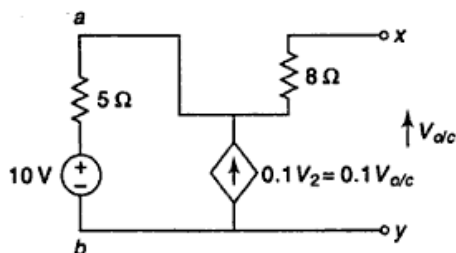Fig. 4.171(a) Determination of $V_{O/c}$

Next, when we short terminals x - y (Fig. 4.171(b)), we find $V_2 = 0$ due to short circuit, thus $0.1 V_2 = 0$.

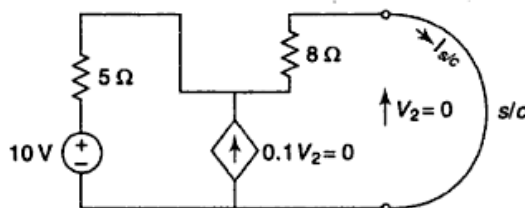Fig. 4.171(b) Determination of $I_{s/c}$

$$\therefore I_{s/c} = \frac{10}{5+8} = \frac{10}{13} \text{ A}$$

$$\begin{aligned} \therefore R_{int} &= \frac{V_{o/c}}{I_{s/c}} \\ &= \frac{20}{\frac{10}{13}} = 26 \Omega. \end{aligned}$$

From Thevenin's equivalent circuit, we can then write

$$I = \frac{V_{o/c}}{R_{int} + 14} = \frac{20}{26 + 14} = 0.5 \text{ A}$$

\therefore Current through 14 ohm resistor is 0.5 A.

■ EXERCISES ■

1. State and explain Thevenin's theorem. What are the limitations of this theorem?
2. State and prove maximum power transfer theorem.
3. State and explain Kirchhoff's voltage law and current law.
4. Distinguish between dependent and independent sources. How do you transform a voltage source into a current source?
5. Distinguish between
 - (a) Linear and non-linear elements
 - (b) Active and passive elements
 - (c) Unilateral and bilateral elements.

6. State superposition theorem and explain it.
7. State Norton's theorem and explain it.
8. Prove that under maximum power transfer condition the power transfer efficiency of the circuit is only 50%.
9. Find the equivalent resistance for the circuit shown in Fig. 4.172. [Ans: $10\ \Omega$]
10. Find R_1 and R_2 for the potential divider in Fig. 4.173 so that current I is limited to 1 A when $V_o = 20\text{ V}$.

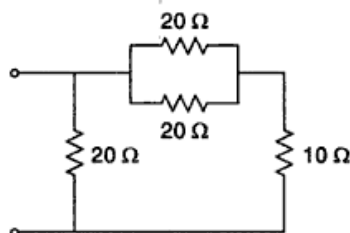


Fig. 4.172

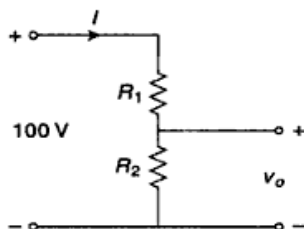
[Ans: $R_2 = 20\ \Omega$, $R_1 = 80\ \Omega$]

Fig. 4.173

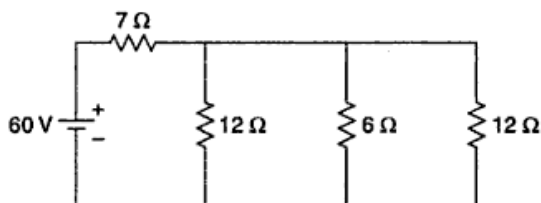


Fig. 4.174

11. Use branch currents in the network shown in Fig. 4.174 to find the current supplied by a 60 V source. [Ans: 6 A]
12. Solve problem no. 11 by mesh current method.
13. Two ammeters x and y are connected in series and a current of 20 A flows through them. The potential difference across the ammeters are 0.2 V and 0.3 V respectively. Find how the same current will divide between x and y when they are connected in parallel. [Ans: 12 A and 8 A]
14. Obtain the source current I and the power delivered to the circuit in Fig. 4.175.

[Ans: 6 A, 228 W]

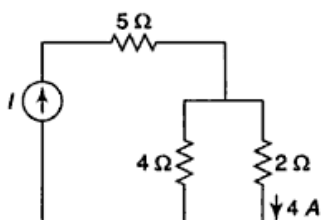
[Hint: $I_{2\Omega} = 4\text{ A}$; $V_{\text{drop}(2\Omega)} = 4 \times 2 = 8\text{ V}$;Hence $I_{4\Omega} = \frac{8}{4} = 2\text{ A}$. $\therefore I = I_{2\Omega} + I_{4\Omega} = 6\text{ A}$; $P = 6^2 \times 5 + 2^2 \times 4 + 4^2 \times 2 = 228\text{ W}$]

Fig. 4.175

15. For the circuit shown in Fig. 4.176 find the potential difference between x and y . [Ans: -2.85 V]

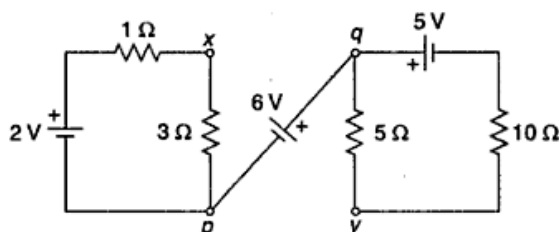


Fig. 4.176

[Hint: In left loop, $I = \frac{2}{1+3} = 0.5$ A; in right loop, $I = \frac{5}{15} = 0.33$ A.]

$$V_{x-y} = V_{xp} + (-6) + V_{py} = 0.5 \times 3 - 6 + 0.33 \times 5 = -2.85 \text{ V}$$

16. Reduce the circuit in Fig. 4.177 to a voltage source in series with a resistance between terminals A and B.

$$\left[\text{Ans: } V = \frac{90}{34} \text{ V and } R = \frac{15}{23} \Omega \right]$$

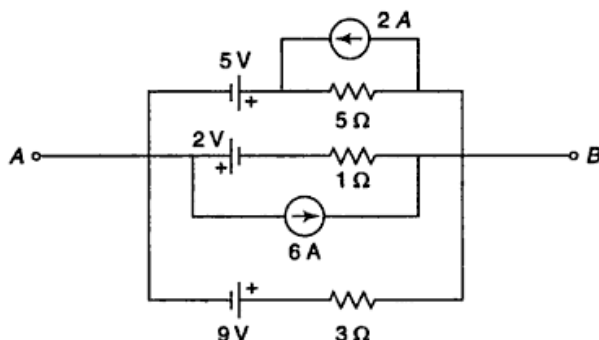


Fig. 4.177

17. For the network shown in Fig. 4.178 find V which makes $I = 7.5$ mA.

$$[\text{Ans: } 1.02 \text{ V}]$$

$$\left[I = 7.5 \text{ mA; } I_{6\Omega} = \frac{7.5 \text{ mA} \times 6 \Omega}{6 \Omega} \right]$$

$$= 7.5 \text{ mA}$$

$$\therefore I_{5\Omega} = 15 \text{ mA. Drop in } 5 \Omega = 15 \text{ mA} \times 5 \Omega = 75 \text{ mV.}$$

$$\text{Then drop across } 4 \Omega \text{ is } 75 \text{ mV} + 7.5 \text{ mA} \times 6 \Omega = 120 \text{ mV.}$$

$$\therefore I_{4\Omega} = \frac{120}{4} = 30 \text{ mA. Current from}$$

$$\text{battery is then } (30 + 15) \text{ i.e., } 45 \text{ mA. Hence voltage drop in } 8 \Omega \text{ is } 45 \text{ mA} \times 8 = 360 \text{ mV. Drop in } 12 \Omega \text{ is } 45 \text{ mA} \times 12 = 540 \text{ mV.}$$

$$\therefore V = 360 + 75 + 45 + 540 = 1020 \text{ mV. i.e., } 1.02 \text{ V}$$

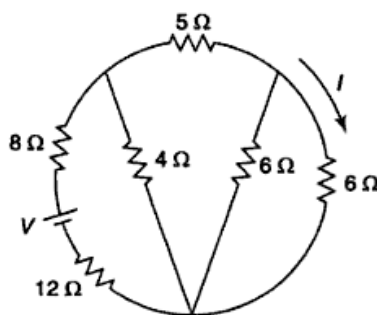


Fig. 4.178

18. In the network shown in Fig. 4.179 find the resistance between (i) A and a (ii) C and A.

$$\left[\text{Ans: (i) } 1 \Omega \text{ (ii) } \frac{7}{12} \Omega \right]$$

[Hint: Convert delta (abc) to star first and proceed]

19. For the ladder network shown in Fig. 4.180, find the applied voltage V .

$$[\text{Ans: } 800 \text{ V}]$$

[Hint: Find current through the 40Ω resistor and then proceed as shown in Problem no. 17]

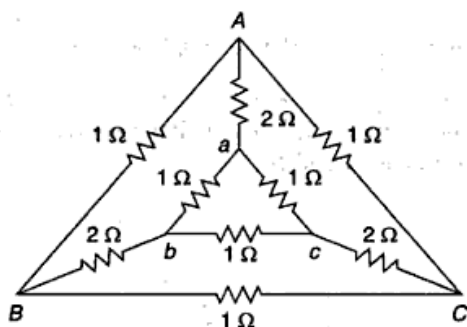


Fig. 4.179

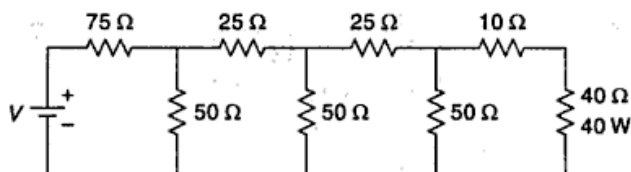


Fig. 4.180

20. Find the current in the $10\ \Omega$ resistance in the network shown in Fig. 4.181 using Thevenin's theorem. [Ans: 4 A]

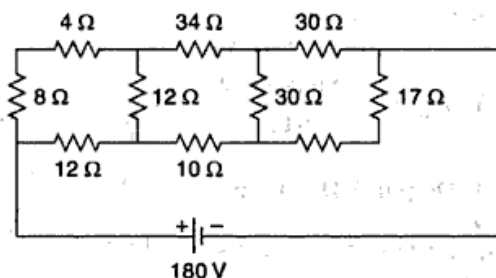


Fig. 4.181

21. Using Norton's theorem find the current through $64\ \Omega$ resistance in the circuit shown in Fig. 4.182. [Ans: 0.3 A from A to B]

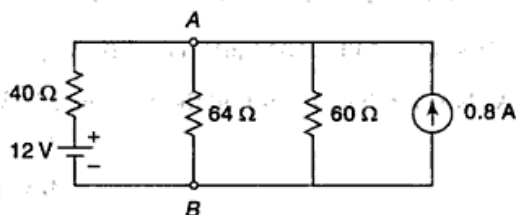


Fig. 4.182

22. In the circuit shown in Fig. 4.183 find the value of R_L so that it abstracts maximum power and also calculate that power. What percentage of power delivered by the battery reached R_L ? [Ans: $25\ \Omega$, 900 W, 35.7%]

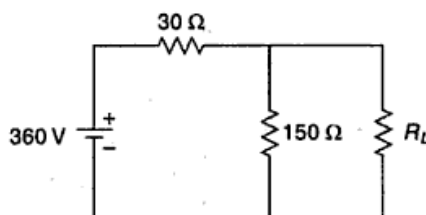


Fig. 4.183

23. In the network shown in Fig. 4.184, find Thevenin's equivalent network across $x - y$ terminals. [Ans: $V_{oc} = V_{x-y} = 25$ V; $R_{Th} = 17$ Ω]

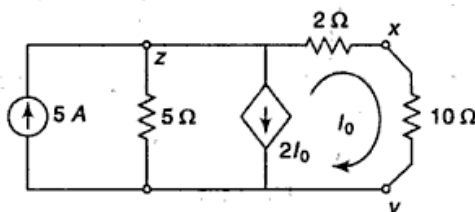


Fig. 4.184

[Hint: $10\ \Omega$ resistor is removed. $V_{oc} = 5\text{ A} \times 5\ \Omega = 25$ V. Next $x - y$ is shorted. At node z , we can write

$$5 = \frac{V}{5} + 2I_{sc} + I_{sc}; \text{ But } I_{sc} = \frac{V}{2} \text{ (V being the voltage at node z).}$$

$$\therefore I_{sc} = 1.47\text{ A and } R_{Th} = \frac{V_{oc}}{I_{sc}} = 17\ \Omega]$$

24. In the circuit shown in Fig. 4.185 use loop analysis to determine the loop currents i_1 , i_2 and i_3 .

$$[\text{Ans: } i_1 = -\frac{1}{11}\text{ A, } i_2 = \frac{10}{11}\text{ A, } i_3 = \frac{2}{11}\text{ A}]$$

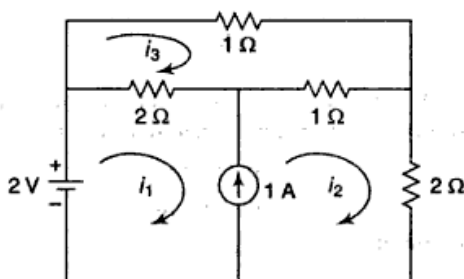


Fig. 4.185

25. Find the Thevenin's equivalent circuit at terminals A, B for the network shown in Fig. 4.186. [Ans: $V_{Th} = 25$ V, $R_{Th} = 20\ \Omega$]
 26. Find V_1 and V_2 in Fig. 4.187 using nodal voltages analysis method. [Ans: $V_1 = 2.468$ V and $V_2 = 1.156$ V]

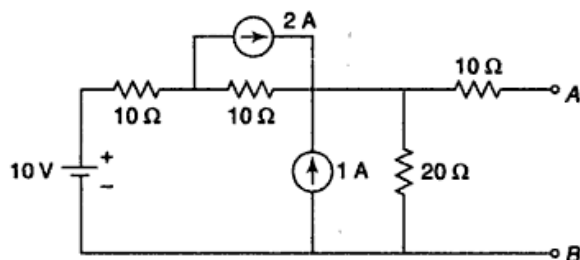


Fig. 4.186

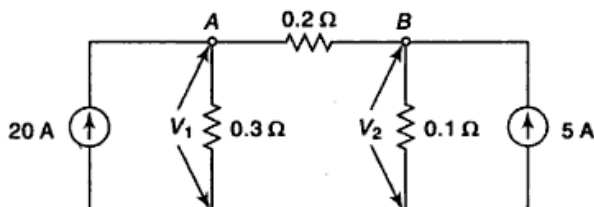


Fig. 4.187

[Hint: At node A, $20 = \frac{V_1}{0.3} + \frac{V_1 - V_2}{0.2}$; At node B, $5 = \frac{V_2}{0.1} + \frac{V_2 - V_1}{0.2}$].

27. Find the current through the resistance R in Fig. 4.188 by nodal voltage analysis. [Ans: 0 A]

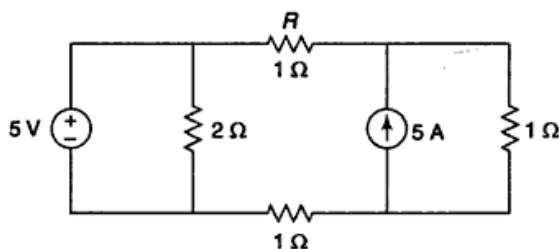


Fig. 4.188

28. In the network shown in Fig. 4.189 show that the internal impedance of the network when looked into it through terminals 1-2 is

$$z_{\text{int}} = \frac{r_1 r_2 (1-m)}{r_2 + r_1 (1-m)}$$

Apply Thevenin's theorem.

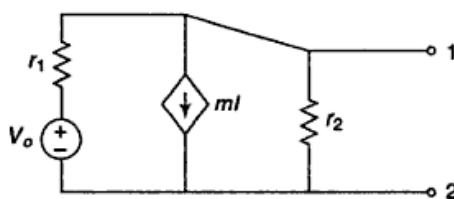


Fig. 4.189

29. Obtain Thevenin's equivalent with respect to terminals A and B of the network shown in Fig. 4.190. [Ans: $V_{Th} = 10.637 \text{ V}$, $R_{Th} = 2.182 \Omega$]

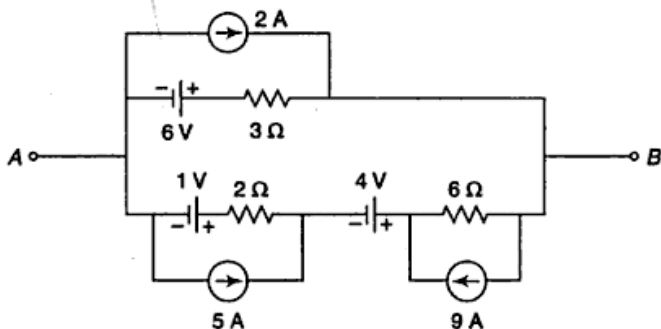


Fig. 4.190

30. Determine the value of R_L for maximum power transfer to the load and determine the load power in the circuit shown in Fig. 4.191.

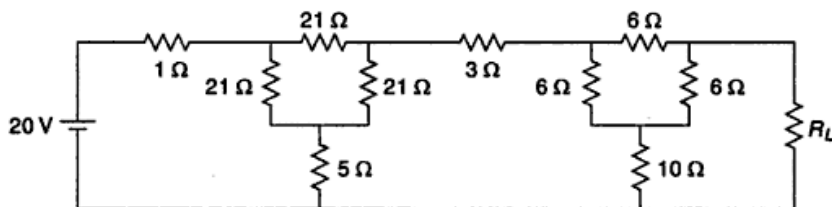
[Ans: 9Ω , 0.694 W]

Fig. 4.191

31. Using superposition theorem find the value of V_x in the circuit shown in Fig. 4.192.

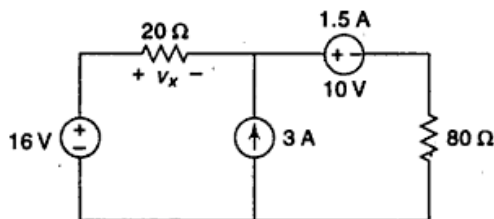
[Ans: -46.8 V]

Fig. 4.192

32. Determine Thevenin's equivalent circuit as viewed from the open circuit terminals a and b of the network shown in Fig. 4.193. [Ans: 3 V , 5Ω]

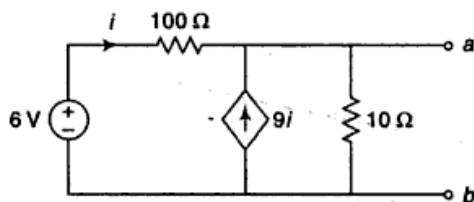


Fig. 4.193

33. Find i_0 , i_2 and the value of the dependent source for the network shown in Fig. 4.194. [Ans: 2 A, -4 A ; 4 A]

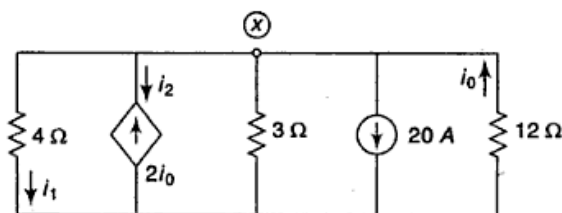


Fig. 4.194

[Hint: At node x , assuming node voltage to be v , we have, $\frac{v}{4} + \frac{v}{3} + \frac{v}{12} + 20 = 2i_0$

However, $-i_0 = \frac{v}{12}$ A.

$\therefore v = -24$ V and $i_1 = \frac{v}{4} = -6$ A; $i_0 = -\frac{v}{12} = 2$ A.

Value of dependent source is 4 A.

$i_2 = -2i_0 = -4$ A.]

34. Find the current in the $6\ \Omega$ resistor of Fig. 4.195 using Thevenin's theorem. [Ans: 1 A]

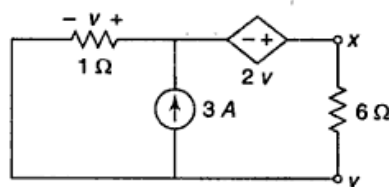


Fig. 4.195

35. Find the loop currents i_1 , i_2 and i_3 in the network shown in Fig. 4.196 by mesh method.

[Ans: $i_1 = \frac{29}{17}$ A, $i_2 = \frac{11}{17}$ A, $i_3 = \frac{57}{17}$ A]

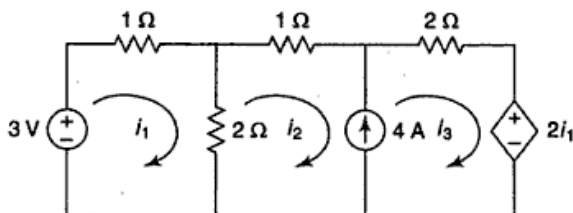


Fig. 4.196

36. What is the power supplied by the dependent source in the circuit of Fig. 4.197.

[Ans: -84 W]

[Hint: In the right loop, $-5 - V_0 + 2i + 2V_0 = 0$ $\therefore V_0 + 2i = 5$.

But $V_0 = -(i + 1) \times 1 = -i - 1$

Solving, $i = 6$ A and $V_0 = -7$ V

\therefore Power supplied by the dependent source is $2V_0 \times i = -84$ W]

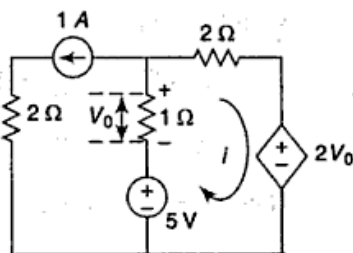


Fig. 4.197

37. Find Norton's equivalent circuit of the network shown in Fig. 4.198.

[Ans: 1.17 A, 6 Ω]

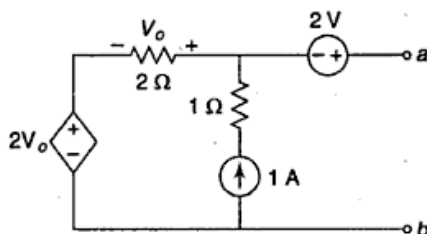


Fig. 4.198

38. Using Norton's theorem find the current in the 5 Ω resistor in the network shown in Fig. 4.199.

[Ans: 4.166 A]

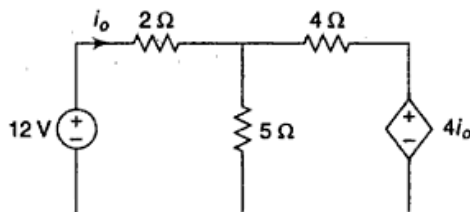


Fig. 4.199

39. In the circuit of Fig. 4.200, if $r = 5$ Ω , $R_L = 10$ Ω , $v_o = 10$ V, $i_o = 2$ A, find the current through R_L using Thevenin's theorem.

[Ans: 1.33 A]

[Hint: R_L is removed.

$$V_{oc} = i_o \times r + v_o = 20 \text{ V}$$

$$R_{Th} = 5 \Omega (= r)$$

$$\therefore I_{R_L} = \frac{V_{oc}}{R_{Th} + R_L} = 1.33 \text{ A}]$$

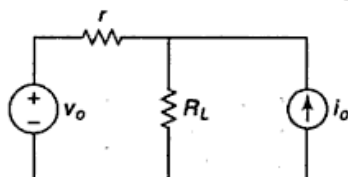


Fig. 4.200

40. Find v by superposition theorem (Fig. 4.201).

[Ans: $v = 23.37$ V]

[Hint: With 10 V source only,

$$v_1 = 10 \times i = 10 \times \frac{10}{5+10} = 6.67 \text{ V}$$

With 5 A source only,

$$i_{10} = 5 \times \frac{5}{5+10} = 1.67 \text{ A}$$

$$\therefore v_2 = 1.67 \times 10 = 16.7 \text{ V}$$

$$\text{Thus, } v = v_1 + v_2 = 23.37 \text{ V}$$

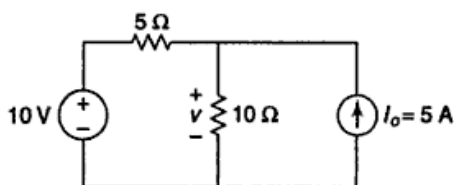


Fig. 4.201

41. The galvanometer in Fig. 4.202 has a resistance of 5Ω . Find the current through the galvanometer using Thevenin's theorem. [Ans: 15.9 mA]

[Hint: Open circuiting BD , current through 10Ω resistor]

$$I_1 = \frac{10}{10+15} \text{ A} = 0.4 \text{ A.}$$

Current through the 12Ω resistor

$$I_2 = \frac{10}{12+16} \text{ A} = 0.357 \text{ A.}$$

$$V_{Th} = V_{BD} = V_{AD} - V_{AB} = 12 \times 0.357 - 10 \times 0.4 = 0.284 \text{ V}$$

$$R_{Th} = \frac{10 \times 15}{10+15} + \frac{12 \times 16}{12+16} = 12.857 \Omega.$$

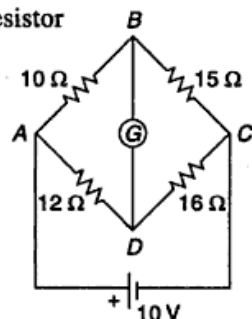


Fig. 4.202

$$\text{Current through galvanometer} = \frac{0.284}{12.857 + 5} \text{ A} = 0.0159 \text{ A [B to D]}$$

42. For the electrical network shown in Fig. 4.203 find the value of load resistance R_L for which source will supply maximum power to the load. Find also the maximum power. [Ans: 8 W]

$$\left[\text{Hint: } R_L = \frac{6 \times 3}{6+3} \Omega = \frac{18}{9} \Omega = 2 \Omega \right. \\ \left. (= R_{int}) \right]$$

$$\therefore I_L = \frac{12}{3 + \frac{6 \times 2}{6+2}} \times \frac{6}{6+2} = 2 \text{ A}$$

$$P_{max} = (2)^2 \times 2 \text{ W} = 8 \text{ W}$$

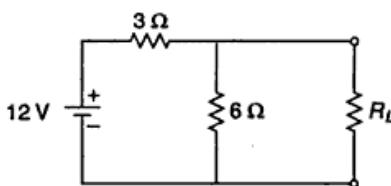


Fig. 4.203

43. Determine the current passing through the 20Ω (BD) resistor of the network as shown in Fig. 4.204 with the help of Thevenin's theorem.

$$[\text{Ans: } I(B \text{ to } D) = -7.79 \text{ A}]$$

[Hint: Removing the 20Ω resistor the open circuit voltage

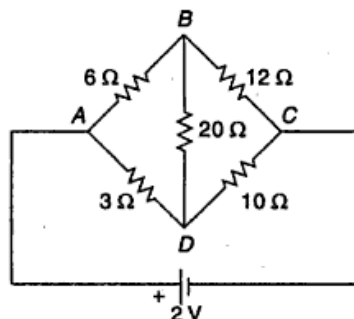


Fig. 4.204

$$V_{BD} = V_{Th} = V_{AD} - V_{AB} = \frac{2}{3+10} \times 3 - \frac{2}{6+12} \times 6 = -0.205 \text{ V}$$

$$R_{Th} = \frac{6 \times 12}{6+12} + \frac{3 \times 10}{3+10} = 6.307 \Omega.$$

$$\text{Current through the } 20 \Omega \text{ resistor} = \frac{-0.205}{20+6.307} \text{ A from } B \text{ to } D \text{ or } 7.79 \text{ mA}$$

from D to B]

44. Find the current in each branch of the network shown in Fig. 4.205 using Kirchhoff's law.

$$\begin{aligned} \text{[Ans: } I_{1\Omega} &= 1.978 \text{ A; } I_{2\Omega} \\ &= 1.12 \text{ A (AD)} \\ I_{4\Omega} &= 0.066 \text{ A (BD); } I_{2\Omega} \\ &= 1.912 \text{ A (BC)} \\ I_{3\Omega} &= 1.186 \text{ A (DC);} \end{aligned}$$

$$\text{Current through battery} = 3.098 \text{ A}]$$

[Hint: Taking 3 mesh currents I_1 , I_2 and I_3 in loops $ABDA$, $BCDB$ and ADC (12 V) A,

$$I_1 + (I_1 - I_2)4 + (I_1 - I_3)2 = 0$$

$$2I_2 + 3(I_2 - I_3) + 4(I_2 - I_1) = 0$$

$$2I_3 + 2(I_3 - I_1) + 3(I_3 - I_2) = 12$$

Solving $I_1 = 1.978 \text{ A}$; $I_2 = 1.912 \text{ A}$; $I_3 = 3.098 \text{ A}$ currents in all branches can be found out from I_1 , I_2 and I_3]

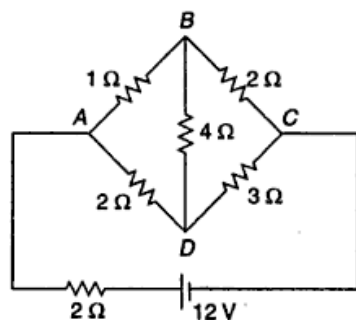


Fig. 4.205



STEADY STATE ANALYSIS OF AC CIRCUIT

5.1 GENERATION OF ALTERNATING EMF

Let us consider a rectangular coil (Fig. 5.1), having N number of turns and $A \text{ m}^2$ cross-sectional area, which is rotating in a uniform magnetic field with an angular velocity ω radian/s. If in t seconds the coil rotates through an angle $\theta = \omega t$ from the X -axis, the component of the flux perpendicular to the plane of the coil is $\phi = \phi_m \cos \omega t$ (where ϕ_m = maximum flux density perpendicular to the axis of rotation, when the plane of the coil coincides with the X -axis).

We know from Faraday's laws of electromagnetic induction that, "the induced emf in the coil is equal to the rate of change of flux linkages of the coil". Again, Lenz's law states that, "when a circuit and a magnetic field move relatively to each other the electric current induced in the circuit will have a magnetic field opposing the motion". Combining these two laws, the instantaneous induced emf at time t is given by

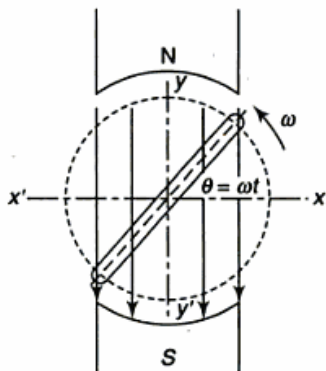


Fig 5.1 Generation of alternating emf

$$e = -N \frac{d\phi}{dt} = -N \frac{d}{dt} (\phi_m \cos \omega t) \quad [\because \phi = \phi_m \cos \omega t]$$

$$= \omega N \phi_m \sin \omega t = (\omega N \phi_m \sin \theta) \text{ V.}$$

when $\theta = 90^\circ$, $e = \omega N \phi_m = E_m$ (say) where (E_m) is the maximum value of the instantaneous induced emf.

Now, if f be the frequency of rotation of coil in Hertz and B_m the maximum flux density in wb/m^2 ,

$$e = E_m \sin \theta = (2\pi f N B_m A) \sin \theta \text{ V} \quad [\because B_m \cdot A = \phi_m]$$

Let i be the instantaneous value of the current in the coil. Therefore, $i = I_m \sin \omega t$, where I_m is the maximum value of the current.

As both the induced emf and induced current varies sinusoidally hence the emf or current can be plotted against (time). A sinusoidal curve is obtained as shown in Fig. 5.2

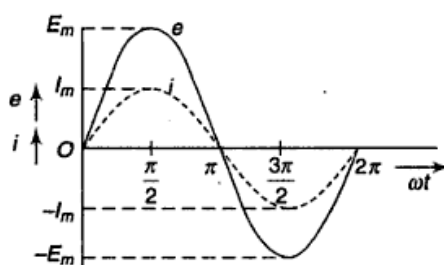


Fig. 5.2 AC Sinusoidal wave form

5.2 DEFINITIONS RELATING TO ALTERNATING QUANTITY

1. Amplitude (Peak Value) It is the maximum value, positive or negative of an alternating quantity.

2. Instantaneous Value It is the value of the alternating quantity at any instant.

3. Cycle One complete set of positive and negative values of an alternating quantity is known as cycle.

4. Time Period It is the time required by an alternating quantity to complete 1 cycle; so for a 50 Hz a.c the time period is 1/50 second.

5. Frequency The number of cycles per second is called the frequency of the alternating quantity. Its unit is Hertz (Hz).

6. Phase Phase of an alternating quantity is fraction of the time period that has elapsed since the quantity last passed through the chosen zero position of reference.

7. Phase Angle It is the equivalent of phase in radians or degrees. So phase angle is $\left(2\pi \frac{t}{T}\right)$, where t is the instantaneous time and T is the time period.

8. Phase Difference Phase difference between two alternating quantities is the fractional part of a period by which one has advanced over or lags behind the other. To measure phase difference the frequency of the alternating quantities should be same.

- The alternating quantities are in phase when each pass through their zero value, maximum and minimum values at the same instant of time.
- A leading alternating quantity is one which reaches its maximum, minimum or zero value earlier than the other quantity. A lagging quantity is one which reaches the maximum, minimum and zero values later than the other quantity.

In Fig. 5.3 alternating quantity e_B is leading with respect to e_C and is lagging with respect to e_A . If we consider e_B as reference then

$$e_B = E_m \sin \omega t,$$

where E_m is the amplitude and ω is the angular frequency of (e_B).

Therefore

$$e_A = E_m \sin (\omega t + \alpha) \text{ and } e_C = E_m \sin (\omega t - \beta)$$

where α is the phase difference between e_A and e_B and (β) is the phase difference between (e_B) and (e_C).

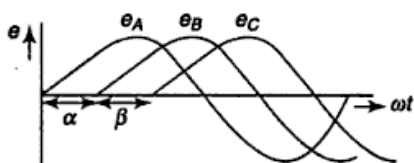


Fig. 5.3 Lagging and leading alternating quantities

9. Roots Mean Square (RMS Value) The rms value of the alternating current is that steady current, i.e., d.c current which if passed through a circuit produces the same amount of heat as produced by the alternating current flowing through the same circuit for the same period of time. The heat produced by direct current I or its equivalent rms value of the alternating quantity i is proportional to i^2 . So the area under the curve i^2 vs. 2π is the total heat produced by an alternating current [Fig. 5.4(a) and Fig. 5.4(b)].

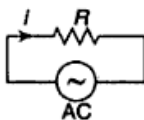


Fig. 5.4(a) AC through pure resistance

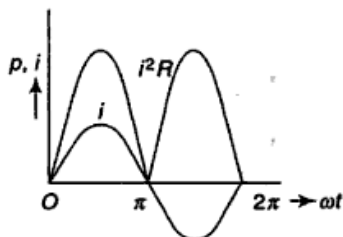


Fig. 5.4(b) RMS value of alternating quantity

Rms value is given by

$$\begin{aligned} I_{\text{rms}} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2 dt} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 \theta d\theta} \quad [\text{substituting } i = I_m \sin \theta] \\ &= \sqrt{\frac{I_m^2}{4\pi} \int_0^{2\pi} 2 \sin^2 \theta d\theta} \\ &= \frac{I_m}{2} \sqrt{\frac{1}{\pi} \int_0^{2\pi} (1 - \cos 2\theta) d\theta} \end{aligned}$$

$$\begin{aligned}
 &= \frac{I_m}{2} \sqrt{\frac{1}{\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{2\pi}} \\
 &= \frac{I_m}{2} \sqrt{\frac{1}{\pi} (2\pi)} \\
 &= \frac{I_m}{\sqrt{2}} = 0.707 I_m.
 \end{aligned}$$

Hence, the rms value of an alternating quantity = $0.707 \times$ maximum value of that alternating quantity.

10. Average (or Mean) Value The average value of an alternating current is that steady or d.c. current which transfers across any circuit the same amount of charge as transferred by that alternating current during the same period of time.

The average value of an alternating current is given by

$$\begin{aligned}
 I_{av} &= \frac{1}{\pi} \int_0^{\pi} i \, d\theta \\
 &= \frac{1}{\pi} \int_0^{\pi} I_m \sin \theta \, d\theta \\
 &= \frac{I_m}{\pi} [-\cos \theta]_0^{\pi} = \frac{2I_m}{\pi} = 0.637 I_m.
 \end{aligned}$$

Thus, the average value of an alternating quantity = $0.637 \times$ maximum value of that alternating quantity.

11. Crest or Amplitude or Peak Factor K_a It is the ratio of the peak or maximum value to the rms value of an alternating quantity. For a sinusoidal wave,

$$K_a = \frac{I_m}{I_{rms}} = \frac{I_m}{0.707 I_m} = 1.414$$

The knowledge of crest factor is important for measuring iron losses, as iron loss depends on the value of maximum flux. Also in dielectric insulation testing the dielectric stress to which the insulation is subjected, is proportional to the maximum or peak value of the applied voltage.

12. Form factor K_f It is the ratio of the rms value to the average value of an alternating quantity. For a sinusoidal wave

$$K_f = \frac{I_{rms}}{I_{av}} = \frac{0.707 I_m}{0.637 I_m} = 1.11.$$

5.1 An alternating emf of frequency 50 Hz, has an amplitude of 100 V. Write down the equation for the instantaneous value. Also find the instantaneous value of the emf after 1/600 second.

Solution

The instantaneous equation for the emf is

$$e = 100 \sin 2\pi ft = 100 \sin 2\pi \times 50t = 100 \sin 100\pi t$$

At $t = \frac{1}{600} \text{ sec},$

$$\begin{aligned} e &= 100 \sin 100\pi \times \frac{1}{600} = 100 \sin \frac{100 \times 180^\circ}{600} \\ &= 100 \sin 30^\circ = 50 \text{ A.} \end{aligned}$$

5.2 An alternating current has rms value of 50 A and frequency 60 Hz. Find the time taken to reach 50 A for the first time.

Solution

$$\text{rms value} = 50 \text{ A i.e. } I_{\text{rms}} = 50 \text{ A}$$

So $I_m = 50\sqrt{2} = 70.71 \text{ A.}$

The instantaneous equation of the current is

$$i = I_m \sin 2\pi ft = 70.71 \sin 2\pi \times 60t = 70.71 \sin 120\pi t$$

when $i = 50 \text{ A}$
 $50 = 70.71 \sin 120\pi t$

$$\therefore \sin 120\pi t = \frac{50}{70.71} = \frac{1}{\sqrt{2}} = \sin \frac{\pi}{4}$$

Hence $t = \frac{1}{120 \times 4} = 0.0021 \text{ sec.}$

5.3 An alternating sinusoidally varying voltage with angular frequency of 314 radian/second has an average value of 127.4 V. Find the instantaneous value of the emf (a)

$\frac{1}{300} \text{ sec}$ and (b) $\frac{1}{75} \text{ sec}$ after passing through a positive maximum value.

Solution

$$E_{\text{av}} = 127.4 \text{ V}$$

$$\therefore E_m = \frac{E_{\text{av}}}{0.637} = 200 \text{ V.}$$

Reckoning the time from the instant when the voltage waveform has maximum value, the equation of the sinusoidal voltage wave is $e = E_m \cos \omega t = 200 \cos 314 t$.

(a) When $t = \frac{1}{300} \text{ sec}$

$$\begin{aligned} e &= 200 \cos 314 t = 200 \cos 100\pi \times \frac{1}{300} \\ &= 200 \cos \frac{\pi}{3} = 100 \text{ V.} \end{aligned}$$

(b) When $t = \frac{1}{75}$ sec

$$e = 200 \cos 314 t = 200 \cos 100 \pi t$$

$$= 200 \cos 100 \pi \times \frac{1}{75} = 200 \cos \frac{4\pi}{3} = -100 \text{ V}$$

.....

5.4 An alternating voltage is given by the equation $v = 282.84 \sin \left(377 t + \frac{\pi}{6} \right)$. Find the (a) rms value, (b) frequency, and (c) the time period.

Solution

(a) $V_m = 282.84 \text{ V}$

$$V_{\text{rms}} = \frac{282.84}{\sqrt{2}} = 200 \text{ V}$$

(b) $\omega = 377 \text{ rad/s}$

$$f = \frac{377}{2\pi} = \frac{377}{3.14 \times 2} = 60 \text{ Hz}$$

(c) $T = \frac{1}{f} = \frac{1}{60} = 0.0167 \text{ sec.}$

.....

5.5 If the form factor of a current wave form is 2 and the amplitude factor is 2.5, find the average value of the current if the maximum value of the current is 500 A.

Solution

$$K_f = 2 \text{ and } K_a = 2.5, I_m = 500 \text{ (Given)}$$

Therefore $K_f = 2 = \frac{I_{\text{rms}}}{I_{\text{av}}}$ and $K_a = 2.5 = \frac{I_m}{I_{\text{rms}}} = \frac{500}{I_{\text{rms}}}$

So $I_{\text{rms}} = \frac{500}{2.5} = 200 \text{ A}$ and $I_{\text{av}} = \frac{I_{\text{rms}}}{2} = \frac{200}{2} = 100 \text{ A.}$

.....

5.6 Find the average and rms value of the wave form shown in Fig. 5.5.

Solution

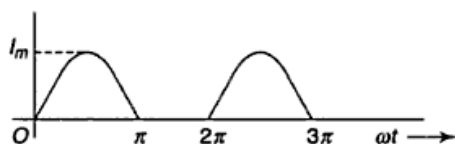


Fig. 5.5 Waveform of Ex. 5.6

$$I_{\text{av}} = \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t \, d(\omega t)$$

$$= \frac{I_m}{2\pi} [-\cos \omega t]_0^{\pi} = \frac{I_m}{\pi} = 0.318 I_m$$

$$I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} I_m^2 \sin^2 \omega t \, d(\omega t)} = \sqrt{\frac{I_m^2}{4\pi} \int_0^{\pi} (1 - \cos 2\omega t) \, d(\omega t)}$$

$$= \frac{I_m}{2} \sqrt{\frac{1}{\pi} \left[\omega t - \frac{\sin^2 \omega t}{2} \right]_0^{\pi}} = \frac{I_m}{2} \sqrt{\frac{1}{\pi} (\pi)} = 0.5 I_m$$

5.7 Find the rms and average value of the waveform shown in Fig. 5.6

Solution

$$E_{\text{rms}} = \sqrt{\frac{1}{\pi} \int_0^{\pi} E_m^2 \sin^2 \omega t d(\omega t)}$$

$$= \sqrt{\frac{E_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\omega t) d(\omega t)}$$

$$= \frac{E_m}{\sqrt{2\pi}} \left[\omega t - \frac{\sin 2\omega t}{2} \right]_0^{\pi} = \frac{E_m}{\sqrt{2\pi}} \sqrt{\pi} = \frac{E_m}{\sqrt{2}}$$

$$= 0.707 E_m$$

$$E_{\text{av}} = \frac{1}{\pi} \int_0^{\pi} E_m \sin \omega t d(\omega t) = \frac{E_m}{\pi} [-\cos \omega t]_0^{\pi} = \frac{E_m}{\pi} \times 2$$

$$= 0.637 E_m$$

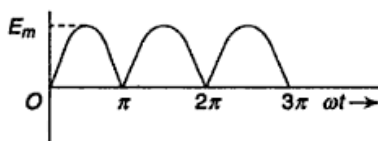


Fig. 5.6 Waveform of Ex. 5.7

5.8 Find the average and rms of the wave form shown in Fig. 5.7.

Solution

$$I_{\text{av}} = \frac{1}{2} \int_0^2 i dt = \frac{1}{2} \left[\int_0^1 i_1 dt + \int_1^2 i_2 dt \right]$$

$$i_1 = \frac{500}{1} t + 0 = 500t$$

$$i_2 = 500$$

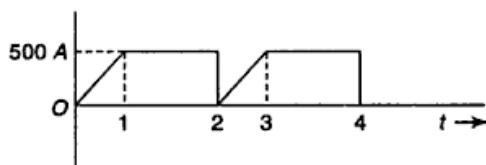


Fig. 5.7 Waveform of Ex. 5.8

$$\text{Therefore } I_{\text{av}} = \frac{1}{2} \left[\int_0^1 500 t dt + \int_1^2 500 dt \right] = \frac{1}{2} \left[500 \left[\frac{t^2}{2} \right]_0^1 + 500 [t]_1^2 \right]$$

$$= \frac{1}{2} \left[500 \times \frac{1}{2} + 500 \right] = \frac{1}{2} \times 750 = 375 \text{ A}$$

$$I_{\text{rms}} = \sqrt{\frac{1}{2} \left\{ \int_0^1 i_1^2 dt + \int_1^2 i_2^2 dt \right\}}$$

$$= \sqrt{\frac{1}{2} \left\{ \int_0^1 (500 t)^2 dt + \int_1^2 (500)^2 dt \right\}} = 500 \sqrt{\left[\frac{t^3}{3} \right]_0^1 + [t]_1^2}$$

$$= 500 \sqrt{\frac{1}{3} + 1} = 500 \frac{2}{\sqrt{3}} = 577.35 \text{ A.}$$

5.3 PHASOR REPRESENTATION OF AN ALTERNATING QUANTITY

Alternating quantities have varying magnitude and direction. So they are represented by a rotating vector. A phasor is a vector rotating at a constant angular velocity.

Let us consider that an *alternating or sinusoidal quantity* be represented by a phasor Oa . It rotates in the counter clockwise direction with a velocity of (ω) radian/s as shown in Fig. 5.8. The projection of this vector on the vertical axis gives the instantaneous value e of the induced emf (i.e. $\sin \omega t$). When $\omega t = 0$, then instantaneous value = $Oa \sin \omega t = 0$. When $\omega t = \pi/2$, the instantaneous value = $Oa \sin \pi/2$; $Oa = E_m$ (peak value).

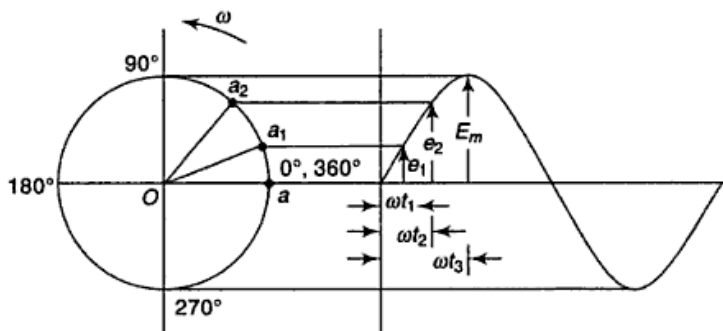


Fig. 5.8 Phasor representation of alternating quantity

The instantaneous value of emf at various intervals of time are:

at t_1 , $e_1 = E_m \sin \omega t_1$,

at t_2 , $e_2 = E_m \sin \omega t_2$

at t_3 , $e_3 = E_m \sin \omega t_3$; and so on.

Phasor diagram is one in which different alternating or sinusoidal quantities of the same frequency are represented by phasors with their phase relationship.

Now consider two similar single turn coils A and B displaced from each other by an angle (θ) rotating in a uniform magnetic field with the same angular velocity [Fig. 5.9(a)]. Suppose the emf wave of coil A passes through zero in the positive direction at instant $t = 0$ and at the same instant emf of coil B attains a fixed positive value due to its advancement through an angle (θ) from its zero value [Fig. 5.9(b)]. This can be represented as a still picture with the help of phasors in the phase diagram. [Fig. 5.9(c)] Obviously the angle between the two phasors is the phase difference between the two emfs.

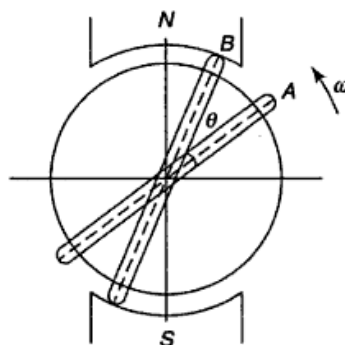


Fig. 5.9(a) Coil rotating in magnetic field

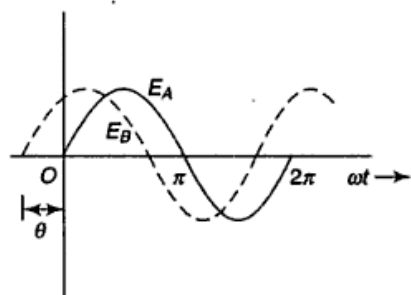
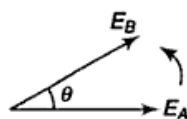


Fig. 5.9(b) Phasor diagram of ac emf

Fig. 5.9(c) Phase difference between E_A and E_B

It should be noted that normally phasors are drawn to represent the *rms* values and the reference phasor is drawn horizontally, e.g., the phasor (E_A). Also the phasors are assumed to rotate in the anticlockwise direction. So the phasor ahead in an anticlockwise direction from a given reference phasor is said to be *leading*, e.g., (E_B) leads phasor (E_A) by angle (θ). The phasor which is behind the reference phasor is said to be *lagging*.

5.3.1 Addition and Subtraction of Sinusoidal Alternating Quantities

Draw the phasor diagram of the alternating quantity and then resolve each phasor into its horizontal and vertical components. Then add or subtract the horizontal components and the vertical components separately. Suppose I_x represents the addition or subtraction of the phasors in the horizontal axis and I_y represents the addition and subtraction in the vertical axis. The diagonal of the rectangle formed by I_x and I_y denotes the resultant phasor I as shown in Fig. 5.10. The magnitude of I is given by

$$|I| = \sqrt{I_x^2 + I_y^2}$$

If θ represents the angle between the resultant phasor and the reference phasor (or horizontal line) then

$$\theta = \tan^{-1} \frac{I_y}{I_x}$$

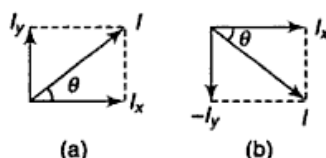


Fig. 5.10 (a) Addition of alternating quantities (b) Subtraction of alternating quantities

5.3.2 Graphical Method

Let us take an example of adding voltages: $v_1 = 8 \sin(\omega t - 30^\circ)$ and $v_2 = 6 \sin(\omega t + 45^\circ)$.

Magnitude of v_1 is 8 and that of v_2 is 6, i.e. $V_1 = 8$ V and $V_2 = 6$ V. Choose the scale 1 cm = 2 V. Draw one horizontal line OP as the reference line. Draw $OA = 8/2 = 4$ cm at -30° and $OB = 6/2 = 3$ cm at an angle of 45° with respect to the reference OP to represent (V_1) and (V_2) respectively. Complete the parallelogram $OACB$. The diagonal of the parallelogram, i.e., OC represents the resultant voltage V_r (Fig. 5.11). By measurement $OC = 5.58$ cm. So $OC = (5.58 \times 2) = 11.16$ V. The angle θ between OC and $OP = 1.2^\circ$ (by measurement). So, $v_r = 11.16 \sin(\omega t + 1.2^\circ)$ volts or $v_r = 11.16 \angle 1.2^\circ$ V.

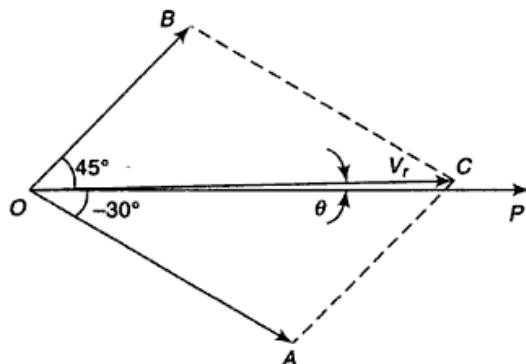


Fig. 5.11 Addition of two vectors (graphical method)

5.3.3 Analytical Method

At first draw the phasor diagram. The horizontal component of the resultant voltage

$$V_x = 8 \cos(-30^\circ) + 6 \cos 45^\circ = 8 \times \frac{\sqrt{3}}{2} + 6 \times \frac{1}{\sqrt{2}} = 11.17$$

The vertical component of the resultant voltage

$$V_y = 8 \sin(-30^\circ) + 6 \sin(45^\circ) = -8 \times \frac{1}{2} + 6 \times \frac{1}{\sqrt{2}} = 0.24.$$

So the resultant voltage as shown in Fig. 5.12 is

$$V_r = \sqrt{V_x^2 + V_y^2} = \sqrt{11.17^2 + 0.24^2} = 11.1726 \text{ V.}$$

$$\theta = \tan^{-1} \frac{V_y}{V_x} = \tan^{-1} \frac{0.24}{11.17} = 1.23^\circ$$

i.e. $V_r = 11.1726 \sin(\omega t + 1.23^\circ)$ V.

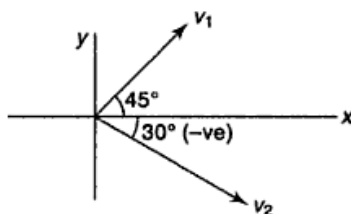


Fig. 5.12 Addition of two phasors (analytical method)

5.4 AC VOLTAGE AS APPLIED TO PURE RESISTANCE, PURE INDUCTANCE AND PURE CAPACITANCE

AC through Pure Resistance Alone

When a pure resistance is placed across a sinusoidal emf [Fig. 5.13(a)], the current will be in phase with the emf [Fig. 5.13(b)]. The corresponding phasor diagram is shown in Fig. 5.13(c):

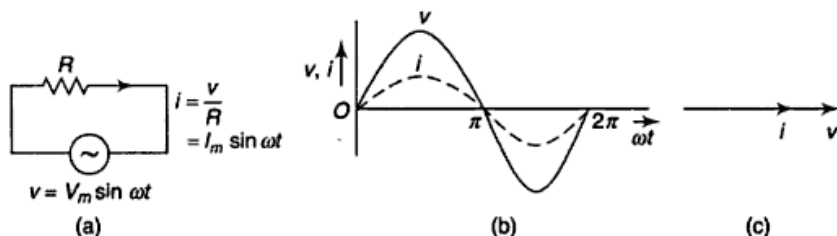


Fig. 5.13 (a) AC through pure resistance (b) Phasor diagram of voltage and current through R (c) phasor diagram of voltage and current through R .

The current is given by, $i = \frac{v}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t = I_m \sin \omega t$

where $I_m = \frac{V_m}{R}$.

Also, $I = \frac{V}{R}$

where V = rms value of the applied voltage

I = rms value of current

and R = resistance in ohms.

AC through Pure Inductance Alone

Whenever an alternating sinusoidal voltage is applied to a purely inductive coil [Fig. 5.14(a)] a back emf is produced due to the self-inductance of the coil. The

applied voltage has to overcome this self-induced emf and therefore, $v = L \frac{di}{dt}$,

where L is the self-inductance of the coil, v the back emf and (di/dt) the rate of change of current.

i.e. $\frac{di}{dt} = \frac{v}{L} = \frac{V_m}{L} \sin \omega t$ [$\because v = V_m \sin \omega t$]

or $i = \frac{V_m}{L} \int \sin \omega t \, dt = -\frac{V_m}{\omega L} \cos \omega t = \frac{V_m}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$

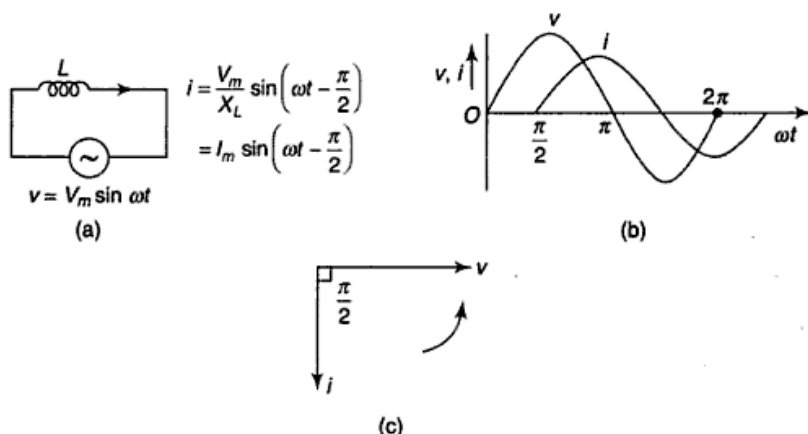


Fig. 5.14 (a) AC through pure inductance (b) Phasor diagram of voltage and current through L (c) Current lags voltage by 90° in pure inductive circuit

or
$$i = \frac{V_m}{X_L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

where $X_L = \omega L$ (= inductive reactance)

$\therefore i = I_m \sin\left(\omega t - \frac{\pi}{2}\right)$, where $I_m = \frac{V_m}{X_L}$.

So the current *lags* behind the voltage by $\left(\frac{\pi}{2}\right)$ and the phasor diagram is shown in Fig. 5.14(b) and (c).

Also,
$$I = \frac{V}{X_L}; \text{ where } I = \text{rms value of the current}$$

V = rms value of the voltage and
 $X_L = \omega L$ = inductive reactance in ohms.

AC through Pure Capacitance Alone

If a sinusoidal voltage is applied to the plates of a capacitor [Fig. 5.15(a)] then the instantaneous charge in the capacitors $q = Cv$, where v is the instantaneous value of the applied voltage and C is the capacitance.

If current i is the rate of flow of charge, then

$$\begin{aligned} i &= \frac{dq}{dt} = C \frac{dv}{dt} = C \frac{d}{dt} (V_m \sin \omega t) \\ &= V_m \omega C \cos \omega t \\ &= \frac{V_m}{\frac{1}{\omega C}} \sin\left(\omega t + \frac{\pi}{2}\right) = \frac{V_m}{X_C} \sin\left(\omega t + \frac{\pi}{2}\right) \end{aligned}$$

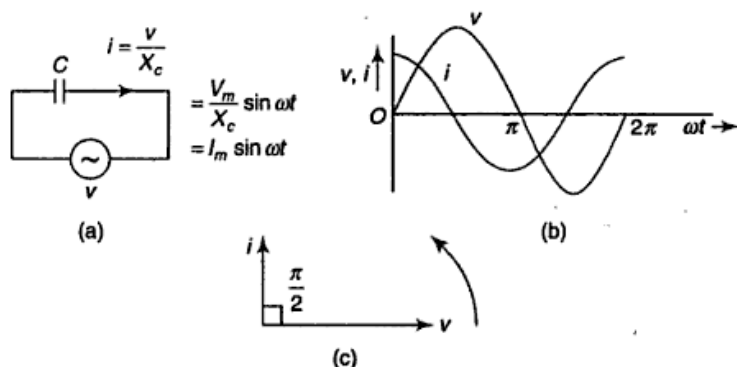


Fig. 5.15 (a) AC through pure capacitance (b) Phasor diagram of voltage and current through pure capacitance (c) Current leads voltage by 90° in pure capacitance circuit.

where $X_c = \frac{1}{\omega C}$ (= capacitive reactance).

Also, $i = I_m \sin \left(\omega t + \frac{\pi}{2} \right)$, where $I_m = \frac{V_m}{X_c}$.

So the current *leads* the applied voltage by $\left(\frac{\pi}{2} \right)$ and the phasor diagram is shown in Fig. 5.15(b) and (c).

Also $I = \frac{V}{X_c}$, where I = rms value of the current,

V = rms value of the voltage

and X_c = capacitive reactance in ohms.

5.5 SERIES RL CIRCUIT

Consider a coil of resistance R ohms and inductance L henries. The coil is represented by R in series with L [Fig. 5.16(a)]. Let V = rms value of applied voltage, I = rms value of resultant current, V_R = voltage drop across R and V_L = voltage drop across L .

In the phasor diagram of Fig. 5.16(b) the current I flowing in the circuit is drawn in the horizontal axis as reference. V_R is drawn in the same direction as that of I and $V_R = IR$. V_L is drawn leading with respect to I by 90° and $V_L = IX_L$. The resultant of the phasors V_R and V_L gives the supply voltage V . The magnitude

of the supply voltage is $|V| = \sqrt{V_R^2 + V_L^2} = \sqrt{(IR)^2 + (IX_L)^2} = |I| \sqrt{R^2 + X_L^2} = |I|Z$, where Z is the *impedance* of the circuit and is expressed in ohms;

also, $|I| = \frac{|V|}{|Z|}$ and $|Z| = \sqrt{R^2 + X_L^2}$

or $(\text{Impedance})^2 = (\text{Resistance})^2 + (\text{Inductive reactance})^2$.

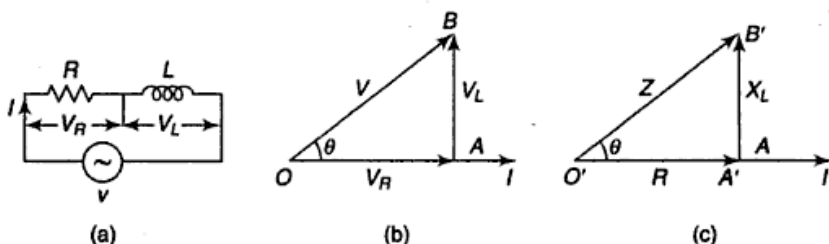


Fig. 5.16 (a) AC through inductive coil (b) Voltage triangle (c) Impedance triangle.

Triangle OAB [Fig. 5.16(b)] is called the *voltage triangle* and triangle $O'A'B'$ [Fig. 5.16(c)] is called the *impedance triangle*. It is noticed that current I lags the applied voltage V by an angle (θ) where θ

$$= \tan^{-1} \frac{V_L}{V_R} = \tan^{-1} \frac{IX_L}{IR} = \tan^{-1} \frac{X_L}{R}. \text{ So,}$$

if $v = V_m \sin \omega t$ then, $i = I_m \sin(\omega t - \theta) = \frac{V_m}{Z} \sin(\omega t - \theta)$. The phasor diagrams of the applied voltage and current are shown in Fig. 5.17.

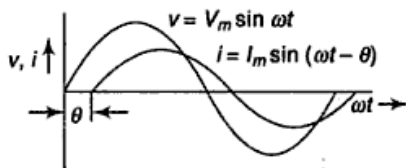


Fig. 5.17 Phasor diagram of voltage and current through inductive coil.

5.6 SERIES RC CIRCUIT

Consider a simple ac circuit in which a resistor of R ohms and capacitance of C farad are connected in series [Fig. 5.18(a)]. Let V = rms value of applied voltage, I = rms value of resultant current, V_R = voltage drop across R and V_C = voltage drop across C .

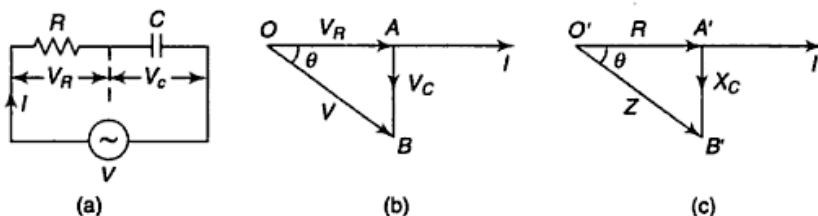


Fig. 5.18 (a) AC through series R circuit (b) Voltage triangle (c) Impedance triangle.

In the phasor diagram of Fig. 5.18(b) the current I flowing in the circuit is drawn in the horizontal axis as reference V_R is drawn in the same direction as that of I and $V_R = IR$. V_C is drawn lagging with respect to I by 90° and $V_C = IX_C$. The resultant of the vectors V_R and V_C gives the supply voltage V . The magnitude of the supply voltage is

$$|V| = \sqrt{V_R^2 + V_C^2} = \sqrt{(IR)^2 + (IX_C)^2} = |I| \sqrt{R^2 + X_C^2} = |I|Z.$$

where Z is the impedance of the circuit and is expressed in ohms.

So, $|I| = \frac{|V|}{|Z|}$ and $|Z| = \sqrt{R^2 + X_C^2}$

or $(\text{Impedance})^2 = (\text{Resistance})^2 + (\text{Capacitive reactance})^2$.

Triangle OAB [Fig. 5.18(b)] is called the *voltage triangle* and the triangle $O'A'B'$ [Fig. 5.15(c)] is called the *impedance triangle*. It is seen that the current I leads the applied voltage V by an

angle θ where $\theta = \tan^{-1} \frac{V_C}{V_R} = \tan^{-1} \frac{IX_C}{IR}$

So, if $v = V_m \sin \omega t$

then $i = I_m \sin (\omega t + \theta) = \frac{V_m}{Z} \sin (\omega t + \theta)$.

The phasor diagram of the applied voltage and currents are shown in Fig. 5.19.

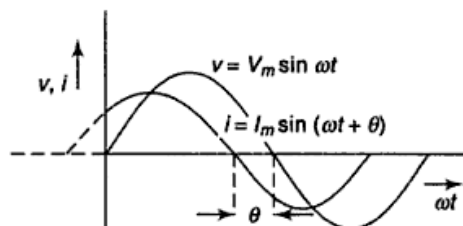


Fig. 5.19 Phasor diagram of voltage and current in RC circuit.

5.7 SERIES RLC CIRCUIT

Consider a simple series ac circuit containing a resistor of resistance R ohms, an inductor of inductance L henries and a capacitor of capacitance C farad across an ac supply of rms voltage V volts [Fig. 5.20(a)].

I = rms value of the current flow in the circuit

V_R = rms value of voltage across $R = IR$

V_L = rms value of voltage across $L = IX_L$

and V_C = rms value of the voltage across the capacitor = IX_C .

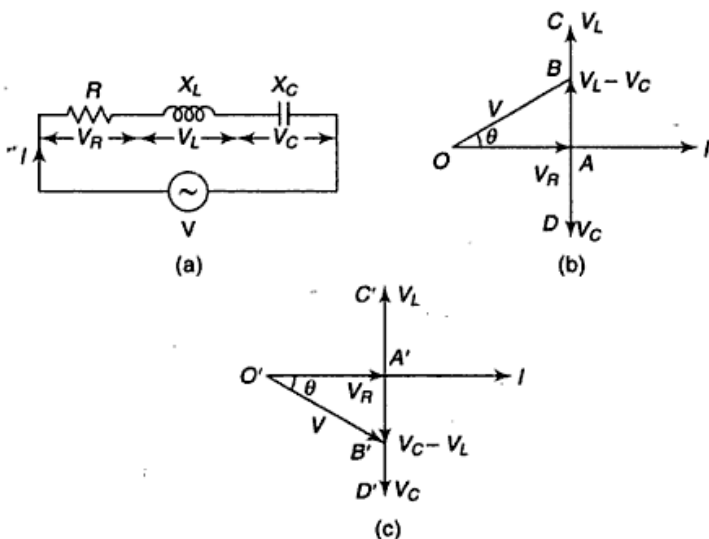


Fig. 5.20 (a) AC through-RLC series circuit. (b) Voltage triangle for lagging p.f. (c) Voltage triangle for leading p.f.

In the voltage triangle OAB [Fig. 5.20(b)] OA , AC and AD represents V_R , V_L and V_C respectively. If $|V_L| > |V_C|$ then AB represents the resultant of $(V_L - V_C)$. The vector sum of (V_R) and $(V_L - V_C)$ gives the resultant voltage (V) .

$$\text{Hence, } |V| = \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$= I\sqrt{R^2 + (X_L - X_C)^2} = I\sqrt{R^2 + X^2} = IZ$$

where $X = \text{Net reactance in ohm} = (X_L - X_C)$

The phase angle of (V) is given by, $\theta = \tan^{-1} \frac{(V_L - V_C)}{(V_R)}$

$$= \tan^{-1} \frac{(IX_L - IX_C)}{IR}$$

$$= \tan^{-1} \frac{(X_L - X_C)}{R}$$

$$= \tan^{-1} \frac{X}{R}; X \text{ (say)} = (X_L - X_C),$$

If, $v = V_m \sin \omega t$,

then $i = \frac{V_m}{Z} \sin(\omega t - \theta) = I_m \sin(\omega t - \theta)$

Hence, when $|V_L| > |V_C|$, we have

$X_L > X_C$ and current I is lagging with respect to V by an angle less than 90° .

In the voltage triangle $O'A'B'$ in Fig. 5.20(c) $|V_C| > |V_L|$. OA' represents V_R , $A'C'$ represents V_L and $A'D'$ represents V_C . The phasor $(V_C - V_L)$ is represented by $A'B'$ and $O'B'$ denotes resultant voltage V .

$$\text{Here, } |V| = \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$= I\sqrt{R^2 + (X_L - X_C)^2} = I\sqrt{R^2 + X^2} = IZ$$

where $X = X_L - X_C = \text{Net reactance in ohms.}$

The phase angle of V is given by, $\theta = \tan^{-1} \frac{(V_L - V_C)}{V_R}$

$$= \tan^{-1} \frac{IX_L - IX_C}{IR}$$

$$= \tan^{-1} \frac{X_L - X_C}{R} = \tan^{-1} \frac{X}{R}.$$

If $v = V_m \sin \omega t$ then

$$i = \frac{V_m}{Z} \sin(\omega t + \theta) = I_m \sin(\omega t + \theta).$$

When $V_C > V_L$ or $IX_C > IX_L$ or $X_C > X_L$ then current I is leading with respect to the resultant voltage V by an angle less than 90° .

The impedance triangle when $V_L > V_C$ is shown in Fig. 5.21(a) and the impedance triangle when $V_C > V_L$ is shown in Fig. 5.21(b).

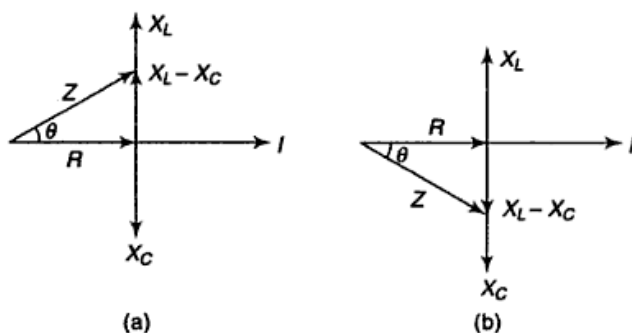


Fig. 5.21 (a) Impedance triangle for lagging p.f. (b) Impedance triangle for leading p.f.

5.8 IMPEDANCES IN SERIES

When several impedances are connected in series the net impedance can be found out by using the following steps:

- Add all the resistances in the circuit to get total R .
- Add all the inductive reactances to get total X_L .
- Add all the capacitive reactances to get total X_C .

(d) Total impedance is given by $Z = \sqrt{R^2 + (X_L - X_C)^2}$

[Note: all additions in step (b) and (c) are phasor additions.]

5.9 A coil has an inductance of 50 mH and negligible resistance. Find its reactance at 100 Hz.

Solution

$$L = 50 \text{ mH} \quad \text{and} \quad f = 100 \text{ Hz}$$

Inductive reactance $X_L = \omega L = 2\pi fL$, where ω is the angular frequency.

$$\begin{aligned} \text{So,} \quad X_L &= 2 \times 3.14 \times 100 \times 50 \times 10^{-3} \\ &= 31.4159 \, \Omega. \end{aligned}$$

5.10 If the frequency of applied voltage is 5 kHz, calculate the reactance of a 10 μF capacitor.

Solution

$$f = 5 \text{ kHz} = 5000 \text{ Hz} \quad \text{and} \quad C = 10 \, \mu\text{F} = 10 \times 10^{-6} \text{ F}$$

$$\begin{aligned} \therefore \text{Capacitive reactance } (X_C) &= \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 5000 \times 10 \times 10^{-6}} \\ &= \frac{10^6}{2 \times 3.14 \times 5000 \times 10} = 3.18 \, \Omega \end{aligned}$$

5.11 A circuit containing a (a) resistance of $20\ \Omega$ alone (b) inductance of $10\ \text{mH}$ alone and (c) capacitance of $300\ \mu\text{F}$ alone is connected across an alternating voltage source; write the expressions for the current when $v = 100 \sin 100\pi t$.

Solution

$$v = 100 \sin 100\pi t, \therefore V_m = 100\ \text{V and } \omega = 100\pi\ \text{rad/s.}$$

$$(a) R = 20\ \Omega \therefore i_R = \frac{V_m}{R} \sin 100\pi t = \frac{100 \sin 100\pi t}{20} = 5 \sin 100\pi t$$

$$(b) L = 10\ \text{mH} = 0.01\ \text{H}$$

$$\text{Therefore } X_L = \omega L (= \text{Inductive reactance}) = 100\pi \times 0.01 = 3.14\ \Omega.$$

$$\begin{aligned} i_L &= \frac{V_m}{X_L} \sin \left(100\pi t - \frac{\pi}{2} \right) = \frac{100}{3.14} \sin \left(100\pi t - \frac{\pi}{2} \right) \\ &= 31.85 \sin \left(100\pi t - \frac{\pi}{2} \right) \end{aligned}$$

$$(c) C = 300\ \mu\text{F} = 300 \times 10^{-6}\ \text{F}$$

$$\therefore \text{capacitive reactance } (X_C) = \frac{1}{\omega C} = \frac{10^6}{100\pi \times 300}\ \Omega$$

$$= 10.61\ \Omega$$

$$\begin{aligned} i_C &= \frac{V_m}{X_C} \sin \left(100\pi t + \frac{\pi}{2} \right) = \frac{100}{10.61} \sin \left(100\pi t + \frac{\pi}{2} \right) \\ &= 9.425 \sin \left(100\pi t + \frac{\pi}{2} \right). \end{aligned}$$

.....

5.12 A coil of resistance $100\ \Omega$ and inductive reactance $200\ \Omega$ is connected across a supply voltage of $230\ \text{V}$. Find the supply current.

Solution

$$R = 100\ \Omega, X_L = 200\ \Omega$$

$$\text{Impedance } |Z| = \sqrt{R^2 + X_L^2} = \sqrt{(100)^2 + (200)^2} = 223.61\ \Omega$$

$$\therefore \text{supply current } I = \frac{V}{Z} = \frac{230}{223.61} = 1.028\ \text{A.}$$

.....

5.13 A circuit takes a current $i = 50 \sin \left(314t - \frac{\pi}{3} \right)$ when the supply voltage is $v = 400 \sin 314t$. Find the impedance, resistance, and the inductance of the circuit.

Solution

$$v = 400 \sin 314t$$

$$i = 50 \sin \left(314t - \frac{\pi}{3} \right)$$

$$I_m = 50\ \text{A}$$

and

$$\theta = \frac{\pi}{3}$$

Hence $V_m = 400 \text{ V}$ and $\omega = 314 \text{ rad/s}$

$$\therefore \text{Impedance } |Z| = \frac{|V|}{|I|} = \frac{V_m}{I_m} = \frac{400}{50} = 8 \Omega$$

$$\theta = \frac{\pi}{3} = \tan^{-1} \frac{X_L}{R} \quad \text{or,} \quad \frac{X_L}{R} = \tan \frac{\pi}{3} = 1.732 = \sqrt{3}$$

$$\therefore X_L = 1.732 R \text{ or, } X_L^2 = (1.732)^2 R^2 \text{ or, } Z^2 - R^2 = 3R^2$$

$$\text{or} \quad 4R^2 = Z^2 = (8)^2 = 64. \quad \text{So, } R = \sqrt{\frac{64}{4}} = 4 \Omega$$

$$\text{Thus, } X_L = 1.732 \times 4 = 6.93 \Omega$$

$$\text{Therefore } L = \frac{X_L}{\omega} = \frac{6.93}{314} = 0.022 \text{ H} = 22 \text{ mH.}$$

5.14 When a resistor and coil in series are connected to a 240 V supply, a current of 5 A is flowing lagging 60° behind the supply voltage, and the voltage across the coil is 220 V. Find the resistance of the resistor and the resistance and reactance of coil.

Solution

Let R_L be the resistance of the coil and X_L be the reactance of the coil. If θ be the angle of the current then, $\cos \theta = \cos 60^\circ = 0.5 = R/Z$ where R and Z are the resistance and reactance of the whole circuit respectively.

$$\text{Therefore, } R = Z \times 0.5$$

$$\text{But, } |Z| = \frac{|V|}{|I|} = \frac{240}{5} = 48 \Omega$$

$$\therefore R = 48 \times 0.5 = 24 \Omega$$

$$\text{Also, } \frac{X_L}{Z} = \sin 60^\circ = 0.866.$$

$$\text{Hence } X_L = 48 \times 0.8666 = 41.57 \Omega.$$

$$\text{Now, impedance of the coil} = \sqrt{R_L^2 + X_L^2} = \frac{220}{5} = 44 \Omega$$

$$\therefore R_L = \sqrt{(44)^2 - (41.57)^2} = 14.42 \Omega.$$

Thus resistance of the resistor is $(24 - 14.42) = 9.58 \Omega$, resistance of coil is 14.42Ω and reactance of coil is 41.57Ω .

5.15 When a certain inductive coil is connected to a dc supply at 200 V, the current in the coil is 10 A. When the same coil is connected to an ac supply at 200 V, 50 Hz the current is 8 A. Calculate the resistance and reactance of the coil.

Solution

For dc the reactance of the coil is zero ($\because f = 0$).

$$\text{Hence, resistance of the coil} = \frac{200}{10} = 20 \Omega$$

$$\text{For ac supply, impedance} = \frac{200}{8} = 25 \Omega$$

Hence reactance of the coil = $\sqrt{(25)^2 - (20)^2} = \sqrt{625 - 400} = 15 \Omega$

5.16 A 200 V, 120 W lamp is to be operated on 240 V, 50 Hz. supply. Calculate the value of the capacitor that would be placed in series with the lamp in order that it may be used at its rated voltage.

Solution


Let R be the resistance of the lamp as shown in Fig. 5.22. The current flowing through the

$$\text{circuit} = \frac{P}{V} = \frac{120}{200} = 0.6 \text{ A.}$$

Let Z be the impedance of the whole circuit,

$$|Z| = \frac{|V|}{|I|} = \frac{240}{0.6} = 400 \Omega.$$

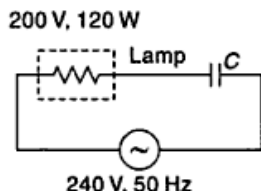Now, $\frac{V^2}{R} = P$ or, $R = \frac{(200)^2}{120} = 333.33 \Omega.$ **Fig. 5.22 Circuit for Ex. 5.16**



Hence the capacitive reactance is

$$\begin{aligned} X_C &= \sqrt{Z^2 - R^2} \\ &= \sqrt{(400)^2 - (333.33)^2} = 221.11 \Omega. \end{aligned}$$

$$\begin{aligned} \therefore C &= \frac{1}{2\pi f X_C} = \frac{1}{2 \times 3.14 \times 50 \times 221.11} \text{ F} \\ &= 0.0000144 \text{ F} = 14.4 \mu\text{F}. \end{aligned}$$

Hence the value of the capacitor is 14.4 μF

5.17 A capacitor and a 50 Ω resistor are connected in series to an alternating current supply. The voltage across the capacitor is 200 V rms and across the resistor is 150 V rms. Determine (a) rms value of supply voltage, (b) peak value of the voltage across the capacitor assuming sinusoidal wave form, (c) power used in the resistor.

Solution

Resistance $R = 50 \Omega$

Voltage across resistor, $V_R = 150 \text{ V}$

Voltage across capacitor $V_C = 200 \text{ V}$

$$\therefore \text{current } |I| = \frac{V_R}{R} = \frac{150}{50} = 3 \text{ A.}$$

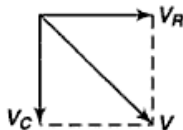


Fig. 5.23 Determination of $|V|$

$$\text{Supply voltage} = \sqrt{V_R^2 + V_C^2} = \sqrt{(150)^2 + (200)^2} = 250 \text{ V.}$$

$$\begin{aligned} \text{Peak value of the voltage across capacitor} &= \sqrt{2} V_{C \text{ rms}} \\ &= \sqrt{2} \times 200 = 282.8 \text{ V.} \end{aligned}$$

$$\begin{aligned} \text{Power used in the resistor} &= I^2 R = (3)^2 \times 50 \\ &= 450 \text{ W.} \end{aligned}$$

.....

5.18 A resistance of 10 Ω is connected in series with an inductance of 0.05 H and a capacitance of 300 μF to a 100 V ac supply. Calculate the value and phase angle of the current when the frequency is (a) 25 Hz (b) 50 Hz.

Solution

- (a) $f = 25 \text{ Hz}$, $R = 10 \Omega$, $L = 0.05 \text{ H}$, $C = 300 \times 10^{-6} \text{ F}$;
 $V = 100 \text{ V}$; Hence $X_L = 2\pi fL = 2\pi \times 25 \times 0.05 = 7.85 \Omega$,

and
$$X_C = \frac{1}{2\pi fC} = \frac{10^6}{2 \times 3.14 \times 25 \times 300} = 21.23 \Omega.$$

\therefore impedance
$$|Z| = \sqrt{R^2 + (X_C - X_L)^2}$$

$$= \sqrt{(10)^2 + (21.23 - 7.85)^2} = 16.7 \Omega;$$

and net reactance $|X| = |X_C - X_L| = 13.38 \Omega$.

As $X_C > X_L$ so the current is leading.

If θ be the angle of lead then,

$$\theta = \tan^{-1} \frac{X}{R} = \tan^{-1} \frac{13.38}{10} = 53.23^\circ.$$

Current
$$|I| = \frac{|V|}{|Z|} = \frac{100}{16.7} = 5.988 \text{ A}.$$

- (b) $f = 50 \text{ Hz}$

So
$$X_L = 2\pi \times 50 \times 0.05 = 15.7 \Omega$$

and
$$X_C = \frac{10^6}{2\pi \times 50 \times 300} = 10.61 \Omega.$$

$\therefore |X_L - X_C| = 5.09 \Omega$

and
$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 11.22 \Omega$$

As $X_L > X_C$ so the current is lagging.

It θ be the angle of lag then,

$$\theta = \tan^{-1} \frac{5.09}{10} = 26.97^\circ$$

and current
$$|I| = \frac{100}{11.22} = 8.91 \text{ A}.$$

5.19 A 230 V, 50 Hz voltage is applied to a coil $L = 5 \text{ H}$ and $R = 2 \Omega$ is in series with a capacitance C . What value must C have in order that the voltage across the coil be 400 V?

Solution

Impedance of the coil $= \sqrt{R^2 + X_L^2} = \sqrt{2^2 + (2\pi \times 50 \times 5)^2} = 1570 \Omega$

Voltage across the coil $= 400 \text{ V}$

\therefore current $I = \frac{400}{1570} = 0.2547 \text{ A}$

Impedance of the circuit $= \frac{230}{0.2547} = 903.21 \Omega.$

If X_C be the capacitive reactance,

$$\sqrt{R^2 + (X_L - X_C)^2} = 903.21$$

$$\begin{aligned} \therefore 2^2 + (100 \pi \times 5 - X_C)^2 &= (903.21)^2 \\ 500 \pi - X_C &= 903.2 \\ \text{So } X_C &= 666.8 \, \Omega \text{ and } X_L > X_C \\ \therefore C &= \frac{1}{2\pi \times 50 \times 666.8} \, F = 4.77 \, \mu F. \end{aligned}$$

5.20 A voltage of 400 V is applied to a series circuit containing a resistor, an inductor and a capacitor. The respective voltages across the components are 250 V, 200 V and 180 V and the current is 5 A. Determine the phase angle of the current.

Solution

$$\text{Resistance } R = \frac{250}{5} = 50 \, \Omega.$$

$$\text{Inductive reactance } |X_L| = \frac{200}{5} = 40 \, \Omega.$$

$$\text{Capacitive reactance } |X_C| = \frac{180}{5} = 36 \, \Omega$$

$$\begin{aligned} \text{Impedance } |Z| &= \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(50)^2 + (40 - 36)^2} \\ &= \sqrt{2500 + 16} = 50.61 \, \Omega \end{aligned}$$

$$\therefore \text{Phase angle of the current} = \tan^{-1} \frac{X}{R} (X = X_L - X_C) = \tan^{-1} \frac{4}{50} = 4.57^\circ \text{ lagging.}$$

5.9 PARALLEL AC CIRCUIT

Two circuits are said to be connected in parallel if the voltage across them is the same. Consider a parallel ac circuit where an inductive coil is in parallel with a resistor and capacitor in series [Fig. 5.24(a)]. The inductive coil in branch 1 consists of a resistance of $R_L \, \Omega$ and inductance L henry. The resistance in the other branch, i.e. branch 2 is R_C and the capacitance is C Farad. So for branch 1

$$Z_1 = \sqrt{R_L^2 + X_L^2} \text{ and } I_1 = V/Z_1, \text{ where } V \text{ is the supply voltage and } X_L = \omega L \text{ (the}$$

$$\text{inductive reactance). The phase angle of the current } \theta_1 = \tan^{-1} \frac{X_L}{R_L}.$$

Similarly, for branch 2

$$Z_2 = \sqrt{R_C^2 + X_C^2}, \text{ where } X_C = \frac{1}{\omega C} \text{ is the capacitive reactance and } I_2 = \frac{V}{Z_2}.$$

$$\text{The phase angle of the current is } \theta_2 = \tan^{-1} \frac{X_C}{R_C}.$$

The current I_1 lags behind the applied voltage by θ_1 and current I_2 leads the applied voltage by θ_2 as shown in Fig. 5.24(b).

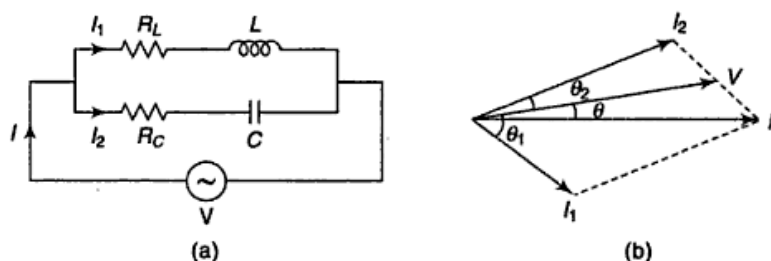


Fig. 5.24 (a) *RL circuit in parallel with RC circuit* (b) *Phasor diagram of voltage and current of Fig. 5.24(a)*

The resultant current I is the vector sum of I_1 and I_2 . Resolving I_1 and I_2 into the X and Y components and then by adding or subtracting [as in Fig. 5.25 (a)] we get

$$\text{Sum of } X \text{ axis components of } I_1 \text{ and } I_2 = I_1 \cos \theta_1 + I_2 \cos \theta_2.$$

$$\text{Sum of } Y \text{ axis components of } I_1 \text{ and } I_2 = -I_1 \sin \theta_1 + I_2 \sin \theta_2.$$

If θ be the phase angle of the resultant current I then

$$I \cos \theta = I_1 \cos \theta_1 + I_2 \cos \theta_2$$

$$I \sin \theta = -I_1 \sin \theta_1 + I_2 \sin \theta_2.$$

Squaring the above two equations on both sides and then by adding, we get

$$I^2 \cos^2 \theta + I^2 \sin^2 \theta = (I_1 \cos \theta_1 + I_2 \cos \theta_2)^2 + (-I_1 \sin \theta_1 + I_2 \sin \theta_2)^2$$

$$I = \sqrt{(I_1 \cos \theta_1 + I_2 \cos \theta_2)^2 + (-I_1 \sin \theta_1 + I_2 \sin \theta_2)^2}$$

$$\text{and the phase angle } \theta = \tan^{-1} \frac{-I_1 \sin \theta_1 + I_2 \sin \theta_2}{I_1 \cos \theta_1 + I_2 \cos \theta_2}.$$

The resultant current is shown in Fig. 5.25(b). If θ is positive the current I leads the applied voltage V and if θ is negative the current I lags the applied voltage V .

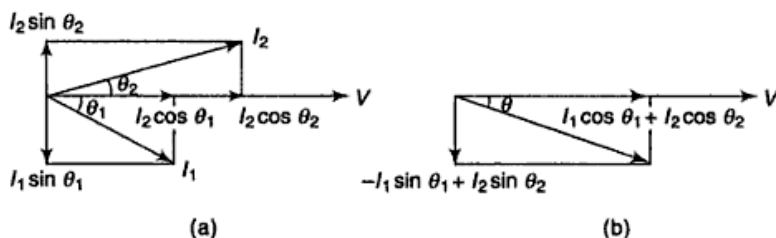


Fig. 5.25 *Branch currents in ac parallel circuit*

5.10 ADMITTANCE, CONDUCTANCE AND SUSCEPTANCE OF AC CIRCUIT

Admittance Y is the reciprocal of impedance Z of an ac circuit.

$$Y = \frac{1}{Z} = \frac{I}{V}$$

Just as impedance has two components viz., resistance R and reactance X , the admittance also has two components, viz. conductance G along the horizontal axis and susceptance B along the vertical axis [Fig. 5.26].

Hence, conductance (G) = $Y \cos \theta =$

$$\frac{1}{Z} \cdot \frac{R}{Z} = \frac{R}{Z^2}$$

and susceptance (B) = $Y \sin \theta = \frac{1}{Z} \cdot \frac{X}{Z} = \frac{X}{Z^2}$

$$\text{Admittance } (Y) = \sqrt{G^2 + B^2}$$

The units of Y , G and B are mho or ohm^{-1} or Siemens (S). It is to be noted that inductive susceptance is considered negative and capacitive susceptance is considered positive.

Use of Admittance in Solving Parallel Circuits

Consider a three branch parallel circuit, as shown in Fig. 5.27.

The total conductance, $G = g_1 +$

$g_2 + g_3$

and total susceptance, $B = -b_1 + b_2$

$$\text{Current in branch 1, } I_1 = \frac{V}{y_1}$$

$$\text{Current in branch 2, } I_2 = \frac{V}{y_2}$$

$$\text{Current in branch 3, } I_3 = \frac{V}{y_3}$$

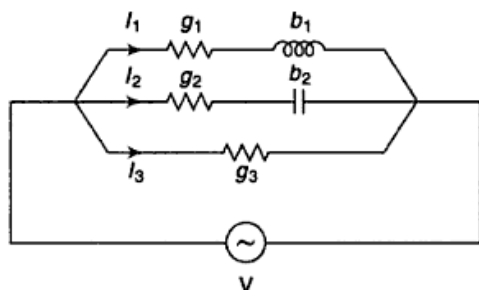


Fig. 5.27 Parallel ac circuit

$$\begin{aligned} \text{Net admittance } Y &= \sqrt{G^2 + B^2} = \sqrt{(g_1 + g_2 + g_3)^2 + (-b_1 + b_2)^2} \\ &= y_1 + y_2 + y_3. \end{aligned}$$

The current, $I = (V \cdot y)$ and the phase angle of the current is, $\theta = \tan^{-1} \frac{B}{G}$.

5.11 AVERAGE POWER IN AC CIRCUITS

Power in a dc circuit is given by $P_{dc} = VI = I^2 R = \frac{V^2}{R}$. In an ac circuit the instantaneous power is the power at any instant of time. It is equal to the product of voltage and current at that instant.

$$p = v \cdot i.$$

Like voltage and current, power is also continuously changing with time. So the average power is given by

$$P = \frac{1}{T} \int_0^T p \, dt.$$

By convention, P always means average power and no subscript is used.

$$\text{Also, } P = \frac{1}{2\pi} \int_0^{2\pi} p \, d\theta = \frac{1}{2\pi} \int_0^{2\pi} vi \, d\theta$$

Average power is also called *active power* or *real power* or *true power*. Its unit is watts.

5.11.1 Power in a Purely Resistive Circuit

In a purely resistive circuit voltage and current are in phase. Hence, $v = V_m \sin \theta$ and $i = I_m \sin \theta$.

Instantaneous power $p = vi = V_m I_m \sin^2 \theta = \frac{1}{2} V_m I_m (1 - \cos 2\theta)$. The voltage, current and power waveform are shown in Fig. 5.28.

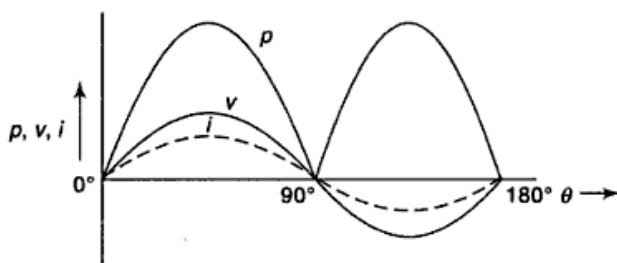


Fig. 5.28 Instantaneous power in a pure resistive circuit

The power waveform in Fig. 5.28 is obtained by multiplying together at every instant the corresponding (instantaneous) values of voltage and current. It is seen that p remains positive throughout the cycle irrespective of the direction of voltage and current in the circuit. This is due to the fact that as voltage and current are in phase so either both voltage and current are positive or both are negative at any instant of time. So their product (p) is always positive. This shows that power flow is only in the direction from the source to the load resistance (R) and this power is called active or real or true power (P_R).

$$\begin{aligned} \text{Active power } (P_R) &= \frac{1}{2\pi} \int_0^{2\pi} p \, d\theta = \frac{1}{2\pi} \int_0^{2\pi} \frac{1}{2} V_m I_m (1 - \cos 2\theta) \, d\theta \\ &= \frac{V_m I_m}{4\pi} \int_0^{2\pi} d\theta - \frac{V_m I_m}{4\pi} \int_0^{2\pi} \cos 2\theta \, d\theta \end{aligned}$$

$$\begin{aligned}
 &= \frac{V_m I_m}{4\pi} \times 2\pi - \frac{V_m I_m}{4\pi} \left[\frac{\sin 2\theta}{2} \right]_0^{2\pi} \\
 &= \frac{V_m I_m}{2} - \frac{V_m I_m}{4\pi} \times 0 = \frac{V_m I_m}{2} \\
 &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} = VI
 \end{aligned}$$

In a purely resistive circuit $P_R = VI = (IR)I = I^2 R = \left(\frac{V}{R}\right)^2 R = \frac{V^2}{R}$.

Also, the active or real power in ac circuit is $VI \cos \theta$. A simple reasoning leads to the conclusion that p.f. of a pure resistive circuit is 1 (one) and $\cos \theta$ is 1 ($\because VI \cos \theta = VI$, in pure resistive circuit). $VI = (V^2/R) = I^2 R$ is the energy dissipated in resistive circuit.

5.11.2 Power in a Purely Inductive Circuit

In a purely inductive circuit current lags the applied voltage by 90° .

So, $v = V_m \sin \theta$ and $i = I_m \sin \left(\theta - \frac{\pi}{2} \right)$

Instantaneous power (p) = $vi = V_m \sin \theta I_m \sin \left(\theta - \frac{\pi}{2} \right)$

$$= \frac{1}{2} \times 2V_m I_m \sin \theta \cos \theta = \frac{V_m I_m}{2} \sin 2\theta.$$

The voltage, current and power waveform are shown in Fig. 5.29.

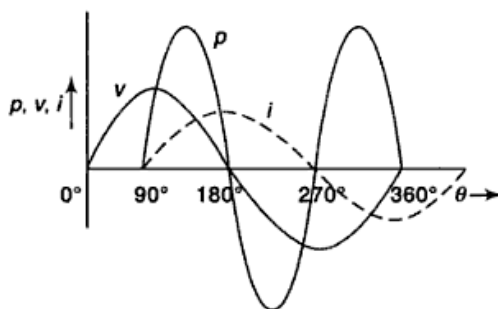


Fig. 5.29 Instantaneous power in pure inductive circuit

The power waveform in Fig. 5.29 is obtained by multiplying at every instant together the corresponding (or instantaneous) values of voltage and current.

The power curve is a sine wave of twice the frequency of the current and voltage wave. During the first quarter cycle, the power curve is above the hori-

zontal axis and is positive. The circuit draws energy from the source. This energy is stored in the magnetic field of the inductance. During the second quarter cycle the power curve is below the horizontal axis and is negative. The previously stored energy is now returned to the source. Thus energy stored in the circuit during the first quarter cycle is equal to the energy returned to the source during the second quarter cycle in ideal inductive circuits. So the total energy dissipated, called the *active energy*, during every cycle of the current is zero. The rate of energy dissipated, called the active or average power over the complete cycle of the current in a purely inductive circuit, is also zero.

$$\begin{aligned}\text{Active power } P_L &= \frac{1}{2\pi} \int_0^{2\pi} p \, d\theta = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \sin 2\theta \, d\theta \\ &= \frac{V_m I_m}{4\pi} \times \frac{1}{2} [-\cos 2\theta]_0^{2\pi} \\ &= -\frac{V_m I_m}{8\pi} [\cos 4\pi - \cos 0] \\ &= -\frac{V_m I_m}{8\pi} [1 - 1] \\ &= 0.\end{aligned}$$

Thus in a purely inductive circuit the active power over a complete cycle is zero.

The peak value of (p) is $\frac{V_m I_m}{2} = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} = VI$

Reactive power Q_L

In a purely inductive circuit $V = V_L = X_L I$, where X_L is the inductive reactance.

$$\text{Reactive power } Q_L = V_L I = I^2 X_L$$

or
$$Q_L = \frac{V_L^2}{X_L} \text{ VAR (volt-ampere reactive).}$$

Q_L is called the *reactive volt amperes* for an inductive circuit. It is measured in VAR. The energy which is continually exchanged between the source and the reactive load is called the *reactive energy*. By convention Q_L is considered positive for inductive circuits.

Also, $Q_L = VI \sin \theta$, (θ) being 90° for pure inductive circuits. Obviously ($\cos \theta$) for inductance is zero.

5.11.3 Power in a Purely Capacitive Circuit

In a purely capacitive circuit the current leads the applied voltage by 90° .

So,
$$v = V_m \sin \theta \text{ and } i = I_m \sin \left(\theta + \frac{\pi}{2} \right)$$

$$\text{Instantaneous power } p = vi = V_m I_m \sin \theta \sin \left(\theta + \frac{\pi}{2} \right)$$

$$= V_m I_m \sin \theta \cos \theta = \frac{1}{2} V_m I_m \cdot 2 \sin \theta \cos \theta$$

$$= \frac{V_m I_m}{2} \sin 2\theta.$$

The voltage, current and power waveform are shown in Fig. 5.30.

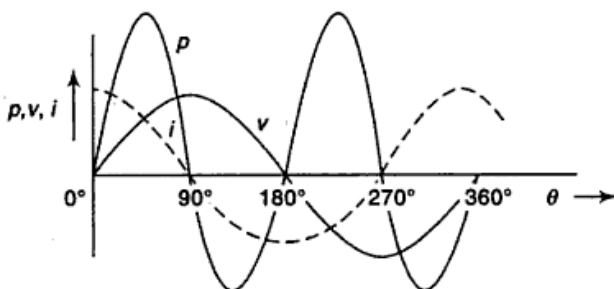


Fig. 5.30 Instantaneous power in pure capacitive circuit

The power curve is a sine wave of twice the frequency of the current or voltage curve. During the first quarter cycle the power curve is above the horizontal axis and is positive. The circuit draws energy from the source and the capacitor is charged. The energy is stored in the electric field of the capacitor. During the second quarter cycle the power curve is below the horizontal axis and is negative. The capacitor is discharged and the energy from the dielectric field is returned to the source. The energy stored in the electric field during the first quarter cycle is equal to the energy returned to the source during the second quarter cycle in a purely capacitive circuit. Therefore the total active energy during each cycle of the current is zero. The active power over a complete cycle of current in a purely capacitive circuit is zero.

$$\text{Active power } (P_C) = \frac{1}{2\pi} \int_0^{2\pi} p \, d\theta = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \sin 2\theta \, d\theta$$

$$= \frac{V_m I_m}{4\pi} \left[\frac{-\cos 2\theta}{2} \right]_0^{2\pi}$$

$$= \frac{-V_m I_m}{8\pi} [\cos 4\pi - \cos 0^\circ]$$

$$= \frac{-V_m I_m}{8\pi} [1 - 1] = 0$$

Reactive power (Q_C)

The peak value of (p) is $\frac{I_m V_m}{2} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} = VI$.

In a purely capacitive circuit

$$V = V_C = IX_C,$$

$$\therefore Q_C = V_C I = I^2 X_C = \frac{V_C^2}{X_C} \text{ VAR.}$$

Q_C is called the reactive volt amperes for a capacitive circuit. It is measured in VAR. It is the rate of interchange of reactive energy between a capacitive load and the source. By convention Q_C is considered negative. Obviously, $Q_C = VI \sin \theta$, θ being 90° . Power factor of such a circuit is also zero.

5.11.4 Power in a General Series Circuit

Consider a general case where $v = V_m \sin \theta$ and $i = I_m \sin(\theta - \phi)$, where ϕ is the phase angle of the current with respect to the voltage.

Instantaneous power $p = vi$

$$\begin{aligned} &= V_m I_m \sin \theta \sin(\theta - \phi) \\ &= \frac{V_m I_m}{2} [\cos \phi - \cos(2\theta - \phi)] \end{aligned}$$

Active power

$$\begin{aligned} P &= \frac{1}{2\pi} \int_0^{2\pi} p \, d\theta = \frac{V_m I_m}{2\pi \times 2} \int_0^{2\pi} [\cos \phi - \cos(2\theta - \phi)] \, d\theta \\ &= \frac{V_m I_m}{4\pi} \int_0^{2\pi} \cos \phi \, d\theta - \frac{V_m I_m}{4\pi} \int_0^{2\pi} \cos(2\theta - \phi) \, d\theta \\ &= \frac{V_m I_m}{4\pi} \cos \phi [\theta]_0^{2\pi} - \frac{V_m I_m}{4\pi} \left[\frac{1}{2} \sin(2\theta - \phi) \right]_0^{2\pi} \\ &= \frac{(\sqrt{2}V)(\sqrt{2}I)}{4\pi} (\cos \phi) (2\pi) - \frac{V_m I_m}{8\pi} [\sin(4\pi - \phi) - \sin(-\phi)] \\ &= VI \cos \phi - \frac{V_m I_m}{8\pi} [-\sin \phi + \sin \phi] \\ &= VI \cos \phi. \end{aligned}$$

The voltage, current and power waveform are shown in Fig. 5.31.

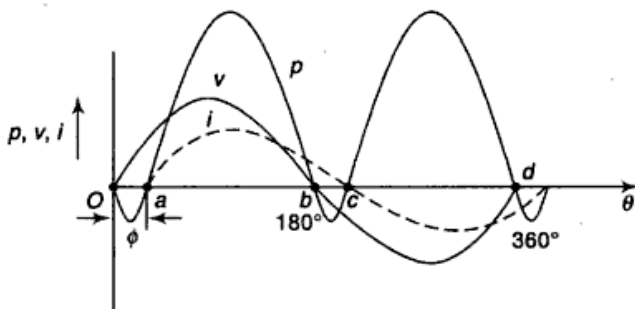


Fig. 5.31 Instantaneous power in RLC series circuit

From the power curve it is observed that during the interval Oa the power is negative. During the interval ab the power is positive. The interval bc is the repetition of interval Oa and interval cd is the repetition of interval ab . The negative area under curve p between interval Oa represents the energy returned from the circuit to the source. The positive area under curve p in the interval ab represents the energy supplied from the source to the load. So, during each current or voltage cycle a part of the energy called active energy is consumed, while the other part called the reactive energy is interchanged between the source and the load. The rate of energy consumption is the active power. The difference between the total positive and total negative areas during a cycle of current or voltage gives the net active energy of the circuit.

5.11.5 Voltamperes Power (Complex Power)

The product of rms values of voltage and current in a circuit is called the *circuit voltamperes*. It is also called *apparent power* or *complex power*. It is denoted by S and is measured in voltamperes VA.

$$S = VI = (IZ)I = I^2Z; \text{ Also, } S = P + jQ = \sqrt{P^2 + Q^2} \left(\tan^{-1} \frac{Q}{P} \right)$$

5.11.6 Power Triangle

From the previous sections we know that

$$P_R = V_R I \quad \text{and} \quad Q_R = 0, \text{ for purely resistive circuit}$$

$$P_L = 0 \quad \text{and} \quad Q_L = (V_L I) \text{ for purely inductive circuit}$$

$$P_C = 0 \quad \text{and} \quad Q_C = (V_C I) \text{ for purely capacitive circuit.}$$

The net reactive power in the RLC series circuit is $Q = Q_L - Q_C$

[$\because Q_L$ is considered positive and Q_C negative]

$$= I^2 X_L - I^2 X_C = I^2 (X_L - X_C) = I^2 X$$

The active power $P = P_R = I^2 R$.

The impedance triangle is represented in Fig. 5.32

Multiplying each side of the impedance triangle by I^2 we get the power triangle as shown in Fig. 5.32(b).

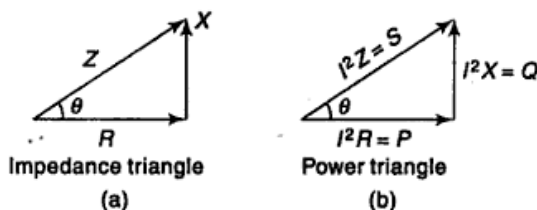


Fig. 5.32 (a) Impedance triangle (b) Power triangle

Here, $P = S \cos \theta$ and $Q = S \sin \theta$

As $S = VI$,

Hence, $P = VI \cos \theta$ and $Q = VI \sin \theta$

Also $|S| = \sqrt{P^2 + Q^2}$ and $\theta = \tan^{-1} \frac{Q}{P}$.

A power triangle can be obtained from a voltage triangle by multiplying each of its sides by the current as shown in Fig. 5.33.

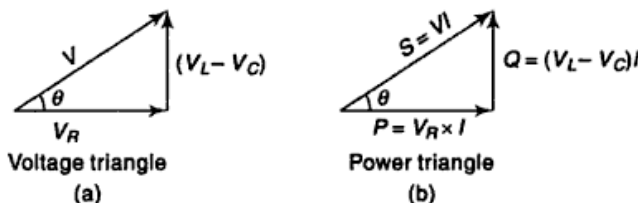


Fig. 5.33 (a) Voltage triangle and (b) Power triangle

5.11.7 Power Factor in Resistive, Inductive and Capacitive Circuit

The ratio of the active power to the apparent power in an ac circuit is defined as the *power factor* (p.f.) of the circuit.

$$\text{Power factor} = \frac{P}{S} = \frac{VI \cos \theta}{VI} = \cos \theta$$

So power factor in an ac circuit is also equal to the cosine of the phase angle between the applied voltage and the circuit current.

The power factor is lagging in a circuit in which the current lags the applied voltage. An inductive circuit has lagging power factor.

The power factor is leading in a circuit where the current leads the applied voltage. A capacitive circuit has the leading power factor.

From the impedance triangle, power factor is also given by

$$\cos \theta = \frac{R}{Z}$$

From voltage triangle power factor can be obtained as

$$\cos \theta = \frac{V_R}{V}$$

Combining all results,

$$\text{p.f.} = \cos \theta = \frac{P}{S} = \frac{R}{Z} = \frac{V_R}{V}.$$

For purely resistive circuit $\text{p.f.} = \cos 0^\circ = 1$.

For purely inductive and capacitive circuits $\text{p.f.} = \cos 90^\circ = 0$.

We know that power consumed in a circuit is $VI \cos \theta$

Power consumed in a purely resistive circuit $= VI \cos 0^\circ = VI$

Power consumed in a purely inductive or purely capacitive circuit $= VI \cos 90^\circ = 0$.

Hence, we can conclude that the power is consumed only in the resistor and there is no power consumption in either the pure inductor or the pure capacitor.

5.11.8 Active and Reactive Components of Current

When the current is not in phase with the voltage it lags or leads the applied voltage by an angle θ . The component of the current which is in phase with the voltage namely ($I \cos \theta$) is called the *active component* of current. The other component which is in quadrature with the voltage namely ($I \sin \theta$) is called the *reactive component* of current.

5.21 Two inductive coils A and B are connected in parallel across a 200 V, 50 Hz. supply. Coil A takes 15 A and 0.85 p.f. and the supply current is 30 A and 0.8 p.f. Determine the (a) equivalent resistance and equivalent reactance and (b) resistance and reactance of each coil.

Solution

Considering supply voltage V as the reference phasor,

$$V = 200 \angle 0^\circ$$

$$I_1 = 15 \angle -\cos^{-1} 0.85 = 15 \angle -31.79^\circ \text{ A}$$

The power factor is lagging since the coil is inductive.

$$\text{Total current } I = 30 \angle -\cos^{-1} 0.8 = 30 \angle -36.86^\circ \text{ A.}$$

(a) Equivalent impedance of the circuit

$$Z_{eq} = \frac{V}{I} = \frac{200 \angle 0^\circ}{30 \angle -36.86^\circ} = 6.67 \angle 36.86^\circ \Omega.$$

Hence, equivalent resistance (R_{eq}) $= 6.67 \cos 36.86^\circ = 5.336 \Omega$ and equivalent reactance (X_{eq}) $= 6.67 \sin 36.86^\circ = 4 \Omega$.

(b) If I_2 be the current in coil B lagging by θ angle with respect to the supply voltage, then the horizontal and vertical components of I_2 are

$$I_{2x} = I_2 \cos (-\theta) \text{ and } I_{2y} = I_2 \sin (-\theta)$$

$$\text{Similarly, } I_{1x} = I_1 \cos (-31.79^\circ) = 15 \cos (-31.79^\circ) = 12.75 \text{ A}$$

$$\text{and } I_{1y} = I_1 \sin (-31.79^\circ) = -15 \sin 31.79^\circ = -7.9 \text{ A.}$$

The two components of I are

$$I_x = 30 \cos (-36.86^\circ) = 24 \text{ A}$$

$$\text{and } I_y = 30 \sin (-36.86^\circ) = -18 \text{ A.}$$

$$\text{Since, } I_x = I_{1x} + I_{2x}$$

$$\text{and } I_y = I_{1y} + I_{2y}$$

So $24 = 12.75 + I_{2x}$
 or $I_{2x} = 24 - 12.75 = 11.25 \text{ A}$
 and $-18 = -7.9 + I_{2y}$
 or $I_{2y} = +7.9 - 18 = -10.1 \text{ A}.$

Thus the current in coil 2 is $\sqrt{(11.25)^2 + (10.1)^2} \angle \tan^{-1} \frac{-10.1}{11.25}$
 $= 15.1186 \angle -41.917^\circ \text{ A}.$

The impedance of coil 2 is $(Z_2) = \frac{V}{I_2} = \frac{200 \angle 0^\circ}{15.1186 \angle -41.917^\circ}$
 $= 13.229 \angle 41.917^\circ \Omega.$

The resistance of coil 2 is $(R_2) = 13.229 \cos 41.917^\circ = 9.844 \Omega$ and the reactance of coil 2 is $X_2 = 13.229 \sin 41.917^\circ = 8.837 \Omega.$

5.22 Find the branch currents, total current, Z and Y , apparent, active and reactive power and power factor in the parallel circuit shown in Fig. 5.34.

Solution

Let us consider the supply voltage as reference.

The current in second branch 2,

$$I_2 = \frac{100 \angle 0^\circ}{20 \Omega} = 5 \angle 0^\circ \text{ A}.$$

The current in branch 1, $I_1 = \frac{V}{z_1}$.

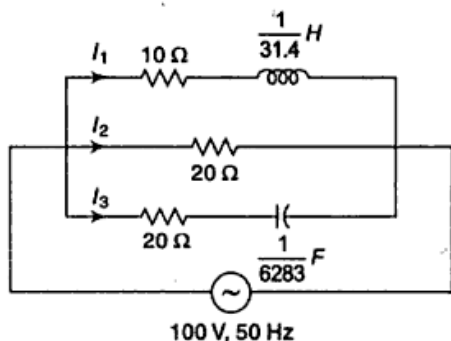


Fig. 5.34 Circuit diagram for Ex. 5.22

$$Z_1 = \sqrt{(10)^2 + \left(100\pi \times \frac{1}{31.4}\right)^2} \angle \tan^{-1} \frac{100\pi \times \frac{1}{31.4}}{10}$$

$$= 14.14 \angle 45^\circ \Omega$$

$$\therefore I_1 = \frac{100 \angle 0^\circ}{14.14} \angle -45^\circ = 7.07 \angle -45^\circ \text{ A}.$$

The impedance of branch 3, $Z_3 = \sqrt{(20)^2 + \left(\frac{6283}{100\pi}\right)^2} \angle -\tan^{-1} \frac{6283}{20}$
 $= 28.29 \angle -45^\circ \Omega.$

The current in branch 3, $I_3 = \frac{100 \angle 0^\circ}{28.29 \angle -45^\circ} = 3.53 \angle 45^\circ \text{ A}.$

Total admittance

$$y = y_1 + y_2 + y_3$$

$$= \frac{1}{z_1} + \frac{1}{z_2} + \frac{1}{z_3}$$

$$= \frac{1}{14.14 \angle 45^\circ} + \frac{1}{20} + \frac{1}{28.29 \angle -45^\circ}$$

$$= 0.0707 \angle -45^\circ + 0.05 + 0.035 \angle 45^\circ.$$

Now, horizontal component of y is

$$y_x = 0.0707 \cos(-45^\circ) + 0.05 \cos 0^\circ + 0.035 \cos 45^\circ \\ = 0.1247 \text{ Siemens}$$

and vertical component of y is

$$y_y = 0.0707 \sin(-45^\circ) + 0.05 \sin 0^\circ + 0.035 \sin 45^\circ \\ = -0.025 \text{ Siemens.}$$

Therefore

$$y = \sqrt{y_x^2 + y_y^2} \angle \tan^{-1} \frac{y_y}{y_x} \\ = \sqrt{(0.1247)^2 + (-0.025)^2} \angle \tan^{-1} \frac{-0.025}{0.1247} \\ = 0.127 \angle -11.336^\circ \text{ Siemens}$$

$$\therefore Z = \frac{1}{y} = \frac{1}{0.127 \angle -11.336^\circ} = 7.87 \angle 11.336^\circ \Omega.$$

Total current $I = VY = 100 \angle 0^\circ \times 0.127 \angle -11.336^\circ = 12.7 \angle -11.336^\circ \text{ A.}$

Apparent power $(VI) = 100 \times 12.7 = 1270 \text{ VA.}$

Active power $(VI \cos \theta) = 100 \times 12.7 \cos(11.336^\circ) = 1245 \text{ W.}$

Reactive power $(VI \sin \theta) = 100 \times 12.7 \sin(11.336^\circ) = 249.63 \text{ VAR (inductive).}$

Power factor $(\cos \theta) = \cos 11.336^\circ = 0.98 \text{ lagging.}$

5.23 A lamp rated 400 W takes a current of 4 A when in series with an inductance.

(a) Find the value of the inductance connected in series to operate the combination from 240 V, 50 Hz mains (b) Also find the value of the capacitance which should be connected in parallel with the above combination to raise the overall power factor to unity.

Solution

The resistance of the lamp $R = \frac{P}{I^2} = \frac{400}{(4)^2} = 25 \Omega.$

Voltage across the lamp $= IR = 4 \times 25 = 100 \text{ V.}$

(a) The impedance of the circuit $\frac{V}{I} = \frac{240}{4} = 60 \Omega.$

If V_L is the voltage across inductance

$$V^2 = V_R^2 + V_L^2$$

or $V_L = \sqrt{V^2 - V_R^2} = \sqrt{(240)^2 - (100)^2} = 218.17 \text{ V.}$

So the inductive reactance $= \frac{V_L}{I} = \frac{218.17}{4} = 54.54 \Omega$

and the inductance $= \frac{54.54}{\omega} = \frac{54.54}{2\pi \times 50} = 0.173 \text{ H.}$

(b) Let I_C be the current through the capacitance.

The current through the inductive coil is I_L . If the overall power factor is unity the vertical component of total current (I) is 0.

$$\therefore I_C + 4 \sin(-65.37^\circ) = 0$$

or $I_C = 4 \sin 65.37^\circ = 3.636 \text{ A.}$

Hence, capacitive reactance $(X_C) = \frac{V}{I_C} = \frac{100}{3.636} = 27.5 \Omega$

and capacitance $= \frac{1}{100\pi \times 27.5} \text{ F} = 115.79 \mu\text{F}.$

.....

5.24 A fluorescent lamp taking 100W at 0.75 p.f. lagging from a 240 V, 50 Hz. supply is to be corrected to unity p.f. Determine the value of the correcting apparatus required.

Solution

Power = 100 W

p.f. = 0.75 lagging

Voltage = 240 V

$\therefore VI \cos \theta = P,$

$\therefore I = \frac{100}{240 \times 0.75} = 0.555 \angle -\cos^{-1} 0.75 = 0.555 \angle -41.41^\circ \text{ A}$

and impedance $(Z) = \frac{V}{I} = \frac{240}{0.555} \Omega = 432.43 \Omega.$

If the power factor becomes unity the net reactive components of current is zero and to improve p.f. from 0.75 lag to 1, a capacitance should be connected in parallel. If I_C be the capacitive current,

net reactive component of current $= I_C + 0.555 \sin(-41.41^\circ) = 0.$

So $I_C = 0.555 \sin 41.41^\circ = 0.367 \text{ A}.$

\therefore capacitive reactance $(X_C) = \frac{V}{I_C} = \frac{240}{0.367} = 653.95 \Omega$

and capacitance $= \frac{1}{100\pi \times 653.95} \text{ F} = 4.87 \mu\text{F}.$

.....

5.25 A 40 kW load takes a current of 20 A from a 240 V ac supply. Calculate the kVA and KVAR of the load.

Solution

$V = 240 \text{ V}$

$I = 20 \text{ A}$

$P = 40 \text{ kW}.$

If $\cos \theta$ be the power factor then

$VI \cos \theta = P$ or, $240 \times 20 \times \cos \theta = 4000$

or $\cos \theta = \frac{4000}{240 \times 20} = 0.833.$

Therefore, $\sin \theta = 0.553$

$\text{kVA} (= VI) = \frac{240 \times 20}{10^3} = 4.8 \text{ kVA}$

and $\text{KVAR} (= VI \sin \theta) = \frac{240 \times 20 \times 0.553}{10^3} \text{ KVAR} = 2.65 \text{ KVAR}.$

.....

5.26. A 240 V, single phase induction motor delivers 15 kW at full load. The efficiency of the motor at this load is 82% and the p.f. is 0.8 lagging. Calculate (a) the input current of the motor, (b) the kW input and (c) kVA input.

Solution

$$\left. \begin{array}{l} V = 240 \text{ V} \\ \eta = 82\% \\ \cos \theta = 0.8 \text{ lag} \end{array} \right\} \text{(given)}$$

$$\text{Output power} = 15 \text{ kW} = 15,000 \text{ W}$$

$$\text{So, input power (P)} = \frac{\text{Output power}}{\text{Efficiency}} = \frac{15,000}{0.82} = 18292.68 \text{ W.}$$

$$(a) \text{ If } I \text{ be the input current then } VI \cos \theta = P$$

$$\text{or } I = \frac{P}{V \cos \theta} = \frac{18292.68}{240 \times 0.8} \text{ A} = 95.27 \text{ A.}$$

$$(b) \text{ kW input} = \frac{18292.68}{10^3} = 18.29.$$

$$(c) \text{ kVA input} = VI = \frac{240 \times 95.27}{10^3} = 22.86.$$

.....

5.27. A single phase 50 Hz motor takes 100 A at 0.85 p.f. lagging from a 240 V supply. Calculate the (a) active and reactive components of the current and (b) the power taken from the supply.

Solution

$$\begin{aligned} I &= 100 \text{ A} \\ \cos \theta &= 0.85 \\ V &= 240 \text{ V.} \end{aligned}$$

$$(a) \text{ Active component of current } (I \cos \theta) = 100 \times 0.85 = 85 \text{ A.}$$

$$\begin{aligned} \text{Reactive component of current } (I \sin \theta) &= 100 \sqrt{1 - (0.85)^2} \\ &= 52.67 \text{ A.} \end{aligned}$$

$$(b) \text{ Real power taken from the supply } (VI \cos \theta) = 240 \times 100 \times 0.85 = 20400 \text{ W} = 20.4 \text{ kW.}$$

.....

5.28. A series RL circuit having $R = 15 \Omega$ and $L = 0.03 \text{ H}$ is connected across a 240 V, 50 Hz. supply. Find the (a) rms current in the circuit; (b) average power absorbed by the inductance and (c) the power factor of the circuit.

Solution

$$\begin{aligned} R &= 15 \Omega \\ X_L &= 2\pi fL = 2\pi \times 50 \times 0.03 = 9.42 \Omega \\ Z &= \sqrt{R^2 + X_L^2} = \sqrt{(15)^2 + (9.42)^2} = 17.71 \Omega. \end{aligned}$$

$$(a) \text{ rms current } |I| = \frac{V}{Z} = \frac{240}{17.71} = 13.55 \text{ A.}$$

(b) Average power absorbed by the inductance is 0.

(c) Power factor of the circuit $\frac{R}{Z} = \frac{15}{17.71} = 0.847$ lag.

.....

5.29. A 200 V, 50 Hz. inductive circuit takes a current of 15 A, lagging the voltage by 45° . Calculate the resistance and inductance of the circuit.

Solution

$$V = 200 \text{ V}$$

$$I = 15 \text{ A}$$

$$\cos \theta = \cos 45^\circ = 0.707$$

$$\text{Impedance } Z = \frac{V}{I} = \frac{200}{15} = 13.33 \Omega.$$

$$\text{Resistance } R = Z \cos \theta = 13.33 \cos 45^\circ = 9.42 \Omega.$$

$$\text{Inductive reactance } X_L = Z \sin \theta = 13.33 \sin 45^\circ = 9.42 \Omega.$$

$$\text{Hence the inductance } L = \frac{X_L}{\omega} = \frac{9.42}{2\pi \times 50} \text{ H} = 0.03 \text{ H}.$$

.....

5.30. A 2-element series circuit consumes 700 W and has a p.f. of 0.707 leading. If the applied voltage is $v = 141 \sin(314t + 30^\circ)$ find the circuit constants.

Solution

As p.f. is leading so the circuit contains a capacitor along with a resistor.

$$\text{Power } (P) = 700 \text{ W}$$

$$\text{p.f. } (\cos \theta) = 0.707, \text{ hence } (\sin \theta) = \sin(\cos^{-1} 0.707) = 0.707$$

$$\text{Instantaneous voltage } (v) = 141 \sin(314t + 30^\circ)$$

$$\text{rms value of voltage } (V) = \frac{141}{\sqrt{2}} = 100 \text{ V}.$$

$$\text{Angular frequency } (\omega) = 314 \text{ rad/s}.$$

If I be the rms value of current then,

$$P = VI \cos \theta$$

$$\text{or } I = \frac{P}{V \cos \theta} = \frac{700}{100 \times 0.707} \text{ A} = 9.9 \text{ A}.$$

$$\text{Now, Impedance } Z = \frac{V}{I} = \frac{100}{9.9} \Omega = 10.1 \Omega.$$

$$\therefore \text{Resistance } (R) = Z \cos \theta = 10.1 \times 0.707 = 7.14 \Omega \text{ and capacitive reactance } (X_C) = Z \sin \theta = 10.1 \times 0.707 = 7.14 \Omega.$$

$$\text{Therefore, capacitance } C = \frac{1}{\omega X_C} = \frac{1}{314 \times 7.14} \text{ F} = 446 \mu\text{F}.$$

Hence the circuit constants are 7.14Ω and $446 \mu\text{F}$.

.....

5.31. A circuit takes a current of 3 A at a p.f. of 0.6 lagging when connected to a 115 V, 50 Hz supply. Another circuit takes a current of 5 A at a p.f. of 0.707 leading when connected to the same supply. If the two circuits are connected in series across a 230 V, 50 Hz. supply, calculate (a) the current (b) the power consumed and (c) the p.f. of the circuit.

Solution

As the p.f. is lagging in the first circuit so it contains a resistor along with an inductor. The second circuit contains a resistor along with a capacitor as the p.f. is leading in that circuit. The circuit is shown in Fig. 5.35.

Supply voltage $V = 230$ V,

Frequency $f = 50$ Hz.

For circuit 1,

$$I = 3 \text{ A, } \cos \theta = 0.6 \text{ lag, and } V = 115 \text{ V}$$

$$\therefore |Z| = \frac{V}{I} = \frac{115}{3} = 38.33 \Omega$$

$$R_L = Z \cos \theta = 38.33 \times 0.6 = 22.998 \Omega$$

$$X_L = Z \sin \theta = 38.33 \times \sin (\cos^{-1} 0.6) = 30.664 \Omega.$$

For circuit 2,

$$I = 5 \text{ A, } \cos \theta = 0.707 \text{ lead and } V = 115 \text{ V.}$$

$$\therefore |Z| = \frac{V}{I} = \frac{115}{5} = 23 \Omega$$

$$R_C = Z \cos \theta = 23 \times 0.707 = 16.261 \Omega$$

$$X_C = Z \sin \theta = 23 \times \sin (\cos^{-1} 0.707) \\ = 16.261 \Omega$$

when the two circuits are connected in series,

$$\begin{aligned} \text{Impedance} &= \sqrt{(R_L + R_C)^2 + (X_L - X_C)^2} \\ &= \sqrt{(39.259)^2 + (14.403)^2} = 41.81 \Omega \end{aligned}$$

$$(a) \text{ The current } (I) = \frac{V}{Z} = \frac{230}{41.81} \text{ A} = 5.5 \text{ A.}$$

(b) The power is consumed in the resistors only.

$$\begin{aligned} \therefore \text{the power consumed} &= I^2(R_L + R_C) \\ &= (5.5)^2 (39.259) \\ &= 1187.58 \text{ W} \\ &= 1.187 \text{ kW.} \end{aligned}$$

$$\begin{aligned} (c) \text{ Power factor of the circuit} &= \frac{\text{Net resistance}}{\text{Net impedance}} \\ &= \frac{39.259}{41.81} = 0.94. \end{aligned}$$

As $X_L > X_C$ so the p.f. is lagging. Therefore p.f. of the circuit is 0.94 lagging.

5.32 The impedances Z_1 and Z_2 are connected in parallel across a 200 V, 50 Hz single phase ac supply. Z_1 carries 2 A at 0.8 lag p.f. If the total current is 5 A at 0.985 lagging p.f., determine (a) value of Z_1 and Z_2 (b) total power and power consumed by Z_2 .

Solution

For the 1st circuit,

$$V = 200 \text{ V}$$

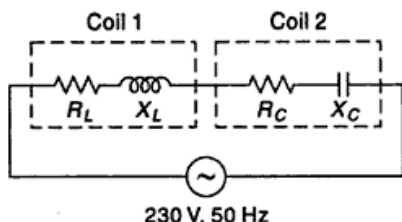


Fig. 5.35 Circuit diagram for Ex. 5.31

$$I_1 = 2 \text{ A}$$

$$\cos \theta_1 = 0.8 \text{ lag so } \theta_1 = \cos^{-1} 0.8 = 36.86^\circ (\text{lag}).$$

$$|Z_1| = \frac{V}{I} = \frac{200}{2} = 100 \Omega. \text{ Also, } \sin \theta_1 = 0.6$$

$$\text{Resistance } R_1 = Z_1 \cos \theta_1 = 100 \times 0.8 = 80 \Omega.$$

$$\text{Inductive reactance } X_L = Z \sin \theta = 100 \times 0.6 = 60 \Omega.$$

$$\text{Total current } (I) = 5 \text{ A and net p.f. } (\cos \theta) = 0.985 \text{ lag.}$$

$$\text{So } \theta = \cos^{-1} (0.985) = 9.93^\circ$$

$$\text{and } \sin \theta = 0.172$$

$$\begin{aligned} \text{Total power} &= VI \cos \theta \\ &= 200 \times 5 \times 0.985 \\ &= 985 \text{ W} \end{aligned}$$

$$\text{Total } |Z| = \frac{V}{I} = \frac{200}{5} = 40 \Omega.$$

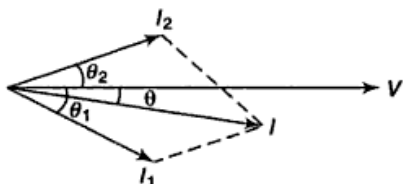


Fig. 5.36 Phasor diagram

The phasor diagram is shown in Fig. 5.36

$$\text{Horizontal component of } I_1 \text{ is } I_{1x} = I_1 \cos \theta_1 = 2 \times 0.8 = 1.6 \text{ A}$$

$$\text{Horizontal component of } I \text{ is } I_x = I \cos \theta = 5 \times 0.985 = 4.925 \text{ A}$$

$$\text{Vertical component of } I_1 \text{ is } I_{1y} = -I_1 \sin \theta_1 = 2 \times 0.6 = -1.2 \text{ A}$$

$$\text{Vertical component of } I \text{ is } I_y = -I \sin \theta = -5 \times 0.172 = -0.86 \text{ A.}$$

If I_{2x} and I_{2y} be the horizontal and vertical component of the current in the second circuit then

$$I_x = I_{1x} + I_{2x}$$

$$\text{and } I_y = I_{1y} + I_{2y}$$

$$\text{So, } I_{2x} = I_x - I_{1x} = 4.925 - 1.6 = 3.325$$

$$\text{and } I_{2y} = I_y - I_{1y} = -0.86 + 1.2 = +0.34.$$

$$\begin{aligned} \text{The current in circuit 2 is } (I_2) &= \sqrt{I_x^2 + I_y^2} = \sqrt{(3.325)^2 + (0.34)^2} \\ &= 3.34 \text{ A.} \end{aligned}$$

$$\text{Impedance } Z_2 = \frac{V}{I_2} = \frac{200}{3.34} \Omega = 59.88 \Omega.$$

$$\text{Power factor of circuit 2} = \frac{I_{2x}}{I_2} = \frac{3.325}{3.34} = 0.9955.$$

$$\begin{aligned} \text{Hence power consumed by } Z_2 \text{ is } P_2 &= VI_2 \cos \theta_2 \\ &= 200 \times 3.34 (0.9955) \\ &= 665 \text{ W.} \end{aligned}$$

.....

5.33 An iron cored electromagnet has a dc resistance of 7.5Ω and when connected to a 400 V, 50 Hz supply takes 10 A and consumes 2 kW. Calculate for this value of current (a) power loss in iron core, (b) the inductance of coil, (c) the p.f., and (d) the value of series resistance which is equivalent to the effect of iron loss.

Solution

When the electromagnet is connected to a dc source it is required to consider the resistance of the coil only.

$$\text{Given, resistance of coil } (R_c) = 7.5 \Omega.$$

When connected to ac source both the resistance of the coil and the equivalent resistance of iron part should be considered.

However, $V = 400$ V; $I = 10$ A and $P (= 2 \text{ kW}) = 2000$ W.

$$\text{Equivalent impedance } Z = \frac{V}{I} = \frac{400}{10} = 40 \Omega.$$

$$\text{Power factor } (\cos \theta) = \frac{P}{VI} = \frac{2000}{400 \times 10} = 0.5.$$

$$\text{Total resistance} = Z \cos \theta = 40 \times 0.5 = 20 \Omega$$

$$\text{Total reactance} = Z \sin \theta = 40 \sin (\cos^{-1} 0.5) = 34.64 \Omega.$$

$$\therefore \text{resistance of iron core} = 20 - 7.5 = 12.5 \Omega.$$

$$(a) \text{ Power loss in iron core is } I^2 \times 12.5 = (10)^2 \times 12.5 = 1250 \text{ W} = (1.25 \text{ kW}).$$

$$(b) \text{ Inductance of coil} = \frac{34.64}{\omega} = \frac{34.64}{100\pi} = 0.1103 \text{ H}$$

$$(c) \text{ Power factor } (\cos \theta) = 0.5$$

$$(d) \text{ The value of series resistance is } 12.5 \text{ ohm which is equivalent to iron loss.}$$

5.34 An iron cored choking coil takes 4 A at p.f. of 0.5 when connected to a 200 V, 50 Hz. supply. When the core is removed and the applied voltage is reduced to 50 V 50 Hz, the current is 8 A and the p.f. 0.8 lag. Calculate the (a) core loss and (b) inductance of the choke with and without the core.

Solution

With core,

$$V = 200 \text{ V}; \cos \theta = 0.5 \text{ and } I = 4 \text{ A.}$$

$$\text{Hence } |Z| = \frac{V}{I} = \frac{200}{4} = 50 \Omega.$$

$$\text{Resistance of core along with coil} = Z \cos \theta = 50 \times 0.5 = 25 \Omega.$$

$$\text{Reactance of the core and coil} = Z \sin \theta = 50 \sin (\cos^{-1} 0.5) = 43.3 \Omega.$$

Without core,

$$V = 50 \text{ V}; I = 8 \text{ A and } \cos \theta = 0.8.$$

$$\text{Hence } |Z| = \frac{V}{I} = \frac{50}{8} = 6.25 \Omega.$$

$$\text{Resistance of coil } (Z \cos \theta) = 6.25 \times 0.8 = 5 \Omega$$

$$\text{Reactance of coil } (Z \sin \theta) = 6.25 \times \sin (\cos^{-1} 0.8) = 3.75 \Omega.$$

$$\therefore \text{Resistance of core} = 25 - 5 = 20 \Omega.$$

$$\text{Core loss} = I^2 \times (\text{Resistance of core}) = (4)^2 \times 20 = 320 \text{ W.}$$

$$\begin{aligned} \text{Inductance of choke with core} &= \frac{43.3}{\omega} = \frac{43.3}{2\pi \times 50} = 0.13791 \\ &= 137.9 \text{ mH} \end{aligned}$$

$$\begin{aligned} \text{Inductance of choke without core} &= \frac{3.75}{\omega} = \frac{3.75}{2\pi \times 50} = 0.01191 \text{ H} \\ &= 11.9 \text{ mH.} \end{aligned}$$

5.35 The following loads are connected in parallel:

$$(a) 100 \text{ kVA at } 0.8 \text{ p.f. lagging.}$$

(b) 250 kVA at 0.8 p.f. leading,

(c) 200 kVA at 0.6 p.f. lagging

(d) 50 kW at unity p.f.

Determine (a) the total kVA, (b) total kW, (c) total KVAR and (d) the overall p.f.

Solution

$$\begin{aligned}\text{Total kW} &= 100 \times 0.8 + 250 \times 0.8 + 200 \times 0.6 + 50 \\ &= 80 + 200 + 120 + 50 = 450 \text{ kW.}\end{aligned}$$

$$\begin{aligned}\text{Total KVAR} &= 100 \sin(\cos^{-1} 0.8) \\ &\quad - 250 \sin(\cos^{-1} 0.8) + 200 \sin(\cos^{-1} 0.6) + 0 \\ &= 100 \times 0.6 - 250 \times 0.6 + 200 \times 0.8 \\ &= 60 - 150 + 160 = 70.\end{aligned}$$

or Total KVAR is 70 (lagging)

$$\text{Total kVA} = \sqrt{(450)^2 + (70)^2} = 455.4.$$

$$\text{Overall p.f.} = \frac{\text{Total kW}}{\text{Total KVA}} = \frac{450}{455.4} = 0.988.$$

As KVAR is lagging, p.f. is also 0.988 (lagging).

5.12 COMPLEX NOTATION APPLIED TO AC CIRCUITS

For solving complicated ac circuit problems complex algebra is used. In this method a phasor is resolved into two components at right angles to each other. If a phasor V is resolved into two components V_x (horizontal component) and V_y (vertical component) [Fig. 5.37] then $V^2 = (V_x^2 + V_y^2)$ and (V) can be represented in cartesian form as, $V = V_x + j V_y = V(\cos \theta + j \sin \theta)$.

The symbol j is an operator indicating the anticlockwise rotation of the phasor by 90° . It is assigned by a value $\sqrt{-1}$.

In polar form, the phasor V is represented by

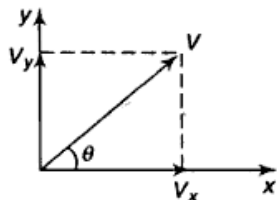


Fig. 5.37 Horizontal and vertical components of phasor V

$$V = V \angle \theta, \text{ where } V = \sqrt{V_x^2 + V_y^2} \text{ and } \theta = \tan^{-1} \frac{V_y}{V_x}.$$

Addition and Subtraction of Complex Quantities

Let us consider two phasors v_1 and v_2 which are represented in cartesian form as

$$v_1 = a_1 + j b_1 \text{ and } v_2 = a_2 + j b_2.$$

Then, $v_1 + v_2 = (a_1 + a_2) + j(b_1 + b_2)$

and $v_1 - v_2 = (a_1 - a_2) + j(b_1 - b_2).$

Multiplication and Division of Complex Quantities

$$\begin{aligned}v_1 v_2 &= (a_1 + j b_1)(a_2 + j b_2) \\ &= (a_1 a_2 - b_1 b_2) + j(b_1 a_2 + a_1 b_2).\end{aligned}$$

$$\begin{aligned}
 \text{Also, } \frac{v_1}{v_2} &= \frac{a_1 + jb_1}{a_2 + jb_2} = \frac{(a_1 + jb_1)(a_2 - jb_2)}{(a_2 + jb_2)(a_2 - jb_2)} \\
 &= \frac{(a_1 a_2 + b_1 b_2) + j(b_1 a_2 - a_1 b_2)}{a_2^2 + b_2^2} \\
 &= \frac{a_1 a_2 + b_1 b_2}{a_2^2 + b_2^2} + j \frac{b_1 a_2 - a_1 b_2}{a_2^2 + b_2^2}
 \end{aligned}$$

During calculations the horizontal and vertical components of phasors are summed up separately in cartesian form. This form is convenient for addition and subtraction while the polar form is convenient for multiplication and division.

$$\text{Let } v_1 = a_1 + jb_1 = |V_1| \angle \theta_1$$

$$\text{and } v_2 = a_2 + jb_2 = |V_2| \angle \theta_2$$

$$\text{where } |V_1| = \sqrt{a_1^2 + b_1^2} \text{ and } \theta_1 = \tan^{-1} \frac{b_1}{a_1}$$

$$\text{and } |V_2| = \sqrt{a_2^2 + b_2^2} \text{ and } \theta_2 = \tan^{-1} \frac{b_2}{a_2}$$

$$v_1 v_2 = |V_1| \angle \theta_1 \times |V_2| \angle \theta_2 = |V_1| |V_2| \angle (\theta_1 + \theta_2)$$

$$\text{and } \frac{v_1}{v_2} = \frac{|V_1| \angle \theta_1}{|V_2| \angle \theta_2} = \frac{|V_1|}{|V_2|} \angle (\theta_1 - \theta_2).$$

5.13 SERIES PARALLEL AC CIRCUITS

Consider a series parallel ac circuit as shown in Fig. 5.38.

First, the impedance of the parallel branches 1 and 2 are considered.

For branch 1:

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R_1 + jX_1}$$

$$\text{For branch 2: } Y_2 = \frac{1}{Z_2} = \frac{1}{R_2 - jX_2}$$

The admittance for parallel circuits 1 and 2 is obtained as

$$Y_{12} = Y_1 + Y_2 = \frac{1}{R_2 + jX_1} + \frac{1}{R_2 - jX_2}.$$

$$\text{and impedance } (Z_{12}) = \frac{1}{Y_{12}}.$$

Total impedance of series parallel ac circuit

$$Z = Z_{12} + Z_3 = Z_{12} + (R_3 + jX_3)$$

$$\text{Thus, current } I = \frac{E}{Z}.$$

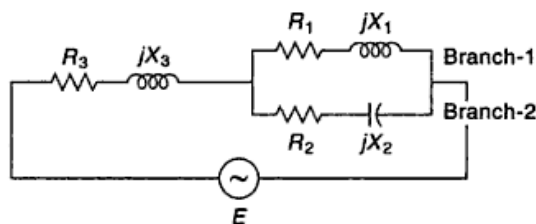


Fig. 5.38 Series parallel ac circuit

5.36 The voltage across a circuit is given by $(300 + j60)$ V and the current through it by $(10 - j5)$ A. Determine the (a) active power, (b) reactive power and (c) apparent power.

Solution

$$V = 300 + j60 = \sqrt{(300)^2 + (60)^2} \angle \tan^{-1} \frac{60}{300} \\ = 305.94 \angle 11.31^\circ \text{ V}$$

$$I = 10 - j5 = \sqrt{(10)^2 + (5)^2} \angle -\tan^{-1} \frac{5}{10} = 11.18 \angle -26.56^\circ \text{ A.}$$

Angle between voltage and current is $\theta = 11.31^\circ - (-26.56^\circ) = 37.87^\circ$, and current is lagging with respect to the voltage.

$$(a) \text{ Active power } (VI \cos \theta) = 305.94 \times 11.18 \cos 37.87^\circ \\ = 2700 \text{ W} = 2.7 \text{ kW.}$$

$$(b) \text{ Reactive power } (VI \sin \theta) = 305.94 \times 11.18 \sin 37.87^\circ \\ = 2099.68 \text{ VAR} \\ = 2.099 \text{ KVAR (lagging).}$$

$$(c) \text{ Apparent power } (VI) = 305.94 \times 11.18 = 3420.4 \text{ VA} = 3.42 \text{ kVA.}$$

5.37 Three impedances $(4 - j6) \Omega$, $(6 + j8) \Omega$ and $(5 - j3) \Omega$ are connected in parallel. Calculate the current in each branch when the total supply current is 20 A.

Solution

$$Z_1 = (4 - j6) \Omega; \quad y_1 = \frac{1}{Z_1} = \frac{1}{(4 - j6)} = \frac{(4 + j6)}{(4)^2 + (6)^2} = 0.077 + j0.115$$

$$Z_2 = (6 + j8) \Omega; \quad y_2 = \frac{1}{Z_2} = \frac{1}{6 + j8} = \frac{6 - j8}{(6)^2 + (8)^2} = 0.06 - j0.08$$

$$Z_3 = (5 - j3) \Omega; \quad y_3 = \frac{1}{Z_3} = \frac{1}{5 - j3} = \frac{5 + j3}{(5)^2 + (3)^2} = 0.147 + j0.088$$

$$\text{Total admittance } y = y_1 + y_2 + y_3 = (0.077 + 0.06 + 0.147) + j(0.115 - 0.08 + 0.088) \\ = 0.284 + j0.123 = 0.31 \angle 23.4^\circ.$$

$$\text{Supply voltage } V = \frac{I}{y} = \frac{20}{0.31 \angle 23.4^\circ} = 64.5 \angle -23.4^\circ \text{ V.}$$

$$I_1 = Vy_1 = 64.5 \angle -23.4^\circ (0.077 + j0.115) \\ = 64.5 \angle -23.4^\circ \times 0.138 \angle 56.19^\circ$$

$$I_2 = Vy_2 = 64.5 \angle -23.4^\circ (0.06 - j0.08) \\ = 64.5 \angle -23.4^\circ \times 0.1 \angle -53.13^\circ$$

$$I_3 = Vy_3 = 64.5 \angle -23.4^\circ (0.147 + j0.088) \\ = 64.5 \angle -23.4^\circ \times 0.171 \angle 30.9^\circ$$

$$\text{i.e.,} \quad I_1 = 8.9 \angle 32.79^\circ \text{ A} \\ I_2 = 6.45 \angle -76.5^\circ \text{ A} \\ I_3 = 11.03 \angle 7.5^\circ \text{ A.}$$

5.38 Find the value of unknown reactance 'X' so that p.f. of the circuit will be unity in Fig. 5.39. Also calculate the current drawn from the supply.

Solution

The combined impedance of the two parallel branches

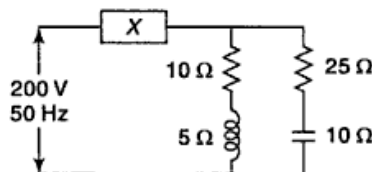


Fig. 5.39 Circuit diagram for Ex. 5.38

$$Z = \frac{(10 + j5)(25 - j10)}{(10 + j5) + (25 - j10)} = \frac{(250 + 50) + j(125 - 100)}{35 - j5}$$

$$= \frac{300 + j25}{35 - j5} = \frac{(300 + j25)(35 + j5)}{(35)^2 + (5)^2} = \frac{10375 + j2375}{1250}$$

$$= (8.3 + j 1.9) \Omega$$

If the p.f. becomes unity then the net reactance of the circuit should be zero i.e., $X = -j1.9$ or $X = 1.9 \Omega$ (capacitive).

So, total impedance is 8.3Ω . Therefore current is $200/8.3 = 24.1 \text{ A}$ at u.p.f.

5.39 Determine the current drawn by the series parallel circuit shown in Fig. 5.40 and find the overall p.f.

Solution

The equivalent impedance of the two parallel branches is

$$\frac{(10 - j40)(14 + j18)}{(10 - j40) + (14 + j18)} = \frac{860 - j380}{24 - j22}$$

$$= 27.358 + j9.24 \Omega.$$

$$\therefore \text{The impedance of the whole circuit} = 8 + j6 + 27.358 + j9.24$$

$$= 35.358 + j15.24$$

$$= 38.5 \angle 23.32^\circ.$$

$$\text{Hence the current drawn by the circuit} = \frac{440}{38.5 \angle 23.3^\circ} = 11.43 \angle -23.3^\circ.$$

Overall power factor ($= \cos 23.3^\circ \text{ lag}$) = 0.918 lag.

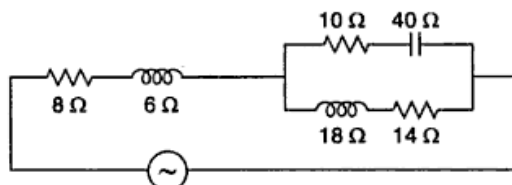


Fig. 5.40 Circuit diagram for Ex. 5.39

5.40 In the circuit shown in Fig. 5.41 determine what voltage of 50 Hz frequency is to be applied across AB that will cause a current of 10 A to flow in the capacitor?

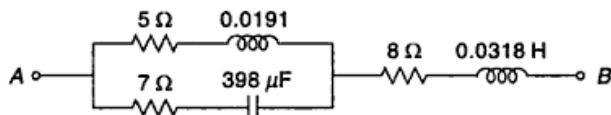


Fig. 5.41 Circuit diagram for Ex. 5.40

Solution

The combined impedance of the two parallel branches is

$$\frac{(5 + j2\pi \times 50 \times 0.0191) \times \left(7 + \frac{10^6}{j2\pi \times 50 \times 398}\right)}{(5 + j2\pi \times 50 \times 0.0191) + \left(7 + \frac{10^6}{j2\pi \times 50 \times 398}\right)}$$

$$= \frac{(5 + j6)(7 - j8)}{5 + j6 + 7 - j8} = \frac{35 + 48 + j42 - j40}{12 - j2} = \frac{83 + j2}{12 - j2}$$

$$= \frac{83.024 \angle 1.38^\circ}{12.16 \angle -9.46^\circ} = 6.83 \angle 10.84^\circ = 6.7 + j1.28 \Omega.$$

The impedance of the whole circuit

$$\begin{aligned}(Z) &= 6.7 + j 1.28 + 8 + j 2\pi \times 50 \times 0.0318 \\ &= 14.7 + j(1.28 + 10) \\ &= 14.7 + j11.28 \\ &= 102.34 \angle 81.74^\circ.\end{aligned}$$

The impedance of the capacitor branch = $7 - j8 \Omega$

The voltage across this branch = $10 \times (7 - j8) = (70 - j80) \text{ V}$.

\therefore the current in the other parallel branch

$$= \frac{70 - j80}{5 + j6} = \frac{106.3 \angle -48.8^\circ}{7.81 \angle 50.19^\circ} = 13.61 \angle -99^\circ = -2.129 - j13.44.$$

Thus total current = $10 - 2.129 - j13.44$

$$= 7.87 - j13.44 = 15.57 \angle -59.65^\circ$$

The voltage across the third branch is = $15.57 \angle -59.65^\circ \times (8 + j10)$

$$= 15.57 \angle -59.65^\circ \times 12.8 \angle 51.34^\circ$$

$$= 200 \angle -8.31^\circ = (198 - j28) \text{ V}.$$

Hence the supply voltage is $[(70 - j80) + (198 - j28)] \text{ V}$,

i.e., $(268 - j108) \text{ V}$ or, $288.9 \angle -21.95^\circ \text{ V}$.

[Note that in this problem we have assumed 10 A current to be the reference phasor having angle $10 \angle 0^\circ$. Other currents and voltages are expressed accordingly.]

5.41. Two circuits having the same numerical value of impedance are connected in parallel. The p.f. of one circuit is 0.8 (lead) and the other is 0.6 (lead). What is the p.f. of the combination?

Solution

Let the numerical value of impedance be Z . So Impedance of one circuit is $Z_1 = Z(\cos \theta_1 + j \sin \theta_1)$ and that of the second circuit is $Z_2 = Z(\cos \theta_2 + j \sin \theta_2)$.

However, $\cos \theta_1 = 0.8$ and $\cos \theta_2 = 0.6$

$\therefore \sin \theta_1 = 0.6$ and $\sin \theta_2 = 0.8$.

Hence, $Z_1 = Z(0.8 + j 0.6)$ and $Z_2 = Z(0.6 + j 0.8)$.

$$\begin{aligned}\text{Now net impedance} &= \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(0.8 + j0.6)(0.6 + j0.8)}{0.8 + j0.6 + 0.6 + j0.8} \\ &= \frac{1 \angle 36.86^\circ \times 1 \angle 53.13^\circ}{1.4 + j1.4} = \frac{1 \angle 90^\circ}{2.56 \angle 45^\circ} = 0.31 \angle 45^\circ\end{aligned}$$

So the p.f. of the circuit is $\cos 45^\circ = 0.707$ (lead).

5.42. A circuit with two branches having admittances $y_1 = 0.16 + j0.12$ and $y_2 = -j0.15$ are in parallel and connected to a 100 V supply. Find the total loss and phase relationship between the branch currents and the supply current.

Solution

$$y_1 = (0.16 + j 0.12) \text{ S}$$

$$y_2 = (-j 0.15) \text{ S}$$

$$I_1 = Vy_1 = 16 + j12 = 20 \angle 36.87^\circ \text{ A}$$

and $I_2 = Vy_2 = -j15 = 15 \angle -90^\circ \text{ A}$.

$$\begin{aligned}\text{Total current } I &= I_1 + I_2 = 16 + j12 - j15 = 16 - j3 \\ &= 16.28 \angle -10.62^\circ \text{ A}.\end{aligned}$$

$$\begin{aligned}\therefore \text{total loss} &= VI \cos \theta \\ &= 100 \times 16.28 \cos 10.62^\circ \\ &= 1600 \text{ W}.\end{aligned}$$

I_1 leads I by $(36.87^\circ + 10.62^\circ) = 47.5^\circ$
 and I_2 lags I by $(90^\circ - 10.62^\circ) = 79.38^\circ$.

5.43 A small single phase 240 V induction motor is tested in parallel with a 160 Ω resistor, the motor takes 2 A and the total current is 3 A. Find the power and p.f. of (a) the whole circuit and (b) the motor.

Solution

(a) The current in the resistor is $(I_1) = \frac{240}{160} = 1.5$ A.

The impedance of the motor is $\frac{240}{2} = 120 \Omega$.

Let the motor current is $(a + jb)$ A.

$$\therefore a^2 + b^2 = 2^2 = 4.$$

The total current is $(a + jb + 1.5)$

$$\text{or } (a + 1.5)^2 + b^2 = 3^2 = 9$$

$$\text{or } 4 + 2.25 + 3a = 9 \quad [\therefore a^2 + b^2 = 4]$$

$$\text{or } 3a = 2.75 \text{ or, } a = 0.917$$

$$\text{and } b = \pm \sqrt{4 - (0.917)^2} = 1.78.$$

In induction motor current is lagging. So $b = -1.78$.

The motor current is thus $(0.917 - j1.78)$ A.

The total current = $1.5 + 0.917 - j1.78$

$$= 2.417 - j1.78$$

$$= 3 \angle -36.37^\circ \text{ A.}$$

p.f. of the whole circuit is $\cos 36.37^\circ = 0.8$ lagging.

Power of the whole circuit is $VI \cos \theta = 240 \times 3 \times 0.8 = 576$ W.

(b) p.f. of the motor is $\cos \left(\tan^{-1} \frac{1.78}{0.917} \right)$ lagging = 0.458 lagging.

Power of the motor is $240 \times 2 \times 0.458 = 220$ W.

5.44 Find the phase angle of the input impedance of a series circuit consisting of a 500 Ω resistor, a 60 mH inductor and a 0.053 μF capacitor at frequencies of (a) 2000 Hz. and (b) 4000 Hz.

Solution

(a) Phase angle of impedance $\theta = \tan^{-1} \frac{\text{Reactance}}{\text{Resistance}} = \tan^{-1} \frac{X_L - X_C}{R}$

When $f = 2000$ Hz,

$$(X_L - X_C) = 2\pi \times 2000 \times 60 \times 10^{-3} - \frac{10^6}{2\pi \times 2000 \times 0.053}$$

$$= 753.6 - 1502 = -748.6$$

$$\text{so } \theta = \tan^{-1} \frac{-748.6}{500} = -56.26^\circ.$$

(b) When $f = 4000$ Hz

$$X_L - X_C = 2\pi \times 4000 \times 60 \times 10^{-3} - \frac{10^6}{2\pi \times 4000 \times 0.053}$$

$$= 1507.2 - 751$$

$$= 756.$$

Therefore phase angle $\theta = \tan^{-1} \frac{756}{500} = 56.52^\circ$.

5.45 A resistor R in series with a capacitor C is connected to a 50 Hz, 240 V supply. Find the value of C so that R absorbs 300 W at 100 V. Find also the maximum charge and the maximum stored energy in C .

Solution

Supply voltage = 240 V

Voltage across R is 100 V.

Power across R is 300 W

$$\therefore \text{Current through } (R) \text{ is } \frac{300}{100} = 3 \text{ A}$$

$$\text{Voltage across capacitor} = \sqrt{(240)^2 - (100)^2} = 218.17 \text{ V.}$$

$$\text{Hence, maximum voltage } (V_m) = \sqrt{2} \times 218.17 = 308.54 \text{ V.}$$

Thus maximum charge is $(C V_m)$

$$\text{Now, capacitive reactance } X_C = \frac{218.17}{3} = 72.72 \Omega.$$

$$\text{Hence, } C = \frac{1}{72.72 \times 2\pi \times 50} \text{ F} = 43.79 \mu\text{F}$$

$$\text{Maximum charge } (= C V_m) = 43.79 \times 10^{-6} \times 308.54 = 0.0135 \text{ C.}$$

$$\text{Maximum energy stored} = \frac{1}{2} C V_m^2 = \frac{1}{2} \times 43.79 \times 10^{-6} \times (308.54)^2 = 2.08 \text{ J.}$$

.....

5.14 SERIES RESONANCE

An ac circuit is said to be in resonance when the circuit current is in phase with the applied voltage. So the power factor of the circuit becomes unity at resonance and the impedance of the circuit consists of only resistance.

In the series RLC circuit in Fig. 5.42 the impedance is given by

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

The current in the circuit is

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

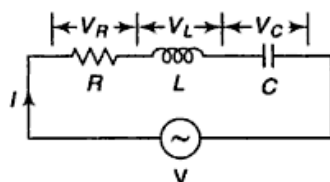


Fig. 5.42 RLC series circuit

$$\text{The power factor is: } \cos \theta = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

At resonance $Z = R$

$$\therefore \omega L - \frac{1}{\omega C} = 0$$

$$\text{or } \omega = \frac{1}{\sqrt{LC}}$$

If f_o be the resonant frequency then

$$2\pi f_o = \frac{1}{\sqrt{LC}}$$

or
$$f_o = \frac{1}{2\pi\sqrt{LC}}.$$

The p.f. at resonance: $\cos \theta = \frac{R}{Z} = \frac{R}{R} = 1$ [\because at resonance, $Z = R$]

and the current $I = \frac{V}{Z} = \frac{V}{R}.$

Properties of Series Resonant Circuits

(a) The circuit impedance Z is minimum and equal to the circuit resistance R .

(b) The power factor is unity.

(c) The circuit current $I = \frac{V}{R}$, and the current is maximum.

(d) The power dissipated is maximum, i.e. $P_o = \frac{V^2}{R},$

(e) The resonant frequency is $f_o = \frac{1}{2\pi\sqrt{LC}},$

(f) The voltage across inductor is equal and opposite to the voltage across capacitor.

Since the circuit current is maximum at resonance it produces large voltage drops across L and C . But as these voltages are equal and opposite to each other so the net voltage across L and C is zero however large the current is flowing. If R is not present then the circuit would act like a short circuit at resonant frequency. Hence a series circuit is sometimes called an *acceptor circuit* and the series resonance is often referred to as the *voltage resonance*. Figure 5.43 represents variation of R, X_L, X_C, Z and I with frequency. As R is the independent of frequency so it is a straight line. Inductive reactance X_L is directly proportional to the frequency so it is a straight line passing through origin. Capacitive reactance X_C is inversely proportional to frequency and its characteristic is a rectangular hyperbola. At resonant frequency Z is minimum and I is maximum.

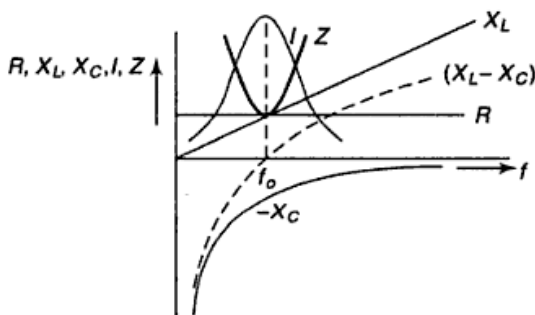


Fig. 5.43 Variation of R, X_L, X_C, Z, I with frequency

5.15 Q FACTOR IN SERIES RESONANCE

Q factor of a series RLC circuit is defined as the voltage magnification produced in the circuit at resonance.

Voltage magnification is the ratio of voltage drop across the inductor or capacitor to the voltage drop across the resistor.

$$\text{Hence, } Q \text{ factor} = \frac{IX_L}{IR} = \frac{\omega_o L}{R} = \frac{2\pi f_o L}{R} = \frac{2\pi \frac{1}{\sqrt{LC}} L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}.$$

Q factor is also referred as the *magnification factor* of the circuit.

5.16 DIFFERENT ASPECTS OF RESONANCE

5.16.1 Variation of Current and Voltage Across L and C with Frequency

The voltage across the capacitor is $V_C = I \cdot \frac{1}{\omega C}$

$$\text{In an } RLC \text{ series circuit } I = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\therefore V_C = \frac{V}{\omega C \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\begin{aligned} \text{or } V_C^2 &= \frac{V^2}{\omega^2 C^2 \left\{ R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 \right\}} \\ &= \frac{V^2}{\omega^2 C^2 \left\{ R^2 + \frac{(\omega^2 LC - 1)^2}{\omega^2 C^2} \right\}} = \frac{V^2}{R^2 \omega^2 C^2 + (\omega^2 LC - 1)^2}. \end{aligned}$$

To find the frequency at which V_C is maximum $\left(\frac{dV_C}{d\omega}\right)$ should be zero i.e., $\left(\frac{dV_C^2}{d\omega}\right)$ should be zero.

As $\frac{dV_C^2}{d\omega} = 0$, we have

$$\frac{dV_C^2}{d\omega} = V^2 \left[\frac{-\{2\omega C^2 R^2 + 2(\omega^2 LC - 1) 2\omega LC\}}{\{R^2 \omega^2 C^2 + (\omega^2 LC - 1)^2\}^2} \right] = 0$$

$$\text{or } 2\omega C^2 R^2 + (2\omega^2 LC - 2) 2\omega LC = 0$$

$$\text{or } \omega^2 = \frac{1}{2L^2 C} (2L - CR^2) = \frac{1}{LC} - \frac{R^2}{2L^2}.$$

$$\text{Hence the frequency at which } V_C \text{ is maximum is } f_C = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}.$$

To find the frequency at which voltage across L is maximum, we have

$$\frac{dV_L}{d\omega} = 0 \quad \text{or,} \quad \frac{dV_L^2}{d\omega} = 0.$$

$$\text{Now,} \quad V_L = IX_L = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \omega L$$

$$V_L^2 = \frac{V^2 \omega^2 L^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \frac{V^2 \omega^4 L^2 C^2}{\omega^2 C^2 R^2 + (\omega^2 LC - 1)^2}$$

By differentiating (V_L^2) with respect to ω and setting $\frac{dV_L^2}{d\omega} = 0$, we have on simplification,

$$2\omega^2 LC - \omega^2 C^2 R^2 - 2 = 0$$

$$\text{or} \quad \omega^2 [2LC - C^2 R^2] = 2$$

$$\text{or} \quad \omega^2 = \frac{2}{2LC - R^2 C^2} = \frac{1}{LC - \frac{R^2 C^2}{2}}$$

$$\text{or} \quad \omega = \frac{1}{\sqrt{LC - \frac{R^2 C^2}{2}}}$$

The variation of voltages across the capacitor and the inductor with frequency are shown in Fig. 5.44. It is seen that maximum value of V_C occurs at f_C below f_o (resonant frequency) and maximum value of V_L occurs at f_L which is above f_o .

If R is very small then f_L , f_C and f_o correspond to a single value of frequency

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

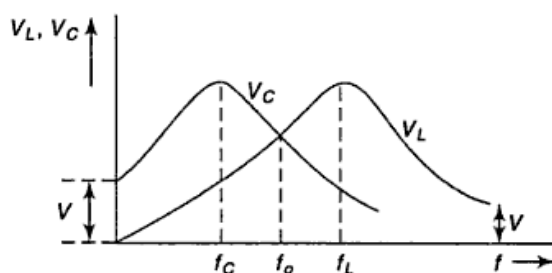


Fig. 5.44 Variation of voltage across L and C with frequency

5.16.2 Effect of Resistance on the Frequency Response Curve

Figure 5.45 shows the nature of resonance curve for different values of R .

As seen from the Fig. 5.45 that when the resistance is small the curve rises steeply while with large resistance value the curve has a low peak.

A circuit with a flat frequency response curve will be more responsive

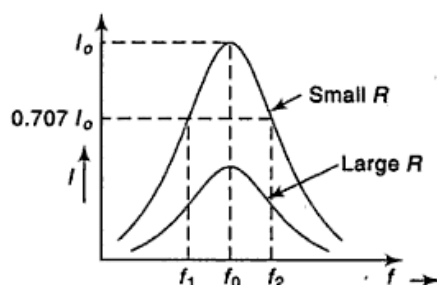


Fig. 5.45 Effect of resistance on frequency response curve

and so less selective at frequencies in the neighbourhood of the resonant frequency. On the other hand, a circuit for which the curve has a tall narrow peak will be less responsive and so more selective at frequencies in the neighbourhood of resonant frequency.

5.16.3 Bandwidth and Selectivity in Series Resonance Circuit

The bandwidth of a given circuit is given by the band of frequencies which lies between two points on either side of resonant frequency where the current is $1/\sqrt{2}$ times of the current at resonance and hence the power is half of the power at resonance.

Figure 5.46 shows the variation of circuit current with frequency and this curve is known as the resonance curve. f_1 and f_2 are known as half power frequency where current is $I_o/\sqrt{2}$ (I_o is the current at resonance). f_1 and f_2 are also called *corner* or *edge frequencies*. The power at the two points of frequencies f_1 and f_2 is

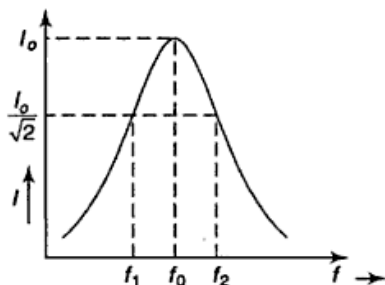


Fig. 5.46 Variation of current with frequency

$$P_1 = P_2 = I^2 R = \left(\frac{I_o}{\sqrt{2}} \right)^2 R = \frac{I_o^2 R}{2} = \frac{1}{2} \times (\text{power at resonance})$$

Now
$$I = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}} \text{ at any frequency } (\omega)$$

At half power frequencies
$$I = \frac{I_o}{\sqrt{2}} = \frac{V}{R\sqrt{2}} \quad \left(\text{As } I_o = \frac{V}{R} \right)$$

Squaring both sides and comparing above expressions we have

$$I^2 = \frac{V^2}{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} = \frac{V^2}{2R^2}$$

or
$$\frac{V^2}{2R^2} = \frac{V^2}{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} \text{ or, } \left(\omega L - \frac{1}{\omega C} \right)^2 = R^2.$$

or
$$\omega L - \frac{1}{\omega C} = \pm R \text{ or } \omega = \pm \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}.$$

As $\left(\frac{R^2}{4L^2} \right)$ is much less than $\left(\frac{1}{LC} \right)$ so,

$$(\omega) = \pm \frac{R}{2L} \pm \frac{1}{\sqrt{LC}} = \pm \frac{R}{2L} \pm \omega_o.$$

Since only positive values of ω_o is considered so

$$\omega = \pm \frac{R}{2L} + \omega_o$$

or $\omega_1 = \omega_o - \frac{R}{2L}$ and $\omega_2 = \omega_o + \frac{R}{2L}$

or $f_1 = f_o - \frac{R}{4\pi L}$ and $f_2 = f_o + \frac{R}{4\pi L}$.

Bandwidth $(\Delta\omega) = \omega_2 - \omega_1 = \frac{R}{L}$ rad/s,

and $(\Delta f) = f_2 - f_1 = \frac{R}{2\pi L}$ Hz.

The ratio of the bandwidth to the resonant frequency is defined as the *selectivity* of the circuit. Thus selectivity = $\frac{(f_2 - f_1)}{f_o}$.

Thus, *narrower the bandwidth higher is the selectivity property of the circuit.*

5.46 A circuit consists of a coil of resistance 100Ω and inductance 1 H in series with a capacitor of capacitance $1 \mu\text{F}$. Calculate (a) the resonant frequency, (b) current at resonant frequency and (c) voltage across each element when the supply voltage is 50 V .

Solution

Resistance $R = 100 \Omega$

Inductance $L = 1 \text{ H}$

Capacitance $C = 1 \times 10^{-6} \text{ F}$.

$$\begin{aligned} \text{(a) Resonant frequency } f_o &= \frac{1}{2\pi\sqrt{LC}} \\ &= \frac{1}{2\pi\sqrt{1 \times 1 \times 10^{-6}}} \text{ Hz} \\ &= 159 \text{ Hz.} \end{aligned}$$

$$\text{(b) Current at resonant frequency } I_o = \frac{V}{R} = \frac{50}{100} = 0.5 \text{ A.}$$

$$\text{(c) Voltage across resistance } V_R = I_o \times R = 0.5 \times 100 = 50 \text{ V.}$$

$$\begin{aligned} \therefore \text{Voltage across inductance } V_L &= I_o X_L = 0.5 \times 2\pi f_o L \\ &= 0.5 \times 2\pi \times 159 \times 1 \\ &= 500 \text{ V} \end{aligned}$$

$$\text{and voltage across capacitance } V_C = I_o X_C = 0.5 \times \frac{10^6}{2\pi \times 159 \times 1} = 500 \text{ V.}$$

5.47 An inductive coil is connected in series with a $8 \mu\text{F}$ capacitor. With a constant supply voltage of 400 V the circuit takes minimum current of 80 A when the supply frequency is 50 Hz . Calculate the (a) resistance and inductance of the coil and (b) voltage across the capacitor.

Solution

Supply voltage $V = 400 \text{ V}$

The current is minimum at 50 Hz , so the resonant frequency is 50 Hz and the current at resonant frequency $(I_o) = 80 \text{ A}$.

Capacitance

$$C = 8 \times 10^{-6} \text{ F.}$$

Hence, resistance

$$R = \frac{V}{I_o} = \frac{400}{80} = 5 \Omega.$$

At resonance,

$$X_L = X_C$$

or

$$\omega L = \frac{1}{\omega C}$$

or

$$\omega = \frac{1}{\sqrt{LC}}$$

or

$$2\pi f = \frac{1}{\sqrt{L \times 8 \times 10^{-6}}}$$

or

$$2\pi \times 50 = \frac{10^3}{\sqrt{8L}}$$

or

$$L = \left(\frac{10^3}{2\pi \times 50} \right)^2 \times \frac{1}{8} = \left(\frac{10}{\pi} \right)^2 \times \frac{1}{8} = 1.266 \text{ H}$$

.....

5.48. The resistor and a capacitor are connected in series with a variable inductor. When a circuit is connected to a 240 V, 50 Hz supply, the maximum current by varying the inductance is 0.5 A. At this current the voltage across the capacitor is 250 V. Calculate R , C and L .

SolutionSupply voltage $V = 240 \text{ V}$.Resonant frequency (f_o) = 50 Hz.Current at resonant frequency $I_o = 0.5 \text{ A}$.Voltage across capacitor $V_C = 250 \text{ V}$ Now if X_C and X_L be the capacitive and inductive reactance then

$$I_o X_C = 250$$

and

$$I_o X_L = 250.$$

At resonance,

$$X_C = X_L = \frac{250}{0.5} = 500 \Omega$$

Therefore,

$$\frac{1}{2\pi f_o C} = 2\pi f_o L = 500$$

or

$$C = \frac{1}{2\pi \times 50 \times 500} \text{ F} = 6.37 \mu\text{F},$$

and

$$L = \frac{500}{2\pi \times 50} \text{ H} = 1.59 \text{ H}.$$

Resistance

$$R = \frac{V}{I_o} = \frac{240}{0.5} = 480 \Omega.$$

.....

5.49. A constant voltage at a frequency of 1 MHz is applied to an inductor in series with a variable capacitor. When the capacitor is set at 500 pF, the current has its maximum value, and it is reduced to half of its maximum value when the capacitance is 600 pF. Find (a) the resistance, (b) the inductance and (c) Q factor of the inductor.

Solution

The current is maximum at resonant frequency.

$$\therefore f_o = 10^6 \text{ Hz.}$$

It is given that is $C = 500 \times 10^{-12} \text{ F}$.

$$\text{Now, } f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{500 \times 10^{-12} L}} = 10^6$$

$$\text{or } \frac{10^6}{2\pi\sqrt{500L}} = 10^6$$

$$\text{or } 2\pi\sqrt{500L} = 1$$

$$\text{or } L = \left(\frac{1}{2\pi}\right)^2 \times \frac{1}{500} \text{ H} = 0.05 \text{ mH}$$

$$\text{when } C = 600 \times 10^{-12} \text{ F.}$$

$$\therefore \text{Capacitive reactance } X_C = \frac{1}{2 \times 10^6 \times 600 \times 10^{-12}} = \frac{10^6}{2\pi \times 600} = 265 \Omega.$$

$$\text{Inductive reactance } X_L = 2\pi f_o L = 2\pi \times 10^6 \times 0.05 \times 10^{-3} = 314 \Omega.$$

$$\therefore \text{Net reactance is } (X_L - X_C) = 314 - 265 = 49 \Omega.$$

Current $I = \frac{I_o}{2} \left(\frac{V}{2R} \right)$, where R is the resistance of the circuit and I_o is the current at resonance.

$$\text{So, } I = \frac{V}{2R} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\text{or } 2R = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{or } 4R^2 = R^2 + (49)^2$$

$$\text{or } 3R^2 = (49)^2$$

$$\text{or } R = 28.29 \Omega$$

$$\therefore Q \text{ factor of the inductor is } \frac{\omega_o L}{R} = \frac{2\pi \times 10^6 \times 0.05 \times 10^{-3}}{28.29} = 11.1. \quad \dots\dots\dots$$

5.50. A series resonant circuit has an impedance of 500Ω at resonant frequency and cut off frequencies are 10 kHz and 100 kHz . Determine (a) the resonant frequency, (b) value of R , L and C , (c) quality factor at resonant frequency and (d) p.f. of the circuit at resonant frequency.

Solution

At resonance

Impedance = Resistance or $Z_o = R = 500 \Omega$.

$$f_1 = 10 \times 10^3 \text{ Hz} \text{ \& } f_2 = 100 \times 10^3 \text{ Hz.}$$

$$(f_2 - f_1) = 90 \times 10^3 = \frac{R}{2\pi L} = \frac{500}{2\pi L}$$

$$\text{Now } L = \frac{500}{2\pi \times 90 \times 10^3} = 0.88 \text{ mH}$$

$$\text{Again, } f_1 = f_o - \frac{R}{4\pi L}$$

$$\therefore \text{Resonant frequency } f_o = f_1 + \frac{R}{4\pi L} = 10 \times 10^3 + \frac{500}{4\pi \times 0.88 \times 10^{-3}} = 55 \text{ kHz.}$$

$$\text{As } f_o = \frac{1}{2\pi\sqrt{LC}},$$

$$\text{so } C = \left(\frac{1}{2\pi \times 55 \times 10^3} \right)^2 \times \frac{1}{0.88 \times 10^{-3}} = 0.095 \times 10^{-7} \text{ F}$$

$$Q \text{ factor} = \frac{2\pi f_o L}{R} = \frac{2\pi \times 55 \times 10^3 \times 0.88 \times 10^{-3}}{500} = 0.61$$

and the p.f. of the circuit at resonant frequency is 1.

5.51. A series RLC circuit has $R = 10 \Omega$, $L = 0.1 \text{ H}$ and $C = 8 \mu\text{F}$. Determine (a) the resonant frequency (b) Q factor of the circuit at resonance (c) half power frequencies.

Solution

$$(a) \text{ Resonant frequency } f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 8 \times 10^{-6}}} = 178 \text{ Hz.}$$

$$(b) Q_{\text{factor}} = \frac{2\pi f_o L}{R} = \frac{2\pi \times 178 \times 0.1}{10} = 11.18.$$

$$(c) \text{ Lower half power frequency } (f_1) = f_o - \frac{R}{4\pi L} \\ = 178 - \frac{10}{4\pi \times 0.1} = 178 - 7.96 = 170 \text{ Hz.}$$

$$\text{Upper half power frequency } (f_2) = 178 + 7.96 = 186 \text{ Hz.}$$

5.52. Calculate the half power frequencies of a series resonant circuit when the resonant frequency is $150 \times 10^3 \text{ Hz}$ and the bandwidth is 75 kHz .

Solution

$$\text{Resonant frequency } f_o = 150 \times 10^3 \text{ Hz.}$$

$$\text{Bandwidth } (\Delta f) = \frac{R}{2\pi L} = 75 \times 10^3.$$

$$\text{Lower half power frequency } \left(f_o - \frac{R}{4\pi L} \right) = \left(150 - \frac{75}{2} \right) 10^3 = 112.5 \text{ kHz.}$$

$$\text{Upper half power frequency } \left(f_o + \frac{R}{4\pi L} \right) = \left(150 + \frac{75}{2} \right) 10^3 \text{ Hz.} = 187.5 \text{ kHz.}$$

5.53. A $25 \mu\text{F}$ condenser is connected in series with a coil having an inductance of 5 mH . Determine the frequency of resonance, resistance of the coil if a 25V source operating at resonance frequency causes a circuit current of 4 mA . Determine the Q factor of the coil.

Solution

$$C = 25 \times 10^{-6} \text{ F} \quad L = 5 \times 10^{-3} \text{ H}$$

$$I_o = 4 \times 10^{-3} \text{ A} \quad V = 25 \text{ V.}$$

$$\begin{aligned}\text{Frequency of resonance } (f_o) &= \frac{1}{2\pi\sqrt{LC}} \\ &= \frac{1}{2\pi\sqrt{5 \times 10^{-3} \times 25 \times 10^{-6}}} \\ &= 450 \text{ Hz.}\end{aligned}$$

$$\therefore \text{Resistance of the circuit} = \frac{V}{I_o} = \frac{25}{4 \times 10^{-3}} = 6250 \, \Omega$$

$$\text{and } Q_{\text{factor}} = \frac{2\pi f_o L}{R} = \frac{2\pi \times 450 \times 5 \times 10^{-3}}{6250} = 2.26 \times 10^{-3}.$$

.....

5.17 RESONANCE IN PARALLEL CIRCUIT

Let us consider a circuit where a capacitance C is connected in parallel with an inductive coil of resistance R and inductive reactance X_L as shown in Fig. 5.47.

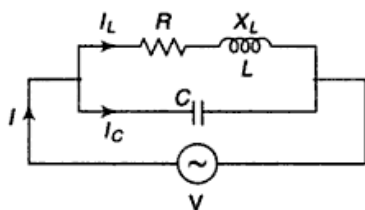


Fig. 5.47 AC parallel circuit

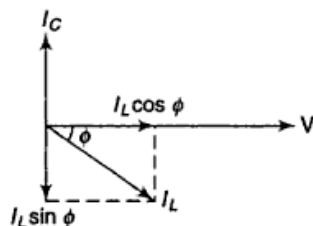


Fig. 5.48 Branch currents of Fig. 5.47

If I_L be the current through the coil, I_C be the current through the capacitor and the total current is I , then the vector diagram is shown in Fig. 5.48.

From Fig. 5.48 it is clear that under resonance as the p.f. is unity the reactive component of the total current is zero. The reactive component of the current $(I_C - I_L \sin \phi) = 0$, where ϕ is the power factor angle of the coil. Therefore

$$I_C = I_L \sin \phi$$

$$\text{or } \frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L}$$

where Z_L is the impedance of the coil and $[Z_L = \sqrt{R^2 + X_L^2}]$

$$\text{or } X_C X_L = Z_L^2$$

$$\text{or } \frac{\omega L}{\omega C} = Z_L^2 = R^2 + \omega^2 L^2$$

$$\text{or } \omega^2 L^2 = \frac{L}{C} - R^2$$

$$\text{or at resonance } \omega_o = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\text{and resonant frequency } f_o = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

If resistance is neglected then

$$\omega_o = \frac{1}{\sqrt{LC}}$$

and

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

Thus if resistance is neglected the resonant frequency of the parallel circuit is equal to that of series circuit. Also at resonance the net susceptance is zero.

$$\text{Net susceptance} = \left(\omega C - \frac{1}{\omega L} \right) = 0$$

$$\therefore \omega_o = \frac{1}{\sqrt{LC}}$$

As the net reactive component of the current is zero at resonance so the supply current I is equal to the active component of the current.

$$\text{So } I = I_L \cos \phi = \frac{V}{Z_L} \frac{R}{Z_L} = \frac{VR}{Z_L^2} = \frac{VR}{L/C} \quad (\because Z_L^2 = X_C \cdot X_L = L/C)$$

from previous equation

$$\text{or } I = \frac{V}{L/CR}$$

Thus at resonance the net impedance is given by L/CR and is known as the *dynamic impedance* of the parallel circuit at resonance. This impedance is resistive only.

The current is minimum at resonance as its reactive part is zero and thus, (L/CR) represent the maximum impedance of the circuit. It is called a *rejector circuit*.

5.18 PROPERTIES OF PARALLEL RESONANT CIRCUITS

- (a) At resonance the net reactive component of the line current is zero and the circuit current is equal to the active component of the total current, i.e.

$$I = I_L \cos \phi.$$

- (b) The line current is minimum at resonance or $I = \frac{V}{L/CR}$.

- (c) The power factor is unity at resonance.

- (d) Net susceptance is zero at resonance i.e. $\left(\omega C - \frac{1}{\omega L} \right) = 0$.

- (e) The resonant frequency is $f_o = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$.

Since the current at resonance is minimum hence such a circuit is sometimes known as *rejector circuit* because it rejects (or takes minimum current) at resonant frequency. This resonance is often referred to as current resonance because the current, circulating between the two branches, is many times greater than the line current taken from the supply.

Figure 5.49 represents the variation of R , B_L (inductive susceptance), B_C (capacitive susceptance) Z and I with frequency. As R is independent of frequency so it is a straight line. The capacitive susceptance ($B_C = \omega C$) is a straight line passing through the origin and the characteristic of inductive susceptance ($B = -\frac{1}{\omega L}$) is a rectangular hyperbola. At resonance I is minimum and so Z is maximum.

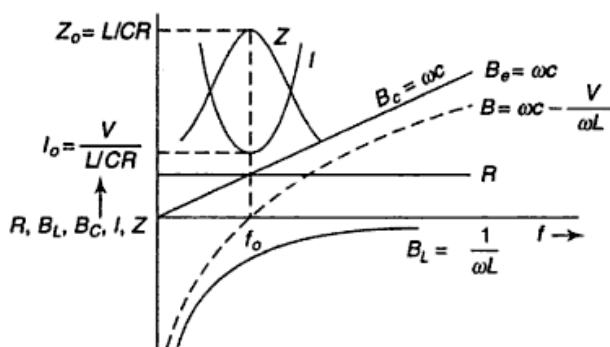


Fig. 5.49 Variation of R , B_L , B_C , Z , I with frequency

5.19 Q FACTOR IN PARALLEL CIRCUIT

It is defined as the ratio of the current, circulating between the two branches of the parallel circuit to the line current.

$$\therefore Q_{\text{factor}} = \frac{\frac{V}{XC}}{I_o} = \frac{I_C}{I_o} = \frac{V\omega C}{I_o}$$

$$I_o = \frac{V}{L/CR}$$

Therefore $Q_{\text{factor}} = \frac{\omega CL}{CR} = \frac{\omega L}{R}$

Now Q_{factor} at resonance is $\left(\frac{\omega_o L}{R}\right) = \frac{1}{\sqrt{LC}} \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$

In a series circuit Q_{factor} gives the voltage magnification while in a parallel circuit it gives the current magnification.

5.20 PARALLEL RESONANCE IN RLC CIRCUIT

In the circuit of Fig. 5.50 the resonance occurs when the net susceptance is zero.

$$\text{Admittance } y = G + jB = \frac{1}{R} + j\omega C - j\frac{1}{\omega L}$$

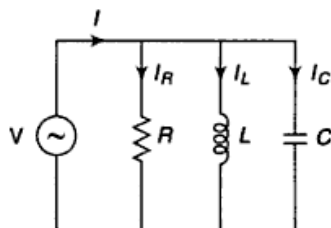


Fig. 5.50 RLC parallel circuit

At resonance net susceptance $\left(\omega C - \frac{1}{\omega L}\right) = 0$

$$\therefore \omega_o = \frac{1}{\sqrt{LC}}$$

and $(f_o) = \frac{1}{2\pi\sqrt{LC}}$

At resonant frequency (f_o) the admittance is minimum so the impedance is maximum and the current is minimum.

5.21 PARALLEL RESONANCE IN RC-RL CIRCUIT

A parallel combination of RL and RC branches connected to a source of emf E is shown in Fig. 5.51.

The above circuit will produce parallel resonance when the resultant current is in phase with the applied voltage or the net susceptance of the above circuit is zero.

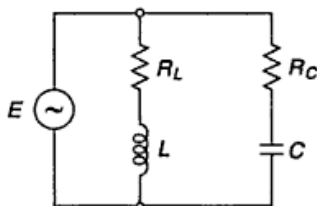


Fig. 5.51 RL and RC parallel circuit

$$\begin{aligned} \text{Total admittance } Y = y_1 + y_2 &= \frac{1}{R_L + j\omega L} + \frac{1}{R_C - j\frac{1}{\omega C}} \\ &= \frac{R_L - j\omega L}{R_L^2 + \omega^2 L^2} + \frac{R_C - j\frac{1}{\omega C}}{R_C^2 + \frac{1}{\omega^2 C^2}} \end{aligned}$$

So the net susceptance $\frac{-\omega L}{R_L^2 + \omega^2 L^2} + \frac{\frac{1}{\omega C}}{R_C^2 + \frac{1}{\omega^2 C^2}}$

$$\frac{\omega L}{R_L^2 + \omega^2 L^2} = \frac{\omega C}{\omega^2 C^2 R_C^2 + 1}$$

$$\omega^2 R_C^2 C^2 L + L = R_L^2 C + \omega^2 L^2 C$$

or $\omega^2 (R_L^2 C^2 L - L^2 C) = R_L^2 C - L$

or $\omega^2 = \frac{R_L^2 C - L}{LC(R_C^2 C - L)}$ or, $\omega = \sqrt{\frac{1}{LC} \frac{R_L^2 C - L}{R_C^2 C - L}}$

So, Resonant frequency is $\left(\frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 C - L}{R_C^2 C - L}}\right)$ rad/s.

or $f_o = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_L^2 C - L}{R_C^2 C - L}}$ Hz.

5.54 A coil of $10\ \Omega$ resistance has an inductance of 0.1 H and is connected in parallel with a $200\ \mu\text{F}$ capacitor. Calculate the frequency at which the circuit will act as a non-inductive resistor of $R\ \Omega$. Find also the value of R .

Solution

Resistance of coil $R_L = 10\ \Omega$
 Inductance of coil $L = 0.1\text{ H}$
 Capacitance $C = 200 \times 10^{-6}\text{ F}$

$$\text{Resonant frequency } f_o = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = \frac{1}{2\pi} \sqrt{\frac{1}{0.1 \times 200 \times 10^{-6}} - \frac{(10)^2}{(0.1)^2}} = 31.8\text{ Hz.}$$

The value of non-inductive resistor R at resonance is the dynamic impedance of the circuit.

$$\therefore R = \frac{L}{CR} = \frac{0.1}{200 \times 10^{-6} \times 10} = 50\ \Omega.$$

5.55 In the circuit shown in Fig. 5.52 show that the circulating current at resonance is

given by $(I) = V \sqrt{\frac{C}{L}}$ for a supply voltage of V volts.

Solution

At resonance, Inductive reactance = Capacitive reactance

$$\therefore X_L = X_C \text{ or, } \omega L = \frac{1}{\omega C}$$

$$\text{Therefore } \omega_o = \frac{1}{\sqrt{LC}}.$$

$$\text{Current through } L \text{ (or } C) = \frac{V}{X_L} = \frac{V}{\omega_o L} = \frac{V}{\frac{1}{\sqrt{LC}} L} = V \sqrt{\frac{C}{L}}.$$

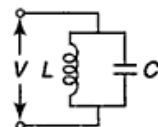


Fig. 5.52 Circuit diagram for Ex. 5.55

5.56 Calculate the value of R_C in the circuit shown in Fig. 5.53 which yields resonance.

Solution

Admittance of the inductive branch

$$y_1 = \frac{1}{10 + j10} = \frac{10 - j10}{100 + 100}$$

Admittance of the capacitive branch

$$y_2 = \frac{1}{R_C - 2j} = \frac{R_C + 2j}{R_C^2 + 4}.$$

$$\text{Net admittance } y = y_1 + y_2 = \frac{10 - j10}{100 + 100} + \frac{R_C + 2j}{R_C^2 + 4}$$

$$= \left(\frac{10}{200} + \frac{R_C}{R_C^2 + 4} \right) + j \left(\frac{-10}{200} + \frac{2}{R_C^2 + 4} \right).$$

As net susceptance is zero at resonance, so

$$\therefore \frac{-10}{200} + \frac{2}{R_C^2 + 4} = 0$$

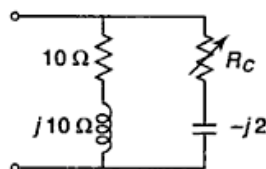


Fig. 5.53 Circuit diagram for Ex. 5.56

so, $400 - 40 - 10R_C^2 = 0$

or $R_C = \sqrt{\frac{360}{10}} = 6 \Omega.$

5.57 Show that no value of R_L in the circuit shown in Fig. 5.54 will make it resonant.

Solution

$$\text{Net admittance} = \frac{1}{R_L + j10} + \frac{1}{4 - j5} = \frac{(R_L - j10)}{R_L^2 + 100} + \frac{(4 + j5)}{16 + 25}$$

At resonance net susceptance is 0.

$$\therefore \frac{-10}{R_L^2 + 100} + \frac{5}{16 + 25} = 0$$

or $\frac{10}{R_L^2 + 100} = \frac{5}{41}$

or, $R_L^2 = \frac{41 \times 10}{5} - 100 = (\sqrt{-18})^2.$

This value of R_L is physically impossible and so no value of R_L can make the circuit resonant.

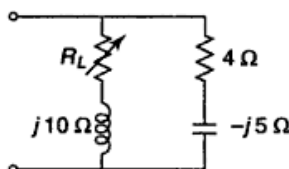


Fig. 5.54 Circuit diagram for Ex. 5.57

5.58 A 200 V, 50 Hz. source is connected across a $10\angle 30^\circ \Omega$ branch in parallel with a $10\angle -60^\circ \Omega$ branch. Find the impedance of the circuit element which when connected in series with the supply produces resonance.

Solution

$$V = 200 \text{ V}$$

$$Z_1 = 10\angle 30^\circ \Omega = 8.66 + j5$$

$$Z_2 = 10\angle -60^\circ = 5 - j8.66$$

Combined impedance of the parallel branches

$$\begin{aligned} &= \frac{Z_1 Z_2}{Z_1 + Z_2} \\ &= \frac{10\angle 30^\circ \times 10\angle -60^\circ}{8.66 + j5 + 5 - j8.66} \\ &= \frac{100\angle -30^\circ}{13.66 - j3.66} = \frac{100\angle -30^\circ}{14.14\angle -15^\circ} \\ &= 7.07\angle -15^\circ = 6.83 - j1.83. \end{aligned}$$

At resonance the net reactance of the circuit should be zero. So the element which is connected in series to produce resonance must have reactance of $j1.83$. So inductive reactance $X_L = 1.83 \Omega$ and inductance

$$L = \frac{X_L}{\omega} = \frac{1.83}{2\pi \times 50} \text{ H} = 5.83 \text{ mH}.$$

5.59 For the circuit shown in Fig. 5.55 find the frequency at which the circuit will be at resonance. If the capacitor and inductor are interchanged what would be the value of new resonant frequency.

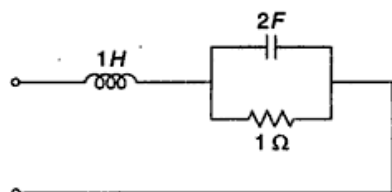


Fig. 5.55 Circuit diagram for Ex. 5.59

Solution

$$\begin{aligned} \text{Total impedance} &= j\omega \times 1 + \frac{1 \times \frac{1}{2j\omega}}{1 + \frac{1}{2j\omega}} = j\omega + \frac{1}{1 + 2j\omega} = j\omega + \frac{1 - j2\omega}{1 + 4\omega^2} \\ &= \frac{1}{1 + 4\omega^2} + j\left(\omega - \frac{2\omega}{1 + 4\omega^2}\right) \end{aligned}$$

\therefore Net reactance is zero at resonance

Hence,
$$\omega - \frac{2\omega}{1 + 4\omega^2} = 0$$

or
$$1 + 4\omega^2 = 2 \quad \text{or,} \quad \omega^2 = \frac{1}{4} \quad \text{or,} \quad \omega = \frac{1}{2} = 0.5 \text{ rad/s}$$

when the capacitor and inductor are interchanged

$$\begin{aligned} \text{Net impedance is } \frac{1}{2j\omega} + \frac{1 \times j\omega}{1 + j\omega} &= -\frac{1}{j2\omega} + \frac{j\omega}{1 + j\omega} \\ &= -\frac{j}{2\omega} + \frac{j\omega(1 - j\omega)}{1 + \omega^2} \\ &= -\frac{j}{2\omega} + \frac{j\omega + \omega^2}{1 + \omega^2} \\ &= \frac{\omega^2}{1 + \omega^2} + j\left(\frac{\omega}{1 + \omega^2} - \frac{1}{2\omega}\right) \end{aligned}$$

so
$$\frac{\omega}{1 + \omega^2} - \frac{1}{2\omega} = 0$$

or
$$2\omega^2 = 1 + \omega^2$$

or
$$\omega^2 = 1 \quad \text{or,} \quad \omega = 1 \text{ rad/s.}$$

■ ADDITIONAL PROBLEMS ■

5.60 A voltage of 400 V is applied across a pure resistor, a pure capacitor and an inductive coil which are in parallel. The resultant current is 6 A and the currents in the above components are 3 A, 4 A and 2 A respectively. Find the power factor of the inductive coil and the power factor of the whole circuit.

Solution

The current in the resistor $I_R = 3$ A.

The current in the capacitor $(I_C) = 4$ A.

The current in the inductive coil $(I_L) = 2$ A.

Let the current in the inductive coil be $(x - jy)$

$\therefore \sqrt{x^2 + y^2} = 2 \quad \text{or,} \quad x^2 + y^2 = 4. \quad \text{(i)}$

Total current $I = 3 + j4 + x - jy$

so
$$\sqrt{(3+x)^2 + (4-y)^2} = 6 \quad \text{(ii)}$$

or
$$x^2 + y^2 + 6x - 8y + 9 + 16 = 36$$

or
$$4 + 6x - 8y = 36 - 25 = 11$$

$$\text{or } 6x - 8y = 7$$

$$\text{or } x = \frac{7+8y}{6}$$

Substituting x in Eq. (1)

$$\left(\frac{7+8y}{6}\right)^2 + y^2 = 4$$

$$\text{or } 49 + 112y + 64y^2 + 36y^2 = 144$$

$$\text{or } 100y^2 + 112y - 95 = 0$$

$$\text{or } y^2 + 1.12y - 0.95 = 0$$

$$\text{or } y = 0.564 \quad (\text{taking positive value of } y)$$

$$\text{so } x = \frac{7+8 \times 0.564}{6} = 1.92.$$

$$\text{p.f. of the inductive coil} = \frac{x}{I_L} = \frac{1.92}{2} = 0.96 \text{ lag.}$$

$$\text{p.f. of the whole circuit} = \frac{\text{Real part of total current}}{I} = \frac{(3+x)}{6} = \frac{(3+1.92)}{6} = 0.82.$$

As the j component of total current is positive, i.e. $(4 - 0.564) = 3.436$ so the p.f. of the circuit is leading, i.e. p.f. of the whole circuit is 0.82 lead.

5.61 A 400 V single phase ac motor is tested in parallel with a 100Ω resistor. The motor takes 5 A current at lagging p.f. and the total current is 7 A. Find the p.f. and power of the whole circuit and for the motor alone.

Solution

$$\text{Current through resistor} \quad (I_R) = \frac{400}{100} \text{ A} = 4 \text{ A.}$$

$$\text{Current through motor} \quad (I_m) = 5 \text{ A.}$$

$$\text{Total current} \quad (I) = 7 \text{ A.}$$

Let the motor current be $(x - jy)$.

$$\therefore x^2 + y^2 = 5^2 = 25.$$

$$\text{Total current} = 4 + x - jy.$$

$$\therefore (4+x)^2 + y^2 = 7^2 = 49.$$

$$\text{or } 16 + x^2 + y^2 + 8x = 49$$

$$\text{or } 25 + 8x = 49 - 16 = 33$$

$$\text{or } 8x = 8$$

$$\text{or } x = 1.$$

$$\text{Thus } y = \sqrt{25 - 1^2} = \sqrt{24} = 4.9.$$

$$\text{p.f. of the motor} = \frac{x}{I_m} = \frac{1}{5} = 0.2 \text{ lagging.}$$

The complex part of the total current negative. So the p.f. of the whole circuit is lagging.

$$\therefore \text{the p.f. of the whole circuit} = \frac{4+x}{7} = \frac{4+1}{7} = \frac{5}{7} = 0.714 \text{ (lag).}$$

$$\begin{aligned} \text{Power of the whole circuit} &= 400 \times \text{real part of total current} \\ &= 400 \times (4+x) = 400 \times 5 = 2000 \text{ W.} \end{aligned}$$

$$\begin{aligned} \text{Power of motor alone} &= 400 \times \text{real part of motor current} \\ &= 400 \times 1 = 400 \text{ W.} \end{aligned}$$

.....

5.62. A coil of resistance $5\ \Omega$ and inductance 0.1 H is connected in parallel with a circuit containing a coil of resistance $4\ \Omega$ and inductance 0.05 H in series with a capacitor C and a pure resistor R . Calculate the values of C and R so that currents in either branch are equal but differ in phase by 90° .

Solution

$$\begin{aligned}\text{The impedance of coil 1 is } Z_1 &= 5 + j\omega \times 0.1 \\ &= 5 + j 2\pi \times 50 \times 0.1 \\ &= 5 + j 31.4.\end{aligned}$$

$$\begin{aligned}\text{The impedance of coil 2 is } (Z_2) &= 4 + R + j \left(2\pi \times 50 \times 0.05 - \frac{1}{2\pi \times 50 C} \right) \\ &= 4 + R + j \left(15.7 - \frac{1}{314 C} \right).\end{aligned}$$

As the currents in either branch are equal but differ in phase by 90°

$$\begin{aligned}\therefore Z_2 &= -jZ_1, \\ \text{i.e. } Z_2 &= 31.4 - j 5\end{aligned}$$

$$\text{Thus, } 4 + R = 31.4 \quad \text{and} \quad 15.7 - \frac{1}{314 C} = -5$$

$$\text{or } R = 31.4 - 4 = 27.4\ \Omega$$

$$\text{and } C = \frac{1}{314(15.7 + 5)}\text{ F} = 153.85\ \mu\text{F}.$$

.....

5.63. A 230 V 50 Hz supply is applied across a resistor of $10\ \Omega$ in parallel with a pure inductor. The total current is 25 A . What should be the value of the frequency if the total current is 36 A ?

Solution

Let the inductance of the pure inductor be L .

When frequency is 50 Hz the admittance of the circuit is

$$Y_1 = \frac{1}{10} + \frac{1}{j \times 2\pi \times 50 L} = 0.1 - \frac{j}{314 L}.$$

$$\therefore \sqrt{(0.1)^2 + \left(\frac{1}{314 L} \right)^2} = \frac{25}{230}$$

$$\text{or } 0.01 + \frac{1}{98596 L^2} = 0.0118$$

$$\text{or } L = \frac{1}{\sqrt{98596(0.0118 - 0.01)}}\text{ H} = 0.075\text{ H}$$

Let at frequency f the total current be 36 A .

$$\text{Then, } \sqrt{(0.1)^2 + \frac{1}{2 \times 3.14 f \times 0.075}} = \frac{36}{230} = 0.156$$

$$\text{or } \frac{1}{0.471 f} = (0.156)^2 - 0.01 = 0.014$$

$$\text{or } f = \frac{1}{0.471 \times 0.014}\text{ Hz} = 151\text{ Hz}.$$

.....

5.64 In the arrangement shown in Fig. 5.56 calculate the impedance between A and B and the phase angle between voltage and current.

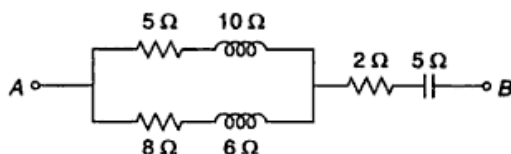


Fig. 5.56 Circuit diagram for Ex. 5.64

Solution

$$\begin{aligned}
 Z_{AB} &= \frac{(5 + j10)(8 + j6)}{5 + j10 + 8 + j6} + (2 - j5) \\
 &= \frac{40 - 60 + j(80 + 30)}{13 + j16} + (2 - j5) \\
 &= \frac{-20 + j110}{13 + j16} + (2 - j5) = \frac{11.8 \angle 100.3^\circ}{20.61 \angle 50.9^\circ} + (2 - j5) \\
 &= 5.42 \angle 49.4^\circ + 2 - j5 \\
 &= 5.53 - j 0.88 \\
 &= 5.6 \angle -9.04^\circ.
 \end{aligned}$$

The impedance is 5.6Ω and the angle between voltage and current is 9.04° (current is lagging w.r.t voltage).

5.65 How a current of 50 A is shared among three parallel impedances of $(5 + j 8)$, $(6 - j 8)$ and $(8 + j 9) \Omega$?

Solution

$$\begin{aligned}
 Z_1 &= 5 + j 8 = 9.43 \angle 58^\circ \\
 Z_2 &= 6 - j 8 = 9.16 \angle -53.13^\circ \\
 Z_3 &= 8 + j 9 = 12 \angle 48.37^\circ.
 \end{aligned}$$

The admittances of the three branches

$$\begin{aligned}
 y_1 &= \frac{1}{9.43 \angle 58^\circ} = 0.106 \angle -58^\circ \\
 y_2 &= \frac{1}{9.16 \angle -53.13^\circ} = 0.109 \angle +53.13^\circ \\
 y_3 &= \frac{1}{12 \angle 48.37^\circ} = 0.08 \angle -48.37^\circ.
 \end{aligned}$$

Net admittance $y = y_1 + y_2 + y_3 = \frac{10}{V}$, where V is the supply voltage.

$$\therefore (0.056 - j 0.09) + (0.065 + j 0.087) + (0.053 - j 0.06) = \frac{10}{V}$$

$$\text{or } 0.174 - j 0.063 = \frac{10}{V}$$

$$\text{or } V = \frac{10}{0.185} = 54 \text{ V.}$$

So the currents in the three impedances are

$$I_1 = y_1 V = 0.106 \times 54 = 5.724 \text{ A}$$

$$I_2 = y_2 V = 0.109 \times 54 = 5.886 \text{ A}$$

$$I_3 = y_3 V = 0.08 \times 54 = 4.32 \text{ A.}$$

5.66 Two coils of resistances 5Ω and 10Ω and inductance 0.01 H and 0.03 H respectively are connected in parallel. Calculate (a) the conductance, susceptance and admittance

of each coil (b) the total current taken by the circuit, when it is connected to a 230 V, 50 Hz. supply (c) the characteristics of single coil which will take the same current and power as taken by the original circuit.

Solution

$$\begin{aligned} \text{(a) Admittance of coil 1, } (y_1) &= \frac{1}{Z_1} = \frac{1}{5 + j100\pi \times 0.01} = \frac{1}{5 + j3.14} \\ &= \frac{1}{5.9 \angle 32.13^\circ} \\ &= 0.169 \angle -32.13^\circ = 0.143 - j 0.089. \end{aligned}$$

$$\begin{aligned} \text{Admittance of coil 2, } (y_2) &= \frac{1}{Z_2} = \frac{1}{10 + j100\pi \times 0.03} = \frac{1}{10 + j9.42} \\ &= \frac{1}{13.74 \angle 43.3^\circ} \\ &= 0.073 \angle -43.3^\circ = 0.053 - j 0.05. \end{aligned}$$

Conductance of coils 1 and 2 are 0.143 S and 0.053 S respectively, while susceptance of coils 1 and 2 are 0.089 S (inductive) and 0.05 S (inductive) respectively.

Admittance of coils 1 and 2 are 0.169 S and 0.073 S respectively.

(b) Total current taken by the circuit is

$$\begin{aligned} V_y &= 230(y_1 + y_2) \\ &= 230(0.143 - j 0.089 + 0.053 - j 0.05) \\ &= 230(0.196 - j 0.139) \\ &= 55.26 \text{ A.} \end{aligned}$$

$$\text{(c) } Z = \frac{1}{y} = \frac{1}{0.196 - j 0.139} = \frac{1}{0.24 \angle -35.34^\circ} = 4.167 \angle 35.34^\circ = 3.4 + j2.14.$$

The resistance of the single coil is 3.4 Ω and the inductive reactance is 2.14 Ω .

5.67 A coil of resistance 50 Ω and inductance 0.5 H forms part of a series circuit for which the resonant frequency is 60 Hz. If the supply voltage is 230 V, 50 Hz. find (a) the line current, (b) power factor and (c) the voltage across the coil.

Solution

$$60 = \frac{1}{2\pi\sqrt{0.5C}}, \text{ where } C \text{ is the capacitance}$$

$$\text{or } C = \frac{1}{0.5(2\pi \times 60)^2} = 14 \mu\text{F.}$$

$$\begin{aligned} \text{(a) Line current} &= \left(\frac{V}{Z} \right) = \frac{V}{\sqrt{(50)^2 + \left(314 \times 0.5 - \frac{10^6}{314 \times 14} \right)^2}} \\ &= \frac{230}{\sqrt{(50)^2 + (157 - 227.48)^2}} \\ &= \frac{230}{85.27} \text{ A} = 2.697 \text{ A.} \end{aligned}$$

$$\text{(b) Power factor} = \left(\frac{R}{Z} \right) = \frac{50}{85.27} = 0.586.$$

As capacitive reactance is greater than the inductive reactance so p.f. is leading.

$$\begin{aligned} \text{(c) Voltage across coil} &= 2.697 \sqrt{(50)^2 + (2\pi \times 50 \times 0.5)^2} \\ &= 2.697 \times 164.77 = 444.38 \text{ V.} \end{aligned}$$

.....

5.68 Two impedances $Z_1 = (5 + j\theta)$ and $(Z_2) = (10 - j5)$ are connected in parallel across a 200 V, 50 Hz supply. Find the current through each impedance and total current. What are the angles of phase difference of the branch currents with respect to the applied voltage?

Solution

Current through impedance Z_1 is

$$I_1 = \frac{200}{5 + j8} = \frac{200}{9.43 \angle 58^\circ} = 21.21 \angle -58^\circ \text{ A.}$$

Current through impedance Z_2 is

$$I_2 = \frac{200}{10 - j5} = \frac{200}{11.18 \angle -26.56^\circ} = 17.89 \angle 26.56^\circ \text{ A.}$$

$$\begin{aligned} \text{Total current } (I) &= I_1 + I_2 = 21.21 \angle -58^\circ + 17.89 \angle 26.56^\circ \\ &= 17.17 + j 6.12 = 18.23 \angle 19.62^\circ \text{ A.} \end{aligned}$$

Current in branch 1 is lagging the applied voltage by 58° and current in branch 2 is leading the applied voltage by 26.56° .

.....

5.69 In a circuit two parallel branches Z_1 and Z_2 are in series with Z_3 . The impedances are $Z_1 = 5 + j8$, $Z_2 = 3 - j4$ and $Z_3 = 8 + j11$. The voltage across Z_3 is 50 V. Find currents through the parallel branches and phase angle between them.

Solution

$$\begin{aligned} \text{Current through } Z_3 = \text{Total current} &= \frac{50 \angle 10^\circ}{8 + j10} = \frac{50}{12.8 \angle 51.34^\circ} \\ &= 3.9 \angle -51.34^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} \text{Current through } Z_1 \text{ is } I_1 &= 3.9 \angle -51.34^\circ \times \frac{(3 - j4)}{5 + j8 + 3 - j4} \\ &= 3.9 \angle -51.34^\circ \times \frac{5 \angle -53.13^\circ}{8.9 \angle 26.56^\circ} \\ &= 2.19 \angle -131.03^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} \text{Current through } Z_2 \text{ is } I_2 &= 3.9 \angle -51.34^\circ \times \frac{(5 + j8)}{5 + j8 + 3 - j4} \\ &= 3.9 \angle -51.34^\circ \times \frac{9.4 \angle 58^\circ}{8.9 \angle 26.56^\circ} \\ &= 4.12 \angle -19.9^\circ \text{ A.} \end{aligned}$$

Phase angle between the two currents $(131.03^\circ - 19.9^\circ) = 111.13^\circ$.

.....

5.70 The total current I in Fig. 5.57 is 15 A at lagging p.f. and the power consumed is 4 kW. The voltmeter reading is 300 V. Find the values of R_1 , X_1 , and X_2 .

Solution

The voltmeter reading is the voltage across 15Ω and X_2 . I is the current through that branch

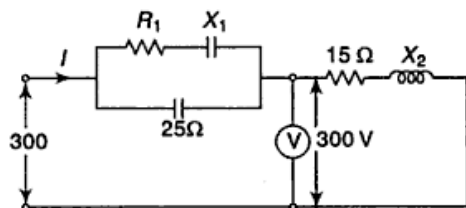


Fig. 5.57 Circuit diagram for Ex. 5.70

$$\frac{300}{15} = \sqrt{(15)^2 + X_2^2}$$

$$\text{or } X_2 = \sqrt{\left(\frac{300}{15}\right)^2 - (15)^2} = 13.23 \, \Omega.$$

Let $(R + jX)$ be the equivalent impedance of the parallel circuit

So net impedance, $Z = (R + 15) + j(X + 13.23)$

$$\therefore (R + 15)(15)^2 = 4000 \quad (\text{i})$$

$$\text{and } (R + 15)^2 + (X + 13.23)^2 = \left(\frac{300}{15}\right)^2 = 400 \quad (\text{ii})$$

$$\text{From Eq. (i)} \quad R = \frac{4000}{225} - 15 = 2.78 \, \Omega$$

$$\text{From Eq. (ii)} \quad (X + 13.23)^2 = 400 - (2.78 + 15)^2 = 83.87$$

$$\text{or } X = -4.072 \, \Omega.$$

Net admittance of the parallel branch

$$y = \frac{1}{2.78 - j4.072} = \frac{2.78 + j4.072}{24.31} = 0.114 + j 0.1675.$$

$$\text{So, } \frac{1}{R_1 - jX_1} + \frac{1}{-j25} = 0.114 + j 0.1675$$

$$\text{or } \frac{R_1 + jX_1}{R_1^2 + X_1^2} + j 0.04 = 0.114 + j 0.1675$$

$$\text{or } \frac{R_1}{R_1^2 + X_1^2} = 0.114 \quad (\text{iii})$$

$$\text{and } \frac{X_1}{R_1^2 + X_1^2} + 0.04 = 0.1675$$

$$\text{or } \frac{X_1}{R_1^2 + X_1^2} = 0.1275. \quad (\text{iv})$$

$$\text{Now, } \frac{R_1}{X_1} = \frac{0.114}{0.1275} = 0.89.$$

$$\text{From Eq. (iii)} \quad 0.89X_1 = 0.114 \{ (0.89)^2 X_1^2 + X_1^2 \}$$

$$\text{or } 0.204 X_1 = 0.89 \text{ or } X_1 = 4.35$$

$$\text{and } R_1 = 0.89 \times 4.35 = 3.88 \, \Omega.$$

5.71 Prove that the impedance of a parallel ac circuit containing R and L in one branch and R and C in the other branch (Fig. 5.58) is equal to R when $R^2 = \frac{L}{C}$.

If $L = 0.01 \, \text{H}$ and $C = 90 \, \mu\text{F}$, determine the impedance and current in each branch. Assume supply voltage to be $220 \, \text{V}$, $50 \, \text{Hz}$.

Solution

$$\text{Impedance } Z = \frac{(R + j\omega L) \left(R - \frac{j}{\omega C} \right)}{2R + j \left(\omega L - \frac{1}{\omega C} \right)} = \frac{R^2 + \frac{L}{C} + j \left(R\omega L - \frac{R}{\omega C} \right)}{2R + j \left(\omega L - \frac{1}{\omega C} \right)}$$

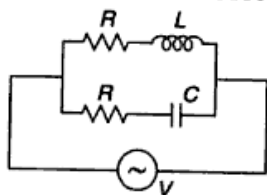


Fig. 5.58 Circuit diagram for Ex. 5.71

Since, $\frac{L}{C} = R^2$ we have

$$Z = \frac{R^2 + R^2 + jR\left(\omega L - \frac{1}{\omega C}\right)}{2R + j\left(\omega L - \frac{1}{\omega C}\right)} = R \frac{2R + j\left(\omega L - \frac{1}{\omega C}\right)}{2R + j\left(\omega L - \frac{1}{\omega C}\right)} = R.$$

When $L = 0.01 \text{ H}$ & $C = 90 \mu\text{F}$,

$$Z = R = \frac{L}{C} = \frac{0.01}{90 \times 10^{-6}} = \frac{1}{9} \times 10^3 = 111.11 \Omega$$

$$I_1 = \frac{220}{111.11 + j\omega 0.01} = \frac{220}{111.11 + j3.14} = 1.98 \angle -1.62^\circ \text{ A}$$

$$I_2 = \frac{220}{111.11 - j\frac{10^6}{90\omega}} = \frac{220}{111.11 - j35.385} = 1.98 \angle 17.66^\circ \text{ A}.$$

.....

5.72 A series connected RLC circuit has $R = 15 \Omega$, $L = 40 \text{ mA}$ and $C = 40 \mu\text{F}$. Find the resonant frequency and under resonant condition calculate the current, power, voltage drops across various elements if the applied voltage is 75 V .

Solution

$$\text{Resonant frequency } f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \times 3.14 \sqrt{0.04 \times 0.40 \times 10^{-6}}} = 125.88 \text{ Hz}.$$

$$\text{Current at resonant condition } (I_o) = \frac{V}{R} = \frac{75}{15} = 5 \text{ A}.$$

$$\text{Power } (= VI_o) = 75 \times 5 = 375 \text{ W}.$$

$$\text{Voltage drop across } R = I_o R = 5 \times 15 = 75 \text{ V} = \text{Applied voltage}.$$

$$\text{Voltage drop across } L = I_o X_L = 5 \times 2\pi \times 125.88 \times 0.04 = 158.1 \text{ V}.$$

$$\text{Voltage drop across } C = I_o X_C = \frac{5 \times 10^6}{2\pi \times 125.88 \times 40} = 158.1 \text{ V}.$$

.....

5.73 A series circuit consists of a capacitor and a coil takes a maximum current of 0.314 A at 200 V , 50 Hz . If the voltage across the capacitor is 300 V at resonance determine the capacitance, inductance, resistance and Q of the coil.

Solution

$$I_o = 0.314 \text{ A}$$

$$I_o R = 200 \text{ or } R = \frac{200}{0.314} \Omega = 636.943 \Omega$$

$$I_o X_C = 300 \text{ V or } X_C = \frac{300}{0.314} \Omega = 955.4 \Omega = \frac{1}{\omega_o C}.$$

$$\therefore C = \frac{1}{2\pi \times 50 \times 955.4} \text{ F} = 3.33 \mu\text{F}.$$

$$\text{Again } I_o X_L = 300 \text{ or } X_L = \frac{300}{0.314} = 955.4 = \omega_o L$$

$$\therefore L = \frac{955.4}{2\pi \times 50} \text{ H} = 3.04 \text{ H}.$$

$$'Q' \text{ of the coil} = \frac{\omega_o L}{R} = \frac{2\pi \times 50 \times 3.04}{636.943} = 1.5.$$

5.74 In a series resonant circuit, the resistance is 6Ω , the resonant frequency is 4.1×10^6 rad/s and the bandwidth is 10^5 rad/s. Find L and C of the network, half power frequencies and Q_{factor} of the circuit.

Solution

$$R = 6 \Omega, \quad \omega_o = 4.1 \times 10^6 \text{ rad/s}$$

$$\text{Bandwidth} \quad (\omega_2 - \omega_1) = \Delta\omega = 10^5 \text{ rad/s}$$

$$\therefore \quad Q = \frac{\omega_o}{\Delta\omega} = \frac{4.1 \times 10^6}{10^5} = 41$$

$$\text{Also,} \quad Q = \frac{\omega_o L}{R} = 41$$

$$\text{or} \quad \frac{4.1 \times 10^6 \times L}{R} = 41$$

$$\text{or} \quad L = \frac{41 \times 6}{4.1 \times 10^6} = 6 \times 10^{-5} \text{ H.}$$

As at resonance, $X_L = X_C$,

$$C = \frac{1}{L\omega_o^2} = \frac{1}{6 \times 10^{-5} \times (4.1 \times 10^6)^2} = \frac{10^{-6}}{1008.6} = 9.91 \times 10^{-10} \text{ F.}$$

$$\text{Lower half power frequency } (\omega_1) = \left(\omega_o - \frac{R}{2\pi L} \right) = 4.1 \times 10^6 - \frac{6 \times 10^5}{2 \times 6} = 4.05 \times 10^6 \text{ rad/s.}$$

$$\begin{aligned} \text{Upper half power frequency } (\omega_2) &= \left(\omega_o + \frac{R}{2\pi L} \right) \\ &= 4.1 \times 10^6 + \frac{6 \times 10^5}{2 \times 6} \\ &= 4.15 \times 10^6 \text{ rad/s.} \end{aligned}$$

5.75 A coil having a resistance of 25Ω and an inductance of 25 mH is connected in parallel with a variable capacitor. For what value of C will the circuit be resonant if a 90 V , 400 Hz . source is applied? What will be the line current under this condition?

Solution

$$\begin{aligned} (f_o) &= \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}, \text{ where } (f_o) = \text{Resonant frequency} \\ &= \frac{1}{2\pi} \sqrt{\frac{1}{0.025 X_C} - \left(\frac{25}{0.025} \right)^2} = 400 \text{ Hz} \end{aligned}$$

$$\text{or} \quad \frac{1}{0.025 C} - 10^6 = (400 \times 2\pi)^2 = 6310144$$

$$\therefore \quad C = 5.47 \mu\text{F}$$

$$\begin{aligned} \text{Line current} \quad (I_o) &= \frac{V}{(L/CR)} = \frac{90}{\frac{0.025}{5.47 \times 10^{-6} \times 25}} \text{ A} = 0.492 \text{ A.} \end{aligned}$$

5.76 Two impedances $Z_1 = (10 + j15) \Omega$ and $Z_2 = (20 - j25) \Omega$ are connected in parallel and this parallel combination is connected in series with impedance (Z_3) = $(25 + jX) \Omega$. Find for what value of X resonance occurs.

Solution

The net impedance of the whole circuit

$$\begin{aligned} Z &= \frac{Z_1 Z_2}{Z_1 + Z_2} + Z_3 = \frac{(10 + j15)(20 - j25)}{10 + j15 + 20 - j25} + 25 + jX \\ &= \frac{18.03 \angle 56.31^\circ \times 32 \angle -51.34^\circ}{30 - j10} + 25 + jX \\ &= \frac{576.96 \angle 4.97^\circ}{31.62 \angle -18.43^\circ} + 25 + jX \\ &= 18.247 \angle 23.4^\circ + 25 + jX \\ &= 16.74 + j7.24 + 25 + jX \\ &= 41.74 + j(X + 7.25). \end{aligned}$$

For resonance the reactive part of the impedance must be zero, i.e. net reactance is 0.

$$\therefore X + 7.25 = 0$$

$$\text{or } X = -7.25 \Omega; \quad \text{*****}$$

5.77 A coil having a resistance of 30Ω and inductive reactance of 33.3Ω is connected to a 125 V, 50 Hz. source. A series circuit consisting of 200Ω resistor and a variable capacitor is then connected in parallel with the coil. For what value of capacitance will the circuit be in resonance? Given that resonant frequency is 60 Hz.

Solution

Here a series R-L circuit is in parallel with a series R-C circuit.

$$\text{Resonant frequency } f_o = \frac{1}{2\pi} \sqrt{\frac{1}{LC} \left[\frac{L - CR_L^2}{L - CR_C^2} \right]}$$

$$\text{Now at 50 Hz., } (X_{SL}) = 33.3 \Omega$$

$$\text{or } L = \frac{33.3}{2\pi \times 50} \text{ H} = 0.106 \text{ H.}$$

$$\text{Again, resonant frequency} = 60 = \frac{1}{2\pi} \sqrt{\frac{1}{0.106 C} - \frac{0.106 - C(30)^2}{0.106 - C(200)^2}}$$

$$\text{or } \frac{1}{0.106 C} - \frac{0.106 - 900 C}{0.106 - 40000 C} = (376.8)^2 = 141978.24$$

$$\text{or } \frac{0.106 - 40000 C - 0.106 C(0.106 - 900 C)}{0.106 C(0.106 - 40000 C)} = 141978.24$$

$$\begin{aligned} 0.106 - 40000 C + 95.4 C^2 &= 1595.27 C - 601987737 C^2 \\ \text{or } C &= 66 \mu\text{F.} \end{aligned}$$

5.78 An inductor in series with a variable capacitor is connected across a constant voltage source of frequency 10 kHz. When the capacitor is 700 pF the current is maximum, when the capacitance is 900 pF the current is half of its maximum value. Find the resistance, inductance and Q factor of the inductor.

Solution

$$\text{Resonant frequency } f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$\text{or } 10 \times 10^3 = \frac{1}{2\pi\sqrt{L \times 700 \times 10^{-12}}} = \frac{10^6}{2\pi\sqrt{700L}}$$

$$\text{or } 700L = \left(\frac{10^6}{10 \times 10^3 \times 2\pi} \right)^2 = 253.56$$

$$\text{or } L = 0.362 \text{ H.}$$

The maximum current = $\frac{V}{R}$, where V is the supply voltage and R is the resistance.

When capacitor value = 900 pF.

$$\text{Current} = \frac{1}{2} \times \text{max. value of current}$$

$$\therefore \text{current} = \frac{1}{2} \times \frac{V}{R} = \frac{V}{2R}$$

$$\text{Again } \frac{V}{2R} = \frac{V}{\sqrt{R^2 + \left\{ 2\pi \times 10 \times 10^3 \times 0.362 - \frac{10^{12}}{2\pi \times 10 \times 10^3 \times 900} \right\}^2}}$$

$$\text{or } 4R^2 = R^2 + 25409139.5 \quad \text{or } R = 2910.3 \, \Omega$$

$$Q_{\text{factor}} = \frac{\omega_o L}{R} = \frac{2\pi \times 10 \times 10^3 \times 0.362}{2910.3} = 7.8.$$

.....

5.79 A coil of resistance $10 \, \Omega$ and inductance 0.5 H is connected in series with a capacitor across a voltage source. When the frequency is 50 Hz the current is maximum. Another capacitor is connected in parallel with the circuit. What capacitance must it have so that the combination acts as a pure resistor at 100 Hz ?

Solution

The current is maximum at resonance. So 50 Hz is the resonant frequency.

$$\therefore f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$\text{or } 50 = \frac{1}{2\pi\sqrt{0.5C}}$$

$$\text{or } C = \left(\frac{1}{50 \times 2\pi} \right)^2 \times \frac{1}{0.5} = 20.28 \, \mu\text{F.}$$

At 100 Hz the impedance of the series branch is

$$\begin{aligned} Z_1 &= 10 + j \left(2\pi \times 100 \times 0.5 - \frac{10^6}{2\pi \times 100 \times 20.28} \right) \\ &= 10 + j 235.48 = 235.69 \angle 87.57^\circ \end{aligned}$$

If C' is the capacitor connected in parallel with the circuit, impedance of the parallel branch is

$$= -jX_C$$

$$= -j \frac{1}{2\pi \times 100 C'}$$

Admittance of the combined circuit

$$= \frac{1}{235.69 \angle 87.57^\circ} + j200\pi C'$$

$$= 0.0042 \angle -87.57^\circ + j628 C'$$

$$= 0.000178 - j0.0042 + j628 C'$$

Net susceptance should be zero if the circuit acts as a pure resistor.

So, $0.0042 = 628 C'$ i.e., $C' = 6.68 \mu\text{F}$

5.80 A voltage of $100 \angle 30^\circ \text{ V}$ is applied to a circuit having two parallel branches. If the currents are $20 \angle 60^\circ \text{ A}$ and $10 \angle -45^\circ \text{ A}$ respectively find the kW, KVAR and kVA in each branch and in the whole circuit. What is the p.f. of the combined load?

Solution

For 1st branch

$$\text{kVA} = \frac{100 \times 20}{10^3} = 2$$

$$\text{kW} = \frac{100 \times 20}{10^3} \cos (60^\circ - 30^\circ) = 1.732$$

$$\text{KVAR} = \frac{100 \times 20}{10^3} \sin (60^\circ - 30^\circ) = 1 \text{ (lead)}.$$

For the 2nd branch

$$\text{kVA} = \frac{100 \times 10}{10^3} = 1$$

$$\text{kW} = \frac{100 \times 10}{10^3} \cos (30^\circ + 45^\circ) = 0.2588$$

$$\text{KVAR} = \frac{100 \times 10}{10^3} \sin (30^\circ + 45^\circ) = 0.9659 \text{ (inductive)}$$

$$\text{Total current} = 20 \angle 60^\circ + 10 \angle -45^\circ$$

$$= 10 + j 17.32 + 7.07 - j 7.07$$

$$= 17.07 + j 9.62 = 19.59 \angle 29.4^\circ.$$

For the whole circuit

$$\text{kVA} = \frac{100 \times 19.59}{10^3} = 1.959$$

$$\text{kW} = 1.959 \cos (30^\circ - 29.4^\circ) = 28.3$$

$$\text{KVAR} = 1.959 \sin (30^\circ - 29.4^\circ) = 1.175 \text{ (inductive)}$$

P.f. of combined load = $\cos (30^\circ - 29.4^\circ) = 1$

5.81 A choke coil has a resistance of 40Ω and Q factor of 5 at 1000 Hz. It is connected in parallel with a variable capacitor to a 10 V, 1000 Hz ac supply. Find (a) X_C for resonance (b) equivalent impedance as seen by the source and (c) current drawn from the supply.

Solution

$$Q \text{ factor} = \frac{\omega_o L}{R} = 5$$

$$\text{or } \frac{2\pi \times 1000 L}{40} = 5$$

$$\text{so } L = \frac{40 \times 5}{2\pi \times 1000} = 0.0318 \text{ H}$$

(a) If C is the capacitance then

$$\omega_o = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\text{or } (2\pi \times 1000)^2 = \frac{1}{0.0318 C} - \left(\frac{40}{0.0318}\right)^2$$

$$\text{or } \frac{1}{0.0318 C} = 41020615.89$$

$$\text{or } C = 0.766 \mu\text{F}$$

$$\text{or } X_C = \frac{1}{\omega_o C} = (2\pi \times 1000 \times 0.766 \times 10^{-6})^{-1} \\ = 207.7 \Omega.$$

(b) Equivalent impedance as seen by the source is

$$\frac{L}{CR} = \frac{0.0318}{40 \times 0.766} \times 10^{-6} = 1037.86 \Omega.$$

$$\text{(c) Current taken from supply} = \frac{10}{1037.86} = 9.6 \text{ mA.}$$

5.82 A pure capacitor of $60 \mu\text{F}$ is in parallel with another single circuit element. If the applied voltage and total current are $v = 100 \sin(2000t)$ and $i = 15 \sin(2000t + 75^\circ)$ respectively find the other element.

Solution

$$V = 100 \sin 2000t$$

$$i = 15 \sin(2000t + 75^\circ)$$

$$\text{Power factor} = \cos \theta = \cos 75^\circ = 0.2588 \text{ leading}$$

As the total current is leading by an angle less than 90° (i.e. 75°) so the other element must be a resistor.

$$\therefore \tan \theta = \tan 75^\circ = 3.73 = \frac{X_C}{R}$$

$$\text{or } R = \frac{X_C}{3.73} = \frac{1}{\omega C 3.73} = \frac{10^6}{2000 \times 50 \times 3.73} \Omega = 2.68 \Omega.$$

5.83 A resistor and a capacitor are in series with a variable inductor across a 100 V , 50 Hz supply. The maximum current obtained by varying inductance is 5 A . The voltage across capacitance is 200 V . Find the circuit elements.

Solution

$$\text{At resonance } (I) = \frac{V}{R} = 5 \text{ A}$$

$$\text{or } R = \frac{V}{5} = \frac{100}{5} = 20 \Omega$$

$$\text{Voltage across capacitor } (V_C) = I \times \frac{1}{\omega C} = 200$$

or

$$C = \frac{I}{200 \omega} = \frac{5}{200 \times 2\pi \times 50} \text{ F} = 79.6 \mu\text{F}$$

At resonance,

$$\omega L = \frac{I}{\omega C}$$

So,

$$L = \frac{I}{\omega^2 C} = \frac{10^6}{(2\pi \times 50)^2 \times 79.6} \text{ H} \\ = 0.127 \text{ H.}$$

.....

5.84 For the network shown in Fig. 5.59 determine the resonant frequency and input admittance at resonance.

Solution

The net admittance of the circuit

$$y = \frac{1}{5 \times 10^3} + j \frac{1}{X_C} + \frac{1}{50 + jX_L} \\ = \frac{1}{5 \times 10^3} + j\omega_o \times 10^{-6} + \frac{1}{50 + j\omega_o} \\ = \frac{1}{5 \times 10^3} + j\omega_o \times 10^{-6} + \frac{50 - j\omega_o}{(50)^2 + \omega_o^2}$$

For resonance the net susceptance should be zero.

$$\text{so } \omega_o \times 10^{-6} - \frac{\omega_o}{(50)^2 + \omega_o^2} = 0$$

$$\text{or } 2500 + \omega_o^2 = 10^6$$

$$\text{or } \omega_o = 998.75 \text{ rad/s}$$

$$\text{so } f_o = \frac{998.75}{2\pi} \text{ Hz} = 159 \text{ Hz.}$$

Input admittance at resonance is given by

$$y = \frac{1}{5 \times 10^3} + \frac{50}{(50)^2 + (998.75)^2} = 0.00025 \text{ S}$$

.....

5.85 For the network shown in Fig. 5.60 find the maximum value of R_C beyond which the circuit will not resonate.

Solution

Net admittance of the circuit is given as

$$y = \frac{1}{4 + j3} + \frac{1}{R_C - jX_C} \\ = \frac{1}{4 + j3} + \frac{1}{R_C - jX_C}$$

Under resonance condition,

$$\frac{-3}{16 + 9} + \frac{X_C}{R_C^2 + X_C^2} = 0$$

$$\text{or } 3X_C^2 + 3R_C^2 = 25 X_C$$

$$\text{or } 3X_C^2 - 25X_C + 3R_C^2 = 0$$

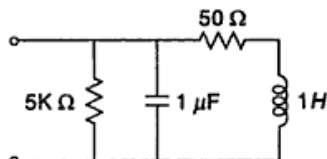


Fig. 5.59 Circuit diagram for Ex. 5.84

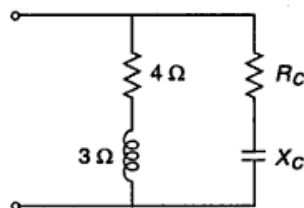


Fig. 5.60 Circuit diagram for Ex. 5.85

$$\text{or } X_C = \frac{25 \pm \sqrt{(25)^2 - 4 \times 3 \times 3R_C^2}}{3 \times 2}$$

If X_C is real then $(4 \times 3 \times 3R_C^2)$ should be less than or equal to $(25)^2$.
So maximum value of R_C is

$$R_C = \sqrt{\frac{(25)^2}{4 \times 3 \times 3}} = 4.167 \, \Omega.$$

5.86 Find the average and rms value of the waveform shown in Fig. 5.61.

Solution

The slope of the curve is obtained as

$$i = \frac{10}{T}t$$

Average value of the waveform is given by

$$I_{av} = \frac{1}{T} \int_0^T i \, dt = \frac{1}{T} \int_0^T \frac{10}{T}t \, dt = \frac{1}{T} \left[\frac{10}{T} \frac{t^2}{2} \right]_0^T = \frac{10 \times T^2}{T^2 \times 2} = 5 \, \text{A}.$$

rms value of the waveform is obtained as

$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{T} \int_0^T i^2 \, dt} = \sqrt{\frac{1}{T} \int_0^T \frac{100}{T^2} t^2 \, dt} = \sqrt{\frac{100}{T^3} \left[\frac{t^3}{3} \right]_0^T} \\ &= \sqrt{\frac{100 \times T^3}{T^3 \times 3}} = \frac{10}{\sqrt{3}} = 5.77 \, \text{A}. \end{aligned}$$

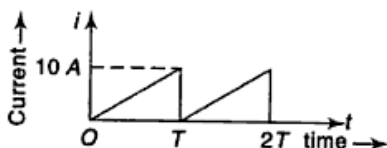


Fig. 5.61 Circuit diagram for Ex. 5.86

5.87 Find the average and rms value of the waveform shown in Fig. 5.62.

Solution

The average value of the waveform over a full cycle ($t = 0$ to $t = 1$) is 0. Considering half cycle ($t = 0.5$ to $t = 1$)

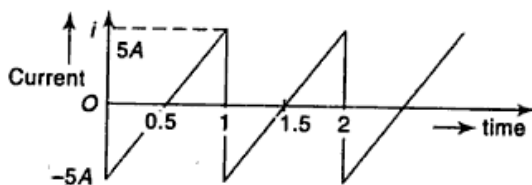


Fig. 5.62 Waveform for Ex. 5.87

$$I_{av} = \frac{1}{0.5} \int_{0.5}^1 i \, dt.$$

Now,
$$i = \frac{5}{0.5}t - 5 = 10t - 5$$

Hence
$$\begin{aligned} I_{av} &= \frac{1}{0.5} \int_{0.5}^1 (10t - 5) \, dt = 2 \left[\frac{10t}{2} - 5t \right]_{0.5}^1 \\ &= 2[5 \times 1^2 - 5 \times 1 - 5 \times (0.5)^2 + 5 \times 0.5] \\ &= 2[2.5 - 1.25] \\ &= 2.5 \, \text{A}. \end{aligned}$$

$$\begin{aligned}
 I_{r.m.s.} &= \sqrt{\frac{1}{0.5} \int_{0.5}^1 (10t - 5)^2 dt} \\
 &= \sqrt{\frac{1}{0.5} \int_{0.5}^1 (100t^2 + 25 - 100t) dt} \\
 &= \sqrt{2 \left[100 \frac{t^3}{3} - 50 \frac{t^2}{2} + 25t \right]_{0.5}^1} \\
 &= \sqrt{2 \left\{ \frac{100}{3} \times 1^3 - 50 \times \frac{1^2}{2} + 25 \times 1 \right.} \\
 &\quad \left. - \left[\frac{100}{3} (0.5)^3 + 50 \times (0.5)^2 \times \frac{1}{2} - 25 \times (0.5) \right] \right\}} \\
 &= 7.90 \text{ A}
 \end{aligned}$$

.....

5.88 Find the average and rms value of the waveform shown in Fig. 5.63.

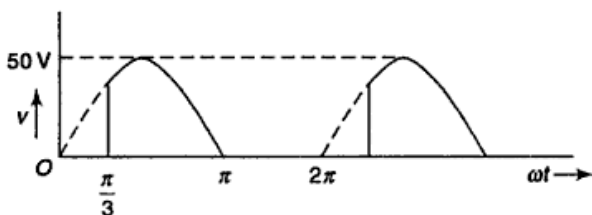


Fig. 5.63 Wave form for Ex. 5.88

Solution

The average value of the waveform

$$\begin{aligned}
 I_{av} &= \frac{1}{2\pi} \int_{\frac{\pi}{3}}^{\pi} 50 \sin \omega t \, d(\omega t) = \frac{50}{2\pi} [-\cos \omega t]_{\frac{\pi}{3}}^{\pi} \\
 &= \frac{50}{2\pi} \left[\cos \frac{\pi}{3} - \cos \pi \right] \\
 &= \frac{25}{\pi} [0.5 + 1] \\
 &= 11.937 \text{ V.}
 \end{aligned}$$

The rms value of the waveform

$$\begin{aligned}
 I_{rms} &= \sqrt{\frac{1}{2\pi} \int_{\frac{\pi}{3}}^{\pi} (50)^2 \sin^2 \omega t \, d(\omega t)} \\
 &= \frac{50}{\sqrt{2\pi}} \sqrt{\int_{\frac{\pi}{3}}^{\pi} \frac{1}{2} (1 - \cos 2\omega t) \, d(\omega t)}
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{1}{2} \times 19.95 \sqrt{\left[\omega t - \frac{\sin 2\omega t}{2} \right]_{\frac{\pi}{3}}^{\pi}} \\
 &= 14.11 \sqrt{\pi - \frac{\sin 2\pi}{2} - \frac{\pi}{3} + \frac{\sin \frac{2\pi}{3}}{2}} \\
 &= 14.11 \sqrt{\pi - \frac{\pi}{3} + 0.433} = 22.142 \text{ A.}
 \end{aligned}$$

.....

5.89 If the waveform of a current has form factor 1.2 and peak factor 1.7 find the average and rms value of the current if the maximum value of the current is 100 A.

Solution

$$\text{Form factor} = \frac{I_{\text{rms}}}{I_{\text{av}}} = 1.2$$

$$\text{Peak factor} = \frac{I_m}{I_{\text{rms}}} = \frac{100}{I_{\text{rms}}} = 1.7$$

$$\text{Hence } I_{\text{r.m.s.}} = \frac{100}{1.7} = 58.82 \text{ A}$$

$$\text{and } I_{\text{av}} = \frac{I_{\text{rms}}}{1.2} = \frac{58.82}{1.2} \text{ A} = 49 \text{ A.}$$

.....

5.90 A sinusoidal signal has a value of (-5) A at $t = 0$ and reached its first negative maximum of (-10) A at 2 ms. Write the equation for the current.

Solution

Let us consider the equation for the current is

$$i(t) = I_m \sin(\omega t + \theta)$$

$$\text{At } t = 0, i(t) = I_m \sin \theta = -5$$

$$\text{At } t = 2 \times 10^{-3} \text{ s, } i(t) = I_m \sin(\omega \times 2 \times 10^{-3} + \theta) = -10$$

Now, $I_m = 10$ A (negative and positive maximum values are same)

$$\text{Hence } \sin \theta = -\frac{5}{10} = -0.5 = \sin\left(-\frac{\pi}{6}\right) = \sin 210^\circ$$

$$\text{i.e. } \theta = 210^\circ$$

$$\text{Again } \sin(\omega \times 2 \times 10^{-3} + 210^\circ) = -\frac{10}{10} = -1 = \sin 270^\circ$$

$$\text{Hence } \omega \times 2 \times 10^{-3} = 270^\circ - 210^\circ = 60^\circ = \frac{\pi}{3}$$

$$\text{i.e. } \omega = \frac{\pi \times 10^3}{6} = 523.6$$

$$i = 10 \sin(523.6t + 210^\circ) \text{ A.}$$

.....

5.91 In a circuit the voltage and impedance are given by $v = (100 + j80) \text{ V}$ and $Z = (10 + j8) \Omega$. Find the active and reactive power of the circuit.

Solution

It is given that,

$$Z = 10 + j 8 = 12.8 \angle 36.86^\circ \Omega$$

$$v = 100 + j 80 = 128 \angle 36.86^\circ \text{ V.}$$

Hence current $i = \frac{v}{Z} = \frac{128 \angle 36.86^\circ}{12.8 \angle 36.86^\circ} = 10 \angle 0^\circ \text{ A.}$

Power factor angle = angle between v and $i = 36.86^\circ$

Active power of the circuit

$$v \cdot i \cos \theta = 128 \times 10 \cos (36.86^\circ) = 1024 \text{ W.}$$

Reactive power of the circuit

$$v \cdot i \sin \theta = 128 \times 10 \sin (36.86^\circ) = 768 \text{ VAR.}$$

.....

5.92 Find an expression for the current and calculate the power when a voltage for $v = 283 \sin (100 \pi)$ is applied to a coil having $R = 50 \Omega$ and $L = 0.159 \text{ H}$.

Solution

Impedance $(Z) = R + j\omega L$

$$\omega = 100\pi = 314$$

Hence $Z = 50 + j \times 314 \times 0.159$

$$= 50 + j 49.95$$

$$= 70.67 \angle 44.97^\circ.$$

Now $v = 283 \sin 100 \pi$

rms value of $v = \frac{283}{\sqrt{2}} = 200 \text{ V.}$

$$\therefore \text{Rms value of current } (i_{\text{rms}}) = \frac{283 \angle 10^\circ}{\sqrt{2} \times 70.67 \angle 44.97^\circ} = 2.83 \angle -34.97^\circ \text{ A}$$

Now $(i_{\text{max}}) = \sqrt{2} \times 2.83 = 4 \text{ A.}$

The expression for current $i = 4 \sin (100 \pi - 44.97^\circ) \text{ A}$

Power = $VI \cos \theta$, where V and I are the rms values of voltage, and current and θ is the power factor angle.

Hence Power = $200 \times 2.83 \cos (44.97^\circ) = 400 \text{ W.}$

.....

5.93 An emf given by $100 \sin \left(314t - \frac{\pi}{4} \right) \text{ V}$ is applied to a circuit and the current is $20 \sin (314t - 1.5708) \text{ A}$. Find (a) frequency and (b) circuit elements.

Solution

$$V = 100 \sin \left(314t - \frac{\pi}{4} \right)$$

$\therefore \omega = 314 \text{ rad/s}$

(a) Frequency $f = \frac{\omega}{2\pi} = \frac{314}{2 \times 3.14} = 50 \text{ Hz.}$

(b) $i = 20 \sin (314 t - 1.5708) \text{ A} = 20 \sin \left(314t - \frac{\pi}{4} \right) \text{ A}$

Current i is lagging w.r.t v by an angle of $\frac{\pi}{2} - \frac{\pi}{4}$ i.e. $\frac{\pi}{4}$.

Hence the circuit contains R and L only. If Z is the impedance then

$$R = Z \cos \theta = \frac{100}{20} \cos \left(\frac{\pi}{4} \right) = 3.536 \, \Omega$$

and $\omega L = Z \sin \theta = \frac{100}{20} \sin \left(\frac{\pi}{4} \right) = 3.536 \, \Omega$

or, $L = \frac{3.536}{314} = 11.26 \, \text{mH}.$

5.94. A two element series circuit consumes 700 W and has a power factor of 0.707 leading. If the applied voltage is $v = 141 \sin(314t + 30^\circ)$, find the circuit elements.

Solution

$$\text{Active power} = VI \cos \theta = 700 \, \text{W}.$$

$$\text{Power factor } \cos \theta = 0.707 \, (\text{lead}).$$

Hence $VI = \frac{700}{0.707} = 990.$

Now $V = \text{rms value of voltage} = \frac{141}{\sqrt{2}} = 99.7 \, \text{V}.$

Hence, $I = \frac{990}{99.7} = 9.93 \, \text{A}$

and $Z = \frac{V}{I} = \frac{99.7}{9.93} \, \Omega = 10 \, \Omega.$

As the power factor is leading so the circuit contains resistance R and capacitance C .

Hence $R = Z \cos \theta = 10 \times 0.707 = 7.07 \, \Omega$

and $\frac{1}{\omega C} = Z \sin \theta = 10 \times 0.707 = 7.07 \, \Omega$

or $C = \frac{1}{314 \times 7.07} \, \text{farad} = 45.03 \, \mu\text{F}.$

5.95. For the circuit shown in Fig. 5.64 determine the equivalent admittance at terminals AB if $f = 50 \, \text{Hz}.$

Solution

Equivalent admittance of the parallel branches:

$$(y) = y_1 + y_2$$

$$= \frac{1}{4 + j100\pi \times 0.01} + \frac{1}{-j \times 10^6}$$

$$= \frac{1}{4 + 3.14j} + j \frac{31.4}{10^6}$$

$$= \frac{1}{5.08 \angle 38.13^\circ} + j \frac{31.4}{10^6}$$

$$= 0.1968 \angle -38.13^\circ + j31.4 \times 10^{-6}$$

$$= 0.155 - j0.1215 + j0.0000314$$

$$= 0.155 - j0.12147 \, \text{s}.$$

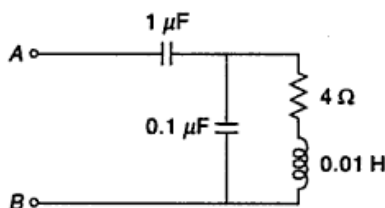


Fig. 5.64

Now admittance of $1 \mu\text{F}$ capacitor (y_3) = $j\omega C$
 $= j100 \pi \times 1 \times 10^{-6}$
 $= j0.000314.$

In the circuit y and y_3 are in series.

Hence equivalent admittance is

$$\begin{aligned}\frac{y y_3}{y + y_3} &= \frac{j0.000314(0.155 - j0.12147)}{j0.000314 + 0.155 - j0.12147} \\ &= \frac{0.000038 + j0.00004867}{0.155 - j0.121} \\ &= \frac{0.00006 \angle 52^\circ}{0.01967 \angle -47.98^\circ} = 0.003 \angle 99.98^\circ \text{ S.}\end{aligned}$$

5.96 A series circuit consists of a 10Ω resistor, a 30 mH inductor and a $1 \mu\text{F}$ capacitor is supplied from a 10 V variable frequency supply. Determine the frequency for which voltage developed across the capacitor is maximum and the magnitude of this maximum voltage.

Solution

$$\begin{aligned}\text{Resonant frequency } f_o &= \frac{1}{2\pi\sqrt{LC}} \\ &= \frac{1}{2 \times 3.14 \times \sqrt{30 \times 10^{-3} \times 1 \times 10^{-6}}} \text{ Hz} \\ &= 919 \text{ Hz.}\end{aligned}$$

Hence voltage across capacitor will be maximum when frequency is 919 Hz .

$$\text{Voltage across capacitor} = (I_o X_C) = \frac{V}{R} X_C = \frac{10}{10} \times \frac{1}{2\pi \times 919 \times 10^{-6}}$$

(where I_o is the current at resonance or maximum current).
 $= 173.27 \text{ V.}$

5.97 A coil of resistance 10Ω and inductance 10 mH is connected in parallel with a $25 \mu\text{F}$ capacitor. Calculate the frequency at resonance and the effective impedance of the circuit.

Solution

$$R = 10 \Omega \quad L = 10 \text{ mH} \quad C = 25 \times 10^{-6} \text{ F.}$$

$$\begin{aligned}\text{Resonant frequency } f_o &= \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \\ &= \frac{1}{2\pi} \sqrt{\frac{1}{10 \times 10^{-3} \times 25 \times 10^{-6}} - \frac{(10)^2}{(10 \times 10^{-3})^2}} \\ &= \frac{1}{2\pi} \sqrt{\frac{10^8}{25} - 10^6} \\ &= 275.8 \text{ Hz.}\end{aligned}$$

$$\text{The effective impedance of the circuit } \left(\frac{L}{CR} \right) = \frac{10 \times 10^{-3}}{25 \times 10^{-6} \times 10} = 40 \Omega.$$

5.98 Two coils are connected in parallel across 200 V, 50 Hz mains. One coil takes 0.8 kW and 1.5 kVA and the other coil takes 1 kW and 0.6 KVAR. Calculate the resistance and reactance of a single coil that would take the same current and power as the original circuit.

Solution

For the 1st coil

$$VI_1 = 1.5 \times 10^3$$

and $VI_1 \cos \theta_1 = 0.8 \times 10^3$

where I_1 and θ_1 are the current and power factor angle of the coil.

Now, $V = 200$

Hence, $I_1 = \frac{1.5 \times 10^3}{200} = 7.5 \text{ A}$

For the 2nd coil

$$VI_2 = 0.6 \times 10^3$$

and $VI_2 \cos \theta_2 = 1 \times 10^3$

(where I_2 and θ_2 are the current and power factor angle of the 2nd coil).

$$I_2 = \frac{0.6 \times 10^3}{200} = 3 \text{ A.}$$

Total current $I = I_1 + I_2 = (7.5 + 3) \text{ A} = 10.5 \text{ A.}$

$$\text{Total power} = (0.8 + 1) \text{ kW} = 1.8 \text{ kW.}$$

Let the resistance and the reactance of the single coil be R and X .

Now, $V = 200 \text{ V.}$

$$I = 10.5 \text{ A.}$$

Hence $Z = \frac{200}{10.5} = 19.07$

Also, $VI \cos \theta = 1.8 \times 10^3$

where $\cos \theta$ is the power factor of the single coil.

Hence $\cos \theta = \frac{1800}{200 \times 10.5} = 0.857$

$\therefore R = Z \cos \theta = 19.07 \times 0.857 = 16.34 \Omega$

and $X = Z \sin \theta = 19.07 \times 0.515 = 9.82 \Omega.$

.....

5.99 A capacitor is placed in parallel with two inductive loads, one 20 A at 30° lag and another one of 40 A at 60° lag. What must be the current in the capacitor so that the current from the external circuit shall be at unity power factor?

Solution

$$I_1 = 20 \angle -30^\circ \text{ A}$$

$$I_2 = 40 \angle -60^\circ \text{ A}$$

Horizontal component of

$$I_1 = I_{1x} = 20 \cos (-30^\circ) \text{ A} = 17.32 \text{ A.}$$

Vertical component of

$$I_1 = I_{1y} = 20 \sin (-30^\circ) \text{ A} = -10 \text{ A.}$$

Horizontal component of

$$I_2 = I_{2x} = 40 \cos (-60^\circ) \text{ A} = 20 \text{ A.}$$

Vertical component of

$$I_2 = I_{2y} = 40 \sin (-60^\circ) \text{ A} = -34.64 \text{ A.}$$

If I be the total current vertical component of

$$I = I_y = (-10 - 34.64) \text{ A} = -44.64 \text{ A.}$$

If the power factor is unity then vertical component of I should be zero.

Hence if I_c be the current from the capacitor then, $I_c + I_y = 0$, i.e. $I_c = -I_y = 44.64 \text{ A.}$

5.100. Two circuits having the same numerical ohmic impedance are joined in parallel. The power factor of one circuit is 0.8 lag and that of the other is 0.6 lag. Find the power factor of the whole circuit.

Solution

Let the supply voltage be V and the numerical value of impedance of each circuit be Z .

$$\text{Current in the 1st circuit } I_1 = \frac{V}{Z} \angle -\cos^{-1}(0.8) = \frac{V}{Z} \angle -36.87^\circ.$$

$$\text{Current in the 2nd circuit } I_2 = \frac{V}{Z} \angle -\cos^{-1}(0.6) = \frac{V}{Z} \angle -53.13^\circ.$$

The resultant current is $I_1 + I_2$

$$\begin{aligned} &= \frac{V}{Z} [\cos(-36.87^\circ) + j \sin(-36.87^\circ) + \cos(-53.13^\circ) \\ &\quad + j \sin(-53.13^\circ)] \\ &= \frac{V}{Z} (1.4 - j 1.4) = 1.98 \frac{V}{Z} \angle -45^\circ \end{aligned}$$

Hence power factor of the whole circuit is $\cos(45^\circ) \text{ lag} = 0.707 \text{ lag.}$

5.101. A cosine wave is represented by $v_{ab} = V_m \cos(\omega t + \theta)$, where the frequency is 50 Hz. In the expression of v_{ab} , the angle ωt and θ are usually expressed in radians. Express the angle in degrees and write down in the expression for V_{ab} .

Solution

$$v_{ab} = V_m \cos(\omega t + \theta) \text{ [given, } \omega t \text{ and } \theta \text{ in radians]}$$

\therefore In degrees we can represent as

$$\begin{aligned} v_{ab} &= V_m \cos(2 \times 180 \times 50 t + \theta) \\ &= V_m \cos(18000 t + \theta); \theta \text{ in degree.} \end{aligned}$$

[Note that in radian the same expression can be simplified as

$$\begin{aligned} v_{ab} &= V_m \cos(2\pi f \cdot t + \theta) \\ &= V_m \cos(2 \times 3.14 \times 50 t + \theta) \\ &= V_m \cos(314 t + \theta), \theta \text{ in radians}] \end{aligned}$$

5.102. A cosine wave is expressed as $v_{ab} = V_m \cos(360 ft + \theta)$, where θ is in degree. Convert it to sine wave expression.

Solution

$$\text{Given, } v_{ab} = V_m \cos(360 ft + \theta)$$

(Note that '360' stands for 2π , where $\pi = 180^\circ$) since we can convert a cosine function into a sine function by adding 90° to the angle (θ), we now can write

$$v_{ab} = V_m \sin(360 ft + \theta + 90^\circ), \theta \text{ in degree.}$$

[Similarly, we can convert a sine function $V_{ab} = V_m \sin(360 ft + \theta)$ to a cosine function by subtracting 90° from θ .

$$\text{i.e. } v_{ab} = V_m \cos(360 ft + \theta - 90^\circ), \theta \text{ in degree.}]$$

5.103. A voltage wave is applied across a load at input terminals marked "x - y". The voltage wave is denoted by a conventional cosine wave $v_{x-y} = V_m \cos(360 ft + \theta)$, θ being

expressed in degree and has a fixed value of 60° in the present case. If $V_m = 50$ V, find the voltage at $t = 0$, $t = 0.01$, $t = 0.05$ and $t = 1$ sec. Assume a 50 Hz frequency system.

Solution

$$v_{x-y} = V_m \cos(360 ft + \theta), \theta \text{ in degree}$$

Here
$$v_{x-y} = 50 \cos(360 \times 50 \times 0 + 60^\circ)$$

$$= 50 \cos 60^\circ = 25 \text{ Volts [at } t = 0 \text{ sec.]}$$

Similarly, for $t = 0.01, 0.05$ and 1.0 sec,
 we get

$$v_{x-y} = 50 \cos(360 \times 50 \times 0.01 + 60^\circ)$$

$$= -25 \text{ volts [at } t = 0.01 \text{ sec.]}$$

$$v_{x-y} = 50 \cos(360 \times 50 \times 0.05 + 60^\circ)$$

$$= -25 \text{ volts [at } t = 0.05 \text{ sec.]}$$

$$v_{x-y} = 50 \cos(360 \times 50 \times 1 + 60^\circ)$$

$$= +25 \text{ volts [at } t = 1.0 \text{ sec.]}$$

Observing the above result we may infer that v_{x-y} is +ve at $t = 0$ and 1.0 sec while v_{x-y} is -ve at $t = 0.01$ and $t = 0.05$ sec. This clearly indicates that at $t = 0$ or at $t = 1.0$ sec, terminal 'x' of that load is +ve with respect to terminal 'y' while for $t = 0.01$ or $t = 0.05$ sec., the terminal 'y' is +ve with respect to terminal 'x'.

[Note that the instantaneous values of v_{x-y} alternate in magnitude and sign depending on the instant of 't' while the rms value remains the same which can be calculated for the

given problem as $(V_{rms}) = \frac{V_m}{\sqrt{2}} = \frac{50}{\sqrt{2}} = 35.36 \text{ V.}]$

.....

5.104. A voltage applied across a load terminal 1-2, is expressed as $v_{1-2} = V_m \cos(2\pi ft + \theta)$ in a system having 50 Hz frequency and $\theta = 30^\circ$. Obtain the value of instantaneous voltage at $t = 27.15$ sec. and find how many cycles the voltage wave corresponds when $t = 27.15$ sec. Assume the peak voltage of the wave to be 100 V.

Solution

It is given that

$$v_{1-2} = V_m \cos(2\pi ft + \theta)$$

when π and θ are expressed in degrees.

Here
$$v_{1-2} = 100 \cos(360 \times 50 \times 27.15 + 30^\circ)$$

$$= 100 \cos(488700 + 30^\circ)$$

$$= -86.6 \text{ V.}$$

\therefore The instantaneous value of v_{1-2} is (-86.6) volts at $t = 27.15$ sec. and terminal 1 is negative with respect to 2.

For the second part of the given problem we would like to check the number of cycles that corresponds to $t = 27.15$ sec. It may be noted here that an angle of $(488700 + 30^\circ)$ corresponds to $(488730 + 360^\circ)$ cycles (or, 1357.5833 cycles). Then at $t = 27.15$ sec, the system completed 1357 full cycles and 0.5833 cycles. The latter corresponds to $0.5833 \times 360^\circ = 209.988^\circ$. [Also, $100 \cos(209.988^\circ) = (-86.6)$ volts].

.....

5.105. AC voltage of 230 V (rms) is applied across a load that takes a current of 10 A (rms) from the source. The current lags the voltage by 30° . Assuming the source ac voltage to be a sine wave of 50 Hz frequency, write down the expression for the voltage and current. Draw the respective wave shapes as well as the phasors.

Solution

Given: $V_{rms} = 230 \text{ V.}$

$$\therefore V_{\max} = V_{\text{rms}} \times \sqrt{2} = 325.22 \text{ V.}$$

$$\text{Also, } I_{\max} = 10 \times \sqrt{2} = 14.14 \text{ A}$$

$$[\because I_m = I_{\text{rms}} \times \sqrt{2} \text{ and } I_{\text{rms}} = 10 \text{ A}]$$

The voltage expression can be written as

$$\begin{aligned} v &= V_{\max} \sin(\omega t) \\ &= 325.22 \sin(314 t) \text{ V,} \end{aligned}$$

when ω is expressed in rad/sec.

$$\text{Also, } v = 325.22 \sin(2 \times 180 \times 50t)$$

(when the angle is expressed in degree.)

$$\text{i.e. } v = 325.22 \sin(18000 t) \text{ V.}$$

Since the current lags voltage by 30° , we can write

$$\begin{aligned} i &= I_m \sin(\omega t - \phi) \\ &= 14.14 \sin\left(314t - \frac{\pi}{6}\right) \text{ A} \end{aligned}$$

when the angle is expressed in radian

$$\text{and } i = 14.14 \sin(2 \times 180 \times 50t - 30^\circ)$$

$$= 14.14 \sin(18000t - 30^\circ),$$

when the angle is expressed in degree.

The phasor representation is given in Fig. 5.65

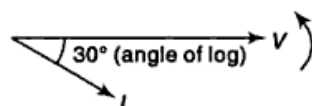


Fig. 5.65 I lagging V by 30°

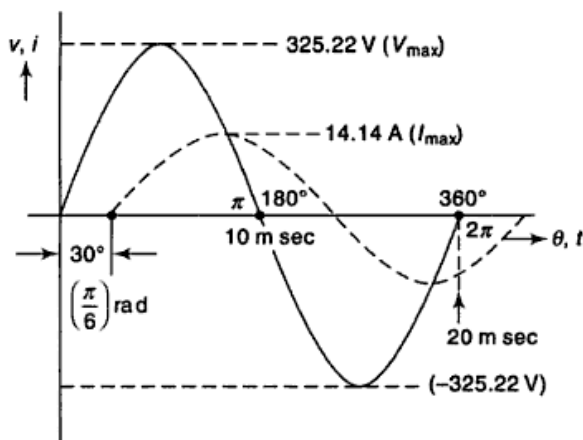


Fig. 5.66 V, I waves shapes

5.106. Obtain the average value of the current waveform $i = I_m \sin \omega t$ for (a) one complete period T and (b) half period $T/2$.

Solution

$$\begin{aligned} (a) \quad I_{av} &= \int_0^T I_m \sin \omega t \, dt = \frac{1}{T} \int_0^T I_m \sin \frac{2\pi}{T} \cdot t \, dt \\ &= -\frac{I_m}{2\pi} \left[\cos \frac{2\pi}{T} \cdot t \right]_0^T = 0. \end{aligned}$$

Thus average value of a sine wave (or even a cosine wave) for one complete period is zero.

$$\begin{aligned}
 (b) \quad I_{av} &= \frac{1}{T/2} \int_0^{T/2} I_m \sin \frac{2\pi}{T} \cdot t \cdot dt \\
 &= -\frac{I_m}{\pi} \left[\cos \frac{2\pi}{T} \cdot t \right]_0^{T/2} = +\frac{2I_m}{\pi}.
 \end{aligned}$$

It may be noted here that we have assumed the current waveform starting from the origin. As a general case we may think of the ac waveform starting from $t = t_0$ in the time scale on x-axis instead of assuming it starting from $t = 0$.

This gives us

$$\begin{aligned}
 I_{av} &= \frac{1}{T} \int_{t_0}^{t_0+T} I_m \sin \frac{2\pi}{T} \cdot t \cdot dt \\
 &= -\frac{I_m}{2\pi} \left[\cos \frac{2\pi}{T} \cdot t \right]_{t_0}^{t_0+T} = 0, \text{ for the complete cycle.}
 \end{aligned}$$

For the half cycle,

$$\begin{aligned}
 I_{av} &= \frac{1}{T/2} \int_{t_0}^{t_0+T} I_m \sin \frac{2\pi}{T} \cdot t \cdot dt \\
 &= -\frac{I_m}{\pi} \left[\cos \frac{2\pi}{T} \cdot t \right]_{t_0}^{t_0+T/2} \\
 &= -\frac{I_m}{\pi} \left(-\cos \frac{2\pi t_0}{T} - \cos \frac{2\pi t_0}{T} \right) \\
 &= \frac{2I_m}{\pi} \cos \omega t_0.
 \end{aligned}$$

Check: if we assume $t_0 = 0$, I_{av} for the half cycle of the ac wave becomes $\left(\frac{2I_m}{\pi} \right)$.

It may be noted here we could have written I_{av} for full cycle as

$$I_{av} = \frac{1}{2\pi} \int_0^{2\pi} I_m \sin \omega t \, d(\omega t)$$

and for half cycle as



$$I_{av} = \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t \, d(\omega t)$$

.....

5.107. Draw the power triangles for inductive and capacitive loads.

Solution

We start drawing with voltage and current phasors and in next step we draw power triangles (Fig. 5.67) and (Fig. 5.68). The steps are shown as follows:

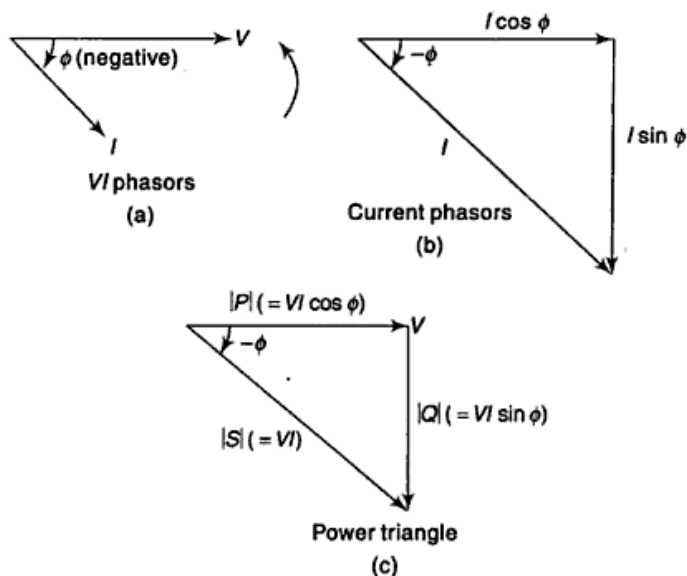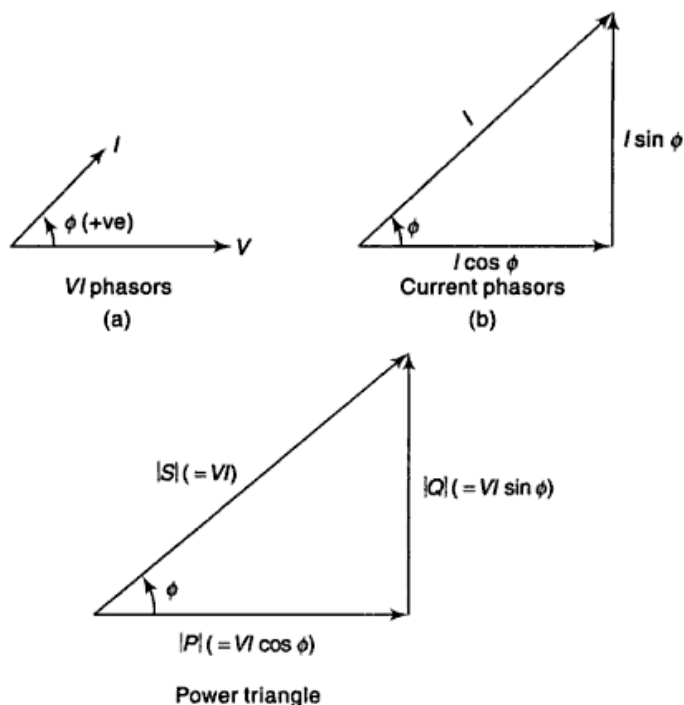For inductive loads**Fig. 5.67****For capacitive loads****Fig. 5.68**

Note: $P = VI \cos \phi = (IZ) I \times \frac{R}{Z} = I^2 R$

$Q = VI \sin \phi = (IZ) \times I \times \frac{X}{Z} = I^2 X$

$|S| = \sqrt{P^2 + Q^2}, \quad \angle \phi = \tan^{-1} \frac{Q}{P}$

$\cos \phi = \frac{P}{\sqrt{P^2 + Q^2}} = \frac{P}{|S|}.$

5.108 AC voltage (v) = $V_m \sin \omega t$ is applied across a load R . Obtain the expressions for instantaneous and average power.

Solution

Instantaneous power (p) = $\frac{v^2}{R}$

or $p = \frac{V_m^2}{R} \cdot \sin^2 \omega t = \frac{V_m^2}{2R} (1 - \cos 2 \omega t)$

In the expression of p , the constant part is $\left(\frac{V_m^2}{2R}\right)$ and hence it represents the magnitude of average power.

$\therefore P_{av} = \frac{V_m^2}{2R}.$

5.109 A voltage and a current in a circuit are expressed as

$v = V_m \sin \omega t$

$i = I_m \sin(\omega t - \theta).$

Find the instantaneous power.

Solution

Instantaneous power p is given by

$$\begin{aligned} p &= v \cdot i = V_m \sin \omega t \times I_m \sin(\omega t - \theta) \\ &= V_m \times I_m \times \frac{1}{2} [\cos(\omega t - \omega t + \theta) - \cos(\omega t + \omega t - \theta)] \\ &= \frac{1}{2} V_m I_m [\cos \theta - \cos(2\omega t - \theta)]. \end{aligned}$$

[It can be observed that

$$P_{av} = \frac{1}{2} V_m I_m \cos \theta,$$

but, $V_m = \sqrt{2} \times V_{rms}; I_m = \sqrt{2} I_{rms}$

$\therefore P_{av} = \frac{1}{2} \times 2 V_{rms} I_{rms} \cos \theta$

$$= V_{rms} \times I_{rms} \times \cos \theta$$

' $\cos \theta$ ' being known as power factor.]

5.110 The following voltages are expressed in time domain. Convert it to phasor domain.

- (a) $100 \sin \left(\omega t + \frac{\pi}{3} \right)$ (b) $100 \sin \omega t$ (c) $75 \cos \omega t$
 (d) $170 \sin \left(\omega t - \frac{2\pi}{9} \right)$ (e) $\sqrt{2} \times 165 \sin \left(\omega t - \frac{7\pi}{18} \right)$

Solution

$$(a) 100 \sin \left(\omega t + \frac{\pi}{3} \right) = \frac{100}{\sqrt{2}} \angle 60^\circ = 70.7 \angle 60^\circ.$$

$$(b) 100 \sin \omega t = \frac{100}{\sqrt{2}} \angle 0^\circ = 70.7 \angle 0^\circ.$$

$$(c) 75 \cos \omega t = 75 \sin \left(\omega t + \frac{\pi}{2} \right) = \frac{75}{\sqrt{2}} \angle 90^\circ = 53 \angle 90^\circ.$$

$$(d) 170 \sin \left(\omega t - \frac{2\pi}{9} \right) = \frac{170}{\sqrt{2}} \angle -40^\circ = 120 \angle -40^\circ.$$

$$(e) \sqrt{2} \times 165 \sin \left(\omega t - \frac{7\pi}{18} \right) = \frac{\sqrt{2} \times 165}{\sqrt{2}} \angle -70^\circ = 165 \angle -70^\circ$$

5.111 (a) Why the p.f. of ac circuit is always positive?

(b) Discuss when the reactive power is positive or negative.

Solution

(a) p.f. is represented by $\cos \theta$. Since $\cos \theta$ is an even function [$\cos \theta = \cos (-\theta)$] hence the power factor is always positive. Moreover, it is obviously always ≤ 1.0 .

(b) Q (reactive power) = $VI \sin \theta$

The sine wave is an odd function [$\sin \theta = -\sin(-\theta)$]. Hence Q is +ve when θ is negative Q is -ve when θ is +ve.

\therefore Lagging current (inductive circuit) produces +ve and leading current (capacitive circuit) produces (- Q). In resistive circuit $\theta = 0$ giving $Q = 0$.

5.112 A saw-tooth current waveform is shown in Fig. 6.69. Determine the average value, rms value and form factor.

Solution

The average value is obtained as

$$I_{av} = \frac{1}{T} \int_0^T i \, dt.$$

Here, $T = 100 \times 10^{-3}$ sec.

and $i = \frac{40 \times t}{100 \times 10^{-3}}$, a linear function

$$\begin{aligned} \therefore I_{av} &= \frac{1}{100 \times 10^{-3}} \int_0^{100 \times 10^{-3}} \frac{40}{100 \times 10^{-3}} \cdot t \, dt \\ &= \frac{40}{(100 \times 10^{-3})^2} \cdot \frac{t^2}{2} \Big|_0^{100 \times 10^{-3}} = 20 \text{ A.} \end{aligned}$$

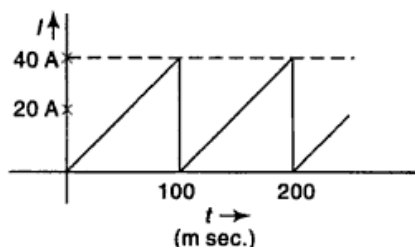


Fig. 5.69 Waveform for Ex. 5.112

rms value can be obtained as

$$\begin{aligned}
 I_{\text{rms}} &= \left[\frac{1}{T} \int_0^T i^2 dt \right]^{1/2} \\
 &= \left[\frac{1}{100 \times 10^{-3}} \int_0^{100 \times 10^{-3}} \left(\frac{40 \times t}{100 \times 10^{-3}} \right)^2 dt \right]^{1/2} \\
 &= \left[\frac{1}{100 \times 10^{-3}} \times \int_0^{100 \times 10^{-3}} (400t)^2 dt \right]^{1/2} \\
 &= \left[\frac{(400)^2}{100 \times 10^{-3}} \times \frac{t^3}{3} \Big|_0^{100 \times 10^{-3}} \right]^{1/2} \\
 &= 23.1 \text{ A.}
 \end{aligned}$$

The form factor is given by $\left(\frac{I_{\text{rm}}}{I_{\text{av}}} \right)$. Here form factor $\left(= \frac{23.1}{20} \right) = 1.155$.

5.113 For the waveform shown in Fig. 5.70, find the average and rms values for full cycle.

Solution

$$\begin{aligned}
 V_{\text{av}} &= \frac{1}{T} \int_0^{T/2} V_m \sin \omega t dt \\
 [\because \text{voltage between interval } T/2 \text{ and } T \text{ is zero}]
 \end{aligned}$$

$$= \frac{V_m}{\omega T} [-\cos \omega t]_0^{T/2} = \frac{V_m}{\pi}$$

$$\begin{aligned}
 V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T V_m^2 \sin^2 \omega t dt} \\
 &= \sqrt{\frac{1}{2T} \int_0^{T/2} V_m^2 (1 - \cos 2\omega t) dt} \\
 &= \frac{V_m}{2}
 \end{aligned}$$

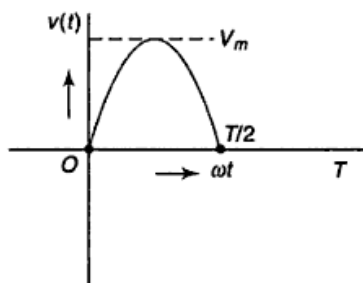


Fig. 5.70 Waveform for Ex. 5.113
[$T = 2\pi$; $T/2 = \pi$]

[The form factor can be calculated as $V_{\text{rms}}/V_{\text{av}}$ i.e. $(V_m/2)/(V_m/\pi)$ or, 1.57.]

5.114 Find the rms value of the resultant current in a wire that simultaneously carries a direct current of 10 A and a sinusoidal alternating current of peak value 10 A.

Solution

As per the given question,

$$\begin{aligned}
 I &= I_{\text{dc}} + I_{\text{ac}} = 10 + 10 \sin \omega t \\
 &= 10 (1 + \sin \omega t).
 \end{aligned}$$

$$\begin{aligned}
 \therefore I_{\text{rms}} &= \left[\frac{1}{2\pi} \int_0^{2\pi} \{10(1 + \sin \omega t)\}^2 d\omega t \right]^{1/2} \\
 &= \left[\frac{10^2}{2\pi} \int_0^{2\pi} (1 + 2\sin \omega t + \sin^2 \omega t) d\omega t \right]^{1/2} \\
 &= 10 \left\{ \frac{1}{2\pi} \left[(\omega t) - 2\cos(\omega t) + \frac{\omega t}{2} - \frac{\sin 2\omega t}{4} \right]_0^{2\pi} \right\}^{1/2} \\
 &= 10 \left\{ \frac{1}{2\pi} \times 3\pi \right\}^{1/2} = 12.25 \text{ A.}
 \end{aligned}$$

It may be noted here that we may replace 2π by T , the time period of the function and may write as

$$I_{\text{rms}} = \left[\frac{1}{T} \int_0^T \{10(1 + \sin \omega t)\}^2 dt \right]^{1/2}$$

where $\omega = \frac{2\pi}{T}$.

.....

5.115 Obtain average and effective value of waveform shown in Fig. 5.71.

Solution

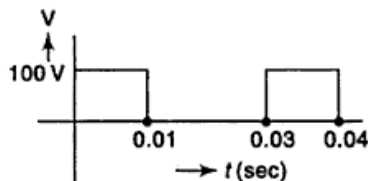


Fig. 5.71 Waveform for Ex. 5.115

$$\begin{aligned}
 V_{\text{av}} &= \frac{1}{T} \int_0^{T/3} v dt \\
 &= \frac{1}{0.03} \int_0^{0.01} 100 dt \\
 &= \frac{1}{0.03} \times 100 [t]_0^{0.01} \\
 &= 33.33 \text{ V.}
 \end{aligned}$$

$$\begin{aligned}
 \because v(t) &= 100 \text{ for } 0 \leq t \leq 0.01; \\
 v(t) &= 0 \text{ for } 0.01 \leq t \leq 0.03
 \end{aligned}$$

$$\begin{aligned}
 V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^{T/3} v^2 dt} \\
 &= \sqrt{\frac{1}{0.03} \int_0^{0.01} 100^2 dt} \\
 &= \sqrt{\frac{1}{0.03} \times 100^2 \times [t]_0^{0.01}} \\
 &= 57.74 \text{ V.}
 \end{aligned}$$

.....

5.116. Obtain the average and rms values of the waveform shown in Fig. 5.72.

Solution

From the given figure,

$$v(t) = 10, \text{ for } 0 \leq t \leq 1 \text{ sec}$$

$$v(t) = -10t + 10, \text{ for } 1 \leq t \leq 2 \text{ sec}$$

$$\therefore V_{av} = \frac{1}{2} \left[\int_0^1 10 dt + \int_1^2 (-10t + 10) dt \right]$$

$$= \frac{1}{2} \times 10 \times 1 + \frac{1}{2} \times (-10) \times \left[\frac{2^2 - 1^2}{2} \right] + \frac{1}{2} \times 10 \times [2 - 1]$$

$$= 5 - 7.5 + 5 = 2.5 \text{ V.}$$

$$V_{rms} = \sqrt{\frac{1}{2} \left[\int_0^1 10^2 dt + \int_1^2 (-10t + 10)^2 dt \right]}$$

$$= \frac{1}{\sqrt{2}} \left[100 \times t \Big|_0^1 + \int_1^2 10^2 (1-t)^2 dt \right]^{1/2}$$

$$= \frac{1}{\sqrt{2}} \times \left[100 + 100 \int_1^2 (1+t^2 - 2t) dt \right]^{1/2}$$

$$= \frac{1}{\sqrt{2}} \left[100 + 100 \left\{ (t^2) \Big|_1^2 + \frac{t^3}{3} \Big|_1^2 - 2 \cdot \frac{t^2}{2} \Big|_1^2 \right\} \right]^{1/2}$$

$$= \frac{1}{\sqrt{2}} \left[100 + 100 + \left\{ 1 + \frac{7}{3} - 3 \right\} \right]^{1/2}$$

$$= 8.17 \text{ V.}$$

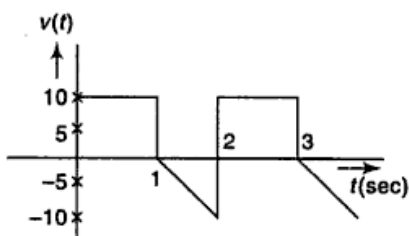


Fig. 5.72 Waveform for Ex. 5.116

5.117. Determine the average and the rms values of the waveform shown in Fig. 5.73.

Solution

It is evident that

$$v(t) = 100, \text{ for } 0 \leq t \leq \frac{T}{2}$$

$$= -20 \text{ for } \frac{T}{2} \leq t \leq T$$

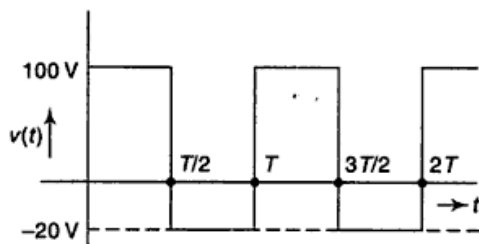


Fig. 5.73 Waveform for Ex. 5.117

$$V_{av} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \left[\int_0^{T/2} 100 dt + \int_{T/2}^T -20 dt \right]$$

$$= \frac{100}{T} [t]_0^{T/2} + \frac{-20}{T} [t]_{T/2}^T$$

$$= 50 - 10 = 40 \text{ V.}$$

$$\begin{aligned}
 V_{\text{rms}} &= \left[\frac{1}{T} \int_0^T v^2(t) dt \right]^{1/2} \\
 &= \left[\frac{1}{T} \int_0^{T/2} (100)^2 dt + \int_{T/2}^T (-20)^2 dt \right]^{1/2} \\
 &= \left[\frac{10^4}{T} \cdot t \Big|_0^{T/2} + \frac{400}{T} \cdot t \Big|_{T/2}^T \right]^{1/2} \\
 &= [5 \times 10^3 + 200]^{1/2} = (5200)^{1/2} = 72.1 \text{ V.}
 \end{aligned}$$

5.118 Obtain the rms value of the clipped waveform shown in the Fig. 5.74

Solution

By observation we can say (with $\theta = \omega t$),

$$v(\theta) = 10 \sin \theta, \text{ when } 0 < \theta < \frac{\pi}{4}$$

$$v(\theta) = 7.07, \text{ when } \frac{\pi}{4} < \theta < \frac{3\pi}{4}$$

$$v(\theta) = 10 \sin \theta, \text{ when } \frac{3\pi}{4} < \theta < \pi.$$

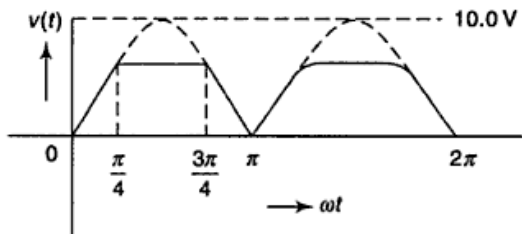


Fig. 5.74 Waveform for Ex. 5.118

[It may be noted that at $\theta = \frac{\pi}{4}$, since $10 \sin \theta = 10 \sin \frac{\pi}{4} = 7.07$, hence the equation of the wave for the period $\frac{\pi}{4}$ to $\frac{3\pi}{4}$ is 7.07 (constant magnitude).]

$$\begin{aligned}
 \therefore V_{\text{rms}} &= \left[\frac{1}{\pi} \int_0^{\pi/4} (10 \sin \theta)^2 d\theta + \int_{\pi/4}^{3\pi/4} (7.07)^2 d\theta + \int_{3\pi/4}^{\pi} (10 \sin \theta)^2 d\theta \right]^{1/2} \\
 &= \left[\frac{1}{\pi} \left\{ \int_0^{\pi/4} 100 \frac{(1 - \cos 2\theta)}{2} d\theta + \int_{\pi/4}^{3\pi/4} 50 d\theta + \int_{3\pi/4}^{\pi} 100 \frac{1 - \cos 2\theta}{2} d\theta \right\} \right]^{1/2} \\
 &= \left[\frac{50}{\pi} (\pi - 1) \right]^{1/2} = (34.1)^{0.5} \\
 &= 5.75 \text{ V.}
 \end{aligned}$$

5.119 The voltage and currents in a circuit element are given as $v = 141 \sin (314 t + 30^\circ)$ V and $i = 14.1 \sin (314 t - 60^\circ)$ A. Identify the element and find its value.

Solution

Since the angle associated with voltage is +ve while that for the current is -ve, hence the voltage leads the current. The angle of lead is $30 - (-60)$, i.e. 90° . Hence the element is an inductor.

$$X_L = \frac{V_m}{I_m} = \frac{141}{14.1} = 10 \Omega$$

or $\omega L = 10$, giving $L = \frac{10}{2\pi f} = \frac{10}{314} = 31.8 \text{ mH}$.

5.120. The voltage and current in an element are

$$v = 100 \sin(314 t - 20^\circ) \text{ V}$$

$$i = 10 \sin(314 t - 20^\circ) \text{ A}.$$

Identify the element and find its values.

Solution

It may be observed that the voltage and current are in same phase. Thus the element is a resistor.

$$R = \frac{V_m}{I_m} = \frac{100}{10} = 10 \Omega.$$

5.121. The voltage and current in a circuit element are $v = 100 \cos(314 t - 80^\circ) \text{ V}$ and $i = 100 \cos(314 t + 10^\circ) \text{ A}$. Identify the element and find its value.

Solution

It may be observed that the current leads the voltage (angle associated with current is +ve while that associated with voltage is -ve).

The angle of lead for the current is $10 - (-80^\circ) = 90^\circ$.

Thus the element is a capacitor.

$$X_C = \frac{V_m}{I_m} = \frac{100}{100} = 1 \Omega = \frac{1}{\omega C}$$

$$\therefore C = \frac{1}{314 \times 1} = 3184.7 \mu\text{F}.$$

5.122. What is the reactance of a $10 \mu\text{F}$ capacitor at $f = 0 \text{ Hz}$ (dc) and $f = 50 \text{ Hz}$?

Solution

At dc, $X_C = \frac{1}{2\pi \times 0 \times 10 \times 10^{-6}} = (\text{infinite}) \Omega$ i.e. across a dc voltage, the capacitor would act as an open circuit at steady state.

When $f = 50 \text{ Hz}$,

$$X_C = \frac{1}{2\pi \times 50 \times 10 \times 10^{-6}} = 318.47 \Omega.$$

[If the element is an inductor, the reactance X_L at $f = 0 \text{ Hz}$ would have been $X_L = 2\pi \times 0 \times L = 0 \Omega$, indicating that the inductor acts as a short circuit across a dc voltage at steady state.]

5.123. At what frequency will a $100 \mu\text{F}$ capacitor offer a reactance of 100Ω ?

Solution

$$X_C = \frac{1}{\omega C}$$

$$\therefore \omega = \frac{1}{X_C \times C} = \frac{1}{100 \times 100 \times 10^{-6}} = 100 \text{ rad/sec}.$$

$$\therefore f = \frac{100}{2\pi} = 15.9 \text{ Hz.}$$

At 15.9 Hz, the given capacitor will offer a reactance of 100 Ω

5.124 An inductor draws a current $i = I_m \sin \omega t$. Obtain the expression of instantaneous voltage across it.

Solution

$v_L = L \frac{di}{dt}$; (v) being the voltage developed across the inductor opposing the supply voltage.

$$\begin{aligned} \text{Here, } v_L &= L \cdot \frac{d}{dt} (I_m \sin \omega t) \\ &= \omega L I_m \cos \omega t = V_m \cos \omega t \\ &= V_m \sin (\omega t + 90^\circ). \end{aligned}$$

\therefore If (v) be the applied voltage

$$v = V_m \sin (\omega t - 90^\circ)$$

$$i = I_m \sin \omega t$$

$$v_L = V_m \sin (\omega t + 90^\circ).$$

$[(v_L)]$ is in direct opposition to v as phase angle between (v) and (v_L), is 180°

5.125 In an ac circuit

$$v = 200 \sin 314 t \text{ V}$$

$$i = 20 \sin (314 t - 30^\circ)$$

Determine (a) the power factor

(b) True or active power

(c) Apparent or total power

(d) Reactive power.

Solution

The phase angle ϕ between the voltage and current is 30° while the current lags the voltage.

$$\text{Here, } V_{\text{rms}} (=V) = \frac{200}{\sqrt{2}} = 141.44 \text{ V.}$$

$$I_{\text{rms}} (=I) = \frac{20}{\sqrt{2}} = 14.14 \text{ A.}$$

$$\begin{aligned} \therefore \text{ True power} &= V_{\text{rms}} \times I_{\text{rms}} \times \cos \phi \text{ [} \cos \phi \text{ being the power factor]} \\ &= 141.44 \times 14.14 \times \cos 30^\circ \\ &= 1732 \text{ W.} \end{aligned}$$

Hence we have observed that p.f. of the circuit is 0.866 while the true or active power consumed is 1732 W. The apparent (or total power) being given by ($V \times I$), we find that its value in the given problem is (141.44×14.14), i.e. 2000 VA (2 kVA). The reactive power is obtained as $VI \sin \phi$, i.e. $141.44 \times 14.14 \times \sin 30^\circ$ or 1 kVAR (app).

5.126 AC voltage of $79\angle 71.50^\circ$ V is applied across a load which draws $2.83\angle 45^\circ$ A. Find the value of active power.

Solution

$$\begin{aligned} P &= \text{Re } [VI^*] = \text{Re } [(25 + j75)(2 - j2)] \\ &= 200 \text{ W} \end{aligned}$$

$$[\because 79\angle 71.50^\circ = 25 + j75]$$

and $2.83\angle 45^\circ = 2 + j2$

while $(2.83\angle 45^\circ)^* = 2 - j2$

Also to have a check we see

$$\begin{aligned} P &= VI \cos \phi \\ &= 79 \times 2.83 \times \cos(71.5^\circ - 45^\circ) \\ &= 200 \text{ W.} \end{aligned}$$

5.127. An inductive coil consumes active power of 500 W and draws 10 A from a 60 Hz AC supply of 110 V. Obtain the values of resistance and inductance of the coil.

Solution

$$\therefore I^2 R = 500 \text{ W; } I = 10 \text{ A}$$

we find $R = 500/10^2 = 5 \Omega$.

However, $Z = \frac{V}{I} = \frac{110}{10} = 11 \Omega$

$$\therefore Z = \sqrt{R^2 + (\omega L)^2}.$$

Here $(\omega L)^2 = (11)^2 - (5)^2 = 96$

$$\therefore L = \frac{\sqrt{96}}{\omega} = \frac{\sqrt{96}}{2 \times \pi \times 60} = 26 \text{ mH.}$$

Thus, the given coil has 5 Ω resistance and 26 mH inductance.

5.128. In the given circuit currents through r_1 and C are equal in magnitude. If power consumed by the circuit is 12 kW, calculate the values of r_1 , r_2 and C . Assume current through the circuit as $5\angle 45^\circ$ A.

Solution

$$Z_{x-y} = \frac{r_1 \times (-jX_C)}{r_1 - jX_C} = \frac{-jr_1^2}{r_1 - jr_1}$$

\therefore Currents in r_1 and C are equal hence R_1 must be equal to $|X_C|$

$$\begin{aligned} \text{i.e. } Z_{x-y} &= \frac{-jr_1^2(r_1 + jr_1)}{r_1^2 + r_1^2} = \frac{r_1^3 - jr_1^3}{r_1^2} \\ &= \frac{r_1 - jr_1}{2} = \frac{r_1}{\sqrt{2}} \angle -45^\circ \Omega. \end{aligned}$$

$$\therefore V_{x-y} = IZ_{x-y}$$

or $I = \frac{V_{x-y}}{Z_{x-y}}$

$$\text{or } 5\angle 45^\circ = \frac{100\angle 0^\circ}{\frac{r_1}{\sqrt{2}} \angle -45^\circ} = \frac{100\sqrt{2}}{r_1 \angle -45^\circ}$$

$$\therefore r_1 = 100\sqrt{2} \Omega$$

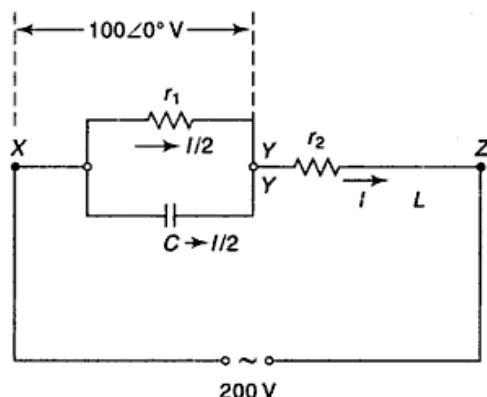


Fig. 5.75 Circuit diagram for Ex. 5.128

given that $P = 12 \text{ kW}$

i.e. $I^2(r_1 + r_2) = 12000$

$$\therefore r_1 + r_2 = \frac{12000}{25} = 480 \Omega$$

$$\therefore r_2 = 400 - 100\sqrt{2} = 259 \Omega$$

Also we have seen, $r_1 = X_C$

$$\therefore X_C = 100\sqrt{2} = 141 \Omega$$

$$\text{or } \frac{1}{2\pi f C} = 141$$

$$C = \frac{1}{2\pi \times 50 \times 141} = 22.6 \mu\text{F}$$

$$\therefore r_1 = 141 \Omega; r_2 = 259 \Omega$$

$$C = 22.6 \mu\text{F}.$$

.....


5.129. Calculate the real and reactive power to each load and the total complex power provided by the source (Fig. 5.76)

Solution

$$I_R = \frac{V}{R} = \frac{120 \angle 0^\circ}{40} = 3 \angle 0^\circ \text{ A}$$

$$I_L = \frac{V}{X_L} = \frac{120 \angle 0^\circ}{j60} = 2 \angle -90^\circ \text{ A}$$
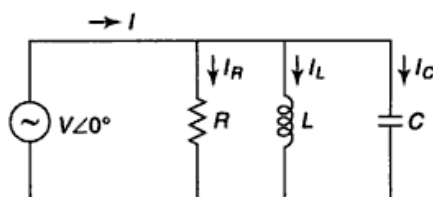
$$I_C = \frac{V}{X_C} = \frac{120 \angle 0^\circ}{-j80} = 1.5 \angle 90^\circ \text{ A}.$$



$$R = 40 \Omega; X_L = j60 \Omega$$

$$X_C = -j80 \Omega; V = 120 \text{ V}$$

Fig. 5.76 Circuit diagram for Ex. 5.129

$$\therefore \text{total current } (I) = I_R + I_L + I_C \text{ (vector sum)}$$

$$= 3 \angle 0^\circ + 2 \angle -90^\circ + 1.5 \angle 90^\circ$$

$$= 3 - j0.5 = 3.041 \angle -9.46^\circ \text{ A}.$$

Active power in R being given by P , we find

$$P = V \times I_R = 120 \times 3 = 360 \text{ W}$$

$$P = I_R^2 \times R = 3^2 \times 40 = 360 \text{ W}$$

$$P = \frac{V^2}{R} = \frac{(120)^2}{40} = 360 \text{ W}.$$

Since $\phi = 0$ in the expression of current I_R i.e., as I_R and V are in phase, hence reactive power consumed in R is zero.

Again for L and C elements, ϕ is either -90° or $+90^\circ$, i.e. $\cos \phi = 0$ in both the cases. Hence reactive power consumption by L or C element is zero.

Reactive power for L is obtained as

$$Q_L = V \times I_L = 120 \times 2 = 240 \text{ VAR}$$

$$Q_L = I_L^2 X_L = 2^2 \times 60 = 240 \text{ VAR}$$

$$Q_L = \frac{V^2}{X_L} = \frac{120^2}{60} = 240 \text{ VAR}.$$

Reactive power for C element is obtained as

$$Q_C = V \times I_C = 120 \times 1.5 = 180 \text{ VAR}$$

$$Q_C = I_C^2 \times X_C = (1.5)^2 \times 80 = 180 \text{ VAR}$$

$$Q_C = (V^2/X_C) = 120^2/80 = 180 \text{ VAR}.$$

For total complex power we can write

$$S = P + j(Q_L - Q_C).$$

[Q_L is +ve in inductive circuit while Q_C is negative for capacitive circuit]

$$= 360 + j(240 - 180) = (360 + j60) \text{ VA}$$

$$\begin{aligned} \text{[Also, } S &= VI^* = 120\angle 0^\circ \times 3.041\angle -9.46^\circ \\ &= 364.9\angle -9.46^\circ \text{ VA} = 360 + j60 \text{ VA.}] \end{aligned}$$

The real power provided by the source is 360 W. The reactive power provided by the source is 60 VAR (inductive circuit requirement is actually 240 VAR but capacitor generates 180 VAR hence net requirement is only 60 VAR).

5.130 A resistor and a capacitor are connected in series across a 150 V AC 40 Hz supply. The current in the circuit is measured as 5 A. If the frequency of the supply be raised to 50 Hz, the current becomes 6 A. Find the values of the resistance and capacitance.

Solution

When $V = 150 \text{ V}$, $f_1 = 40 \text{ Hz}$, $I_1 = 5 \text{ A}$

$$\therefore Z_1 = \frac{V}{I_1} = \frac{150}{5} = 30 \Omega.$$

[Z_1 is the circuit impedance of the RC series circuit at 40 Hz supply frequency.]

When $V = 150 \text{ V}$, $f_2 = 50 \text{ Hz}$, $I_2 = 6 \text{ A}$.

$$\therefore Z_2 = \frac{V}{I_2} = \frac{150}{6} = 25 \Omega.$$

[Z_2 is the circuit impedance of the same RC series circuit at 50 Hz supply frequency.]

\therefore In a series RC circuit,

$$Z = \sqrt{R^2 + (1/2\pi \times f \times C)^2},$$

for the first case we can write

$$\sqrt{R^2 + \left(\frac{1}{2\pi \times 40 \times C}\right)^2} = 30$$

and in the second case we can write

$$\sqrt{R^2 + \left(\frac{1}{2\pi \times 50 \times C}\right)^2} = 25.$$

Solving these two equations for two unknown R and C , we get

$$R = 30 \text{ ohm and } C = 492 \mu\text{F}.$$

5.131 For the circuit shown in Fig. 5.77, find the value of C such that the input current is 45° out of phase with the input voltage. Assume $\omega = 2 \times 10^3 \text{ rad/sec}$.

Solution

For the input current to be 45° out of phase with the input voltage, the net reactance of the parallel portion of LC circuit must be $\pm 20 \Omega$.

$$\text{i.e. } \pm \frac{j}{20} = -\frac{j}{\omega L} + j\omega C$$

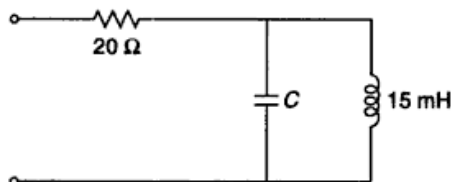


Fig. 5.77 Circuit diagram for Ex. 5.131

or

$$C = \frac{1}{\omega} \left(\frac{1}{\omega L} \pm \frac{1}{20} \right)$$

$$= \frac{1}{2000} \left(\frac{1}{2000 \times 15 \times 10^{-3}} \pm \frac{1}{20} \right)$$

$$= (\text{neglecting -ve value})$$

The feasible value is $C = 41.67 \times 10^{-6} \mu\text{F}$.

5.132 Given, $I = 11.81 \angle -7.12^\circ$

$$R_1 = 10 \Omega$$

$$R_2 = 15 \Omega$$

$$X_C = -j15 \Omega$$

$$V = 220 \angle 0^\circ.$$

Obtain the reactance offered by the inductance L at 50 Hz in Fig. 5.78.

Solution

Current through $(R_2 - C)$ circuit is given by

$$I_{R-C} = \frac{V}{Z_{ac}} = \frac{220 \angle 0^\circ}{15 - j15} = \frac{220 \angle 0^\circ}{21.2 \angle -45^\circ}$$

$$= 10.35 \angle 45^\circ = (7.34 + j7.34) \text{ A.}$$

\therefore Current through $R - L$ circuit is

$$I_{R-L} = I - I_{R-C}$$

$$= 11.81 \angle -7.12^\circ - 10.35 \angle 45^\circ = 4.38 - j8.8$$

$$= 9.83 \angle -63.6^\circ \text{ A.}$$

However,
$$I_{R-L} = \frac{V}{Z_{R-L}} = \frac{220 \angle 0^\circ}{10 + jX_L}$$

or
$$(4.38 - j8.8) = \frac{220 + j.0}{10 + jX_L}.$$

$\therefore X_L = 20 \Omega.$

We can now find L as shown below;

$$X_L = \omega L = 20, \text{ where } (\omega) = 2\pi f = 314$$

$\therefore L = \frac{20}{314} = 63.7 \text{ mH.}$

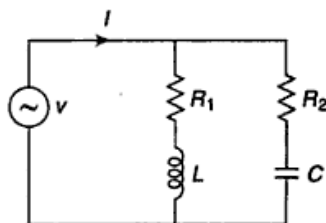


Fig. 5.78 Circuit diagram for Ex. 5.132

5.133 A choke coil having a resistance of 4Ω and inductance of 2 H is in parallel to a capacitor C . The supply voltage applied to this parallel combination is $(v) = 10 \cos 2t \text{ V}$.

(a) Obtain the current passing through the choke.

(b) Obtain the value of C such that the supply voltage V and the supply current I are in same phase.

Solution

Let us first draw the circuit as per given data (Fig. 5.79)

Here,
$$I_1 = \frac{(V_m / \sqrt{2})}{(4 + j4)} \text{ A.}$$

(\because for the choke coil, the impedance is $4 + j \times \omega \times L = 4 + j \times 2 \times 2 = 4 + j4 \Omega$)

$$\begin{aligned}
 \text{i.e. } I_1 &= \frac{10/\sqrt{2}}{4 + j4} = \frac{7.072\angle 0^\circ}{5.66\angle 45^\circ} = 1.25\angle -45^\circ \\
 &= (0.884 - j0.884) \text{ A.} \\
 I_2 &= \frac{10/\sqrt{2}}{1/j \times 2 \times C} \quad [\because X_C = (j \times \omega \times C)^{-1} \\
 &= (j \times 2 \times C)^{-1}] \\
 &= j \frac{20}{\sqrt{2}} \times C.
 \end{aligned}$$

For I to be in same phase with V , the imaginary parts of I_1 and I_2 must cancel each other;

$$\text{i.e., } j \frac{20}{\sqrt{2}} \times C = j 0.884$$

$$\therefore C = 0.0625 \text{ F.}$$

Then for $C = 0.0625 \text{ F}$, the input current will be in phase with input voltage.

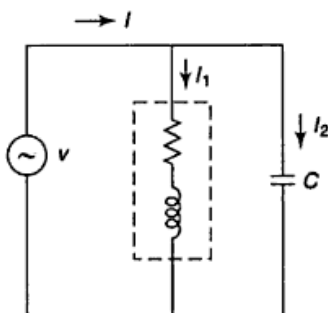


Fig. 5.79 Circuit diagram for Ex. 5.133

5.134. An inductive circuit takes 50 A of current at a power factor 0.8 (lag) from a 250 V, 50 Hz supply. Calculate the value of the capacitance that is required to be connected across the inductive circuit to make the power factor unity.

Solution

When the capacitor is in parallel to the inductive circuit, the net power factor would be unity provided the capacitor's capacitive current cancel the inductive current of the inductive circuit i.e., $I_C = I_L \sin \phi$ [I_C being the capacitor current while I_L the inductive circuit current; ϕ is the p.f. of the inductive circuit]

$$\text{or } I_C = 50 \times 0.6 = 30 \text{ A.}$$

Again, $I_C = \frac{V}{X_C}$, X_C being the capacitive reactance.

$$\therefore X_C = \frac{V}{I_C} = \frac{250}{30} = 8.33 \Omega.$$

$$\text{Also, } X_C = \frac{1}{2\pi f C}$$

$$\begin{aligned}
 \therefore C &= \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 8.33} \\
 &= 382.32 \mu\text{F.}
 \end{aligned}$$

.....

5.135. In the series circuit shown in Fig. 5.80 the source impedance is $(5 + j3) \Omega$ while the source frequency is 2 kHz. At what values of C the power in the 10Ω resistor will be maximum?

Solution

$$\begin{aligned}
 Z \text{ (total impedance of the circuit)} &= Z_{\text{source}} + Z_{\text{load}} \\
 &= (5 + j3) + (10 - jX_C) \Omega \\
 &= [15 + j(3 - X_C)] \Omega
 \end{aligned}$$

At resonance of any series circuit, the current is maximum. Hence to achieve flow of maximum power in the 10Ω resistor, we need to make this series circuit resonant. However, Z being the total impedance of the circuit, it will be purely resistive at resonance. So, the imaginary part of Z is zero, at resonance.

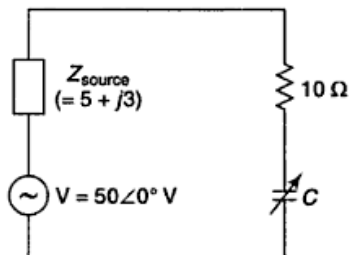


Fig. 5.80 Circuit diagram for Ex. 5.135

$$\text{i.e.} \quad (3 - X_C) = 0$$

$$\therefore X_C = 3$$

$$\text{Since} \quad f = 2 \text{ kHz} \quad \text{and} \quad \frac{1}{\omega C} (= X_C) = 3$$

$$\therefore \frac{1}{2\pi \times 2 \times 10^3 \times C} = 3$$

$$\therefore C = 26.54 \mu\text{F}$$

Thus at $C = 26.54 \mu\text{F}$, maximum power will flow in the 10Ω resistor.

5.136. Obtain the values of I_1 , I_2 and I for the circuit shown in Fig. 5.81.

Solution

$$Z_{L-R} = 2 + j10 = 10.2 \angle 78.7^\circ \Omega$$

$$Z_{R-C} = 7 - j5 = 8.6 \angle -35.6^\circ \Omega$$

Between terminals X-Y in the given circuit, Z_{L-R} and Z_{R-C} are in parallel.

$$\text{i.e.} \quad \frac{1}{Z_{X-Y}} = \frac{1}{Z_{L-R}} + \frac{1}{Z_{R-C}}$$

$$= \frac{1}{2 + j10} + \frac{1}{7 - j5}$$

$$= 0.0194 - j0.0960 + 0.0943 + j0.0695$$

$$= 0.1137 - j0.0285.$$

$$\therefore Z_{X-Y} = \frac{1}{0.1137 - j0.0285} = 8.54 \angle 14.5^\circ \Omega$$

$$= (8.27 + j2.08) \Omega.$$

Total impedance of the circuit is then given by

$$Z = Z_{8\Omega} + Z_{X-Y} = (16.27 + j2.08) \Omega$$

$$= 16.43 \angle 7.3^\circ.$$

$$\therefore I = \frac{V}{Z} = \frac{220 \angle 0^\circ}{16.43 \angle 7.3^\circ} = 18.4 \angle -7.3^\circ \text{ A}$$

$$V_{X-Y} = Z_{X-Y} \times I = 1142 \angle 6.8^\circ \text{ A}$$

$$I_1 = V_{X-Y} / Z_{L-R} = 11.2 \angle -71.9^\circ \text{ A}$$

$$I_2 = V_{X-Y} / Z_{R-C} = 13.3 \angle 42.4^\circ \text{ A}.$$

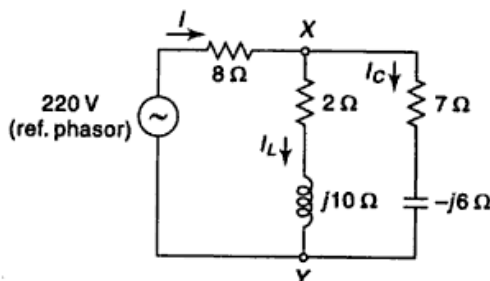


Fig. 5.81 Circuit diagram for Ex. 5.136

5.137. A resistance R_1 is in series with a choke coil having resistance R_2 and inductance L as shown in Fig. 5.82. The circuit current is given by $I = 3 \angle -37^\circ \text{ A}$, while the supply voltage is $V = 240 \angle 0^\circ$ volts. If the voltage drop across the choke is 171 volts, Find R_1 , R_2 and X_L .

Solution

$$|Z| = \frac{240}{3} = 80 \Omega = [(R_1 + R_2)^2 + (X_L)^2]^{1/2}$$

Since current lags source voltage by 37° , we find p.f. ($\cos \phi$) is $\cos 37^\circ = 0.798$.

$$\therefore (R_1 + R_2) = Z \cos \phi = 80 \times 0.798 = 63.7 \Omega$$

But we have obtained from above

$$80 = [(R_1 + R_2)^2 + (X_L)^2]^{1/2}$$

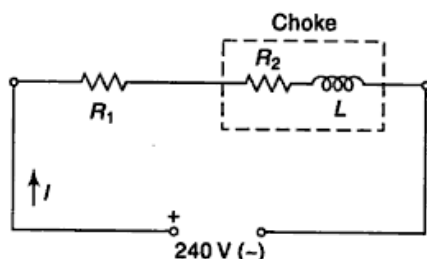


Fig. 5.82 Circuit diagram for Ex. 5.137

$$\therefore X_L = [(80)^2 - (R_1 + R_2)^2]^{1/2} = [(80)^2 - (63.7)^2]^{1/2} = 48.2 \Omega.$$

Again the impedance of the choke coil is given by

$$|Z_C| = \frac{\text{Drop across the choke}}{\text{Current through the choke}} = \frac{171}{3} = 57 \Omega.$$

However, for the choke, $R_2^2 + X_L^2 = Z_C^2$.

$$\therefore \text{we find } R_2^2 = Z_C^2 - X_L^2 = (57^2 - 48.2^2) \text{ or, } R_2 = 30.4 \Omega.$$

But $(R_1 + R_2) = 63.7 \Omega$ (as obtained earlier)

$$\therefore R_1 = (63.7 - R_2) = 63.7 - 30.4 = 33.3 \Omega$$

.....

5.138 A 0.5 HP induction motor operates at an efficiency of 89%. If the operating p.f. is 0.8 lag, find the reactive power taken by the motor.

Solution

$$0.5 \text{ HP} = 0.5 \times 746 = 373 \text{ W} = P_{\text{out}}$$

$$\therefore P_{\text{input}} = \frac{P_{\text{out}}}{\eta}; \eta \text{ being efficiency (89\%)}$$

$$\text{Here, } P_{\text{input}} = \frac{373}{0.89} = 419.10 \text{ W}$$

Since $\text{PF} = 0.8 (= \cos \phi)$,

hence, $\sin \phi = 0.6$ (reactive power factor).

$$\begin{aligned} \text{Here, } Q_{\text{in}} &= VI \sin \phi = \frac{P_{\text{in}}}{\cos \phi} \sin \phi \\ &\left[\because P = VI \cos \phi \text{ hence } VI = \frac{P}{\cos \phi} \right] \\ &= \frac{419.10}{0.8} \times 0.6 = 314.325 \text{ VAR.} \end{aligned}$$

\therefore Reactive power taken by the motor is 314.325 VAR.

5.139 Determine R_1 and R_2 which would make the circuit (Fig. 5.83) resonant for all frequencies.

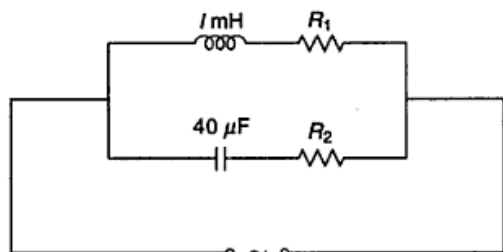


Fig. 5.83 Circuit diagram for Ex. 5.139

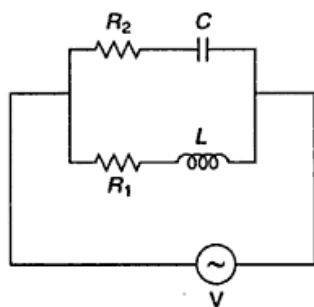


Fig. 5.83(a) General parallel circuit diagram for Ex. 5.139

Solution

Let us assume a general parallel circuit as shown in Fig. 5.83(a).

The total admittance of the parallel branch is $y = y_1 + y_2$, where y_1 is the admittance for $(L - R_1)$ branch and y_2 is the admittance for the $(R_2 - C)$ branch.

$$\begin{aligned} \therefore y &= \frac{1}{R_1 + jX_L} + \frac{1}{R_2 - jX_C} \\ &= \left(\frac{R_1}{R_1^2 + X_L^2} + \frac{R_2}{R_2^2 + X_C^2} \right) + j \left(\frac{X_C}{R_2^2 + X_C^2} - \frac{X_L}{R_1^2 + X_L^2} \right). \end{aligned}$$

The circuit will be at resonance when the imaginary parts of the capacitive and inductive admittances are equal.

This gives
$$\frac{X_C}{R_2^2 + X_C^2} = \frac{X_L}{R_1^2 + X_L^2}$$

or
$$X_2(R_1^2 + X_L^2) = X_L \left(R_2^2 + \frac{1}{\omega^2 C^2} \right).$$

Now, if $R_1^2 = R_2^2 = \frac{L}{C}$, then we find

$$\frac{1}{\omega C} \left(\frac{L}{C} + \omega^2 L^2 \right) = \omega L \left(\frac{L}{C} + \frac{1}{\omega^2 C^2} \right)$$

or
$$\frac{L}{\omega C^2} + \frac{\omega L^2}{C} = \frac{\omega L^2}{C} + \frac{L}{\omega C^2}$$

\therefore L.H.S = R.H.S for any value of ω provided.

This indicates that the circuit will be in resonance for all frequencies provided $R_1^2 = R_2^2 = \frac{L}{C}$.

Then, for the given problem, $R_1 = R_2 = \sqrt{\frac{L}{C}} = \sqrt{\frac{1 \times 10^{-3}}{40 \times 10^{-6}}} = 5 \Omega$.

Hence for $R_1 = R_2 = 5 \Omega$, the given circuit is always resonant.

5.140. A current of $8.59 \angle 26.56^\circ$ passes through a circuit having series connection of two elements. The voltage drop across element 1 is $v_1 = 80 \sin \omega t$ while that across element 2 is $v_2 = 40 \sin (\omega t - 35^\circ)$ V. Find the complex power in the circuit.

Solution

$$v_1 = 80 \sin \omega t$$

$$\begin{aligned} \therefore V_1(\text{rms}) &= \frac{80}{\sqrt{2}} \angle 0^\circ = 56.57 \angle 0^\circ \\ &= (56.57 + j0) \text{ V.} \end{aligned}$$

Also, $v_2 = 40 \sin (\omega t - 35^\circ)$

$$\therefore V_2 = \frac{40}{\sqrt{2}} \angle -35^\circ = (23.17 - j16.22) \text{ V.}$$

$$\begin{aligned} \therefore V_1 + V_2 \text{ (phasor sum)} &= (56.57 + j0 + 23.17 - j16.22) \text{ V} \\ &= (79.74 - j16.22) \text{ V} = 81.37 \angle -11.49^\circ \text{ V.} \end{aligned}$$

Since the current is $I = 8.95 \angle 26.56^\circ$, hence we can write,

Complex power $S = VI^*$

$$\begin{aligned} &= 81.37 \angle -11.49^\circ \times (8.95 \angle 26.56^\circ)^* \\ &= 81.37 \angle -11.49^\circ \times 8.95 \angle -26.56^\circ \\ &= 727.78 \angle -38^\circ \text{ VA} = (572.71 - j449.10) \text{ VA.} \end{aligned}$$

.....

5.141. A circuit consists of resistance of $35\ \Omega$ in series with an unknown coil impedance Z . For a sinusoidal current of 2 A , the observed voltages are 200 V across R and Z together and 150 V across the impedance Z . Find the value of the impedance. Draw the phasor diagram.

Solution

$$V_R = 35 \times 2 = 70\text{ V} \quad [\because R = 35\ \Omega, I = 2\text{ A}]$$

$$V_Z = 150\text{ V (given)}$$

$$\therefore Z = \frac{150}{2} = 75\ \Omega.$$

In the phasor diagram, Fig. 5.84 V is the reference phasor, I the lagging current while V_R and V_Z are the drops across R and the coil impedance Z respectively. As per the given and obtained data, $|V_R| = 70\text{ V}$, $|V_Z| = 150\text{ V}$ while $|V| = 200\text{ V}$.

If ϕ be the angle of lag for the current (and thus for V_R), we can write in $\triangle Oab$,

$$V^2 = V_R^2 + V_Z^2 + 2V_R V_Z \cos \phi$$

$$\text{or} \quad (200)^2 = (70)^2 + (150)^2 + 2 \times 70 \times 150 \times \cos \phi.$$

$$\therefore \cos \phi = 0.6.$$

In the coil let us assume the resistance is r while the inductance is l so that $(Z) = r + j\omega l$.

Since the power factor is 0.6 , hence $\sin \phi = 0.8$.

$$\therefore \frac{X_L}{Z} = 0.8,$$

while x_L is the inductive reactance of the coil.

$$\text{Here, } x_L = 0.8 \times 75 = 60\ \Omega$$

$$\text{and } \left(\frac{R+r}{Z} \right) = 0.6$$

$$\text{or } (R+r) = 0.6 \times 75 = 45\ \Omega$$

$$\text{or } r = 45 - 35 = 10\ \Omega.$$

Then the coil has a $10\ \Omega$ resistance and $60\ \Omega$ inductive reactance [the value of the impedance being $(10 + j45)\ \Omega$].

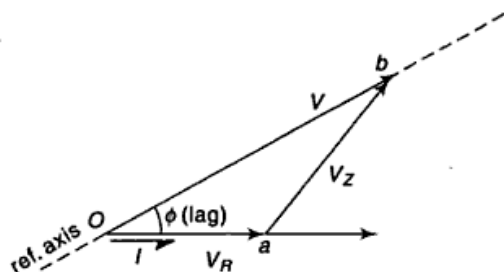


Fig. 5.84 Phasor diagram for Ex. 5.141

■ EXERCISES ■

1. Explain with the help of a diagram how alternating current is generated.
2. Define the following:
 - (a) Amplitude of an alternating quantity
 - (b) Instantaneous value of an alternating quantity
 - (c) Frequency
 - (d) Phase
 - (e) Phase difference
 - (f) Time period
3. Define rms and average value of an alternating quantity. Explain how these value can be obtained.
4. Define form factor and peak factor of an alternating quantity.
5. Explain with the help of diagrams what you understand by in phase, lagging and leading as applied to sinusoidal quantities.

6. Define power factor as applied to ac circuits. What do you mean by active power, reactive power and apparent power?
7. Explain the meaning of the following terms in connection with alternating current:

(a) inductance	(b) capacitance	(c) reactance
(d) impedance	(e) admittance	(f) susceptance
(g) conductance.		
8. Show that power consumed in a purely inductive circuit and purely capacitive circuit is zero when sinusoidal voltage is applied across it.
9. Explain with the help of a diagram the phenomenon of resonance in series R - L - C circuit.
10. Derive an expression for the resonant frequency of a parallel circuit, one branch consisting of a coil of inductance L and resistance R and the other branch of capacitance C .
11. Derive the quality factor of a series R - L - C circuit at resonance.
12. Define quality factor in a series R - L - C circuit. Determine the half power frequencies in terms of quality factor and the resonant frequency for series R - L - C circuit.
13. Why is a series resonant circuit called an acceptor circuit and parallel resonant circuit a rejector circuit?
14. Explain dynamic impedance in connection with parallel resonant circuit.
15. Define bandwidth in a series R - L - C circuit. Prove that in a series R - L - C

$$\text{circuit } (Q_0) = \frac{\omega_o L}{R} = \frac{f_o}{\text{Bandwidth}}$$

16. Find the average value, rms value, form factor and peak factor of the waveform shown in Fig. 5.85

[Ans: 15 A, 17.8 A, 1.187, 1.685]

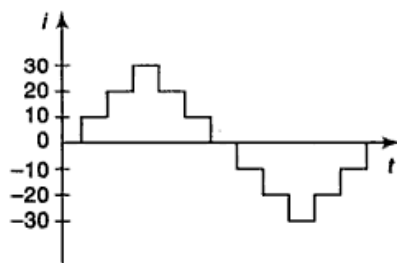


Fig. 5.85 Waveform for Ex. 5.16

17. The maximum value of a sinusoidally alternating voltage is 100 volts. Find the instantaneous value at $\frac{1}{9}$ cycle and $\frac{1}{18}$ cycle. [Ans: 64.28 V, 34.2 V]
18. The voltage given by $(v_1) = 50 \sin (377t - 30^\circ)$ and $(v_2) = 20 \sin (377t + 45^\circ)$ act in the series circuit. Determine the frequency and rms value of the resultant voltage.
19. Define phasors as used in the study of ac circuits. Use phasors to find the sum of the sinusoids $40 \sin 314t$ and $30 \cos \left(314t - \frac{\pi}{4} \right)$.

[Ans: $64.78 \sin (314t + 19.11^\circ)$]

[Hint: $a = 40 \sin 314t$

$$b = 30 \cos \left(\frac{\pi}{4} - 314t \right)$$

$$= 30 \sin \left(\frac{\pi}{2} - \frac{\pi}{4} + 314t \right)$$

$$= 30 \sin \left(314t + \frac{\pi}{4} \right)$$

Using the method described in Art 5.3.3, we get the required sum is $64.78 \sin(314t + 19.11^\circ)$.

20. The equation of an alternating current is $i = 62.35 \sin 323t$ A.

Determine its

- (a) maximum value (b) frequency (c) r.m.s. value
(d) average value and (e) form factor

$$[\text{Ans: } I_{\max} = 62.35 \text{ A; } f = 51.41 \text{ Hz; } I_{\text{rms}} = 44.1 \text{ A; } I_{\text{av}} = 39.69 \text{ A, FF} = 1.11]$$

[Hint:

- (i) Maximum value 62.35 A

(ii) Frequency $= \frac{323}{2\pi} \text{ Hz} = 51.41 \text{ Hz}$

(iii) r.m.s. value $= \frac{62.35}{\sqrt{2}} = 44.1 \text{ A}$

(iv) Average value $= \frac{62.35}{\frac{\pi}{2}} = 39.69 \text{ A}$

(v) Form factor $= \frac{\text{r.m.s. value}}{\text{average value}} = \frac{44.1}{39.69} = 1.11]$

21. An ac series circuit consisting of a pure resistance of 25Ω , inductance of 0.15 H and capacitance of $80 \mu\text{F}$ is supplied from a 230 V , 50 Hz ac source.

- (a) Find the impedance of the circuit, the current, the power drawn by the circuit and the power factor.

- (b) Draw the phasor diagram. $[\text{Ans: } Z = 26.04/16.25^\circ \Omega \text{ } |I| = 8.83 \text{ A; } P = 1950.2 \text{ W; } \cos \phi = 0.96 \text{ (lag)}]$

$$[\text{Hint: (a) } Z = 25 + j 100\pi \times 0.15 - j \frac{1}{100\pi \times 80 \times 10^{-6}}]$$

$$= 25 + j 7.29 = 26.04 \angle 16.25^\circ \Omega$$

$$I = \frac{230}{26.04} \text{ A} = 8.832 \text{ A.}$$

Power factor $\cos \theta = \cos 16.25^\circ = 0.96$ lagging

Power $= 230 \times 8.832 \times 0.96 = 1950.2 \text{ W}$

22. Figure 5.86 shows a circuit in which a coil having resistance R and inductance L is connected in series with a resistance of 80Ω . The combination is fed from a sinusoidal source.

The following measurements (rms value) are taken at 50 Hz . When the circuit is in steady state.

$$|V_S| = 145 \text{ V, } |V_R| = 50 \text{ V}$$

and $|V_C| = 110 \text{ V}$

Find the value of R and L .

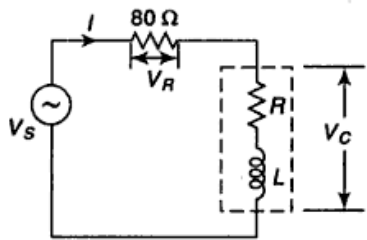


Fig. 5.86

$$[\text{Ans: } R = 102.8 \Omega; L = 45.5 \text{ mH}]$$

[Hint: $I = \frac{50}{80} \text{ A} = \frac{5}{8} \text{ A}$

$$Z^2 = R^2 + X_L^2 = \left(\frac{110}{\frac{5}{8}}\right)^2 = (176)^2 \quad (i)$$

$$\text{Again } \left(\frac{145}{\frac{5}{8}}\right)^2 = (80 + R)^2 + X_L^2 \quad (ii)$$

Solving (i) and (ii)

$$R = 102.8 \, \Omega \text{ and } X_L = 142.857 \text{ or } L = \frac{142.857}{2\pi \times 50} \text{ H} = 0.455 \text{ H}.$$

23. A coil of resistance $10 \, \Omega$ and inductance 0.02 H is connected in series with another coil of resistance $6 \, \Omega$ and inductance 15 mH across a 230 V , 50 Hz supply. Calculate (i) impedance of the circuit, (ii) voltage drop across each coil, (iii) the total power consumed by the circuit.

$$[\text{Ans: } Z = 19.41 \angle 34.48^\circ \, \Omega; V_{\text{drop}(1)} = 19139.92 \angle -2.35^\circ; \\ V_{\text{drop}(2)} = 90.38 \angle 3.65^\circ \text{ V}; P = 2.25 \text{ kW}]$$

[Hints: (i) Impedance $= 10 + j2\pi \times 50 \times 0.02 + 6 + j2\pi \times 50 \times 0.015$

$$= 10 + j6.28 + 6 + j4.71 = 16 + j10.99 \\ = 19.41 \angle 34.48^\circ \, \Omega.$$

(ii) Voltage across the 1st coil

$$(10 + j6.28) \times \frac{230}{19.41 \angle 34.48^\circ} = 139.92 \angle -2.35^\circ \text{ V}$$

Voltage across the 2nd coil is

$$(6 + j4.71) \times \frac{230}{19.41 \angle 34.48^\circ} = 90.38 \angle 3.65^\circ \text{ V}$$

$$(iii) \text{ Total power} = \left(\frac{230}{19.41}\right)^2 \times 16 = 2246.6 \text{ W}]$$

24. A circuit consists of three parallel branches. The branch currents are represented by $i_1 = 10 \sin \omega t$ and $i_2 = 20 \sin (\omega t + 60^\circ)$. If the supply frequency is 50 Hz . Calculate the resultant current at $t = 0$ and at $t = 1 \text{ ms}$.

$$[\text{Ans: } 13.55 \text{ A and } 22.33 \text{ A}]$$

25. A 100 V , 80 W lamp is to be operated on a 240 V , 50 Hz supply. Calculate the value of (a) non-inductive resistor, (b) pure inductor to be connected in series with the lamp so that it can be used at its rated voltage.

$$[\text{Ans: } 175 \, \Omega, 0.868 \text{ H}]$$

26. A resistance of $12 \, \Omega$ and inductance of 0.15 H and a capacitance of $130 \, \mu\text{F}$ are connected in series across a 100 V , 50 Hz supply. Determine the impedance, current and power factor of the circuit.

$$[\text{Ans: } 25.6 \, \Omega, 3.9 \text{ A}, 0.4687 \text{ lag}]$$

27. A coil takes a current of 10 A when connected to a dc supply of 100 V . When connected to an ac supply of 100 V , the current is 5 A . Find the reactance of the coil.

$$[\text{Ans: } 17.32 \, \Omega]$$

28. The voltage across a circuit is given by $(300 + j60) \text{ V}$ and the current through it is $(10 - j5) \text{ A}$. Determine the (i) active power, (ii) reactive power and (iii) apparent power.

$$[\text{Ans: (i) } 2.7 \text{ kW, (ii) } 2.1 \text{ KVAR (lagging) and (iii) } 3.42 \text{ kVA}]$$

29. A coil of resistance $15\ \Omega$ and reactance $25\ \Omega$ is connected in parallel with a capacitor of reactance $10\ \Omega$ and series resistance of $12\ \Omega$ to a 100 V , 50 Hz supply. Determine the supply current and the circuit phase angle.

[Ans: 6.782 A and 9.82°]

30. Three impedances $(4 - j6)$, $(6 + j8)$ and $(5 - j3)\ \Omega$ are connected in parallel. Calculate the current in each branch when the total supply current is 20 A .

[Ans: $8.96\angle 32.79^\circ$, $6.46\angle -76.65^\circ$, $11.08\angle 7.44^\circ$]

31. Determine the total current, power factor and power consumed by the circuit shown in Fig. 5.87.

[Ans: $30.03\angle 123.5^\circ\text{ A}$, 0.552 lead, 1657.4 W]

32. Find the current through each element in the circuit shown in Fig. 5.88.

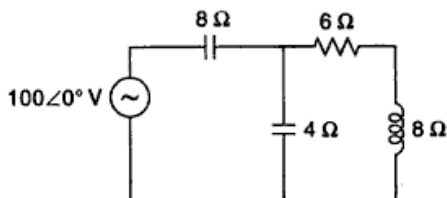


Fig. 5.87 Circuit diagram for Ex. 5.26

[Ans: $I_1 = 10.23\angle -67.3^\circ$, $I_2 = 3.93\angle 53.14^\circ$, $I_3 = 8.91\angle -44.96^\circ$]

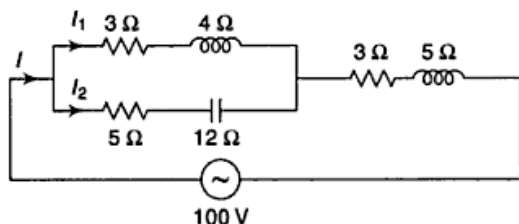


Fig. 5.88 Circuit diagram for Ex. 5.27

33. A resistor and a capacitor are connected in series with a variable inductor. When the circuit is connected to a 240 V , 50 Hz supply the maximum current obtained by varying the inductance is 0.5 A . At this the voltage across the capacitor is 250 V . Determine the values of resistance, capacitance and inductance.

[Ans: $480\ \Omega$, $6.36\ \mu\text{F}$, 1.59 H]

34. A coil of $20\ \Omega$ resistance has an inductance of 0.2 H and is connected in parallel with a $100\ \mu\text{F}$ capacitor. Calculate the frequency at which the circuit will act as a non-inductive resistance of $R\ \Omega$. Find also the value of R .

[Ans: 31.8 Hz , $100\ \Omega$]

35. A series circuit consists of a resistance of $10\ \Omega$, an inductance of 8 mH and a capacitance of $500\ \mu\text{F}$. A sinusoidal emf of constant amplitude 5 V with variable frequency is applied. At what frequencies will the current be (i) maximum (ii) half the maximum?

[Ans: (i) 79.6 kHz , (ii) 79.872 kHz and 79.528 kHz .]

36. A coil of inductance 9 H and resistance $50\ \Omega$ in series with a capacitor is supplied at constant voltage from a variable frequency source. If the maximum current of 1 A occurs at 75 Hz , find the frequency when the current is 0.5 A .

[Ans: 75.75 Hz]



AC NETWORK ANALYSIS

6.1 SUPERPOSITION THEOREM (AC APPLICATION)

Just like the dc application, superposition theorem applied to linear ac networks eliminates the need for solving simultaneous linear equations considering the effects of each source independently. The only variation in applying the principle of superposition to the ac networks with independent source is that the circuit will have to be worked out with ac voltage or current sources and impedances involving phasors (i.e. operation with complex numbers) instead of just real numbers (i.e. operation with resistors).

The statement of superposition theorem for ac network is as follows:

If a number of voltage or current sources act simultaneously in a linear network, the resultant current (or voltage) in any branch is the phasor sum of the currents or (voltages) that would be produced in it, when each source acts alone replacing all other independent sources by their internal impedances.

6.1 Find the current through inductive reactance ($j2 \Omega$) in the circuit of Fig. 6.1 using the superposition theorem.

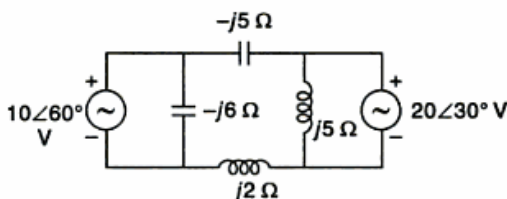


Fig. 6.1 Circuit of Ex.6.1

Solution

Considering $10\angle 60^\circ$ V source acting alone in the circuit and removing the other source as shown in Fig. 6.1(a), the current through the ($j2 \Omega$) reactor is

$$I_1 = \frac{10 \angle 60^\circ}{-j5 + j2} = \frac{10 \angle 60^\circ}{-j3}$$

$$= 3.33 \angle 150^\circ \text{ A (from B to A).}$$

Considering the $20 \angle 30^\circ \text{ V}$ source acting alone in the circuit and removing the other source as shown in Fig. 6.1(b), the current through ($j2 \Omega$) reactor is

$$I_2 = \frac{20 \angle 30^\circ}{-j5 + j2} = \frac{20 \angle 30^\circ}{-j3}$$

$$= 6.66 \angle 120^\circ \text{ A (from A to B).}$$

According to the superposition theorem, when both the sources are acting simultaneously the current through the ($j2 \Omega$) inductive reactance is

$$3.33 \angle 150^\circ - 6.67 \angle 120^\circ$$

$$= 0.455 - j 4.11$$

$$= 4.126 \angle -83.72^\circ$$

$$\text{A (from B to A).}$$

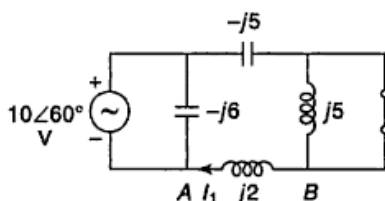


Fig. 6.1(a) $10 \angle 60^\circ \text{ V}$ source acting alone

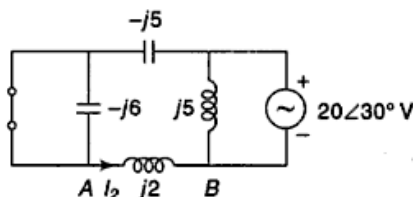


Fig. 6.1(b) $20 \angle 30^\circ \text{ V}$ source acting alone

6.2 Using the superposition theorem find the current flowing in the branch AB of the circuit shown in Fig. 6.2.

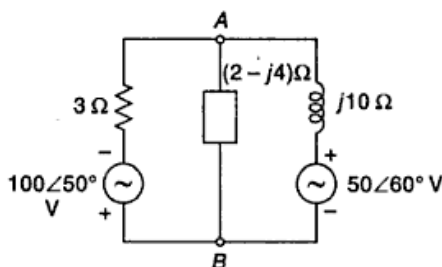


Fig. 6.2 Circuit of Ex. 6.2

Solution

Considering the $100 \angle 50^\circ$ voltage source acting alone and removing the other, the current through branch AB as shown in Fig. 6.2(a) is given by

$$I_1 = \frac{100 \angle 50^\circ}{3 + \frac{j10(2 - j4)}{j10 + 2 - j4}} \times \frac{j10}{j10 + 2 - j4}$$

$$= \frac{100 \angle 50^\circ}{3 + 10 \frac{4 + j2}{2 + j6}} \times \frac{j10}{2 + j6}$$

$$= \frac{100 \angle 50^\circ}{6 + j18 + 40 + j20} \times j10$$

$$= \frac{1000 \angle 140^\circ}{46 + j38}$$

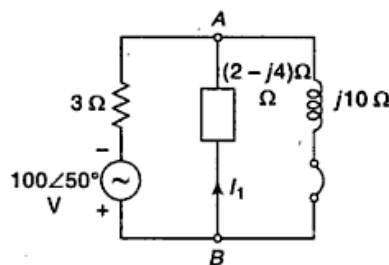


Fig. 6.2(a) $100 \angle 50^\circ \text{ V}$ source acting alone

$$= \frac{1000 \angle 140^\circ}{59.66 \angle 39.56^\circ}$$

$$= 16.76 \angle 100.44^\circ \text{ A (from B to A).}$$
 Considering $50 \angle 60^\circ \text{ V}$ source acting alone and removing the other, the current through branch AB as shown in Fig. 6.2(b) is obtained as

$$\begin{aligned}
 I_2 &= \frac{50 \angle 60^\circ}{j10 + \frac{3(2-j4)}{3+2-j4}} \times \frac{3}{3+2-j4} \\
 &= \frac{150 \angle 60^\circ}{j50 + 40 + 6 - j12} \\
 &= \frac{150 \angle 60^\circ}{46 + j38} \\
 &= \frac{150 \angle 60^\circ}{59.66 \angle 39.56^\circ} = 2.51 \angle 20.44^\circ \text{ A (from A to B).}
 \end{aligned}$$

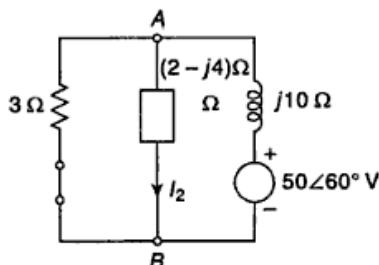


Fig. 6.2(b) $50 \angle 60^\circ \text{ V}$ source acting alone

According to the superposition theorem when both the sources are acting simultaneously the current through AB is obtained as

$2.51 \angle 20.44^\circ - 16.76 \angle 100.44^\circ = 5.388 - j15.6 = 16.5 \angle -70.96^\circ \text{ A (from A to B).}$

6.3 Find the current through the capacitor of $(-j5 \Omega)$ reactance in Fig. 6.3 using superposition theorem.

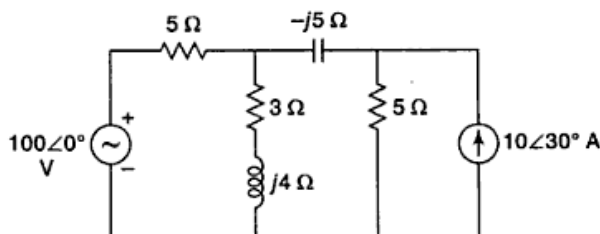


Fig. 6.3 Circuit of Ex. 6.3

Solution

Considering the voltage source acting alone in the circuit and removing the current source, as shown in Fig. 6.3(a), the current through $(-j5 \Omega)$ reactance is given by

$$I_1 = \frac{100 \angle 0^\circ}{5 + \frac{(5-j5)(3+j4)}{3+j4+5-j5}} \times \frac{3+j4}{3+j4+5-j5}$$

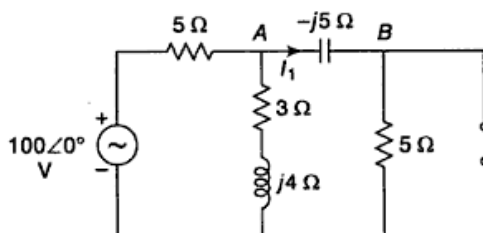


Fig. 6.3(a) Voltage source acting alone

$$\begin{aligned}
 &= \frac{100 \angle 0^\circ \times 5 \angle 53.13^\circ}{5(8-j) + (15+20+j20-j15)} \\
 &= \frac{500 \angle 53.13^\circ}{40-j5+35+j5} = \frac{500 \angle 53.13^\circ}{75} = 6.67 \angle 53.13^\circ \text{ A (from A to B).}
 \end{aligned}$$

Considering the current source acting alone and removing the voltage source the current through $(-j5 \Omega)$ reactance, as shown in Fig. 6.3(b) and Fig. 6.3(c), is found as

$$\begin{aligned}
 I_2 &= 10 \angle 30^\circ \times \frac{5}{5-j5 + (2.5+j1.25)} \\
 &= \frac{50 \angle 30^\circ}{7.5-j3.75} \\
 &= \frac{50 \angle 30^\circ}{8.385 \angle -26.56^\circ} = 5.963 \angle 56.56^\circ \text{ A (from B to A).}
 \end{aligned}$$

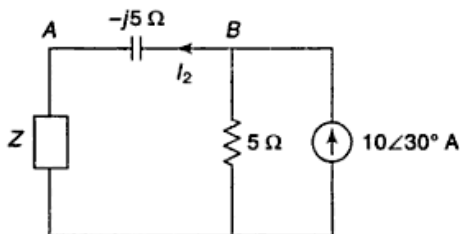


Fig. 6.3(c) Simplified circuit $\left[Z = \frac{5(3+j4)}{5+3+j4} = (2.5+j1.25) \Omega \right]$

According to the superposition theorem when both the sources are acting simultaneously the current through the $(-j5 \Omega)$ reactance is obtained as

$$\begin{aligned}
 I &= 6.67 \angle 53.13^\circ - 5.963 \angle 56.56^\circ \\
 &= 0.801 \angle 26^\circ \text{ A (from A to B).}
 \end{aligned}$$

6.4 Find the current in the resistor of the 10Ω resistance in Fig. 6.4 using the principle of superposition theorem.

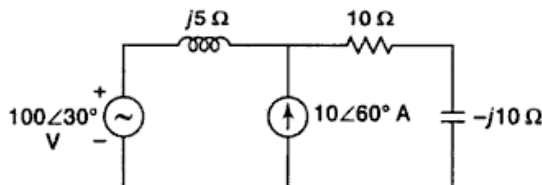


Fig. 6.4 Circuit of Ex. 6.4

Solution

When the voltage source $100 \angle 30^\circ \text{ V}$ acts alone in the circuit (the corresponding figure being shown in Fig. 6.4(a)), we have

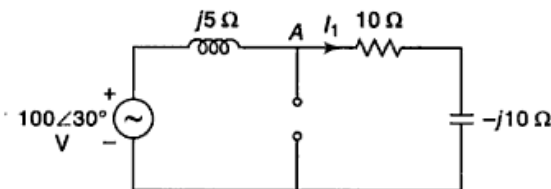


Fig. 6.4(a) Voltage source acting alone

$$\begin{aligned}
 I_1 &= \frac{100 \angle 30^\circ}{j5 + 10 - j10} \\
 &= \frac{100 \angle 30^\circ}{10 - j5} = \frac{100 \angle 30^\circ}{11.18 \angle -26.56^\circ} = 8.94 \angle 56.56^\circ \text{ A (from A to B).}
 \end{aligned}$$

When the current source $10 \angle 60^\circ$ A acts alone in the circuit (the corresponding figure being shown in Fig. 6.4(b)), we can write

$$\begin{aligned}
 I_2 &= 10 \angle 60^\circ \times \frac{j5}{j5 + 10 - j10} \\
 &= 10 \angle 60^\circ \times \frac{j5}{10 - j5} \\
 &= \frac{50 \angle 150^\circ}{11.18 \angle -26.56^\circ} \\
 &= 4.47 \angle 176.56^\circ \text{ A (from A to B).}
 \end{aligned}$$

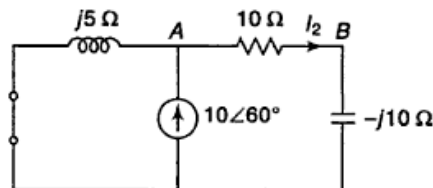


Fig. 6.4(b) Current source acting alone

When both the sources are acting simultaneously following the superposition theorem, the current through 10Ω resistor is

$$\begin{aligned}
 I &= 8.94 \angle 56.56^\circ + 4.47 \angle 176.56^\circ \\
 &= 4.92 + j 7.46 - 4.46 + j 0.268 \\
 &= 0.46 + j 7.728 \\
 &= 7.74 \angle 86.59^\circ \text{ A (from A to B).}
 \end{aligned}$$

.....

6.2 THEVENIN'S THEOREM (AC APPLICATION)

Similar to the dc network, Thevenin's theorem is equally applied to ac networks since they also contain linear circuit elements like resistors, capacitors and inductors. In dc circuits, voltage sources are replaced by their internal resistances while evaluating Thevenin's equivalent resistance; in ac circuits voltage sources need to be replaced by their internal impedances while obtaining Thevenin's equivalent impedance. Since reactances of a circuit are frequency dependent, the Thevenin's theorem is applicable to a particular network at a particular frequency.

Thevenin's theorem in ac circuits can be stated as follows:

Any active, two terminal, linear network can be replaced by an equivalent voltage source in series with an impedance, the voltage being equal to the open circuit voltage between the terminals and the impedance being equal to the impedance between the terminals with all independent sources being replaced by their internal impedances.

6.5 Find the Thevenin's equivalent circuit of the network shown in Fig. 6.5.

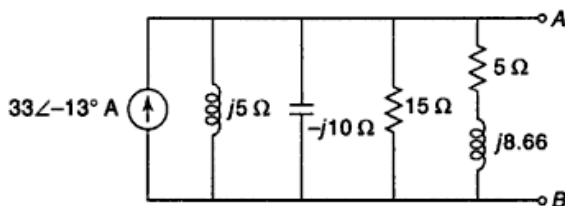


Fig. 6.5 Circuit of Ex. 6.5

Solution

The admittances of the branches are

$$y_1 = \frac{1}{j5} = (-0.2j) \text{ Siemens (S)}$$

$$y_2 = \frac{1}{-j10} = (0.1j) \text{ S}$$

$$y_3 = \frac{1}{15} = (0.067) \text{ S}$$

$$y_4 = \frac{1}{5 + j8.66} = (0.05 - j.0866) \text{ S}$$

The equivalent admittance

$$Y = -0.2j + 0.1j + 0.067 + 0.05 - j.0866 \\ = (0.117 - j.0866) \text{ S}$$

∴ the voltage across the open circuited terminals is given by

$$V_{AB} = V_{Th} = \frac{33 \angle -13^\circ}{0.117 - j.1866} = \frac{33 \angle -13^\circ}{0.22 \angle -57.9^\circ} \\ = 150 \angle 44.9^\circ \text{ V}$$

Thevenin's equivalent impedance Z_{Th} can be found from Fig. 6.5(a).

$$Z_{Th} = \frac{1}{\frac{1}{j5} + \frac{1}{-j10} + \frac{1}{15} + \frac{1}{5 + j8.66}} \\ = \frac{1}{0.117 - j.1866} = \frac{1}{0.22 \angle -57.9^\circ} = 4.545 \angle 57.9^\circ \Omega$$

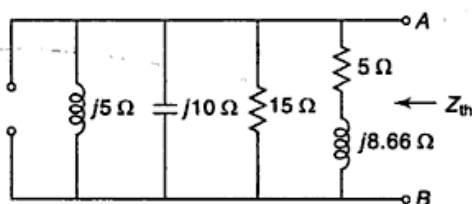


Fig. 6.5(a) Determination of Z_{Th}

Hence the Thevenin's equivalent circuit can be obtained with $V_{Th} = 150 \angle 44.9^\circ \text{ V}$ and $Z_{Th} = 4.545 \angle 57.9^\circ \Omega$.

6.6 Find the current through the 10Ω resistor using Thevenin's theorem in the network shown in Fig. 6.6.

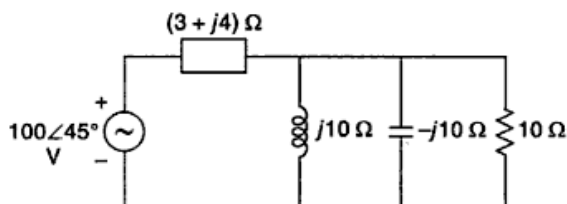


Fig. 6.6 Circuit of Ex. 6.6

Solution

Removing the 10 Ω resistor, the open circuit voltage V_{oc} can be found out from Fig. 6.6(a).

Let us consider two mesh currents I_1 and I_2 .

The mesh equations are as follows:

$$100\angle 45^\circ - I_1(3 + j4) - (I_1 - I_2)j10 = 0 \quad (i)$$

$$\text{and } -j10(I_2 - I_1) - I_2(-j10) = 0. \quad (ii)$$

Solving equations (i) and (ii)

$$I_1 = 0$$

$$\text{and } I_2 = \frac{100\angle 45^\circ}{-j10} = 10\angle 135^\circ \text{ A.}$$

Hence $V_{oc} = (-j10) \times 10\angle 135^\circ = 100\angle 45^\circ \text{ V.}$

Therefore, Thevenin's equivalent voltage $V_{Th} = 100\angle 45^\circ \text{ V.}$

Removing the voltage source from Fig. 6.6(a), Thevenin's equivalent impedance (Z_{Th}) can be found out from Fig. 6.6(b).

$$Z_{Th} = \frac{1}{\frac{1}{j10} + \frac{1}{-j10} + \frac{1}{3 + j4}} = (3 + j4) \Omega$$

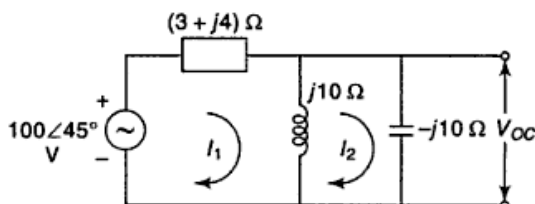
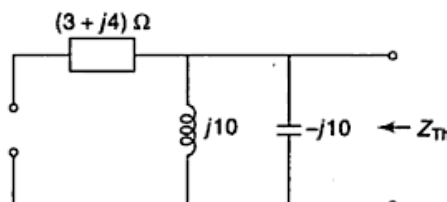
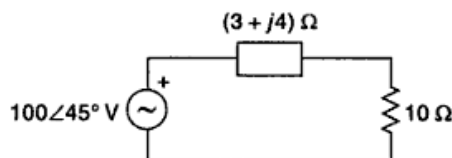
Fig. 6.6(a) Determination of V_{OC} Fig. 6.6(b) Determination of Z_{Th} 

Fig. 6.6(c) Thevenin's equivalent circuit of Ex. 6.6

The Thevenin's equivalent circuit is shown in Fig. 6.6(c).

Hence the current through 10 Ω resistor is

$$= \frac{100\angle 45^\circ}{3 + j4} = \frac{100\angle 45^\circ}{5\angle 53.13^\circ} = 20\angle -8.13^\circ \text{ A.}$$

.....

6.7 Find the current through the impedance of $(10 + j5) \Omega$ in Fig. 6.7.

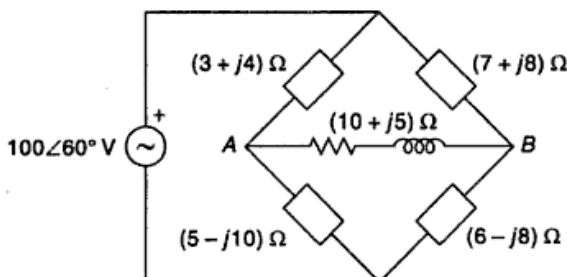


Fig. 6.7 Circuit of Ex. 6.7

Solution

Open circuiting the terminals of $(10 + j5) \Omega$ as shown in Fig. 6.7(a), Thevenin's equivalent voltage can be obtained.

Here,

$$I_1 = \frac{100 \angle 60^\circ}{3 + j4 + 5 - j10}$$

$$= \frac{100 \angle 60^\circ}{8 - j6} = \frac{100 \angle 60^\circ}{10 \angle -36.87^\circ} = 10 \angle 96.87^\circ \text{ A}$$

$$I_2 = \frac{100 \angle 60^\circ}{7 + j8 + 6 - j8} = \frac{100 \angle 60^\circ}{13} = 7.69 \angle 60^\circ \text{ A}$$

$$V_{Th} = V_{AB} = V_{PB} - V_{PA}$$

$$= I_2(7 + j8) - I_1(3 + j4)$$

$$= 7.69 \angle 60^\circ \times 10.63 \angle 48.8^\circ - 10 \angle 96.87^\circ \times 5 \angle 53.13^\circ$$

$$= 81.745 \angle 108.8^\circ - 50 \angle 150^\circ$$

$$= 16.96 + j52.38 = 55.06 \angle 72.06^\circ \text{ V}$$

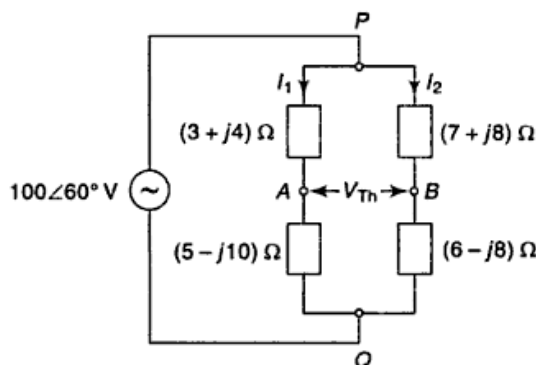


Fig. 6.7(a) Determination of V_{Th}

Thevenin's equivalent impedance can be found out from Fig. 6.7(b) and Fig. 6.7(c) by removing voltage source,

$$Z_{Th} = \frac{1}{\frac{1}{3 + j4} + \frac{1}{5 - j10}} + \frac{1}{\frac{1}{7 + j8} + \frac{1}{6 - j8}}$$

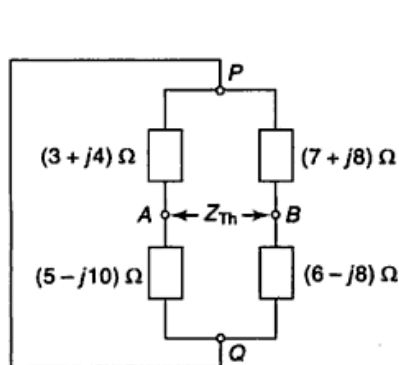
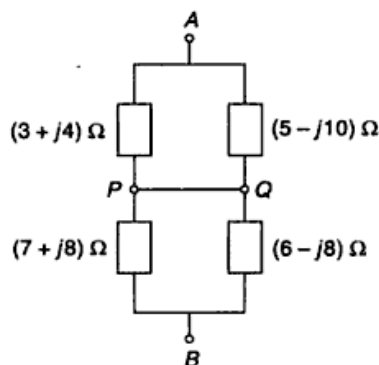
Fig. 6.7(b) Determination of Z_{th} 

Fig. 6.7(c) Simplified circuit of Fig. 6.7(b)

$$\begin{aligned}
 &= \frac{15 + 40 + j(20 - 30)}{8 - j6} + \frac{42 + 64 + j(48 - 56)}{13} \\
 &= \frac{55 - j10}{8 - j6} + \frac{106 - j8}{13} \\
 &= \frac{55.9 \angle -10.3^\circ}{10 \angle -36.87^\circ} + 8.15 - j0.615 \\
 &= 5.59 \angle 26.57^\circ + 8.15 - j0.615 \\
 &= 5 + j2.5 + 8.15 - j0.615 = (13.15 + j1.885) \Omega
 \end{aligned}$$

Thevenin's equivalent circuit is shown in Fig. 6.7(d).

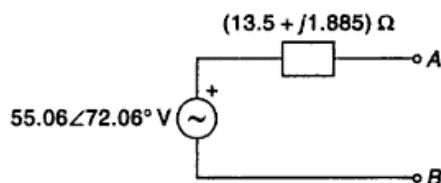


Fig. 6.7(d) Thevenin's equivalent circuit of Ex. 6.7

The current through $(10 + j5) \Omega$ impedance is obtained as

$$\begin{aligned}
 I &= \frac{55.06 \angle 72.06^\circ}{13.15 + j1.885 + 10 + j5} \\
 &= \frac{55.06 \angle 72.06^\circ}{23.15 + j6.885} = \frac{55.06 \angle 72.06^\circ}{24.15 \angle 16.56^\circ} = 2.28 \angle 55.5^\circ \text{ A.}
 \end{aligned}$$

.....

6.8 Find the Thevenin's equivalent circuit of the network shown in Fig. 6.8.

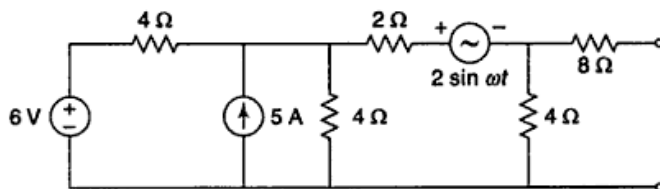


Fig. 6.8 Circuit of Ex. 6.8

Solution

Let us redraw the given network with mesh currents indicated in Fig. 6.8(a). The 5 A source has been converted to equivalent voltage source as shown in the figure.

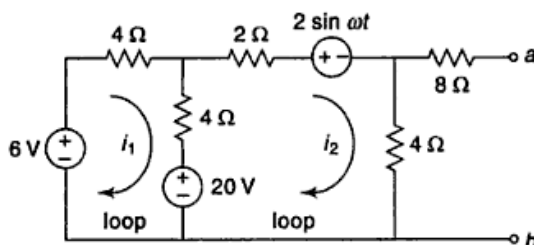


Fig. 6.8(a) Determination of V_{Th}

In loop 1 mesh analysis gives

$$4i_1 - 6 + 20 + 4(i_1 - i_2) = 0$$

or

$$8i_1 - 4i_2 = -14$$

(i)

In loop 2 the mesh analysis gives

$$2i_2 + 4(i_2 - i_1) - 20 + 4i_2 + 2 \sin \omega t = 0$$

or

$$-4i_1 + 10i_2 = 20 - 2 \sin \omega t$$

or

$$-2i_1 + 5i_2 = 10 - \sin \omega t$$

(ii)

Solving equations (i) and (ii)

$$i_2 = 1.625 - 0.25 \sin \omega t.$$

Therefore Thevenin's equivalent voltage is obtained as

$$V_{Th} = V_{ab} = 4i_2 = 6.5 - \sin \omega t.$$

To find Thevenin's internal impedance the sources are replaced by their internal impedance as shown in Fig. 6.8(b).

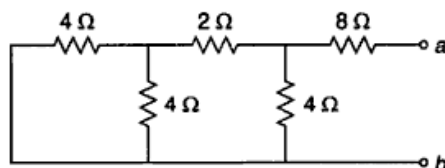


Fig. 6.8(b) Determination of Z_{Th}

Hence

$$Z_{Th} = \{(4 \parallel 4) + 2\} \parallel 4 + 8 = (4 \parallel 4) + 8 = 2 + 8 = 10 \Omega.$$

Thevenin's equivalent circuit is shown in Fig. 6.8(c).

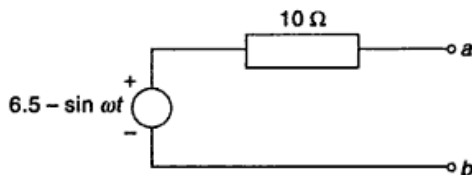


Fig. 6.8(c) Thevenin's equivalent circuit of Ex. 6.8

6.3 NORTON'S THEOREM (AC APPLICATION)

In application of Norton's theorem in ac circuits the resistances of dc circuits are replaced by impedances, the circuit variables being current or voltage phasors.

The statement of Norton's theorem for ac network is as follows:

Any two terminal active network containing voltage sources and impedances when viewed from its output terminals is equivalent to a constant current source and a parallel impedance. The constant current is equal to the current which should flow in a short circuit placed across the terminals and the parallel impedance is the impedance of the network when viewed from open circuited terminals after independent energy sources have been replaced by their internal impedances (if any).

6.9 Use Norton's theorem to find current in the load connected across terminals *a* and *b* of the circuit shown in Fig. 6.9.

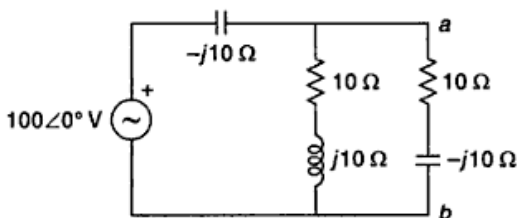


Fig. 6.9 Circuit of Ex. 6.9

Solution

Short circuiting the terminals *ab* of the circuit shown in Fig. 6.9 Norton's equivalent current can be found out. The corresponding circuit is shown in Fig. 6.9(a).

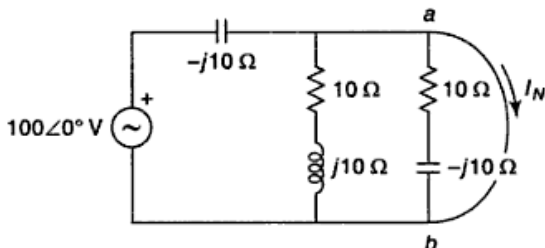


Fig. 6.9(a) Determination of Norton's current

The current through the short circuited path

$$I_N = \frac{100 \angle 0^\circ}{-j10} = 10 \angle 90^\circ \text{ A.}$$

Removing the voltage source and open circuiting the terminals *a* and *b* Norton's equivalent impedance can be found out as shown in Fig. 6.9(b).

$$\text{Hence } Z_N = \frac{-j10(10 + j10)}{-j10 + 10 + j10} = (10 - j10) \Omega$$

The Norton's equivalent circuit is shown in Fig. 6.9(c). Hence the current across terminals *a* and *b* is

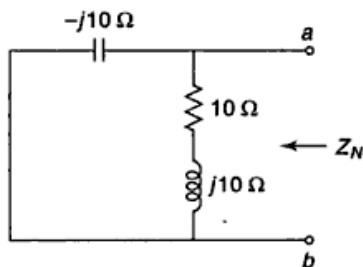


Fig. 6.9(b) Determination of Z_N

$$I = 10 \angle 90^\circ \times \frac{1}{2} \quad (\text{as both the impedances in parallel are of equal value})$$

$$= 5 \angle 90^\circ \text{ A.}$$

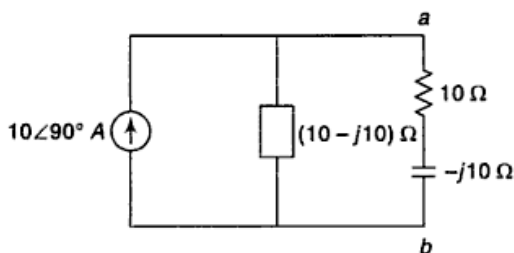


Fig. 6.9(c) Norton's equivalent circuit of Ex. 6.9

6.10 Find Norton's equivalent circuit for the network shown in Fig. 6.10 across terminals $a - b$. Assume $I = 5\angle 0^\circ$ A.

Solution

Short circuiting terminals a and b as shown in Fig. 6.10(a), Norton's equivalent current (I_N) can be found out.

$$\begin{aligned} I_N &= I \times \frac{j5 + 2}{j5 + 2 + 4} \\ &= 5\angle 0^\circ \times \frac{2 + j5}{6 + j5} \\ &= 5\angle 0^\circ \times \frac{5.385\angle 68.2^\circ}{7.81\angle 39.8^\circ} = 3.45\angle 28.4^\circ \text{ A} \end{aligned}$$

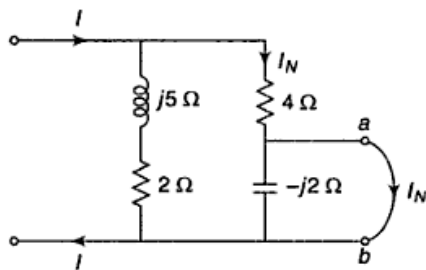
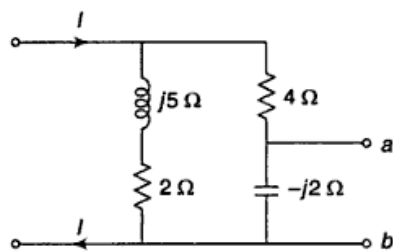
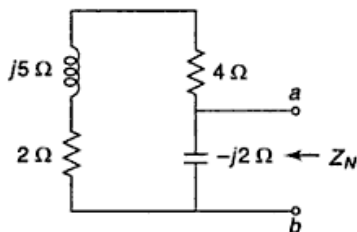
Fig. 6.10(a) Determination of I_N 

Fig. 6.10 Circuit of Ex. 6.10

Fig. 6.10(b) Determination of Z_N

Open circuiting the terminals $a - b$ as shown in Fig. 6.10(b), Norton's equivalent impedance can be found out.

$$\begin{aligned} Z_N &= \frac{-j2(4 + j5 + 2)}{-j2 + 4 + j5 + 2} \\ &= \frac{-j2(6 + j5)}{6 + j3} \\ &= \frac{10 - j12}{6 + j3} \\ &= \frac{15.62\angle -50.2^\circ}{6.71\angle 26.56^\circ} \\ &= 2.328\angle -76.76^\circ \Omega \end{aligned}$$

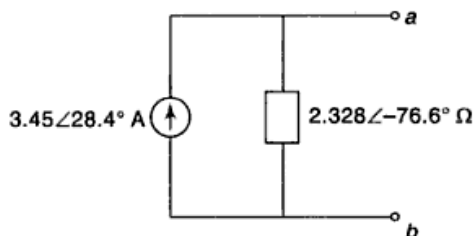


Fig. 6.10(c) Norton's equivalent circuit of Ex. 6.10

Norton's equivalent circuit is shown in Fig. 6.10(c).

6.11 Find current through the $1\ \Omega$ resistor in the circuit shown in Fig. 6.11 using Norton's theorem.

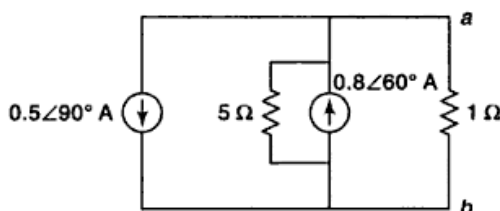


Fig. 6.11 Circuit of Ex. 6.11

Solution

Removing $1\ \Omega$ resistor in the circuit shown in Fig. 6.11 and short circuiting the terminals, Norton's equivalent current can be found out. The corresponding circuit is shown in Fig. 6.11(a).

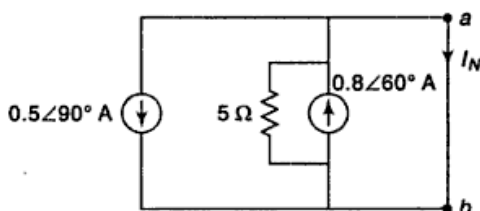


Fig. 6.11(a) Determination of I_N

The current through the short circuited path ab in Fig. 6.11(a) is the Norton's equivalent current (I_N).

$$\begin{aligned}\text{Therefore } I_N &= 0.8\angle 60^\circ - 0.5\angle 90^\circ \\ &= 0.4 + j0.69 - j0.5 = 0.4 + j0.19 = 0.443\angle 25.4^\circ \text{ A.}\end{aligned}$$

To find out Norton's equivalent resistance R_N terminal ab is open circuited and current sources are removed as shown in Fig. 6.11(b).

$$\text{Therefore, } R_N = 5\ \Omega.$$

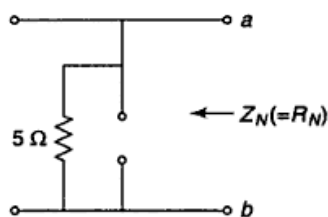


Fig. 6.11(b) Determination of Z_N

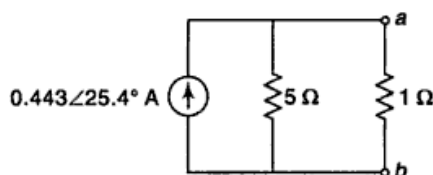


Fig. 6.11(c) Norton's equivalent circuit of Ex. 6.11

Norton's equivalent circuit is shown in Fig. 6.11(c).

Current through $1\ \Omega$ resistor is given by

$$\begin{aligned}&= 0.443\angle 25.4^\circ \times \frac{5}{5+1} \\ &= 0.37\angle 25.4^\circ \text{ A.}\end{aligned}$$

.....

6.12 In the circuit of Fig. 6.12, find Norton's equivalent circuit across AB.

Solution

Terminals A and B are short circuited and the current through the short circuited path is found out as shown in Fig. 6.12(a).

Hence Norton's equivalent current is obtained as

$$I_N = \frac{20 \angle 0^\circ}{j5} \text{ A} = 4 \angle -90^\circ \text{ A.}$$

Removing the voltage source and open circuiting terminals AB, Norton's equivalent impedance can be found out from Fig. 6.12(b).

Here Norton's equivalent impedance is

$$\begin{aligned} Z_N &= j5 \parallel (10 - j15) = \frac{j5(10 - j15)}{j5 + 10 - j15} \\ &= \frac{75 + j50}{10 - j10} = \frac{15 + j10}{2 - j2} = \frac{18 \angle 33.7^\circ}{2.828 \angle -45^\circ} \\ &= 6.36 \angle 78.7^\circ \Omega = (1.246 + j6.23) \Omega \end{aligned}$$

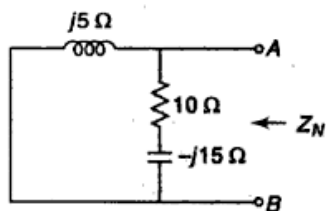


Fig. 6.12(b) Determination of Z_N

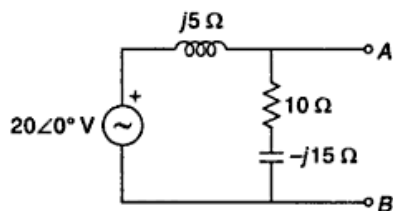


Fig. 6.12 Circuit of Ex. 6.12

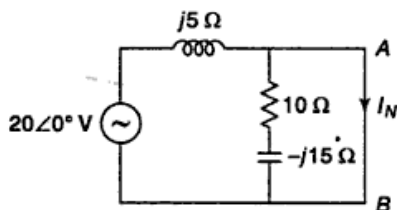


Fig. 6.12(a) Determination of I_N

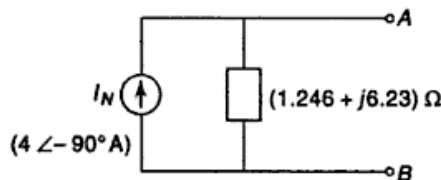


Fig. 6.12(c) Norton's equivalent circuit of Ex. 6.12

Norton's equivalent circuit is shown in Fig. 6.12(c).

6.4 MAXIMUM POWER TRANSFER THEOREM (AC APPLICATION)

This theorem finds useful application while evaluating the impedance of load to be connected to a two-terminal active network so that maximum power gets transferred from the network to the load. Three different cases have been considered here.

Case1:

When the load is purely resistive

We assume a circuit as shown in Fig. 6.13 where load resistance is R_L , source impedance $Z_g = R_g + jX_g$ and source voltage is E_g .

The current delivered to the load is

$$I = \frac{E_g}{R_g + R_L + jX_g} \quad (6.1)$$

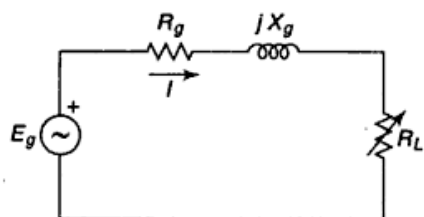


Fig. 6.13 Power transfer in pure resistive load

Power delivered to the load

$$P_L = (\text{Magnitude of current})^2 \times R_L = \frac{E_g^2}{(R_g + R_L)^2 + X_g^2} R_L \quad (6.2)$$

If maximum power is to be delivered

$$\frac{dP_L}{dR_L} = 0$$

$$\text{or} \quad \frac{d}{dR_L} \left\{ \frac{E_g^2}{(R_g + R_L)^2 + X_g^2} R_L \right\} = 0$$

$$\text{or} \quad \{(R_g + R_L)^2 + X_g^2\} E_g^2 - E_g^2 R_L \{2(R_g + R_L)\} = 0$$

$$\text{or} \quad R_g^2 + R_L^2 + X_g^2 + 2 R_g R_L - 2 R_g R_L - 2 R_L^2 = 0$$

$$\text{or} \quad R_g^2 + X_g^2 = R_L^2$$

$$\text{or} \quad R_L = \sqrt{R_g^2 + X_g^2} \quad (6.3)$$

Therefore load resistance $R_L = |Z_g|$, for maximum power transfer to resistive load

$$\text{If } X_g = 0 \text{ then } R_L = R_g \quad (6.4)$$

Case 2:

When the load constitutes of variable reactance and fixed resistance as shown in Fig. 6.14.

The load impedance $Z_L = R_L + jX_L$ where R_L is fixed and X_L is variable as shown in Fig. 6.14.

The net circuit impedance

$$Z = Z_g + Z_L = (R_g + R_L) + j(X_g + X_L)$$

The circuit current

$$I_L = \frac{E_g}{\sqrt{(R_g + R_L)^2 + (X_g + X_L)^2}} \quad (6.5)$$

The power delivered to the load

$$P_L = I_L^2 R_L = \frac{E_g^2 R_L}{(R_g + R_L)^2 + (X_g + X_L)^2} \quad (6.6)$$

Since R_L is fixed and X_L is variable so for maximum power transfer is obtained

$$\text{when } \frac{dP_L}{dX_L} = 0.$$

$$\text{i.e.} \quad \frac{d}{dX_L} \left\{ \frac{E_g^2 R_L}{(R_g + R_L)^2 + (X_g + X_L)^2} \right\} = 0$$

$$\text{or} \quad -2(X_g + X_L) = 0$$

$$\text{or} \quad X_L = -X_g \quad (6.7)$$

Therefore for maximum power transfer, the reactance of the load is of the same magnitude as the source reactance of the network, but is of opposite sign.

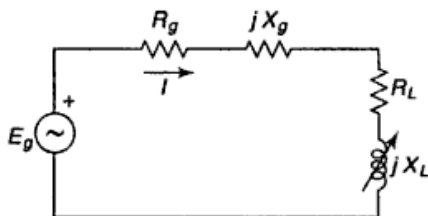


Fig. 6.14 Power transfer to R-L load (L is variable)

Case 3:

When the load reactance is of fixed magnitude and load resistance is variable as shown in Fig. 6.15.

The load impedance $Z_L = R_L + jX_L$ where X_L is fixed and R_L is variable.

The power delivered to the load

$$P_L = I_L^2 R_L = \frac{E_g^2 R_L}{(R_g + R_L)^2 + (X_g + X_L)^2} \quad (6.8)$$

If X_L is of fixed magnitude and R_L is variable the condition for maximum power transfer is

$$\frac{dP_L}{dR_L} = 0.$$

$$\text{Therefore } \frac{d}{dR_L} \left[\frac{E_g^2 R_L}{(R_g + R_L)^2 + (X_g + X_L)^2} \right] = 0$$

$$\text{or } (R_g + R_L)^2 + (X_g + X_L)^2 - R_L \{2(R_g + R_L)\} = 0$$

$$\text{or } R_g^2 + (X_g + X_L)^2 - R_L^2 = 0$$

$$\text{or } R_L^2 = R_g^2 + (X_g + X_L)^2$$

$$\text{or } R_L = \sqrt{R_g^2 + (X_g + X_L)^2} \quad (6.9)$$

Equation (6.9) gives the condition of maximum power transfer when R_L is variable.

General Case

If the load is such that both its resistance and reactance are variable, maximum power would be delivered when $Z_L = Z_g^*$ i.e. load impedance is the complex conjugate of the network impedance (i.e., $R_L = R_g$ and $X_L = -X_g$).

Proof:

We have seen that when the load reactance X_L alone is variable the condition for maximum power transfer is $X_L = -X_g$.

Maximum power transferred

$$P_{\max} = I_L^2 R_L = \frac{E_g^2 R_L}{(R_L + R_g)^2 + (X_L + X_g)^2} \quad (6.10)$$

Substituting $X_L = -X_g$

$$P_{\max} = \frac{E_g^2 R_L}{(R_g + R_L)^2} \quad (6.11)$$

If the load resistance R_L is also variable then

$$\frac{dP_{\max}}{dR_L} = 0$$

$$\text{or } (R_g + R_L)^2 - R_L^2 (R_g + R_L) = 0$$

$$\text{or } R_L^2 = R_g^2 \text{ or } R_L = R_g \quad (6.12)$$

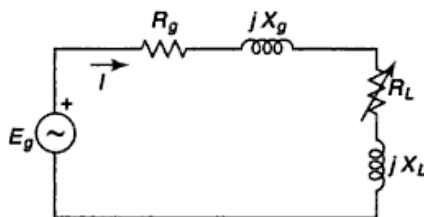


Fig. 6.15 Power transfer to R-L load (R is variable)

Statement of the Theorem:

The power delivered by an active network to a load connected across its terminals is maximum when the impedance of the load is the complex conjugate of the active network impedance.

The maximum power transferred under this condition is given by $P_{\max} = \frac{E_s^2}{4R_L}$

as $R_g = R_L$ and $X_g = X_L$.

6.13 In the circuit shown in Fig. 6.16 find the value of R_L which results in maximum power transfer. Also calculate the value of the maximum power.

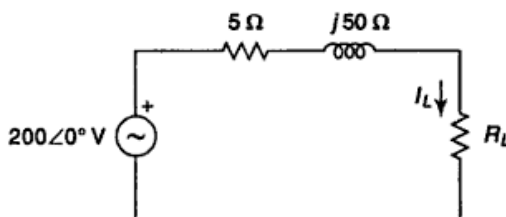


Fig. 6.16 Circuit of Ex. 6.13

Solution

As the load consists of resistance only hence for maximum power transfer

$$R_L = |Z_g| = \sqrt{R_g^2 + X_g^2} = \sqrt{(5)^2 + (50)^2} = 50.25 \Omega$$

The current flowing in the circuit

$$\begin{aligned} I_L &= \frac{200 \angle 0^\circ}{5 + 50.25 + j50} \\ &= \frac{200 \angle 0^\circ}{55.25 + j50} \\ &= \frac{200 \angle 0^\circ}{74.52 \angle 42.14^\circ} = 2.684 \angle -42.14^\circ \text{ A.} \end{aligned}$$

$$\text{Maximum power} = I_L^2 R_L = (2.684)^2 \times 50.25 = 362 \text{ W.}$$

6.14 In the network shown in Fig. 6.17 the load consists of a fixed inductance having reactance 20Ω and a variable resistance. Find the value of R_L for which power transfer is maximum and also find the value of the maximum power.

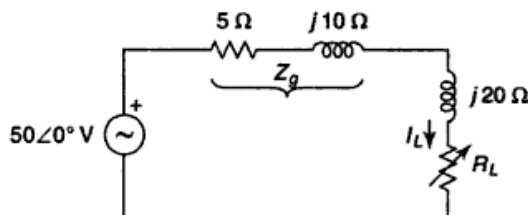


Fig. 6.17 Circuit of Ex. 6.14

Solution

When the load reactance is fixed but load resistance is variable then under maximum power transfer condition load resistance R_L is given by

$$R_L = \sqrt{(R_g)^2 + (X_g + X_L)^2}$$

$$= \sqrt{(5)^2 + (20 + 10)^2} = \sqrt{25 + 900} = 30.414 \, \Omega$$

The circuit current $I_L = \frac{50 \angle 0^\circ}{(5 + 30.414) + j(10 + 20)} = 1.1 \angle -40.26^\circ \text{ A.}$

The maximum power transferred is

$$I_L^2 R_L = (1.1)^2 \times 30.414 = 36.8 \text{ W.}$$

6.15 If in Problem 6.14 the load reactance X_L is variable and the load resistance R_L is fixed having value $10 \, \Omega$, find the value of X_L for which power transfer is maximum and find the value of the maximum power.

Solution

When the load reactance is variable but load resistance is fixed then for maximum power transfer,

$$X_L = -X_g.$$

Hence load reactance

$$X_L = -j10 \, \Omega.$$

The circuit current I_L is obtained as

$$I_L = \frac{50 \angle 0^\circ}{(5 + 10) + j(10 - 10)} = \frac{50 \angle 0^\circ}{15} = 3.33 \text{ A.}$$

Maximum transferred power $P_{\max} = I_L^2 R_L = (3.33)^2 \times 10 = 111.09 \text{ W}$

■ ADDITIONAL PROBLEMS ■

6.16 Find the current through the load in Fig. 6.18 using Thevenin's theorem.

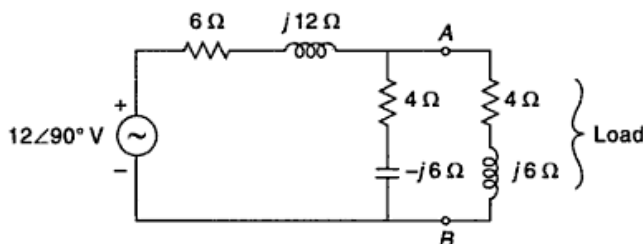


Fig. 6.18 Circuit of Ex. 6.16

Solution

Removing the load impedance the terminals AB is open circuited and the open circuit voltage is found out as shown in Fig. 6.18(a).

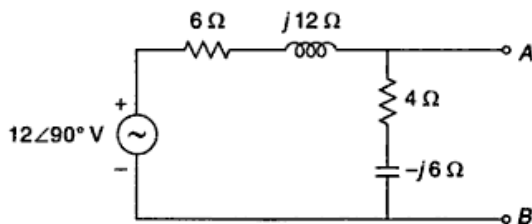


Fig. 6.18(a) Determination of V_{Th}

Thevenin's equivalent voltage:

V_{Th} = Voltage across terminals AB

$$= \frac{12 \angle 90^\circ}{6 + j12 + 4 - j6} \times (4 - j6) = \frac{12 \angle 90^\circ}{10 + j6} (4 - j6) = 7.42 \angle 2.73^\circ \text{ Volts.}$$

Now removing the voltage source, Thevenin's equivalent impedance (Z_{Th}) is found from the circuit shown in Fig. 6.18(b).

$$\begin{aligned} Z_{Th} &= (6 + j12) \parallel (4 - j6) \\ &= \frac{(6 + j12)(4 - j6)}{10 + j6} \\ &= 8.3 \angle -23.83^\circ \\ &= (7.6 - j3.35) \Omega \end{aligned}$$

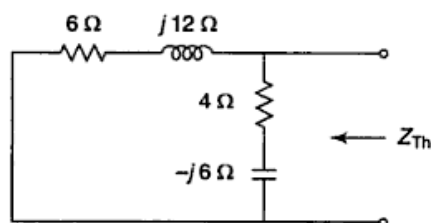


Fig. 6.18(b) Determination of Z_{Th}

Hence current through the load = $\frac{7.42 \angle 2.73^\circ}{7.6 - j3.35 + 4 + j6} = 0.624 \angle -10.14^\circ \text{ A.}$

6.17. Solve Example 6.16 using Norton's theorem.

Solution

The load impedance is removed and the terminals AB is open circuited as shown in Fig. 6.18(c).

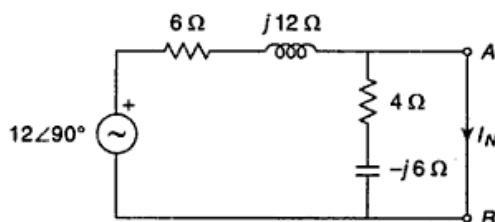


Fig. 6.18(c) Determination of I_N

The current through the short circuited path AB is the Norton's equivalent current I_N .

$$\text{Hence } I_N = \frac{12 \angle 90^\circ}{6 + j12} \text{ A} = \frac{12 \angle 90^\circ}{13.41 \angle 63.43^\circ} \text{ A} = 0.89 \angle 26.56^\circ \text{ A.}$$

Norton's equivalent impedance (Z_N) can be found in the same way as that of Thevenin's equivalent impedance.

$$\begin{aligned} \text{Hence, } Z_N &= \frac{(6 + j12)(4 - j6)}{10 + j6} \\ &= \frac{96.74 \angle 7.125^\circ}{11.66 \angle 30.96^\circ} = 8.3 \angle -23.83^\circ = (7.6 - j3.35) \Omega \end{aligned}$$

\therefore The current through the load (I) is given by

$$I = 0.89 \angle 26.56^\circ \times \frac{7.6 - j3.35}{7.6 - j3.35 + 4 + j6} = 0.62 \angle -10.06^\circ \text{ A.}$$

6.18 Find the current through the capacitor in Fig. 6.19 using superposition theorem.

Solution

Considering the current source of $15 \angle 30^\circ \text{ A}$ acting alone in the circuit and removing the voltage source, the current through the capacitor [as shown in Fig. 6.19(a)] is given by

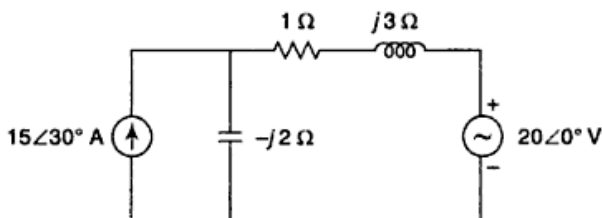


Fig. 6.19 Circuit of Ex. 6.18

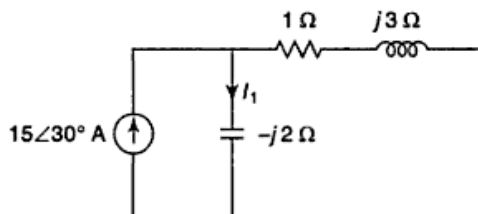


Fig. 6.19(a) Current source acting alone

$$\begin{aligned}
 I_1 &= 15\angle 30^\circ \times \frac{1+j3}{1+j3-j2} \\
 &= 15\angle 30^\circ \times \frac{1+j3}{1+j} = 15\angle 30^\circ \times \frac{3.16\angle 71.56^\circ}{1.414\angle 45^\circ} = 33.54\angle 56.56^\circ \text{ A}
 \end{aligned}$$

Next considering the voltage source of $20\angle 0^\circ$ V acting alone in the circuit and removing the current source, the current through the capacitor [as shown in Fig. 6.19(b)] is obtained as

$$I_2 = \frac{20\angle 0^\circ}{1+j3-j2} \text{ A} = \frac{20\angle 0^\circ}{1+j} = 14.14\angle -45^\circ \text{ A}.$$

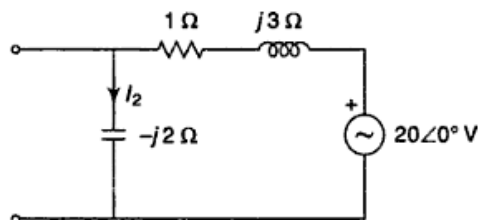


Fig. 6.19(b) Voltage source acting alone

According to superposition theorem when both the sources are acting simultaneously the current through the capacitor (I) is

$$\begin{aligned}
 I &= I_1 + I_2 = 33.54\angle 56.56^\circ + 14.14\angle -45^\circ \\
 &= 28.47 + j17.97 = 33.68\angle 32.28^\circ \text{ A}
 \end{aligned}$$

.....

6.19 In the circuit shown in Fig. 6.20 find the load resistance and load reactance if maximum power is transferred to the load considering both the load resistance and load reactance to be variable.

Solution

When both the load resistance and reactance are variable, the load impedance (Z_L) is the complex conjugate of the internal impedance of the network (Z_g) under maximum power transfer condition.

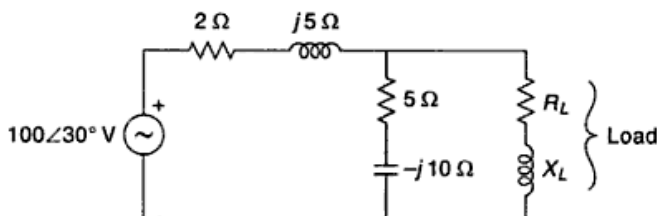
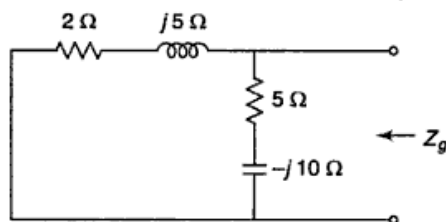


Fig. 6.20 Circuit of Ex. 6.19

Now removing the source and open circuiting the terminals of the load impedance as shown in Fig. 6.20(a), (Z_g) can be found out.

$$\begin{aligned} Z_g &= (5 - j10) \parallel (2 + j5) \\ &= \frac{(5 - j10)(2 + j5)}{5 - j10 + 2 + j5} \\ &= \frac{60 + j5}{7 - j5} \\ &= \frac{60.2 \angle 4.76^\circ}{8.6 \angle -35.53^\circ} \\ &= 7 \angle 40.29^\circ = (5.34 + j4.53) \Omega. \end{aligned}$$

Fig. 6.20(a) Determination of (Z_g)

Hence $Z_L = Z_g^* = (5.34 - j4.53) \Omega$

or, $R_L = 5.34 \Omega$ and $X_L = 4.53 \Omega$ (Capacitive)

6.20 What is the Thevenin's equivalent circuit with respect to the terminals A and B of the circuit shown in Fig. 6.21.

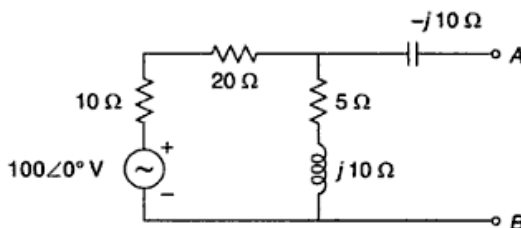


Fig. 6.21 Circuit of Ex. 6.20

Solution

Thevenin's equivalent voltage (V_{Th}) is the voltage across the terminals AB of the network;

$$\begin{aligned} V_{Th} = V_{AB} &= \frac{100 \angle 0^\circ}{10 + 20 + 5 + j10} (5 + j10) \\ &= \frac{100 \angle 0^\circ}{35 + j10} (5 + j10) = 30.7 \angle 47.48^\circ \end{aligned}$$

Removing the voltage source, Thevenin's equivalent impedance Z_{Th} can be found.

$$\begin{aligned} Z_{Th} &= -j10 + \frac{(5 + j10)(20 + j10)}{5 + j10 + 20 + j10} \\ &= -j10 + \frac{150 + j300}{35 + j10} = -j10 + 9.21 \angle 47.48^\circ = (6.22 - j3.21) \Omega \end{aligned}$$

Thevenin's equivalent circuit is shown in Fig. 6.21(a).

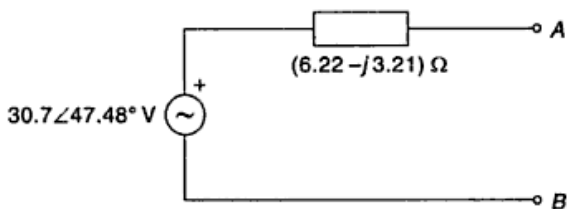


Fig. 6.21(a) Thevenin's equivalent circuit of Ex. 6.20

6.21 In the circuit shown in Fig. 6.22 the circuit consists of fixed inductance and variable load resistance (R_L). Find (R_L) for maximum power transfer and the value of the maximum power.

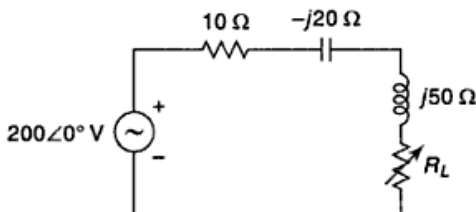


Fig. 6.22 Circuit of Ex. 6.21

Solution

The internal impedance of network is obtained as

$$Z_g = (10 - j20) \Omega = (R_g + jX_g) \Omega.$$

For maximum power transfer when R_L is variable and X_L is fixed,

$$\begin{aligned} R_L &= \sqrt{R_g^2 + (X_g + X_L)^2} \quad (\text{Equation (6.9)}) \\ &= \sqrt{(10)^2 + (-20 + 50)^2} = \sqrt{100 + 900} = 31.62 \Omega. \end{aligned}$$

Under maximum power transfer condition the current through the circuit is obtained as

$$I = \frac{200 \angle 0^\circ}{10 - j20 + j50 + 31.62} = \frac{200 \angle 0^\circ}{41.62 + j30} = 3.9 \angle -35.78^\circ \text{ A}.$$

Maximum transferred power

$$P_{\max} = I^2 R_L = (3.9)^2 \times 31.62 \text{ W} = 481 \text{ W}.$$

6.22 Find Norton's equivalent circuit with respect to terminals A and B of the network shown in Fig. 6.23.

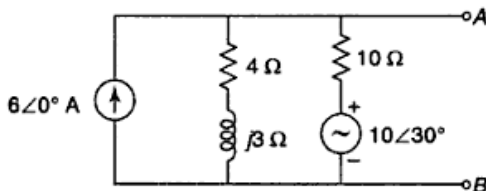
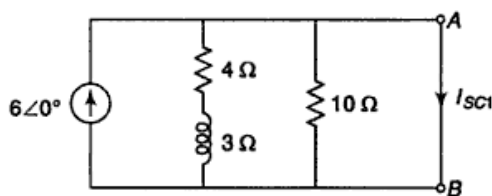


Fig. 6.23 Circuit of Ex. 6.22

Solution


Short circuiting terminals A and B and removing the voltage source, the current through the short circuited path (as shown in Fig. 6.23(a)) due to current source is

$$I_{sc1} = 6 \angle 0^\circ \text{ A (from A to B)}$$

Fig. 6.23(a) Determination of I_{sc1}

Now removing the current source from the network in Fig. 6.23 and short circuiting the terminals AB , the current through the short circuited path [as shown in Fig. 6.23(b)] due to the voltage source is

$$I_{sc2} = \frac{10 \angle 30^\circ}{10} \text{ A} \\ = 1 \angle 30^\circ \text{ A (from A to B).}$$

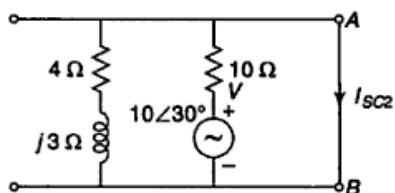Fig. 6.23(b) Determination of I_{sc2}


According to superposition theorem, when both the sources are acting simultaneously the current through the short circuited path is given by

$$I_{sc} = I_{sc1} + I_{sc2} \\ = 6 \angle 0^\circ + 1 \angle 30^\circ \\ = 6 + 0.866 + j0.5 \\ = 6.866 + j0.5 = 6.88 \angle 4.16^\circ \text{ A.}$$

Hence Norton's equivalent current $I_N = 6.88 \angle 4.16^\circ \text{ A}$.

Next, removing the sources, Norton's equivalent impedance Z_N can be found as shown in Fig. 6.23(c).

$$Z_N = 10 \parallel (4 + j3) \\ = \frac{10(4 + j3)}{14 + j3} \\ = 3.49 \angle 24.77^\circ \text{ A} \\ = (3.17 + j1.46) \Omega.$$

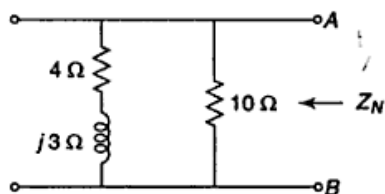Fig. 6.23(c) Determination of (Z_N)

Norton's equivalent circuit is shown in Fig. 6.23(d).

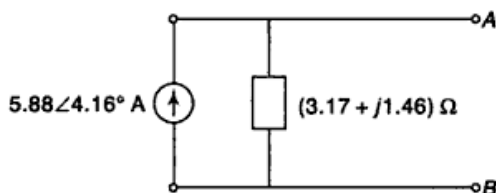


Fig. 6.23(d) Norton's equivalent circuit of Ex. 6.22

6.23 Using the superposition theorem find the current in branch AB of the circuit given in Fig. 6.24.

Solution

Let us consider the $100 \angle 0^\circ \text{ V}$ source acting alone and $50 \angle 0^\circ \text{ V}$ source removed. The circuit is shown in Fig. 6.24(a).

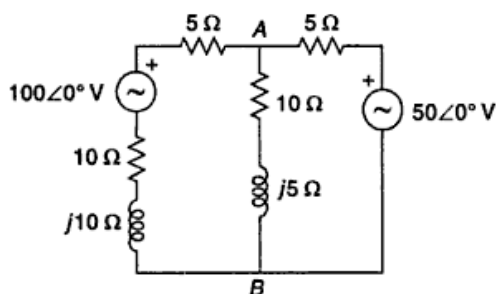
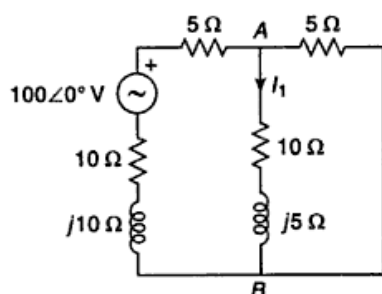


Fig. 6.24 Circuit of Ex. 6.23

Fig. 6.24(a) $100\angle 0^\circ$ V source acting alone


$$\begin{aligned}\text{Total impedance} &= 5 + 10 + j10 + \frac{5(10 + j5)}{5 + 10 + j5} \\ &= 15 + j10 + \frac{10 + j5}{3 + j} \\ &= 15 + j10 + \frac{11.18 \angle 26.56^\circ}{3.16 \angle 18.43^\circ} \\ &= 15 + j10 + 3.54 \angle 8.125^\circ \\ &= 18.5 + j10.5 = 21.27 \angle 29.58^\circ \Omega.\end{aligned}$$

$$\text{Total current} = \frac{100 \angle 0^\circ}{21.27 \angle 29.58^\circ} = 4.7 \angle -29.58^\circ \text{ A.}$$

Hence current through AB is

$$\begin{aligned}I_1 &= 4.7 \angle -29.58^\circ \times \frac{5}{5 + 10 + j5} \\ &= 4.7 \angle -29.58^\circ \times \frac{1}{3 + j} \\ &= 4.7 \angle -29.58^\circ \times 0.316 \angle -18.43^\circ = 1.486 \angle -48.02^\circ \text{ A}\end{aligned}$$

Now let us consider $50\angle 0^\circ$ V source acting alone while $100\angle 0^\circ$ V source is removed. The corresponding circuit is shown in Fig. 6.24(b).

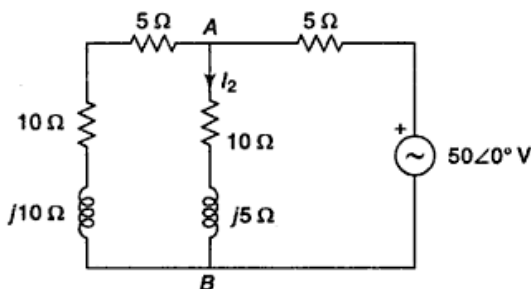Fig. 6.24(b) $50\angle 0^\circ$ V source acting alone

$$\begin{aligned}\text{Total impedance} &= \frac{(5 + 10 + j10)(10 + j5)}{5 + 10 + j10 + 10 + j5} + 5 \\ &= \frac{(15 + j10)(10 + j5)}{25 + j15} + 5\end{aligned}$$

$$\begin{aligned}
 &= \frac{(3+j2)(2+j)}{5+j3} + 5 \\
 &= \frac{4+j7}{5+j3} + 5 \\
 &= \frac{8.062 \angle 60.25^\circ}{5.83 \angle 30.96^\circ} + 5 \\
 &= 1.383 \angle 29.29^\circ + 5 \\
 &= 6.243 \angle 6.23^\circ \Omega
 \end{aligned}$$

$$\text{Total current} = \frac{50 \angle 0^\circ}{6.243 \angle 6.23^\circ} = 8 \angle -6.23^\circ \text{ A}$$

Hence current through AB is obtained as

$$\begin{aligned}
 I_2 &= 6.243 \angle 6.23^\circ \times \frac{5+10+j10}{5+10+j10+10+j5} \\
 &= 6.243 \angle -6.23^\circ \times \frac{18.03 \angle 33.69^\circ}{29.15 \angle 30.96^\circ} = 3.86 \angle 8.96^\circ \text{ A.}
 \end{aligned}$$

Applying superposition theorem the current through branch AB of the circuit when both the sources are acting simultaneously is

$$\begin{aligned}
 I &= I_1 + I_2 = 1.486 \angle -48.02^\circ + 3.86 \angle 8.96^\circ \\
 &= 4.807 - j0.504 = 4.833 \angle 5.985^\circ \text{ A}
 \end{aligned}$$

6.24 Apply superposition theorem to find the current through the capacitor of $(-j5)$ in Fig. 6.25. *****

Solution

Let us consider $20 \angle 90^\circ \text{ A}$ source acting alone in the circuit. The corresponding circuit is

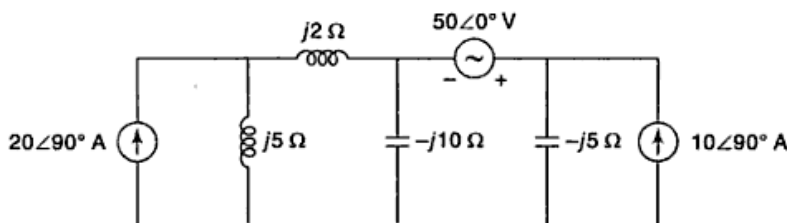


Fig. 6.25 Circuit of Ex. 6.24

shown in Figs 6.25(a) and 6.25(b).

$$X = \frac{(-j10)(-j5)}{-j10 - j5} = \frac{-50}{-j15} = -j \frac{50}{15} = -j3.33 \Omega$$

Current through X is found as

$$\begin{aligned}
 I_X &= 20 \angle 90^\circ \times \frac{j5}{j5 + j2 - j3.33} \\
 &= 20 \angle 90^\circ \times \frac{5 \angle 90^\circ}{3.67 \angle 90^\circ} = 27.25 \angle 90^\circ \text{ A.}
 \end{aligned}$$

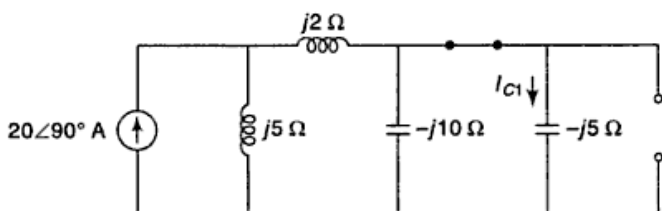


Fig. 6.25(a) Current source $20\angle 90^\circ \text{ A}$ acting alone

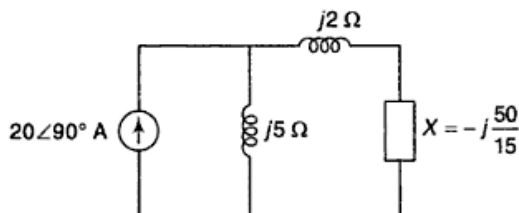


Fig. 6.25(b) Simplified circuit of Fig. 6.25(a)

Hence from Fig. 6.25(a) current through capacitor of $(-j5) \Omega$ is

$$I_{C1} = 27.25\angle 90^\circ \times \frac{-j10}{-j10 - j5} = 18.167\angle 90^\circ \text{ A.}$$

Now let us consider $50\angle 0^\circ \text{ V}$ source acting alone as shown in Fig. 6.25(c).

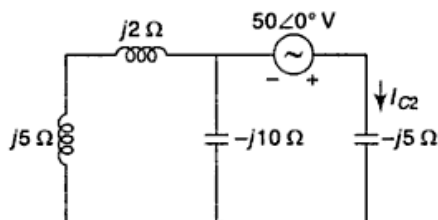


Fig. 6.25(c) Voltage source considered alone

The total impedance is $\left[-j5 + \frac{(-j10)(j5 + j2)}{-j10 + j5 + j2} \right] \Omega$

$$\text{i.e., } Z = -j5 + \frac{70}{-j3} = -j5 + j23.33 = j18.33 = 18.33\angle 90^\circ \Omega.$$

Hence current through capacitor of $(-j5) \Omega$ is

$$I_{C2} = \frac{50\angle 0^\circ}{18.33\angle 90^\circ} = 2.73\angle -90^\circ \text{ A.}$$

Let us consider $10\angle 90^\circ \text{ A}$ source acting alone as shown in Fig. 6.25(d).

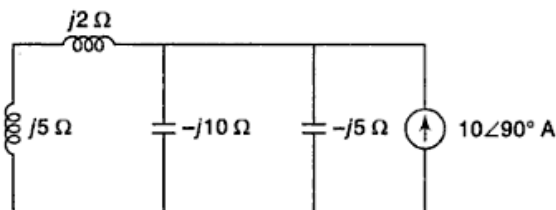


Fig. 6.25(d) $10\angle 90^\circ \text{ A}$ source acting alone

Combined impedance of $j5$, $j2$ and $-j10$ is

$$= \frac{j7(-j10)}{j7 - j10} = \frac{70}{-j3} = j23.33 \Omega$$

Hence current through capacitance of $(-j5) \Omega$ is

$$I_{C3} = 10 \angle 90^\circ \times \frac{j23.33}{j23.33 - j5} = 12.73 \angle 90^\circ \text{ A.}$$

Using the superposition theorem the current I through the capacitor of $(-j5) \Omega$ is $I = I_{C1} + I_{C2} + I_{C3} = 18.167 \angle 90^\circ + 2.73 \angle -90^\circ + 12.73 \angle 90^\circ = 28.167 \angle 90^\circ \text{ A.}$

6.25 Find the current through Z_L in Fig. 6.26 using the superposition theorem.

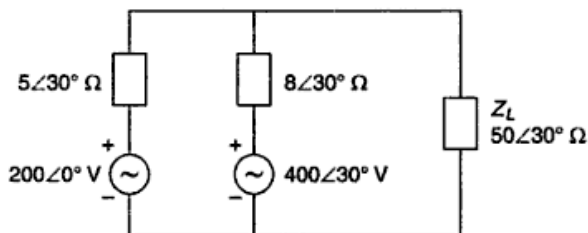


Fig. 6.26 Circuit of Ex. 6.25

Solution

Considering the $200 \angle 0^\circ \text{ V}$ source acting alone in the circuit, the total current supplied by the source is

$$\begin{aligned} \frac{200 \angle 0^\circ}{5 \angle 30^\circ + \frac{8 \angle 30^\circ \times 50 \angle 30^\circ}{8 \angle 30^\circ + 50 \angle 30^\circ}} &= \frac{200 \angle 0^\circ}{5 \angle 30^\circ + \frac{400 \angle 60^\circ}{57.99 \angle 30^\circ}} \\ &= \frac{200 \angle 0^\circ}{5 \angle 30^\circ + 6.89 \angle 30^\circ} = \frac{200 \angle 0^\circ}{10.297 + j5.945} \\ &= \frac{200 \angle 0^\circ}{11.89 \angle 30^\circ} = 16.8 \angle -30^\circ \text{ A.} \end{aligned}$$

Hence, current through $Z_L = 16.8 \angle -30^\circ \times \frac{8 \angle 30^\circ}{8 \angle 30^\circ + 50 \angle 30^\circ}$

$$= \frac{16.8 \times 8}{58 \angle 30^\circ} = 2.317 \angle -30^\circ \text{ A.}$$

Now considering $400 \angle 30^\circ \text{ V}$ source acting alone in the circuit the total current supplied by the source is

$$\begin{aligned} \frac{400 \angle 30^\circ}{8 \angle 30^\circ + \frac{50 \angle 30^\circ \times 5 \angle 30^\circ}{50 \angle 30^\circ + 5 \angle 30^\circ}} &= \frac{400 \angle 30^\circ}{8 \angle 30^\circ + 4.545 \angle 30^\circ} \\ &= \frac{400 \angle 30^\circ}{12.545 \angle 30^\circ} = 31.88 \text{ A} \end{aligned}$$

Hence current through $(Z_L) = 31.88 \times \frac{5 \angle 30^\circ}{5 \angle 30^\circ + 50 \angle 30^\circ}$

$$= \frac{31.88 \times 5}{55} = 2.898 \text{ A}$$

Using the superposition theorem the current through Z_L , when both the sources are acting simultaneously, is

$$\begin{aligned}(2.317\angle-30^\circ + 2.898) \text{ A} &= 4.898 - j1.1585 \\ &= 5.033\angle-13.31^\circ \text{ A}.\end{aligned}$$

6.26 Find current through Z_L in Fig. 6.27 applying Thevenin's theorem.

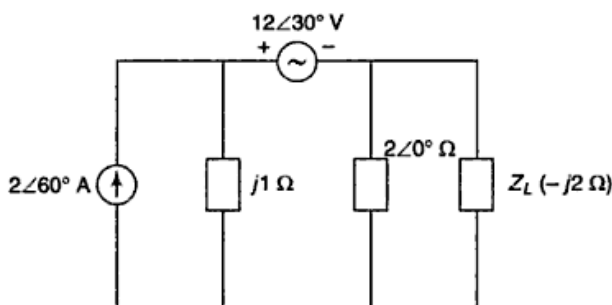


Fig. 6.27 Circuit of Ex. 6.26

Solution

Let us open circuit the terminals of Z_L to find the open circuit voltage V_{oc} as shown in Fig. 6.27(a).

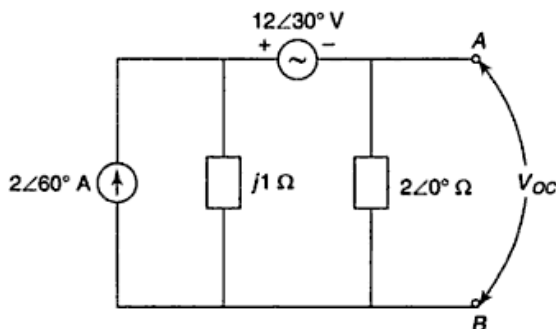


Fig. 6.27(a) Determination of V_{OC}

Current through the 2Ω impedance due to current source only is

$$\begin{aligned}I_1 &= 2\angle 60^\circ \times \frac{j1}{j1 + 2\angle 0^\circ} \\ &= \frac{2\angle 60^\circ \times 1\angle 90^\circ}{2 + j} \\ &= \frac{2\angle 150^\circ}{2.236\angle 26.56^\circ} = 0.89\angle 123.44^\circ \text{ A (from A to B)}.\end{aligned}$$

Current through the 2Ω impedance due to voltage source acting alone is

$$\begin{aligned}I_2 &= \frac{12\angle 30^\circ}{j1 + 2\angle 0^\circ} \\ &= \frac{12\angle 30^\circ}{2.236\angle 26.56^\circ} = 5.367\angle 3.44^\circ \text{ A (from B to A)}.\end{aligned}$$

Applying the superposition theorem current through the $2\ \Omega$ impedance is

$$I = 5.367\angle 3.44^\circ - 0.89\angle 123.44^\circ \\ = 5.86\angle -4.11^\circ\text{ A.}$$

Hence $V_{oc} = 2\angle 0^\circ \times 5.86\angle -4.11^\circ = 11.72\angle -4.11^\circ\text{ V } (= V_{Th})$

Now, Thevenin's equivalent impedance is obtained as

$$Z_{Th} = \frac{j1 \times 2\angle 0^\circ}{j1 + 2\angle 0^\circ} = \frac{2\angle 90^\circ}{2.236\angle 26.56^\circ} = 0.89\angle 63.44^\circ\ \Omega$$

Thevenin's equivalent circuit is shown in Fig. 6.27(b).

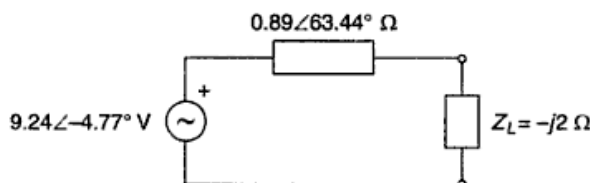


Fig. 6.27(b) Thevenin's equivalent circuit of Ex. 6.26

Hence current through Z_L is obtained as

$$I = \frac{11.72\angle -4.11^\circ}{0.89\angle 63.44^\circ - j2} = 9.243\angle 67.54^\circ\text{ A.}$$

Ex. 6.27. Find the voltage drop across $2\ \Omega$ resistor in the circuit shown in Fig. 6.28 using Thevenin's theorem.

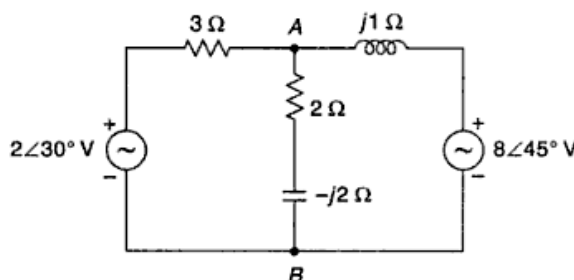


Fig. 6.28 Circuit of Ex. 6.27

Solution

Let us open circuit the terminals AB to find the Thevenin's equivalent voltage as shown in Fig. 6.28(a).

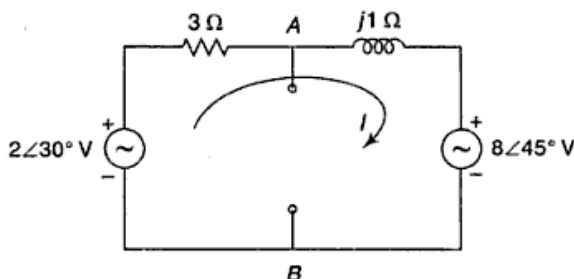


Fig. 6.28(a) Determination (V_{Th})

The current flowing through the circuit is

$$\begin{aligned} I &= \frac{2 \angle 30^\circ - 8 \angle 45^\circ}{3 + j1} \\ &= \frac{-3.925 - j4.65}{3.162 \angle 18.43^\circ} \\ &= \frac{6.09 \angle -130^\circ}{3.162 \angle 18.43^\circ} = 1.92 \angle -148.6^\circ \text{ A.} \end{aligned}$$

$$\begin{aligned} V_{Th} &= \text{Voltage across } V_{AB} \\ &= j1 \times 1.92 \angle -148.6^\circ + 8 \angle 45^\circ \\ &= 1.92 \angle -58.6^\circ + 8 \angle 45^\circ \\ &= 6.657 + j4.02 = 7.77 \angle 31.127^\circ \text{ V} \end{aligned}$$

Thevenin's equivalent impedance is obtained as

$$Z_{Th} = \frac{3 \times j1}{3 + j1} = \frac{3 \angle 90^\circ}{3.162 \angle 18.43^\circ} = 0.9487 \angle 71.57^\circ \Omega.$$

Hence current through 2Ω resistor is

$$\begin{aligned} I_{2\Omega} &= \frac{7.77 \angle 31.127^\circ}{0.9487 \angle 71.57^\circ + 2 - j2} \\ &= \frac{7.77 \angle 31.127^\circ}{2.3 - j1.1} \\ &= \frac{7.77 \angle 31.127^\circ}{2.55 \angle -25.56^\circ} = 3.05 \angle 56.687^\circ \text{ A.} \end{aligned}$$

6.28 Find Thevenin's equivalent circuit across the load in the network shown in Fig. 6.29.

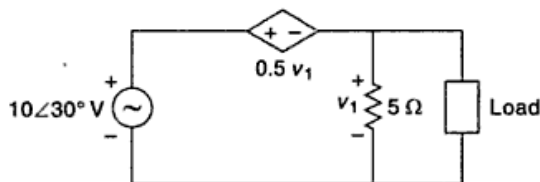


Fig. 6.29 Circuit of Ex. 6.28

Solution

Removing the load it is seen that open circuit voltage $V_{oc} = v_1$ as shown in Fig. 6.29(a).

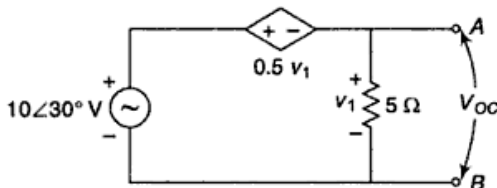


Fig. 6.29(a) Determination of V_{oc}

Applying KVL

$$10 \angle 30^\circ - 0.5v_1 - v_1 = 0$$

or

$$1.5v_1 = 10 \angle 30^\circ$$

i.e.

$$v_1 = 6.67 \angle 30^\circ \text{ V } (= V_{oc}).$$

Considering loop $CPQE$

$$10\angle 0^\circ - V_o - 0.5 V_o = 0$$

or $V_o = 6.67\angle 0^\circ \text{ V}$

$\therefore V_{Th} = V_{oc} = 6.67\angle 0^\circ \text{ V}$.

Next, terminals AB is short circuited as shown in Fig. 6.30(a).

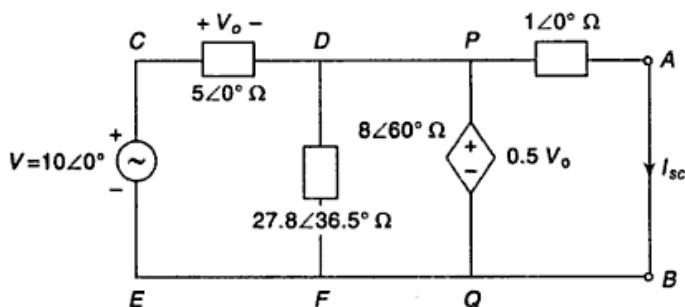


Fig. 6.30(a) Determination of (I_{sc}) and (Z_{in})

Applying KVL in loop $CABE$, we get

$$10\angle 0^\circ - 6.67\angle 0^\circ - 1\angle 0^\circ \times I_{sc} = 0$$

i.e. $I_{sc} = 3.33 \text{ A}$.

Hence internal impedance of the circuit is obtained as

$$Z_{in} = \frac{V_o}{I_{sc}} = \frac{6.67\angle 0^\circ}{3.33} = 2 \Omega.$$

Thevenin's equivalent network is shown in Fig. 6.30(b).

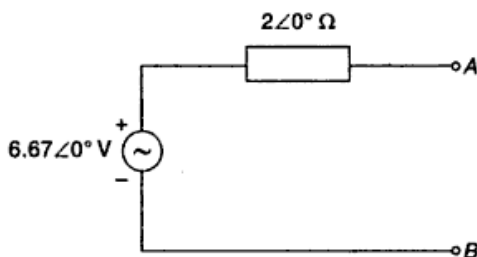


Fig. 6.30(b) Thevenin's equivalent circuit of Ex. 6.29

6.30 Find the current through 10Ω resistor shown in Fig. 6.31 using Norton's theorem.

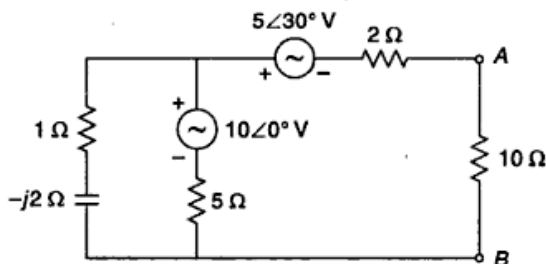


Fig. 6.31 Circuit of Ex. 6.30

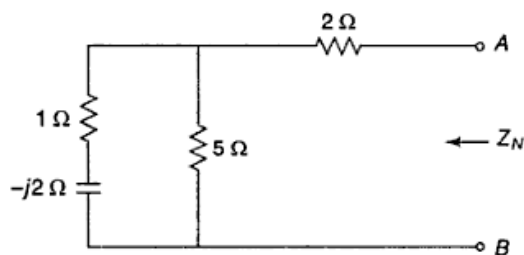


Fig. 6.31(b) Determination of (Z_N)

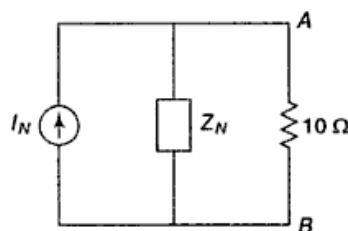


Fig. 6.31(c) Norton's equivalent circuit of Ex. 6.30

Hence current through the $10\ \Omega$ resistor

$$\begin{aligned}
 &= 1.53\angle -91.05^\circ \times \frac{3.48\angle -21^\circ}{10 + 3.48\angle -21^\circ} \\
 &= 1.53\angle -91.05^\circ \times \frac{3.48\angle -21^\circ}{13.3\angle -5.39^\circ} \\
 &= 0.4\angle -106.66^\circ\text{ A.}
 \end{aligned}$$

6.31 Find Norton's equivalent circuit across terminals AB for the network shown in Fig. 6.32.

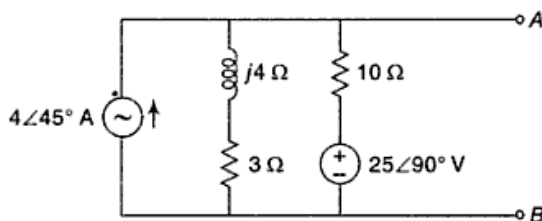


Fig. 6.32 Circuit of Ex. 6.31

Solution

Short circuiting the terminals AB , Norton's equivalent current is found out from Fig. 6.32(a).

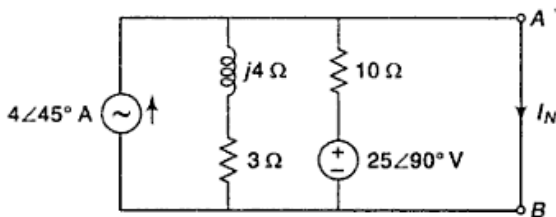


Fig. 6.32(a) Determination of (I_N)

$$\begin{aligned}
 I_N &= 4\angle 45^\circ + \frac{25\angle 90^\circ}{10} \\
 &= 4\angle 45^\circ + 2.5\angle 90^\circ = 2.83 + j5.328 = 6\angle 62^\circ\text{ A.}
 \end{aligned}$$

Removing the sources and looking into the network from terminals AB , Norton's equivalent impedance is obtained from Fig. 6.32(b).

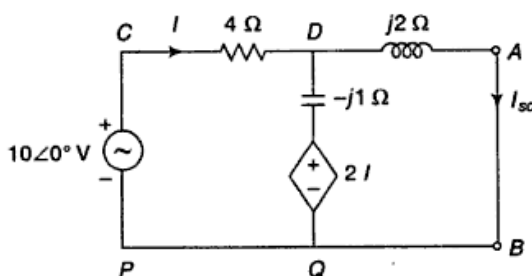


Fig. 6.33(a) Determination of (I_{sc})

Solving the two equations (1) and (2), we get

$$10\angle 0^\circ - I(6 - j) - (2 - j)I = 0$$

$$8I = 10\angle 0^\circ$$

$$I = 1.25\angle 0^\circ \text{ A.}$$

$$\therefore I_{sc} = \frac{2 - j}{j} 1.25\angle 0^\circ = \frac{2.236 \times 1.25}{\angle 90^\circ} \angle -26.56^\circ = 2.79\angle -116.56^\circ \text{ A.}$$

$$\text{Hence, } Z_{int} = \frac{3.67\angle -17^\circ}{2.79\angle -116.56^\circ} = 1.315\angle 99.56^\circ \Omega.$$

Norton's equivalent circuit is shown in Fig. 6.33(b).

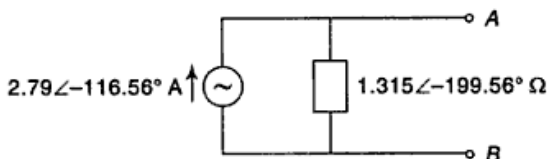


Fig. 6.33(b) Norton's equivalent circuit of Ex. 6.32

6.33 Obtain Norton's equivalent circuit across terminals xy in Fig. 6.34.

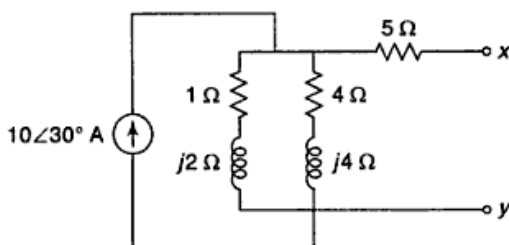


Fig. 6.34 Circuit of Ex. 6.33



Solution

Let us short circuit the terminals xy to find the short circuit current from Fig. 6.34(a). The combined impedance of $(1 + j2) \Omega$ and $(4 + j4) \Omega$ in parallel gives

$$\frac{(1 + j2)(4 + j4)}{5 + j6} = \frac{12.649\angle 108.43^\circ}{7.81\angle 50.19^\circ} = 1.62\angle 58.24^\circ \Omega.$$


$$\text{Hence } I_{sc} = 10\angle 30^\circ \times \frac{1.62\angle 58.24^\circ}{5 + 1.62\angle 58.24^\circ} = 10\angle 30^\circ \times \frac{1.62\angle 58.24^\circ}{6\angle 13.245^\circ} = 2.7\angle 75^\circ \text{ A.}$$

Now removing the source and open circuiting terminals xy , (Z_{int}) is obtained from Fig. 6.34(b).

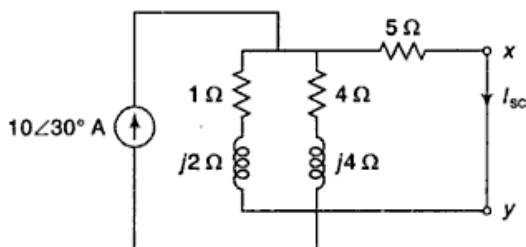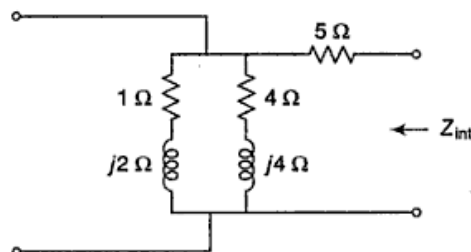Fig. 6.34(a) Determination of (I_{sc})Fig. 6.34(b) Determination of (Z_{int})

Here,
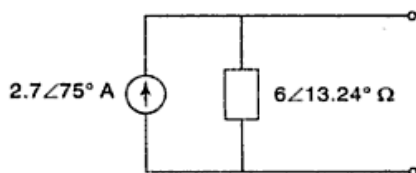
$$\begin{aligned} Z_{int} &= 5 + \frac{(1 + j2)(4 + j4)}{1 + j2 + 4 + j4} \\ &= 5 + 1.62 \angle 58.24^\circ \\ &= 5.853 + j1.377 \\ &= 6 \angle 13.24^\circ \Omega. \end{aligned}$$



Norton's equivalent circuit is shown in Fig. 6.34(c)

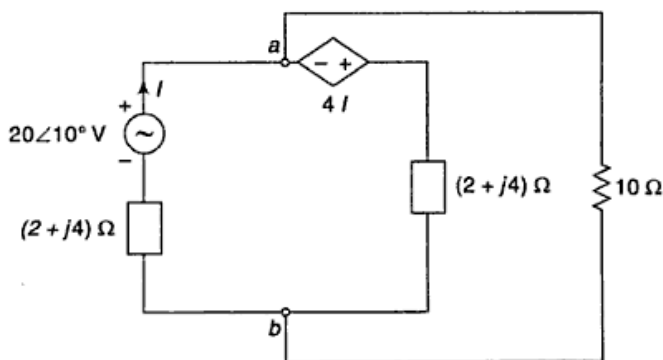
Fig. 6.34(c) Norton's equivalent circuit of Ex. 6.33
.....**6.34** Find Norton's equivalent circuit across terminals ab and find current through $10\ \Omega$ resistor in Fig. 6.35.

Fig. 6.35 Circuit of Ex. 6.34

SolutionLet us remove $10\ \Omega$ resistor and find out the open circuit voltage from Fig. 6.35(a).

Applying KVL in the closed loop

$$\begin{aligned} 20 \angle 10^\circ + 4I - (2 + j4)I - (2 + j4)I &= 0 \\ j8I &= 20 \angle 10^\circ \end{aligned}$$

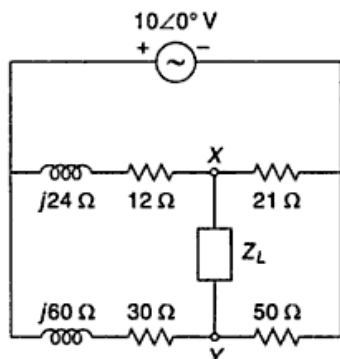
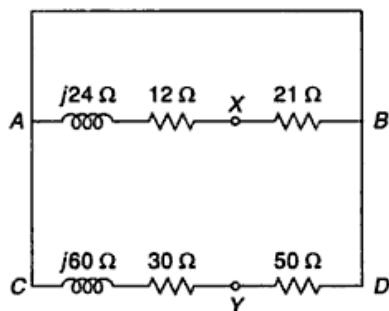


Fig. 6.36 Circuit of Ex. 6.35

Fig. 6.36(a) Determination of (Z_{int})

The internal impedance of the circuit

$$\begin{aligned}
 Z_{int} &= \frac{21(12 + j24)}{21 + j24 + 12} + \frac{50(30 + j60)}{50 + 30 + j60} \\
 &= \frac{252 + j504}{33 + j24} + \frac{1500 + j3000}{80 + j60} \\
 &= \frac{563.489 \angle 63.43^\circ}{40.8 \angle 36^\circ} + \frac{3354 \angle 63.43^\circ}{100 \angle 36.87^\circ} \\
 &= 13.81 \angle 27.43^\circ + 33.54 \angle 26.56^\circ \\
 &= (42.258 + j21.36) \Omega.
 \end{aligned}$$

According to maximum power transfer theorem (Z_L) should be complex conjugate of Z_{int} .

Hence, $Z_L = (42.258 - j21.36) \Omega$.

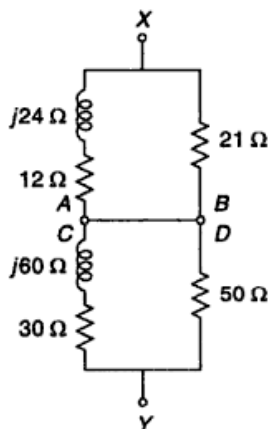


Fig. 6.36(b) Simplified circuit of Ex. 6.36(a)

EXERCISES

1. State and prove maximum power transfer theorem when applied to ac circuits.
2. State and explain Thevenin's theorem when applied to ac circuits.
3. State and explain Norton's theorem when applied to ac circuits.
4. State and explain the superposition theorem when applied to ac circuits.
5. Find current I in Fig. 6.37 using superposition theorem.

[Ans: $3.33 \angle 50^\circ$ A]

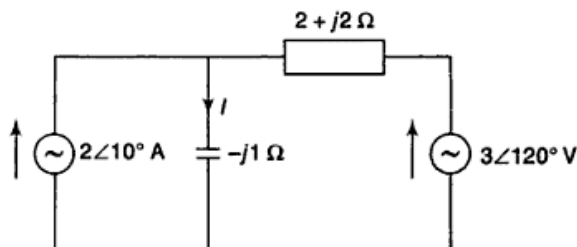


Fig. 6.37

6. Find the power loss in R_L in Fig. 6.38 using superposition theorem. [Ans: 35 W]

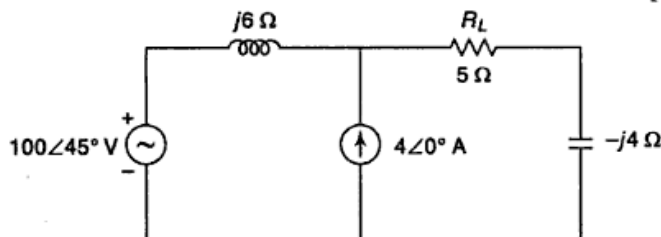


Fig. 6.38

7. Use Thevenin's theorem to find the current in the impedance connected to terminals x and y of the network shown in Fig. 6.39. [Ans: 15.42 A]

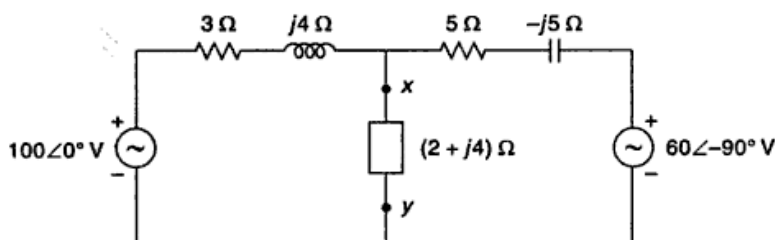


Fig. 6.39

8. Find the amount of maximum power transfer in Fig. E6.40 when Z_L is variable. [Ans: 1.81 W]

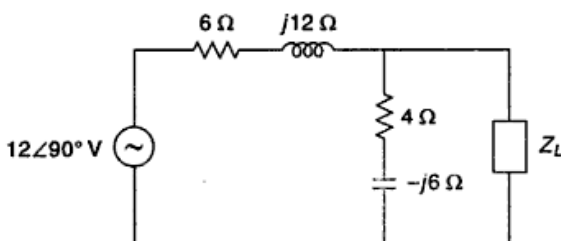


Fig. 6.40

9. In the network of Fig. 6.41 find Norton's equivalent circuit across AB . [Ans: $I_N = 5.78\angle20.22^\circ$ A, $Z_N = (2.08 + j1.44) \Omega$]

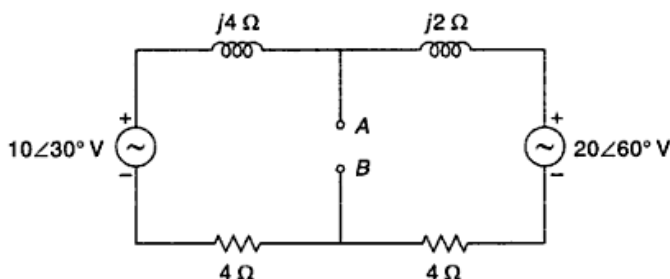


Fig. 6.41

10. Using the superposition theorem find the current through Z_3 in the network shown in Fig. 6.42. [Ans: $47.6\angle-9.7^\circ$ mA]

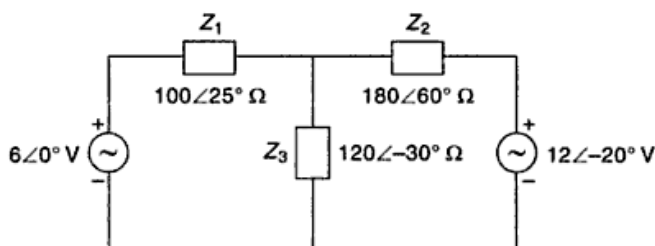


Fig. 6.42

11. Solve example number 6.7 in the text using Thevenin's theorem.
 12. A voltage source has an equivalent circuit consisting of $R = 500\ \Omega$ in series with $C = 0.01\ \mu\text{F}$. Calculate the required component values for a series LR circuit that will draw maximum power from the source when the signal frequency is 1 MHz. [Ans: $R = 500\ \Omega$, $L = 0.00253\ \text{mH}$]
 13. Replace the network of Fig. 6.43 at terminals (a-b) with the Norton's equivalent circuit. [Ans: $I_N = 0.439\angle105.26^\circ$ A, $Z_N = 8.37\angle-69.23^\circ\ \Omega$]

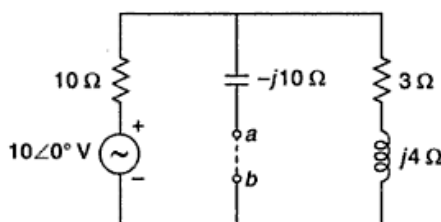


Fig. 6.43

14. Obtain Thevenin's and Norton's equivalent circuits at terminals (a-b) for the network of Fig. 6.44. [Ans: $V_{Th} = 11.5\angle-95.8^\circ$ V, $I_N = 1.39\angle-80.6^\circ$ A, $Z = 8.26\angle-15.2^\circ\ \Omega$]

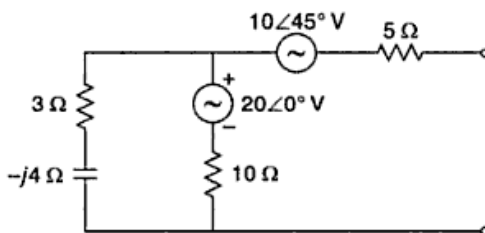


Fig. 6.44



THREE-PHASE CIRCUITS

7.1 THREE-PHASE SYSTEM

A three-phase electric system may be considered as three separate single-phase systems displaced from each other by 120° [Fig. 7.1].

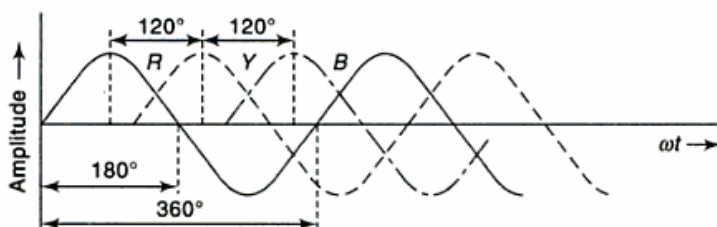


Fig. 7.1 Graphical representation of a three-phase system

7.2 ADVANTAGES OF A THREE-PHASE SYSTEM

The advantages of a three-phase system over a single-phase system are:

- (a) The amount of conductor material required is less for three-phase system,
- (b) domestic power and industrial/commercial power can be provided from the same source,
- (c) voltage regulation of a three-phase system is better, and
- (d) three-phase motors are self-starting while single-phase motors are not self-starting.

7.3 GENERATION OF A THREE-PHASE SUPPLY

When three identical coils are placed with their axes at 120° displaced from each other and rotated in a uniform magnetic field, a sinusoidal voltage is generated across the coil. Figure 7.2 shows three sets of coils RR' , YY' and BB' displaced from each other by 120° and rotating in an anticlockwise direction with angular

velocity ω in a uniform magnetic field. Since the three coils are identical the generated voltages have the same magnitude. The generated voltages in the coils are given by

$$\begin{aligned}v_R &= V_m \sin \omega t \\v_Y &= V_m \sin (\omega t - 120^\circ) \\v_B &= V_m \sin (\omega t - 240^\circ) \\&= V_m \sin (\omega t + 120^\circ).\end{aligned}$$

[Here voltage generated in coil R is taken as reference. So v_Y lags v_R by 120° and v_B lags v_R by 240° .]

In polar form

$$\begin{aligned}v_R &= |V| \angle 0^\circ \\v_Y &= |V| \angle -120^\circ \\v_B &= |V| \angle -240^\circ = |V| \angle 120^\circ.\end{aligned}$$

The three phases may be numbered a, b, c or $1, 2, 3$ or R, Y and B as customary and they may be given three colours—red, yellow and blue. The phase sequence is usually RYB . Vector rotation is usually anticlockwise.

The voltage waveform is shown in Fig. 7.1 and the phasor diagram is shown in Fig. 7.3. It can be shown that the phasor sum of three-phase emfs is zero.*

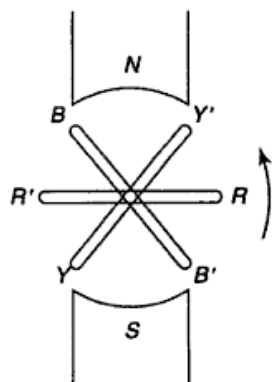


Fig. 7.2 Three-phase emf generation

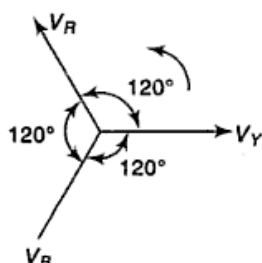


Fig. 7.3 Vector representation of phase voltages

7.4 INTERCONNECTION OF PHASES

If the three coils RR' , YY' and BB' are not interconnected but kept separate as shown in Fig. 7.4 then each phase would require two conductors and so the total number of conductors would be six. This would make the whole system complicated. Hence the three phases are usually interconnected which results in substantial saving of copper.

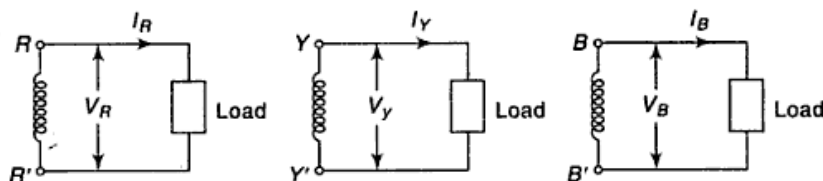


Fig. 7.4 Three-phase coils not interconnected

*Resultant instantaneous emf

$$\begin{aligned}&= v_R + v_Y + v_B = V_m \sin \omega t + V_m \sin (\omega t - 120^\circ) + V_m \sin (\omega t - 240^\circ) \\&= V_m [\sin \omega t + 2 \sin (\omega t - 180^\circ) \cos 60^\circ] \\&= V_m [\sin \omega t - 2 \sin \omega t \times \frac{1}{2}] = 0.\end{aligned}$$

The general methods of interconnections are

- Star (or Y) connection
- Mesh or delta (Δ) connection.

7.4.1 Star (or Y) Connection

Here the similar ends of the coils, i.e. either a, b and c are joined together (or a', b' and c' are joined together) at point N known as "neutral" point or star point. In Fig. 7.5 a conductor is connected at point N which is known as the *neutral conductor*. Such a system is known as a *three-phase four wire system*.

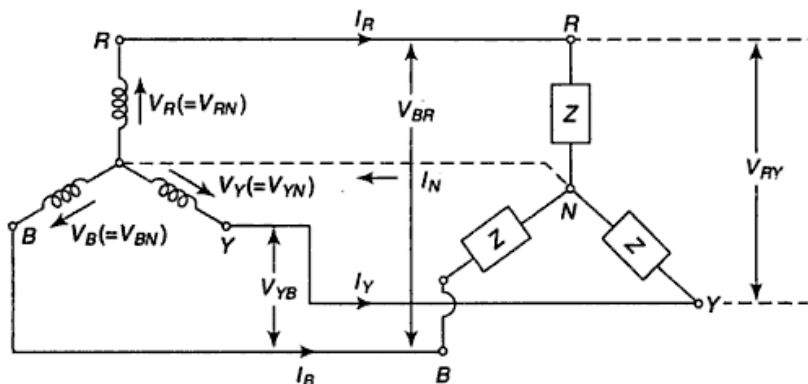


Fig. 7.5 Diagrammatic view of star connection

If a balanced symmetrical load Z is connected across terminals RY, YB and BR then the currents in each phase will be exactly equal in magnitude but displaced 120° from each other (provided the supply voltage is balanced).

The resultant current is then given by

$$i_R + i_Y + i_B = I_m \sin \omega t + I_m \sin (\omega t - 120^\circ) + I_m \sin (\omega t - 240^\circ).$$

The current through the neutral in case of balanced load is zero

$$\text{i.e. } I_N = I_R + I_Y + I_B = 0.$$

The potential difference between any terminal and neutral gives the *phase voltage* and that between any two line terminals, i.e. R, Y, B gives the *line voltage*. In Fig. 7.5, V_R, V_Y and V_B are phase voltages of phases R, Y and B respectively while V_{RY}, V_{YB} and V_{BR} are the line voltages. If these voltages are equal in magnitude and displaced from each other by 120° (elect.) then they are called balanced voltages.

Relation between line and phase voltages in star connection: The potential difference between lines R and Y is

$$V_{RY} = V_R - V_Y \text{ (vector difference).}$$

V_{RY} can be found by compounding V_R and V_Y (reversed). Its value is given by the diagonal of the parallelogram of Fig. 7.6. Obviously, the angle between V_R and V_Y (reversed) is 60° .

Assuming $|V_R| = |V_Y| = |V_B| = |V_{ph}|$ (the phase emf),

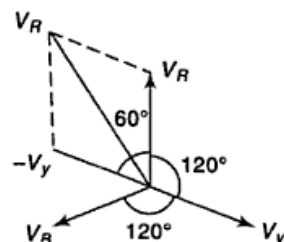


Fig. 7.6 Vectorial addition of phase voltages

$$|V_{RY}| = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \cos 60^\circ} = \sqrt{V_{Ph}^2 + V_{Ph}^2 + 2V_{Ph}^2 \times \frac{1}{2}}$$

$$= \sqrt{3} V_{Ph} \text{ (i.e., } \sqrt{3} \text{ times magnitude of } V_{Ph}\text{).}$$

Similarly, $V_{YB} = V_Y - V_B$ (vector difference)

$$= \sqrt{3} V_{Ph} \text{ and}$$

$$V_{BR} = V_B - V_R = \sqrt{3} V_{Ph}.$$

However, $|V_{RY}| = |V_{YB}| = |V_{BR}| = \text{Line voltage } |V_L|.$

Hence in star connection

$$|V_L| = \sqrt{3} |V_{Ph}|. \quad (7.1)$$

It may be noted from Fig. 7.7 that

- Line voltages are also 120° apart.
- Line voltages are 30° ahead of their respective phase voltages.
- The angle between the line currents and the corresponding line voltages is $(30^\circ + \theta)$ assuming current lagging by an angle θ° (for lagging loads)

Relation between line and phase currents in star connection: Observation of Fig. 7.5 reveals that each line is in series with its individual phase winding. Hence the line current in each line is the same as the current in the phase winding to which the line is connected.

Let current in line R be I_R , current in line Y be I_Y and current in line B be I_B .

Since $|I_R| = |I_Y| = |I_B| = |I_{Ph}|$ (say phase current), in star connection, *line current is same as the phase current* i.e. $|I_L| = |I_{Ph}|$.

Power in star connection: The total active or real power P in the circuit is the sum of the three phase powers. Hence total active power

$$P = 3 \times \text{individual phase power} = 3V_{Ph}I_{Ph} \cos \theta$$

$$= 3 \times \frac{V_L}{\sqrt{3}} I_L \cos \theta$$

$$= \sqrt{3} V_L I_L \cos \theta \quad [\because V_L = \sqrt{3} V_{Ph} \text{ and } I_L = I_{Ph}]. \quad (7.2)$$

It should be noted that θ is the angle between phase voltage and phase current and V_L, I_L are magnitude vectors.

$$\text{Similarly, total reactive power } Q \text{ is given by } Q = \sqrt{3} V_L I_L \sin \theta \quad (7.3)$$

[By convention reactive power of an inductive coil is taken as positive and that of a capacitor as negative]

S , the total apparent power or complex power of the three phases is

$$S = \sqrt{P^2 + Q^2} = \sqrt{3} V_L I_L. \quad (7.4)$$

Also,

$$S = P + jQ. \quad (7.4(a))$$

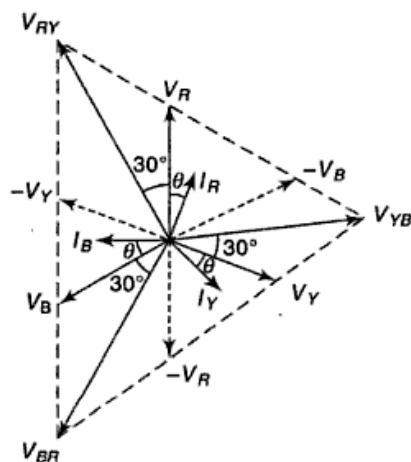


Fig. 7.7 Complete vector diagram for voltages in star connection

7.4.2 Delta (Δ) or Mesh Connection

In this configuration, the dissimilar ends of three phase windings are joined together, i.e. R is joined with Y' , Y with B' and B with R' (or R is joined with B' , B with Y' and Y with R'). In other words, the three windings are joined in series to form a closed mesh as shown in Fig. 7.8. The leads are taken out from the three junctions for external connection. If the system is balanced then the sum of the three voltages round the closed mesh is zero, hence no current (of fundamental frequency) can flow around the mesh when the terminals are open. At any instant, the emf of one phase is equal and opposite to the resultant of those in the other two phases. This type of connection is referred to as a three-phase, three-wire delta connection.

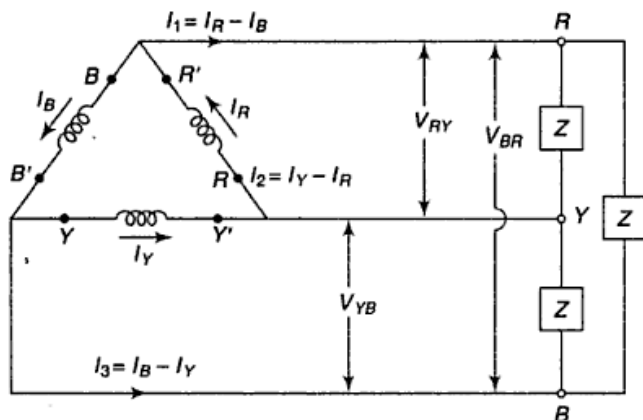


Fig. 7.8 Delta connection

Relation between Line Voltages and Phase Voltages in Delta Connection It is seen from Fig. 7.8 that there is only one phase winding completely included between any pair of terminals. Hence in Δ connection, the voltage between any pair of lines is equal to the corresponding phase voltage. Since the common phase sequence is RYB , V_{RY} leads V_{YB} by 120° , V_{YB} leads V_{BR} by 120° (as shown in Fig. 7.9).

If $|V_{RY}| = |V_{YB}| = |V_{BR}| = \text{line voltage } |V_L|$, then it is seen that $|V_L| = |V_{Ph}|$.

Relation between line currents and phase currents in delta connection It is seen from Fig. 7.8 that current in each line is the vector difference of the two-phase currents flowing through that line (i.e. vector difference of corresponding phase currents).

Hence,
$$\left. \begin{array}{l} \text{Current in line } R \text{ is } I_1 = I_R - I_B \\ \text{Current in line } Y \text{ is } I_2 = I_Y - I_R \\ \text{Current in line } B \text{ is } I_3 = I_B - I_Y \end{array} \right\} \text{vector difference}$$

Current in line R is found by compounding I_R and I_B (reversed) and its value is given by the diagonal of the parallelogram shown in Fig. 7.9. The angle between I_R and I_B (reversed) is 60° .

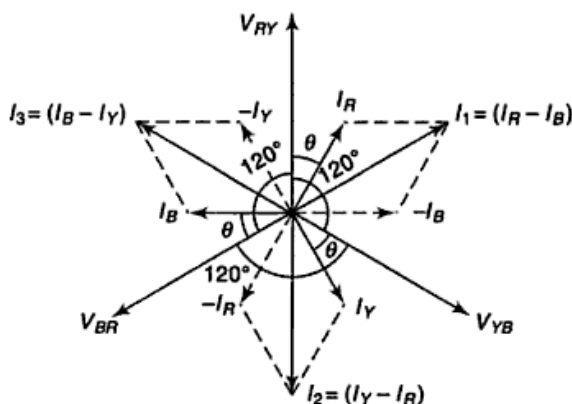


Fig. 7.9 Vector resolution of currents

The current in line R is: $I_1 = \sqrt{I_R^2 + I_B^2 + 2 I_R I_B \cos 60^\circ}$
 $= \sqrt{I_{Ph}^2 + I_{Ph}^2 + 2 I_{Ph}^2 \times \frac{1}{2}}$
 $= \sqrt{3} I_{Ph}$ (i.e., $\sqrt{3}$ times magnitude of phase current).

Current in line Y is: $I_2 = I_Y - I_R$ (vector difference) $= \sqrt{3} I_{Ph}$ and current in line B is: $I_3 = I_B - I_Y$ (vector difference) $= \sqrt{3} I_{Ph}$.

Assuming all the line currents are equal in magnitude,

$$[|I_1| = |I_2| = |I_3| = |I_L|] \quad I_L = \sqrt{3} I_{Ph} \quad (7.5)$$

With reference to Fig. 7.9 it should be noted that:

- line currents are 120° apart
- line currents are 30° behind the respective phase currents
- the angle between the line currents and corresponding line voltages is $(30^\circ + \theta)$ with the current lagging by an angle θ .

Power in Delta Connection

Three-phase power

$$\begin{aligned} P &= 3 \times \text{individual phase powers} \\ &= 3 V_{Ph} I_{Ph} \cos \theta \\ &= 3 V_L \frac{I_L}{\sqrt{3}} \cos \theta = \sqrt{3} V_L I_L \cos \theta \end{aligned} \quad (7.6)$$

$$(\because V_{Ph} = V_L \text{ and } I_L = \sqrt{3} I_{Ph})$$

[Here, V_{Ph} , I_{Ph} , V_L and I_L are magnitude of the respective phasors.]

Similarly, the total reactive power is given by

$$Q = \sqrt{3} V_L I_L \sin \theta \quad (7.7)$$

and the total apparent or complex power of the 3-phase delta circuit is given by

$$S = \sqrt{P^2 + Q^2} = \sqrt{3} V_L I_L \quad (7.8)$$

$$\text{Also,} \quad S = P + jQ \quad [7.8(a)]$$

7.5 ONE LINE EQUIVALENT CIRCUIT FOR BALANCED LOADS

We know that a set of three equal impedances in delta connection is equivalent to another set of three equal star connected impedances. Therefore, a more direct computation of the star circuit is possible for balanced three phase loads of either type.

The one line equivalent circuit is one phase of the three phase, four wire, star connected circuit in Fig. 7.10 except that a voltage is used which has the line to neutral magnitude and a zero phase angle. The line current calculated for this circuit has a phase angle with respect to the phase angle of zero on the voltage. Then the actual line currents I_R , I_Y and I_B will lead or lag their respective line to neutral voltages by this same phase angle.

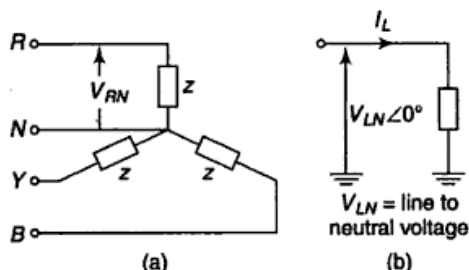


Fig. 7.10 One line equivalent of one phase

7.1 Three chokes each of resistance $40\ \Omega$ and reactance $30\ \Omega$ are connected in star to a 3-phase 440 V balanced supply. What is the line current and the total power dissipated?

Solution

Given, Resistance $R = 40\ \Omega$
Reactance $X = 30\ \Omega$.

\therefore impedance $Z = \sqrt{R^2 + X^2} = \sqrt{(40)^2 + (30)^2} = 50\ \Omega$

Also, line voltage $V_L = 440\ \text{V}$.

\therefore In a star connected system

Phase voltage $|V_{Ph}| = \frac{|V_L|}{\sqrt{3}} = \frac{440}{\sqrt{3}} = 254.04\ \text{V}$:

phase current $|I_{Ph}| = \frac{|V_{Ph}|}{|Z|} = \frac{254.04}{50} = 5.08\ \text{A}$.

In a star connected system

Line current = Phase current = 5.08 A.

Total power dissipated is $(\sqrt{3} |V_L| |I_L| \cos \theta)$, where

$$\cos \theta = \text{power factor} = \frac{|R|}{|Z|} = \frac{40}{50} = 0.8.$$

Hence total power dissipated is $(\sqrt{3} \times 440 \times 5.08 \times 0.8) = 3097.18\ \text{W}$ or $3.097\ \text{kW}$.

7.2 The load in each branch of a star connected three-phase circuit consists of $10\ \Omega$ resistance and 0.06 H inductance in series. The line voltage is 430 V . Calculate the phase voltage and the phase current.

Solution

Resistance $R = 10\ \Omega$

Reactance $X = \omega L = 2\pi fL = 2\pi \times 50 \times .06 = 18.85\ \Omega$

\therefore Impedance $|Z| = \sqrt{R^2 + X^2} = \sqrt{(10)^2 + (18.85)^2} = 21.34\ \Omega$

Line voltage $|V_L| = 430\text{ V}$ (given).

In a star connected system, line voltage $= \sqrt{3} \times$ phase voltage

So phase voltage $|V_{Ph}| = \frac{|V_L|}{\sqrt{3}} = \frac{430}{\sqrt{3}} = 248.27\text{ V}$

Phase current $I_{Ph} = \frac{|V_{Ph}|}{Z} = \frac{248.27}{21.34} = 11.63\text{ A}.$

7.3 Three similar coils each having series resistance of $20\ \Omega$ and capacitance $100\ \mu\text{F}$ are connected in star to a 3-phase, 400 V , 50 Hz balanced supply. Find the line current, power factor, total KVA and total kW.

Solution

Resistance $R = 20\ \Omega$

Capacitance $C = 100 \times 10^{-6}\text{ F}.$

\therefore Capacitive reactance $|X_C| = \frac{1}{\omega C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = \frac{100}{\pi}$
 $= 31.83\ \Omega.$

Impedance $|Z| = \sqrt{R^2 + X_c^2}$
 $= \sqrt{(20)^2 + (31.82)^2} = 37.59\ \Omega.$

Line voltage $|V_L| = 400\text{ V}$ (given)

\therefore Phase voltage is $|V_{Ph}| = \frac{|V_L|}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.95\text{ V},$

while, phase current $I_{Ph} = \frac{|V_{Ph}|}{Z} = \frac{230.95}{37.59} = 6.144\text{ A}.$

\therefore Line current $I_L = I_{Ph} = 6.144\text{ A}$

Power factor $(\cos \theta) = \frac{R}{|Z|} = \frac{20}{37.59} = 0.53$

Total power (KVA) $= 3|V_{Ph}| I_{Ph} = (3 \times 230.95 \times 6.144 \times 10^{-3})\text{ KVA}$
 $= 4.257\text{ KVA}$

Total active power (kW) $= 3|V_{Ph}| I_{Ph} \cos \theta$
 $= (3 \times 230.95 \times 6.144 \times 0.53 \times 10^{-3})\text{ kW} = 2.256\text{ kW}.$

7.4 Each phase of a delta connected load comprises a resistor of $50\ \Omega$ and a series capacitor of $50\ \mu\text{F}$. Calculate the line and phase currents when the load is connected to a 440 V , 3 phase, 50 Hz supply.

Solution

Load resistance $R = 50\ \Omega$

$$\text{Capacitive reactance } |X_C| = \frac{1}{\omega C} = \frac{1}{2\pi fc} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} \\ = 63.67 \, \Omega.$$

$$\therefore \text{Load impedance per phase } |Z| = \sqrt{R^2 + X_C^2} = 80.96 \, \Omega.$$

$$\text{Phase current } |I_{ph}| = \frac{|V_{ph}|}{|Z|}, \text{ where } V_{ph} \text{ is the phase voltage.}$$

In delta connected system line voltage $|V_L|$ = phase voltage $|V_{ph}|$

$$\text{Here, } |V_{ph}| = |V_L| = 440 \, \text{V}$$

$$\text{Therefore, } |I_{ph}| = \frac{440}{80.96} = 5.434 \, \text{A.}$$

$$\text{In delta connected system line current } |I_L| = \sqrt{3} I_{ph}$$

$$\therefore |I_L| = \sqrt{3} \times 5.434 = 9.412 \, \text{A.}$$

7.5 The load in each branch of a delta connected balanced three-phase circuit consists of an inductance of 0.0318 H in series with a resistance of 10 Ω . The line voltage is 400 V (balanced) at 50 Hz. Calculate the (i) line current and (ii) the total power in the circuit.

Solution

$$\text{Inductive reactance } |X_L| = \omega L = 2\pi fL = 2\pi \times 50 \times 0.0318 = 10 \, \Omega$$

$$\text{Resistance } R = 10 \, \Omega.$$

$$\text{So load impedance, } |Z| = \sqrt{(10)^2 + (10)^2} = 14.14 \, \Omega.$$

$$\text{Line voltage, } |V_L| = 400 \, \text{V (given)}$$

$$\therefore \text{Phase voltage } |V_{ph}| = |V_L| = 400 \, \text{V} \quad [\because \text{connection is delta}]$$

$$\text{Phase current } |I_{ph}| = \frac{|V_{ph}|}{|Z|} = \frac{400}{14.14} \, \text{A} = 28.288 \, \text{A.}$$

$$(i) \text{ Line current } |I_L| = \sqrt{3} \times \text{phase current} = \sqrt{3} \times 28.29 = 49 \, \text{A.}$$

$$(ii) \text{ Total power in the circuit } (P) = \sqrt{3} |V_L| |I_L| \cos \theta$$

$$\therefore \cos \theta = \text{power factor} = \frac{R}{|Z|} = \frac{10}{14.14} = 0.707.$$

Also, total power in the circuit

$$(P) = \sqrt{3} \times 400 \times 49 \times 0.707 = 24,000.37 \, \text{W} = 24 \, \text{kW.}$$

7.6 A star connected three-phase load draws a current of 20 A at a lagging p.f. of 0.9 from a balanced 440 V, 50 Hz supply. Find the circuit elements in each phase if the elements are connected in series.

Solution

$$\text{Line current, } |I_L| = 20 \, \text{A}$$

$$\text{Power factor, } \cos \theta = 0.9 \text{ (lagging)}$$

$$\text{Line voltage } = |V_L| = 440 \, \text{V (given).}$$

$$\therefore \text{Phase voltage, } |V_{ph}| = \frac{|V_L|}{\sqrt{3}} = \frac{440}{\sqrt{3}} \, \text{V.}$$

As the power factor is lagging hence the circuit contains resistance R in series with inductance L .

$$\text{If } X_L \text{ be the inductive reactance and } Z \text{ be the impedance then, } \frac{R}{|Z|} = 0.9$$

and
$$|Z| = \frac{|V_{ph}|}{|I_{ph}|} = \frac{\frac{440}{\sqrt{3}}}{|I_L|} = \frac{440}{\sqrt{3} \times 20} \Omega = 12.7 \Omega$$

$\therefore R = 12.7 \times 0.9 = 11.43 \Omega$

and
$$|X_L| = \sqrt{Z^2 - R^2} = \sqrt{(12.7)^2 - (11.43)^2} = 5.536 \Omega$$

Therefore,
$$L = \frac{X_L}{\omega} = \frac{5.536}{2\pi f} = \frac{5.536}{2\pi \times 50} = 0.0176 \text{ H.}$$

The circuit elements are resistance of 11.43Ω and inductor of 0.0176 H connected in series in each phase.

7.7 Three coils are connected in star to a balanced three-phase, 3-wire, 440 V , 50 Hz supply and takes a line current of 10 A at 0.9 p.f. lagging. Calculate the resistance and reactance of the coils assuming they are series connected in each phase. If the coils are delta connected to the same supply calculate the line current and the real power.

Solution

Line voltage $|V_L| = 440 \text{ V}$

Line current $|I_L| = 10 \text{ A}$

When the coils are star connected,

phase voltage $|V_{ph}| = \frac{|V_L|}{\sqrt{3}} = \frac{440}{\sqrt{3}} = 254 \text{ V,}$

phase current $|I_{ph}| = |I_L| = 10 \text{ A}$

If R , X and Z be the resistance, reactance and impedance respectively then,

$$|Z| = \frac{|V_{ph}|}{|I_{ph}|} = \frac{254}{10} = 25.4 \Omega$$

$$\text{p.f.} = \cos \theta = 0.9 = \frac{|R|}{|Z|}$$

So $R = 25.4 \times 0.9 = 22.86 \Omega.$

Therefore,
$$|X| = \sqrt{Z^2 - R^2} = \sqrt{(25.4)^2 - (22.86)^2} = 11.19 \Omega.$$

The resistance and reactance of the coil are 22.86Ω and 11.9Ω respectively.

Line voltage of supply system $|V_{L_1}| = \sqrt{3} |V_{ph_1}|$
 $= \sqrt{3} \times 230 \text{ V}$
 $= 398.36 \text{ V (as it is star connected).}$

Line voltage of load $|V_{L_2}| = |V_{L_1}| = 398.36 \text{ V}$

and phase voltage of load $|V_{ph_2}| = |V_{L_2}| = 398.36 \text{ V (as load is delta connected).}$

Hence phase current in load is given by $|I_{ph_2}| = \frac{|V_{ph_2}|}{Z}$
 $= \frac{398.36}{10} = 39.8 \text{ A.}$

Line current of load is obtained as $|I_{L_2}| = \sqrt{3} |I_{ph_2}|$
 $= \sqrt{3} \times 39.836 = 69 \text{ A.}$

$$\text{Also, } W_1' - W_2' = \frac{(W_1' + W_2') \tan \theta}{\sqrt{3}} = \frac{200 \times 0.75}{\sqrt{3}} \text{ kW} = 86.6 \text{ kW}$$

From above we get

$$W_1' = 143.3 \text{ kW and } W_2' = 56.7 \text{ kW.}$$

The readings of two wattmeters when the power factor of the motor is 0.75 leading are 143.3 kW and 56.7 kW.

7.17 The input power to a three-phase motor was measured by two wattmeters whose readings were 12 kW and -4 kW and the line voltage was 200 V. Calculate the power factor and the line current.

Solution

$$W_1 = 12 \text{ kW} \quad W_2 = -4 \text{ kW}$$

$$\text{Line voltage } |V_L| = 200 \text{ V}$$

If θ be the power factor angle then

$$\tan \theta = \sqrt{3} \frac{W_1 - W_2}{W_1 + W_2} = \sqrt{3} \frac{12 - (-4)}{12 + (-4)} = \sqrt{3} \times \frac{16}{8} = 3.464.$$

$$\text{So, power factor} = \cos \theta = \cos(\tan^{-1} 3.464) = 0.277.$$

$$\text{Now, } \sqrt{3} |V_L| |I_L| \cos \theta = W_1 + W_2 = 12 + (-4) = 8 \text{ kW} = 8000 \text{ W}$$

where I_L is the line current.

$$\text{So, } |I_L| = \frac{8000}{\sqrt{3} \times 200 \times 0.277} = 83.37 \text{ A.}$$

.....

7.18 Three coils each having resistance of 10Ω and series reactance of 10Ω are connected in star across a 400 V, three-phase line. Calculate the line current and readings on the two wattmeters which are connected to measure the total power.

Solution

$$R = 10 \Omega, X = 10 \Omega, \text{ Impedance } |Z| = \sqrt{R^2 + X^2} = 14.14 \Omega$$

$$\text{Power factor } \cos \theta = \frac{|R|}{|Z|} = \frac{10}{14.14} = 0.707.$$

$$\text{Line voltage } |V_L| = 400 \text{ V, phase voltage } |V_{ph}| = \frac{|V_L|}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 \text{ V.}$$

$$\text{Phase current} = \frac{|V_{ph}|}{|Z|} = \frac{230.94}{14.14} = 16.33 \text{ A.}$$

$$\text{Line current } |I_L| = \text{phase current} = 16.33 \text{ A.}$$

If W_1 and W_2 are the readings of the two wattmeters then

$$\begin{aligned} W_1 + W_2 &= \sqrt{3} |V_L| |I_L| \cos \theta \\ &= \sqrt{3} \times 400 \times 16.33 \times 0.707 = 7999 \text{ W} = 8 \text{ kW} \end{aligned}$$

$$\begin{aligned} \text{and } W_1 - W_2 &= |V_L| |I_L| \sin \theta = 400 \times 16.33 \sin(\cos^{-1} 0.707) \\ &= 4619.5 \text{ W} = 4.62 \text{ kW} \end{aligned}$$

$$\text{Hence, } W_1 = 6.31 \text{ and } W_2 = 1.69 \text{ kW.}$$

.....

■ ADDITIONAL PROBLEMS ■

7.19 A balanced three-phase delta connected load of 100 kW takes a lagging current of 50 A with a line voltage of 11 kV, 50 Hz. Find the circuit constants of the load per phase.

Solution

$$\text{Total power} = 100 \text{ kW} (= 100,000 \text{ W}).$$

$$\text{Line current } |I_L| = 50 \text{ A}$$

$$\text{Line voltage } |V_L| = 11 \text{ kV} (= 11,000 \text{ V}).$$

As the system is delta connected,

$$\text{phase current } |I_{ph}| = \frac{|I_L|}{\sqrt{3}} = \frac{50}{\sqrt{3}} \text{ A},$$

$$\text{and phase voltage } |V_{ph}| = (|V_L|) = 11,000 \text{ V}$$

$$\text{Impedance per phase } |Z| = \frac{|V_{ph}|}{|I_{ph}|} = \frac{11,000}{50/\sqrt{3}} = 381 \Omega.$$

$$P = \sqrt{3} |V_L| |I_L| \cos \theta = 100,000 \text{ where } (\cos \theta = \text{power factor})$$

$$\text{i.e. } \cos \theta = \frac{10,000}{\sqrt{3} \times 11,000 \times \frac{50}{\sqrt{3}}} = 0.0182.$$

$$\text{Also, } |R|/|Z| = \cos \theta$$

$$\therefore \frac{|R|}{|Z|} = 0.0182, \text{ where } R \text{ is the resistance per phase}$$

$$\text{So, } R = 6.93 \Omega.$$

$$\text{If } (X) \text{ be the reactance per phase then } |X| = \sqrt{Z^2 - R^2} = 380.94 \Omega.$$

$$\begin{aligned} \text{As the current is lagging so the reactance is inductive in nature, i.e. inductance, } L &= \frac{|X|}{\omega} \\ &= \frac{380.94}{2\pi \times 50} = 1.213 \text{ H.} \end{aligned}$$

We have assumed R and L to be series connected in each phase and the circuit constants of the load per phase are 3.99Ω (resistor) and 1.213 H (inductor).

7.20 Three impedances Z_A , Z_B and Z_C are connected in star and are supplied from a 400 V, 50 Hz, three-phase ac source. Determine the line currents. Assume $Z_A = 5\angle 0^\circ \Omega$, $Z_B = 40\angle 30^\circ \Omega$ and $Z_C = 20\angle -30^\circ \Omega$.

Solution

Referring to Fig. 7.17

$$I_A = \frac{V_{AN}}{Z_A} = \frac{(400/\sqrt{3}) \angle 0^\circ}{5 \angle 0^\circ} = 46.19 \angle 0^\circ \text{ A}$$

$$I_B = \frac{V_{BN}}{Z_B} = \frac{(400/\sqrt{3}) \angle -120^\circ}{40 \angle 30^\circ} = 5.77 \angle -150^\circ \text{ A}$$

$$\begin{aligned} I_C &= \frac{V_{CN}}{Z_C} = \frac{(400/\sqrt{3}) \angle -240^\circ}{20 \angle -30^\circ} \\ &= 11.55 \angle -270^\circ \text{ A} = 11.55 \angle 90^\circ \text{ A.} \end{aligned}$$

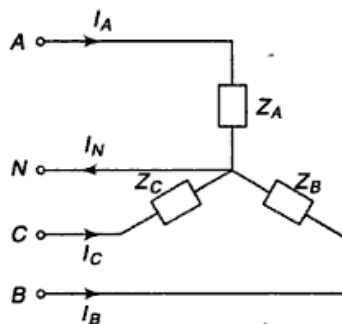


Fig. 7.17 Circuit of Ex. 7.20

7.21 A balanced star connected load with impedances of $2\angle-30^\circ \Omega$ is supplied from a three-phase, 4-wire system, the voltages to neutral being $V_{AN} = 100\angle-90^\circ$, $V_{BN} = 100\angle30^\circ$, $V_{CN} = 100\angle150^\circ$ V. Determine the current in the line conductors and the current in the neutral.

Solution

Referring to Fig. 7.18

$$I_A = \frac{V_{AN}}{Z} = \frac{100\angle-90^\circ}{2\angle-30^\circ} = 50\angle-60^\circ \text{ A}$$

$$I_B = \frac{V_{BN}}{Z} = \frac{100\angle30^\circ}{2\angle-30^\circ} = 50\angle60^\circ \text{ A}$$

$$I_C = \frac{V_{CN}}{Z} = \frac{100\angle150^\circ}{2\angle-30^\circ} = 50\angle180^\circ \text{ A.}$$

$$I_N = (I_A + I_B + I_C) = 50(\angle-60^\circ + \angle60^\circ + \angle180^\circ) \\ = 50(0.5 - j0.866 + 0.5 + j0.866 - 1) = 0 \text{ A.}$$

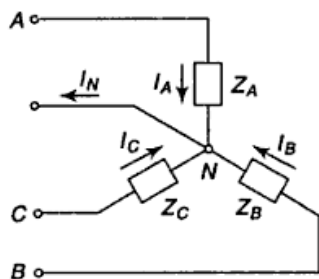


Fig. 7.18 Circuit of Ex. 7.21

7.22 In a three-phase four-wire power distribution system phase B is open while currents through phase R and Y are $100\angle-30^\circ$ and $50\angle60^\circ$. Find the current through the neutral connection.

Solution

The three-phase four-wire system is a star connected system with a neutral wire.

$$I_R = 100\angle-30^\circ \text{ A}$$

$$I_Y = 50\angle60^\circ \text{ A.}$$

As B phase is open

$$I_B = 0$$

Neutral current

$$I_N = (I_R + I_Y + I_B) \\ = (100\angle-30^\circ + 50\angle60^\circ) \\ = (86.6 - j50 + 25 + j43.3) \\ = +111.6 - j6.67 = 111.8\angle-3.414^\circ \text{ A.}$$

7.23 Figure 7.18 shows a three-phase load connected in star. Here $I_A = 20\angle100^\circ$ A and $I_B = 10\angle-50^\circ$ A. Find the voltage drops across the three impedances of Z_A , Z_B and Z_C where $Z_A = 6\angle0^\circ$, $Z_B = 6\angle30^\circ$ and $Z_C = 5\angle45^\circ$. Assume phasor sum of I_A , I_B and I_C as zero.

Solution

$$I_A = 20\angle100^\circ \text{ A}$$

$$I_B = 10\angle-50^\circ \text{ A.}$$

\therefore

$$I_A + I_B + I_C = 0,$$

$$I_C = -(I_A + I_B) = -(20\angle100^\circ + 10\angle-50^\circ) \\ = -(-3.47 + j19.69 + 6.43 - j7.66) \\ = (-2.96 - j12.03) = 12.38\angle76.18^\circ \text{ A.}$$

Voltage drop across

$$Z_A = I_A Z_A = 20\angle100^\circ \times 6\angle0^\circ = 120\angle100^\circ \text{ V.}$$

Voltage drop across

$$Z_B = I_B Z_B = 10\angle-50^\circ \times 6\angle30^\circ = 60\angle-20^\circ \text{ V.}$$

Voltage drop across

$$Z_C = I_C Z_C = 12.38\angle76.18^\circ \times 5\angle45^\circ = 61.9\angle121.18^\circ \text{ V.}$$

7.24 The input power to a three-phase motor was measured by the two wattmeter method. The readings were 5.2 kW and 1.7 kW, the latter reading has been obtained after reversal

of current coil connections. The line voltage was 400 V. Calculate (a) the real power (b) the power factor and (c) the line current.

Solution

$$W_1 = 5.2 \text{ kW} = 5200 \text{ W and } W_2 = 1.7 \text{ kW} = 1700 \text{ W.}$$

As the reading of W_2 has been obtained after reversal of current coil so $W_2 = -1700 \text{ W}$.

Line voltage (given) $|V_L| = 400 \text{ V}$

(a) Total power = $W_1 + W_2 = (5200 - 1700) \text{ W} = 3500 \text{ W} = 3.5 \text{ kW}$.

(b) If θ be the power factor angle then

$$\tan \theta = \sqrt{3} \frac{W_1 - W_2}{W_1 + W_2} = \sqrt{3} \frac{5200 + 1700}{5200 - 1700} = \sqrt{3} \frac{6900}{3500} = 3.414$$

\therefore Power factor

$$(\cos \theta) = \cos(\tan^{-1} 3.414) = 0.28.$$

(c) Total power = $W_1 + W_2 = \sqrt{3} |V_L| |I_L| \cos \theta$, where I_L is the line current.

$$\therefore |I_L| = \frac{W_1 + W_2}{\sqrt{3} V_L \cos \theta} = \frac{3500}{\sqrt{3} \times 400 \times .28} = 18 \text{ A.}$$

7.25 Three impedances each of resistance 10Ω and series inductive reactance of 5Ω are connected in (i) star (ii) in delta across a 3 phase 400 V supply. Find the line current in each case and the total power.

Solution

$$|R| = 10 \Omega, |X| = 5 \Omega, \text{ so impedance } |Z| = \sqrt{R^2 + X^2} = \sqrt{10^2 + 5^2} = 11.18 \Omega.$$

Line voltage $|V_L| = 400 \text{ V}$.

$$\text{Power factor } \cos \theta = \frac{|R|}{|Z|} = \frac{10}{11.18} = 0.89.$$

(i) In star connection

$$\text{Phase voltage } |V_{Ph}| = \frac{|V_L|}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.95 \text{ V}$$

$$\text{and phase current } |I_{Ph}| = \frac{|V_{Ph}|}{|Z|} = \frac{230.95}{11.18} = 20.66 \text{ A.}$$

\therefore Line current $|I_L| = \text{phase current} = 20.66 \text{ A}$.

$$\text{Total power} = \sqrt{3} |V_L| |I_L| \cos \theta = \sqrt{3} \times 400 \times 20.66 \times .89 = 12739.16 \text{ W} = 12.74 \text{ kW}$$

(ii) In delta connection

Phase voltage $|V_{Ph}| = |V_L| = 400 \text{ V}$

$$\text{So phase current } |I_{Ph}| = \frac{|V_{Ph}|}{|Z|} = \frac{400}{11.18} = 35.78 \text{ A and}$$

$$\text{line current } |I_L| = \sqrt{3} |I_{Ph}| = \sqrt{3} \times 35.78 = 61.97 \text{ A}$$

$$\text{Total power} = \sqrt{3} |V_L| |I_L| \cos \theta = \sqrt{3} \times 400 \times 61.97 \times .89 = 38211.33 \text{ W} = 38.21 \text{ kW}$$

It may be noted here that the arm impedances being same, a delta load consumes more real power than the equivalent star load.

7.26 A three-phase balanced voltage of 230 V is applied to a balanced delta connected load consisting of thirty 40 W lamps connected in parallel in each phase. Calculate the phase and line currents, phase voltages, power consumption of all lamps.

Solution

Line voltage $|V_L|$ = Phase voltage $|V_{Ph}| = 230$ V (\because the load is delta connected)

$$\therefore |V_{Ph}| = 230 \text{ V}$$

Power consumption of each lamp = 40 W.

$$\therefore \text{Total power consumption is } 30 \times 40 = 1200 \text{ W}$$

If I_{Ph} be the phase current

$$|V_{Ph}| |I_{Ph}| = 1200 \text{ W}$$

$$\text{Hence } I_{Ph} = \frac{1200}{230} = 5.2 \text{ A.}$$

$$\text{Line current} = \sqrt{3} I_{Ph} = \sqrt{3} \times 5.2 \text{ A} = 9 \text{ A.}$$

$$\text{Power consumption of all lamps} = 3 \times 1200 \text{ W} = 3600 \text{ W} = 3.6 \text{ kW.}$$

.....

7.27 The load connected to a three-phase supply contains three similar impedances connected in star. The line currents are 50 A and the KVA and kW inputs are 50 and 27 respectively. Find the line and phase voltages, KVAR input and the resistance and reactance of each coil.

Solution

$$\text{Line current } |I_L| = 50 \text{ A}$$

$$\text{KVA} = 50 \text{ and kW} = 27$$

$$\therefore \text{KVAR} = \sqrt{\text{KVA}^2 - \text{KW}^2} = \sqrt{(50)^2 - (27)^2} = 42.$$

As the load is star connected

$$\text{Phase current } |I_{Ph}| = |I_L| = 50 \text{ A.}$$

If V_L be the line voltage and $\cos \theta$ be the power factor then

$$\sqrt{3} |V_L| |I_L| \cos \theta = 27 \times 10^3$$

$$\text{or } \cos \theta = \frac{27000}{\sqrt{3} \times V_L I_L}$$

$$\text{and } \sqrt{3} |V_L| |I_L| \sin \theta = 42 \times 10^3$$

$$\text{or } \sin \theta = \frac{42000}{\sqrt{3} V_L I_L}$$

$$\therefore \tan \theta = \frac{42}{27} = \frac{X}{R},$$

where X and R are the reactance and resistance of the load.

$$\text{or } X = 1.56 R.$$

$$\text{Again } \sqrt{3} |V_L| |I_L| = 50 \times 10^3$$

$$\text{or, } |V_L| = \frac{50 \times 10^3}{\sqrt{3} \times 50} = 577.35 \text{ V}$$

$$\text{Phase voltage } |V_{Ph}| = \frac{|V_L|}{\sqrt{3}} = \frac{577.35}{\sqrt{3}} = 333.33 \text{ V}$$

If Z is the impedance per phase then

$$|Z| = \frac{|V_{Ph}|}{|I_{Ph}|} = \frac{333.35}{50} \Omega = 6.67 \Omega$$

$$\text{or } R^2 + X^2 = (6.67)^2 = 44.49$$

$$\text{or } R^2 + (1.56 R)^2 = 44.49$$

$$\text{Hence } R = 3.6 \Omega$$

$$\text{and } X = 1.56 R = 1.56 \times 3.6 = 5.62 \Omega.$$

$$\begin{aligned}
 Q &= \sqrt{3} |V_L| |I_L| \sin \phi \\
 &= \sqrt{3} \times 200 \times 23.094 \times \sin (\cos^{-1} 0.6) = 6399.99 \text{ VAR.} \\
 \therefore |S| &= \sqrt{P^2 + Q^2} = \sqrt{(4800)^2 + (6399.99)^2} = 7999.99 \text{ VA } (\approx 8 \text{ KVA}).
 \end{aligned}$$

7.37 A 440 V, three-phase, 50 Hz balanced source supplies electrical energy to the following three phase balanced loads:

- A 200 HP, three-phase 50 Hz induction motor operating at 94% efficiency and 0.88 p.f. (lag).
- A 50 kW three-phase electric heating element.
- A mixed load of 40 kW (three-phase) operating at 0.7 lagging p.f.

Obtain

- the total load in kW supplied by source
- the total KVAR supplied by the source
- the total apparent power
- the line current.

Solution

(a) *Real power*

$$(i) \text{ For motor: } P_M = \frac{\text{HP} \times 746}{\text{Efficiency}} = \frac{200 \times 746}{0.94} \times 10^{-3} = 158.72 \text{ kW}$$

$$(ii) \text{ For heater: } P_H = 50 \text{ kW.}$$

$$(iii) \text{ For mixed load: } P_X = 40 \text{ kW.}$$

$$\therefore \text{ Total real power supplied} = 158.72 + 50 + 40 \\ = 248.72 \text{ kW (3-phase).}$$

$$(b) \text{ For motor: } \phi_m = \cos^{-1} 0.88 = 28.36^\circ$$

$$\text{However, } \tan \phi_m = \frac{Q_m}{P_m} \quad [Q_m = \text{reactive power input to motor} \\ P_m = \text{real power input to motor}]$$

$$\text{or } Q_M = P_m \tan \phi_m = 158.72 \tan 28.36^\circ = 85.68 \text{ KVAR.}$$

$$\text{For heating load, } \phi_H = 0 \text{ [as heater is a pure resistive load]}$$

$$\text{Hence } Q_H = 0$$

For mixed load:

$$\phi_X = \cos^{-1}(0.70) = 45.57^\circ \text{ (lag)}$$

$$\therefore Q_X = P_X \tan \phi_X = 40 \tan 45.57^\circ = 40.81 \text{ KVAR.}$$

Thus we find total KVAR supplied

$$(Q) = 85.68 + 0 + 40.81 = 126.49 \text{ KVAR}$$

(c) Total apparent power $|S|$ is given by

$$|S| = \sqrt{P^2 + Q^2} = \sqrt{248.72^2 + 126.49^2} = 279.04 \text{ KVA}$$

$$\text{and } \phi = \tan^{-1} \frac{Q}{P} = \tan^{-1} \frac{126.49}{248.72} = 26.96^\circ \text{ (lag).}$$

$$(d) \therefore |S| = \sqrt{3} |V_L| |I_L|$$

$$\therefore |I_L| = \frac{|S|}{\sqrt{3} |V_L|} = \frac{279.04 \times 10^3}{\sqrt{3} \times 440} = 366.15 \text{ A.}$$

7.38 Two wattmeters measure the three-phase power of a load and read 80 and 50 kW (for W_1 and W_2 respectively). Find the total complex power and the power factor. Also find the total power and reactive power.

Solution

$$P = W_1 + W_2 = 80 + 50 = 130 \text{ kW}$$

$$\tan \phi = \sqrt{3} \frac{W_2 - W_1}{W_2 + W_1} = \sqrt{3} \frac{50 - 80}{80 + 50} = -0.4$$

$$\therefore \phi = -21.78^\circ \text{ and P.F. } (\cos \phi) = 0.9286 \text{ (lag)}$$

Since real power = (total power) $\times \cos \phi$,

We can write,

$$\text{Complex power } (S) = \frac{P}{\cos \phi} = \frac{130}{0.9286} = 140 \text{ KVA.}$$

Reactive power (Q) is obtained as

$$Q = \sqrt{S^2 - P^2} = \sqrt{(140)^2 - (130)^2} = 52 \text{ KVAR.}$$

.....

7.39 A three phase induction motor, operating from a 400 V, 50 Hz supply, takes 25 A. The power factor of the motor is poor and found to be 0.5 lagging. If the two wattmeter method is used to measure the three-phase power supplied to the motor, what would each wattmeter read?

Solution

The connection diagram is shown in Fig. 7.21 while the phasor diagram in Fig. 7.22. Here, $\phi = \cos^{-1}(0.5) = 60^\circ$ (lagging)

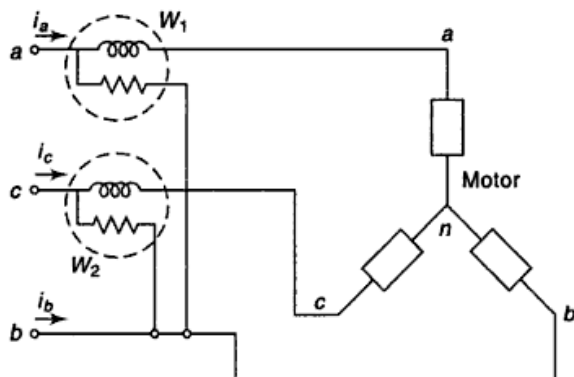


Fig. 7.21 Power measurement for the system in Ex. 7.39

[Voltage across $W_1 = V_{a-c} (= \bar{V}_a - \bar{V}_c)$; V_{ac} is lagging I_a by $(30^\circ - \phi)$. Then the reading of W_1 is $V_{ac} I_a \cos (30^\circ - \phi)$. Similarly, $W_2 = V_{L} I_L \cos (30^\circ - \phi)$.

$$W_1 = V_L I_L \cos (\phi + 30^\circ)$$

$$\begin{aligned} [\text{Actually } W_1 &= V_L I_L \cos (30^\circ - \phi) \\ &= V_L I_L \cos (30^\circ - (-\phi)) \\ &= V_L I_L \cos (30^\circ + \phi)] \end{aligned}$$

$$= 400 \times 25 \times \cos (60^\circ + 30^\circ) = 0.$$

$$W_2 = V_L I_L \cos (\theta - 30^\circ)$$

$$\begin{aligned} [\because W_2 &= V_L I_L \cos (30^\circ + \phi) \\ &= V_L I_L \cos (30^\circ - \phi)] \end{aligned}$$

$$= 400 \times 25 \times \cos (60^\circ - 30^\circ)$$

$$= 8.66 \text{ kW.}$$

Thus, W_1 will read zero while W_2 will read 8.66 kW.

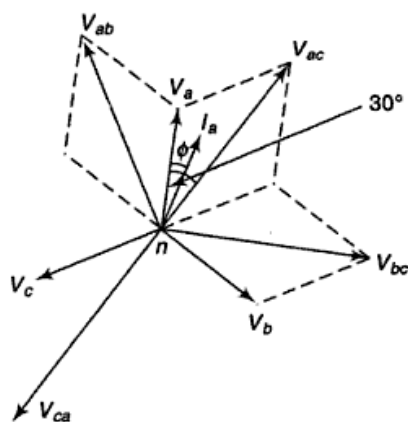


Fig. 7.22 Phasor diagram of Ex. 7.39

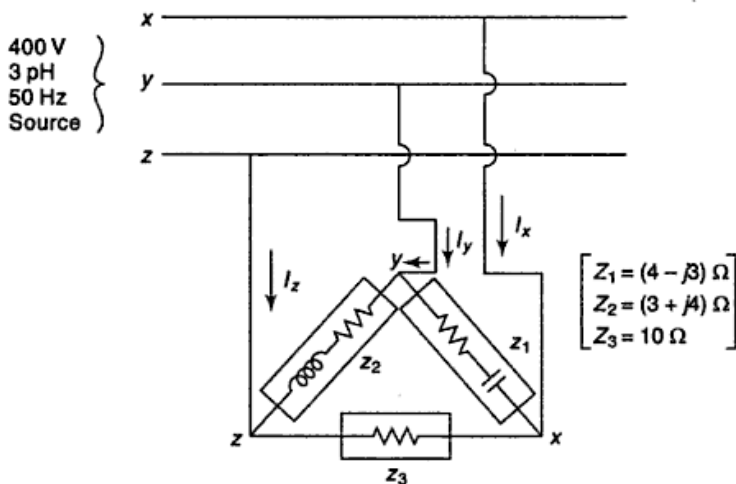


Fig. 7.24 Circuit of Ex. 7.41

$$I_{yz} = \frac{V_{y-z}}{Z_2} = \frac{400 \angle -120^\circ}{(3 + j4)} = 80 \angle -173.13^\circ \text{ A}$$

$$I_{zx} = \frac{V_{z-x}}{Z_3} = \frac{400 \angle +120^\circ}{10 \angle 0^\circ} = 40 \angle -120^\circ \text{ A}$$

We can calculate the active power consumed as follows.

$$P = I_{xy}^2 \times 4 + I_{yz}^2 \times 3 + I_{zx}^2 \times 10$$

or
$$P = 80^2 \times 4 + 80^2 \times 3 + 40^2 \times 10 = 60.8 \text{ kW}.$$

Also, the reactive power can be obtained as

$$Q = I_{xy}^2 \times (-3) + I_{yz}^2 \times (4) + I_{zx}^2 \times 0$$

$$= 80^2 \times (-3) + 80^2 \times 4 = 6.4 \text{ KVAR}.$$

[We can also calculate P and Q as follows:

$$P = V_{XY} I_{XY} \cos \left(\tan^{-1} \frac{3}{4} \right) + V_{YZ} I_{YZ} \cos \left(\tan^{-1} \frac{4}{3} \right) + V_{ZX} I_{ZX} \cos 0^\circ$$

$$= 400 \times 80 \times \cos 36.87^\circ + 400 \times 80 \times \cos 53.13^\circ + 400 \times 40$$

$$= 25600 + 19200 + 16000 = 60.8 \text{ kW}$$

$$Q = V_{XY} I_{XY} \sin (-36.87^\circ) + V_{YZ} I_{YZ} \sin 53.13^\circ + V_{ZX} I_{ZX} \sin 0^\circ$$

$$= -19200 + 25600 = 6.4 \text{ KVAR}.$$

.....

7.42 A 1000 HP 6000 V 50 Hz three-phase induction motor operates at an efficiency of 95% at p.f. of 0.85 (lag). Assuming the motor operating at rated load, find the input real and reactive power of the motor. Obtain the value of line current taken by the motor. If a 350 KVAR capacitor bank is installed parallel to the motor, find the new line current and new p.f.

Solution

$$P_{\text{out}} = 1000 \text{ HP} = 746 \text{ kW},$$

$$P_{\text{in}} = \frac{P_{\text{out}}}{\eta} = \frac{746}{0.95} = 785 \text{ kW}.$$

Thus input power at rated load of the motor is 785 kW at 0.85 p.f. (lag).

$$\therefore |S_{in}| = \frac{P_{in}}{\cos \phi} = \frac{785}{0.85} = 923.5 \text{ KVA}$$

$$|I_L| = \frac{|S_{in}|}{\sqrt{3} |V_L|} = \frac{923.5 \times 10^3}{\sqrt{3} \times 6000} = 88.87 \text{ A}$$

$$|Q_{in}| = \sqrt{|S_{in}|^2 - P_{in}^2} = \sqrt{(923.5)^2 - (785)^2} = 486.44 \text{ KVAR.}$$

The capacitor bank being installed now in parallel to the motor, we find $Q_C = 350 \text{ KVAR}$ and hence it would supply a part of reactive demand of the load (i.e. 350 KVAR).

The motor would now draw less reactive power from the supply and the new reactive demand is $[(486.44) - 350]$ i.e., 136.44 KVAR.

Obviously, this would reduce the KVA burden on the source. The new KVA demand of the load is

$$|S_{new}| = \sqrt{P_{in}^2 + Q_{new}^2} = \sqrt{785^2 + (136.44)^2} = 796.77 \text{ KVA.}$$

It may be observed that new KVA demand is 796.77 KVA instead of 923.5 KVA.

$$\therefore |I_{L_{new}}| = \frac{|S_{new}|}{\sqrt{3} |V_L|} = \frac{796.77 \times 10^3}{\sqrt{3} \times 6000} = 76.67 \text{ A.}$$

Thus, with installation of 350 KVAR capacitor bank, the line current also reduces from 88.87 A to 76.67 A. This means lesser loss in cable of the supply feeding the motor and lesser power loss in the motor. Installation of capacitor bank also releases the supply of reactive power burden. The new power factor of the system is now

$$\cos \phi = \frac{|P_{3\phi}|}{|S_{new}|} = 0.985 \text{ (lag).}$$

7.43 A balanced 25 kW load operates at 0.85 p.f. (lag) from a 440 V, 50 Hz, three-phase supply. Calculate the total power, line current and reactive power drawn by the load.

Solution

$$|S_{3\phi}| = \frac{P_{3\phi}}{\cos \phi} = \frac{25 \times 10^3}{0.85} = 29.4 \text{ KVA}$$

$$|I_L| = \frac{|S_{3\phi}|}{\sqrt{3} |V_L|} = \frac{29.4 \times 10^3}{\sqrt{3} \times 440} = 38.58 \text{ A}$$

$$\begin{aligned} \text{and } Q_{3\phi} &= \sqrt{3} |V_L| |I_L| \sin \phi \\ &= \sqrt{3} \times 440 \times 38.58 \times \sin (\cos^{-1} 0.85) = 15.49 \text{ KVAR.} \end{aligned}$$

7.44 In the preceding problem, let us intend to improve the power factor of the load from 0.85 lag to 0.98 (lag) while the real power demand remains the same. Obtain the value of capacitive KVAR per phase to be inserted in parallel to the load.

Solution

We obtained earlier, for 0.85 p.f. (lag), $|S_{3\phi}| = 29.4 \text{ KVA}$ while $|Q_{3\phi}|$ is 15.49 KVAR.

However, with improved power factor of 0.98 (lag), the new $|S_{3\phi}|$ would be

$$|S_{3\phi_{new}}| = \frac{P_{3\phi}}{\cos \phi_{new}} = \frac{25 \times 10^3}{0.98} = 25.51 \text{ KVA.}$$

$$\begin{aligned}
 &= \frac{400 \angle 0^\circ}{5 \angle 30^\circ} + \frac{-400 \angle +120^\circ}{10 \angle 0^\circ} \\
 &= 80 \angle -30^\circ - 40 \angle 120^\circ \\
 &= 80(\cos 30^\circ - j \sin 30^\circ) - 40(\cos 120^\circ + j \sin 120^\circ) \\
 &= 69.28 - j40 + 20 - j34.64 \\
 &= (89.28 - j74.64) \text{ A} = 116.37 \angle -39.896^\circ \text{ A.}
 \end{aligned}$$

.....

7.49 In the circuit shown in Fig. 7.27 find I_a .

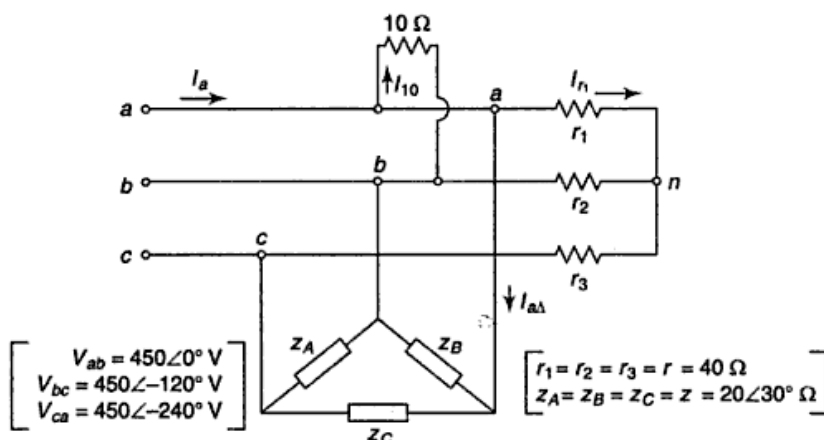


Fig. 7.27 Circuit of Ex. 7.49

Solution

It may be observed that

$$I_a = I_{10} + I_{r_1} + I_{a\Delta} \text{ (phasor sum)}$$

Hence

$$I_{10} = \frac{V_{ab}}{10} = \frac{450 \angle 0^\circ}{10 \angle 0^\circ} = 45 \text{ A with phase lag } 0^\circ$$

$$I_{r_1} = \frac{V_{a-n}}{r_1} = \frac{(450/\sqrt{3}) \angle -30^\circ}{40 \angle 0^\circ} = 6.5 \angle -30^\circ \text{ A.}$$

[\because phase voltage lags by 30° the corresponding line voltage (ref. Fig. 7.28)]

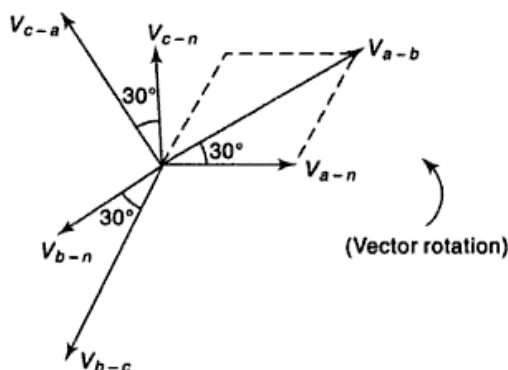


Fig. 7.28 Voltage phasor diagram for Ex. 7.49

Again we see that $I_{a\Delta}$ is phasor sum of currents through Z_B and Z_C in the delta circuit.

$$\begin{aligned}
 \therefore I_{a\Delta} &= \frac{V_{ab}}{Z_B} + \frac{V_{ac}}{Z_C} = \frac{V_{ab}}{Z_B} - \frac{V_{ca}}{Z_C} \\
 &= \frac{450 \angle 0^\circ}{20 \angle 30^\circ} - \frac{450 \angle -240^\circ}{20 \angle 30^\circ} \\
 &= \frac{450 \angle 0^\circ}{20 \angle 30^\circ} - \frac{450 \angle +120^\circ}{20 \angle 30^\circ} \\
 &= 22.5 \angle -30^\circ - 22.5 \angle +90^\circ \\
 &= 22.5 (\cos 30^\circ - j \sin 30^\circ) - 22.5 (\cos 90^\circ + j \sin 90^\circ) \\
 &= 22.5(0.866 - j0.5) - 22.5(0 + j) \\
 &= 19.485 - j11.25 - j22.5 = 19.485 - j33.75 = 38.97 \angle -60^\circ \text{ A} \\
 \therefore I_a &= I_{a0} + I_{r1} + I_{a\Delta} \\
 &= 45 \angle 0^\circ + 6.5 \angle -30^\circ + 38.97 \angle -60^\circ \\
 &= 45 + 5.629 - j3.25 + 19.485 - j33.75 \\
 &= (70.114 - j37) \text{ A} = 79.28 \angle -27.82^\circ \text{ A}
 \end{aligned}$$

7.50 A 2500 HP, star connected three-phase induction motor is connected across a 11 KV (line to line) 50 Hz balanced supply. A delta connected capacitor bank of 400 KVAR is connected across the motor. If the motor produces an output power of 2000 HP at an efficiency of 95% and operates at a power factor of 0.9 (lag), calculate the following:

- The input active and total power to the motor.
- The reactive power input to the motor.
- The reactive power supplied by the source.
- The apparent power supplied by the source.
- The motor line current.
- The impedance of the motor per phase.
- Line current drawn by capacitor bank.

Solution

Rated power of the motor = 2500 HP = $2500 \times 0.746 = 1865 \text{ kW}$,
while the operating power = $2000 \times 0.746 = 1492 \text{ kW}$

$$\therefore \text{Active operating power input } (P_{in}) = \frac{1492}{\text{efficiency}} = \frac{1492}{0.95} = 1570.53 \text{ kW} \quad (i)$$

Total power absorbed by the motor

$$|S_{in}| = \frac{P_{in}}{\cos \phi} = \frac{1492}{0.9} = 1657.78 \text{ KVA} \quad (ii)$$

Reactive power input to the motor is obtained as

$$\begin{aligned}
 Q_{in} &= \sqrt{|S_{in}|^2 - |P_{in}|^2} \\
 &= \sqrt{(1657.78)^2 - (1570.53)^2} = 530.72 \text{ KVAR.} \quad (iii)
 \end{aligned}$$

Since the capacitor bank supplies 400 KVAR hence the source would supply (530.72 - 400) 130.72 KVAR. (iv)

Apparent power supplied by the source is

$$|S| = \sqrt{(1570.53)^2 + (130.72)^2} = 1575.96 \text{ KVA} \quad (v)$$

Motor line current is

$$|I_m| = \frac{|S_{in}|}{\sqrt{3} |V_L|} = \frac{1657.78 \times 10^3}{\sqrt{3} \times 11000} = 87 \text{ A.} \quad (vi)$$

Impedance of motor/phase is obtained as

$$Z_{in(Ph)} = \frac{|V_{ph}|}{|I_{ph}|} = \frac{11000/\sqrt{3}}{87} = 73 \, \Omega. \quad (vii)$$

[\because in star connection $|V_{ph}| = \sqrt{3} |V_L|$ and $|I_{ph}| = |I_L|$]

[Note that this is not static impedance and it changes with motor loading]

The current drawn by the capacitor bank is given by

$$I_C = \frac{Q_c/3}{|V_{ph}|} = \frac{(400/3)10^3}{11000/\sqrt{3}} = 21 \text{ A per phase} \quad (viii)$$

$$\therefore I_{C(line)} = \sqrt{3} \times 21 = 36.36 \text{ A.}$$

Figure 7.29 represents the schematic of the system.

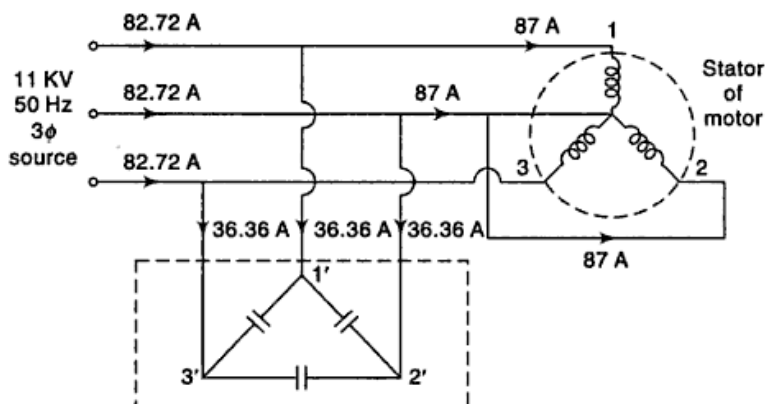


Fig. 7.29 Delta connected capacitor bank (Ex. 7.50)

It may be noted here that it is erroneous if one wishes to add the motor current and the capacitor current algebraically to get the supply current. On the other hand, the addition should be done vectorially. If we want to draw the phasor diagram, we should take care of the location of the respective phasors (ref. Fig. 7.30)

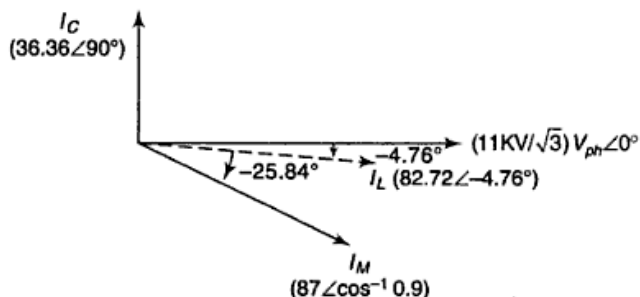


Fig. 7.30 Phasor diagram of system in Fig. 7.29

I_L , the source current can be obtained as

$$|I_L| = \frac{|S|}{\sqrt{3} V_L} = \frac{1575.96}{\sqrt{3} \times 11} = 82.72 \text{ A}$$

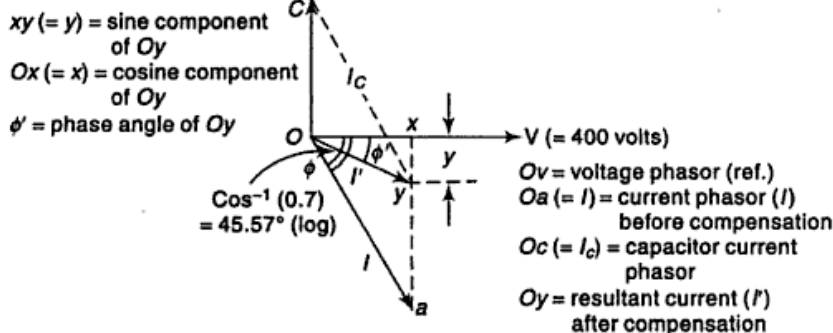


Fig. 7.31(c) Phasor diagram for Ex. 7.51

From 7.31(c), we can write

$$I' (= Oy) = \frac{Ox}{\cos \phi'} = \frac{Oa \cos \phi}{\cos \phi'} = \frac{35.72 \times 0.7}{0.85} = 29.42 \text{ A} \quad [\because \text{p.f. before adding capacitor is 0.7 and after adding capacitor is 0.85}]$$

\therefore The current drawn from the supply is 29.42 A after installation of capacitors at load terminals.

Again, $xy = I' \sin \phi' = 29.42 \times \sin (\cos^{-1} 0.85) = 15.5 \text{ A}$

$\therefore I_c = ay = xa - xy = I \sin \phi - xy = 35.72 \times \sin (\cos^{-1} 0.7) - 15.5 = 10 \text{ A}$

But $|I_c| = \frac{|V|}{|X_C|}$

$$\therefore X_C = \frac{|V|}{|I_c|} = \frac{400}{10} = 40 \Omega \quad [\because \text{capacitors are connected in } \Delta \text{ fashion, hence } |V_L| = |V_{ph}| = 400 \text{ V}]$$

or $\frac{1}{\omega C} = 40$

$$\therefore C = \frac{1}{2 \times \pi \times 50 \times 40} = 79.61 \mu\text{F (for each capacitor.)}$$

7.52 Two three-phase loads, one star and another in delta connection as shown in Fig. 7.32 are connected to a three-phase 400 V, 50 Hz balanced supply. Assuming $Z_1 = 2 \angle 20^\circ \Omega$; $Z_2 = 6 \angle 75^\circ \Omega$; $Z_3 = 30 \angle 50^\circ \Omega$ and $Z_A = 50 \angle 30^\circ \Omega$, $Z_B = 33.33 \angle -60^\circ \Omega$, $Z_C = 17.3 \angle 90^\circ \Omega$, find the current in y-phase. The phase sequence is (r - y - b) (anti-clockwise).

Solution

Let us first see how many loads are connected from phase y. By observation we note that for the Δ load, Z_A is connected across phases (y - r) and Z_B is connected across phases, (y - b). If $I_{y(\Delta)}$ is the line current for Δ -connected load in line y, we can write

$$\begin{aligned}
 I_{y(\Delta)} &= \text{Phasor sum of currents due to load across phases (y - r) and (y - b)} \\
 &= \frac{V_{y-r}}{Z_A} + \frac{V_{y-b}}{Z_B} \\
 &= \frac{-V_{r-y}}{Z_A} + \frac{V_{y-b}}{Z_B} \\
 &= \frac{-400 \angle 0^\circ}{50 \angle 30^\circ} + \frac{400 \angle -120^\circ}{33.33 \angle -60^\circ} = (-8 \angle -30^\circ + 12 \angle -60^\circ) \text{ A}
 \end{aligned}$$

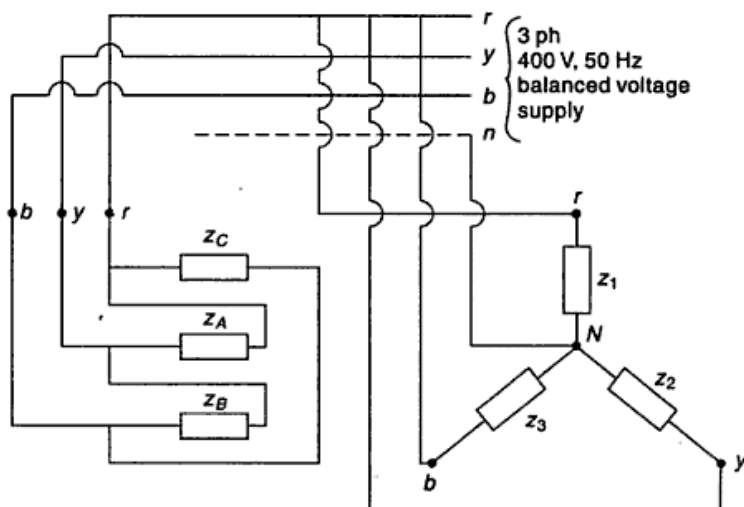


Fig. 7.32 Circuit of Ex. 7.52

It may be noted that line-*y* also supplies star load phase Z_2 for which

$$I_{y(Y)} = \frac{V_{y-n}}{Z_2} = \frac{(400/\sqrt{3}) \angle -150^\circ}{6 \angle 75^\circ} = 38.49 \angle -75^\circ \text{ A.}$$

[$\because V_{r-y} (= 400 \angle 0^\circ)$ is reference phasor and since V_{y-n} will be 120° phase lag than V_{r-n} while V_{r-n} itself lags V_{r-y} by 30° , it is evident that V_{r-n} lags V_{r-y} by 150° .]

$$\begin{aligned} \therefore I_y (\text{line current in } y \text{ phase}) &= I_{y(\Delta)} + I_{y(Y)} \\ &= -8 \angle -30^\circ + 12 \angle -60^\circ + 38.49 \angle -75^\circ \\ &= 31.38 \angle 146.4^\circ \text{ A.} \end{aligned}$$

7.53 A balanced three-phase load consists of impedances $(4 + j3) \Omega$ per phase and is connected to a 400 V source. Assuming V_{1-n} to be the reference phasor calculate the current per phase, power per phase and the total three phase power for a Y-connected load. Repeat the calculation for a Δ -connected load.

Solution

For star (Y) load:

Phase voltages are as follows

$$V_{1-n} \angle 0^\circ, V_{2-n} \angle -120^\circ, V_{3-n} \angle 120^\circ$$

while line voltages would be

$$V_{1-2} \angle 30^\circ, V_{2-3} \angle -90^\circ, V_{3-1} \angle 150^\circ.$$

$$\therefore I_{Ph_1} = \frac{V_{Ph_1}}{Z_{Ph_1}} = \frac{\frac{400}{\sqrt{3}} \angle 0^\circ}{(4 + j3)} = 46.2 \angle -37^\circ \text{ A}$$

Similarly, for phases 2 and 3, the phase currents would be

$$I_{Ph_2} = 46.2 \angle -37^\circ - 120^\circ = 46.2 \angle -157^\circ \text{ A}$$

$$I_{Ph_3} = 46.2 \angle -37^\circ + 120^\circ = 46.2 \angle 83^\circ \text{ A.}$$

The phasor diagram is shown in Fig. 7.33. Since the voltages are balanced, the load and the phase currents are balanced. The line currents for the star connected load will be same to those of phase currents.

We can solve this problem by another method as described below:

Since $I_{RY} \angle \phi_{RY} \times V_{RY} \angle 0^\circ = P_{RY} / \cos \phi_{RY}$

[where ϕ_{RY} is p.f. angle for load connected between (R - Y), which is obviously zero as the load p.f. of load P_{RY} is unity (given). Also, V_{RY} is the reference phasor and P_{RY} is the connected load of 6 kW (L_1). ($P_{RY} / \cos \phi_{RY}$) represents the total power i.e., the VA power]. We can now write,

$$|I_{RY}| = \frac{P_{RY} / \cos \phi}{V_{RY} \angle 0^\circ} = \frac{6000/1}{415 \angle 0^\circ} = 14.458 \text{ A } (= I_1)$$

[Please note that, I_{RY} is the current phasor with magnitude of 14.458 A and angle zero.]

Similarly, for L_2 we can write

$$I_{YB} \angle -\phi_{YB} \times V_{YB} \angle -120^\circ = \frac{P_{YB}}{\cos \phi_{YB}}$$

where ϕ_{YB} is p.f. angle for load L_2 connected between Y and B. V_{YB} is the line voltage (i.e., the phase voltage across the delta load) for line (Y - B) (at 120° lagging angle to V_{RY}).

As per given values, $\phi_{YB} = \cos^{-1}(0.8) = 36.87^\circ$ (lag). It may be noted that I_{YB} lags V_{YB} by 36.87° .

$$\begin{aligned} \therefore I_{YB} (\cos 36.87^\circ - j \sin 36.87^\circ) &= \frac{P_{YB} / \cos \phi_{YB}}{V_{YB} \angle -120^\circ} \\ &= \frac{4500}{0.8 \times 415 \angle -120^\circ} \end{aligned}$$

or $I_{YB} = (-12.464 - j5.324) \text{ A } (= I_2).$

For L_3 we can write

$$I_{BR} \angle +\phi_{BR} \times V_{BR} \angle +120^\circ = \frac{P_{BR}}{\cos \phi_{BR}} \quad [\text{p.f. is 0.5 lead hence } \phi_{BR} \text{ is +ve}]$$

or $I_{BR} \angle 60^\circ = \frac{2700/0.5}{415 \angle +120^\circ}$

$\therefore I_{BR} = 13.012 \angle -180^\circ = 13.012 (\cos 180^\circ - j \sin 180^\circ) = -13.012 \text{ A } (= I_3).$

Thus we have obtained phase currents of the Δ load as

$$I_1 = 14.458 \angle 0^\circ \text{ A } = (14.458 + j0) \text{ A}$$

$$I_2 = (-12.464 - j5.324) \text{ A}$$

$$I_3 = (-13.012 - j0) \text{ A}.$$

The line currents can now be obtained as

$$I_R = I_1 - I_3 = 14.458 + j0 + 13.012 + j0 = 27.47 \text{ A}$$

$$I_Y = I_2 - I_1 = -12.464 - j5.324 - 14.458 - j0 = (-26.922 - j5.324) \text{ A}$$

$$I_B = I_3 - I_2 = (-13.012 - j0 + 12.464 + j5.324) \text{ A} = (-0.548 + j5.324) \text{ A}.$$

EXERCISES

1. A three-phase four wire 208 V, system supplies a star connected load in which $Z_A = 10 \angle 0^\circ \Omega$, $Z_B = 15 \angle 30^\circ \Omega$ and $Z_C = 10 \angle -30^\circ \Omega$. Find the line currents, the neutral current and the load power.

[Ans: $12 \angle 90^\circ \text{ A}$, $8 \angle -60^\circ \text{ A}$, $12 \angle -120^\circ \text{ A}$, $5.69 \angle 69.4^\circ \text{ A}$, 3519 W]

2. Calculate the active and reactive components for the current in each phase of a star connected 5000 V, three-phase alternator supplying 3000 kW at power factor 0.8.

[Ans: 346.2 A , 260 A]

3. Three similar coils of resistance $9\ \Omega$ and reactance $12\ \Omega$ are connected in delta to a three-phase, 440 V , 50 Hz supply. Find the line current, power factor, total KVA and total kW. [Ans: 50.8 A , 0.6 , 38.7 KVA , 23.23 kW]
4. For the unbalanced delta connected load shown in Fig. 7.35 find the phase currents, line currents and the total power consumed by the load.

[Ans: $10\angle-53.8^\circ$, $10\angle-156.5^\circ$,
 $20\angle156.5^\circ$, $29.1\angle-33.2^\circ$,
 $15.73\angle165.3^\circ$,
 $14.94\angle52.3^\circ$ 3000 W]

5. A balanced three-phase load consists of three coils each of resistance $4\ \Omega$ and inductance 0.02 H . Determine the total power when the coils are

(i) star connected and

(ii) delta connected to a 440 V , 3 phase, 50 Hz supply

[Ans: 13.99 kW ; 41.97 kW]

[Hint: $Z = 4 + j(2\pi \times 50 \times 0.02) = (4 + j6.28) = 7.44\angle57.5^\circ\ \Omega$

$$\cos \theta = \frac{R}{Z} = \frac{4}{7.44} = 0.5376.$$

(i) Star connection

$$V_L = 440\text{ V} \therefore V_{Ph} = \frac{440}{\sqrt{3}}\text{ V}$$

$$|I_{Ph}| = \frac{440\sqrt{3}}{7.44} = 34.14\text{ A} = |I_L|$$

$$P = \sqrt{3} |V_L| |I_L| \cos \theta = \sqrt{3} \times 440 \times 34.14 \times 0.5376 = 13987.855\text{ W} = 13.988\text{ kW}.$$

(ii) Delta connection

$$|V_L| = |V_{Ph}| = 440\text{ V}$$

$$|I_{Ph}| = \frac{440}{7.44} = 59.14\text{ A}$$

$$\therefore P = 3 V_{Ph} I_{Ph} \cos \theta = 3 \times 440 \times 59.14 \times 0.5376 = 41967.48\text{ W} = 41.97\text{ kW}.$$

6. Three equal impedances of $(8 + j12)\ \Omega$ are connected in star across 415 V , 3 phase, 50 Hz supply. Calculate (i) line current (ii) Power factor (iii) Active and reactive power drawn by the load.

[Ans: 6629 W ; 9935.28 VAR]

[Hint: $Z = (8 + j12) = 14.42\angle56.32^\circ\ \Omega$

$$|V_L| = 415\text{ V}; |V_{Ph}| = \frac{415}{\sqrt{3}}\text{ V}$$

$$(i) \text{ Line current} = \text{phase current} = \frac{V_{Ph}}{Z} = \frac{\frac{415}{\sqrt{3}}}{14.42}\text{ A} = 16.616\text{ A}.$$

$$(ii) \text{ Power factor } \cos \theta = \frac{R}{Z} = \frac{8}{14.42} = 0.555.$$

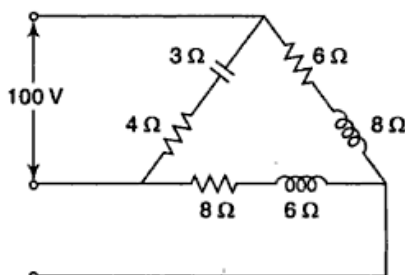


Fig. 7.35

(iii) Active power $\sqrt{3} \times 415 \times 16.616 \times 0.555 = 6628.7 \text{ W}$.

Reactive power $= \sqrt{3} \times 415 \times 16.616 \sin (\cos -10.555)$
 $= 9935.28 \text{ VAR}$

7. In a balanced three-phase system load 1 draws 60 kW and 80 KVA leading while load 2 draws 160 kW and 120 KVAR lagging. If line voltage of the supply is 1000 V find the line current drawn by each load.

[Ans: 57.8 A, 115.5 A]

8. In the network shown in Fig. 7.36 three resistors are connected in star to a three-phase supply of 400 V. The wattmeter W is connected as shown. Calculate the currents in the three lines and the readings of the wattmeter.

[Ans: 15.9 A, 13.1 A, 9.8 A, 5.82 kW]

10. A balanced three-phase star connected load draws 10 kW from a three-phase balanced systems of 400 V, 50 Hz while the line current is 75 A (leading). Find the circuit elements of the load.

[Ans: 0.6 Ω , 1083 μF]

11. An inductive motor draws a three phase power. Two wattmeter method is applied to find the total power. If $W_1 = 10 \text{ kW}$, $W_2 = 5 \text{ kW}$, find the total three phase active power, reactive power and power factor.

[Ans: 15 kW, 8.66 KVAR, 0.866]

12. A delta connected load has following impedances: $Z_{RY} = j10 \Omega$, $Z_{YB} = 10 \angle 0^\circ \Omega$, $Z_{BR} = -j10 \Omega$. If the load is connected across a three phase 100 V supply find the line currents.

[Ans: $8.66 - j5 \text{ A}$, $-5 + j1.34 \text{ A}$, $-3.66 + j3.6 \text{ A}$]

13. The power in a three-phase circuit is measured by two wattmeters. If the total power is 50 kW, power factor being 0.8 leading, what will be the reading of each wattmeter? For what p.f. will one of the wattmeter reading will be zero?

[Ans: 35.825 W, -14.175 W, 0.5]

14. Derive the relation between phase and line voltages and currents for (i) star connected load (ii) delta connected load across a three-phase balanced system.

15. Show that sum of three emf's is zero in a three-phase balanced ac circuit.

16. Show that the power in a three-phase circuit can be measured using 2 wattmeters. Draw the circuit diagram and vector diagram.

17. What are the advantages of a polyphase system over the single-phase system?

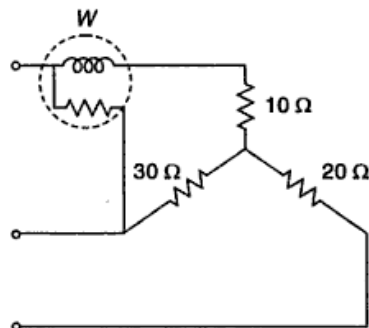


Fig. 7.36



TRANSFORMERS

8.1 DEFINITION

A transformer may be defined as a static electric device that transfers electrical energy from one circuit to another circuit at the same frequency but with changed voltage (or current or both) through a magnetic circuit.

8.2 PRINCIPLE OF OPERATION

When alternating voltage V_1 is applied to the primary winding of a transformer a current (termed as exciting current, I_ϕ) flows through it as shown in Fig. 8.1. The exciting current produces an alternating flux (ϕ) in the core, which links with both the winding (primary and secondary). According to Faraday's laws of electromagnetic induction, the flux will cause self-induced emf E_1 in the primary and mutually induced emf E_2 in the secondary winding. But according to Lenz's law primary induced emf will oppose the applied voltage and in magnitude this primary induced emf is (almost) equal to the applied voltage. Therefore, in brief we can say emf induced in the primary winding is equal and opposite to the applied voltage.*

When a load is connected to the secondary side, current will start flowing in the secondary winding. Voltage induced in the secondary winding is responsible

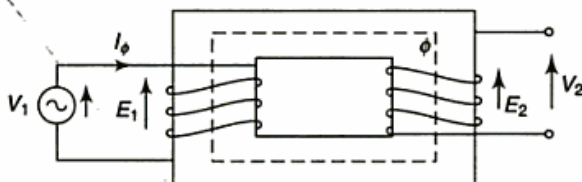


Fig. 8.1 Schematic diagram of single phase transformer

*If all the losses are neglected, the transformer is said to be ideal and hence for open circuited secondary, we can write $|V_1| = |E_1|$; $|V_2| = |E_2|$.

to deliver power to the load connected to it. In this way power is transferred from one circuit (primary) to another (secondary) winding through a magnetic circuit by electromagnetic induction. This is the working principle of the transformer. The induced emf in the secondary E_2 is also in phase opposition to the applied voltage V_1 at primary. If the secondary is open circuited, terminal voltage V_2 at the secondary is equal in magnitude and in phase with the induced emf at secondary.

8.3 EMF EQUATION

Since the applied voltage is sinusoidal at the primary, the flux produced by the exciting current is also sinusoidal (assuming $\phi \propto I$).

Thus core flux is given by $\phi = \phi_{\max} \sin \omega t$. If the coil has N turns then instantaneous value of the induced emf e is given by

$$e = -N \frac{d\phi}{dt}$$

$$\text{or} \quad e = -N \frac{d}{dt} (\phi_{\max} \sin \omega t)$$

$$\text{or} \quad e = -2\pi f \phi_{\max} N \cos \omega t \text{ V} \quad (\because \omega = 2\pi f)$$

The maximum value of the induced emf will be obtained when $(\cos \omega t)$ is 1.

$$\text{i.e.} \quad E_{\max} = 2\pi f \phi_{\max} N \text{ V} \quad (8.1)$$

Dividing both sides of equation (8.1) by $\sqrt{2}$, we have

$$\frac{E_{\max}}{\sqrt{2}} = \frac{2\pi}{\sqrt{2}} \phi_{\max} f N$$

$$\text{or} \quad E_{\text{rms}} = 4.44 \phi_{\max} f N \text{ V.} \quad (8.2)$$

If N_1 be the primary number of turns, then the rms values of induced voltage at primary is given by

$$E_1 = 4.44 \phi_{\max} f N_1 \text{ V.} \quad (8.2a)$$

(As the induced voltage in the primary winding is equal and opposite to the applied voltage, so $V_1 = 4.44 \phi_{\max} f N_1 \text{ V}$).

Similarly, the rms value of the induced emf at secondary is obtained as

$$E_2 = 4.44 \phi_{\max} f N_2 \text{ V} \quad (8.2b)$$

Thus for a single phase *ideal* transformer, the expressions for the induced voltages at the primary as well as at the secondary windings can be obtained from Eqns (8.2a) and (8.2b). In these equations V denotes voltage.

8.4 CONSTRUCTION OF SINGLE-PHASE TRANSFORMERS

A single-phase transformer consists of primary and secondary windings placed on a *magnetic core*. The magnetic core is a stack of thin silicon steel laminations (CRGO steel). The laminations reduce eddy current loss and silicon steel reduces hysteresis loss. There are two general types of transformers, *core type* and *shell type*.

In core type transformers, the windings surround a considerable part of the steel core. The core consists of two vertical legs (or *limbs*) and the horizontal portions (called *yokes*) as shown in Fig. 8.2. For reduction of the leakage flux

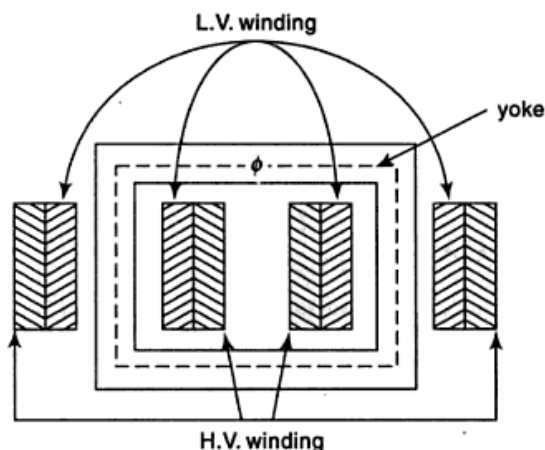


Fig. 8.2 Core type transformer

half of each winding is placed on each leg of the core. The low voltage winding is placed usually adjacent to the steel core and high voltage is placed outside in order to minimise the amount of insulation required.

In shell type transformers the steel core surrounds a major part of the winding as shown in Fig. 8.3. The low voltage and high voltage windings are wound over the central limb and are *interleaved* (or) *sandwiched*. The shell type transformer requires more conductor material as compared to core type transformer.

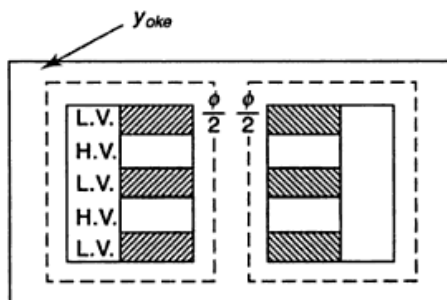


Fig. 8.3 Shell type transformer

In core type transformers the flux has a single path around the legs whereas in shell type transformers the flux in the central limb divides equally and returns through the outer two legs. Concentric coils are used for core type transformers and interleaved (or sandwiched) coils are used for shell type transformers.

8.5 TRANSFORMATION RATIO (OR TURNS RATIO)

Let

N_1 = Number of turns in the primary winding

N_2 = Number of turns in the secondary winding

E_1 = RMS value of the primary induced emf

E_2 = RMS value of the secondary induced emf.

Using the emf equation, we can write

$$E_1 = 4.44 f N_1 \phi_m \text{ and } E_2 = 4.44 f N_2 \phi_m$$

$$\therefore \frac{E_1}{E_2} = \frac{N_1}{N_2} \quad (8.3)$$

Thus the ratio of primary voltage to secondary voltage is same as the ratio of primary winding turns to the secondary winding turns. The ratio N_1/N_2 is known as the *transformation ratio* (or *turns ratio*). It is usually denoted by K . By selecting this ratio properly, transformation can be done from any input voltage to any convenient output voltage. There can be two cases:

- (a) If $N_1 > N_2$, then $E_2 < E_1$; the transformer is known as a *step-down* transformer ($k > 1$).
- (b) If $N_2 > N_1$, then $E_2 > E_1$; the transformer is known as a *step-up* transformer ($k < 1$).

Let us again consider a two-winding transformer. In the process of transforming electrical power from one voltage to the other, there occurs some losses in the transformer. These losses are actually very small as compared to the total amount of power handled by the transformer. If we neglect these losses for the time being, we must have the same power (volt-ampere) in the primary and in the secondary winding. If I_1 and I_2 are the currents in the primary and secondary windings of an ideal transformer (i.e. having no losses), we should have

$$E_1 I_1 = E_2 I_2$$

[$E_1 I_1$ and $E_2 I_2$ are the primary and secondary powers (voltamperes)]

$$\text{or} \quad \frac{I_1}{I_2} = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{1}{K} \left(= \frac{V_2}{V_1} \right) \quad (8.4)$$

Thus we find that the current is transformed in the reverse ratio of the voltage. If a transformer steps up the voltage, it steps down the current. If it steps down the voltage, it steps up the current.

8.6 IMPEDANCE TRANSFORMATION

In Fig. 8.4 an impedance Z_2 is connected across the secondary winding at its output. The primary winding is connected to a voltage source V_1 . The number of turns in the two windings are assumed to be N_1 and N_2 . Induced emfs E_1 and E_2 are in phase opposition to V_1 . Since V_2 is the secondary terminal voltage, it is also in the opposite phase of V_1 .

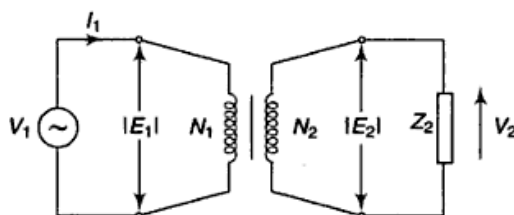


Fig. 8.4 Schematic diagram of two-winding transformers

$$\therefore E_1 = 4.44 \phi_m f N_1,$$

$$\text{So } \phi_m = \frac{500}{4.44 \times 50 \times 400} = 0.0056 \text{ Wb.}$$

$$(i) \text{ Peak value of core flux density} = \frac{0.0056}{0.006} \text{ Wb/m}^2 = 0.938 \text{ Wb/m}^2.$$

$$(ii) \text{ Emf induced in the secondary } E_2 = 4.44 \phi_m f N_2$$

$$= 4.44 \times 0.0056 \times 50 \times 1000 \text{ V} = 1243.2 \text{ V.}$$

8.3 The primary winding of a 50 Hz transformer is supplied from a 440 V, 50 Hz source and has 200 turns. Find the (i) peak value of flux (ii) voltage induced in the secondary winding if it has 50 turns.

Solution

$$f = 50 \text{ Hz}$$

$$E_1 = 440 \text{ V}$$

$$N_1 = 200.$$

(i) If ϕ_m is the peak value of flux then

$$E_1 = 4.44 f \phi_m N_1$$

or

$$\phi_m = \frac{440}{4.44 \times 50 \times 200} \text{ Wb} = 0.0099 \text{ Wb.}$$

(ii) $N_2 = 50$

Voltage induced in the secondary

$$E_2 = 4.44 f \phi_m N_2 = 4.44 \times 50 \times 0.0099 \times 50 \text{ V} = 110 \text{ V.}$$

8.4 A 200 kVA single-phase transformer has 1000 turns in the primary and 600 turns on the secondary. The primary winding is supplied from a 440 V, 50 Hz source. Find the (i) secondary voltage at no load and (ii) primary and secondary currents at the full load.

Solution

Let primary and secondary currents at full load be I_1 and I_2 .

$$\text{Primary kVA} = \text{Secondary kVA} = 200$$

$$\therefore E_1 I_1 = E_2 I_2 = 200 \times 10^3 \text{ VA}$$

$$N_1 = 1000; N_2 = 600$$

$$E_1 = 440 \text{ V.}$$

$$(i) \text{ Now, } \frac{E_1}{E_2} = \frac{N_1}{N_2} \text{ or, } E_2 = \frac{E_1 N_2}{N_1} = 440 \times \frac{600}{1000} = 264 \text{ V.}$$

$$(ii) I_1 = \frac{200 \times 10^3}{E_1} = \frac{200 \times 10^3}{440} \text{ A} = 454.54 \text{ A.}$$

$$I_2 = \frac{200 \times 10^3}{E_2} = \frac{200 \times 10^3}{264} \text{ A} = 757.57 \text{ A.}$$

8.5 The emf per turn for a single-phase 440/220 V, 50 Hz transformer is approximately 15 V. Find (i) the number of primary and secondary turns and (ii) the net cross sectional area of the core, for a maximum flux density of 1 Wb/m².

Solution

$$E_1 = 440 \text{ V}$$

$$E_2 = 220 \text{ V}$$

$$f = 50 \text{ Hz.}$$

$$\text{Voltage per turn} = 15 \text{ V.}$$

Solution

$$A = 100 \times 10^{-4} \text{ m}^2 = 0.01 \text{ m}^2$$

$$E_1 = 200 \text{ V}; E_2 = 50 \text{ V}; B_m = 1 \text{ Wb/m}^2$$

Assuming 9% loss of area, net area of core = $0.01 \times 0.9 \text{ m}^2 = 0.009 \text{ m}^2$

$$\text{Primary turns } N_1 = \frac{E_1}{4.44 f B_m A} = \frac{200}{4.44 \times 50 \times 1 \times 0.009} = 100$$

$$\text{Secondary turns } N_2 = \frac{E_2}{E_1} N_1 = \frac{50}{200} \times 100 = 25$$

$$\text{Transformation ratio } \frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{100}{25} = 4.$$

.....

8.8 A 1000 kVA transformer has primary and secondary turns of 400 and 100 respectively and induced voltage in the secondary is 1000 V. Find (i) the primary volt (ii) the primary and secondary full load current and (iii) the secondary current when 100 kW load at 0.8 p.f. is connected at the output.

Solution

Given: kVA = 1000

$$N_1 = 400$$

$$N_2 = 100$$

$$E_2 = 1000.$$

$$(i) \text{ Primary voltage } E_1 = \frac{N_1}{N_2} E_2 = \frac{400}{100} \times 1000 = 4000 \text{ V.}$$

$$(ii) \text{ Primary full load current } I_1 = \frac{VA}{E_1} = \frac{1000 \times 10^3}{4000} = 250 \text{ A}$$

$$\text{Secondary full load current } I_2 = I_1 \times \frac{N_1}{N_2} = 250 \times \frac{400}{100} = 1000 \text{ A.}$$

(iii) Secondary current at 100 kW and 0.8 p.f. load

$$I_2 = \frac{100 \times 10^3}{0.8 \times 1000} = 125 \text{ A.}$$

.....

8.7 NO LOAD OPERATION OF A TRANSFORMER

A transformer is said to be on no load, if its primary winding is connected to an ac supply source and the secondary is open. The instantaneous flux (ϕ) linking with both the windings is given as $\phi = \phi_m \sin \omega t$.

Therefore, the induced emf in primary winding is given as

$$\begin{aligned} E_1 &= -N_1 \frac{d\phi}{dt} = -N_1 \frac{d}{dt} (\phi_m \sin \omega t) \\ &= -N_1 \omega \phi_m \cos \omega t = N_1 \omega \phi_m \sin \left(\omega t - \frac{\pi}{2} \right) \end{aligned}$$

Similarly, the induced emf in the secondary winding is given as

$$E_2 = N_2 \omega \phi_m \sin \left(\omega t - \frac{\pi}{2} \right)$$

We consider the transformer to be ideal (i.e. there are no voltage drops in the windings). E_1 and E_2 are in phase opposition to V_1 .

It is thus evident that

- The induced emfs in primary and secondary windings (E_1 and E_2) lag behind the main flux ϕ by an angle $\pi/2$, and E_1 and E_2 are in the same phase with each other [as shown in the phasor diagram (Fig. 8.5)].
- Applied voltage to the primary winding V_1 , leads the main flux ϕ by an angle $\pi/2$. Also it is in phase opposition to the induced emfs in the primary winding and secondary winding in ideal transformers. In ideal transformers there is no voltage drop in the secondary winding and hence $|V_2| = |E_2|$.
- The no load current or exciting current I_o lags behind the applied voltage by an angle ϕ_o . It has two components I_m and I_w . The magnetising component I_m is in phase with the main flux ϕ , whereas, the other component I_w is in phase with the applied voltage. (This current is required to meet the hysteresis and eddy-current losses occurring in the core.)

Thus, from the phasor diagram of Fig. 8.5, we have

$$I_o = \sqrt{I_m^2 + I_w^2}; I_w = I_o \cos \phi_o, I_m = I_o \sin \phi_o$$

and $\phi_o = \tan^{-1} \frac{I_m}{I_w}$. (In practice, ϕ_o is close to 90° and is called *no load power factor angle*.)

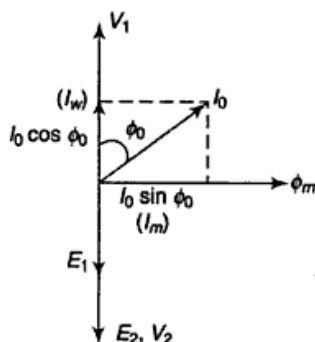


Fig. 8.5 Phasor diagram under no load condition ($N_2 > N_1$)

When a transformer is connected to a supply, there actually occurs eddy-current loss and hysteresis loss in the iron-core and appear as heat. This power is taken from the ac supply at primary.

The no load current component I_m is used in magnetizing the core. (There is no power loss due to this current). The current I_m lags behind the applied voltage V_1 by $\pi/2$. The product of I_m and V_1 does not represent active power. This product is called the *reactive power*. Therefore, the input active power at no-load is

$$P_o = V_1 I_w = V_1 I_o \cos \phi_o \quad (8.6)$$

and, the reactive power is

$$W_o = V_1 I_m = V_1 I_o \sin \phi_o. \quad (8.7)$$

8.8 WORKING OF A TRANSFORMER ON LOAD

When the transformer is loaded, load current I_2 flows in the secondary winding. Secondary number of turns being N_2 , the secondary ampere-turns is $I_2 N_2$; it sets up flux ϕ_2 in the core, which opposes the flux ϕ already set up by the no load current. As a result the flux linking with primary is reduced. The difference between applied voltage and induced voltage in the primary will however exist

Fig. 8.8(a) shows the phasor diagram of a transformer under lagging load power factor and considering internal voltage drop (the transformer is now not an ideal one). The voltage $(-E_1)$ has been replaced by V_1' for convenience. Alternatively V_1' may be treated as a voltage drop in the primary in the direction of flow of primary current. The primary current I_1 flows through primary resistance R_1 and primary leakage reactance X_1 . Hence primary voltage is given as

$$V_1 = V_1' + I_1(R_1 + jX_1), \text{ where } V_1' \text{ is } (-E_1).$$

Similarly, $E_2 = V_2 + I_2(R_2 + jX_2)$ where R_2 and X_2 are the resistance and leakage reactance of the secondary side of the transformer.

Here, V_1 = the supply voltage (input voltage at primary)

E_1 = the induced voltage at primary

$V_1' = -E_1$ (phasor E_1 reserved to the primary side in the phasor diagram)

I_o = the no load (magnetising) current at primary $(= I_w + I_m)$

E_2 = the secondary induced voltage

V_2 = the output voltage, i.e. terminal voltage at the secondary

I_2 = the secondary load current

ϕ = the p.f. angle

I_2' = the referred secondary current to primary.

Figures 8.8(b) and 8.8(c) represent the phasor diagrams of the transformer (not an ideal one) operating with unity power factor and leading power factor respectively.

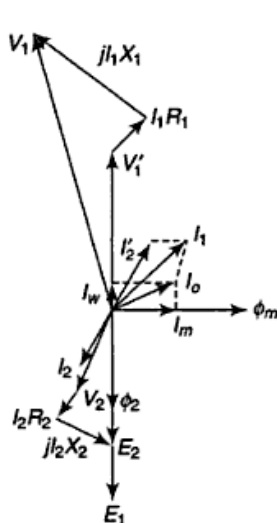


Fig. 8.8(a) Exact phasor diagram for lagging power factor I_1 = (primary current); R_1 , X_1 and R_2 , X_2 = primary and secondary winding resistance and reactances.

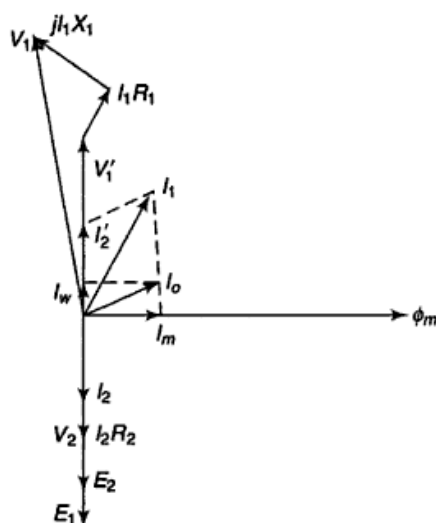


Fig. 8.8(b) Exact transformer phasor diagram for unity power factor [I_2 and V_2 in phase]

The equivalent circuit gives the interpretation of the above equations. Further, we know the primary current I_1 is composed of two currents I_2' and I_o . Also, the current I_o consists of two components, I_m and I_w . Therefore, the current I_o can be considered to be split into two parallel branches. The current I_w accounts for the core-loss, and hence is shown to flow through resistance R_o . The current I_m represents the magnetising current and is shown to flow through a pure reactance X_o . This branch consisting of the parallel R_o and X_o is called the *magnetising branch* of the transformer.

Using the impedance transformation, we can draw the simplified equivalent circuit of a transformer, as referred to the primary side only or to the secondary side only.

We have seen earlier that an impedance connected across the secondary appears as K^2 times, when referred to the primary. (Here, $K = N_1/N_2$, where K is the transformation ratio). Therefore to simplify the equivalent circuit of Fig. 8.9, we can transfer the resistance R_2 and the reactance X_2 to the primary side, by simply multiplying each of them by K^2 . The total resistance and the total reactance in the primary side then becomes

$$R_{o1} = R_1 + K^2 R_2 \quad \text{and} \quad X_{o1} = X_1 + K^2 X_2$$

where $R_2' = K^2 R_2$ and $X_2' = K^2 X_2$.

The equivalent circuit of the transformer now simply reduces to the one as shown in Fig. 8.10(a).

Here,

$$I_2' = \frac{1}{K} I_2$$

$$V_2' = K V_2$$

$$R_{o1} = R_1 + X_2'$$

$$R_2' = K^2 R_2$$

$$X_{o1} = X_1 + X_2'$$

$$X_2' = K^2 X_2$$

$$I_1 = I_o + I_2'$$

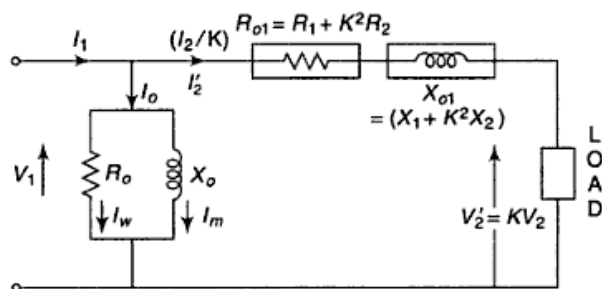


Fig. 8.10(a) Equivalent circuit of transformer referred to primary

Similarly, the equivalent circuit as referred to secondary side can also be drawn. But in this case the equivalent resistance and reactance as referred to secondary side will be

$$R_{o2} = R_2 + (1/K^2) R_1 \quad \text{and} \quad X_{o2} = X_2 + (1/K^2) X_1.$$

The equivalent circuit referred to the secondary is shown in Fig. 8.10(b). Here R_o' and X_o' represent the core resistance and the magnetizing reactance referred to the secondary.

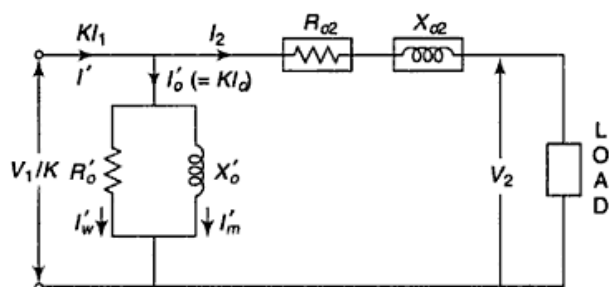


Fig. 8.10(b) Equivalent circuit of transformer referred to secondary

8.9.1 Approximate Equivalent Circuit

Since in a transformer the magnitude of I_o is very low (1 – 3% of the full load current), we can neglect the magnetising branch for simplicity. The equivalent circuit neglecting the magnetising branch is called the approximate equivalent circuit (Fig. 8.10(c) and Fig. 8.10(d)).

$$R_{o2} = R_2 + \frac{1}{K^2} R_1; R_{o1} = R_1 + K^2 R_2$$

$$X_{o2} = X_2 + \frac{1}{K^2} X_1; X_{o1} = X_1 + K^2 X_2$$

$$V_1' = \frac{1}{K} V_1; V_2' = K V_2$$

$$I_1' = K I_1; I_2' = (I_2/K)$$

$$I_o' = K I_o$$

$$R_o' = \frac{1}{K^2} R_o$$

$$X_o' = \frac{1}{K^2} X_o$$

$$K I_1 = I_1' = K I_o + I_2$$

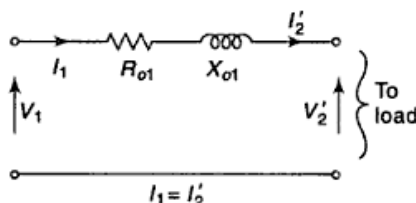


Fig. 8.10(c) Approximate equivalent circuit of transformer referred to as primary

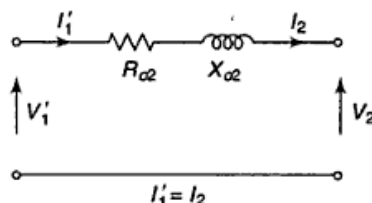


Fig. 8.10(d) Approximate equivalent circuit of transformer referred to as secondary

8.10 REGULATION OF A TRANSFORMER

The *regulation* of a transformer (generally expressed as percentage regulation) may be defined as

$$\left[\frac{\text{Secondary no load voltage} - \text{Secondary full load voltage}}{\text{Secondary no load voltage}} \right] \times 100$$

If E_2 = the secondary no load voltage
 V_2 = the terminal voltage at secondary

$$\text{then percentage regulation} = \frac{E_2 - V_2}{E_2} \times 100 \quad (8.10)$$

Therefore percentage regulation of a transformer is defined as the *percentage decrease in the terminal voltage of the transformer from no-load to full load condition at a constant applied voltage.*

8.10.1 Expression for Regulation

Let us consider the equivalent circuit of the transformer referred to the secondary (as shown in Fig. 8.11)

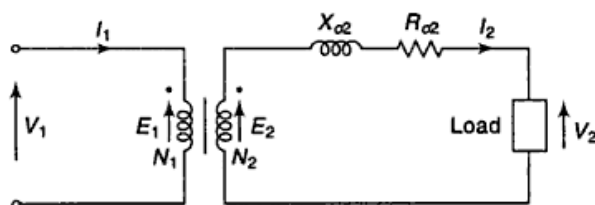


Fig. 8.11 Approximate equivalent circuit of transformer referred to as secondary

When the load is connected to the secondary side, current I_2 will start flowing. Depending upon the nature of the load, current I_2 may be lagging the voltage V_2 for inductive load, in phase of the voltage V_2 for resistive load and leading the voltage V_2 for capacitive load.

Hence on the basis of the above current-voltage phasor relation, the load has a lagging power factor, a unity power factor and a leading power factor respectively. Expressions for regulation in each case will be as discussed below.

(i) *Lagging power factor* The phasor diagram of the transformer referred to as the secondary, when supplying a load of lagging power factor load, has been shown in Fig. 8.12, where,

E_2 = the no load voltage

V_2 = the load voltage

$I_2 R_{02}$ = the resistive drop referred to secondary

$I_2 X_{02}$ = the reactive drop referred to secondary

and θ_2 = the angle between V_2 and I_2 i.e. $\cos \theta_2$ is p.f. of the load.

$$[Oa = V_2; ab = I_2 R_{02} \cos \theta_2; bc = I_2 X_{02} \sin \theta_2; cd = (I_2 X_{02}) \cos \theta_2 - I_2 R_{02} \sin \theta_2]$$

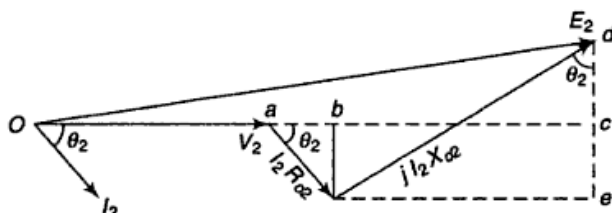


Fig. 8.12 Phasor diagram of a transformer on lagging load, referred to as secondary

From Fig. 8.12

$$\begin{aligned} E_2^2 &= (Oc)^2 + (cd)^2 = (Oa + ab + bc)^2 + (cd)^2 \\ &= (V_2 + I_2 R_{o2} \cos \theta_2 + I_2 X_{o2} \sin \theta_2)^2 \\ &\quad + (I_2 X_{o2} \cos \theta_2 - I_2 R_{o2} \sin \theta_2)^2 \end{aligned}$$

where I_2 is the secondary current lagging V_2 by angle θ_2 .

As $(I_2 X_{o2} \cos \theta_2 - I_2 R_{o2} \sin \theta_2)$ is very small (being the difference of two quantities) it can easily be neglected.

$$\text{Hence } E_2 = V_2 + I_2 R_{o2} \cos \theta_2 + I_2 X_{o2} \sin \theta_2$$

$$\text{or } E_2 - V_2 = (I_2 R_{o2} \cos \theta_2 + I_2 X_{o2} \sin \theta_2). \quad (8.11)$$

$$\text{Percentage voltage regulation} = \frac{E_2 - V_2}{E_2} \times 100\%$$

$$= \left(\frac{I_2 R_{o2}}{E_2} \cos \theta_2 + \frac{I_2 X_{o2}}{E_2} \sin \theta_2 \right) \times 100\% \quad (8.12)$$

$$= (R_{p.u} \cos \theta_2 + X_{p.u} \sin \theta_2) \times 100\% \quad (8.13)$$

where $(R_{p.u})$ and $(X_{p.u})$ are the total p.u resistance and reactance respectively

$$\left[R_{p.u} = \frac{I_2 R_{o2}}{E_2}; X_{p.u} = \frac{I_2 X_{o2}}{E_2} \right]$$

(ii) *Unity power factor:* Phasor diagram at unity p.f. has been shown in Fig. 8.13.

From Fig. 8.13 we have

$$E_2^2 = (V_2 + I_2 R_{o2})^2 + (I_2 X_{o2})^2 \quad (8.14)$$

If the second term is neglected

$$E_2 = V_2 + I_2 R_{o2} \quad (8.15)$$

{The second term $(I_2 X_{o2})$ is neglected as it does not contribute much in changing the magnitude of V_2 . On the other hand, it is responsible for the phase shift between E_2 and V_2 . Hence we can reasonably neglect $(I_2 X_{o2})$.

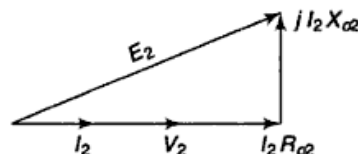


Fig. 8.13 Phasor diagram of the transformer for unity p.f. load.

$$\text{Hence percentage voltage regulation} = \frac{E_2 - V_2}{E_2} \times 100\%$$

$$= \frac{I_2 R_{o2}}{E_2} \times 100\%$$

$$= R_{p.u} \times 100\% \quad (8.16)$$

Leading power factor: For leading power factor ($\cos \theta_2$),

$$I_2 = I_2 \cos \theta_2 + j I_2 \sin \theta_2$$

$$E_2 = V_2 + I_2 Z_{o2} = V_2 + j.0 + (I_2 \cos \theta_2 + j I_2 \sin \theta_2) (R_{o2} + j X_{o2})$$

$$\text{or } E_2 = V_2 + I_2 R_{o2} \cos \theta_2 - I_2 X_{o2} \sin \theta_2 + j(I_2 R_{o2} \sin \theta_2 + I_2 X_{o2} \cos \theta_2)$$

$$\text{Hence } E_2^2 = (V_2 + I_2 R_{o2} \cos \theta_2 - I_2 X_{o2} \sin \theta_2)^2 + (I_2 R_{o2} \sin \theta_2 + I_2 X_{o2} \cos \theta_2)^2$$

The phasor diagram is shown in Fig. 8.14.

Now $(I_2 R_{o2} \sin \theta_2 + I_2 X_{o2} \cos \theta_2)$ is very small compared to $(V_2 + I_2 R_{o2} \cos \theta_2 - I_2 X_{o2} \sin \theta_2)$. Hence $(I_2 R_{o2} \sin \theta_2 + I_2 X_{o2} \cos \theta_2)$ is neglected.

$$\therefore E_2 = V_2 + I_2 R_{o2} \cos \theta_2 - I_2 X_{o2} \sin \theta_2$$

$$\text{or } E_2 - V_2 = I_2 R_{o2} \cos \theta_2 - I_2 X_{o2} \sin \theta_2 \quad (8.17)$$

Percentage voltage regulation is

$$\frac{E_2 - V_2}{E_2} \times 100\% = \left(\frac{I_2 R_{o2}}{E_2} \cos \theta_2 - \frac{I_2 X_{o2}}{E_2} \sin \theta_2 \right) \times 100\% \quad (8.18)$$

$$= (R_{p.u} \cos \theta_2 - X_{p.u} \sin \theta_2) \times 100\% \quad (8.19)$$

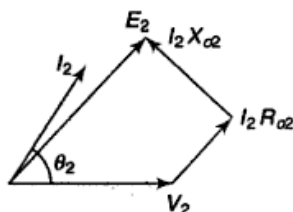


Fig. 8.14 Phasor diagram of transformer for leading power factor load.

8.11 CONDITION FOR ZERO (MINIMUM) REGULATION

We can use the expression of regulation to find the condition for which the regulation is zero. We can write at zero regulation,

$$I_2 R_{o2} \cos \theta_2 + I_2 X_{o2} \sin \theta_2 = 0$$

$$\text{or } \tan \theta_2 = - \frac{R_{o2}}{X_{o2}} \quad (8.20)$$

The negative sign in the above condition indicates that zero regulation is possible at a leading power factor. Also, if the transformer is not loaded at all, $E_2 = V_2$ and this also gives zero regulation. Thus the regulation is zero if the transformer is open circuited or operated at a leading p.f. so that $\theta_2 = \tan^{-1} \frac{R_{o2}}{X_{o2}}$. Also

from the expression of regulation, it is evident that for a leading power factor load if the magnitude of θ_2 is high, the magnitude of $(I_2 X_{o2} \sin \theta_2)$ would become more than that of $(I_2 R_{o2} \cos \theta_2)$. The regulation then may become negative. It means, on increasing the load the terminal voltage increases at leading power factor operation of the transformer.

8.11.1 Condition for Maximum Regulation

We can derive the condition for maximum regulation using the expression for regulation. The regulation will be maximum if the differentiation of regulation with respect to phase angle θ_2 is equal to zero. That is

$$\frac{d}{d\theta_2} = (I_2 R_{o2} \cos \theta_2 + I_2 X_{o2} \sin \theta_2) = 0$$

$$\text{or} \quad -I_2 R_{o2} \sin \theta_2 + I_2 X_{o2} \cos \theta_2 = 0$$

$$\text{or} \quad \tan \theta_2 = \frac{X_{o2}}{R_{o2}} \quad (8.20)$$

Hence maximum regulation occurs only at lagging power factor and when $\theta_2 =$

$$\tan^{-1} \frac{X_{o2}}{R_{o2}}.$$

8.9 A single-phase transformer has 200 and 100 turns respectively in its secondary and primary windings. The resistance of the primary winding is 0.05Ω and that of the secondary is 0.3Ω . Find the resistance of (i) the primary winding referred to the secondary, (ii) the secondary winding referred to the primary. Also find the equivalent resistance of the transformer referred to the primary.

Solution

Number of turns of primary winding $N_1 = 100$

Number of turns of secondary winding $N_2 = 200$

Resistance of primary winding $R_1 = 0.05 \Omega$

Resistance of secondary winding $R_2 = 0.3 \Omega$

(i) Resistance of primary winding referred to secondary

$$= R_1' = R_1 \left(\frac{N_2}{N_1} \right)^2 = 0.05 \times \left(\frac{200}{100} \right)^2 = 0.05 \times 4 = 0.2 \Omega.$$

(ii) Resistance of secondary winding referred to primary

$$R_2' = R_2 \times \left(\frac{N_1}{N_2} \right)^2 = 0.3 \times \left(\frac{100}{200} \right)^2 = \frac{0.3}{4} \Omega = 0.075 \Omega$$

Equivalent resistance of the transformer referred to the primary

$$R_{01} = R_1 + R_2' = 0.05 + 0.075 = 0.125 \Omega.$$

$$[\text{Also, } R_{02} = R_2 + R_1' = 0.3 + 0.2 = 0.5 \Omega].$$

.....

8.10 A 20 kVA, 1000/200 V single-phase transformer has a primary resistance of 1Ω and a secondary resistance of 0.2Ω . Find the equivalent resistance of the transformer referred to the secondary and the total resistance drop on full load.

Solution

If N_1 and N_2 be the number of turns of the primary and secondary winding then

$$\frac{N_1}{N_2} = \frac{1000}{200}.$$

Resistance of the primary winding $R_1 = 1 \Omega$.

Resistance of the secondary winding $R_2 = 0.2 \Omega$.

Total equivalent resistance in terms of the secondary winding is $(R_1' + R_2)$

$$\text{i.e.} \quad R_{o2} = R_1 \left(\frac{N_2}{N_1} \right)^2 + R_2 = 1 \times \left(\frac{200}{1000} \right)^2 + 0.2 = 0.04 + 0.2 = 0.24 \Omega.$$

Full load secondary current

$$I_2 = \frac{20 \times 10^3}{200} = 100 \text{ A.}$$

Total resistance drop on full load = $I_2 R_{02} = 100 \times 0.24 = 24 \text{ V.}$

8.11 A single-phase transformer has turns ratio of 8. The resistances of the high voltage and low voltage windings are 1.5Ω and 0.05Ω respectively and the reactances are 10Ω and 0.5Ω respectively. Find (i) the voltage to be applied to the high voltage side to obtain a full load current of 100 A on the low voltage winding on short circuit and (ii) the power factor on short circuit.

Solution

If N_H and N_L be the number of turns on the high voltage and low voltage windings then

$$\frac{N_H}{N_L} = 8 \text{ (given).}$$

Resistance of high voltage winding $R_H = 1.5 \Omega$

Resistance of low voltage winding $R_L = 0.05 \Omega$

Reactance of high voltage winding $X_H = 10 \Omega$

Reactance of low voltage winding $X_L = 0.5 \Omega$

Full load current on the low voltage side = 100 A.

$$\therefore \text{ full load current on the high voltage side} = 100 \times \frac{N_L}{N_H} = \frac{100}{8} = 12.5 \text{ A.}$$

Equivalent impedance referred to the high voltage side

$$= (R_H + R'_L) + j(X_H + X'_L)$$

$$= \{1.5 + 0.05(8)^2\} + j\{10 + 0.5(8)^2\} = 4.7 + j42 = 42.26 \angle 83.6^\circ \Omega.$$

(i) The voltage to be applied to the high voltage side to obtain full load current is $12.5 \times 42.26 = 528.25 \text{ V}$

(ii) Power factor on short circuit is $\cos 83.6^\circ = 0.111.$

8.12 A 6600/440 V, 50 Hz single-phase transformer has high voltage and low voltage winding resistances of 0.5Ω and 0.0007Ω respectively and reactances of 2Ω and 0.001Ω respectively. Find the current and the input power when the high voltage winding is connected to a 220 V 50 Hz supply, the low voltage being short circuited.

Solution

$$\frac{N_H}{N_L} = \frac{6600}{440}, \quad R_H = 0.5 \Omega, \quad R_L = 0.0007 \Omega, \\ X_H = 2 \Omega, \quad X_L = 0.001 \Omega.$$

Equivalent impedance referred to the high voltage side

$$Z_{eH} = R_H + R_L \left(\frac{N_H}{N_L} \right)^2 + j \left\{ X_H + X_L \left(\frac{N_H}{N_L} \right)^2 \right\} \\ = 0.5 + 0.0007 \left(\frac{6600}{440} \right)^2 + j \left\{ 2 + 0.001 \left(\frac{6600}{440} \right)^2 \right\} \\ = 0.6575 + j2.225 = 2.32 \angle 73.54^\circ \Omega.$$

\therefore Current in the high voltage side when low voltage is short circuited is $\frac{220}{2.32} \text{ A} = 94.83 \text{ A.}$

Input power = $220 \times 94.83 \cos 73.54^\circ = 5911 \text{ W} = 5.9 \text{ kW.}$

8.13 The equivalent impedance of a 10 kVA, 220/440 V, single-phase, 50 Hz transformer referred to the low voltage side is $(0.2 + j0.5) \Omega$. The core loss resistance and magnetizing reactance are 100Ω and 150Ω respectively, both referred to the low voltage side. If the high voltage current is 20 A at a lagging p.f. of 0.8 find the low voltage input current and the high voltage terminal voltage.

Solution

$$\left. \begin{aligned} R_{OL} &= 0.2 \Omega \\ X_{OL} &= 0.5 \Omega \end{aligned} \right\} \text{ [Low voltage side resistance and reactance]}$$

$$\left. \begin{aligned} R_O &= 100 \Omega \\ X_O &= 150 \Omega \end{aligned} \right\} \text{ [Magnetizing branch resistance and reactance at low voltage side]}$$

$$\therefore Z_{OL} = 0.5385 \angle 68.2^\circ \Omega.$$

$$\text{High voltage current } (I_H) = 20 \angle -\cos^{-1} 0.8 = 20 \angle -36.86^\circ \text{ V}$$

$$\text{The high voltage current referred to low voltage side} = I'_H = 20 \times \frac{440}{220} = 40 \text{ A.}$$

$$\begin{aligned} \text{The no load component of current } (I_O) &= \frac{220}{100} - j \frac{220}{150} \\ &= (2.2 - j1.47) \text{ A} \end{aligned}$$

$$\begin{aligned} \text{Input current on the low voltage side} &= 40(0.8 - j0.6) + 2.2 - j1.47 \\ &= 34.2 - j25.47 \\ &= 42.64 \angle -36.67^\circ \text{ A.} \end{aligned}$$

$$\begin{aligned} \text{High voltage side terminal voltage } (V_2) &= \left\{ 220 - 42.64 \angle -36.67^\circ (0.2 + j0.5) \right\} \frac{440}{220} \\ &= \left\{ 220 - 42.64(0.8 - j0.6)(0.2 + j0.5) \right\} \frac{440}{220} \\ &= \left\{ 220 - 42.64(0.46 + j0.28) \right\} \frac{440}{220} \\ &= (200.38 - j11.94) \times 2 = 401.47 \angle -3.41^\circ \text{ V.} \end{aligned}$$

8.14 A 500 kVA, single-phase, 2000/200 V, 50 Hz. transformer has a high voltage resistance 0.2Ω and a leakage reactance of 0.4Ω . The low voltage winding resistance is 0.002Ω and the leakage reactance is 0.008Ω . Find (i) the equivalent winding resistance and reactance referred to the high voltage side and the low voltage side, (ii) the equivalent resistance and equivalent reactance drops in volts and in percent of the rated winding voltages expressed in terms of high voltage quantities.

Solution

(i) Equivalent winding resistance referred to the high voltage side

$$R_{o1} = R_1 + R_2 \left(\frac{N_1}{N_2} \right)^2 = 0.2 + 0.002 \times \left(\frac{2000}{200} \right)^2 = 0.2 + 0.2 = 0.4 \Omega.$$

Equivalent reactance referred to the high voltage side

$$X_{o1} = X_1 + X_2 \left(\frac{N_1}{N_2} \right)^2 = 0.4 + 0.008 \times \left(\frac{2000}{200} \right)^2 = 0.4 + 0.8 = 1.2 \Omega.$$

Equivalent resistance referred to low voltage side

$$R_{o2} = R_{o2} + R_{o1} \left(\frac{N_2}{N_1} \right)^2 = 0.002 + 0.2 \times \left(\frac{200}{2000} \right)^2 = 0.002 + 0.002 = 0.004 \Omega.$$

Equivalent reactance referred to low voltage side

$$X_{o2} = X_2 + X_1 \left(\frac{N_2}{N_1} \right)^2 = 0.008 + 0.4 \times \left(\frac{200}{2000} \right)^2 = 0.008 + 0.004 = 0.012 \Omega.$$

(ii) Equivalent resistance drop referred to the high voltage side $= I_1 R_{o1} = \frac{500 \times 10^3}{2000} \times 0.4 = 250 \times 0.4 = 100 \text{ V}.$

Percent equivalent resistance drop $= \frac{I_1 R_{o1}}{V_1} \times 100\% = \frac{100}{2000} \times 100\% = 5\%.$

Equivalent reactance drop referred to the low voltage side

$$I_1 X_{o1} = \frac{500 \times 10^3}{2000} \times 1.2 = 250 \times 1.2 = 300 \text{ V}$$

Percent equivalent reactance drop

$$\frac{I_1 X_{o1}}{V_1} \times 100\% = \frac{300}{2000} \times 100\% = 15\%.$$

.....

8.15 A 5 kVA 440/220 V single-phase transformer has a primary and secondary winding resistance of 2 Ω and 0.8 Ω respectively. The primary and secondary reactances are 10 Ω and 1.5 Ω respectively. Find the secondary terminal voltage at full load, 0.8 p.f. lagging.

Solution

If V_2 be the secondary terminal voltage at full load and E_2 the secondary terminal voltage at no load then

$$E_2 = V_2 + I_2 R_{o2} \cos \theta_2 + I_2 X_{o2} \sin \theta_2$$

or $V_2 = E_2 - I_2 R_{o2}(0.8) - I_2 X_{o2}(0.6)$

$$R_{o2} = 2 \times \left(\frac{220}{440} \right)^2 + 0.8 = 0.5 + 0.8 = 1.3 \Omega$$

$$X_{o2} = 10 \times \left(\frac{220}{440} \right)^2 + 1.5 = 2.5 + 1.5 = 4 \Omega$$

$$I_2 = \frac{5 \times 10^3}{220} = 22.73 \text{ A}.$$

$\therefore V_2 = 220 - 22.73(1.3 \times 0.8 + 4 \times 0.6) = 220 - 22.73 \times 3.44 = 141.8 \text{ V}.$

.....

8.16 A transformer has 4% resistance and 6% reactance drop. Find the voltage regulation at full load (a) 0.8 p.f. lagging (b) 0.8 p.f. leading and (c) unity p.f.

Solution

(a) Regulation at 0.8 p.f. lagging $= R_{p.u} \cos \theta_2 + X_{p.u} \sin \theta_2$
 $= 0.04 \times 0.8 + 0.06 \times 0.6$
 $= 0.032 + 0.036 = 0.068 \text{ or } 6.8\%.$

(b) Regulation at 0.8 p.f. leading $= R_{p.u} \cos \theta_2 - X_{p.u} \sin \theta_2$
 $= 0.04 \times 0.8 - 0.06 \times 0.6$
 $= 0.032 - 0.036 = -0.004 \text{ or } -0.4\%.$

(c) Regulation at unity p.f. $(= R_{p.u} \cos \theta_2) = 0.04 \times 1 = 0.04 \text{ or } 4\%.$

8.19 A 40 kVA, 2500/500 V single phase transformer has the following parameters: $R_1 = 8 \Omega$, $R_2 = 0.5 \Omega$, $X_1 = 20 \Omega$, $X_2 = 0.8 \Omega$. Find the voltage regulation and the secondary terminal voltage at full load for a p.f. of 0.8 lagging. The primary voltage is held constant at 2500 V.

Solution

Equivalent resistance referred to low voltage side

$$R_{o2} = 0.5 + 8 \times \left(\frac{500}{2500} \right)^2 = 0.5 + 0.32 = 0.82 \Omega$$

Equivalent reactance referred to low voltage side

$$X_{o2} = 0.8 + 20 \times \left(\frac{500}{2500} \right)^2 = 0.8 + 0.8 = 1.6 \Omega$$

$$\text{Full load secondary current } I_2 = \frac{40 \times 10^3}{500} = 80 \text{ A}$$

$$\begin{aligned} \text{Voltage regulation} &= (I_2 R_{o2} \cos \theta_2 + I_2 X_{o2} \sin \theta_2) / E_2 \\ &= \frac{80}{500} \{0.82 \times (0.8) + 1.6 \times (0.6)\} \\ &= \frac{129.28}{500} = 0.258 \text{ or } 25.6\%. \end{aligned}$$

If V_2 be the secondary terminal voltage then

$$\frac{E_2 - V_2}{E_2} = 0.256 \quad \text{or,} \quad V_2 = (1 - 0.256) 500 = 372 \text{ V.}$$

8.20 A 2000/400 V single phase transformer has an equivalent resistance of 0.03 p.u. and an equivalent reactance of 0.08 p.u. Find the full load voltage regulation at 0.8 p.f. lag if the primary voltage is 1500 V. Find also the secondary terminal voltage at full load.

Solution

$$\text{Voltage regulation} = \frac{E_2 - V_2}{E_2} = R_{p.u.} \cos \theta_2 + X_{p.u.} \sin \theta_2$$

$$\text{or,} \quad \frac{E_2 - V_2}{E_2} = 0.03 \times 0.8 + 0.08 \times 0.6 = 0.072$$

So, voltage regulation is 0.072 or, 7.2%.

When primary voltage is 1500 V secondary voltage is $1500 \times \frac{400}{2000} = 300 \text{ V}$ at no load
or, $E_2 = 300 \text{ V}$. Hence, secondary terminal voltage $V_2 = E_2(1 - 0.072) = 300 \times 0.928 = 278.4 \text{ V}$.

8.12 LOSSES AND EFFICIENCY OF TRANSFORMER

Like any other machine, the *efficiency* of a transformer is defined as

$$\begin{aligned} \eta &= \frac{\text{Power output}}{\text{Power input}} \\ &= \frac{\text{Power output}}{\text{Power output} + \text{Power losses in the transformer}} \end{aligned}$$

To find the efficiency, we are to know various types of losses. There are two types of losses in a transformer:

- (a) *Copper losses* (or I^2R losses or *ohmic losses*) in the primary and secondary windings.
 (b) *Iron losses* (or *core losses*) in the core. This again has two components: (i) *hysteresis losses* and (ii) *eddy current losses*.

The copper losses (P_C) also have two components: (i) the primary winding copper loss, and (ii) the secondary winding copper loss.

$$\begin{aligned}\therefore \text{Copper losses, } (P_C) &= I_1^2 R_1 + I_2^2 R_2 \\ &= I_1^2 R_1 + I_1^2 R_2' = I_1^2 R_{o1} \\ \text{Also, } P_C &= I_2^2 R_2 + I_2^2 R_1' = I_2^2 R_{o2}\end{aligned}\quad (8.22)$$

(For correct determination of copper losses, the winding resistance should be determined at the operating temperature of windings.)

When alternating current flows through the windings, the core material undergoes cyclic processes of magnetisation and demagnetisation.

This process is called *hysteresis*.

The hysteresis losses (in watts) is given as,

$$P_h = K_h B_m^n f v \quad (8.23)$$

where, K_h = hysteresis coefficient whose value depends upon the material (K_h is 0.025 for cast steel, 0.001 for silicon steel and 0.0001 for permalloy)

B_m = maximum flux density (in tesla)

n = a constant, $1.5 \leq n \leq 2.5$ depending upon the material

f = frequency (in hertz)

v = volume of the core material (in m^3)

The eddy currents are the circulating currents set up in the core. These are produced due to magnetic flux being cut by the core. The loss due to these eddy currents is called *eddy current losses*. This loss (in watts) is given by

$$P_e = K_e B_m^2 f^2 t^2 v \quad (8.24)$$

where K_e = constant dependent upon the material

t = thickness of laminations (in metre)

A comparison of the expressions of hysteresis and eddy current losses reveals that the eddy-current loss varies as the square of the frequency, whereas the hysteresis loss varies directly with the frequency. The hysteresis losses can be minimised by selecting suitable ferromagnetic material for the core. The eddy-current losses can be minimised by using thin laminations in building the core.

The total iron losses (P_i) is given as

$$P_i = P_h + P_e$$

The efficiency of the transformer is thus given as

$$\begin{aligned}\eta &= \frac{\text{Power output}}{\text{Power input}} = \frac{P_o}{P_o + P_e + P_i} \\ &= \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \theta_2 + I_2^2 R_{o2} + P_i}\end{aligned}\quad (8.25)$$

8.13 CONDITION FOR MAXIMUM EFFICIENCY

Dividing the numerator and denominator in the above expression of efficiency by (I_2), we get

$$\eta = \frac{V_2 \cos \theta_2}{V_2 \cos \theta_2 + I_2 R_{o2} + P_i / I_2}$$

The transformer being operating at constant terminal voltage and constant power factor, we know the value of (I_2) at which the efficiency is maximum. Obviously, the efficiency will be maximum when ($I_2 R_{o2} + P_i / I_2$) is a minimum. (η) is maximum when its first derivative with respect to I_2 is zero.

$$\text{i.e.,} \quad \frac{d}{dI_2} \left(I_2 R_{o2} + \frac{P_i}{I_2} \right) = 0$$

$$\text{or} \quad R_{o2} - \frac{P_i}{I_2^2} = 0$$

$$\text{or} \quad I_2^2 R_{o2} = P_i \quad (8.26)$$

Thus, the efficiency at a given terminal voltage and load power factor is maximum for such a load current (I_2) which makes copper losses equal to the constant iron losses.

8.14 EXPRESSION FOR LOAD AT WHICH EFFICIENCY IS MAXIMUM

Let I_{2fl} = Full load secondary current
 I_{2m} = secondary current when efficiency is maximum
 R_{o2} = equivalent resistance referred to the secondary
 P_i = core loss

Full load copper losses = $I_{2fl}^2 R_{o2} = P_{cfl}$

Copper losses (when efficiency is maximum) are, $I_{2m}^2 R_{o2} (= P_c)$

$$\text{So,} \quad I_{2m}^2 = \frac{P_c}{R_{o2}} = \frac{I_{2fl}^2 P_c}{I_{2fl}^2 R_{o2}} = \frac{I_{2fl}^2 P_c}{P_{cfl}}$$

$$\text{or,} \quad I_{2m} = I_{2fl} \sqrt{\frac{P_c}{P_{cfl}}} = I_{2fl} \sqrt{\frac{P_i}{P_{cfl}}} \quad (8.27)$$

$$\text{Current at maximum efficiency} = \text{current at full load} \times \left(\sqrt{\frac{\text{Core loss}}{\text{Full load copper loss}}} \right)$$

$$\text{Now,} \quad V_2 I_{2m} = V_2 I_{2fl} \sqrt{\frac{P_c}{P_{cfl}}} \quad (8.28)$$

or, (VA) output at maximum efficiency

$$= \text{full load (VA) output} \times \sqrt{\frac{\text{Core loss}}{\text{Full load copper loss}}}$$

Hence, if the maximum efficiency occurs at n times the full load, then $n = \sqrt{(P_C/P_{cf})}$. (8.28a)

Maximum efficiency = $\frac{nV_2 I_f \cos \theta_2}{nV_2 I_f \cos \theta_2 + 2P_C}$, where $(\cos \theta_2)$ is the load p.f.

8.21 In a 25 kVA, 2000/200 V transformer the iron and full load copper losses are 350 W and 400 W respectively. Find the efficiency at unity p.f. at (a) full load (b) half load. Determine the load for maximum efficiency.

Solution

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}} = \frac{\text{Output}}{\text{Output} + \text{Losses}}$$

(a) At full load and unity p.f.

$$\text{Output} = 25 \times 10^3 \times 1 = 25 \times 10^3 \text{ W}$$

$$\text{Losses} = 350 + 400 = 750 \text{ W}$$

$$\therefore \text{efficiency} = \frac{25,000}{25,000 + 750} = 0.97 \text{ or } 97\%$$

(b) At half load and unity p.f.

$$\text{Output} = 25 \times 10^3 \times \frac{1}{2} = 12.5 \times 10^3 \text{ W}$$

$$\text{Iron losses} = 350 \text{ W}$$

$$\text{Copper losses} = \left(\frac{1}{2}\right)^2 \times 400 = 100 \text{ W}$$

$$\text{Total losses} = 450 \text{ W}$$

$$\text{Efficiency} = \frac{12,500}{12,500 + 450} = 0.965 \text{ or } 96.5\%$$

If maximum efficiency occurs when load is (x) times the full load then copper losses = $(x^2 \times 400)$ W

As core losses = copper losses, under maximum efficiency condition then $(x^2 \times 400) = 350$, or $(x) = \sqrt{\frac{35}{40}} = 0.935$

Hence, load for maximum efficiency = $0.935 \times 25 \text{ kVA} = 23.375 \text{ kVA}$

8.22 Find the efficiency of a 150 kVA transformer at 25% full load at 0.8 p.f. lagging if copper losses are 1600 W at full load and iron losses are 1400 W.

Solution

Output at 25% full load and 0.8 p.f. lagging is

$$150 \times 10^3 \times 0.25 \times 0.8 = 30,000 \text{ W}$$

$$\text{Copper losses} = 1600 \times (0.25)^2 \text{ W} = 100 \text{ W}$$

$$\text{Iron losses} = 1400 \text{ W}$$

$$\text{Total losses} = (100 + 1400) \text{ W} = 1500 \text{ W}$$

$$\therefore \text{Efficiency} = \frac{\text{Output}}{\text{Output} + \text{Losses}} = \frac{30,000}{30,000 + 1500} = 0.9524 \text{ or } 95.24\%. \dots\dots$$

8.23 Calculate the efficiency at 25% overload for a 100 kVA transformer at 0.7 p.f. The core losses are 800 W and full load copper losses are 1000 W.

Solution

$$\text{Load impedance} = 10 + j5 = 11.18 \angle 26.56^\circ \Omega$$

$$\text{Total series impedance} = (0.5 + 10) + j(1.2 + 5) = 10.5 + j 6.2 = 12.194 \angle 30.56^\circ \Omega$$

$$\text{Load current, } I_2 = \frac{400}{12.194 \angle 30.56^\circ} \text{ A} = 32.8 \angle -30.56^\circ \text{ A}$$

$$(i) \text{ Secondary terminal voltage} = I_2 \times 11.18 \angle 26.56^\circ = 366.7 \text{ V.}$$

$$(ii) \text{ Magnetising current} = \frac{400}{800} - j \frac{400}{600} = 0.5 - j0.667 = 0.833 \angle -53.14^\circ \text{ A.}$$

$$\begin{aligned} \text{Hence primary current} &= \text{load current} + \text{magnetising current} \\ &= 32.8 \angle -30.56^\circ + 0.5 - j0.667 \\ &= (28.74 - j17.34) = 33.57 \angle -31.1^\circ. \end{aligned}$$

$$(iii) \text{ Input} = (VI \cos \theta) = 400 \times 33.57 \cos (31.1^\circ) = 11497.95 \text{ W.}$$

$$\text{Total losses} = \text{Iron losses} + \text{Copper losses}$$

$$= 400 \times 0.833 \cos 53.14^\circ + (33.57)^2 \times 0.5 = 763.34 \text{ W}$$

$$\text{Efficiency} = \left(1 - \frac{\text{Loss}}{\text{Input}} \right) = 1 - \frac{763.34}{11497.95} = 0.9336 \text{ or } 93.36\%.$$

.....

8.26 A 20 kVA, 2000/220 V single-phase transformer has a primary resistance of 2.1Ω and a secondary resistance of 0.026Ω . If the total iron loss is 200 W find the efficiency on (i) full load and at a p.f. of 0.5 (lagging); (ii) half load and a p.f. of 0.8 (leading).

Solution

$$\text{Iron losses} = 200 \text{ W}$$

$$\text{Full load primary current} = \frac{20,000}{2000} = 10 \text{ A}$$

$$\text{Full load secondary current} = \frac{20,000}{220} = 90.91 \text{ A}$$

$$\begin{aligned} \text{Total copper losses at full load} &= I_1^2 R_1 + I_2^2 R_2 \\ &= (10)^2 \times 2.1 + (90.91)^2 \times 0.026 \\ &= 210 + 214.88 = 424.88 \text{ W.} \end{aligned}$$

$$(i) \text{ Output at full load and 0.5 p.f. lag} = 20 \times 10^3 \times 0.5 = 10,000 \text{ W}$$

$$\begin{aligned} \text{Input} &= \text{Output} + \text{Iron losses} + \text{Copper losses} \\ &= 10,000 + 200 + 424.88 = 10,624.88 \text{ W.} \end{aligned}$$

$$\text{So, efficiency} = \frac{\text{Output}}{\text{Input}} = \frac{10,000}{10,624.88} = 0.941 = 94.1\%.$$

$$(ii) \text{ Output at half load at 0.8 p.f. leading} = 20 \times 10^3 \times \frac{1}{2} \times 0.8 = 8000 \text{ W.}$$

$$\text{Copper loss at half load} = 424.88 \times \left(\frac{1}{2} \right)^2 = 106.22 \text{ W}$$

$$\text{Input} = 8000 + 106.22 + 200 = 8306.22 \text{ W}$$

$$\text{Efficiency} = \frac{8000}{8306.22} = 0.963 = 96.3\%.$$

.....

8.27 The primary resistance of a 440/110 V single-phase transformer is 0.28Ω and the secondary resistance is 0.018Ω . If the iron losses is measured to be 160 W when the rated primary voltage is applied, find the kW loading to give maximum efficiency at unity p.f.

Secondary copper losses at full load = $(245.53)^2 \times 0.00325 = 195.93$ W.

Total copper losses at full load = $(205.326 + 195.93)$ W = 401.25 W.

Iron losses = 170 W.

(i) Full load efficiency at a p.f. of 0.8 lag

$$= \frac{\text{Output}}{\text{Output} + \text{Total Losses}} = \frac{27.5 \times 10^3 \times 0.8}{27.5 \times 10^3 \times 0.8 + 401.25 + 170} = 0.975 = 97.5\%.$$

(ii) Let maximum efficiency occurs when load is (x) times the full load. As core losses = copper losses under this condition,

$$\therefore x^2 \times 401.25 = 170 \text{ or, } x = 0.65$$

kVA output under this condition is = $0.65 \times 27.5 = 17.9$.

$$\begin{aligned} \text{(iii) Maximum efficiency} &= \frac{17.9 \times 10^3 \times 0.8}{17.9 \times 10^3 \times 0.8 + 170 + (0.65)^2 \times 401.25} \\ &= \frac{14320}{14659.5} = 0.9768 = 97.68\%. \end{aligned}$$

8.30 A 50 kVA, 3.3 kV/230 V single-phase transformer has an impedance of 4.2% and a copper loss of 1.8% at full load. Calculate the ohmic value of resistance, reactance and impedance referred to the primary side. Estimate the primary short circuit current, assuming the supply voltage to be maintained.

Solution

$$\text{Primary full load current} = \frac{50,000}{3300} \text{ A} = 15.15 \text{ A}$$

$$\text{Now, } \frac{4.2}{100} = \frac{I_1 Z_{o1}}{V_1}$$

$$\text{or } 0.042 = \frac{15.15 Z_{o1}}{3300}$$

$$\text{or } Z_{o1} = 9.148 \Omega$$

where Z_{o1} = equivalent impedance referred to the primary.

$$\text{Again, } 0.018 = \frac{I_1^2 R_{o1}}{V_1 I_1} = \frac{I_1 R_{o1}}{V_1} = \frac{15.15 R_{o1}}{3300}$$

$$\text{or } R_{o1} = 3.92 \Omega,$$

where R_{o1} = equivalent resistance referred to the primary.

$$\therefore \text{equivalent reactance referred to the primary} = \sqrt{(9.148)^2 - (3.92)^2} \Omega = 8.26 \Omega.$$

$$\text{Under short circuit condition, the primary current} = \left(\frac{V_1}{Z_{o1}} \right) = \frac{3300}{9.148} \text{ A} = 360.73 \text{ A.}$$

8.31 A 50 kVA, 440/110 V single-phase transformer has an iron loss of 250 W. With the secondary windings short circuited full load currents flow in the windings when 25 V is applied to the primary, and the power input being 500 W. For this transformer determine (i) the percentage voltage regulation at full load, 0.8 p.f. lagging, (ii) the fraction of full load at which the efficiency is maximum.

Solution

Iron loss = 250 W.

which is proportional to the square of the applied voltage is negligibly small as compared to the copper loss. Therefore, the wattmeter reading gives the copper loss. Let the various readings be W_{sc} , V_{sc} and I_{sc} . Then

$$R_{OH} = W_{sc} / I_{sc}^2 \quad (8.31a)$$

$$Z_{OH} = V_{sc} / I_{sc} \quad (8.31b)$$

$$X_{OH} = \sqrt{(Z_{OH})^2 - (R_{OH})^2} \quad (8.31c)$$

where, R_{OH} is the equivalent resistance, (X_{OH}) is the equivalent leakage reactance and Z_{OH} is the equivalent impedance referred to the h.v. winding. These parameters refer to the winding on which measurements are made, i.e. h.v. side. From these, the various parameters as referred to other winding i.e. l.v. winding can be calculated.

8.15.3 Sumpner's test (Back to back test or Regenerative test)

To determine the maximum temperature rise of a transformer Sumpner's test is performed. This test can also be performed to find out the efficiency of a transformer. Sumpner's test is essentially a load test. It requires two identical transformers whose primaries are connected in parallel. The two secondaries are connected in series with their polarities in phase opposition. The primary windings are supplied at rated voltage and frequency. A voltmeter, ammeter and wattmeter are connected to the input as shown in Fig. 8.18. The range of the voltmeter V_2 connected across the two secondaries should be double the rated voltage of either transformer secondary. As the two secondaries are connected in phase opposition, the two secondary emfs oppose each other and no current can flow in the secondary circuit. A regulating transformer excited by an ac mains supply is used to inject voltage in the secondary winding. The injected voltage is adjusted till the ammeter A_2 reads full load secondary current. The secondary

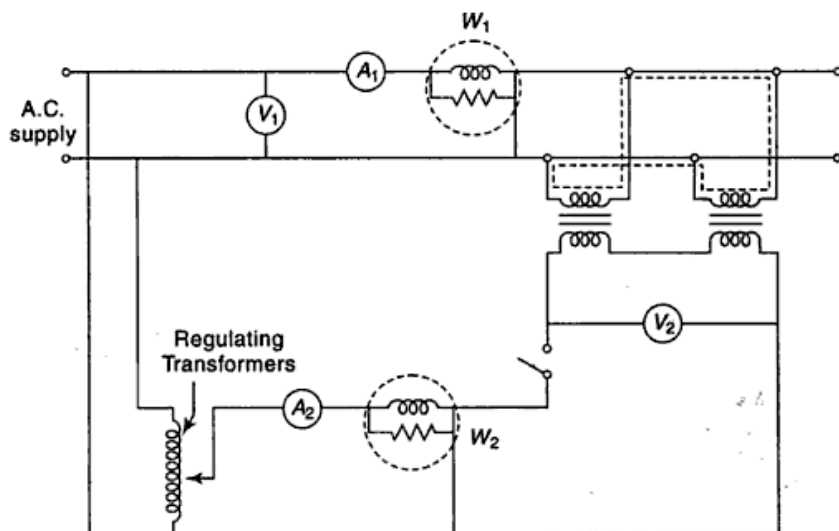


Fig. 8.18 Sumpner's test

current causes full load current to flow through the primary windings whereas the primary current remains confined to the dotted path as shown in Fig. 8.18. The wattmeter W_1 indicates total core losses, W_2 indicates total copper losses and ammeter A_1 indicates total no load current of the two transformers. Thus by this method we can load the transformer to full load but the supplying energy is only equal to that required for the losses only. This test can be continued for a long time to determine the maximum temperature rise of a transformer.

8.32 Calculate the values of R_o , X_o , R_1 and X_1 in the diagram shown in Fig. 8.19 of a single-phase 8 kVA, 22/440 V, 50 Hz transformer of which the following are the test results:

Open circuit test

220 V, 0.9 A, 90 W on the low voltage side.

Short circuit test

20 V, 15 A, 100 W on the high voltage side.

Solution

From the open circuit test data,

$$\text{No load p.f. } \cos \theta_o = \frac{90}{220 \times 0.9} = 0.4545$$

$$\therefore \sin \theta_o = 0.89$$

$$\text{Core loss resistance } R_o = \frac{V_1}{I_o \cos \theta_o} = \frac{220}{0.9 \times 0.4545} \Omega = 537.83 \Omega$$

$$\text{Magnetizing reactance } X_o = \frac{V_1}{I_o \sin \theta_o} = \frac{220}{0.89 \times 0.9} = 274.65 \Omega$$

From short circuit test data,

$$R_{OH} = R_{o2} = \frac{100}{(15)^2} \Omega = 0.444 \Omega$$

$$Z_{OH} = Z_{o2} = \frac{20}{15} \Omega = 1.33 \Omega$$

where R_{o2} and Z_{o2} are the equivalent resistance and impedance referred to the high voltage side.

$$\text{Hence, } X_{OH} = X_{o2} = \sqrt{(1.33)^2 - (0.44)^2} = 1.257 \Omega$$

Figure 8.19 shows the equivalent resistance R_1 and reactance X_1 referred to the low voltage side or primary side.

$$\text{Hence, } R_1 = 0.444 \times \left(\frac{220}{440}\right)^2 = 0.111 \Omega$$

$$\text{and } X_1 = 1.257 \times \left(\frac{220}{440}\right)^2 = 0.314 \Omega$$

$$\text{Also } R_o = 537.83 \Omega \text{ and } X_o = 274.65 \Omega.$$

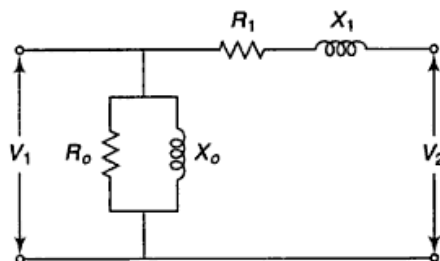


Fig. 8.19 Circuit diagram for Example 8.32

8.33 Short circuit test performed on the h.v. side of a 100 kVA, 6600/440 V, single-phase transformer yields the following results: 100 V, 6 A, 200 W. If the low voltage side is delivering full load current at 0.8 p.f. lag and at 440 V find the voltage applied to the high voltage side.

(iii) From short circuit test data,

$$R_{02} = \frac{20}{(3)^2} = 2.22 \, \Omega, (Z_{02}) = \frac{50}{3} = 16.67 \, \Omega$$

$$\text{and } (X_{02}) = \sqrt{(16.67)^2 - (2.22)^2} = 16.52 \, \Omega.$$

If V_2 be the terminal voltage then,

$E_2 - V_2 = I_2 R_{02} \cos \theta_2 + I_2 X_{02} \sin \theta_2$, where E_2 is the secondary voltage under no load condition and $\cos \theta_2$ is the load p.f. which is unity in this case.

$$\therefore (2000 - V_2) = 4(2.22 \times 1 + 16.52 \times 0)$$

$$\text{or } (V_2) = 2000 - 8.88 = 1991.12 \, \text{V}.$$

8.35 The following results were obtained in tests on a 50 kVA, single-phase, 3300/400 V transformer.

Open circuit test: 3300 V, 430 W

Short circuit test: 124 V, 15.3 A, 535 W.

(supply given on h.v. side)

Calculate (i) the efficiency at full load and half full load both at 0.707 p.f. lagging, (ii) the regulation at full load for p.f. of 0.707 (lagging and leading) and (iii) full load terminal voltage under the condition of 0.707 p.f. (lagging).

Solution

For short circuit test data,

$$Z_{e1} = \frac{124}{15.3} \, \Omega = 8.10 \, \Omega, R_{01} = \frac{535}{(15.3)^2} \, \Omega = 2.285 \, \Omega$$

$$X_{01} = \sqrt{(8.1)^2 - (2.285)^2} = 7.77 \, \Omega$$

$$(i) \text{ Rated current on the h.v. side} = \frac{50,000}{3300} \, \text{A} = 15.15 \, \text{A}$$

$$\text{So, rated copper loss} = 535 \times \left(\frac{15.15}{15.3} \right)^2 = 524.56 \, \text{W}$$

Iron loss = 430 W

Efficiency at full load and 0.707 p.f. lagging

$$= \frac{50 \times 10^3 \times 0.707}{50 \times 10^3 \times 0.707 + 524.56 + 430} = 0.9737 \text{ or } 97.37\%.$$

Efficiency at half load and 0.707 p.f. lagging is

$$= \frac{50 \times 10^3 \times 0.707 \times \frac{1}{2}}{50 \times 10^3 \times (0.707) \times \frac{1}{2} + \left(\frac{1}{2} \right)^2 \times 524.56 + 430} = 0.9623 \text{ or } 96.93\%.$$

(ii) Voltage regulation at full load and 0.707 lagging p.f. is

$$= \frac{I_1 R_{01} \cos \theta + I_1 X_{01} \sin \theta}{E_1} = \frac{15.15 (2.285 \times 0.707 + 7.77 \times 0.707)}{3300} = 0.0326 = 3.26\%$$

Voltage regulation at full load and 0.707 p.f. leading

$$= \frac{I_1 R_{01} \cos \theta - I_1 X_{01} \sin \theta}{E_1} = \frac{15.15 (2.285 \times 0.707 - 7.77 \times 0.707)}{3300} = (-0.0178) \text{ or } (-1.78\%).$$

continuity of supply is maintained. For satisfactory parallel operation of transformers the following two conditions are necessary:

- (a) The polarities of the transformers must be same.
- (b) The turns ratios of the transformers should be equal.

The other two desirable conditions are:

- (a) Equal per unit impedance in magnitude and phase angle
- (b) Equal voltages at full load across transformer terminals.

Figure 8.20 shows two single-phase transformers in parallel, connected to the same voltage source on the primary side. Terminals with proper polarity markings have been connected both on the h.v. and l.v. sides.

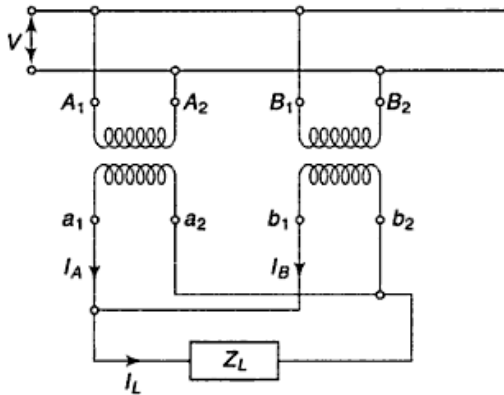


Fig. 8.20 Two-single phase transformers in parallel

Here I_L is the load current and I_A and I_B are the current supplied by the two transformers to the load.

Hence, $I_A + I_B = I_L$.

If K_1 and K_2 be the turns ratio of the two transformers

then $V_L = \frac{V}{K_1} - I_A Z_A$

and $V_L = \frac{V}{K_2} - I_B Z_B = \frac{V}{K_2} - (I_L - I_A) Z_B$

where, Z_A and Z_B are the equivalent impedance of the two transformers referred to the secondary.

Solving the above two equations

$$I_A = \frac{Z_B I_L}{Z_A + Z_B} + \frac{V(K_2 - K_1)}{K_1 K_2 (Z_A + Z_B)} \quad (8.32)$$

$$I_B = \frac{Z_A I_L}{Z_A + Z_B} - \frac{V(K_2 - K_1)}{K_1 K_2 (Z_A + Z_B)} \quad (8.33)$$

Each of these currents has two components; the first component represents the transformer's share of the load current and the other component is a circulating current in the secondary windings. Circulating currents increase the copper loss and may overload one transformer. In order to eliminate the circulating currents the turns ratios must be identical, i.e. $K_1 = K_2 = K$.

Hence,
$$I_A = \frac{Z_B I_L}{Z_A + Z_B} \quad \text{and} \quad I_B = \frac{Z_A I_L}{Z_A + Z_B}$$

Therefore,
$$\frac{I_A}{I_B} = \frac{Z_B}{Z_A}$$

Also,
$$I_A Z_B = I_B Z_A$$

or $S_A = S_B$, where (S_A) and (S_B) are the VA of the two transformers.

$$\therefore S_A = \frac{Z_B}{Z_A + Z_B} S_L \quad (8.34)$$

and
$$S_B = \frac{Z_A}{Z_A + Z_B} S_L \quad (8.35)$$

where S_L is the total load VA.

$$\therefore \frac{S_A}{S_B} = \frac{Z_B}{Z_A} \quad (8.36)$$

8.17 SINGLE-PHASE AUTO TRANSFORMER

An auto transformer is a single winding transformer in which a part of the winding is common to both the high voltage and low voltage side. Figure 8.21 shows a step down auto transformer. The primary winding AB has N_1 number of turns and the secondary winding BC has N_2 number of turns. The winding BC is common to both the primary and secondary. The induced emf in the primary winding AB is

E_1 and in the secondary winding BC is E_2 . Hence $\frac{E_1}{E_2} = \frac{N_1}{N_2} = K$, where K is the

turns ratio. The input current is I_1 and the load current is I_2 . The mmfs $I_1 N_1$ and $I_2 N_2$ will be equal and opposite. If terminal C is a sliding contact, the output voltage V_2 can be varied. The voltampere delivered to the load $V_2 I_2 = V_2 I_1 + V_2(I_2 - I_1)$. ($V_2 I_1$) is the voltamperes transferred conductively to the load through winding AC and $V_2(I_2 - I_1)$ is the voltamperes transferred inductively to the load through winding BC which represents the rating of the equivalent two winding transformer.

Hence,
$$\frac{\text{Output VA of auto transformer}}{\text{Output VA of equivalent a two-winding transformer}} = \frac{V_2 I_2}{V_2 (I_2 - I_1)} = \frac{a}{a - 1} \quad (8.37)$$

Figure 8.22 represents a step up auto transformer. Here input voltampere $V_1 I_1 = V_1 I_2 + V_1(I_1 - I_2)$.

Hence
$$\frac{\text{Output VA of auto transformer}}{\text{Output VA of equivalent two winding transformer}} = \frac{V_1 I_1}{V_1 (I_1 - I_2)} = \frac{a}{a - 1} \quad (8.38)$$

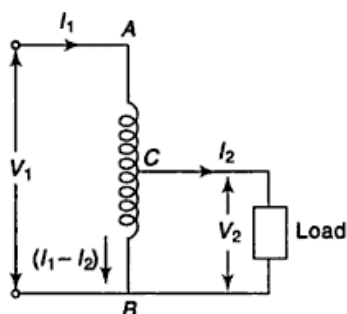


Fig. 8.21 Step down auto transformer

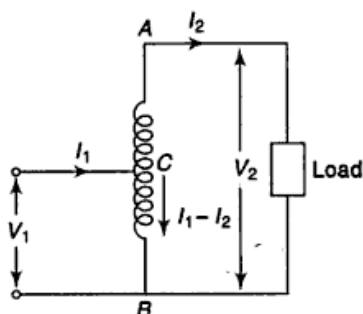


Fig. 8.22 Step up auto transformer

8.17.1 Advantages of an Auto Transformer

- For the same capacity and voltage ratio, an auto transformer requires less winding material than a two-winding transformer. Hence there is saving in copper.
- An auto transformer is smaller in size and cheaper than a two winding transformer of same output.
- An auto transformer has higher efficiency since core loss and ohmic losses are smaller.
- Voltage regulation of an auto transformer is better because of reduced voltage drops in the resistance and reactance.
- An auto transformer has variable output voltage when a sliding contact is used for the secondary.

8.17.2 Disadvantages of an Auto Transformer

- There is direct connection between the high voltage and low voltage side. If there is an open circuit in the winding BC (Fig. 8.21) the full primary voltage would be applied to the secondary. This high voltage may cause serious damage to the equipments connected on the secondary side.
- The short circuit current is larger for an auto transformer due to reduced internal impedance.

8.17.3 Applications of Auto Transformers

- Auto transformers are used for obtaining continuously variable ac voltage.
- They are used for interconnections of power systems of different voltage levels.
- They are applied for boosting of ac mains voltage by a small amount.
- Auto transformers are used for starting the induction motors and synchronous motors.

8.18 TRANSFORMER COOLING

The core and copper losses cause heating of transformers. It is necessary to ensure that the temperature of the transformer does not exceed the maximum value, otherwise it may cause damage to the insulation. The following are the methods for cooling these type of transformers.

- (a) **Air Natural Cooling** Small transformers up to 25 kVA are cooled by natural circulation of air surrounding it.
- (b) **Air Blast Cooling** In this type of cooling continuous blast of filtered air is forced through the core and windings for better cooling.
- (c) **Oil Natural Cooling** A majority of transformers have their core and windings immersed in oil. Oil is a good insulating material and provides better heat dissipation than air. Oil immersed transformers are enclosed in sheet steel tank. The heat produced in the transformer is passed to the oil. The oil is heated and it becomes lighter and rises to the top and its place is taken by cool air from the bottom of the tank.

The heat of the air is transferred to the tank by natural circulation of air. The heat is then transferred to the surrounding atmosphere.

- (d) **Oil Blast Cooling** Here forced air is passed over cooling elements of transformer immersed in oil.
- (e) **Forced Oil and Forced Air Cooling** Heated oil is taken from the top of the transformer tank to a cooling plant. Cooled oil is then circulated through the bottom of the tank.
- (f) **Forced Oil and Water Cooling** In this type of cooling metallic tubes are situated inside the tank, below the oil level. Water is circulated through these tubes to extract heat from the oil.

8.19 CONSERVATOR AND BREATHER

A *conservator* is an air tight metallic drum supported on a transformer top cover. It takes up the expansion of oil with changes in temperature. When the oil is cold the tank is filled with oil. When the temperature of the oil rises, the oil expands and the expansion is taken up in the conservator. When the transformer cools, the level of oil goes down and the air is drawn in. The incoming air is passed through a device called breather for extracting moisture. A *breather* consists of a small vessel which contains a drying agent like silica gel or calcium chloride.

8.20 DISTRIBUTION TRANSFORMERS AND POWER TRANSFORMERS

Distribution transformers are used to step down the transmission voltage to a lower value suitable for distribution. They are kept in operation all 24 hours in a day whether they carry any load or not. They have better voltage regulation and small leakage reactance.

Power transformers are used in generating stations or substations at each end of transmission line for stepping up or stepping down the voltage. They are put in service during load periods and are disconnected during light load periods. They have greater leakage reactance and have maximum efficiency at or near full load.

8.21 NAME PLATE AND RATINGS

The specifications of transformers are given by BIS (Bureau of Indian Standard) 2026. As per this standard every transformer must be provided with the following specifications:

Type (power, distribution, auto, etc.), year of manufacture, number of phases, rated kVA, rated frequency, rated voltage of each winding, connection symbol, percent impedance voltage at rated current, type of cooling, total mass, mass and volume of insulating oil.

8.22 ALL DAY EFFICIENCY

It is usual for the primary of a transformer to be connected permanently to the supply and for the switching of load to be carried out in the secondary circuit. Since the copper loss varies with load but iron loss is constant and the efficiency depending on loading and losses vary throughout the day. For transformers which are continuously excited but supply loads only intermittently, a low iron loss is particularly desirable, but a low copper loss is specially important where the load factor is high. Again for a transformer working on full load for greater part of the day, maximum efficiency should be arranged to occur some where around the full load value but for a transformer whose full load value may be supplied for only 1/4 of the day and the unit is only lightly loaded for the rest of the time, it would be desirable to arrange maximum efficiency to occur at about 1/2 full load value.

Considering the above factors the efficiency of a transformer is better estimated on an energy rather than a power ratio and thus we have the term "all day efficiency".

$$\text{All day efficiency} = \frac{\text{Output in KWh for 24 hr.}}{\text{Input in KWh for 24 hr.}}$$

8.23 THREE-PHASE TRANSFORMER

The present day power system is a three-phase system. The change of voltage in a three-phase system is performed either by a single three-phase transformer or by a three single-phase transformers. The advantages of a three-phase transformer over three single-phase transformers are:

- (a) The space required is smaller.
- (b) It is lighter and cheaper.
- (c) It is more efficient.

A single unit three-phase transformer has a three-limbed core, one limb for each phase winding. On each limb the low voltage winding is placed over the core and the high voltage winding is placed over the low voltage winding with suitable insulation between the core and low voltage winding as well as between the two windings. Figure 8.23 and Fig. 8.24 shows the schematic diagram of a three-phase core type and shell type transformer respectively.

The primary and secondary winding of a three-phase transformer can be connected in star or delta. Hence four main connections are possible,

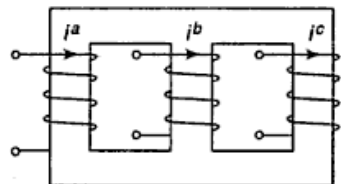


Fig. 8.23 Three-phase core type transformer

star-star, star-delta, delta-star and delta-delta. In star-star connection both the primary and secondary windings are connected in star. The neutral point is denoted by N for high voltage winding and n for low voltage winding and the connection is shown in Fig. 8.25. The phase current is equal to the line current but the line voltage is $(\sqrt{3})$ times the phase voltage in both the primary and secondary windings. For delta-delta connection both the primary and secondary windings are connected in delta as shown in Fig. 8.26. Here the line voltage is equal to phase voltage on each side. The phase current is line current divided by $(\sqrt{3})$. As compared to a star-star connection for the same terminal voltage and current, a delta-delta connection has more number of turns in each phase winding but less cross-sectional area of conductors. Hence a delta-delta connection is more economical for large transformers of relatively lower voltage rating. The star-star connection is not used in a three-phase three-wire system due to undesirable effects of a third harmonic current.

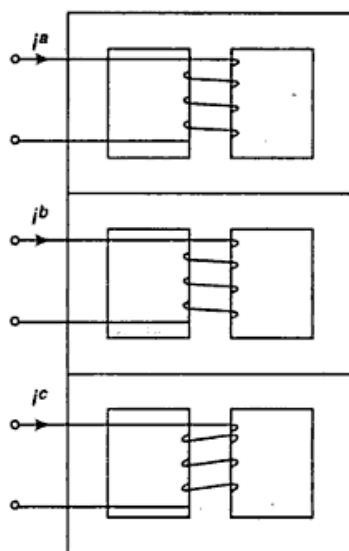


Fig. 8.24 Three-phase shell type transformer

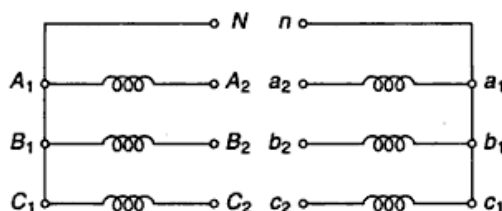


Fig. 8.25 Three-phase star-star transformer

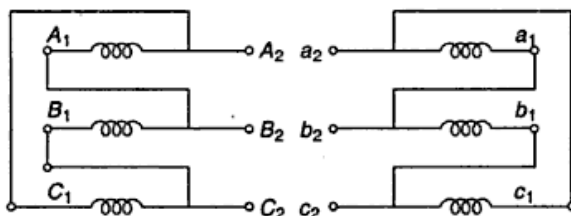


Fig. 8.26 Three-phase delta-delta transformer

Figure 8.27 shows the connection for a three-phase star-delta transformer. On the primary side the line voltage is $(\sqrt{3})$ times the phase voltage while the line and phase voltages are equal on the secondary side. Generally, the high voltage winding is star connected for reducing cost of insulation. This connection is generally used for step down transformers at receiving end substations.

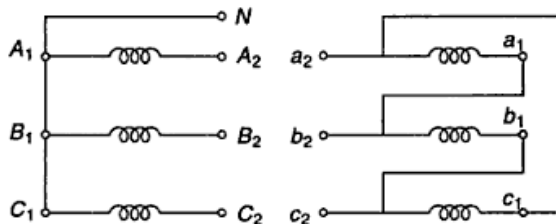


Fig. 8.27 Three-phase star-delta transformer

The connection of a three-phase delta-star transformer is shown in Fig. 8.28. On the primary side the line and phase voltages are equal, but on the secondary side the line voltage is $(\sqrt{3})$ times the phase voltage. These transformers are used at sending and receiving end substations. At power stations the generator feeds the delta winding and the star winding is connected to h.v. transmission lines. In distribution transformers, feeders are connected to delta winding and the star winding supplies three-phase four-wire distributors

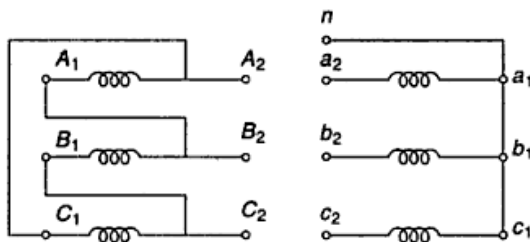


Fig. 8.28 Three-phase delta-star transformer

8.37 A transformer has its maximum efficiency of 0.975 at 20 kVA at unity p.f. During the day it is loaded as follows:

10 hr: 3 kW at 0.6 p.f.

8 hr: 10 kW at 0.8 p.f.

6 hr: 20 kW at 0.9 p.f.

Find the all day efficiency.

Solution

$$\text{kWh output} = (10 \times 3) + (8 \times 10) + (6 \times 20) = 30 + 80 + 120 = 230 \text{ kWh}$$

As maximum efficiency is 0.975 so total losses under this condition is $[1 - 0.975] = 0.025$ of output power.

At unity p.f. output power = $20 \times 1 = 20 \text{ kW}$

Hence losses = $0.025 \times 20,000 = 500 \text{ W}$

$$\therefore \text{core losses} = \text{copper losses} = \frac{500}{2} \text{ W} = 250 \text{ W}$$

As core loss is constant for all p.f. so total core losses in 24 hr.

$$= \frac{250 \times 24}{10^3} \text{ kWh} = 6 \text{ kWh}$$

For the first 10 hr.

$$\text{kVA load} = \frac{3}{0.6} = 5$$

$$\text{Total copper losses} = 10 \times \left(\frac{5}{20}\right)^2 \times \frac{250}{1000} \text{ kWh} = 0.156 \text{ kWh}$$

For the next 8 hr.

$$\text{kVA load} = \frac{10}{0.8} = 12.5$$

$$\text{Total copper losses} = 8 \times \left(\frac{12.5}{20} \right)^2 \times \frac{250}{1000} \text{ kWh} = 0.781 \text{ kWh.}$$

For the last 6 hr.

$$\text{kVA load} = \frac{20}{0.9} = 22.22$$

$$\text{Total copper losses} = 6 \times \left(\frac{22.22}{20} \right)^2 \times \frac{250}{1000} \text{ kWh} = 1.85 \text{ kWh}$$

$$\text{Total copper losses} = 0.156 + 0.781 + 1.85 = 2.79 \text{ kWh}$$

$$\text{Total loss} = 6 \text{ kWh} + 2.79 \text{ kWh} = 8.79 \text{ kWh}$$

$$\text{All day efficiency} = \frac{230}{230 + 8.79} = 0.963 \text{ or } 96.3\%.$$

.....

8.38 A lighting transformer rated at 10 kVA has full load losses of 0.3 kW which is made up equally from the iron losses and the copper losses. The duty cycle consists of full load for 3 hours, half full load for 4 hours and no load for the remainder of a 24 hours period. If the load operates at unity power factor, calculate the all day efficiency.

Solution

The load operates at unity power factor.

For the first three hours,

$$\text{Energy output} = 10 \times 1 \times 3 \text{ kWh} = 30 \text{ kWh}$$

For the next four hours,

$$\text{Energy output} = \frac{1}{2} \times 10 \times 1 \times 4 = 20 \text{ kWh}$$

$$\text{Total energy output} = (30 + 20) \text{ kWh} = 50 \text{ kWh}$$

$$\text{Full load losses} = 0.3 \text{ kW}$$

$$\text{So, iron loss} = \left(\frac{0.3}{2} \right) \text{ kW} = 0.15 \text{ kW}$$

$$\text{and full load copper loss} = \frac{0.3}{2} \text{ kW} = 0.15 \text{ kW}$$

$$\text{Iron loss energy} = (0.15 \times 24) = 3.6 \text{ kWh}$$

$$\text{Copper loss energy} = \left(0.15 \times 3 + \frac{0.15}{(2)^2} \times 4 \right) \text{ kWh} = (0.45 + 0.15) \text{ kWh} = 0.6 \text{ kWh}$$

$$\text{Energy loss} = (3.6 + 0.6) \text{ kWh} = 4.2 \text{ kWh}$$

$$\therefore \text{All day efficiency} = \frac{50}{50 + 4.2} = 0.922 \text{ or } 92.2\%.$$

.....

8.39 The maximum efficiency of a 100 kVA, single-phase transformer is 95% and occurs at 90% of full load at 0.85 p.f. If the leakage impedance of the transformer is 5%, find the voltage regulation at rated load 0.8 p.f. lagging.

Solution

$$\text{Output at maximum efficiency} = 100 \times 0.9 \times 0.85 = 76.5 \text{ kW}$$

$$\text{Efficiency} = (0.95) = \frac{\text{Output}}{\text{Output} + \text{Losses}} = \frac{76.5}{76.5 + \text{Losses}}$$

$$\text{Ohmic losses for 7 hours} = \left(\frac{8.89}{10}\right)^2 \times 120 = 94.84 \text{ W}$$

$$\text{Energy lost as ohmic loss} = 94.84 \times 7 = 663.87 \text{ Wh}$$

$$\text{Daily energy lost as ohmic loss} = (367.36 + 180 + 663.87) \times 10^{-3} \text{ kWh} = 1.211 \text{ kWh}$$

$$\text{Daily energy lost as core loss} = \frac{50 \times 24}{10^3} \text{ kWh} = 1.2 \text{ kWh}$$

$$\text{Total loss} = (1.211 + 1.2) = 1.411 \text{ kWh}$$

$$\text{Daily output} = (30 + 24 + 56) = 110 \text{ kWh}$$

$$\text{All day efficiency} = \frac{110}{110 + 1.411} = 0.9872 \text{ or } 98.73\%.$$

.....

8.41 Two 200 kVA single-phase transformers are to be operated in parallel. The internal impedance of transformer 1 is $(0.006 + j0.08)$ p.u. while transformer 2 has an internal impedance of $(0.008 + j0.05)$ p.u. How will they share a load of 300 kW at 0.8 lagging power factor?

Solution

$$Z_1 = (0.006 + j0.08) = 0.08 \angle 85.71^\circ$$

$$Z_2 = (0.008 + j0.05) = 0.0506 \angle 80.91^\circ$$

$$\text{Load } S_L = \frac{300}{0.8} \angle -\cos^{-1} 0.8 = 375 \angle -36.87^\circ \text{ kVA.}$$

Load shared by transformer 1

$$S_1 = \frac{Z_2}{Z_1 + Z_2} S_L$$

$$\begin{aligned} \therefore S_1 &= \frac{0.0506 \angle 80.91^\circ}{(0.006 + 0.008) + j(0.08 + 0.05)} \times 375 \angle -36.87^\circ \\ &= \frac{0.0506 \angle 80.91^\circ \times 375 \angle -36.87^\circ}{0.13075 \angle 83.85^\circ} = 145.12 \angle -39.81^\circ \text{ kVA.} \end{aligned}$$

Load shared by transformer 2

$$S_2 = \frac{Z_1}{Z_1 + Z_2} S_L$$

$$\therefore S_2 = \frac{0.08 \angle 85.71^\circ}{(0.006 + 0.008) + j(0.08 + 0.05)} \times 375 \angle -36.87^\circ = 229.44 \angle -35^\circ \text{ kVA.}$$

.....

8.42 A 1000 kVA transformer with $(0.02 + j0.1)$ p.u. impedance and a 500 kVA transformer with $(0.015 + j0.05)$ p.u. impedance are operating in parallel. The no load secondary voltages of the two transformers are equal. How will they share a load of 1500 kVA at unity p.f. load?

Solution

Let base kVA = 100 kVA

$$Z_1 = (0.02 + j0.1) = 0.102 \angle 78.69^\circ$$

Converting impedance of second transformer to base kVA

$$Z_2 = \frac{1000}{500} (0.015 + j0.05) = (0.03 + j0.1) = 0.104 \angle 73.3^\circ$$

$$\text{Load } (S_L) = 1500 \angle 0^\circ \text{ kVA.}$$

Hence, load shared by transformer 1

$$S_1 = 1500 \angle 0^\circ \times \frac{0.104 \angle 73.3^\circ}{(0.02 + 0.03) + j(0.1 + 0.1)}$$

$$= \frac{1500 \times 0.104 \angle 73.3^\circ}{0.206 \angle 75.96^\circ} = 757.28 \angle -2.66^\circ \text{ kVA.}$$

Load shared by transformer 2

$$S_2 = 1500 \angle 0^\circ \times \frac{0.102 \angle 78.69^\circ}{(0.02 + 0.03) + j(0.1 + 0.1)} = 742.72 \angle 2.73^\circ \text{ kVA.}$$

8.43 A 200 VA, 240/120 V two-winding transformer is to be used as an auto transformer. The input voltage is 240 V. Find the secondary voltage. What is the maximum VA rating of an auto transformer?

Solution

The auto transformer is shown in Fig. 8.29

Input $V_1 = 240$ V across winding BC

Hence voltage across winding AC is 120 V.

Therefore, the voltage across winding AB, i.e. secondary voltage of the auto transformer is $(240 + 120)$ V i.e. 360 V or $V_2 = 360$ V.

$$\text{Now current in the secondary winding} = \frac{200}{120} \text{ A}$$

for two-winding transformers.

$$\text{Hence for auto transformer } I_2 = \frac{200}{120} \text{ A}$$

The maximum VA rating of auto transformer is $V_2 I_2$

$$\text{i.e. } \left(360 \times \frac{200}{120} \right) \text{ VA or 600 VA.}$$

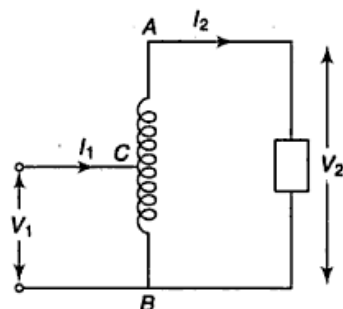


Fig. 8.29 Circuit diagram for Example 8.43

8.44 A 10 kVA, 2400/240 V two-winding transformer is reconnected as a step down auto transformer as shown in Fig. 8.30 and excited by a 2640 V source. The transformer is loaded so that the rated currents of the windings are not exceeded. Calculate the currents in different sections of the auto transformer and kVA output.

Solution

$$\text{Current rating of 2400 V winding is } \frac{10,000}{2400} \text{ A,}$$

$$\text{i.e. 4.167 A}$$

$$\text{Current rating of 240 V winding is } \frac{10,000}{240} \text{ A, i.e. 41.67 A}$$

$$\text{Load current } I_L = (4.167 + 41.67) \text{ A} = 45.837 \text{ A}$$

$$\text{kVA output} = \frac{2400 \times 45.837}{1000} = 110$$

The currents in different sections of auto transformer is shown in Fig. 8.30.

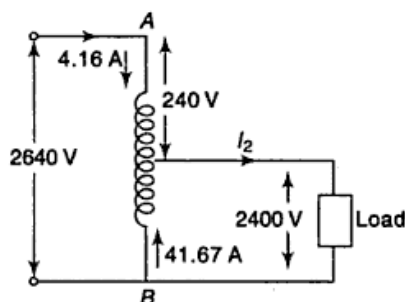


Fig. 8.30 Circuit diagram for Example 8.44

8.45 A three-phase step down transformer is connected to 3300 V on the primary side. The ratio of turns per phase is 15 and the line current drawn from the mains is 30 A. Find the secondary line voltage, line current and output when transformer is (i) YY and (ii) ΔY.

Solution

$$\text{Input} = (\sqrt{3} V_L I_L) = \sqrt{3} \times 3300 \times 30 \text{ VA} = 171.47 \text{ kVA}$$

Neglecting losses, output = 171.47 kVA

$$\text{Turns ratio } \left(\frac{N_1}{N_2} \right) = 15.$$

- (i) $\frac{V_{1\text{Ph}}}{V_{2\text{Ph}}} = \frac{N_1}{N_2} = 15$, where ($V_{1\text{Ph}}$) and ($V_{2\text{Ph}}$) phase voltage of primary and secondary respectively.

$$\text{Now, } V_{1\text{Ph}} = \frac{V_{1L}}{\sqrt{3}} = \frac{3300}{\sqrt{3}} \text{ V}$$

$$\text{Hence, } V_{2\text{Ph}} = \frac{3300}{\sqrt{3} \times 15} \text{ V} = 127 \text{ V.}$$

$$\text{Secondary line voltage} = (127 \times \sqrt{3}) \text{ V} = 220 \text{ V} = V_{2L}$$

For Y connection line current = phase current

$$(\sqrt{3} V_{2L} I_{2L}) = 171.47 \times 10^3$$

$$\text{i.e., Secondary line current } I_{2L} = \frac{171.47 \times 10^3}{\sqrt{3} \times 220} = 450 \text{ A.}$$

- (ii) For ΔY connection primary is connected in delta and secondary in star.

$$\text{Hence, } V_{1\text{Ph}} = V_{1L} = 3300 \text{ V}$$

$$\therefore V_{2\text{Ph}} = \frac{V_{1\text{Ph}}}{15} = \frac{3300}{15} \text{ V} = 220 \text{ V}$$

$$\text{Hence secondary line voltage } (V_{2L}) = 220 \sqrt{3} \text{ V}$$

$$\text{Now, } (\sqrt{3} V_{2L} I_{2L}) = 171.47 \times 10^3$$

$$\therefore \text{secondary line current} = \frac{171.47 \times 10^3}{\sqrt{3} \times 220 \times \sqrt{3}} = 260 \text{ A.}$$

.....

■ ADDITIONAL PROBLEMS ■

8.46 The core of a single-phase 3300/440 V, 50 Hz transformer is of square cross-section, each side being 140 mm. If the maximum flux density in the core is not to exceed 1 T, find the number of turns required for each winding.

Solution

$$\begin{aligned} \text{Flux} &= \text{Flux density} \times \text{Area} \\ &= 1 \times (140 \times 10^{-3})^2 = 0.0196 \text{ Wb.} \end{aligned}$$

If N_1 and N_2 be the number of turns of the primary and secondary windings respectively then,

$$3300 = 4.44 \times 0.0196 \times 50 \times N_1 \quad (\because E_1 = 4.44 \phi_m f N_1)$$

$$\text{or } N_1 = 758.4 \text{ or, } 758 \text{ (say)}$$

As
$$\frac{N_1}{N_2} = \frac{E_1}{E_2}$$

So,
$$N_2 = N_1 \frac{E_2}{E_1} = 758 \times \frac{440}{3300} = 101.$$

8.47 For the no load test on a transformer, the ammeter was found to read 0.18 A and the wattmeter 12 W. The reading on the primary voltmeter was 400 V and on the secondary voltmeter was 240 V. Calculate the magnetizing component of the no load current, the iron loss component and the transformation ratio.

Solution

Core loss or iron loss component of no load current $I_C = \frac{12}{400} = 0.03$ A.

No load current = 0.18 A

So magnetizing component of no load current = $\sqrt{(0.18)^2 - (0.03)^2} = 0.178$ A.

Transformation ratio = $\frac{400}{240} = \frac{5}{3} = 1.67:1.$

8.48 A single-phase transformer with a ratio of 440/200 V takes a no load current of 8 A at a p.f. of 0.25 (lagging). If the secondary supplies a current 220 A at a p.f. of 0.8 (lagging), estimate the current taken by the primary from the supply.

Solution

Secondary load current $I_2 = 220$ A

\therefore load component of the primary current ($= I_1'$) = $I_2 \times \frac{N_2}{N_1} = 220 \times \frac{200}{440} = 100$ A.

No load component of the primary current $I_o = 8$ A.

Referring to Fig. 8.31, the horizontal and vertical components of I_1' are ($I_1' \sin \theta$) and ($I_1' \cos \theta$), where $\cos \theta = 0.8$. Similarly, the horizontal and vertical components of I_o are ($I_o \sin \theta_o$) and ($I_o \cos \theta_o$) where $\cos \theta_o = 0.25$. So, the horizontal component of the primary current

$$= (I_1' \sin \theta + I_o \sin \theta_o)$$

i.e. $I_{1H} = 100 \sin (\cos^{-1} 0.8) + 8 \sin (\cos^{-1} 0.25)$
 $= 67.75$ A

Vertical component of the primary current

$$I_{1V} = (I_1' \cos \theta + I_o \cos \theta_o)$$

$$= 100 \times 0.8 + 8 \times 0.25 = 82$$
 A.

So the total primary current $I_1 = \sqrt{(82)^2 + (67.75)^2} = 106.37$ A.

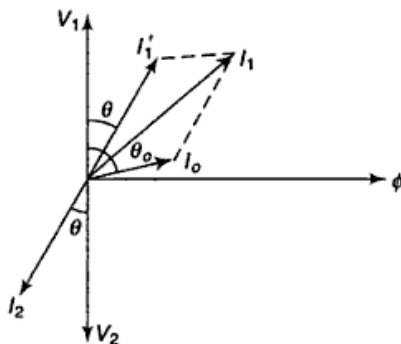


Fig. 8.31 Figure for Example 8.48

8.49 A 6600/440 V single-phase transformer has a primary resistance of 140 Ω and a secondary resistance of 0.25 Ω . Calculate the equivalent resistances referred to the secondary winding and primary winding respectively.

Solution

Primary resistance $R_1 = 140$ Ω

Secondary resistance $R_2 = 0.25$ Ω

Secondary resistance referred to primary $R_2' = 0.25 \times \left(\frac{N_1}{N_2}\right)^2$

$$= 0.25 \times \left(\frac{6600}{440}\right)^2 = 56.25 \Omega.$$

So, equivalent resistance referred to primary

$$R_{o1} = r_1 + r_2' = 140 + 56.25 = 196.25 \Omega$$

Now, primary resistance referred to secondary $R_1' = 140 \times \left(\frac{N_2}{N_1}\right)^2$

$$= 140 \times \left(\frac{440}{6600}\right)^2 = 0.6222 \Omega.$$

So, equivalent resistance referred to secondary

$$R_{o2} = R_1' + R_2 = 0.622 + 0.25 = 0.872 \Omega. \quad \dots\dots$$

8.50 A 17.5 kVA, 460/115 V single-phase, 50 Hz transformer has primary and secondary resistances of 0.36 Ω and 0.02 Ω respectively and the leakage reactances of these windings are 0.82 Ω and 0.06 Ω respectively. Determine the voltage to be applied to the primary to obtain full load current with the secondary winding short circuited. Neglect the magnetizing current.

Full load primary current $I_1 = \frac{17500}{460} = 38.04 \text{ A}$

$$R_1 = 0.36 \Omega \quad \text{and} \quad R_2 = 0.02 \Omega$$

$$X_1 = 0.82 \Omega \quad \text{and} \quad X_2 = 0.06 \Omega.$$

Equivalent resistance referred to the primary

$$R_{o1} = R_1 + R_2' = 0.36 + 0.02 \left(\frac{460}{115}\right)^2 = 0.68 \Omega.$$

Equivalent reactance referred to the primary

$$X_{o1} = X_1 + X_2' = 0.82 + 0.06 \times \left(\frac{460}{115}\right)^2 = 1.78 \Omega.$$

Equivalent impedance referred to the primary

$$Z_{o1} = \sqrt{(0.68)^2 + (1.78)^2} = 1.905 \Omega.$$

As the secondary is short circuited the voltage applied to the primary to obtain full load current $= I_1 Z_{o1}$

$$= (38.04 \times 1.905) = 72.48 \text{ V}. \quad \dots\dots$$

8.51 A 20 kVA, 2000/220 V single-phase transformer has a primary resistance of 2.1 Ω and a secondary resistance of 0.026 Ω . If the total iron loss equals 200 W, find the efficiency on (i) full load and at a p.f of 0.5 lagging (ii) half load and a p.f of 0.8 leading.

Solution

$$\text{Iron loss} = 200 \text{ W}$$

$$\text{Secondary current} = \frac{20 \times 10^3}{220} = 90.91 \text{ A}$$

Equivalent resistance referred to the secondary

$$= 2.1 \times \left(\frac{220}{2000}\right)^2 + 0.026 = 0.0514 \Omega$$

$$\text{Total copper losses} = (90.91)^2 \times 0.0514 = 424.8 \text{ W}$$

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}} = \frac{\text{Output}}{\text{Output} + \text{Losses}}$$

(i) Efficiency at full load and 0.5 lagging p.f.

$$= \frac{20 \times 10^3 \times 0.5}{20 \times 10^3 \times 0.5 + 200 + 424.8} \times 100\% = 94.12\%$$

(ii) Efficiency at half load and p.f. 0.8 leading

$$= \frac{20 \times 10^3 \times 0.8 \times \frac{1}{2}}{20 \times 10^3 \times 0.8 \times \frac{1}{2} + 200 + 424.8 \times \left(\frac{1}{2}\right)^2} \times 100\% = 96.3\%$$

.....

8.52 The primary resistance of a 440/110 V single-phase transformer is 0.28Ω and the secondary resistance is 0.018Ω . If the iron loss is measured to be 160 W when rated voltage is applied, find the kW loading to give maximum efficiency at unity p.f.

Solution

Iron loss = 160 W

For maximum efficiency, iron loss = Copper loss

So, $(I_2^2 R_{02}) = 160$, where I_2 = Secondary full load current
and R_{02} is the equivalent resistance referred to the secondary

$$\text{Now, } R_{02} = 0.28 \times \left(\frac{110}{440}\right)^2 + 0.018 = 0.0355 \Omega$$

$$\text{So, } (I_2^2 \times 0.0355) = 160 \text{ or, } I_2 = 67.13 \text{ A}$$

$$\text{So, kW rating at unity p.f.} = \frac{V_2 I_2 \times 1}{10^3} = \frac{110 \times 67.13}{10^3} = 7.38.$$

.....

8.53 The core of a single-phase transformer has a cross-sectional area of 15000 mm^2 and the windings are chosen to operate the iron at a maximum flux density of 1.1 T from a 50 Hz. supply. If the secondary winding consists of 66 turns estimate the kVA output if the winding is connected to a load of 6Ω impedance value.

Solution

$$\text{Area } A = 15,000 \text{ mm}^2 = 0.015 \text{ sqm}$$

$$\text{Flux density } B_m = 1.1 \text{ Wb/m}^2$$

$$f = 50 \text{ Hz.}$$

$$N_2 = 66$$

$$E_2 = 4.44 \phi_m f N_2 = 4.44 B_m A f N_2$$

$$= 4.44 \times 1.1 \times 0.015 \times 50 \times 66 = 241.758 \text{ V.}$$

$$\text{If load is } 6 \Omega \text{ the current } (I_2) = \frac{241.758}{6} \text{ A} = 40.3 \text{ A}$$

$$\text{kVA output} = \left(\frac{E_2 I_2}{10^3}\right) = \frac{241.758 \times 40.3}{10^3} = 9.743.$$

.....

8.54 A 440/220 V single-phase transformer has a primary resistance of 0.29Ω and a secondary resistance of 0.025Ω . The corresponding reactance values are 0.44Ω and

- (ii) Regulation at (0.5 lagging) p.f. = $\frac{90.91}{220} \{0.0514 \times 0.5 + 0.06025 \sin(\cos^{-1} 0.5)\}$
= 0.322 or 3.22%.
- (iii) Regulation at (0.5 leading) p.f. = $\frac{90.91}{220} \{0.0514 \times 0.5 - 0.06025 \sin(\cos^{-1} 0.5)\}$
= (-0.0109) or, (-1.09%).
-

8.57 A single-phase transformer is designed to operate at 2 V per turn and turns ratio of 3:1. If the secondary winding is to supply a load of 8 kVA at 80 V, find (i) the primary supply voltage, (ii) the number of turns on each winding and (c) the current in each winding.

Solution

$$\frac{N_1}{N_2} = \frac{3}{1} = \frac{E_1}{E_2}$$

$$\frac{E_1}{N_1} = \frac{E_2}{N_2} = 2$$

$$E_2 = 80 \text{ V}$$

where N_1 and N_2 are the number of turns of the primary and secondary windings respectively.

(i) So, $E_1 = 3 \times 80 = 240 \text{ V}$

Primary voltage = 240 V.

(ii) Now, $\left(\frac{E_1}{N_1}\right) = 2$

So, $(N_1) = \frac{E_1}{2} = \frac{240}{2} = 120$

Again, $(N_2) = \frac{E_2}{2} = \frac{80}{2} = 40.$

(iii) Secondary current = $\frac{8000}{80} = 100 \text{ A}$ (\because load is 8 kVA)

Primary current = $\frac{8000}{240} = 33.33 \text{ A}.$

.....

8.58 A single-phase step down transformer has the following particulars: Turns ratio 4:1, no load current 5 A at 0.3 p.f. lagging. Secondary voltage 110 V. Secondary load 10 kVA at 0.8 p.f. (lagging). Find (i) the primary voltage, neglecting the internal voltage drop, (ii) the secondary current on load, (iii) the primary current and (iv) the primary p.f.

Solution

$$\left(\frac{N_1}{N_2}\right) = \frac{4}{1} = \frac{E_1}{E_2}$$

$$E_2 = 110 \text{ V}$$

(a) $\therefore E_1 = 4 \times 110 = 440 \text{ V}.$

(b) Secondary load current (I_2) = $\frac{10,000}{110} = 90.91 \text{ A}.$

- (c) If (I_1') is the load component of the primary current then from $I_1' N_1 = I_2 N_2$ or,

$$I_1' = I_2 \frac{N_2}{N_1} = 90.91 \times \frac{1}{4} = 22.73 \text{ A}$$

if I_1 is the primary current then,

$I_1 \cos \theta_1 = I_o \cos \theta_o + I_1' \cos \theta$, where I_o and I_1' the no load and load component of primary current, $\cos \theta_o$ and $\cos \theta$ are the no load p.f. and secondary load p.f. respectively.

$$\text{So, } I_1 \cos \theta_1 = 5 \times 0.3 + 22.73 \times 0.8 = 19.684 \text{ A.}$$

$$\text{Again, } I_2 \sin \theta_1 = 5 \sin(\cos^{-1} 0.3) + 22.73 \sin(\cos^{-1} 0.8) \\ = 18.4 \text{ A}$$

$$\therefore I_1 = \sqrt{(19.684)^2 + (18.4)^2} = 26.94 \text{ A.}$$

\therefore Primary current is 26.94 A

$$(d) \text{ Primary p.f.} = \cos \theta = \frac{I_1 \cos \theta_1}{I_1} = \frac{19.68}{26.94} = 0.73 \text{ lagging.}$$

.....

8.59 A 6.6 kV, 50 Hz single-phase transformer with a transformation ratio (1:0.06) takes a no load current of 0.7 A and a full load current of 7.827 A when the secondary is loaded to 120 A at a p.f. of 0.8 lagging. What is the no load p.f.?

Solution

$$I_2 = 120 \text{ A}$$

Load p.f. ($\cos \theta = 0.8$ lagging or, $\theta = \cos^{-1} 0.8 = 36.87^\circ$)

$$\frac{N_1}{N_2} = \frac{1}{0.06}$$

No load primary current $I_o = 0.7 \text{ A}$

$$\text{Load component of primary current } (= I_1') = I_2 \frac{N_2}{N_1} = 120 \times 0.06 = 7.2 \text{ A}$$

Full load primary current $I_1 = 7.827 \text{ A}$

Let no load p.f. angle be θ_o

Referring to Fig. 8.31

$$I_1^2 = I_o^2 + I_1'^2 + 2I_o I_1' \cos (\theta_o - \theta)$$

$$\text{or } \cos (\theta_o - \theta) = \frac{(7.827)^2 - (0.7)^2 - (7.2)^2}{2 \times 0.7 \times 7.2} = 0.886$$

$$\text{or } (\theta_o - \theta) = \cos^{-1} 0.886 = 27.625^\circ$$

$$\text{or } \theta_o = 27.625^\circ + 36.87^\circ = 64.495^\circ.$$

.....

8.60 A 1 kVA single-phase transformer has an iron loss of 20 W and a full load copper loss of 40 W. Calculate its efficiency on full load output at a p.f. of (0.8) lagging.

Solution

Efficiency on full load at 0.8 p.f. lagging

$$= \frac{\text{Output}}{\text{Output} + \text{Loss}} = \frac{1000 \times 0.8}{1000 \times 0.8 + 20 + 40} \times 100\% = 93\%.$$

.....

8.63 The following results were obtained in tests on a 50 kVA, single-phase, 3300/400 V transformer.

Open Circuit Test:

Primary voltage 3300 V, Secondary voltage 400 V, Input Power 430 W.

Short Circuit Test:

Reduced voltage on primary (124 V) to give full secondary current, primary current is 15.3 A and input power 535 W.

Calculate

- The efficiency at half load at 0.707 p.f. lagging.
- The regulation and terminal voltage at full load for p.f. 0.707 leading.

Solution

From open circuit test iron losses = 430 W.

From short circuit test copper losses = 535 W.

Under short circuit test applied voltage = 124 V

and primary current = 15.3 A.

Hence equivalent impedance referred to the primary winding

$$Z_{01} = \frac{124}{15.3} \Omega = 8.1 \Omega$$

Equivalent impedance referred to the secondary winding

$$Z_{02} = Z_{01} \times \left(\frac{N_2}{N_1} \right)^2 = 8.1 \times \left(\frac{400}{3300} \right)^2 = 0.119 \Omega$$

If I_1 is the primary current and R_{01} is the equivalent resistance referred to the primary then

$$I_1^2 R_{01} = 535$$

$$\text{or } R_{01} = \frac{535}{(15.3)^2} = 2.285 \Omega.$$

Hence equivalent resistance referred to secondary is

$$R_{02} = 2.285 \times \left(\frac{400}{3300} \right)^2 = 0.03357 \Omega$$

$$X_{02} = \sqrt{(0.119)^2 - (0.03357)^2} = 0.114 \Omega.$$

$$\text{Full load secondary current } I_2 = \frac{50 \times 10^3}{400} \text{ A} = 125 \text{ A}$$

- Efficiency at $\left(\frac{1}{2} \right)$ load at 0.707 p.f. lagging

$$= \frac{50 \times 10^3 \times \frac{1}{2} \times 0.707}{50 \times 10^3 \times \frac{1}{2} \times 0.707 + 430 + \left(\frac{1}{2} \right)^2 \times 535} \times 100\% = 96.92\%.$$

- Regulation at full load for p.f. 0.707 leading

$$\begin{aligned} &= \frac{I_2}{E_2} \{ R_{02} \cos \theta_2 - X_{02} \sin \theta_2 \} \\ &= \frac{125}{400} \{ 0.03357 \times 0.707 - 0.114 \times 0.707 \} = -0.0178 \text{ or, } -1.78\% \end{aligned}$$

$$\text{Again, } \left[1 - \frac{V_2}{E_2} \right] = (-0.0178), \text{ where } (V_2) \text{ is the terminal voltage.}$$

$$\text{Hence, } V_2 = (1 + 0.0178) E_2 = 1.0178 \times 400 = 407.12 \text{ V.}$$

.....

8.64 The daily variation of load on a 100 kVA transformer is as follows:

8 a.m. to 1 p.m.:	65 kW, 45 KVAR
1 p.m. to 7 p.m.:	80 kW, 50 KVAR
7 p.m. to 2 a.m.:	30 kW, 30 KVAR
2 a.m. to 8 a.m.:	No load

The transformer has a no load core loss of 270 W and a full load ohmic loss of 1200 W. Determine the all day efficiency of the transformer.

Solution

From 8 a.m. to 1 p.m.,

$$\text{kVA} = \sqrt{(65)^2 + (45)^2} = 79$$

$$\text{Ohmic loss} = \left(\frac{79}{100}\right)^2 \times 1200 = 749 \text{ W}$$

$$\text{Energy lost as ohmic loss} = \frac{749 \times 5}{10^3} \text{ kWh} = 3.745 \text{ kWh.}$$

From 1 p.m. to 6 p.m.,

$$\text{kVA} = \sqrt{(80)^2 + (50)^2} = 94.34$$

$$\text{Ohmic loss} = \left(\frac{94.34}{100}\right)^2 \times 1200 = 1068 \text{ W}$$

$$\text{Energy lost as ohmic loss} = \frac{1068 \times 6}{10^3} \text{ kWh} = 6.408 \text{ kWh.}$$

From 6 p.m. to 1 a.m.,

$$\text{kVA} = \sqrt{(30)^2 + (30)^2} = 42.426$$

$$\text{Ohmic loss} = \left(\frac{42.426}{100}\right)^2 \times 1200 = 216$$

$$\text{Energy lost as ohmic loss} = \frac{216 \times 7}{10^3} \text{ kWh} = 1.51 \text{ kWh}$$

$$\text{Daily energy lost as ohmic losses} = (3.745 + 6.408 + 1.512) \text{ kWh} = 11.665 \text{ kWh}$$

$$\text{Daily energy lost as core loss} = \frac{24 \times 270}{10^3} \text{ kWh} = 6.48 \text{ kWh}$$

$$\text{Total energy loss} = (11.665 + 6.48) \text{ kWh} = 18.145 \text{ kWh}$$

$$\text{Daily kWh output} = 65 \times 5 + 80 \times 6 + 30 \times 7 + 0 = 1015 \text{ kWh}$$

$$\text{All day efficiency} = \frac{\text{Energy output}}{\text{Energy output} + \text{Energy loss}} = \frac{1015}{1015 + 18.145} \times 100\% = 98.24\%.$$

8.65 A 200 V, 60 Hz single-phase transformer has hysteresis and eddy current losses of 250 W and 90 W respectively. If the transformer is now energized from 230 V, 50 Hz supply, calculate its core losses. Assume Steinmetz's constant equal to 1.6.

Solution

If W_h and W_e are the hysteresis and eddy current loss respective then

$$W_h = K_h f B_m^x \quad \text{and} \quad W_e = K_e f^2 B_m^2$$

where K_h and K_e are constants, f is the frequency, B_m is maximum flux density and x is the Steinmetz constant.

Core loss = $(V_1 I_e \cos \theta_o) = 700$ W, where $\cos \theta_o$ is the no load p.f. and V_1 is the voltage of the primary winding.

So,
$$\cos \theta_o = \frac{700}{2400 \times 0.64} = 0.456$$

The core loss component of exciting current
 $= I_e \cos \theta_o = 0.64 \times 0.456 = 0.292$ A.

The magnetizing component of exciting current
 $= I_e \sin \theta_o = 0.64 \times \sin (\cos^{-1} 0.456) = 0.569$ A.

8.68 A non-sinusoidal voltage $v = 150 \sin 314t - 75 \sin 1570t$ is applied to the 250 turn winding of a transformer. Find the core flux as a function of time.

Solution

If ϕ is the flux then

$$v = -N \frac{d\phi}{dt}, \text{ where } (N) \text{ is the number of turns}$$

or
$$\frac{d\phi}{dt} = -\frac{v}{N}$$

or
$$\phi = -\frac{1}{N} \int v dt = -\frac{1}{N} \int (150 \sin 314t - 75 \sin 1570t) dt$$

$$= -\frac{1}{250} \left[-\frac{150}{314} \cos 314t + \frac{75}{1570} \cos 1570t \right]$$

or
$$\phi = (0.0019 \cos 314t - 0.00019 \cos 1570t) \text{ Wb.} \quad \dots\dots\dots$$

8.69 A voltage $v = 200 \sin 314t$ is applied to the transformer winding in a no load test. The resulting current is found to be $i = 3 \sin(314t - 60^\circ)$. Determine the core loss and rms value of the exciting current.

Solution

The instantaneous exciting current $i = 3 \sin(314t - 60^\circ)$

RMS value of exciting current $I_e = \frac{3}{\sqrt{2}} \text{ A} = 2.12 \text{ A}$

The instantaneous applied voltage $(v) = 200 \sin 314t$

rms value of voltage $V_1 = \frac{200}{\sqrt{2}} \text{ V}$

No load power factor angle $= (\theta_o) = 60^\circ$

\therefore core loss $(= V_1 I_e \cos \theta_o) = \frac{200 \times 3}{\sqrt{2} \sqrt{2}} \cos 60^\circ = \frac{200 \times 3}{2} \times \frac{1}{2} = 150 \text{ W.}$

8.70 A transformer has the following test data:

Test no.1: 100% voltage, 6% current, p.f. = 0.25

Test no.2: 8% voltage, 100% current, p.f. = 0.4.

Identify the tests. Calculate the efficiency and percentage regulation at full load and unity p.f.

Solution

As in test no. 1, full rated voltage is applied and the current is very less so the test must be no load test or open circuit test.

As in test no. 2, rated current is flowing and the applied voltage is very small so the test must be short circuit test.

From test no. 2

$$Z = \frac{0.8}{100} = 0.08 \text{ p.u.}$$

$$R = Z_e \cos \theta = 0.08 \times 0.4 = 0.032 \text{ p.u.}$$

$$X = 0.08 \times \sin (\cos^{-1} 0.4) = 0.0733 \text{ p.u.}$$

where Z , R and X are the p.u. values of equivalent impedance, resistance and reactance.

The regulation at full load and unity p.f. = $(0.032 \times 1 + 0.0733 \times 0) = 0.032$ or 3.2%.

From test 1 core losses = $V_1 I \cos \theta_o = 1 \times 0.06 \times 0.25 = 0.015 \text{ p.u.}$

From test 2 full load ohmic losses = $(I^2 R) = 1^2 \times 0.032 = 0.032 \text{ p.u.}$

Total losses = $(0.015 + 0.032) \text{ p.u.} = 0.047 \text{ p.u.}$

$$\text{Efficiency} = 1 - \frac{\text{Losses}}{\text{Output} + \text{Loss}} = 1 - \frac{0.047}{1 + 0.047} = 0.9551 \text{ or } 95.51\%.$$

8.71 In no load test of a single-phase transformer the following test data were obtained:

Primary voltage = 220 V

Secondary voltage = 110 V

Primary current = 0.5 A

Power input 30 = W.

Find the turns ratio, magnetising component of no load current, loss component of no load current and the iron loss. Resistance of primary winding is 0.6Ω .

Solution

$$\text{Turns ratio} = \left(\frac{N_1}{N_2} \right) = \frac{V_1}{V_2} = \frac{220}{110} = 2$$

No load current $I_o = 0.5 \text{ A}$

Power at no load $(V_1 I_o \cos \theta_o) = 30 \text{ W.}$

Hence, $I_o \cos \theta_o = \frac{30}{220} = 0.136 \text{ A, i.e. loss component of no load current is } 0.136 \text{ A.}$

Hence, $\cos \theta_o = 0.272$, i.e. $\sin \theta_o = 0.962$

Magnetising component of no load current is

$$I_o \sin \theta_o = 0.5 \times 0.962 = 0.481 \text{ A}$$

$$\begin{aligned} \text{Iron loss} &= \text{Input power} - \text{Ohmic loss in primary winding} \\ &= (30 - (0.5)^2 \times 0.6) = 29.85 \text{ W.} \end{aligned}$$

8.72 An auto transformer supplies a load of 2.5 kW at 110 V and at unity p.f. If the primary applied voltage is 220 V, calculate power transferred from the mains and power conducted directly from the supply lines to the load.

Solution

$$V_1 = 220 \text{ V}$$

$$V_2 = 110 \text{ V}$$

Power transferred from mains $(V_1 - V_2)I_1$

Now output power = 2.5 kW at unity p.f.

Hence output kVA = $2.5 \times 1 \text{ kVA} = 2.5 \text{ kVA}$

Neglecting loss input kVA = Output kVA = 2.5

$$\text{Hence primary current } I_1 = \frac{2.5 \times 10^3}{220} \text{ A} = \frac{250}{22} \text{ A}$$

$$\text{Power transferred from mains} = (220 - 110) \times \frac{250}{22} \times 1 \text{ W} = 1.25 \text{ kW}$$

$$\text{Power conducted directly from the supply lines to the load} = 2.5 - 1.25 = 1.25 \text{ kW} \dots\dots\dots$$

8.73 Two 2200/110 V transformers are operated in parallel to share a load of 125 kVA at 0.8 p.f. lagging.

Transformers are rated as below:

A : 100 kVA, 0.9% resistance and 1.0% reactance

B : 50 kVA, 0.1% resistance and 0.5% reactance

Find the load carried by each transformer.

Solution

Let base kVA be 100

$$Z_A = (0.009 + j0.01) \text{ p.u.}$$

$$Z_B = (0.001 + 0.005) \times \frac{100}{50} = (0.002 + j0.01) \text{ p.u. converting on 100 kVA.}$$

Load is 125 kVA at 0.8 p.f. lagging

$$\text{Hence, } S_L = 125 \angle -\cos^{-1} 0.8 \text{ kVA} = 125 \angle -36.87^\circ \text{ kVA}$$

Load carried by transformer A

$$= 125 \angle -36.87^\circ \times \frac{0.002 + j0.01}{(0.009 + 0.002) + j(0.01 + 0.01)}$$

$$= \frac{125 \angle -36.87^\circ \times 0.0102 \angle 78.69^\circ}{0.0228 \angle 61.19^\circ}$$

$$= 55.92 \angle -19.37^\circ \text{ kVA} = 52.75 \text{ kW at lagging p.f.}$$

Load carried by transformer B

$$= 125 \angle -36.87^\circ \times \frac{0.009 + j0.01}{(0.009 + 0.002) + j(0.01 + 0.01)}$$

$$= \frac{125 \angle -36.87^\circ \times 0.01345 \angle 48^\circ}{0.0228 \angle 61.19^\circ}$$

$$= 73.74 \angle -50.06^\circ \text{ kVA} = 47.34 \text{ kW at lagging p.f.} \dots\dots\dots$$

8.74 A three-phase 50 Hz transformer has a delta connected primary and star connected secondary, the line voltages being 22000 V and 400 V respectively. The secondary has a star connected balanced load at 0.8 p.f. lagging. The line current on the primary is 5 A. Determine the current in each coil of the primary and in each secondary line. What is the output of the transformer in kW?

Solution

Primary line voltage $V_{1L} = 22000 \text{ V}$

Secondary line voltage $V_{2L} = 400 \text{ V}$

Primary line current $I_{1L} = 5 \text{ A}$

Since the transformer has delta connected primary and star connected secondary,

$$\therefore \text{Primary phase voltage } V_{1Ph} = 22000 \text{ V}$$

$$\text{Secondary phase voltage } V_{2Ph} = \frac{400}{\sqrt{3}}$$

$$\text{Turns ratio} = \left(\frac{V_{1Ph}}{V_{2Ph}} \right) = \frac{22000 \sqrt{3}}{400} = \frac{220 \sqrt{3}}{4} = 55 \sqrt{3}$$

$$\text{Primary phase current } I_{1\text{Ph}} = \frac{5}{\sqrt{3}} \text{ A}$$

$$\text{Hence secondary phase current } I_{2\text{Ph}} = \frac{5}{\sqrt{3}} \times 55 \sqrt{3} \text{ A} = 275 \text{ A}$$

Secondary line current = 275 A (as secondary is star connected)

$$\begin{aligned} \text{Output of the transformer} &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} V_{2L} I_{2L} \cos \theta \\ &= \sqrt{3} \times 400 \times 275 \times 0.8 = 152420.47 \text{ W} = 152.42 \text{ kW.} \end{aligned}$$

8.75 A 50 HP, 220 V, three-phase motor has full load efficiency of 0.9 and power factor 0.8. It is fed from a 3300 V system from a 3300/220 delta star transformer. Find the phase current of the primary and secondary winding transformer.

Solution

$$\text{Output of motor} = 50 \text{ HP} = 50 \times 735.5 \text{ W} = 36775 \text{ W}$$

$$\text{Efficiency} = 0.9.$$

$$\text{Hence, } \frac{\text{Output of motor}}{\text{Input of motor}} = 0.9$$

$$\text{i.e. Input of motor} = \frac{36775}{0.9} = 40861 \text{ W}$$

$$\text{Therefore output of transformer} = 40861 \text{ W}$$

$$\text{Power factor } (\cos \theta) = 0.8$$

Hence $(\sqrt{3} V_L I_L \cos \theta) = 40861$, where V_L and I_L are line voltage and current of the secondary winding of transformer

$$V_L = 220$$

$$\text{Hence, } I_L = \frac{40861}{\sqrt{3} \times 220 \times 0.8} \text{ A} = 134 \text{ A.}$$

Since the secondary winding of transformer is star connected the phase current is also 134 A.

$$\text{Turns ratio of transformer} = \frac{3300}{220/\sqrt{3}} = 25.98$$

$$\text{Hence, primary phase current} = \frac{134}{25.98} \text{ A} = 5.157 \text{ A.}$$

■ EXERCISES ■

1. Define a transformer. Discuss the principle of operation of a single phase transformer.
2. Distinguish between core type and shell type transformer. Why is the low voltage winding placed near the core? Why is the core of a transformer laminated?
3. Derive an expression for the emf induced in a transformer winding.
4. Define an ideal transformer. Draw and explain the no load phasor diagram of an ideal single phase transformer.
5. Draw the exact equivalent circuit of a transformer and describe briefly the various parameters involved in it.

6. Draw and explain the phasor diagram of a single-phase transformer under lagging p.f.
7. Define voltage regulation of a transformer. Develop an expression for calculating the voltage regulation of a two winding transformer under (i) lagging p.f., (ii) unity p.f. and (iii) leading p.f.
8. What are the different types of losses in a transformer? Write an expression for efficiency and develop a condition for maximum efficiency.
9. Explain why
 - (i) the open circuit test on a transformer is conducted at a rated voltage,
 - (ii) usually the low voltage winding is excited and the high voltage winding is open circuited for open circuit test,
 - (iii) the open circuit test gives core loss and short circuit test gives copper loss,
 - (iv) usually low voltage winding is short circuited and high voltage winding is excited for the short circuit test.
10. Discuss about the Sumpner's test on single-phase transformer.
11.
 - (i) Explain why parallel operation of transformer is necessary.
 - (ii) State the essential and desirable conditions which would be satisfied before two single-phase transformers may be operated in parallel.
 - (iii) Deduce expressions for the load shared by two transformers connected in parallel.
12. What is an auto transformer? State its merits and demerits over a two winding transformer. What are the applications of an auto transformer?
13. Discuss about the different types of cooling used in transformers. Distinguish between a power transformer and a distribution transformer.
14. Define all day efficiency of a single-phase transformer.
15. What are the advantages of a transformer bank of three single-phase transformers over a unit three-phase transformer of the same kVA rating? What are the distinguishing features of YY, YΔ, ΔY and ΔΔ three-phase connections?
16. The primary winding of a single phase transformer connected to a 500 V, 50 Hz supply takes 1.41 A and absorbs 125 W with the secondary winding open circuited. The secondary open circuit voltage is 250 V. When the secondary winding is short circuited and the primary is connected to a 250 V, 50 Hz supply, the primary current is 15.1 A and the power absorbed is 92 W. Determine the shunt and series components of the equivalent circuit.
 [Ans: $R_O = 2000 \Omega$, $X_O = 360.23 \Omega$, $r_{e1} = 0.403 \Omega$, $x_{e1} = 1.606 \Omega$]
17. A 1100/230 V, 150 kVA single-phase transformer has a core loss of 1.4 kW and a full load copper loss of 1.6 kW. Determine (i) the kVA load for maximum efficiency and (ii) the maximum efficiency at unity power factor load.
 [Ans: 140.312 kVA, 98.04%]
18. A 415/220 V transformer takes a no load current of 1 A and operates at a p.f. of 0.19 lagging when the secondary supplies a current of 100 A at 0.8 p.f. lagging; find the primary current.
 [Ans.: 53.27 A]

[Hint:

No load current, $I_o = 1 \text{ A}$

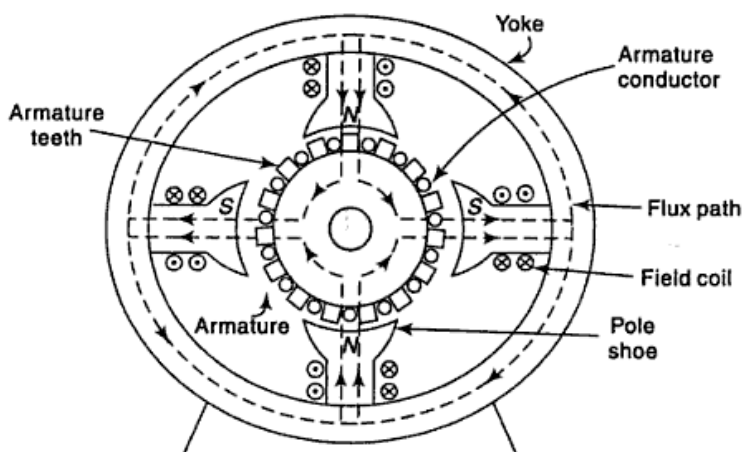


Fig. 9.1 Magnetic flux path of a four pole dc generator

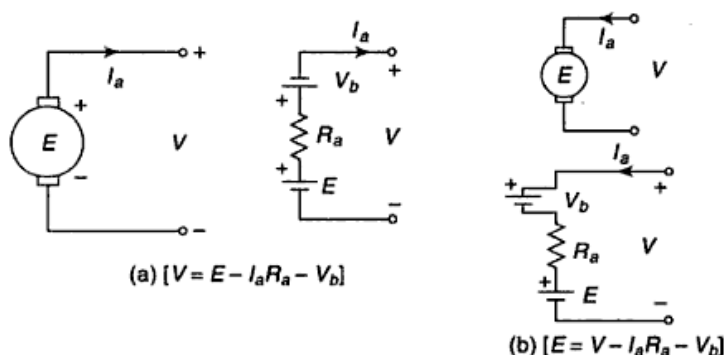


Fig. 9.2 Equivalent circuits of the armature (a) dc generator (b) dc motor

9.5 DIFFERENT TYPES OF EXCITATIONS IN DC MACHINE

There are, in general, two methods of exciting the field windings of dc machines.

- Separate excitation
- Self-excitation.

9.5.1 Separate Excitation

The separately excited field winding consists of several hundred turns of fine wire and is connected to a separate or external dc source as shown in Fig. 9.3(a). The voltage of the external dc source has no relation with the armature voltage, i.e. field winding energised from a separate source can be designed for any suitable voltage.

9.5.2 Self-excitation

When the field winding is excited by its own armature the machine is called a

- (b) **Level or Flat Compounded Generator** the no load voltage is same as that of the full load voltage.
- (c) **Under Compounded Generator** the generated voltage decreases as the load increases.

9.6 PROCESS OF VOLTAGE BUILD UP IN SELF-EXCITED GENERATOR

Figure 9.4 shows the process of voltage build-up in a self-excited shunt generator. The line OA has a slope equal to the shunt field resistance R_{sh} . When the armature of the machine is rotated, a small voltage OB is generated due to residual magnetism in the field poles. This voltage causes field current OC to flow. This current OC increases the field flux and generates voltage OD which in turn results in field current OE which will generate a still higher voltage. This process goes on and the generated voltage continues to increase. This process continues till point P is reached where the generated voltage is equal to $I_{sh} R_{sh}$, I_{sh} being the shunt field current. If the resistance of shunt field be such that R_{sh} is equal to the slope of the line OA' (which is tangent to the curve BP) the generated voltage would remain at value OB only, so no voltage will build up. The value of R_{sh} corresponding to slope of the line OA' is known as *critical field resistance*. The voltage build up is possible only if R_{sh} is less than critical value. If the speed of the generator is decreased the slope of the curve is lower. Hence for each value of R_{sh} there is a value of critical speed. If speed is less than critical speed, no voltage build up will occur.

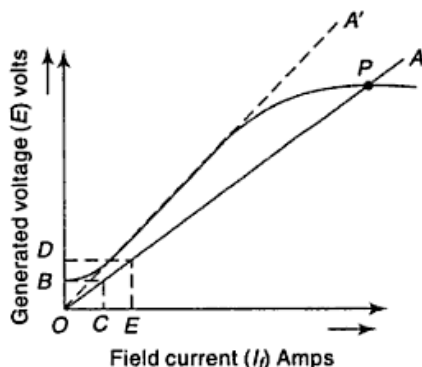


Fig. 9.4 Voltage build up in a self-excited generator

The connections of the field circuit should be such that field current strengthens the residual flux. If the connections are such that field current decreases the residual flux voltage will not build up.

For series generator the resistance of the load should be less than critical resistance and load should be connected so that the load current exists. Then only voltage will build up.

Hence the *conditions for voltage build up in self-excited generators* are:

- (a) Residual magnetism must be present
- (b) Field winding should be properly connected so that field current strengthens the residual magnetism.
- (c) The resistance of the field should be less than the critical resistance
- (d) The speed of the machine should be higher than the critical speed.
- (e) For series generator load should be connected and resistance of load should be less than critical resistance.

9.7 EMF EQUATION OF A DC MACHINE

As the armature of a dc machine rotates, a voltage is generated in its coils. In case of a generator, the emf of rotation E_r is called the generated emf E_g (or armature emf) and $E_r = E_g$. The direction (polarity) of dynamically induced emf can be determined by Fleming's right hand rule.

In case of a motor, the emf of rotation E_r is known as back emf E_b (or counter emf), and $E_r = E_b$. The expression, however, is the same for both conditions of operation, whether generating or motoring; only the polarity is reversed if the rotation of the machine is in the same direction in both the modes.

Let ϕ = Useful flux per pole in webers (Wb)

P = Total number of poles

Z = Total number of conductors in the armature

n = Speed of rotation of armature in revolutions per second (rps)

A = Number of parallel paths in the armature between brushes of opposite polarity

$\therefore \frac{Z}{A}$ = Number of armature conductors in series for each parallel path

Since the flux per pole is (ϕ) , each conductor cuts a flux $(P\phi)$ in one revolution. Generated voltage per conductor

$$= \frac{\text{Flux cut per revolution in Wb}}{\text{Time taken for one revolution in seconds}}$$

Since n revolutions are made in one second, one revolution will be made in $1/n$ second. Therefore, the time for one revolution of the armature is $1/n$ second.

$$\text{The average voltage generated per conductor} = \frac{P\phi}{1/n} = nP\phi \text{ V.}$$

The generated voltage E is determined by the number of armature conductors in series in any one path between the brushes. Therefore, the total voltage generated is obtained as

$$E = (\text{average voltage per conductor}) \times (\text{number of conductors in series per path})$$

$$\text{i.e. } E = nP\phi \times Z/A$$

$$E = \frac{nP\phi Z}{A} = \frac{P\phi ZN}{60A} \quad [N = \text{rpm}]. \quad (9.1)$$

Equation (9.1) is called the *emf equation of a dc machine*.

9.8 TYPES OF WINDINGS

Armature coils can be connected to the commutator to form either lap or wave windings.

Lap Winding

The ends of each armature coil are connected to adjacent segments on the commutators so that the total number of parallel paths (A) is equal to the total number of poles P . Thus for lap winding, $A = P$.

Wave Winding

In this winding, the ends of each of the armature coils is connected to the armature segment some distance apart, and only two parallel paths are provided between the positive and negative brushes. Thus, for wave winding $A = 2$.

In general, lap winding is used in low-voltage, high-current machines and winding is used in high-voltage, low-current machines.

9.1 The armature of a 4-pole 230 V wave wound generator has 400 conductors and runs at 400 rpm. Calculate the useful flux per pole.

Solution

Number of poles $P = 4$;

emf $E = 230$ V

Number of conductors $Z = 400$

$N = 400$ rpm.

As the machine is wave wound the number of parallel paths $A = 2$

$$\therefore E = \frac{P \phi Z N}{60 A}, \text{ where } \phi \text{ is flux per pole}$$

$$\therefore \phi = \frac{60 A E}{P Z N} = \frac{60 \times 2 \times 230}{4 \times 400 \times 400} = 0.043 \text{ Wb.}$$

.....

9.2 A 6-pole lap wound dc generator has 250 armature conductors, a flux of 0.04 Wb per pole and runs at 1200 rpm. Find the generated emf.

Solution

Number of poles (P) = 6.

As the machine is lap wound the number of parallel paths, $A (= P) = 6$ Also, number of armature conductors (Z) = 250

Flux per pole, $\phi = 0.04$ Wb

Speed, $N = 1200$ rpm.

$$\text{So, generated emf } E = \frac{P \phi Z N}{60 A} = \frac{6 \times 0.04 \times 250 \times 1200}{60 \times 6} = 200 \text{ V}$$

.....

9.3 An 8-pole lap wound dc generator has 1000 armature conductors, flux of 20 m Wb per pole and emf generated is 400 V. What is the speed of the machine?

Solution

Number of poles (P) = 8

\therefore Number of parallel paths $A = P = 8$

Number of armature conductors (Z) = 1000;

Flux per pole (ϕ) = 20 m Wb = 0.02 Wb

$$\text{Emf generated } (E) = 400 \text{ V} = \frac{P \phi Z N}{60 A}$$

where N is the speed of the machine in rpm.

$$\therefore N = \frac{60 A \times 400}{P \phi Z} = \frac{60 \times 8 \times 400}{8 \times 0.02 \times 1000} = 1200 \text{ rpm.}$$

.....

9.4 A 4-pole generator with 400 armature conductors has a useful flux of 0.04 Wb per pole. What is the emf produced if the machine is wave wound and runs at 1200 rpm? What must be the speed at which the machine should be driven to generate the same emf if the machine is lap wound?

Figure 9.5 shows a 2-pole dc generator rotating in a clockwise direction where the brushes are placed in the *geometrical neutral plane* (GNP). The currents in the conductors under the influence of North Pole (i.e. above GNP) carry currents inwards while those under the influence of South Pole (i.e. below GNP) carry currents outwards. The direction of the flux due to the armature conductors in the upper and lower half of armature is shown by dotted lines. The resultant flux lies along GNP which is shown by OA while OB represents the main field flux. The net flux is shown by OP . The *magnetic neutral plane* (MNP) coincides with GNP in the absence of armature flux. When armature flux is present, MNP shifts from GNP in the direction of rotation. To facilitate commutator action it is essential to place the brushes along MNP. Figure 9.6 shows brushes placed along MNP. Armature mmf OA can be split into two components OC and OD . The component OC is in opposition with the main field flux and called the demagnetising component and OD is called the cross-magnetising component. Thus, armature reaction distorts the main field flux by its cross-magnetising flux OD and demagnetising flux OC .

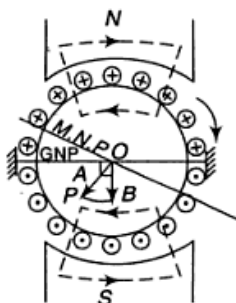


Fig. 9.5 Two-pole dc generator with brushes in GNP

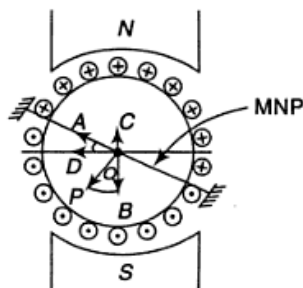


Fig. 9.6 Two-pole dc generator with brushes at MNP

9.9.1 Method of Improving Armature Reaction (Compensating Winding)

The demagnetising effect of armature reaction has a detrimental effect on the operation of dc motors whenever there is a sudden change in load. This causes a sudden change in flux/pole resulting in induction of large static emf which can short-circuit the complete commutator (known as *flashover*). Armature reaction AT (Ampere-turns) in dc machines can be compensated by placing a compensating winding in the pole faces with its axis along the brush axis and excited by the armature current in series connection (Fig. 9.7) so that it causes cancellation of armature reaction AT at all values of armature current.

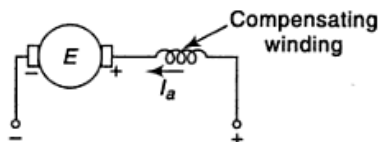


Fig. 9.7 Compensating winding (dc Motor)

9.10 COMMUTATION

Commutation is the process of producing a unidirectional or direct current from the alternating current generated in the armature coils.

The currents generated in the armature conductors of a dc generator are alternating. These currents flow in one direction when the armature conductors are under north pole and in the opposite direction when they are under south pole.

As conductors move out of the influence of the north pole and enter south pole, the current in them is reversed. When a brush spans two commutator segments, the winding element connected to those segments is short-circuited. During the period of short circuit of an armature coil by a brush the current in the coil must be reversed and also brought up to its full value in the reversed direction. The time of short-circuit is called the *period of commutation*. The inductive nature of the coil opposes the reversal of current from $(+I)$ to $(-I)$. If t is the time of short-circuit and L is the inductance of the coil, then the average induced voltage in the coil is

$$e_L = -L \frac{di}{dt} = \frac{-L}{t} [-I - (+I)] = \frac{2LI}{t}.$$

This induced voltage is called the *reactance voltage*. The sudden reversal of current as the brush leaves the segment may form an arc causing sparking at the commutator and the brush.

9.10.1 Methods of Improving Commutation

The main cause of sparking at the commutator being the reactance voltage, it can be minimised by the following methods:

- Use of High Resistance Carbon Brushes** (use of high contact resistance carbon brushes increases the circuit resistance of coils undergoing commutation. Thus the reactance voltage is reduced.)
- Use of Interpoles** (To reduce sparking at the commutator, small auxiliary poles called *interpoles* are provided in the machine. These are narrow cross-section poles with small cross-sectional area placed in-between the main poles. The interpoles are also called *commutating poles* (or *compoles*). The interpoles are wound with a small number of bigger cross-section conductor turns and are connected in series with the armature. Flux is produced in these poles only when current flows in the armature circuit. The flow of current in the interpole winding is such that the polarity of an interpole in a dc generator is the same as that of the next pole ahead, in the direction of rotation. In a dc motor, the polarity of an interpole is opposite to that of the next main pole in the direction of rotation.

9.11 CHARACTERISTICS OF DC GENERATORS

9.11.1 OCC (Open Circuit Characteristics) of DC Shunt Generator

Figure 9.8(a) shows a dc shunt generator on an open circuit being run at speed n rpm by means of a primemover. The field excitation is varied by regulating the resistance placed in the field circuit. The open circuit characteristic (OCC) so obtained is shown in Fig. 9.8(b). The OCC at any other speed would be a scaled version of the original OCC at rated speed (as $V_{OC} \equiv E_g \propto \omega_n$).

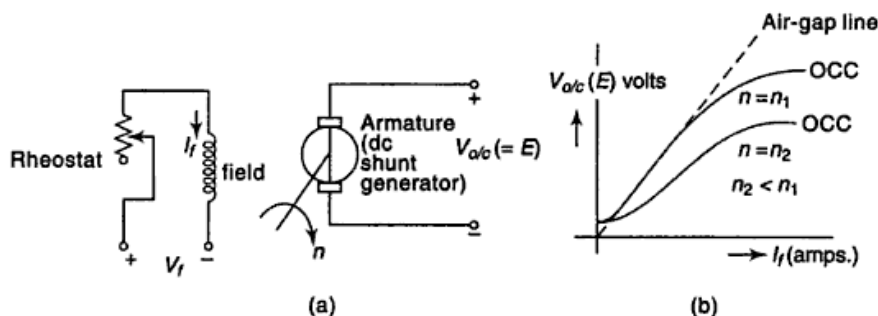


Fig. 9.8 Open circuit characteristic of a dc generator

9.11.2 Load Characteristics of DC Shunt Generator

The terminal voltage V versus armature current I_a characteristic is called the *internal characteristic* of a dc shunt generator and is drawn in Fig. 9.9. The load characteristic of a dc generator is called the *external characteristic*. It will only be slightly shifted from the internal characteristic as $I_L = I_a - I_f$. (I_f (field current) is usually very small).

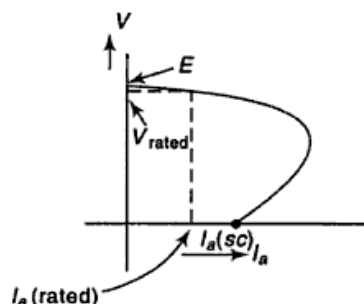


Fig. 9.9 Internal characteristic of dc shunt generator [terminal voltage $V =$ Induced voltage $E -$ drop within the armature]

9.11.3 Characteristics of Other Generators

Figure 9.10 (a) shows a series generator with its external characteristic shown in Fig. 9.10(b). The external characteristic of a long shunt compound generator and its connection diagram are drawn in Fig. 9.11(a) and 9.11(b). The characteristic is a combination of the characteristics of shunt and series generators. Series winding turns can be so adjusted that the *OC* (open circuit) voltage equals the full load voltage. The generator is then known as level compound dc generator.

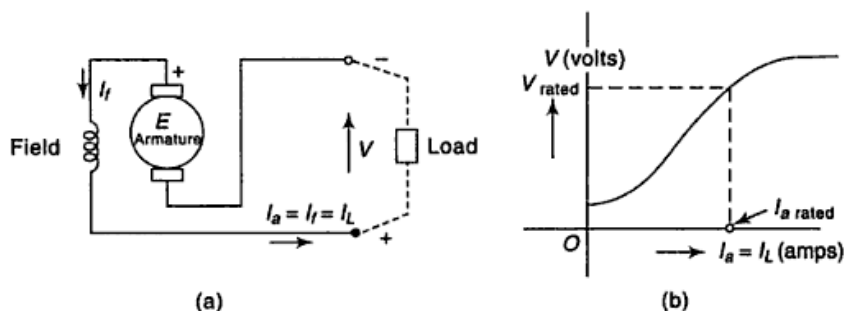


Fig. 9.10 External characteristic of a dc generator (series)

9.13 A 400 V, 6-pole shunt motor has a two-circuit armature winding with 250 conductors. The armature resistance is 0.3Ω , field resistance 200Ω and flux per pole is 0.04 Wb. Find the speed and the electromagnetic torque developed if the motor draws 10 A from the supply.

Solution

Given $P = 6, Z = 250, r_a = 0.3 \Omega, A = 2$
 and $r_{sh} = 200 \Omega$
 Also, $\phi = 0.04$ Wb, $I_L = 10$ A and $V = 400$ V

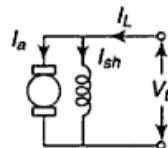


Fig. 9.19 A 400 V, 6-pole dc shunt motor (Ex. 9.13)

$$\therefore I_{sh} = \frac{400}{200} = 2 \text{ A (from Fig. 9.19)}$$

$$I_a = I_L - I_{sh} = 10 - 2 = 8 \text{ A}$$

Back emf $E_b = V_t - I_a r_a = 400 - 8 \times 0.3 = 397.6$ V

i.e. $E_b = 397.6 = \frac{P\phi ZN}{60 A}$ where (N) is the speed in rpm

$$\therefore N = \frac{60 \times 2 \times 397.6}{6 \times 0.04 \times 250} = 795 \text{ rpm}$$

Electromagnetic power $P_e = E_b I_a = 397.6 \times 8 = 3180.8$ W.

Electromagnetic torque $T_e = \frac{E_b I_a}{\omega}$, where ω is the angular velocity

But $\omega = 2\pi \frac{N}{60} \text{ rad/s} = \frac{2\pi \times 795}{60} \text{ rad/s} = 83.21 \text{ rad/s}$

$$\therefore T_e = \frac{397.6 \times 8}{83.21} \text{ Nm} = 38.23 \text{ Nm.}$$

.....

9.14 An 8-pole, 400 V shunt motor has 960 wave connected armature conductors. The full load armature current is 40 A and the flux per pole is 0.02 Wb. The armature resistance is 0.1Ω and the contact drop is 1 V per brush. Calculate the full load speed of the motor.

Solution

Given $P = 8, V = 400$ V, $Z = 960, I_a = 40$ A $\phi = 0.02$ Wb,
 $r_a = 0.1 \Omega$ and $A = 2$. Also total brush drop $= 2 \times 1 = 2$ V

Back emf $E_b = V - I_a r_a - \text{brush drop} = 400 - 40 \times 0.1 - 2 = 394$ V

Again, $E_b = \frac{P\phi ZN}{60 A}$, where (N) is the full load speed

$$\therefore N = \frac{60 A E_b}{P\phi Z} = \frac{60 \times 2 \times 394}{8 \times 0.02 \times 960} \text{ r.p.m} = 308 \text{ rpm.}$$

.....

9.15 A 42 kW, 400 V dc shunt motor has a rated armature current of 100 A at 1500 rpm. The resistance of armature is 0.2Ω . Find (i) the internal torque developed and (ii) the internal torque if the field current is reduced to 0.9 times of its original value.

Solution

Given, $V = 400$ V, $I_a = 100$ A, $N = 1500$ r.p.m and $r_a = 0.2 \Omega$

Back emf $E_b = V - I_a r_a = 400 - 100 \times 0.2 = 400 - 20 = 380$ V

(i) Internal torque developed

$$T_e = \frac{E_b I_a}{\omega}, \text{ where } \omega = \frac{2\pi N}{60} \text{ rad/s} = \text{angular speed}$$

If N be the speed, we can write

$$E_b = 474.72 = \frac{P \phi Z N}{60 A}$$

$$\therefore N = \frac{60 \times 2 \times 474.72}{4 \times 0.0346 \times 944} \text{ rpm} = 436 \text{ rpm.}$$

9.18 A dc series motor has an armature resistance of 0.03Ω and series field resistance of 0.04Ω . The motor is connected to a 400 V supply. The line current is 20 A when the speed of the machine is 1000 rpm . Find the speed of the machine when the line current is 50 A and the excitation is increased by 20% .

Solution

Given, $r_a = 0.03 \Omega$, $r_{se} = 0.04 \Omega$, $V = 400 \text{ V}$, $I_{L_1} = I_{a_1} = 20 \text{ A}$
and $N_1 = 1000 \text{ rpm}$.

When line current is 50 A (i.e. $I_{L_2} = I_{a_2} = 50 \text{ A}$), we assume speed is N_2 .

If ϕ be the flux when speed is 1000 rpm , the flux becomes (1.2ϕ) as this time excitation is increased by 20% .

We know $E_b \propto \phi N$

$$\therefore \frac{E_{b_1}}{E_{b_2}} = \frac{\phi N_1}{1.2 \phi N_2}$$

However, $E_{b_1} = V - I_{a_1}(r_a + r_{se}) = 400 - 20(0.03 + 0.04) = 398.6 \text{ V}$

and $E_{b_2} = 400 - 50(0.03 + 0.04) = 396.5 \text{ V}$

$$\therefore N_2 = \frac{N_1 E_{b_2}}{1.2 E_{b_1}} = \frac{1000 \times 396.5}{1.2 \times 398.6} = 829 \text{ rpm.}$$

9.15 SPEED EQUATION OF A DC MOTOR

The emf equation of a dc machine is given by

$$\text{We have, } E = \frac{N P \phi Z}{60 A}$$

$$\text{or } N = \frac{60 A}{P Z} \frac{E}{\phi}$$

$$\text{Therefore, } N = \frac{E}{K \phi}$$

$$\text{where } K = \frac{P Z}{60 A}$$

This equation shows that the speed of a dc machine is directly proportional to the emf of rotation E and is inversely proportional to flux per pole ϕ . Since the expression for emf of rotation applies equally to motors and generators, it gives the speed for both motors and generators.

If the suffixes 1 and 2 denote the initial and final values, we can write

$$N_1 = \frac{E_1}{k \phi_1}$$

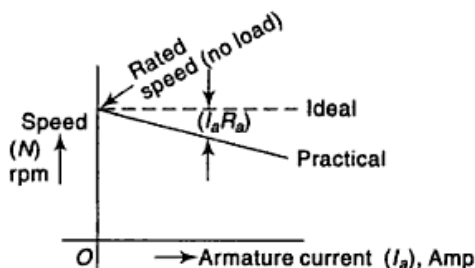


Fig. 9.20 Speed vs current characteristic of a dc shunt motor

9.17.2 Series Motor

The motor speed N for a series motor is given by

$$N \propto \frac{V - I_a (R_a + R_{se})}{\phi} \quad \left(= \frac{E_b}{K\phi} \right)$$

At low values of I_a , the voltage drop $[I_a (R_a + R_{se})]$ is negligibly small in comparison with V

$$\therefore N \propto \frac{V}{\phi}$$

Since V is constant,

$$N \propto \frac{1}{\phi}$$

In a series motor, the field flux ϕ is produced by the armature current flowing in the field winding so that $\phi \propto I_a$. Hence the series motor is a variable flux machine.

$$\text{Also, } N \propto \frac{1}{I_a}$$

Thus, for the series motor, the speed is inversely proportional to the armature (load) current. The speed-load characteristic is a rectangular hyperbola as shown in Fig. 9.21.

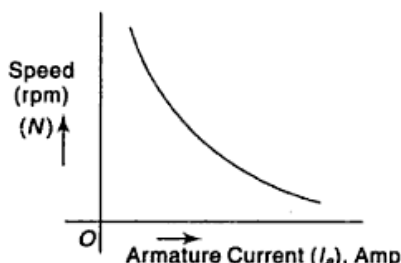


Fig. 9.21 Speed vs current characteristic of a dc series motor

The speed equation shows that when the load decreases, the speed will be very large. Therefore at no load (or at light loads) there is a possibility of dangerously high speed, which may damage the series motor due to large centrifugal forces. Hence a series motor should never be run unloaded. It should always be coupled to a mechanical load either directly or through gearing. It should not be coupled by belt, which may slip at any time making the armature unloaded. With the increase in armature current (i.e. the field current) the flux also increases and therefore the speed is reduced.

9.17.3 Compound Motor

The speed-armature current characteristics are shown in Fig. 9.22. In differentially compound motor, because of weakening of field, speed increases with increase in armature current while in cumulatively compound, the speed drops because of increase of field flux with armature current.

Also,
$$\frac{E_{b1}}{E_{b2}} = \frac{\phi_1 N_1}{\phi_2 N_2} = \frac{I_{a1} N_1}{I_{a2} N_2} \quad (\because \phi \propto I_a)$$

or
$$N_2 = \frac{E_{b2}}{E_{b1}} \times \frac{I_{a1}}{I_{a2}} N_1 = \frac{210}{195} \times \frac{50}{20} \times 400 = 1077 \text{ rpm}$$

$$\frac{T_{e2}}{T_{e1}} = \frac{\phi_2 I_{a2}}{\phi_1 I_{a1}} = \frac{I_{a2}^2}{I_{a1}^2} \quad (\because \phi \propto I_a)$$

or
$$\frac{T_{e2}}{T_{e1}} = \left(\frac{20}{50}\right)^2 = \frac{4}{25}$$

Percentage change in torque is $\left(1 - \frac{4}{25}\right) \times 100\%$ or, 84%

.....

9.23 A 400 V dc shunt motor having an armature resistance of 0.3Ω and shunt field resistance of 200Ω , draws a line current of 100 A at full load. The full load speed is 1500 rpm and the brush contact drop is 2 V. Find (i) the speed at half load (ii) the speed at 150% of full load.

Solution

Given $V = 400 \text{ V}; r_a = 0.3 \Omega; r_{sh} = 200 \Omega$

$N_{fl} = 1500 \text{ rpm} \quad I_{Lfl} = 100 \text{ A}$

$$I_{sh} = \frac{400}{200} = 2 \text{ A.}$$

So $I_{afl} = 100 - 2 = 98 \text{ A}$

$$E_{bfl} = V - I_{afl} r_a - \text{Brush drop} = 400 - 98 \times 0.3 - 2 = 368.6 \text{ V.}$$

(i) At half load

$$I_{L2} = \frac{100}{2} \text{ A} = 50 \text{ A}$$

So $I_{a2} = 50 - 2 = 48 \text{ A}$

$$E_{b2} = V - I_{a2} r_a - 2 = 400 - 48 \times 0.3 - 2 = 383.6 \text{ V}$$

$$\frac{E_{bfl}}{E_{b2}} = \frac{N_{fl}}{N_2} \quad (\because \phi = \text{constant})$$

or $N_2 = \frac{383.6}{368.6} \times 1500 = 1561 \text{ rpm.}$

(ii) At 150% of full load

$$I_{L3} = 100 \times 1.5 = 150 \text{ A}$$

$$I_{a3} = 150 - 2 = 148 \text{ A}$$

So $E_{b3} = 400 - 148 \times 0.3 - 2 = 353.6 \text{ V}$

Therefore $N_3 = \frac{E_{b3}}{E_{bfl}} \times N_{fl} = \frac{353.6}{368.6} \times 1500 = 1439 \text{ rpm.}$

.....

9.19 SPEED CONTROL OF DC MOTORS

The speed of a dc motor is given by the relationship

$$N = \frac{V - I_a R_a}{K\phi}$$

- (b) Speed control is limited to give speeds below rated and increase of speed is not possible by this method.
- (c) For a given value of the external resistance the speed reduction is not constant but varies with the motor load.

This method can only be used for small dc motors.

9.19.2 Variation of Field Flux (ϕ)

The flux in the dc motor being produced by the field current, control of speed is possible by field current variation. In the shunt motor, field current control is achieved by connecting a variable resistor R_C in series with the shunt field winding as shown in Fig. 9.29. The resistor R_C is called the *shunt field regulator*.

The connection of R_C in the field reduces the field current which in turn reduces the flux ϕ . The reduction in flux will result in an increase in the speed. This method of speed control is used to give motor speeds above normal speed. The variation of field current in a series motor is done by any one of the following methods:

- (a) A variable resistance R_d is connected in parallel with the series field winding as shown in Fig. 9.30. The parallel resistor is called the *diverter*. A portion of the main current is diverted through R_d , thus the diverter reduces the current flowing through the field winding. This reduces the flux and increases the speed.

- (b) The second method uses a tapped field control as shown in Fig. 9.31.

Here the ampere-turns are varied by varying the number of field turns. This arrangement is used in electric traction.

Figures 9.32(a) and (b) show the typical speed/torque curves for shunt and series motors respectively, whose speeds are controlled by the variation of the field flux.

The advantages of field control are that this method is easy and convenient and since the shunt field current I_{sh} is very small, the power loss in the shunt field is also small.

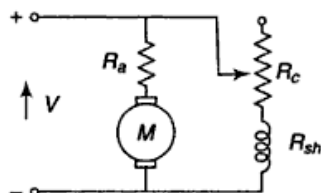


Fig. 9.29 Speed control of dc shunt motor by field flux control

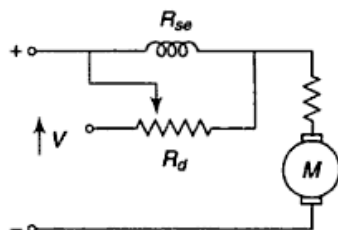


Fig. 9.30 Speed control of dc series motor by using diverter in the field circuit

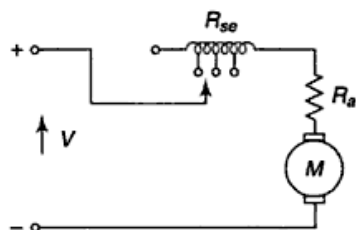


Fig. 9.31 Speed control of dc series motor by using tapped field control

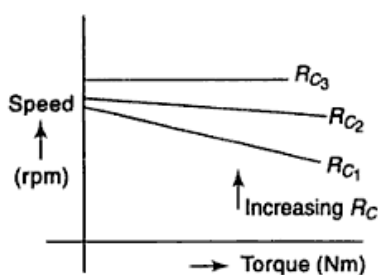


Fig. 9.32(a) Speed torque characteristic of a shunt motor

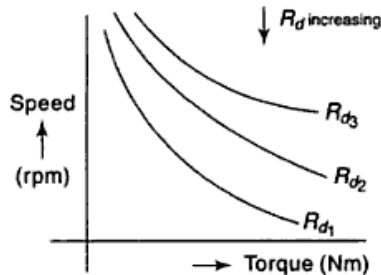


Fig. 9.32(b) Speed torque characteristic of a series motor

9.24 A shunt wound motor with an armature resistance of 0.2Ω is connected across a 400 V supply. The armature current is 40 A and the speed of the motor is 1000 rpm . Calculate the additional resistance which should be connected in series with the armature to reduce its speed to 700 rpm . Assume that the armature current remains the same.

Solution

Here $r_a = 0.2 \Omega$, $V = 400 \text{ V}$, $I_a = 40 \text{ A}$ and $N_1 = 1000 \text{ rpm}$.

Let the additional resistance connected in series with armature R and $N_2 = 700 \text{ rpm}$.

$$E_{b1} = V - I_a r_a = 400 - 40 \times 0.2 = 392 \text{ V}$$

$$E_{b2} = V - I_a(r_a + R) = 400 - 40(0.2 + R)$$

Now for shunt motor $E_b \propto N$ (as ϕ is constant).

$$\text{Hence } \frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2} = \frac{1000}{700}$$

$$\text{or } E_{b2} = \frac{7}{10} E_{b1} = \frac{7 \times 392}{10} = 274.4 \text{ V}$$

$$\therefore 274.4 = 400 - 40(0.2 + R)$$

$$\text{or } 8 + 40R = 400 - 274.4 = 125.6 \text{ V}$$

$$\text{or } R = 2.94 \Omega$$

9.25 A series wound dc motor runs at 500 rpm and is connected across 220 V supply. The line current is 10 A and armature circuit resistance is 0.6Ω . Find the resistance to be inserted in series to reduce the speed of the machine to 400 rpm assuming torque to vary as the square of the speed.

Solution

Given $N_1 = 500 \text{ rpm}$, $V = 220 \text{ V}$, $I_{a1} = 10 \text{ A}$, $(r_a + r_{se}) = 0.6 \Omega$

$N_2 = 400 \text{ r.p.m}$ and $T_e \propto N^2$

$$E_{b1} = V - I_{a1}(r_a + r_{se}) = 220 - 10 \times 0.6 = 214 \text{ V}$$

$$E_{b2} = V - I_{a2}(0.6 + R)$$

where R is the resistance to be inserted in series with the armature.

Now, for series motor $T_e \propto I_a^2$.

$$\text{Hence } \frac{T_{e1}}{T_{e2}} = \frac{I_{a1}^2}{I_{a2}^2} = \frac{N_1^2}{N_2^2} = \frac{(500)^2}{(400)^2} = \frac{25}{16}$$

$$\text{or } I_{a2} = \sqrt{\frac{16}{25}} I_{a1} = \frac{4}{5} I_{a1} = 0.8 I_{a1} = 0.8 \times 10 = 8 \text{ A}$$

$$\therefore T_{e_1} = T_{e_2}$$

$$\text{so, } \frac{T_{e_1}}{T_{e_2}} = 1 = \frac{\phi_1 I_{a_1}}{\phi_2 I_{a_2}} = \frac{I_{sh_1} I_{a_1}}{I_{sh_2} I_{a_2}} = \frac{2 \times 48}{\frac{4}{3} \times \left(I_{L_2} - \frac{4}{3} \right)}$$

$$\text{or } \frac{4}{3} \left(I_{L_2} - \frac{4}{3} \right) = 96$$

$$\text{or } I_{L_2} - \frac{4}{3} = 72$$

$$\text{or } I_{L_2} = 73.33 \text{ A}$$

$$\therefore I_{a_2} = 73.33 - 1.33 = 72 \text{ A}$$

$$\text{Now, } E_{b_1} = 400 - 48 \times 0.3 = 385.6 \text{ V}$$

$$\text{and } E_{b_2} = 400 - 72 \times 0.3 = 378.4 \text{ V}$$

$$\therefore \frac{E_{b_1}}{E_{b_2}} = \frac{N_1 \phi_1}{N_2 \phi_2} = \frac{N_1 I_{sh_1}}{N_2 I_{sh_2}}$$

$$\text{or } \frac{385.6}{378.4} = \frac{1000 \times 2}{N_2 \times 1.33}$$

$$\therefore N_2 = 1476 \text{ rpm.}$$

9.31 A dc shunt machine connected to a 400 V mains has an armature and field circuit resistance of 0.2Ω and 250Ω respectively. Find the ratio of the speed when the machine acts as a generator to the speed when the machine acts as a motor, if the line current in each case is 100 A.

Solution

$$\text{Given } V = 400 \text{ V, } r_a = 0.2 \Omega, r_{sh} = 250 \Omega, I_L = 100 \text{ A}$$

$$\text{Also, } I_{sh} = \frac{400}{250} = 1.6 \text{ A}$$

When the machine acts as a generator

$$I_{a_1} = 100 + 1.6 = 101.6 \text{ A } [\because I_{a(\text{gen})} = I_L + I_f]$$

$$E_1 = V + I_{a_1} r_a = 400 + 101.6 \times 0.2 = 420.32 \text{ V}$$

Let the speed of the generator be N_1 when the machine acts as a motor.

$$I_{a_2} = 100 - 1.6 = 98.4 \text{ A } [I_{a(\text{motor})} = I_L - I_f]$$

$$\text{So, } E_2 = V - I_{a_2} r_a = 400 - 98.4 \times 0.2 = 380.32 \text{ V}$$

$$\therefore \frac{E_1}{E_2} = \frac{\phi_1 N_1}{\phi_2 N_2} = \frac{N_1}{N_2} \quad (\text{As flux is constant})$$

$$\text{or } \frac{N_1}{N_2} = \frac{420.32}{380.32} = 1.105.$$

9.32 A dc shunt motor runs at 1000 rpm and takes an input of 700 W at 220 V under no load conditions. The shunt field current is 1 A and armature resistance is 0.2Ω . Find the speed when the machine is used as a generator if the line current is same in both the cases.

SolutionSpeed of motor $N_1 = 1000 \text{ rpm}$ Terminal voltage $V = 220 \text{ V}$ Input power $P = 700 \text{ W}$ Hence input line current $I_L = \frac{700}{220} \text{ A} = 3.18 \text{ A}$ Armature resistance $r_a = 0.2 \Omega$ Shunt field current $I_{sh} = 1 \text{ A}$ \therefore Armature current $I_a = 3.18 - 1 = 2.18 \text{ A}$ Back emf $E_b = V - I_a r_a = 220 - 2.18 \times 0.2 = 219.56 \text{ V}$

When the machine acts as a generator

Armature current $I_a = 3.18 + 1 = 4.18 \text{ A}$ \therefore Generated emf $E_g = V + I_a r_a = 220 + 4.18 \times 0.2 = 220.836 \text{ V}$ If N_2 be the speed of the generator

$$\frac{E_b}{E_g} = \frac{N_1}{N_2}$$

or $N_2 = \frac{E_g}{E_b} N_1 = \frac{220.836}{219.56} \times 1000 = 1006 \text{ rpm.}$

9.33 A 220 V series motor has a total armature resistance of 0.3Ω . At speed 1500 rpm it draws a line current of 10 A. When a 3Ω resistor is connected in series with the armature circuit it draws a line current of 6 A. Find the speed of the machine when the 3Ω resistor is connected and the ratio of two mechanical outputs. Assume the flux at 6 A is 75% of that with 10 A.

SolutionGiven $V = 220 \text{ V}$, $r_a = 0.3 \Omega$, $N_1 = 1500 \text{ rpm}$, $I_{L1} = I_{a1} = 10 \text{ A}$, $R = 3 \Omega$ Back emf without 3Ω resistor (E_{b1}) $= 220 - 10 \times 0.3 = 217 \text{ V}$ Back emf with 3Ω resistor (E_{b2}) $= 220 - 6 \times (3 + 0.3) = 200.2 \text{ V}$

If ϕ be the (since $I_{a2} = 6 \text{ A}$) flux in the first case, then flux with resistance connected is 0.75ϕ (given).

So $\frac{E_{b1}}{E_{b2}} = \frac{N_1 \phi}{N_2 \times 0.75 \phi}$ (where N_2 is the new speed)

or $N_2 = \frac{N_1 E_{b2}}{0.75 E_{b1}} = \frac{1500 \times 200.2}{0.75 \times 217} = 1895 \text{ rpm.}$

The ratio of the two mechanical outputs $= \frac{E_{b1} I_{a1}}{E_{b2} I_{a2}} = \frac{217 \times 1500}{200.2 \times 1845} = 0.88.$

9.20 LOSSES IN A DC MACHINE

There are three types of major losses in a dc machine.

- (a) **Copper Losses** There are two types of copper losses. One is *armature copper loss* and the other is *field copper loss*. Armature copper loss $= I_a^2 r_a$, where I_a is the armature current and r_a is the armature resistance.

Field copper loss = Shunt field copper loss + Series field copper loss.

$$= I_{sh}^2 r_{sh} + I_{se}^2 r_{se}$$
, where I_{sh} and I_{se} are the shunt and series field current, r_{sh} and r_{se} are the shunt and series field resistance. Brush contact loss is due to resistance of the brush contact. It is included in armature copper losses.

- (b) **Iron Losses (Core or Magnetic Losses)** These losses occur in the armature and field core. They are of two types—*hysteresis loss* and *eddy current loss*. Hysteresis loss = $K_h B_m^{1.6} f$ and Eddy current loss = $K_B B_m^2 f$ where B_m = maximum flux density, f = frequency of magnetic reversal and K_h and K_e are constants.

- (c) **Mechanical Losses** These losses consist of bearing frictional and windage loss.

In a medium-size motor, armature copper losses are about 30% to 40% of the total full load losses and field copper losses are about 20% to 30% of total full load losses. Iron losses are about 20% and mechanical losses are about 5 to 10% of the total full load losses. For small motors mechanical losses are comparable with full load losses while for larger motors, mechanical losses may be neglected.

Iron losses and mechanical losses are constant for a particular machine and they are together known as *no load rotational losses*.

Besides the above three types of losses there is an additional loss known as stray load loss. All the losses which do not belong to any of the above categories may be included in this group. In most machines stray load loss is taken as 1% of the rated output of the machine and is usually neglected.

Efficiency of dc Machines

$$\text{Efficiency } \eta = 1 - \frac{\text{Losses}}{\text{Input}} \quad \left[\because \eta = \frac{\text{Output}}{\text{Input}} = \frac{\text{Input} - \text{Losses}}{\text{Input}} \right]$$

For a generator, $\eta_g = 1 - \frac{\text{losses}}{VI_L + \text{losses}}$, where V is the terminal voltage and I_L is the line current; VI_L is the output power.

For a motor, $\eta_m = 1 - \frac{\text{losses}}{VI_L}$; here VI_L is the input power. η may also be expressed in %, if multiplied by 100.

Condition for Maximum Efficiency for a dc Generator

$$\eta_g = \frac{VI_L}{VI_L + I_a^2 r_a + V_f I_f + W_o}$$

Now, $V_f I_f + W_o = \text{constant} (= C)$ and as (I_f) is negligible so $I_L = I_a$.

Here, $VI_L = \text{output power}$

$I_a^2 r_a = \text{armature copper loss}$

$V_f I_f = \text{shunt field copper loss}$

$W_o = \text{No load rotational loss.}$

Brush contact drop = 1 V per brush

Stray losses are 1% of output.

Find the efficiency at full load. Also find the input torque if the speed is 1000 rpm.

Solution

Given, Output = 100 W

Terminal voltage = 220 V

$$\text{Line current } I_L = \frac{100 \times 10^3}{220} = 454.54 \text{ A}$$

$$\text{Field current } I_{sh} = \frac{220}{220} = 1 \text{ A}$$

$$\text{Armature current } I_a = I_L + I_{sh} = 454.54 + 1 = 455.54 \text{ A}$$

Field copper loss

$$I_{sh}^2 r_{sh} = 1^2 \times 220 = 220 \text{ W}$$

Armature copper loss

$$I_a^2 r_a = (455.54)^2 \times 0.1 = 20751.67 \text{ W}$$

$$\text{Brush contact loss} = 1 \times 2 \times 455.54 = 911.08 \text{ W}$$

$$\text{Mechanical loss} = 5000 \text{ W}$$

$$\text{Iron loss} = 5000 \text{ W}$$

$$\text{Stray losses} = 0.01 \times 100 \times 10^3 = 1000 \text{ W}$$

$$\begin{aligned} \text{Total loss} &= 220 + 20751.67 + 911.08 + 5000 + 5000 + 1000 \\ &= 32882.75 \text{ W} = 32.88 \text{ kW} \end{aligned}$$

$$\text{Input power} = \text{Output} + \text{Loss} = (100 + 32.88) \text{ kW} = 132.88 \text{ kW}$$

$$\therefore \text{Efficiency} = \frac{\text{Output}}{\text{Input}} \times 100\% = \frac{100}{132.88} \times 100\% = 75.25\%$$

Speed = 1000 rpm

$$\therefore \text{Angular velocity } \omega = \frac{2\pi \times 1000}{60} \text{ rad/s} = 104.72 \text{ rad/s}$$

$$\text{Input torque} = \frac{\text{Input power}}{\omega} = \frac{132.88 \times 10^3}{104.72} \text{ Nm} = 1269 \text{ Nm}.$$

9.36 A 400 V shunt motor with armature and field resistance of 0.1 Ω and 200 Ω takes no load current of 10 A at 1500 rpm. If full load current is 100 A find the speed and output torque at full load. Assume that the mechanical losses are same at no load and full load.

Solution

Given, $V = 400 \text{ V}$, $r_a = 0.1 \Omega$, $r_{sh} = 200 \Omega$

At no load

$$I_{L_1} = 10 \text{ A}$$

$$N_1 = 1500 \text{ rpm}$$

$$I_{sh} = \frac{V}{r_{sh}} = \frac{400}{200} = 2 \text{ A}$$

$$\therefore I_{a_1} = I_{L_1} - I_{sh} = 10 - 2 = 8 \text{ A}$$

$$\text{Armature copper loss} = (8)^2 \times 0.1 = 6.4 \text{ W [at no load]}$$

$$\text{Back emf } E_{b_1} = V - I_{a_1} r_a = 400 - 8 \times 0.1 = 399.2 \text{ V}$$

$$\text{Input power at no load} = 400 \times 10 = 4000 \text{ W (= total loss)}$$

$$\text{So, constant losses (i.e mechanical loss + core loss + shunt field copper loss)} = 4000 - 6.4 = 3993.6 \text{ W}$$

$$\therefore I_{sh} = \frac{220}{110} \text{ A} = 2 \text{ A}$$

$$\text{Hence, } I_a = 3 - 2 = 1 \text{ A}$$

Armature copper loss at no load $(= I_a^2 r_a) = (1)^2 \times 0.2 = 0.2 \text{ W}$.

Input at no load $= V \times I_L = 220 \times 3 = 660 \text{ W}$.

Thus, constant loss $= 660 - 0.2 = 659.8 \text{ W}$.

Back emf $E_{b_1} = V - I_a r_a = 220 - 1 \times 0.2 = 219.8 \text{ V}$

At full load,

$$I_L = 30 \text{ A}$$

$$\text{So, } I_a = 30 - 2 = 28 \text{ A}$$

Armature copper loss at full load is $(28)^2 \times 0.2 = 156.8 \text{ W}$

Total loss at full load $= 156.8 + 659.8 = 816.6 \text{ W}$

Input power at full load $= 220 \times 30 = 6600 \text{ W}$.

\therefore output power at full load $= (6600 - 816.6) \text{ W} = 5783.4 \text{ W}$.

$$\text{Therefore, efficiency at full load} = \frac{\text{Output}}{\text{Input}} \times 100\% = \frac{5783.4}{6600} \times 100\% = 87.63\%.$$

Back emf at full load

$$(E_{b_2}) = 220 - 28 \times 0.2 = 214.4 \text{ V}$$

If N_1 and N_2 be the speed at no load and full load respectively then

$$\frac{E_{b_1}}{E_{b_2}} = \frac{N_1}{N_2} = \frac{219.8}{214.4}$$

Change in speed from no load to full load is

$$= \frac{N_1 - N_2}{N_1} \times 100\% = \frac{219.8 - 214.4}{219.8} \times 100\% = 2.46\%.$$

9.41 A 250 V, 200 kW dc generator when at rest takes an armature current of 400 A with 8 V produced across its armature terminals. At no load condition and at rated speed the line and shunt field currents are respectively 36 A and 12 A. Find the generator efficiency at full load and half load.

Solution

When the generator is at rest, back emf $E_b = 0$

$$\therefore 0 = V - I_a r_a$$

$$\text{or } r_a = \frac{V}{I_a} = \frac{8}{400} = 0.02 \Omega.$$

At no load condition,

$$I_L = 36 \text{ A and } I_{sh} = 12 \text{ A}$$

$$\therefore I_a = 36 - 12 = 24 \text{ A}$$

Armature copper loss $= I_a^2 r_a = (24)^2 \times 0.02 = 11.52 \text{ W}$ [at no load]

$$\text{Input} = 36 \times 250 \text{ W}.$$

Constant losses $= 36 \times 250 - 11.52$ (\therefore Constant losses

$$= \text{input} - \text{armature copper loss}) = 8988.48 \text{ W}.$$

At full load,

Output power $= 200,000 \text{ W}$

$$\text{Line current } I_L = \frac{200,000}{250} \text{ A} = 800 \text{ A}.$$

Armature current $(I_a) = 800 + 12 = 812 \text{ A}.$

When the motor is at rest the starter handle S is kept in the "OFF" position by a spring and motor is disconnected from the supply. When the motor is to be started the handle is moved to stud 1. The shunt field and the holding coil gets the supply and entire starting resistance is connected in series with the armature. The armature starts rotating and the handle is gradually moved through all the studs until it touches the holding magnet. The holding magnet is called the *no volt release* or *low voltage release coil*. In case of power failure the holding coil gets demagnetized and the handle is brought back to "OFF" position by a spring action. Again, if by any chance the shunt field winding gets open circuited the holding magnet gets demagnetized and starter handle returns to the "OFF" position.

There is another coil called *overload release coil* which protects the motor against excessive load current. When armature current exceeds a particular value the overload release coil attracts the soft iron armature and as a result the no volt release coil gets short circuited. The starter is pulled back to the "OFF" position by the spring action as the holding coil gets demagnetized. The motor is thus automatically switched off.

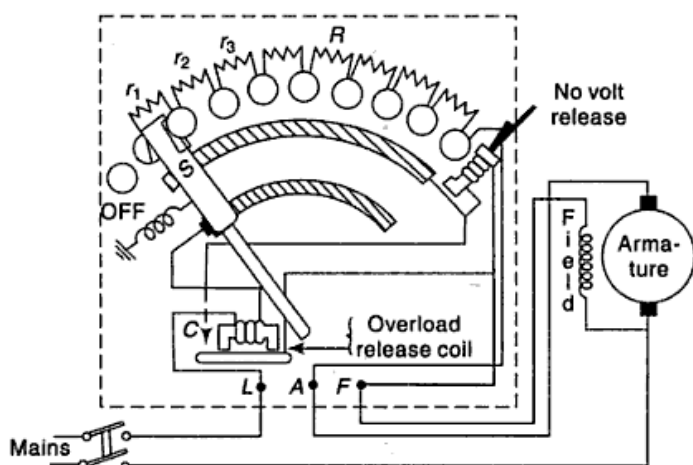


Fig. 9.33 Three-point starter for a dc shunt motor

9.22 REVERSAL OF ROTATION OF DC MOTOR

The direction of rotation of a dc motor can be reversed by reversing the connections of either the field winding or the armature but not both.

It is to be noted that in order to reverse the direction of rotation of a compound motor the reversal of the field connections involves both shunt and series windings.

9.23 DC MACHINE APPLICATIONS

Applications of a dc machine are discussed as follows.

9.48 A shunt motor has a rated armature current 50A when connected to 200 V. The rated speed is 1000 rpm and armature resistance is 0.1 Ω . Find the speed if total torque is reduced to 70% of that at rated load and a 3 Ω resistance is inserted in series with the armature.

Solution

Given, $I_{a1} = 50$ A, $V = 200$ V, $N_1 = 1000$ rpm,

$$r_a = 0.1 \Omega, T_{e2} = 0.7 T_{e1}$$

As $T_e \propto \phi I_a$

So $I_{a2} = 0.7 I_{a1}$ ($\phi = \text{constant}$ for shunt motor)

or $I_{a2} = 0.7 \times 50 = 35$ A

$$E_{b1} = V - I_{a1} r_a = 200 - 50 \times 0.1 = 195 \text{ V}$$

$$E_{b2} = V - I_{a2}(r_a + 3) = 200 - 35(0.1 + 3) = 200 - 35 \times 3.1 = 91.5 \text{ V}$$

Since $\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$ (As $\phi = \text{constant}$)

So $N_2 = \frac{E_{b2}}{E_{b1}} N_1 = \frac{91.5}{195} \times 1000 = 469 \text{ rpm.}$

9.49 A dc series motor drives a load whose torque varies as cube of the speed. The armature and series field resistance together is 2 Ω . The line current is 10 A when connected to a 400 V supply and the speed is 1500 rpm. Find the resistance to be connected in series with the armature to reduce the speed to 1000 rpm.

Solution

$$T_e \propto I_a^2 \text{ (in series motor)}$$

Here, $T_e \propto N^3$. So, $I_a^2 \propto N^3$

Also, $r_a + r_{se} = 2 \Omega$

$$I_{L1} = 10 \text{ A} = (I_{a1}), V = 400 \text{ V and } N_1 = 1500 \text{ rpm}$$

When resistance R is connected in series with armature, let speed $N_2 = 1000$ rpm and armature current is I_{a2}

$$\frac{I_{a1}^2}{I_{a2}^2} = \frac{N_1^3}{N_2^3} = \frac{(1500)^3}{(1000)^3}$$

or $I_{a2} = \left(\frac{1000}{1500}\right)^3 \times (10)^2$

$\therefore I_{a2} = 5.44$ A

$$E_{b2} = V - I_{a2}(r_a + r_{se} + R) = 400 - 5.44(2 + R)$$

Now, $E_{b1} = V - I_{a1}(r_a + r_{se}) = 400 - 10 \times 2 = 380 \text{ V}$

Again $\frac{E_{b1}}{E_{b2}} = \frac{I_{a1} N_1}{I_{a2} N_2}$ (for series motor)

Here, $E_{b2} = \frac{I_{a2} N_2}{I_{a1} N_1} \times 380 = \frac{5.44 \times 1000}{10 \times 1500} \times 380 = 137.897 \text{ V}$

$\therefore 400 - 5.44(2 + R) = 137.897$

or $R = 46.18 \Omega.$

If N_2 be the speed of the motor

$$N_2 = \frac{E_2}{E_1} N_1 = \frac{247.625}{257.125} \times 300 \text{ rpm} = 289 \text{ rpm.}$$

.....

9.54 The electromagnetic torque developed in a motor is 150 Nm. If the field flux is decreased by 20% and armature current is increased by 15% find the new electromagnetic torque developed.

Solution

Electromagnetic torque $T_e \propto \text{flux} \times \text{armature current}$. If ϕ_1 and I_{a1} be the flux and armature current when the developed torque is 150 Nm then

$$150 = K \phi_1 I_{a1} \quad (\text{where } K \text{ is constant}).$$

If T_{e2} be the new electromagnetic torque then

$$T_{e2} = K \times 0.8 \phi_1 \times 1.15 I_{a1} = 150 \times 0.8 \times 1.15 = 138 \text{ Nm.}$$

.....

9.55 A 250 kW, 230 V long shunt compound generator supplies 75% of the rated load at rated voltage. The armature and series field resistance are 0.009 Ω and 0.003 Ω . Find the efficiency of the generator if the shunt field current is 13 A. When the machine is run as a motor at no load the armature current is 25 A at rated voltage.

Solution

Here,

$$P = 250 \times 0.75 \text{ kW} = 187.5 \text{ kW}$$

$$V = 230 \text{ V,}$$

$$r_a = 0.009 \Omega \quad \text{and} \quad r_{se} = 0.003 \Omega$$

$$I_{sh} = 13 \text{ A and } I_L = \frac{P}{V} = \frac{187500}{230} \text{ A} = 815.22 \text{ A.}$$

So,

$$I_a = I_L + I_{sh} = 828.22 \text{ A}$$

$$\text{Armature copper loss} (= I_a^2 r_a) = (828.22)^2 \times 0.009 \text{ W} = 6173.54 \text{ W.}$$

$$\text{Field copper loss} = \text{shunt field copper loss} + \text{series field copper loss}$$

$$= \{230 \times 13 + (828.22)^2 \times 0.003\} \text{ W} = 5047.8 \text{ W.}$$

When the machine runs at no load as a motor,

$$I_a = 25 \text{ A}$$

$$I_{sh} = 13 \text{ A}$$

\therefore

$$I_L = 13 + 25 = 38 \text{ A}$$

$$\text{Input power} = I_L \times V = (38 \times 230) \text{ W} = 8740 \text{ W}$$

$$\text{Total copper losses} = \{(25)^2 \times 0.009 + 230 \times 13 + (25)^2 \times 0.003\} \text{ W} = 2997.5 \text{ W}$$

$$\text{No load rotational loss} = \text{Input power} - \text{Copper losses} = (8740 - 2997.5) \text{ W} = 5742.5 \text{ W.}$$

For a generator,

$$\text{Total losses} = (6173.54 + 5047.8 + 5742.5) \text{ W} = 16963.84 \text{ W} = 16.964 \text{ kW}$$

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}} \times 100 = \frac{\text{Output}}{\text{Output} + \text{Loss}} \times 100$$

$$= \frac{187.5}{187.5 + 16.964} \times 100\% = 91.7\%.$$

.....

9.56 A 600 V dc motor drives a 60 kW load 700 rpm. The shunt field resistance is 100 Ω and armature resistance is 0.16 Ω . If the motor efficiency is 85%, calculate the speed at no load and speed regulation.

Solution

$$\text{Output} = 60000 \text{ W, } V = 600, N_1 = 700 \text{ rpm, } r_{sh} = 100 \Omega,$$

$$r_a = 0.16 \Omega, \eta = 0.85.$$

$$\text{Input power} = \frac{\text{Output power}}{\text{Efficiency}} = \frac{60000}{0.85} = 70588 \text{ W}$$

$$\therefore I_L = \frac{\text{Input power}}{\text{Terminal voltage}} = \frac{70588}{600} = 117.65 \text{ A;}$$

$$I_{sh} = \frac{V}{r_{sh}} = \frac{600}{100} \text{ A} = 6 \text{ A}$$

$$I_a = I_L - I_{sh} \text{ (for motor)} = 117.65 - 6 = 111.65 \text{ A}$$

$$\text{Also, } E_{b1} = V - I_a r_a = 600 - 111.65 \times 0.16 = 582.136 \text{ V}$$

At no load,

$$E_{b2} = V = 600 \text{ V}$$

It no load speed is N_2 then

$$N_2 = N_1 \frac{E_{b2}}{E_{b1}} = 700 \times \frac{600}{582.136} \text{ rpm} = 721 \text{ rpm.}$$

$$\text{Speed regulation} = \frac{721 - 700}{700} \times 100\% = 3\%.$$

.....

9.57 A 200 V shunt motor has $r_a = 0.1 \Omega$, $r_{sh} = 240 \Omega$ and rotational loss is 236 W. On full load the line current is 9.8 A with the motor running at 1450 rpm. Find (i) the mechanical power developed (ii) power output (iii) load torque and (iv) full load efficiency.

Solution

Here, $V = 200 \text{ V}$, $r_a = 0.1 \Omega$, $r_{sh} = 240 \Omega$, $I_{fl} = 9.8 \text{ A}$

$N_{fl} = 1450 \text{ rpm}$. Rotational loss = 236 W

$$\therefore I_{sh} = \frac{V}{r_{sh}} = \frac{200}{240} = 0.833 \text{ A}$$

$$\text{and } I_a = (I_{fl} - I_{sh}) = 9.8 - 0.833 = 8.97 \text{ A}$$

$$\text{Also, } E_b = V - I_a r_a = 200 - 8.97 \times 0.1 = 199 \text{ V}$$

$$(i) \text{ Mechanical power developed is } E_b I_a = 199 \times 8.97 = 1785 \text{ W} = 1.785 \text{ kW.}$$

$$(ii) \text{ Power output} = 1785.9 - 236 = 1549 \text{ W} = 1.55 \text{ kW.}$$

$$(iii) \text{ Load torque} = \frac{\text{Power output}}{\omega} = \frac{1549 \times 60}{2\pi \times 1450} = 10.2 \text{ Nm.}$$

$$(iv) \text{ Full load efficiency} = \frac{\text{Output}}{\text{Input}} = \frac{1549}{200 \times 9.8} = 0.791 = 79.1\%.$$

.....

9.58 A 200 V shunt motor takes 10 A when running at no load. The brush drop is 2 V at full load and negligible at no load. The stray load loss at line current of 100 A is 50% of the no load loss. Find the efficiency at a line current of 100 A if armature and field resistances are 0.2Ω and 100Ω respectively.

Solution

$V = 200 \text{ V}$, $I_{LO} = 10 \text{ A}$, Brush drop = 2V,

$$I_{sh} = \frac{V}{r_{sh}} = \frac{200}{100} \text{ A} = 2 \text{ A}$$

At no load, $I_a = I_{LO} - I_{sh} = 10 - 2 = 8 \text{ A}$

Again, (Input = Loss) = $200 \times 10 = 2000 \text{ W}$ (at no load)

= No load rotational loss + Shunt field copper loss

+ Armature copper loss

\therefore no load rotational loss = $2000 - 200 \times 2 - 8^2 \times 0.2 = 1587.2 \text{ W}$
 $[\because \text{Shunt field copper loss} = V \times I_{sh} = (200 \times 2) \text{ W};$
 Armature copper loss at no load = I_a^2 (no load) $\times r_a = (8^2 \times 0.2) \text{ W}]$
 When $I_L = 100 \text{ A}$

$$I_a = 100 - 2 = 98 \text{ A}$$

Stray load loss = $0.5 \times 2000 = 1000 \text{ W}$

Armature copper loss = $(98)^2 \times 0.2 \text{ W} = 1920.8 \text{ W}$

Field copper loss = $200 \times 2 \text{ W} = 400 \text{ W}$

Total losses = No load rotational loss + Total copper loss + stray load loss
 = $1587.2 + (1920.8 + 400) + 1000 = 4908 \text{ W}$.

\therefore Input = $100 \times 200 = 20,000 \text{ W}$

\therefore Efficiency = $\left(1 - \frac{\text{Losses}}{\text{Input}}\right) = \left(1 - \frac{4908}{20,000}\right) = 0.7546 = 75.46\%$.

9.59 A 24 kW, 240 V, 100 A, 1500 rpm dc series motor has the following full load losses expressed in percentage of motor input:

Armature copper loss = 3%

Field copper loss = 2.5%

Rotational loss = 2%

If the motor draws half the rated current at rated voltage determine the speed and shaft power output.

Solution

Input power = $24 \times 10^3 = 24,000 \text{ W}$

Rotational loss = $0.02 \times 24,000 = 480 \text{ W}$

Armature copper loss = $0.03 \times 24,000 = 720 \text{ W}$

Field copper loss = $0.025 \times 24,000 = 600 \text{ W}$

\therefore Total copper loss = $(720 + 600) \text{ W} = 1320 \text{ W} = I_a^2 (r_a + r_{se})$

or $(r_a + r_{se}) = \frac{1320}{(100)^2} \Omega = 0.132$

$$E_{b1} = V - I_a (r_a + r_{se}) = 240 - 100(0.132) = 226.8 \text{ V}.$$

Now, $I_L = \frac{100}{2} = 50 \text{ A}$

$\therefore E_{b2} = 240 - 50 \times 0.132 = 233.4 \text{ V}$

(i) If N be the required speed

$$\frac{E_{b2}}{E_{b1}} = \frac{\phi_2 N}{\phi_1 \times 1500} = \frac{50 \times N}{100 \times 1500} \quad (\text{As } I_L \propto \phi \text{ in series motor})$$

or $N = \frac{100 \times 1500}{50} \times \frac{233.4}{226.8} = 3087 \text{ rpm}.$

(ii) Power developed = $E_{b2} I_L = 233.4 \times 50 = 11670 \text{ W}$

\therefore Shaft power output = $11670 \text{ W} - \text{Rotational loss}$
 = $11670 - 480 = 11190 \text{ W} = 11.19 \text{ kW}.$

9.60 A dc series motor runs at 1500 rpm and takes 100 A from 400 V supply. The combined resistance of the armature and field is 0.5Ω . If an additional resistance of 5Ω is inserted in series with the armature circuit, find the motor speed if the electromagnetic torque is proportional to the square of the speed.

Solution

$$N = 1500 \text{ rpm}; I_a = I_L = 100 \text{ A}; V = 400 \text{ V};$$

$$(r_a + r_{se}) = 0.5 \Omega$$

$$T_e \propto \phi I_a$$

As

$$\phi \propto I_a$$

$$T_e \propto I_a^2$$

Again

$$T_e \propto N^2$$

Hence,

$$I_a \propto N$$

 \therefore

$$I_a = KN \text{ (K being a constant)}$$

or,

$$K = \frac{100}{1500} = \frac{1}{15}$$

Now,

$$E_{b1} = V - I_a(r_a + r_{se}) = 400 - 100 \times 0.5 = 350 \text{ V}$$

and

$$E_{b2} = V - I_{a2}(r_a + r_{se} + 5) = 400 - I_{a2}(5.5)$$

If the speed is N when 5Ω resistor is connected, then we can write

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2} \quad \text{or,} \quad \frac{350}{400 - 5.5I_{a2}} = \frac{1500}{N} \quad \left[\begin{array}{l} N_1 = \text{initial speed} \\ = 1500 \text{ rpm} \\ N_2 = N \end{array} \right]$$

or,

$$350 N = 600,000 - 5.5 \times K \times N \times 1500.$$

or,

$$N = 667 \text{ rpm.}$$

.....

9.61 A dc shunt motor runs at 750 rpm from 250 V supply and takes a full load line current of 60 A. Its armature and field resistances are 0.4Ω and 125Ω respectively. Assuming 2 V brush drop calculate no load speed for a no load line current of 6 A and the resistance to be added series with the armature circuit to reduce the full load speed to 600 rpm.

Solution

Given,

$$N_{fl} = 750 \text{ rpm}; V = 250 \text{ V}; I_{fl} = 60 \text{ A}$$

$$r_a = 0.4 \Omega, r_{sh} = 125 \Omega$$

$$I_{nl} = 6 \text{ A}$$

$$I_{afl} = 60 - \frac{250}{125} = 58 \text{ A} \quad \left[\because I_{afl} = \left(I_{fl} - \frac{V}{r_{sh}} \right) \right]$$

$$E_{bfl} = 250 - 58 \times 0.4 - 2 = 224.8 \text{ V} \quad [\because E_{bfl} = V - I_{afl} \times r_a]$$

$$I_{anl} = 6 - \frac{250}{125} = 4 \text{ A} \quad \left[\because I_{anl} = I_{nl} - I_{sh} = I_{nl} - \frac{V}{r_{sh}} \right]$$

$$E_{bnl} = 250 - 4 \times 0.4 - 2 = 246.4 \text{ V} \quad [\because E_{bnl} = V - I_{anl} \times r_a - \text{brush drop}]$$

[Suffix nl stands for no load parameters while suffix fl stands for full load parameters]If N be the no load speed then we have

$$N = N_{fl} \times \frac{E_{bnl}}{E_{bfl}} = 750 \times \frac{246.4}{224.8} = 822 \text{ rpm}$$

If R be the resistance connected in series with the armature circuit then we can write,

$$E_b = [250 - I_a(0.4 + R) - 2] \text{ and } N' = 600 \text{ rpm}$$

or

$$E_b = [248 - 60(0.4 + R)] = 224 - 60 R.$$

 \therefore

$$\frac{224 - 60 R}{246.4} = \frac{600}{822} \quad \left[\because \frac{E_b}{E_{bnl}} = \frac{N'}{N} \right]$$

or

$$224 - 60 R = 179.85$$

or

$$R = 0.736 \Omega.$$

.....

Total losses = $(2881.2 + 480 + 2251.3) \text{ W} = 5612.5 \text{ W}$

$$\therefore \% \text{ loss} = \frac{5612.5}{18387.5} \times 100\% = 30.52\%.$$

9.64 A 220 V shunt motor takes 10.25 A on full load. The armature resistance is 0.8Ω and the field resistance is 880Ω . The losses due to friction, windage and the iron amount to 150 W. Find the output power and the efficiency of the motor on full load.

Solution

Motor input on full load = $220 \times 10.25 = 2255 \text{ W}$

$$\text{Field current} = \frac{220}{880} = 0.25 \text{ A}$$

Armature current = $10.25 \text{ A} - 0.25 \text{ A} = 10 \text{ A}$

Armature copper loss = $(10)^2 \times 0.8 = 80 \text{ W}$

Field copper loss = $(0.25)^2 \times 880 = 55 \text{ W}$

Total loss = total copper loss + friction, windage and iron loss
 $= (80 + 55 + 150) = 285 \text{ W}$

Output power = Input - Loss = $2255 - 285 = 1970 \text{ W}$

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}} \times 100\% = \frac{1970}{2255} \times 100\% = 87.36\%.$$

9.65 A 220 V shunt generator is rated to have a full load current of 200 A. The armature and field resistances are 0.06Ω and 55Ω respectively. The rotational losses are 3 kW. Find the input power of the generator and the load current for maximum efficiency.

Solution

$$\text{Field current } I_{sh} = \frac{V}{r_{sh}} = \frac{220}{55} = 4 \text{ A}$$

Armature current $I_a = I_{fl} + I_{sh} = 200 + 4 = 204 \text{ A}$

Armature copper loss ($I_a^2 \times r_a$) = $(204)^2 \times 0.06 = 2496.96 \text{ W}$

Field copper loss = $I_{sh}^2 \times r_{sh} = (4)^2 \times 55 = 880 \text{ W}$

Rotational loss = 3000 W

Constant loss = Field copper loss + Rotational losses = $880 + 3000 = 3880 \text{ W}$

Variable losses (= Armature copper loss) = 2496.96 W

Input power of generator = output power + total losses
 $= 220 \times 200 + 3880 + 2496.96$
 $= 50.377 \text{ kW}$

[\because Total losses = Constant loss + Variable loss]

Condition for maximum efficiency is given by

Variable loss = Constant loss

If I_a be the armature current for maximum efficiency then

$$I_a^2 \times 0.06 = 3880$$

or

$$I_a = 254.3 \text{ A}$$

[\because Variable loss is ($I_a^2 \times 0.06$) W and
 constant loss is 3880 W]

Hence load current for maximum efficiency is $(254.3 - 4)$ or 250.3 A.

9.66 A dc shunt motor has an armature resistance of 0.9Ω and takes an armature current of 18 A from 230 V dc mains. Calculate the power output and overall efficiency of the motor if the rotational losses are measured to be 112 W and the shunt field resistance is 300Ω .

Solution

Armature current = 18 A

$$\text{Field current} = \frac{230}{300} = 0.767 \text{ A}$$

Line current = 18.767 A

$$\text{Armature copper loss} = (18)^2 \times 0.9 = 291.6 \text{ W}$$

$$\text{Field copper loss} = (0.767)^2 \times 300 = 176.48 \text{ W}$$

$$\text{Total losses} = 291.6 + 176.48 + 112 = 580.08 \text{ W}$$

$$\text{Output power} = \text{Input power} - \text{Loss} = 18.767 \times 230 - 580.08 = 3736.33 \text{ W} = 3.74 \text{ kW.}$$

$$\text{Overall efficiency} = \frac{\text{Output}}{\text{Input}} \times 100\% = \frac{3736.33}{18.767 \times 230} \times 100\% = 86.56\%.$$

9.67 A 4 kW, 105 V, 1200 rpm shunt motor when running light at normal speed takes an armature current of 3 A at 102 V, nominal voltage being applied to the field winding. The field and armature resistance are 95 Ω and 0.1 Ω respectively. Calculate the output power and efficiency of the motor when operating at 105 V and taking a line current of 40 A. Allow 2 V drop at the brushes.

Solution

Given, line current I_L is 40 A

$$\text{Field current } I_{sh} = \frac{105}{95} \text{ A} = 1.1 \text{ A}$$

$$\therefore \text{Armature current } I_a = 40 - 1.1 = 38.9 \text{ A} \quad [\because I_a = I_L - I_{sh}]$$

$$\text{Back emf on load } E_b = V - I_a r_a - \text{Brush drop} = 105 - 38.9 \times 0.1 - 2 = 99.11 \text{ V}$$

$$\text{Hence, power developed by the armature} = E_b I_a = 99.11 \times 38.9 = 3855.4 \text{ W}$$

At light load,

$$\text{Input to armature (= Total loss)} = 102 \times 3 = 306 \text{ W}$$

$$\therefore \text{Armature copper loss} + \text{field copper loss} + \text{brush loss} + \text{no load rotational losses} = 306 \text{ W}$$

$$\therefore \text{No load rotational losses} = 306 - \underbrace{(3)^2 \times 0.1}_{\text{no load armature loss}} - \underbrace{105 \times 1.1}_{\text{field loss}} - \underbrace{3 \times 2}_{\text{brush loss}} = 183.6 \text{ W}$$

$$\text{At full load, output power} = 105 \times 40 - 183.6 - 38.9 \times 2 - 105 \times 1.1 - (38.9)^2 \times 0.1 = 3672 \text{ W.}$$

[Here, Output power = input power - total losses in the machine.

$$\begin{aligned} \text{Total losses} &= \text{rotational losses} + \text{brush loss} + \text{field loss} + \text{armature loss} \\ &= 183.6 + 38.9 \times 2 + 105 \times 1.1 + (38.9)^2 \times 0.1 \end{aligned}$$

$$\therefore \text{Efficiency} = \frac{\text{Output}}{\text{Input}} \times 100 = \frac{3672}{105 \times 40} \times 100\% = 87.42\%.$$

9.68 Calculate the no load current taken by a 100 kW, 460 V shunt motor assuming the armature and field resistances to remain constant and equal to 0.03 Ω and 46 Ω respectively. The efficiency at full load is 88%.

Solution

$$\text{Field current} = \frac{460}{46} \text{ A} = 10 \text{ A}$$

At light load,

$$\text{Input (= losses)} = I_a^2 R_a + \text{constant losses}$$

$$\text{or } 460(I_a + 10) = I_a^2 \times 0.03 + \text{constant losses} \quad (i)$$

Let the output power be P_1 .

If the load is increased by 30% the output power $P_2 = 1.3 P_1$ and let the back emf and speed be E_{b_2} and N_2 respectively

We have, $E_{b_2} I_{a_2} = 1.3 E_{b_1} I_{a_1} = 1.3 \times 211 \times 60 = 16458 \text{ W}$

$$\text{Now } E_{b_2} = 220 - I_{a_2} \times 0.15 = 220 - 0.15 \times \frac{16458}{E_{b_2}}$$

$$\text{or } E_{b_2}^2 = 220 E_{b_2} - 2468.7 \text{ or } E_{b_2}^2 - 220 E_{b_2} + 2468.7 = 0$$

$$\text{or } E_{b_2} = \frac{220 \pm \sqrt{48400 - 9874.8}}{2} = \frac{220 \pm 196}{2}$$

$$\text{or } E_{b_2} = 208.14 \text{ V.}$$

$$\text{Speed} = \frac{208.14}{211} \times 1200 = 1184 \text{ rpm.}$$

.....

9.72 A ventilating fan is driven by a 220 V, 10 kW series motor and runs at 800 rpm at full load. The total resistance of the armature circuit is 0.6Ω . Calculate the speed and percentage change in torque if the current taken by the motor is reduced by 50% of the full load value. The efficiency of the motor is 82%. Assume the flux to be proportional to the field current.

Solution

$$\text{Output} = 10,000 \text{ W}$$

$$\therefore \text{Input} = \frac{10,000}{0.82} (\because \text{efficiency} = 0.82) = 12195.12 \text{ W.}$$

$$\text{At full load current } I_1 = \frac{\text{Input}}{\text{Voltage}} = \frac{12195.12}{220} = 55.4 \text{ A}$$

$$\text{and speed } N_1 = 800 \text{ rpm.}$$

Let the flux be ϕ_1 at this speed and load current.

$$\text{Back emf } (E_{b_1}) = 220 - 55.4 \times 0.6 = 186.76 \text{ V } [\because E_{b_1} = V - I_1 r_a]$$

When Current $I_2 = 50\%$ of I_1 i.e. $I_2 = 27.7 \text{ A}$,

$$E_{b_2} = 220 - 27.7 \times 0.6 = 203.35 \text{ V.}$$

Let the flux be ϕ_2 at this input current.

$$\text{If } N_2 \text{ be the new speed then, } \frac{\phi_2 N_2}{\phi_1 N_1} = \frac{E_{b_2}}{E_{b_1}}$$

$$\text{So, } N_2 = \frac{E_{b_2}}{E_{b_1}} \frac{\phi_1}{\phi_2} N_1 = \frac{E_{b_2}}{E_{b_1}} \frac{I_1}{I_2} N_1 (\because \phi \propto I \text{ in the series motor})$$

$$\text{or } N_2 = \frac{203.35}{186.76} \times 2 \times 800 = 1742 \text{ rpm.}$$

If T_1 and T_2 be the torque at full load and 50% of the full load then

$$\frac{T_1}{T_2} = \left(\frac{I_1}{I_2} \right)^2 = \left(\frac{2}{1} \right)^2 = 4.$$

Hence percentage change in torque ($\Delta T\%$) is $\frac{T_1 - T_2}{T_1} \times 100$

$$\text{or } \Delta T = \frac{T_1 - \frac{T_1}{4}}{T_1} \times 100\% = \frac{3}{4} \times 100\% = 75\%.$$

.....

9.73 An engine room ventilator fan series motor has a total resistance of 0.5Ω and runs from a 110 V supply at 1000 rpm when current is 28 A . What resistance in series with the motor will reduce the speed to 750 rpm ? The load torque is proportional to the square of the speed and the field strength can be assumed to be proportional to the current.

Solution

When current $I_1 = 28 \text{ A}$, speed $N_1 = 1000 \text{ rpm}$.

Given, torque $T_1 \propto N_1^2$. If ϕ_1 be the flux then $\phi_1 \propto I_1$

Now for series motor $T \propto I_1^2$

$$\therefore N_1^2 \propto I_1^2 \text{ or } N_1 \propto I_1$$

$$E_{b1} = 110 - 28 \times 0.5 = 96 \text{ V}$$

Let R be the resistance to be added to reduce speed to 750 rpm , i.e. $N_2 = 750 \text{ rpm}$ and let flux be ϕ_2 .

$$\therefore E_{b2} = 110 - I_2(R + 0.5),$$

where I_2 is the current at speed 750 rpm

Also, $N_2 \propto I_2$

$$\therefore \frac{I_2}{I_1} = \frac{N_2}{N_1} \text{ or, } I_2 = \frac{750}{1000} \times 28 = 21 \text{ A.}$$

Also, $E_{b2} = 110 - 21(R + 0.5)$

(i)

$$\frac{E_{b2}}{E_{b1}} = \frac{N_2}{N_1} \frac{\phi_2}{\phi_1} = \frac{N_2}{N_1} \frac{I_2}{I_1};$$

$$E_{b2} = \frac{N_2 \times I_2}{N_1 \times I_1} \times E_{b1} = \frac{750 \times 21}{1000 \times 28} \times 96$$

From Eq. (i) we have

$$110 - 21R - 10.5 = \frac{750}{1000} \times \frac{21}{28} \times 96 = 54$$

or $R = 2.17 \Omega$.

.....

9.74 A 230 V , 10 kW shunt motor with a stated full load efficiency of 85% runs at a speed of 1000 rpm . At what speed should the motor be driven if it is used as a generator to supply an emergency lighting load at 230 V ? The armature resistance is 0.2Ω and the field resistance is 115Ω . Find the kW rating of the machine under this condition. Assume that the line current is same in both the cases.

Solution

$$\text{Output} = 10 \text{ kW} = 10,000 \text{ W}$$

$$\text{Input} = \frac{10000}{0.85} = 11764.7 \text{ W}$$

$$\text{Shunt field current} = \frac{230}{115} \text{ A} = 2 \text{ A} (= I_{sh}).$$

$$\text{Full load line current} = \frac{11764.7}{230} \text{ A} = 51.15 \text{ A} (= I_{fl}).$$

When the machine runs as a motor

$$\text{Armature current } [(I_{a(m)}) = I_{fl} - I_{sh}] = 51.15 - 2 = 49.15 \text{ A}$$

$$\text{Back emf } [(E_{b(m)}) = V - I_{a(m)} \times r_a] = 230 - 49.15 \times 0.2 = 220.17 \text{ V}$$

When used as a generator,

$$\text{Armature current } [I_{a(g)} = I_{fl} + I_{sh}] = 51.15 + 2 = 53.15 \text{ A}$$

$$\text{Generated emf } [E_{b(g)} = V + I_{a(g)} \times r_a] = 230 + 53.15 \times 0.2 = 240.63 \text{ V.}$$

If N_g be the speed of the generator then

$$N_g = 1000 \times \frac{240.63}{220.17} = 1093 \text{ rpm} \left[\because \frac{N_g}{N_m} = \frac{E_{b(g)}}{E_{b(m)}} \right]$$

$$\text{Rating of the machine } (V \times I_{fl} \times 10^{-3}) = \frac{230 \times 51.15}{1000} \text{ kW} = 11.76 \text{ kW.}$$

9.75 A series dc motor is run on a 220 V circuit with a regulating resistance of $R \Omega$ for speed adjustment. The armature and field coils have a total resistance of 0.3Ω . On a certain load with R being zero, the current is 20 A and the speed is 1200 rpm. With another load and R set at 3Ω the current is 15 A. Find the new speed and also the ratio of the two values of the power output of the motor. Assume the field strength at 15 A to be 80% of that at 20 A.

Solution

With $R = 0 \Omega$

Line current $I_1 = 20 \text{ A}$, $N_1 = 1200 \text{ rpm}$

Back emf $(E_{b_1}) = 220 - 20 \times 0.3 = 214 \text{ V.}$

With $R = 3 \Omega$

$I_2 = 15 \text{ A.}$

Hence, Back emf $E_{b_2} = 220 - 15 \times 3.3 = 170.5 \text{ V}$

$$\text{The new speed } N_2 = 1200 \times \frac{170.5}{214 \times 0.8} = 1195 \text{ rpm}$$

\therefore Power output \propto torque \times speed i.e. Power output $\propto \phi I N$

\therefore Ratio of power outputs $= (\phi I_1 N_1 / 0.8 \phi I_2 N_2)$

$$\text{or, ratio of the two values of output is } = \frac{20 \times 1200}{15 \times 1195 \times 0.8} = 1.67.$$

■ EXERCISES ■

1. Draw a neat sketch of a dc machine showing the different parts. State the function of each part.
2. Derive the emf equation of a dc generator.
3. What are the different types of dc generators according to the ways in which fields are excited. Show the connection diagram of each type.
4. Distinguish between
 - (i) self-excited and separately excited dc machines
 - (ii) lap connected and wave connected dc machines
 - (iii) cumulatively wound and differentially wound dc machines.
 - (iv) long shunt and short shunt dc machines.
5. What is armature reaction. Describe the effects of armature reaction on the operation of dc machines. How is the armature reaction minimised?
6. What is commutation in a dc machine? Describe the various methods of improving commutation.

$$\text{Speed } N_2 = N_1 \frac{E_{b_2}}{E_{b_1}} = 1800 \times \frac{116.4}{112.4} = 1864 \text{ rpm.}$$

$$(ii) I_L = 1.25 \times 40 = 50 \text{ A and } I_a = 50 - 2 = 48 \text{ A}$$

$$E_{b_3} = 120 - 48 \times 0.2 = 110.4 \text{ V}$$

$$N_3 = 1800 \times \frac{110.4}{112.4} = 1768 \text{ rpm} \Bigg].$$

28. A 4-pole 240 V dc shunt motor has armature and shunt field resistance of 0.24Ω and 240Ω respectively. It takes 20 A from a 240 V dc supply while running at a speed of 1000 rpm. Find the (i) field current, (ii) armature current, (iii) back emf and (iv) torque developed in Nm.

[Ans. 1 A; 19 A; 235.44 V; 42.74 Nm]

$$\left[\begin{array}{l} \text{Hint: (i) Field current, } I_{sh} = \frac{240}{240} \text{ A} = 1 \text{ A} \\ \text{(ii) Armature current, } I_a = 20 - 1 = 19 \text{ A} \\ \text{(iii) Back emf, } E_b = 240 - 19 \times 0.24 = 235.44 \text{ V} \\ \text{(iv) Torque } T = \frac{E_b I_a}{\omega} = \frac{235.44 \times 19}{2\pi \times \frac{1000}{60}} \text{ Nm} = 42.74 \text{ Nm} \end{array} \right]$$

29. A 220 V separately excited dc machine has an armature resistance of 0.4Ω . If the load current is 20 A, find the induced emf when the machine operates (i) as a generator (ii) as a motor. [Ans. 228 V; 212 V]

$$[\text{Hint: (i) } E = 220 + 20 \times 0.4 = 228 \text{ V}]$$

$$(ii) E = 220 - 20 \times 0.4 = 212 \text{ V}]$$

30. The armature resistance of a 220 V dc shunt motor is 0.4Ω and it takes a no load armature current of 2 A and runs at 1350 rpm. Find its speed when taking on armature current of 50 A if armature reaction weakens the flux by 2%. [Ans. 1257 rpm]

31. The input to a 220 V, dc shunt motor is 11 kW. Calculate (i) the torque developed and (ii) the speed at this load when the particulars of the motor are given as:

$$\text{No load current} = 5 \text{ A}$$

$$\text{No load speed} = 1150 \text{ rpm}$$

$$\text{Armature resistance} = 0.5 \Omega$$

$$\text{Shunt field resistance} = 110 \Omega$$

[Ans. 87.1 Nm, 1031 rpm]

32. The full load current in the armature of a shunt motor is 100 A, the line voltage being 400 V, the resistance of the armature circuit is 0.2Ω , and the speed 600 rpm. What will be the speed if the total torque on the motor is reduced to 60% of the full load value and a resistance of 2Ω is included in the armature circuit, the field strength remaining unaltered? [Ans. 423 rpm]
33. A dc shunt motor runs at 1500 rpm and takes an input of 880 W at 220 V under normal conditions. The shunt field current is 2 A and armature resistance is 0.1Ω . Find the efficiency when the machine is used as a generator supplying 60 A at 220 V. [Ans. 91.26%]

34. A 45 kW, 225 V dc shunt generator runs at 500 r.p.m at full load. The field and armature resistance are $45\ \Omega$ and $0.03\ \Omega$ respectively. Calculate the speed of the machine when running as a shunt motor and taking 45 kW input at 225 V. Assume brush contact drop of 1 V per brush.

[Ans. 465.69 rpm]

35. Find no load and full load speeds of a 220 V, 4 pole shunt motor having following data:

Flux 0.04 m Wb, armature resistance $0.04\ \Omega$, 160 armature conductors, wave connection, full load line current 95 A, no load line current 9 A, field resistance $44\ \Omega$.

[Ans. 1030.5 rpm, 1014.4 rpm]



THREE-PHASE INDUCTION MOTORS

10.1 INTRODUCTION

The whole concept of a polyphase ac, including the *induction motor*, was the idea of the great Yugoslavian engineer, Nikola Tesla.

The induction motor is, by a very considerable margin, the most widely used ac motor in industry. Induction motors normally require no electrical connection to the rotor windings. Instead, the rotor windings are short-circuited. Magnetic flux flowing across the air-gap links these closed rotor circuits. As the rotor moves relative to the air-gap flux, voltages are induced in the short-circuited rotor windings according to Faradays' law of electromagnetic induction causing currents to flow in them. The fact that the rotor current arises from induction, rather than conduction, is the basis for the name of this class of machines. They are also called "asynchronous" (i.e. not synchronous) machines because their operating speed is slightly less than synchronous speed in the motor mode and slightly greater than synchronous speed in the generator mode. Induction machines are usually operated in the motor mode, so they are usually called "induction motors."

Because of its simplicity and ruggedness, relatively less expensive and little maintenance, this motor is often the natural choice, as a drive in industry. The squirrel cage motor is often preferred over when a substantially constant speed of operation is desired, the wound rotor motor is a competitor of the dc motor when adjustable speed is required.

The chief disadvantages of induction motors are:

- (a) The starting current may be five to eight times full-load current if direct on line start is allowed.
- (b) The speed is not easily controlled.
- (c) The power factor is low and also lagging when the machine is lightly loaded.

For most applications, their advantages far outweigh their disadvantages.

10.2 CONSTRUCTION OF INDUCTION MACHINES

Similar to other rotating electrical machines, a three-phase induction motor also consists of two main parts: the *stator* and the *rotor* (the stator is the stationary part and the rotor is the rotating part). Apart from these two main parts, a three-phase induction motor also requires bearings, bearing covers, end plates, etc. for its assembly.

The stator of a three-phase induction motor has three main parts namely, stator frame, stator core and stator windings. The stator frame can either be casted or can be fabricated from rolled steel plates. The stator core is built up of high silicon sheet steel laminations of thickness 0.4 to 0.5 mm. Each lamination is separated from the other by means of either varnish, paper or oxide coating. Each lamination is slotted on the inner periphery so as to house the winding. The laminations for small machines are in the form of complete rings, but for large machines these may be made in sections. The insulated stator conductors are connected to form a three-phase winding, the stator phase windings may be either *star* or *delta-connected*.

The rotor is also built up of their laminations of the same material as the stator. The laminated cylindrical core is mounted directly on the shaft or a spider carried by the shaft. These laminations are slotted on their outer periphery to house the rotor conductors. There are two types of induction motor rotors:

- (a) Squirrel cage or simply cage rotor
- (b) Phase wound or wound rotor or slip ring rotors.

In either case, the rotor windings are contained in slots in a laminated iron core which is mounted on the shaft. In small machines, the lamination stack is pressed directly on the shaft. In larger machines, the core is mechanically connected to the shaft through a set of *spokes* called a “spider”.

The motor having the first type of rotor is known as a squirrel cage induction motor. This type of rotor is cheap and has a simple and rugged construction. It is cylindrical in shape and is made of sheet steel laminations. Here the slots provided to accommodate the rotor conductors, are not made parallel to the shaft but they are *skewed*. The purpose of skewing is (a) to reduce the magnetic hum and (b) to reduce the magnetic locking. The rotor conductors are short-circuited at the ends by brazing the copper rings, resembling the cage of a squirrel and hence the name squirrel cage rotor.

In present days, ‘die-cast rotors’ have become very popular. The assembled rotor laminations are placed in a mould. The molten aluminium is forced under pressure to form the bars. Figure 10.1 (a-c) shows a typical stator and rotor (both squirrel cage type and slip ring type) assembly. Figure 10.1(d) shows the schematic of a cage rotor separately.

The motor having the second type rotor, i.e. wound type rotor, is named as a slip-ring induction motor. In this motor, the rotor is wound for three-phase, similar to stator winding using open type slots in the rotor lamination. Rotor winding is always star connected and thus only three remaining ends of the windings are brought out and connected to the slip rings as shown in Fig. 10.2. With the help of these slip rings and brushes, additional resistances can also be connected in

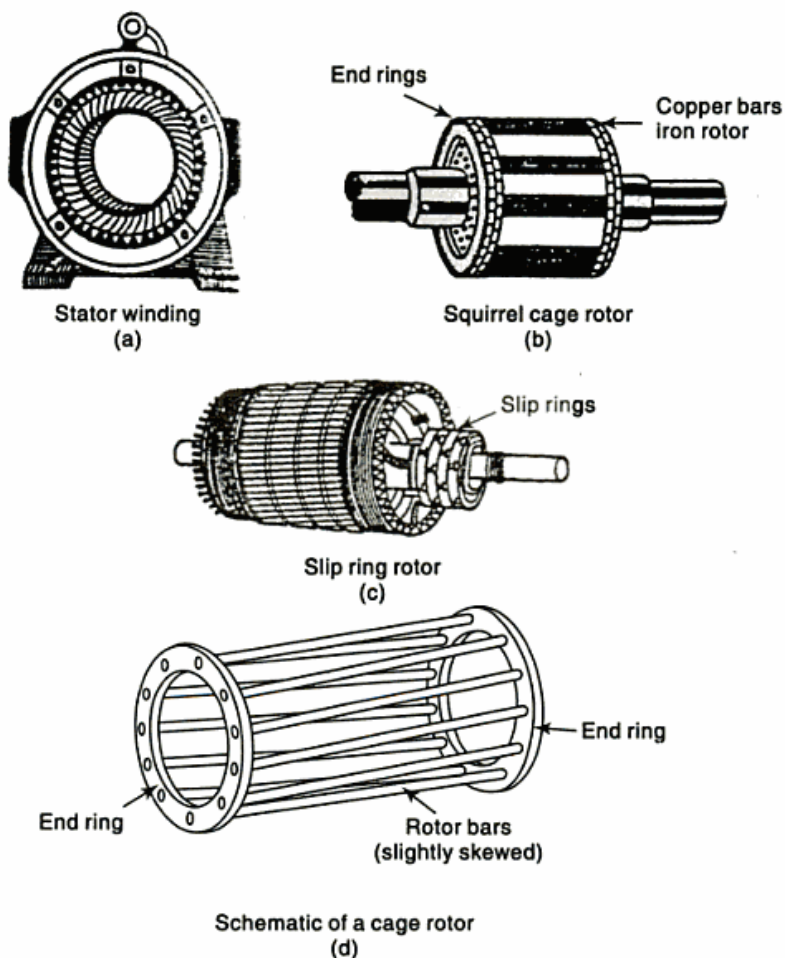


Fig. 10.1 Stator and rotor parts

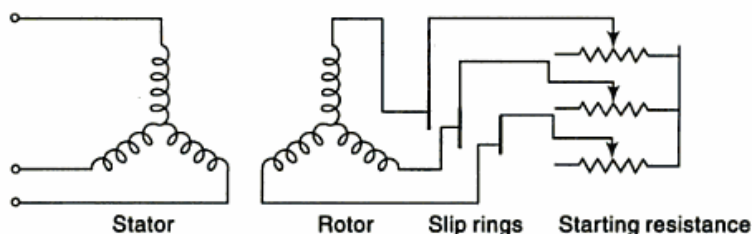


Fig. 10.2 Addition of external resistances to the rotor of wound rotor induction motor

series with each rotor phase (Fig. 10.2). This will increase the starting torque provided by the motor and will also help in reducing the starting current. When running under normal condition, the external resistances are removed completely from the rotor by short circuiting these additional resistances from the rotor circuit and rotor behaves just like a squirrel cage rotor.

10.3 COMPARISON OF SQUIRREL CAGE AND WOUND ROTORS

The advantages of cage rotor induction motor are as follows:

- (a) A rotor is of robust construction and cheaper.
- (b) The absence of brushes reduces the risk of sparking.
- (c) Squirrel cage rotors require lesser maintenance.
- (d) Squirrel cage induction motors have higher efficiency and better power factor.

On the other hand, wound rotors have the following merits:

- (a) High starting torque and low starting current.
- (b) Additional resistance can be connected in the rotor circuit to control speed.

10.4 ADVANTAGES AND DISADVANTAGES OF A THREE-PHASE INDUCTION MOTOR

Advantages

- (a) It is very simple, robust, rugged and capable of withstanding rough use.
- (b) It is quite cheap in cost and reliable in operation.
- (c) Its maintenance cost is low.
- (d) The losses are reasonably small and hence it has sufficiently high efficiency.
- (e) It is mostly a trouble-free motor.
- (f) Its power factor is reasonably good at full load operation.
- (g) It is simple to start (since it has a self starting torque).

An induction motor is equivalent to a static transformer whose secondary is capable of rotating with respect to the primary.

Usually the stator is treated as the primary, while the rotor is treated as the secondary. The induction motor operation is electrically equal even if the rotor is primary and the stator operation is treated as secondary.

Disadvantages

- (a) Its speed cannot be varied without sacrificing efficiency.
- (b) Its speed decreases with an increase in load.
- (c) Its starting torque is inferior to that of a dc shunt motor.
- (d) For direct on line starting, the starting current is usually 5 to 8 times of the full-load rated current.
- (e) It runs at a low lagging power factor when it is lightly loaded.

10.5 PRINCIPLE OF OPERATION

A three-phase induction motor has a stator winding which is supplied by three-phase alternating balanced voltage and has balanced three-phase currents in the winding. The rotor is not excited from any source and has only magnetic coupling with the stator. Under normal running conditions, the rotor winding (cage or slip-ring) is always short circuited to allow induced currents to flow in the rotor

∴ The resultant flux is (Fig. 10.3(d)),

$$\begin{aligned}\phi_r &= \sqrt{(\phi_h)^2 + (\phi_v)^2} = \frac{3}{2}\phi_m \sqrt{\sin^2 \omega t + \cos^2 \omega t} \\ &= \frac{3}{2}\phi_m \quad [\because \sin^2 \omega t + \cos^2 \omega t = 1]\end{aligned}\quad (10.4)$$

and $\tan \theta = \frac{\phi_v}{\phi_h} = \cot \omega t = \tan (90^\circ - \omega t).$

It implies $\theta = (90^\circ - \omega t).$ (10.5)

The above equation shows that the resultant flux (ϕ_r) is free from time factor.

It is a constant flux of magnitude equal to $\left(\frac{3}{2}\right)$ times the maximum flux per phase. However, θ is dependent on time and we can calculate θ at different values of (ωt); when (ωt) = 0, $\theta = \pi/2$ corresponding to position P in Fig. 10.3(c).

Similarly, for $\omega t = \pi/2$, $\theta = 0^\circ$, corresponding to position Q ,
when $\omega t = \pi$, $\theta = -\pi/2$, corresponding to position R ,

when $\omega t = \frac{3\pi}{2}$, $\theta = -\pi$, corresponding to position S .

It is thus observed that the resultant flux ϕ_r rotates in space in the clockwise direction with angular velocity of ω radians per second.

Since $\omega = 2\pi f$ and $f = \frac{PN_s}{120}$, the resultant flux ϕ_r rotates with synchronous speed (N_s).

10.7 THE CONCEPT OF SLIP

The magnitude and frequency of the rotor voltages depend on the speed of the relative motion between the rotor and the flux crossing the air gap. The difference between the synchronous speed and the rotor speed expressed as a fraction (or percent) of synchronous speed is known as *slip*, i.e.

$$\text{Slip speed} = (n_s - n) \text{ rev/sec}$$

and $\text{slip } (s) = \frac{n_s - n}{n_s} \text{ p.u.} \quad (10.6(a))$

or $n = n_s (1 - s) \text{ rps} \quad (10.6(b))$

where n_s = synchronous speed (rev/sec)

n = rotor speed (rev/sec)

s = slip.

When the speed is expressed in rpm, we can write

$$s = \frac{N_s - N}{N_s} \text{ p.u.} = \frac{N_s - N}{N_s} \times 100 \text{ (in \%)}$$

and $N = N_s(1 - s) \text{ rpm.}$

This slip s is a very useful quantity in studying induction motors.

The value of slip at full load is about 4 to 5% for small motors and about 2 to 2.5% for large motors. The slip at no load is about 1%. Thus the speed of an

induction motor is almost constant from no load to full load. If the machine has P number of poles, the frequency of induced emf in the rotor, i.e. f_2 is given by

$$f_2 = \frac{N_s - N}{N_s} \times f_1 \quad \left[\because f_1 = \frac{PN_s}{120}; f_2 = \frac{P(N_s - N)}{120} \right]$$

and hence $(f_2/f_1) = \left(\frac{N_s - N}{N_s} \right)$

i.e. $f_2 = sf_1$

At standstill of the rotor, $s = 1$, i.e. the frequency of rotor currents is f_1 (the same as the supply frequency).

10.8 FREQUENCY OF ROTOR VOLTAGES AND CURRENTS

Let us consider a typical pair of rotor bars. As the rotor "slips" backward through the flux field, the flux linking these bars will vary cyclically. The voltage induced in the rotor circuit is composed of the voltages in these two bars and the end rings. It is at its peak at the instant when the rate of change of flux linkages is a maximum. Thus one cycle of rotor voltage is generated as a given conductor slips past two poles of the air-gap flux field. In other words, one cycle of rotor voltage corresponds to 360 electrical degrees of "slips". Then the frequency of the rotor voltages and currents is given by

f_2 = pole-pairs slipped per second

$$\frac{(n_s - n)}{n_s} \cdot n_s \cdot \frac{P}{2} = s \cdot f_1 \quad \left[\because f_1 = \frac{PN_s}{120} = \frac{PN_s}{2 \times 60} = \frac{Pn_s}{2} \right] \quad (10.7)$$

i.e., Rotor current frequency = Per unit slip \times Supply frequency.

At standstill, rotor speed is zero.

$$\therefore s = \frac{(n_s - n)}{n_s} = \frac{n_s - 0}{n_s} = 1$$

and $f_2 = f_1$. (10.8)

10.1 A three-phase, 4-pole 50 Hz. induction motor runs at 1450 rpm. Find out the percentage slip of the induction motor.

Solution

$$N_s = \frac{120 f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$\therefore \text{Slip} = \frac{N_s - N}{N_s} = \frac{1500 - 1450}{1500} = 0.033 = 3.33\%.$$

.....

10.2 A three-phase, 50 Hz., 6-pole induction motor runs at 950 rpm. Calculate

- (i) the synchronous speed
- (ii) the slip and
- (iii) frequency of the rotor emf.

Solution

$$(i) \text{ We know, } N_s = \frac{120 f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm.}$$

$$(ii) \text{ Slip } (s) = \frac{N_s - N}{N_s} = \frac{1000 - 950}{1000} = 0.05.$$

$$\therefore \text{ percentage of slip} = 0.05 \times 100 = 5.$$

$$(iii) \text{ The frequency of rotor emf} = s \cdot f_1 = 0.05 \times 50 = 2.5 \text{ Hz.}$$

10.3 The frequency of the emf in the stator of a 4-pole induction motor is 50 Hz., and that in the rotor is 2 Hz. What is the slip and at what speed is the motor running?

Solution

$$\text{We know } f_2 = s \cdot f_1$$

$$\therefore s = \frac{f_2}{f_1} = \frac{2}{50} = 0.04 = 4\%.$$

$$\text{Again } f_1 = \frac{P \cdot N_s}{120}$$

$$\therefore N_s = \frac{120 \cdot f_1}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm.}$$

Speed of the motor

$$N = (1 - s) \cdot N_s = (1 - 0.04) \times 1500 = 1440 \text{ rpm.}$$

10.4 A 10-pole induction motor is supplied by a 6-pole alternator, which is driven at 1400 rpm. If the motor runs with a slip of 2%, what is its speed?

Solution

For induction motor: Synchronous speed is given by

$$N_s = \frac{120 f}{P} = \frac{120 \times 70}{10} = 840 \text{ rpm} \quad \left[\because f = \frac{P N_A}{120} = \frac{6 \times 1400}{120} = 70 \text{ Hz.} \right]$$

$$\text{Now slip, } s = \frac{N_s - N}{N_s} = \frac{840 - N}{840}$$

$$\therefore 0.02 = \frac{840 - N}{840}$$

$$\therefore N = 823.2 \text{ rpm.}$$

10.5 A three-phase 60 Hz induction motor has a no load speed of 890 rpm and a full load speed of 855 rpm. Calculate

- the number of poles
- slip s at no load
- slip at full load
- frequency of rotor currents at no load
- frequency of rotor currents at full load.

Solution

- Since the no load slip of an induction motor is about one percent, the synchronous speed is slightly larger than the no load speed of 890 rpm. For 60 Hz frequency, the number of poles and their corresponding synchronous speeds are

P	2	4	6	8	10
N_s (rpm)	3600	1800	1200	900	720

It is obvious that the synchronous speed can be only 900 rpm and therefore the number of poles is 8.

$$(ii) \text{ No load slip } (s) = \frac{900 - 890}{900} \times 100 = 1.11\%.$$

$$(iii) \text{ Full load slip} = \frac{900 - 855}{900} \times 100 = 5\%.$$

$$(iv) \text{ At no load, } f_2 (= sf_1) = \frac{1.11}{100} \times 60 = 0.66 \text{ Hz.}$$

$$(v) \text{ At full load, } f_2 = \frac{5}{100} \times 60 = 3 \text{ Hz.}$$

10.6 A three-phase 6-pole induction motor runs at 760 rpm at full load. It is supplied from an alternator having four poles and running at 1200 rpm. Determine the full-load slip of the induction motor.

Solution

Given the number of poles of alternator $P_A = 4$ and the synchronous speed of the alterna-

tor is 1200 rpm, the frequency f is $\frac{N \cdot P_A}{120} = \frac{1200 \times 4}{120} = 40 \text{ Hz}$.

\therefore Frequency generated by the alternator is 40 Hz.

For the given induction motor, $P = 6$, Speed at full load $N = 760 \text{ rpm}$, supply frequency from the alternator is $f = 40 \text{ Hz}$.

$$\therefore \text{ Synchronous speed of the motor, } N_s = \frac{120 f}{P} = \frac{120 \times 40}{6} = 800 \text{ rpm.}$$

$$\therefore \text{ The percentage slip, } s = \frac{N_s - N}{N_s} \cdot 100 = \frac{800 - 760}{800} \times 100 = 5\%.$$

10.7 A three-phase, 400 V, 50 Hz induction motor has a speed of 900 rpm on full-load. The motor has six poles. (i) Find out the slip. (ii) How many complete alternations will the rotor voltage take per minute?

Solution

(i) Given $N = 900 \text{ rpm}$, $f = 50 \text{ Hz}$ and $P = 6$.

$$\therefore N_s = \frac{120 \times f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$\therefore \text{ slip } (s) = \frac{N_s - N}{N_s} = \frac{1000 - 900}{1000} = 0.1 \text{ or } 10\%.$$

(ii) Alternation of rotor voltage:

$$f' = s \times f = 0.01 \times 50 = 0.5/\text{sec or } 30/\text{min.}$$

10.8 A three-phase, 6-pole, 50 Hz induction motor has a slip of 0.8% at no load and 2% at full load. Calculate:

- the synchronous speed
- the no-load speed
- the full-load speed
- the frequency of rotor current at standstill
- the frequency of rotor current at full load.

Solution

$$(i) N_s = \frac{120 f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm.}$$

$$(ii) \text{ Speed at no load} = (1 - \text{slip at no load}) \times N_s = (1 - 0.008) \times 1000 = 992 \text{ rpm.}$$

$$(iii) \text{ Speed at full load} = (1 - \text{slip at full load}) \times N_s = (1 - 0.02) \times 1000 = 980 \text{ rpm.}$$

$$(iv) \text{ Frequency of rotor current at standstill } f_2 = sf = 1 \times 50 = 50 \text{ Hz.}$$

$$(v) \text{ Frequency of rotor current at full load, } f_2 = (\text{slip at full load}) \times f \\ = 0.02 \times 50 = 1.0 \text{ Hz.}$$

10.9 The voltage applied to the stator of a three-phase, 4-pole induction motor has a frequency of 50 Hz. The frequency of the emf induced in the rotor is 1.5 Hz. Determine slip and speed at which motor is running.

Solution

$$(i) N_s = \frac{120 f}{p} = \frac{120 \times 50}{4} = 1500 \text{ rpm.}$$

$$\text{Rotor emf frequency, } f_2 = sf$$

$$\text{or } 1.5 = s \times 50$$

$$\therefore \text{ slip } (s) = \frac{1.5}{50} = 0.03 \text{ or } 3.0\%.$$

$$(ii) \text{ Actual speed of motor is } N = (1 - s) \cdot N_s = 1500 (1 - 0.03) = 1455 \text{ rpm.}$$

10.10 A three-phase, 50 Hz, 6-pole cage motor is running with a slip of 3%.

Calculate:

- the speed of the rotating field relative to the stator winding
- the motor speed
- the frequency of emf induced in the rotor
- the speed of rotation of rotor mmf relative to rotor winding
- the speed of rotation of rotor mmf relative to stator winding.

Solution

$$(i) N_s = \frac{120 f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm.}$$

$$(ii) N = N_s(1 - s) = 1000 \left(1 - \frac{3}{100}\right) = 970 \text{ rpm.}$$

$$(iii) f_2 = sf_1 = \frac{3}{100} \times 50 = 1.5 \text{ Hz.}$$

$$(iv) \text{ Speed of rotor mmf relative to rotor winding} = \frac{120 \times f_2}{P} = \frac{120 \times 1.5}{6} = 30 \text{ rpm.}$$

$$(v) \text{ Since the rotor is rotating at 970 rpm and the rotor mmf is revolving at 30 rpm with respect to rotor, therefore speed of the rotor mmf relative to the stationary winding (stator) is } (970 + 30) \text{ rpm} = 1000 \text{ rpm.}$$

10.9 TORQUE EXPRESSION OF AN INDUCTION MOTOR

Operating Torque

In the induction motor, the torque T is given by

$$T \propto \phi \cdot I_r \cdot \cos \phi_r \quad (10.9)$$

where ϕ is the stator flux/pole and I_r is the rotor current/phase under running conditions, $\cos \phi_r$ is the rotor power factor.

$$\text{We have } I_r = \frac{E_r}{Z_r} = \frac{E_2 \cdot s}{\sqrt{R_2^2 + (sX_2)^2}} \quad (10.10)$$

$$\text{and } \cos \phi_r = \frac{R_r}{Z_r} = \frac{R_2}{Z_r} = R_2 / \sqrt{R_2^2 + (sX_2)^2} \quad (10.11)$$

(\because Resistance is independent of relative speed)

where E_r is rotor emf/phase

Z_r is the rotor impedance = $\sqrt{R_2^2 + (sX_2)^2}$

R_r is the rotor resistance/phase.

E_r , Z_r , R_r are the respective parameters of the rotor in running conditions. If s be the slip of the motor, operating at rated speed, we can write

$$X_r = sX_2$$

$$E_r = sE_2$$

and $R_r = R_2$

where, X_r is the rotor reactance/phase under running condition.

In the standstill condition,

X_2 is the rotor reactance/phase

E_2 is the rotor emf/phase

and R_2 is the rotor resistance/phase.

From the fundamentals, we have

$$|Z_r| = \sqrt{R_r^2 + X_r^2} = \sqrt{R_2^2 + X_r^2}$$

The equation of the torque can be rewritten as

$$T = K_1 \phi \frac{E_r}{Z_r} \cdot \frac{R_2}{Z_r}$$

[K_1 is the constant of proportionality in Eq. (10.9)]

$$= \frac{K_1 \phi sE_2 R_2}{R_2^2 + X_r^2} = \frac{K_1 \phi sE_2 R_2}{R_2^2 + (sX_2)^2} \quad (10.12)$$

Again, the flux(ϕ) produced by the stator being proportional to the applied phase voltage (E_1), we can write

$$\phi \propto E_1$$

i.e., $\phi = K_2 E_1$

$$\text{Also } \frac{E_1}{E_2} = \frac{N_1}{N_2} = k.$$

$$\therefore E_2 = \frac{1}{k} \cdot E_1$$

Substituting the expressions for ϕ and E_2 in Eq. (10.12) we get

$$T = \frac{K_1 \cdot K_2 E_1 \cdot s \cdot (E_1/k) \cdot R_2}{R_2^2 + (sX_2)^2} = \frac{KE_1^2 \cdot s \cdot R_2}{R_2^2 + (sX_2)^2} \quad (10.13)$$

$$\text{where } K = \frac{K_1 K_2}{k}$$

$$\text{i.e., } T \propto \frac{sE_1^2 R_2}{R_2^2 + (sX_2)^2} \quad (10.13a)$$

Here T is expressed in watts on per phase basis for $K = 1$. In order to get the value of three-phase torque, the expression obtained in (10.13) or (10.13a) is to be multiplied by a factor 3, provided K is known and all the quantities in the RHS of equation (10.13) are expressed in phase values. We will discuss later how K can be obtained. Actually $K = \frac{3}{\omega_s}$, where $\omega_s = 2\pi n_s$, n_s is expressed in rps i.e.,

equal to $\left(\frac{N_s}{60}\right)$. For three phase, the electromagnetic torque T is

$$T_{3\phi} = \frac{3}{\omega_s} \cdot \frac{sE_1^2 R_2}{R_2^2 + (sX_2)^2} \text{ Nm}$$

$$\text{i.e., } T_{3\phi} = 3 \cdot \frac{sE_1^2 R_2}{R_2^2 + (sX_2)^2} \text{ W} \left(= \frac{3}{\omega_s} \cdot \frac{sE_1^2 R_2}{R_2^2 + (sX_2)^2} \text{ Nm} \right) \quad (10.13b)$$

10.9.1 Starting Torque (T_s)

At starting the rotor is stationary, the slip $s = 1$ and the rotor reactance X_2 is much larger compared to the rotor resistance R_2 . So neglecting R_2 in Eq. (10.13 a), we get for $s = 1$,

$$T_s \propto \frac{E_1^2 R_2}{X_2^2} \quad (10.14a)$$

or $T_s \propto R_2$ and $T_s \propto E_1^2$ [assuming (X_2) as constant]

The general expression of starting torque can be obtained from equation (10.13) with $s = 1$.

$$T_s = \frac{KE_1^2 R_2}{R_2^2 + X_2^2} \quad (10.14b)$$

Thus for obtaining large starting torque, the rotor resistance R_2 as well as applied voltage E_1 should be large.

To get the three-phase starting torque, T_s obtained in Eq. 10.14(a) or (b) is to be multiplied by a factor 3.

10.9.2 Effect of Change in Supply Voltage in Torque and Slip

$$\text{Since } T \propto \frac{sE_1^2 R_2}{R_2^2 + (sX_2)^2},$$

at rated speed, with low values of s we have

$$T \propto \frac{sE_1^2 R_2}{R_2^2} \quad (\because (sX_2) \text{ is very low})$$

Again, it is given that $T_{st} = \frac{1}{2} T_{max}$;

$$\therefore \frac{K(0.25 + r) \cdot E_1^2}{(0.25 + r)^2 + (3.73)^2} = \frac{1}{2} \times 0.134 K \cdot E_1^2.$$

Simplifying,

$$r = 13.67 \text{ ohm or } 0.75 \text{ ohm};$$

but we ignore the value of $r = 13.67 \text{ ohm}$ as it corresponds to T_{max} lying in the region where $s > 1$.

$$\therefore r = 0.75 \text{ ohm per phase.} \quad \dots\dots\dots$$

10.15 A three-phase, 24-pole, 50 Hz, 3200 volt star connected induction motor has a slip ring rotor of resistance 0.016Ω and standstill reactance of 0.270Ω per phase. Full load torque is obtained at a speed of 247 rpm. Determine:

- the ratio of maximum to full-load torque.
- the speed at maximum torque, stator impedance being neglected.

Solution

$$(i) \text{ Synchronous speed } N_s = \frac{120 f}{P} = \frac{120 \times 50}{24} = 250 \text{ rpm.}$$

$$\therefore \text{ Slip } (s) = \frac{N_s - N}{N_s} = \frac{250 - 247}{250} = 0.012.$$

$$\text{Also, } s_{max} = \frac{R_2}{X_2} = \frac{0.016}{0.270} = 0.059.$$

$$\text{We know, } \frac{T}{T_{max}} = \frac{2 \cdot s_{max} \cdot s}{s^2 + s_{max}^2}.$$

$$\text{Here, } \frac{T}{T_{max}} = \frac{2 \times 0.059 \times 0.012}{(0.012)^2 + (0.059)^2}$$

$$\text{or } \frac{T_{max}}{T} = \frac{(0.012)^2 + (0.059)^2}{2 \times 0.059 \times 0.012} = 2.56.$$

Let N' be the intended speed at maximum torque

$$\text{Then, } s_{max} = \frac{N_s - N'}{N_s} = \frac{250 - N'}{250}$$

$s_{max} = 0.059$ from calculation we have got earlier.

$$\text{i.e., } 0.059 = \frac{250 - N'}{250}$$

$$\text{or } N' = 235.25 \text{ rpm.} \quad \dots\dots\dots$$

10.16 A three-phase, 6-pole 50 Hz. induction motor develops a maximum torque of 30 Nm at 960 rpm. Calculate the torque produced by the motor at 6% slip. The rotor resistance per phase is 0.6Ω .

Solution

Given, $f = 50 \text{ Hz.}, P = 6$

$$\therefore N_s = \frac{120 f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm.}$$

Speed at maximum torque = 960 rpm

$$\text{Slip at maximum torque} = \frac{N_s - \text{speed at maximum torque}}{N_s} = \frac{1000 - 960}{1000} = 0.04 (= s_{\max})$$

$$\text{Also, } s_{\max} = \frac{R_2}{X_2}$$

$$\therefore X_2 = \frac{R_2}{s_{\max}} = \frac{0.6}{0.04} = 15 \, \Omega.$$

$$\text{If } T \text{ is the torque at slip } s, \frac{T}{T_{\max}} = \frac{2s \cdot s_{\max}}{s^2 + s_{\max}^2}$$

$$\text{here, } s = 0.06, T_{\max} = 30 \text{ Nm}$$

$$\therefore T = \frac{2 \times 0.06 \times 0.04}{(0.06)^2 + (0.04)^2} \times 30 = 27.692 \text{ Nm.}$$

.....

10.17 A 746 kW, three-phase, 50 Hz., 16-pole induction motor has a rotor impedance of $(0.02 + j0.15) \, \Omega$ at standstill. Full load torque is obtained at 350 rpm.

Determine (i) the speed at which maximum torque occurs, (ii) the ratio of maximum to full load torque, (iii) the external resistance per phase to be inserted in the rotor circuit to get maximum torque at starting.

Solution

$$N_s = \frac{120 f}{P} = \frac{120 \times 50}{16} = 375 \text{ rpm}$$

$$\text{Speed at full load} = 350 \text{ rpm}$$

$$\therefore \text{Slip at full load} = \frac{375 - 350}{375} = 0.06$$

Slip at maximum torque

$$s_{\max} = \frac{R_2}{X_2} = \frac{0.02}{0.15} = \frac{2}{15} = 0.133$$

$$(i) \text{ Speed at which maximum torque occurs} = (1 - s_{\max})N_s = \left(1 - \frac{2}{15}\right) \times 375 = 325 \text{ rpm.}$$

$$(ii) \frac{T_{\max}}{T} = \frac{s_{\max}^2 + s^2}{2s \cdot s_{\max}} = \frac{(0.06)^2 + \left(\frac{2}{15}\right)^2}{2 \times 0.06 \times \frac{2}{15}} = 1.33.$$

(iii) Let the external resistance per phase added to the rotor circuit be ' r ' Ω , so that R rotor resistance per phase, $R_2 = (0.02 + r)$.

The starting torque will be maximum when $R_2 = X_2$

$$\therefore 0.02 + r = 0.15$$

$$\text{or } r = 0.13 \, \Omega \text{ per phase.}$$

.....

10.10 TORQUE SLIP CHARACTERISTICS OF A THREE-PHASE INDUCTION MOTOR

The torque T of an induction motor (three-phase) is given by (Eq. 10.13)

$$T = \frac{KE_1^2 R_2 \cdot s}{R_2^2 + X_2^2 s^2}$$

For a constant supply voltage E_1 , the value of E_2 is constant. Assuming R_2 as constant, we can write

$$T \propto \frac{s}{R_2^2 + X_2^2 s^2} \quad (10.22)$$

At synchronous speed, slip s is zero, hence torque T is zero; at starting $s = 1$, thus torque T is maximum.

Consequently, the torque slip curve starts from origin (i.e., $s = 0$), and ends at $s = 1$.

Case study I: When s (slip) is very low (at rotor speeds close to synchronous speed), $sX_2 \ll R_2$ and $T \propto \frac{s}{R_2^2}$ (at low-slips).

i.e., Torque-slip curve at low values of slip is a straight line passing through the origin, and torque is maximum when $s = \frac{R_2}{X_2}$.

Case study II: When the load on the motor increases, the speed of the motor decreases. When slip s is large, compared to R_2 , sX_2 is much large and hence $sX_2 \gg R_2$.

$$\therefore T \propto \frac{s}{(sX_2)^2} \propto \frac{1}{sX_2^2} \propto \frac{1}{s} \quad (\text{at high slips})$$

i.e., the torque T slip s curve for larger values of slip is approximately a rectangular hyperbola. Consequently, any further increase in motor load, beyond the point of maximum torque, results in decrease of the torque developed by the motor. Eventually, the motor slows down. The maximum torque developed in an induction motor is called the *pull-out torque* or *break down torque*. This torque is a measure of the short time over loading capability of the motor. Figure 10.4 Shows the torque-slip characteristics of an induction motor operating with constant applied voltage, and constant frequency.

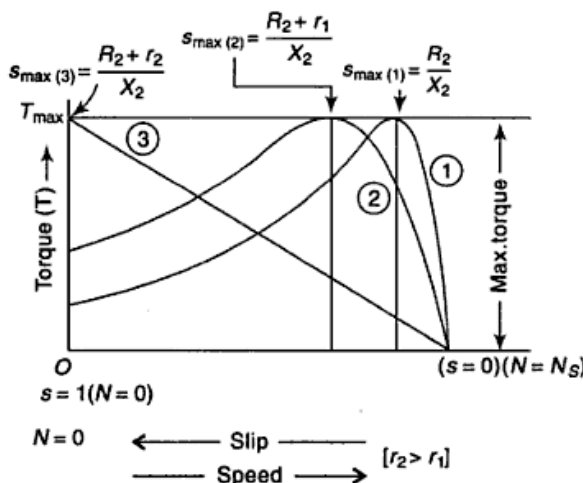


Fig. 10.4 Torque-slip characteristics of an induction motor

Curve 1 represents (T-s) characteristic of an induction motor having low rotor resistance or when no resistance is inserted in the rotor circuit.

Maximum torque is developed at $s_{\max}(1) = \frac{R_2}{X_2}$.

Curve 2 represents the (T-s) characteristic of an induction motor. When an external resistance of $r_1 \Omega/\text{phase}$ is inserted in the rotor circuit the magnitude of the maximum torque remains unchanged, but the slip for maximum torque in $s_{\max}(2) = (R_2 + r_1)/X_2$.

Curve 3 represents the (T-s) characteristic of an induction motor, when an external resistance of $r_2 \Omega/\text{phase}$ is inserted in the rotor circuit such that $R_2 + r_2 = X_2$, a condition for maximum torque is there at starting.

It may be noted here that $(R_2 + r_2) > (R_2 + r_1) > R_2$

It is also seen that *as the rotor resistance is increased, the pull out speed of the motor decreases, but the maximum torque remains constant.* However, for squirrel cage rotors it is not possible to insert any rotor resistance under normal operating conditions and hence *it is not easily possible to enhance the value of the starting or maximum torque for a squirrel cage induction motor.*

10.11 EQUIVALENT CIRCUIT OF INDUCTION MOTOR

In the case of an ideal induction motor, the equivalent circuit can be represented like that of an ideal transformer. The only difference is that the rotor of induction motor is not static and mechanical power is developed.

Figure 10.5(a) shows the equivalent circuit of an induction motor with all quantities referred to the stator. During shifting of impedance or resistance from the secondary to primary, the secondary quantity is multiplied by (k^2) , (where $k =$ transformation ratio = number of stator turns/number of rotor turns). *It is to be remembered that the equivalent circuit is always drawn for the per phase values.*

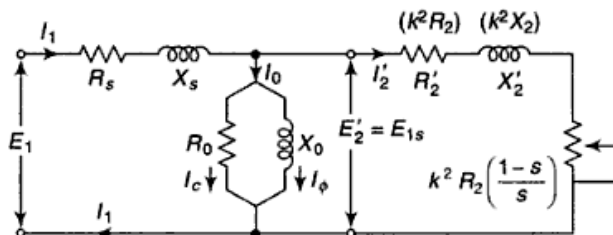


Fig. 10.5(a) Equivalent circuit of an induction motor

Looking at the stator side, counter emfs are generated in all the three phases of stator due to rotating air-gap flux wave. The application of a voltage E_1 to the stator winding creates a mutual flux which sets up induced emf E_{1s} in the stator and rotor. Since $E_{1s} < E_1$, so this difference $(E_1 - E_{1s})$ represents the impedance drop $[I_1 (R_s + jX_s)]$. The effect of no-load current $I_0 (= I_c + I_\phi)$, where I_c is the core loss component and I_ϕ is the magnetizing component lagging by an angle $\pi/2$ and is represented by a shunt consisting of R_0 and X_0 connected in parallel).

Thus, R_0 and X_0 account for *working component* and *magnetizing component* of no-load current respectively.

Now, if we block the rotor and make the total rotor resistance equal to R_2/s by inserting an additional resistance in the rotor circuit, then the rotor current, mmf, reactance of rotor on stator, stator current and input to machine would be same as they were when the rotor was running at slip s .

$$\text{Also, } \frac{R_2}{s} = R_2 + R_2 \left(\frac{1-s}{s} \right)$$

$$= \text{Actual resistance of rotor} + \text{Fictitious resistance} \left(R_2 \cdot \frac{1-s}{s} \right).$$

Let us calculate the rotor quantities with respect to the stator. If k is the effective transformation ratio then total rotor resistance R_2 and reactance X_2 , when referred to the stator, appear as R_2' and X_2' where ($R_2' = R_2 k^2$) and ($X_2' = X_2 k^2$).

Moreover, the rotor current I_2 when referred to the stator, appears as $I_2' \left(= \frac{I_2}{k} \right)$.

Also, $I_2' + I_0 = I_1$ (stator current). In the above expression $\left[R_2 \left(\frac{1-s}{s} \right) \right]$ is the electrical analogue of the variable mechanical load and is the *fictitious resistance* equivalent to load on the motor.

The equivalent circuit can be simplified by transforming no-load current component to the supply side as shown in Fig. 10.5(b).

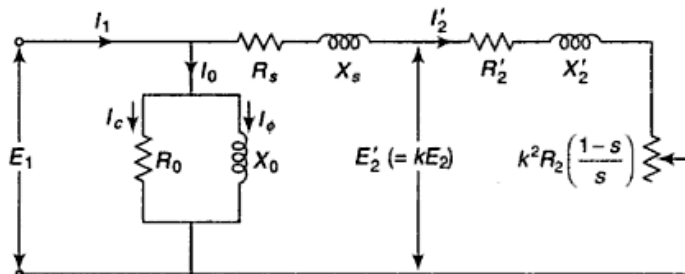


Fig. 10.5(b) Simplified equivalent circuit

The phasor diagram of the induction motor is shown in Fig. 10.5(c).

10.12 LOSSES AND EFFICIENCY

At starting and during acceleration the rotor core losses are high; with the increase in speed these losses decrease to some extent. The friction and windage losses are zero at start and with increase in speed these losses increase. However, the sum of friction, windage and core losses is roughly constant for a motor even with variable speed. Therefore, these categories of losses are sometimes lumped together and called *constant losses* and are then defined as follows:

$$P_{(\text{constant loss})} = P_{\text{core loss}} + P_{\text{mechanical loss}}$$

\therefore Output power P_0 = Total mechanical power developed – Mechanical losses

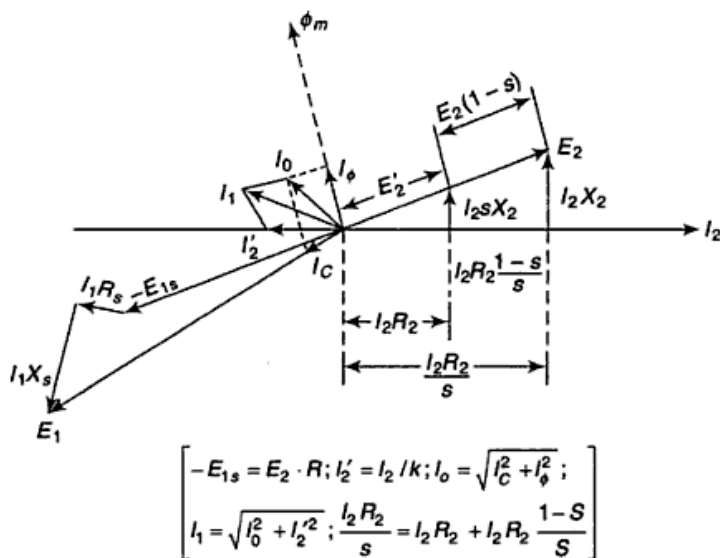


Fig. 10.5(c) Phasor diagram of a 3-phase induction motor on per phase basis

Losses in a three-phase Induction motor are of two types mainly (a) Fixed losses and (b) Variable losses.

- | | |
|---------------------|--|
| (a) Fixed losses | <ul style="list-style-type: none"> — Core loss — Bearing friction loss — Brush friction loss in wound rotors — Windage loss |
| (b) Variable losses | <ul style="list-style-type: none"> — Stator ohmic loss ($I^2 R$ loss in stator) — Rotor ohmic loss ($I^2 R$ loss in rotor) — Brush contact loss for wound rotor motors only — Stray load loss. |

The rotor output gives rise to the development of *gross torque* or *electromagnetic torque* T_g , which is partly “wasted” (in the form of winding, and frictional losses in the rotor), and partly appears as the *useful shaft torque* T_{sh} . Let n be the actual speed of the rotor (in rps) and T_g be the gross torque (or electromagnetic torque) developed by the rotor, then,

$$T_g \times 2\pi n = \text{Rotor output } (P_0)$$

$$\text{or} \quad \text{Gross torque } T_g = \frac{\text{Rotor output } (P_0)}{2\pi n} \quad (10.23)$$

Since the copper losses in the rotor is negligible, so the input of the rotor equals the output of the rotor.

$$\therefore T_g = \frac{\text{Rotor input } (P_{ag})}{2\pi n_s} \quad (10.24)$$

(n_s being the synchronous speed in rps)

From Eqs (10.23) and (10.24) we can write

$$\text{Rotor output } (P_o) = T_g \times 2\pi n$$

$$\text{and} \quad \text{Rotor input } (P_{ag}) = T_g \times 2\pi n_s$$

$$\therefore \text{Copper losses (ohmic loss) of rotor} = \text{Rotor input} - \text{Rotor output} \\ = T_g \cdot 2\pi (n_s - n)$$

$$\text{i.e. } P_{rcu} = T_g \cdot 2\pi \frac{(n_s - n)}{n_s} \quad n_s = T_g \cdot 2\pi \cdot s \cdot n_s = \text{Slip} \times \text{Rotor input } (P_{ag})$$

$$\therefore P_{rcu} = s \times P_{ag} \quad (10.25)$$

when (P_{rcu}) is the rotor copper loss.

Hence gross mechanical power developed in rotor P_m is equal to (rotor input P_{ag} – rotor copper losses).

$$\text{i.e., } P_m = \text{Rotor input} - s \times \text{Rotor input} = \text{Rotor input } (1 - s)$$

$$\text{or, } P_m = P_{ag}(1 - s) \quad (10.26)$$

Hence, rotor efficiency

$$\eta = \frac{\text{Output of rotor}}{\text{Rotor input}} \\ = (1 - s) = 1 - \left(\frac{n_s - n}{n_s} \right) = \frac{n}{n_s} = \frac{\text{Actual speed of rotor}}{\text{Synchronous speed of the motor}} \quad (10.27)$$

[The torque of a polyphase induction motor may be expressed in "Synchronous Watts". It is defined as the torque which develops a power of 1 W at the synchronous speed of the motor.

\therefore Rotor input $= T_g \times 2\pi n_s$, hence we can write

$$T_g (\text{synchronous W}) = \frac{\text{Rotor input in W}}{2\pi \times n_s},$$

where n_s is expressed in rps.]

Also, Copper losses of rotor $(P_{rcu}) = s \times \text{Rotor input } (P_{ag})$

$$\text{or } P_{rcu} = s \times \frac{\text{Mechanical power in rotor } (P_m)}{(1 - s)} \\ = \left(\frac{s}{1 - s} \right) \times \text{Mechanical power developed in rotor } (P_m) \quad (10.28)$$

\therefore Rotor input : rotor copper loss : mechanical power developed in rotor = 1 : s : (1 - s).

It may be noted here that T or T_g (developed torque/gross torque/electromagnetic torque) can thus be obtained from the following formula:

$$T (=T_g) = \frac{P_{ag}}{\omega_s} \text{ Nm, where } \omega_s = 2\pi n_s \text{ and } (P_{ag}) \text{ is the air gap power of the}$$

motor, i.e. the power being transferred from the stator to rotor. We have termed it as rotor input earlier where rotor input (= air gap power) = (stator input – stator copper loss – stator core loss).

The shaft output torque T_{sh} is developed at the output of the motor (i.e., at the shaft) and is due to the output power which is the difference between the air gap power (or rotor input) and the rotor losses. Rotor losses include rotor copper loss and mechanical losses (we neglect the rotor iron loss). Thus the shaft torque is obtained as

$$T_{sh} = \frac{P_0}{\omega} \text{ Nm,}$$

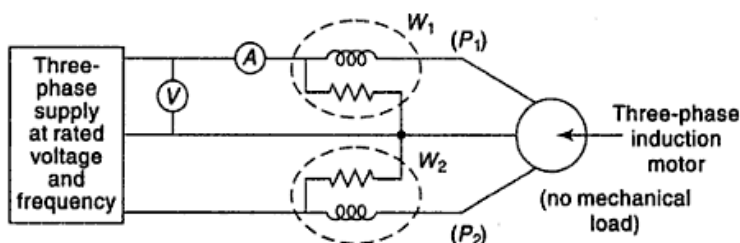


Fig. 10.7(a) Circuit diagram for no-load test on a three-phase induction motor

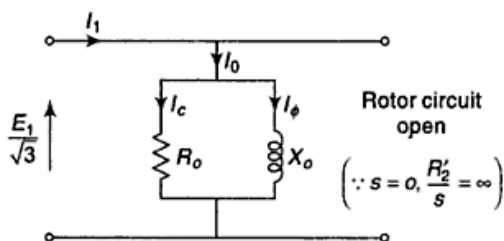


Fig. 10.7(b) Equivalent circuit at no load

Blocked Rotor Test The circuit is the same as shown in Fig. 10.8. The motion of the rotor is blocked by a brake (or a belt). This test is analogous to the short-circuit test of a transformer because the rotor winding is short-circuited through slip rings and in cage motors, the rotor bars are permanently short circuited. Only a reduced voltage needs to be applied to the stator at rated frequency. This voltage should be such that the ammeter reads rated current of the motor.

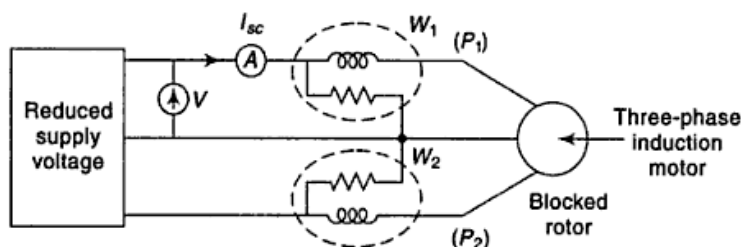


Fig. 10.8(a) Circuit diagram for blocked rotor test

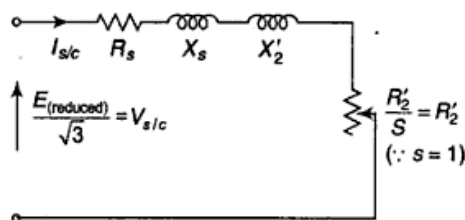


Fig. 10.8(b) Equivalent circuit during blocked-rotor test

The total power input on short circuit $W_{s/c}$ is equal to the algebraic sum of the two wattmeter readings, i.e. equals the copper losses of the stator and rotor. Let $V_{s/c}$ and $I_{s/c}$ be the voltage and current per phase; then the power factor under blocked rotor condition is

$$\cos \theta_{s/c} = \frac{W_{s/c}}{3(V_{s/c})(I_{s/c})} \text{ [neglecting the core and mechanical losses].}$$

Since in a R-L circuit, $R = Z \cos \theta$ and $X = Z \sin \theta$, here we can write

$$(R_s + R_2') = \left(\frac{V_{s/c}}{I_{s/c}} \right) \cos \theta_{s/c} \quad (10.32a)$$

$$(X_s + X_2') = \left(\frac{V_{s/c}}{I_{s/c}} \right) \sin \theta_{s/c} \quad (10.32b)$$

The stator resistance R_s is measured separately by using a battery, ammeter and a voltmeter. Then R_2' can be found from equation 10.32(a). The reactances (X_s) and (X_2') are generally assumed equal.

10.18 A three-phase, 5 HP, 400 V, 50 Hz induction motor is working at full load with an efficiency of 90% at a power factor of 0.8 lagging. Calculate: (i) the input power and (ii) the line current.

Solution

Rating of the motor = 5 HP = $5 \times 735.5 = 3677.50$ watt; $V = 400$ V (line value); $f = 50$ Hz; full-load efficiency = 90% (= 0.9) and p.f = 0.8 (lagging)

$$(i) \because \text{Efficiency } \eta = \frac{\text{Output}}{\text{Input}},$$

$$\therefore \text{Input power} = \frac{\text{Output}}{\eta} = \frac{5 \times 735.5}{0.9} = 4.086 \text{ kW}$$

(ii) For a three-phase induction motor

$$\text{Input power} = \sqrt{3} V_L I_L \cos \phi$$

$$\text{or } 4086 = \sqrt{3} \times 400 \times I_L \times 0.8$$

$$\text{Hence the line current } (I_L) = \frac{4086}{\sqrt{3} \times 400 \times 0.8} = 7.37 \text{ A.}$$

.....

10.19 A three-phase, 4-pole induction motor runs at a speed of 1440 rpm on 500 V, 50 Hz mains. The mechanical power developed by the rotor is 20.3 HP. The mechanical losses are 2.23 HP. Determine (i) the slip, (ii) the rotor copper losses (iii) the efficiency.

Solution

$$(i) N_s = \frac{120 \cdot f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$\therefore \text{Slip} = \frac{N_s - N}{N_s} = \frac{1500 - 1440}{1500} = 0.04 \text{ or } 4\%.$$

(ii) Mechanical power developed in rotor = Power output + rotor losses = $20.3 + 2.23 = 22.53$ HP = $22.53 \times 735.5 = 16.571$ kW

$$\therefore \text{Power transferred from stator to rotor } (P_{ag}) = \frac{16571}{(1-s)} = \frac{16571}{(1-0.04)} = 17261.46 \text{ W}$$

$$\therefore \text{Rotor copper losses} = 17261.46 - 16571.00 = 690.46 \text{ W.}$$

$$(iii) \text{ Efficiency } (\eta) = \frac{\text{Output}}{\text{Input}} = \frac{20.3 \times 735.5}{17261.46} = 0.865 = 86.5\%.$$

10.20 The full-load slip of a 500 HP, 50 Hz three-phase induction motor is 0.03. The rotor winding has a resistance of $0.30 \Omega/\text{phase}$. Determine the slip and the power output, if external resistance of 2 ohms is inserted in each rotor phase. Assume that the torque remains same.

Solution

$$(i) R_2 = 0.3 \Omega, R_2' = 2 + 0.3 = 2.3 \Omega, s = 0.03$$

$$\therefore \text{ Slip } s' = \frac{R_2' \cdot s}{R_2} = \frac{2.3 \times 0.03}{0.3} = 0.23$$

(ii) Let N_s be the synchronous speed, then

$$N = N_s (1 - 0.03) = 0.97 N_s$$

and $N' = N_s (1 - 0.23) = 0.77 N_s$ [N' is the new speed when external resistance of 2 ohm is inserted in each rotor phase]

Since the torque remains same, output is directly proportional to speed.

$$\therefore \text{ New motor output} = 500 \times \frac{0.77 N_s}{0.97 N_s} = 397 \text{ HP.}$$

10.21 A three-phase, 50 Hz, 4-pole induction motor has a star connected wound rotor. The rotor emf is 50 V between the slip rings at standstill. The rotor resistance and standstill reactance are 0.4Ω and 2.0Ω respectively. Calculate

- the rotor current per phase at starting with slip rings short circuited,
- the rotor current per phase at starting if 50Ω per phase resistance is connected between slip rings,
- the rotor emf when the motor is running at full load at 1440 rpm,
- the rotor current at full load, and
- rotor power factor (p.f.) at full load.

Solution

$$N_s = \frac{120 \times 50}{4} = 1500 \text{ rpm.}$$

$$(i) E_2 = \frac{50}{\sqrt{3}} = 28.867 \text{ V.}$$

At standstill with slip rings short circuited

$$I_2 = \frac{E_2}{(R_2^2 + X_2^2)^{0.5}} = \frac{28.867}{\{(0.4)^2 + 2^2\}^{0.5}} = 14.15 \text{ A.}$$

(ii) The total resistance in the rotor circuit is 5.4 ohm per phase.

$$\therefore I_2 = \frac{28.867}{\{(5.4)^2 + 2^2\}^{0.5}} = 5.01 \text{ A.}$$

$$(iii) \text{ Full load slip} = \frac{1500 - 1440}{1500} = 0.04$$

$$\therefore \text{ Rotor emf} = 28.87 \times 0.04 = 1.155 \text{ V/Ph.}$$

$$(iv) I_2 = \frac{sE_2}{[R_2^2 + (sX_2)^2]^{0.5}} = \frac{1.155}{[0.4^2 + (0.04 \times 2)^2]^{0.5}} = 2.82 \text{ A.}$$

$$(v) \text{ Rotor power factor (full load)} = \frac{R_2}{Z_2} = \frac{0.4}{[0.4^2 + (0.04 X_2)^2]^{0.5}} = 0.98 \text{ (lagging)}$$

10.22. A three-phase, 4-pole, 50 Hz induction motor supplies a useful torque of 160 N-m at 4% slip. Determine: (i) rotor input, (ii) motor input, (iii) efficiency. Friction and windage losses are 500 W and stator loss is 1000 W.

Solution

$$(i) \text{ Motor speed, } N = N_s(1 - s) = \frac{120 f (1 - s)}{P} = \frac{120 \times 50 (1 - 0.04)}{4} = 1440 \text{ rpm.}$$

Gross power developed in rotor of motor

$$(P_m) = \frac{T_{\text{shaft}} \times 2\pi N}{60} + \text{friction} + \text{windage losses.}$$

$$\text{or, } (P_m) = \frac{160 \times 2\pi \times 1440}{60} + 500 = 24615 \text{ W.}$$

$$\therefore \text{ Rotor input } (P_g) = \frac{P_m}{(1 - s)} = \frac{24615}{(1 - 0.04)} = 25640 \text{ W.}$$

$$(ii) \text{ Motor input } (P_{in}) = \text{Rotor input } (P_{ag}) + \text{stator losses} = 25640 + 1000 = 26640 \text{ W}$$

$$(iii) \text{ Efficiency } (\eta) = \frac{\text{Net motor output } (P_o)}{\text{Motor input } (P_{in})} = \frac{24615 - 500}{26640} = 0.9052 = 90.52\%$$

10.23. A three-phase, 50 Hz, 4-pole induction motor has a slip of 4%. Determine (i) speed of the motor, (ii) frequency of rotor emf. (iii) if rotor has a resistance of 1 Ω and standstill reactance of 4 Ω , calculate power factor (a) at stand still and (b) at speed of 1400 rpm.

Solution

$$(i) N_s = \frac{120 f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm.}$$

$$\text{Now, slip } (s) = 0.04 = (N_s - N)/N_s = \frac{(1500 - N)}{1500}$$

$$\therefore \text{ Speed of motor, } N = 1440 \text{ rpm.}$$

$$(ii) \text{ Frequency of rotor emf, } f_2 (= sf_1) = 0.04 \times 50 = 2 \text{ Hz} = 120 \text{ rpm.}$$

$$(iii) (a) \text{ at standstill, } N = 0, \text{ so } s = 1$$

$$\therefore \text{ Rotor reactance} = 4 \times s = 4 \times 1 = 4 \Omega$$

$$\therefore \text{ Rotor impedance} = (1 + j4) \text{ ohm} = 4.123 \angle 75.96^\circ \Omega \text{ and p.f. } (\cos \phi) = \cos 75.96^\circ = 0.243 \text{ (lag).}$$

[Rotor resistance is independent of slip and hence $R_2 = 1 \Omega$]

$$(b) \text{ Slip at 1400 rpm speed is given by}$$

$$s' = (1500 - 1400)/1500 = 0.067.$$

$$\therefore \text{ Rotor impedance } (Z') = 1 + j(4 \times 0.067) = (1 + j0.268) \Omega$$

$$\text{and p.f. } (\cos \phi) = \frac{1}{\{1^2 + (0.268)^2\}^{0.5}} = 0.966 \text{ lag.}$$

10.24. The power input to a 6-pole, three-phase, 50 Hz induction motor is 40 kW. Stator loss is 1 kW. Friction and windage loss = 0.2 kW. Speed is 960 RPM. Calculate (i) the slip, (ii) the BHP (iii) the rotor copper loss, and (iv) the efficiency η .

Solution

$$(i) N_s = \frac{120 f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

We know

$$P_{md} = 2\pi NT$$

$$\therefore \text{Torque } (T) = \frac{8840 \times 60}{2\pi \times 950} = 88.90 \text{ Nm}$$

$$\text{Also, } T_{st} = \frac{s^2 + s_{max}^2}{s(1 + s_{max}^2)} \cdot T$$

$$\text{Here, } T_{st} = \frac{(0.05)^2 + (0.2)^2}{0.05[1 + (0.2)^2]} \times 88.9 = 72.63 \text{ Nm.}$$

10.27 A three-phase, 440 V, 50 Hz, 6-pole induction motor running at 950 rpm takes 50 kW at a certain load. The friction and windage loss is 1.5 kW and stator losses = 1.2 kW. Determine (i) the slip (ii) the rotor copper loss (iii) the output from the rotor and (iv) efficiency.

Solution

$$(i) \text{ Slip} = \frac{N_s - N}{N_s} = \frac{1000 - 950}{1000} = 0.05.$$

$$\left(\text{as } N_s = \frac{50 \times 120}{6} = 1000 \text{ rpm} \right).$$

$$(ii) \text{ Rotor copper loss} = \text{slip} \times \text{rotor input} = 0.05 \times 48.8 \text{ kW} = 2.44 \text{ kW.}$$

[rotor input = input – stator loss = 50 – 1.2 = 48.8 kW]

$$(iii) \text{ Rotor output} = \text{Rotor input} - \text{Rotor copper loss} - \text{Friction and windage loss}$$

$$= 48.8 - 2.44 - 1.5 = 44.86 \text{ kW.}$$

$$(iv) \text{ Efficiency } (\eta) = \frac{\text{motor output}}{\text{motor input}} \times 100 = \frac{44.86}{50} \times 100 = 0.897 = 89.7\%.$$

10.28 A three-phase, 415 V, 50 Hz star connected 4-pole induction motor has stator impedance $Z_1 = (0.2 + j0.5) \Omega$ and rotor impedance referred to stator side is $Z_2 = (0.1 + j0.5) \Omega$ per phase. The magnetizing reactance is 10Ω and resistance representing core loss is 50Ω on per phase basis.

Determine (i) the stator current (ii) the stator power factor (iii) the rotor current. Consider slip as 0.04.

Solution

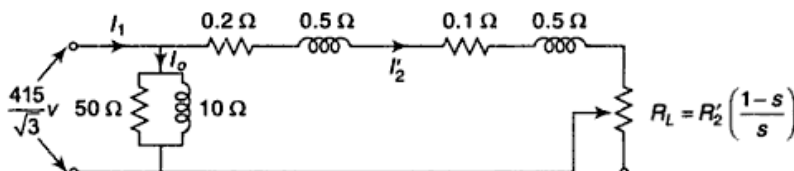


Fig. 10.9 Circuit diagram of Ex. 10.28

Let Z be the total impedance of the circuit (Fig. 10.9).

$$\text{Load resistance } R_L = R_2' \left(\frac{1-s}{s} \right) = 0.1 \left(\frac{1-0.04}{0.04} \right) = 2.4 \Omega.$$

$$\therefore \text{Total resistance } R_{te} = 2.4 + 0.2 + 0.1 = 2.7 \Omega$$

$$\text{and total reactance } X_1 = 0.5 + 0.5 = 1 \Omega$$

$$\text{Impedance } Z_1 = \sqrt{(2.7)^2 + 1} = \sqrt{8.29} = 2.88 \, \Omega.$$

Angle of Z_1 is \tan^{-1} is $(1/2.7)$ i.e., 20.323° (lag.)

Given, $V_L = 415 \, \text{V}.$

$$\therefore V_{\text{phase}} = \frac{415}{\sqrt{3}} = 240 \, \text{V}$$

$$\therefore I_2' = \frac{V_{\text{ph}}}{Z_1} = \frac{240 \angle 0^\circ}{2.88 \angle 20.325^\circ} = 83.36 \angle -20.323^\circ \, \text{A}$$

i.e., rotor current (referred to stator) = $83.36 \, \text{A}$ (Ans. of (iii))

$$[\text{Also, } I_2' = 83.36 \angle -20.323^\circ]$$

$$\therefore \frac{V_{\text{ph}}}{Z_1} = \frac{2400^\circ}{2.88/20.325}$$

$$\therefore I_0 = I_C + I_\phi$$

$$\text{and } I_C = I_0 \cos \phi_0, \text{ we have, } I_C = \frac{240}{50} = 4.8 \, \text{A}$$

$$\text{and } I_\phi = I_0 \sin \phi_0 = \frac{240}{10} = 24 \, \text{A}$$

$$\therefore I_0 = (4.8 - j24) \, \text{A}$$

$$\text{Thus, } I_1 = I_0 + I_2' = (4.8 - j24) + (78.17 - j28.95) = (82.97 - j52.95) \, \text{A}$$

$$\therefore |I_1| = \sqrt{(82.97)^2 + (52.95)^2} = 98.44 \, \text{A} \quad (\text{Ans. of (i)})$$

$$\text{Again, } \tan \phi_1 = \frac{52.95}{82.97} = 0.63818$$

$$\text{or, } \phi_1 = 32.545^\circ.$$

$$\text{i.e., } \cos \phi_1 = \cos (32.545^\circ) = 0.843 \text{ (lagging)} \quad (\text{Ans. of (ii)})$$

10.29 A 20 Hp three-phase, 400 V star connected induction motor gave the following test results:

DC test with the stator windings of two phases in series: 21 V, 30 A.

No load test: Applied voltage 400 V line, line current 8 A, wattmeter reading (2360) W and (-1160) W.

Short circuit test: Applied voltage 140 V, line current 33 A, wattmeter reading 2820 W and -370 W.

Determine the parameters of the equivalent circuit. Assume $X_1 = X_2'$.

Solution

Since two phases of stator windings are in series in the dc test, we have

$$2R_1 = \frac{21}{30} = 0.70 \, \Omega$$

$$\text{or } R_1 = 0.35 \, \Omega.$$

No load test:

$$V_o = \frac{400}{\sqrt{3}} = 230.95 \, \text{V}; I_o = 8 \, \text{A}.$$

$$W_o(W_{10} + W_{20}) = 2360 - 1160 = 1200 \, \text{W}.$$

$$\therefore \cos \theta_o = \frac{1200}{3 \times 230.95 \times 8} = 0.216$$

$$R_o = \frac{V_o}{I_o \cos \theta_o} = \frac{230.95}{8 \times 0.216} = 133.65 \, \Omega.$$

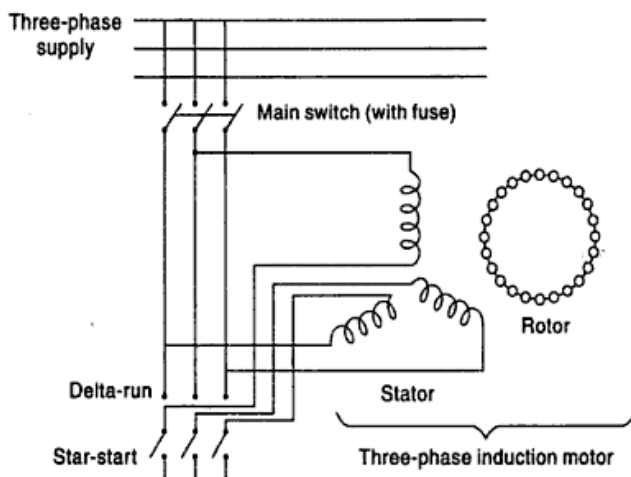


Fig. 10.11 Star-delta starter

At $S = 1$ (i.e., at starting),

$$T_s = \frac{1}{N_s} I_2'^2 \times R_2' \quad [I_2' \text{ is the rotor current reflected at primary at starting}]$$

$$\therefore \frac{T_s}{T} = \frac{I_2'^2}{I_2'^2}$$

If T represents full load figure, I_2' the full load rotor current reflected to primary, we have $I_{f,r} = I_2'$, neglecting the magnetizing branch current. Similarly I_2'' represents the starting current (I_3) at stator, the magnetizing branch being neglected.

$$\therefore \text{We can write, } \frac{T_s}{T} = \left(\frac{I_s}{I_f} \right)^2 \times s_f \quad (10.33)$$

The starting line current of the motor with star-delta starter is thus also reduced to $\frac{1}{\sqrt{3}}$ full voltage starting line current. The starting torque which is

proportional to $\left(\frac{E_1}{\sqrt{3}} \right)^2$ is reduced to $1/3$ of the full load torque. Thus, for star delta start though we are able to reduce the starting current, we sacrifice the torque and the starting torque reduces to $1/3$ of the full load torque.

Let us analyse the star delta starting method to find the torque. We assume that the motor first operates with star connection [Fig. 10.12(a)] and when speeds up it operates with delta connection of the stator [Fig. 10.12(b)].

In Fig. 10.12(a),

Starting line (phase) current ($I_{s(\text{star})}$) is given by

$$I_{s(\text{star})} = \frac{E/\sqrt{3}}{Z_s} = \frac{1}{\sqrt{3}} \cdot \frac{E}{Z_s} = \frac{1}{\sqrt{3}} \cdot I_{P(\text{start})} \quad [I_{P(\text{start})} \text{ is the starting phase current}]$$

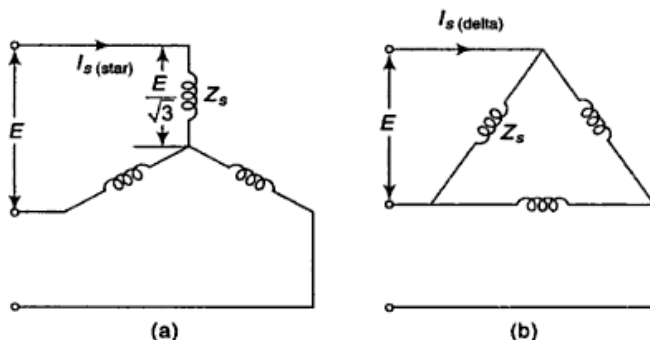


Fig. 10.12 Star-delta starting

In Fig. 10.12(b),

$$\text{Starting phase current } I_{P(\text{start})} = \frac{E}{Z_s}$$

$$\therefore \text{Starting line current } I_{s(\text{delta})} = \sqrt{3} I_{P(\text{start})}$$

$$\therefore \frac{I_{s(\text{start})}}{I_{s(\text{delta})}} = \left(\frac{1}{\sqrt{3}} \cdot I_{P(\text{start})} \right) \div (\sqrt{3} I_{P(\text{start})}) = \frac{1}{3}.$$

Using relation (10.33) we can write $T_{s(\text{star})}/T_{\text{fl}} = \frac{1}{3} (I_{P(\text{start})}/I_{\text{fl}})^2 \times s_{\text{fl}}$. Thus starting torque is $\frac{1}{3}$ of that obtained in DOL starting.

This method is bit economical one but for motors rated beyond 3 KV, this method is not applicable. Like other three-phase motor starters, in this starter also overload coil and no-voltage coils are provided for the protection of the motor (not shown in the star-delta figure). An automatic star-delta starter can also be made by using push button, contactors, time delay relay (TDR), etc.

Auto-Transformer Starter (Fig. 10.13)

In this method reduced voltage is obtained by some fixed tapings on the three-phase auto transformer. Generally 60 to 65% tapings can be used to obtain a safe value of starting current. The full rated voltage is applied to the motor by taking the auto-transformer out of the motor circuit when motor has picked up the speed upto 85% of its normal speed. Figure 10.13 shows the circuit.

Let us assume that the input voltage E is reduced to xE using auto-transformer tapings.

\therefore the motor starting current is, $I_s = xI$, where I is the motor starting current when full voltage E is applied. However, the current drawn from the supply $I_{s(\text{line})}$ is obtained from the relation

$$\frac{I_{s(\text{line})}}{I_{s(\text{motor})}} = x$$

$$\therefore \text{ here we have } I_{s(\text{line})} = x \cdot I_{s(\text{motor})} = x^2 I.$$

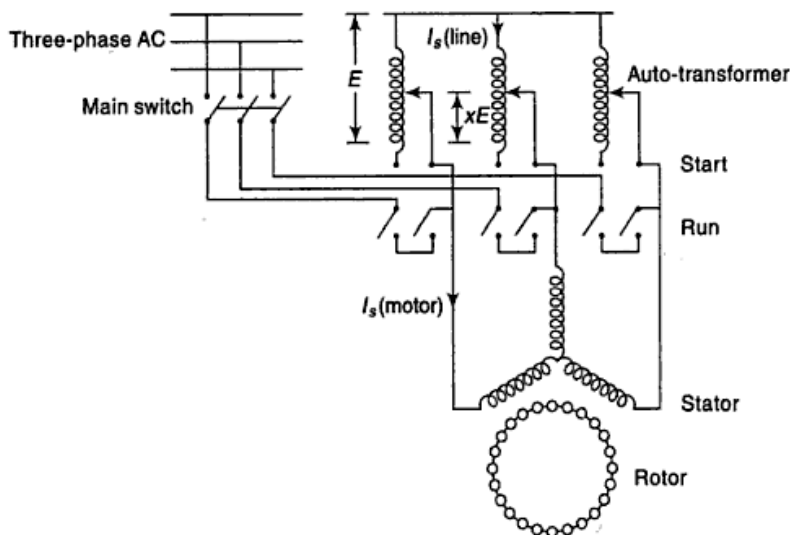


Fig. 10.13 Auto-transformer starter

Hence from relation (10.33) we get

$$\frac{T_s}{T_n} = x^2 \left(\frac{I}{I_n} \right)^2 \cdot s_n$$

It is found that while the starting torque is reduced by x^2 of that of DOL start, starting line current is also reduced by same fraction.

10.15 COMPARISON AMONG DIRECT ON LINE STARTER, STAR DELTA STARTER AND AUTO- TRANSFORMER STARTER

DOL starter	Star delta starter	Auto-transformer starter
1. Full voltage is applied to the motor at the time of starting.	1. Each winding gets 58% of the rated line voltage at the time of starting.	1. The starting voltage can be adjusted according to the requirement.
2. The starting current is 5–6 times of the full load current.	2. The starting current is reduced to $\frac{1}{3}$ that of direct on line starting.	2. The starting current can be reduced as desired.
3. The three windings are connected generally in star.	3. The three windings are connected in star at the time of starting, and then in delta at the time of running.	3. The three windings are generally connected in delta.
4. Only three wires are to be brought out from the motor.	4. Six wires to be brought out from the motor.	4. Only three wires are to be brought out from the motor.

(Contd)

(Contd)

5. Easy to connect motor with direct on line.	5. Identification of three starting leads and three end leads is not so easy.	5. Input and output connections of the auto-transformers are to be made properly.
6. Very easy operation.	6. It is required that connections are first to be made in star, and then in delta either manually or automatically.	6. Skilled operator is needed for connection and starting.
7. Low cost.	7. More cost	7. High cost.
8. Less space required for installation.	8. More space required	8. More space required.
9. Used for motor up to 5 HP.	9. Up to 10 HP	9. Large motors.

10.16 SPEED CONTROL OF A THREE-PHASE INDUCTION MOTOR

The synchronous speed (N_s) of a three-phase induction motor is given by

$$N_s = \frac{N}{1-s} \text{ or } N = N_s (1-s) = \frac{120 f}{P} (1-s)$$

The speed N of induction motor can be changed by the three basic methods.

(a) Frequency Control Changing the supply frequency f the speed can be varied directly proportional to the supply frequency of ac supply.

(b) Pole Changing Speed control can also be obtained by changing the number of poles P on the stator (as speed is inversely proportional to the number of poles). This change can be incorporated by changing the stator winding connections with a suitable switch. The change in the number of stator poles P changes the synchronous speed N_s of the rotating flux, thereby the speed of the motor also changes.

(c) By Changing the Slip This can be accomplished by introducing resistance in the rotor circuit, which causes an increase in slip, thereby bringing down the speed of the motor.

Change of Supply Frequency

If the frequency of the supply to the stator of an induction motor is changed its synchronous speed is changed depending on the frequency and hence provides a direct method of speed control. To keep the magnetization current within limits, the applied voltage must be reduced in direct proportion to the frequency. Otherwise the magnetic circuit will become saturated resulting in excessive magnetization current.

The starting torque at reduced frequency is not reduced in the same proportion, because rotor power factor improves with reduction in frequency. The torque

that can be produced by the maximum permissible rotor current is equal to that at rated conditions. Since power is the product of torque and speed, operation at reduced speed results in lesser permissible output.

This method of speed control is not a common method and hence this method would be used only as a special case.

In earlier days, the variable frequency was obtained from a motor generator set or mercury arc inverter. In recent days frequency control is used by SCR based inverters or by using IGBT inverters.

Pole Changing

If an induction motor is to run at different speeds, one way is to have different windings for the motor so that it will have different synchronous speeds and the running speeds. Another method is used with suitable connections for a change-over to double the number of poles. The principle of formation of consequent poles is used. The method of changing the number of poles is accomplished by producing two sections of coils for each phase which can be reversed with respect to the other section. It is important to note in this connection that slot angle (i.e. electrical degrees), phase spread, breadth factor and pitch factors will be different for the low and high speed connections. The three phases can be connected in star or delta, thus giving a number of connections. If 50% per pole pitch is used for a high speed connection, a full-pitch winding is obtained for low speed connection. The method of connecting coils of a four pole motor is shown in Fig. 10.14 for one phase and also change over connections to obtain eight poles for the same machine with the same winding.

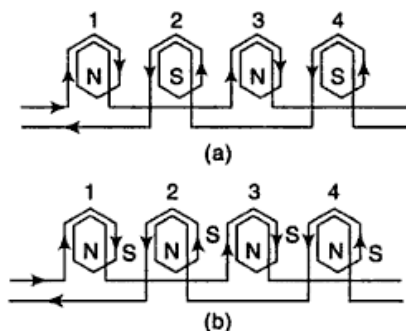


Fig. 10.14 Four-pole/eight-pole connections for one phase of induction motor

The methods of speed control by pole changing are suitable for squirrel cage motors only because, a cage rotor has as many poles induced in it as there are in the stator and can thus adopt when the number of stator poles changes.

By Line Voltage Control

The torque developed by an induction motor is proportional to square of voltage. If the applied voltage to the motor is reduced, the torque is reduced and the slip is increased. Therefore, this method of speed control is applicable over a limited range only. This method is sometimes used on small motors driving fans, whose torque requirement is proportional to square of speed.

10.17 REVERSAL OF ROTATION

The direction of rotation of a three-phase induction motor can be reversed by reversing the direction of the rotation of the magnetic field. This can be done by interchanging the connections of any two of the three wires of the three-phase

power supply. This causes the currents in the phases to interchange their relative timings in going positive and negative with the result that the magnetic field produces reversal in direction of rotation.

10.32 A cage motor has a starting current of 40 A when switched on directly. Auto-transformer with 45% tapping is used.

Determine (i) starting current and (ii) ratio of starting torque with auto-transformer to the starting torque with direct switching.

Solution

The ratio of transformation (x) is 0.45

$$(a) \therefore \text{Starting current with auto-transformer} = (0.45)^2 \times 40 = 8.1 \text{ A.}$$

$$(b) \frac{\text{Starting torque with auto-transformer}}{\text{Starting torque with direct starting}} = (0.45)^2 = 0.2025.$$

10.33 A three-phase, 10 kW, 6-pole, 50 Hz, 400 V of delta connected induction motor runs at 960 rpm on full load. If it draws 85 A on direct on line starting, calculate the ratio for the starting torque to full load torque with Y- Δ starter. Power factor and full load efficiency are 0.88 and 90% respectively.

Solution

Given: Output = 10 kW

No. of poles = 6

Frequency $f = 50$ Hz

$N = 900$ rpm

$\eta = 90\%$

Full load p.f. = 0.88.

Full-load line current drawn by a three-phase Δ -connected induction motor is given as

$$\begin{aligned} (I_{\phi}) &= \frac{\text{Output in watt}}{\sqrt{3} \cdot V_L \times \text{P.f.} \times \text{efficiency}} \\ &= \frac{10 \times 1000}{\sqrt{3} \times 400 \times 0.88 \times 0.9} = \frac{10000}{548.71} = 18.22 \text{ A} \end{aligned}$$

Now, full-load current per phase (Δ -connection)

$$I_{\phi} = \frac{18.22}{\sqrt{3}} = 10.52 \text{ A.}$$

On direct on line start the current I_{sc} drawn by the motor per phase is given as

$$I_{sc} = \frac{85}{\sqrt{3}} = 49.07 \text{ A}$$

$$\text{Synchronous speed } (N_s) = \frac{120 f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$\text{Full-load slip } (s) = \frac{N_s - N}{N_s} = \frac{1000 - 960}{1000} = 0.04$$

$$\therefore \frac{T_s}{T_{\phi}} = \frac{1}{3} \left(\frac{I_{sc}}{I_{\phi}} \right)^2 \times s_{\phi}$$

$$\therefore \text{Here } \frac{T_s}{T_{\phi}} = \frac{1}{3} \left(\frac{49.07}{10.52} \right)^2 \times 0.04 = 0.290.$$

Hence the starting current drawn by the motor is $\left[11.55 \times \frac{239.6}{200} \text{ A} \right]$, i.e., 13.83 A.

At full load condition the motor is delta connected.

Hence full load line current is $\frac{4000}{\sqrt{3} \times 415 \times 0.85 \times 0.8} = 8.184 \text{ A}$.

\therefore The ratio of starting to full load current $\frac{13.83}{8.184} = 1.689$.

10.39 The following are the parameters of the equivalent circuit of a 415 V, three-phase, 6-pole star connected induction motor:

Stator impedance = $(0.2 + j0.5) \Omega$

Magnetizing reactance = 25Ω

Core loss resistance = 150Ω .

Equivalent rotor impedance referred to the stator = $(0.3 + j0.7) \Omega$

Determine the stator current, rotor current, mechanical power output and input power at slip of 4% using the exact equivalent circuit.

Solution

The per phase exact equivalent circuit of the motor is shown in Fig. 10.15.

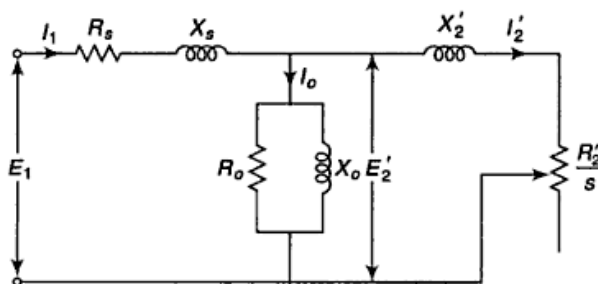


Fig. 10.15 Equivalent circuit of Ex. 10.39

Here, $R_s + jX_s = (0.2 + j0.5) \Omega$

$X_o = 25 \Omega$

$R_o = 150 \Omega$; $s = 0.04$

$\therefore \frac{R_2'}{s} + jX_2' = \frac{0.3}{0.04} + j0.7 = (7.5 + j0.7) \Omega$

The parallel combination of R_o and X_o gives

$$Z_o = \frac{R_o (jX_o)}{R_o + jX_o} = \frac{150(j25)}{150 + j25} = \frac{j150}{6 + j}$$

However, Z_o is in parallel with $\left[\frac{R_2'}{s} + jX_2' \right]$

Hence total input impedance is $Z = Z_s + \frac{Z_o \left[\frac{R_2'}{s} + jX_2' \right]}{Z_o + \left[\frac{R_2'}{s} + jX_2' \right]}$.

Per phase current $I_{s/c} = 115 \text{ A}$

Per phase power $W_{s/c} = \frac{9000}{3} \text{ W} = 3000 \text{ W}$

$$\therefore \text{Per phase impedance } Z_{s/c} = \frac{E_{s/c}}{I_{s/c}} = \frac{86.6}{115} \Omega = 0.753 \Omega$$

$$\text{Per phase resistance } R_{s/c} = \frac{W_{s/c}}{I_{s/c}^2} = \frac{3000}{(115)^2} \Omega = 0.2268 \Omega$$

$$\text{Per phase reactance } X_{s/c} = \sqrt{(0.753)^2 - (0.2268)^2} = 0.718 \Omega$$

Per phase rotor resistance referred to the stator,

$$R_2' = R_{s/c} - R_s = 0.2268 - 0.2 = 0.0268 \Omega.$$

We assume here that per phase stator reactance X_s = Per phase rotor reactance X_2'

$$\therefore X_1 = X_2' = \frac{X_{s/c}}{2} = \frac{0.718}{2} = 0.359 \Omega.$$

Voltage across the magnetizing branch is obtained from the formula $[E_0 - I_0(R_s + jX_s)]$. This gives the required voltage as $[254.03 - 25(0.2 + j0.359)] \text{ V}$.

i.e., $(249.03 - j8.975) \text{ V}$ or $(249.192 \angle -2.064^\circ) \text{ V}$

$$\therefore \text{Core loss resistance } R_C = \frac{249.192}{I_C} = \frac{249.192}{3.2804} \Omega = 75.963 \Omega.$$

$$\text{Magnetizing reactance } X_0 = \frac{249.192}{I_\phi} = \frac{249.192}{24.783} \Omega = 10.054 \Omega.$$

Hence the equivalent circuit parameters are

$$\begin{array}{lll} R_0 = 75.963 \Omega & X_0 = 10.054 \Omega & R_s = 0.2 \Omega \\ R_2' = 0.0268 \Omega & X_s = X_2' = 0.359 \Omega. & \end{array}$$

10.42 A 415 V, 50 Hz, 8-pole three-phase delta connected squirrel cage induction motor has a starting current of 30 A when connected directly to the supply. Find (i) the line and phase current drawn by the motor when connected directly on line, (ii) the line current when started by an auto-transformer with 70% tapping and (iii) the line current when started by a star-delta starter.

Solution

- (i) Line current when connected directly to the supply is 30 A.

As the motor is delta connected the phase current under direct online supply is

$$\frac{30}{\sqrt{3}} \text{ A} = 17.32 \text{ A}.$$

- (ii) At 70% auto-transformer tapping the applied line voltage is $415 \times 0.7 \text{ V} = 290.5 \text{ V}$.

As the motor is delta connected phase voltage is 290.5 V.

When phase voltage is 415 V, the phase current is 17.32 A.

When phase voltage is 290.5 V, the current supplied by the auto transformer is

$$\frac{17.32 \times 290.5}{415} = 12.124 \text{ A}.$$

Hence phase current of the motor = $0.7 \times 12.124 = 8.48 \text{ A}$.

Hence the line current when started by auto-transformer starter is $8.48 \times \sqrt{3} = 14.7 \text{ A}$.

- (iii) When the motor is started by a star delta starter, the motor is connected in star at the instant of starting. Hence, phase voltage of the motor during starting $\frac{415}{\sqrt{3}} \text{ V} =$

239.6 V. Phase current at phase voltage of 239.6 V is $17.32 \times \frac{239.6}{415} = 10 \text{ A}$.

\therefore Line current (= phase current) = 10 A, at start.

10.43 A 5 kW, 4-pole, three-phase star connected inductor motor has slipring rotor resistance of 0.05Ω and standstill reactance of 0.5Ω for phase. The full-load speed is 1450 rpm. Determine the ratio of maximum torque to the full-load torque, starting torque to the full-load torque and ratio of starting torque to the full-load torque.

Solution

$$N_s = \frac{120 f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$N = 1450 \text{ rpm (given)}$$

$$\therefore s_n(\text{full load slip}) = 1 - \frac{1450}{1500} = 0.033 (= s) \text{ (i.e., 3.3\%)}$$

$$s_{\max} (\text{slip at maximum torque}) = \frac{R_2}{X_2} = \frac{0.05}{0.5} = 0.1 \text{ (i.e., 10\%)}$$

$$\therefore \frac{T}{T_{\max}} = \frac{\text{Full load torque}}{\text{Maximum torque}} = \frac{2 \cdot s \cdot s_{\max}}{s^2 + s_{\max}^2}$$

$$\text{Here, } \frac{T}{T_{\max}} = \frac{2 \times 0.033 \times 0.1}{0.033^2 + 0.1^2} = \frac{0.0066}{0.011} = 0.595$$

$$\therefore \frac{T_{\max}}{T} = 1.68$$

$$\text{Also, } \frac{T_{\text{starting}}}{T_{\max}} = \frac{2 \cdot s_{\max}}{1 + s_{\max}^2} = \frac{2 \times 0.1}{1 + 0.1^2} = 0.198.$$

We have seen in the text that

$$T_s = \frac{KE_1^2 R_2}{R_2^2 + X_2^2}$$

$$\text{and } T = \frac{KE_1^2 \cdot s R_2}{R_2^2 + (s X_2)^2}$$

$$\begin{aligned} \therefore \frac{T_s}{T} &= \frac{KE_1^2 R_2}{R_2^2 + X_2^2} \times \frac{R_2^2 + (s X_2)^2}{KE_1^2 s R_2} \\ &= \frac{R_2^2 + (s X_2)^2}{(R_2^2 + X_2^2) s} = \frac{(0.05)^2 + (0.033 \times 0.5)^2}{0.033(0.05^2 + 0.5^2)} = \frac{0.0028}{0.00833} = 0.336 \end{aligned}$$

$$\text{i.e. } T_s/T = 0.336.$$

10.44 A 4 pole, 50 Hz, three-phase induction motor has a starting torque 17.8% of the full load torque and maximum torque 135% of the full load torque. Determine the full load speed and speed at maximum torque.

Solution

$$\frac{\text{Starting torque}}{\text{Full load torque}} = \frac{T_s}{T} = \frac{17.8}{100} = 0.178.$$

$$\frac{\text{Maximum torque}}{\text{Full load torque}} = \frac{T_{\max}}{T} = \frac{135}{100} = 1.35.$$

Hence,
$$\frac{T_s}{T_{\max}} = \frac{0.178}{1.35} = 0.1318.$$

Now, at slip s if the torque be T , then we have $\frac{T}{T_m} = \frac{2}{\frac{s}{s_{\max}} + \frac{s_{\max}}{s}}$ where s_m is the slip

at maximum torque.

$$\left[\because \text{From equation 10.18(c), we have } \frac{T}{T_m} = \frac{2 \cdot s \cdot s_{\max}}{s^2 + s_{\max}^2} = \frac{2}{\frac{s}{s_{\max}} + \frac{s_{\max}}{s}} \right]$$

At starting $s = 1$, hence, from the above relations we can write,

$$\frac{T_{st}}{T_m} = \frac{2}{\frac{1}{s_m} + \frac{s_m}{1}} = 0.1318$$

or $0.1318 s_{\max}^2 - 2s_{\max} + 0.1318 = 0$

or $s_{\max} = 0.066.$

$$\text{Synchronous speed } (N_s) = \frac{120 \times 50}{4} = 1500 \text{ rpm.}$$

If N_1 be the speed at maximum torque

then $N_1 = (1 - s_{\max})N_s = (1 - 0.066) 1500 = 1401 \text{ rpm.}$

$$\therefore \frac{T}{T_{\max}} = \frac{2}{\frac{s_{fl}}{s_m} + \frac{s_m}{s_{fl}}}$$

Here,
$$\frac{1}{1.35} = \frac{2}{\frac{s_{fl}}{0.066} + \frac{0.066}{s_{fl}}}$$

or
$$\frac{1}{1.35} = \frac{2 \times s_{fl} \times 0.066}{s_{fl}^2 + 0.004356}$$

or $s_{fl}^2 - 0.1782 s_{fl} + 0.004356 = 0$

$\therefore s_{fl} = 0.029.$

Hence full load speed is $[(1 - 0.029) 1500]$ or, 1456.5 rpm.

.....

10.45 An 8-pole, 50 Hz, three-phase induction motor has a full-load torque of 200 Nm when the frequency of the rotor emf is 2.5 Hz. If the mechanical loss is 15 Nm determine the rotor copper loss and the efficiency of the motor. The total stator loss is 1000 W.

10.48 A three-phase squirrel cage induction motor has a full-load torque one third of the maximum torque. The rotor resistance and reactance are 0.25 and 3Ω respectively. Determine the ratio of starting torque to full load torque when it is started by (i) direct on line starter (ii) auto-transformer starter with 60% tapping and (iii) star delta starter.

Solution

Given: $\frac{T}{T_{\max}} = \frac{1}{3}, \therefore T_{\max} = 3T$

Slip at maximum torque $s_{\max} = \frac{R_2}{X_2} = \frac{0.25}{3} = 0.083$

Also, $\frac{T}{T_{\max}} = \frac{2s \cdot s_{\max}}{s^2 + s_{\max}^2} = \frac{2}{\frac{s}{s_{\max}} + \frac{s_{\max}}{s}}$, where s is the slip.

At any load if T_{st} be the torque at starting then

$$\frac{T_{st}}{T_{\max}} = \frac{2}{\frac{1}{s_m} + \frac{s_m}{1}} = \frac{2}{0.083 + 0.083}$$

or $T_{st} = 0.16486 T_{\max}$.

(i) During direct on line starting

$$T_{st} = 0.16486 \times 3T = 0.49458 T \quad [\because T_{\max} = 3T].$$

(ii) During auto-transformer starting with 60% tapping $T_{st} = x^2 \cdot T_{st}$ (for direct on line)

i.e. $T_{st} = (0.49458) (0.6)^2 T$

or $T_{st} = 0.178 T$.

(iii) During starting by a star delta starter

$$T_{st} = \frac{1}{3} \times T_{st} \text{ (for direct for line)}$$

i.e., $T_{st} = \frac{1}{3} \times 0.49458 T = 0.165 T$.

10.49 A 6-pole, three-phase induction motor develops 35 HP including 3 HP mechanical losses at a speed of 960 rpm when connected to 440 V, 3-phase mains. The power factor is 0.8. Find (i) the slip (ii) the rotor copper loss (iii) the total input if stator loss is 3 kW and (iv) the efficiency.

Solution

Synchronous speed $N_s = \frac{120 \times 50}{6} = 1000 \text{ rpm}$

Speed of the motor $N = 960 \text{ rpm}$

(i) Slip $= \left(1 - \frac{960}{1000}\right) = 0.04$.

(ii) Gross mechanical power developed is $35 \times 735.5 \text{ W} = 25742.5 \text{ W}$.
or $P_m = 25742.5 \text{ W} = 25.742 \text{ kW}$.

$$\therefore \text{Air gap power } (P_{ag}) = \frac{P_m}{1-s} = \frac{25.742}{1-0.04} = 26.81 \text{ kW}.$$

Hence, rotor copper loss is sP_g , i.e., 0.04×26.81 or 1.072 kW .

(iii) Stator loss 3 kW (given).

Hence, total input $= 26.81 + 3 = 29.81 \text{ kW}$.

- (iv) \therefore Input = 29.81 kW and
 Output = $(35 - 3) = 32$ HP = 32×0.7355 kW = 23.536 kW,
 Hence, efficiency is $\frac{23.536}{29.81} \times 100\% = 78.95\%$.

10.50 A 15 kW, 4-pole, 50 Hz, three-phase induction motor has a mechanical loss 2% of the output. For a full load slip of 3% determine the rotor copper loss and air gap power.

Solution

$$\text{Output} = 15 \text{ kW}$$

$$\text{Mechanical loss} = \frac{2}{100} \times 15 = 0.3 \text{ kW}$$

$$\text{Slip} = 0.03$$

Power developed by the rotor is $P_m = 15 - 0.3 = 14.7$ kW

If P_g be the air gap power then $(1 - s)P_g = P_m$

$$\text{or } P_g = \frac{14.7}{1 - 0.03} \text{ kW} = 15.15 \text{ kW}$$

Rotor copper loss $sP_g = 0.03 \times 15.15 = 0.4545$ kW.

10.51 A 10 kW, 440 V, three-phase star connected, 50 Hz, 8-pole squirrel cage induction motor has the following per phase constants referred to the stator.

$$R_1 = 0.2 \Omega, X_1 = 1 \Omega, R_2 = 0.18 \Omega, X_2 = 1.5 \Omega, X_0 = 30 \Omega$$

The constant loss is 500 W and the slip is 5%.

Determine the stator current, output torque and efficiency.

Solution

The equivalent circuit of the induction motor is shown in Fig. 10.16,

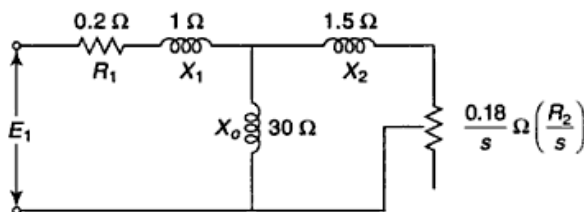


Fig. 10.16 Equivalent circuit of Ex. 10.51

$$\text{The per phase applied stator voltage } E_1 = \frac{440}{\sqrt{3}} \text{ V} = 254 \text{ V}$$

$$\text{Slip } s = 0.05 \text{ (given)}$$

$$\begin{aligned} \text{The total impedance from input} &= (0.2 + j1) + \frac{j30 \left(\frac{0.18}{0.05} + j1.5 \right)}{j30 + \frac{0.18}{0.05} + j1.5} \Omega \\ &= 0.2 + j + \frac{-45 + j108}{3.6 + j31.5} \Omega \\ &= 0.2 + j + \frac{117 \angle 112.62^\circ}{31.7 \angle 83.48^\circ} \Omega \\ &= 0.2 + j + 3.69 \angle 29.14^\circ \Omega \\ &= 1.073 + j1.487 + 1.834 \angle 54.186^\circ \Omega. \end{aligned}$$

$$\therefore \text{Stator current } I_1 = \frac{254}{1.834 \angle 54.186^\circ} = 138.49 \angle -54.186^\circ.$$

$$\begin{aligned} \text{Stator input power} &= \sqrt{3} E_L I_L \cos 54.186^\circ \\ &= \sqrt{3} \times 440 \times 138.49 \cos 54.186^\circ = 61.757 \text{ kW} \end{aligned}$$

$$\text{Air gap power } P_{ag} = 61.757 - \frac{3(138.49)^2 \times 0.2}{1000} = 50.25 \text{ kW} \quad [\therefore P_{ag} = \text{stator input power} - \text{stator copper loss, core loss being neglected in stator.}]$$

Mechanical power developed

$$P_m = (1 - s) P_g = (1 - 0.05) 50.25 = 47.737 \text{ kW.}$$

$$\text{Power output } P_{out} = \left(47.737 - \frac{500}{10^3} \right) = 47.237 \text{ kW.}$$

$$\text{Output torque } T_{out} = \frac{47.237 \times 10^3}{\frac{2\pi \times N}{60}} \text{ Nm, [where } N \text{ (rpm) is the speed of the motor,}$$

$$T_{out} = \frac{P_{out}}{\omega_s}, \omega_s = 2\pi n_s, n_s = \frac{N}{60} \text{ rpm; } N = (1 - 0.05) \times \frac{120 \times 50}{8} = 712.5 \text{ rpm.}]$$

$$\text{Hence output torque} = \frac{47.237 \times 10^3 \times 60}{2\pi \times 712.5} = 633.40 \text{ Nm}$$

$$\text{Efficiency} = \frac{\text{Power output}}{\text{Power input}} = \frac{47.237}{61.757} \times 100\% = 76.48\%.$$

10.52 A three-phase, 15 kW, 440 V, 50 Hz, 6-pole squirrel cage induction motor has a delta connected stator winding. The motor during blocked rotor test yields the following results: 240 V, 25 A, 7 kW.

The dc resistance measured between any two stator terminals is 1 Ω . If the stator core loss at rated voltage is 400 W determine the starting torque when rated voltage is applied.

Solution

If the stator winding resistance per phase is " r " then the resistance between any two terminals (see Fig. 10.17) is

$$\frac{r(r+r)}{r+(r+r)} = 1$$

$$\text{or } \frac{2r^2}{3r} = 1$$

$$\text{or } r = \frac{3}{2} \Omega = 1.5 \Omega$$

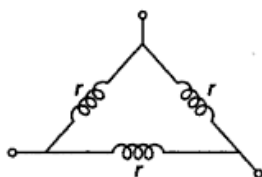


Fig. 10.17 Stator winding (Δ)

At the rated voltage, power input during the blocked rotor test will be $7 \times \left(\frac{440}{240} \right)^2 \text{ kW}$, i.e., 23.52 kW. At rated voltage, stator current during blocked rotor test will be $\left(25 \times \frac{440}{240} \right)$

or 45.83 A. Thus at rated voltage the stator copper loss will be $\left[3 \times \left(\frac{45.83}{\sqrt{3}} \right)^2 \times 1.5 \right]$ or,

3150.768 W.

$$\text{Air gap power } P_{ag} = \text{Power input} - (\text{Stator copper loss} + \text{Stator Core loss}) \\ = (23520 - 3150.768 - 400) = 19.969 \text{ kW}$$

$$\text{Synchronous speed } N_s = \frac{120 f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$\text{Hence starting torque when rated voltage is applied } \frac{P_{ag}}{\omega_s} = \frac{19969}{\frac{2\pi \times 1000}{60}} \text{ Nm} = 190.79 \text{ Nm.}$$

$$\left[\because \omega_s = 2\pi n_s = 2\pi \cdot \frac{N_s}{60}, N_s \text{ being expressed in rpm} \right]$$

.....

10.53 A three-phase squirrel cage induction motor gives a blocked rotor test current of 200% of the rated current when 30% of the rated voltage is applied. The starting torque is 30% of the rated torque. The motor when started by an auto-transformer limits the starting line current to 160% of the rated current. Determine the percentage starting torque with auto-transformer starting.

Solution

At 30% of rated voltage blocked rotor current is 200% (given)

At rated voltage blocked rotor current is

$$I_{sc} = \frac{2}{0.3} \cdot I_n = 6.67 I_n, \text{ where } I_n \text{ is the full load current.}$$

Now, if x be the fraction of the voltage applied to the stator during auto-transformer starting then per phase starting current would be

$$I_{st} = x^2 I_{sc}$$

$$\text{Here, } I_{st} = x^2 (6.67 I_n) \quad (i)$$

$$\text{Again it is given that } (I_{st}) = 1.6 I_n \quad (ii)$$

From the equations (i) and (ii)

$$x^2 = \frac{1.6}{6.67} = 0.23988.$$

$$\text{Also, } T \propto \text{voltage}^2,$$

here, $0.3 T_n \propto (0.3V)^2$, where V is the rated voltage, T_n is the full load torque T .

$$\text{i.e. } V^2 \propto \frac{0.3}{0.09} \cdot T_n.$$

From the text we know that

$$\frac{\text{Starting torque with auto-transformer starting}}{\text{Starting torque with direct on line starting}} = x^2.$$

Hence starting torque with auto-transformer starting is,

$$x^2 \times \frac{0.3}{0.09} T_n = (0.23988)^2 \times \frac{0.3}{0.09} \cdot T_n = 0.1918 T_n$$

i.e., starting torque with auto-transformer starting is 19.18% of the full-load torque.

.....

10.54 The rotor resistance of an 8-pole, 50 Hz. wound rotor induction motor has a resistance of 0.5Ω per phase. The speed of the rotor is 720 rpm at full load.

Determine the external resistance to be connected with the rotor circuit to reduce the speed to 680 rpm for full-load torque.

Solution

$$\text{Synchronous speed } N_s = \frac{120 f}{P} = \frac{120 \times 50}{8} = 750 \text{ rpm.}$$

$$\text{Slip } (s) = \left[1 - \frac{720}{750} \right] = 0.04$$

If R_2 be the rotor resistance then the rotor copper loss is $I_2^2 R_2$, where I_2 is the rotor current. If P_{ag} be the air gap power or power input to the rotor then

$$sP_{ag} = I_2^2 R_2$$

$$\text{or} \quad 0.04 = \frac{I_2^2 R_2}{P_{ag}} = \frac{0.5 I_2^2}{P_{ag}} \quad (i)$$

The new speed $N = 680$ rpm.

$$\therefore s = \left(1 - \frac{680}{750} \right) = 0.093$$

Let R be the total resistance of the rotor circuit.

In order that the full load torque remains same P_{ag} should have the same value as the previous one.

$$\text{Hence,} \quad 0.093 = \frac{I_2^2 R}{P_{ag}} \quad (ii)$$

From equations (i) and (ii)

$$0.093 = \frac{0.04}{0.5} \cdot R$$

$$\text{or} \quad R = 1.1625 \, \Omega$$

Hence the external resistance to be connected is $(R - R_2)$ or $(1.1625 - 0.5)$, i.e., $0.6225 \, \Omega$ per phase.

10.55 A three-phase induction motor has a starting torque 150% of full load torque and maximum torque 200% of full load torque. Determine the slip at maximum torque, full load slip and rotor starting current as a percentage of full load current.

Solution

We know that in any slip s the developed torque can be expressed in terms of maximum torque, i.e.,

$$\frac{T}{T_{\max}} = \frac{2}{\frac{s}{s_{\max}} + \frac{s_{\max}}{s}}$$

where T_{\max} is the maximum torque at slip s_{\max} .

$$\text{Now,} \quad \frac{\text{Starting torque } (T_s)}{\text{Full load torque } (T)} = 1.5 \quad (\text{given})$$

$$\text{as well as} \quad \frac{T_{\max}}{T} = 2 \quad (\text{given})$$

$$\text{Hence,} \quad \frac{T_s}{T_{\max}} = \frac{1.5}{2.0} = \frac{3}{4} = \frac{2}{\frac{1}{s_{\max}} + s_{\max}}$$

During starting slip is 1.

$$\therefore \left(\frac{1}{s_{\max}} + s_{\max} \right) = \frac{8}{3} = 2.67.$$

$$\begin{aligned} \text{or} \quad s_{\max}^2 - 2.67 s_{\max} + 1 &= 0 \\ \text{or} \quad s_{\max} &= \frac{2.67 \pm \sqrt{(2.67)^2 - 4}}{2} \\ &= 0.45 \text{ (the other value is rejected as it is greater than 1)} \end{aligned}$$

$$\text{Also,} \quad \frac{T}{T_{\max}} = \frac{2}{\frac{s_{\text{fl}}}{s_{\max}} + \frac{s_{\max}}{s_{\text{fl}}}} = \frac{2}{\frac{s_{\text{fl}}}{0.45} + \frac{0.45}{s_{\text{fl}}}} = \frac{1}{2}$$

$$\text{or} \quad s_{\text{fl}}^2 - 4 \times 0.45 \cdot s_{\text{fl}} + (0.45)^2 = 0$$

$$\text{or} \quad s_{\text{fl}}^2 - 1.8 s_{\text{fl}} + 0.2025 = 0$$

$$\text{or} \quad s_{\text{fl}} = \frac{1.8 \pm \sqrt{(1.8)^2 - 4(0.2025)}}{2} = 0.12.$$

At full-load rotor current may be obtained as

$$I_{2\text{fl}} = \frac{E}{\frac{R_2}{s_{\text{fl}}} + jX_2}$$

[refer approximate equivalent circuit neglecting the magnetising branch and stator impedance]

$$\text{or} \quad I_{2\text{fl}}^2 = \frac{E^2}{\left(\frac{R_2}{s_{\text{fl}}}\right)^2 + X_2^2}$$

Similarly, starting current

$$I_{2\text{st}}^2 = \frac{E^2}{R_2^2 + X_2^2}$$

$$\text{Hence} \quad \left(\frac{I_{2\text{fl}}}{I_{2\text{st}}}\right)^2 = \frac{R_2^2 + X_2^2}{\left(\frac{R_2}{0.12}\right)^2 + X_2^2}$$

$$\text{Now,} \quad s_{\max} = \frac{R_2}{X_2} = 0.45$$

$$\text{Hence} \quad \left(\frac{I_{2\text{fl}}}{I_{2\text{st}}}\right)^2 = \frac{\left(\frac{R_2}{X_2}\right)^2 + 1}{\left(\frac{R_2}{0.12 X_2}\right)^2 + 1} = \frac{(0.45)^2 + 1}{\left(\frac{0.45}{0.12}\right)^2 + 1} = 0.0798$$

$$\text{Hence} \quad \frac{I_{2\text{fl}}}{I_{2\text{st}}} = \sqrt{0.0798} = 0.28$$

$$\text{or} \quad \frac{I_{2\text{st}}}{I_{2\text{fl}}} = 3.54.$$

.....

18. A 6-pole, 60 Hz induction motor rotates at 3% slip. Find the speed of the stator field, the rotor and the rotor field. What is the frequency of the rotor currents? [Ans: 1200 rpm, 1164 rpm, 1200 rpm, 1.8 Hz]

$$[\text{Hint: } N_s = \frac{120 \times 60}{6} = 1200 \text{ rpm.}]$$

∴ Stator field rotates at 1200 rpm. Rotor field rotates in the air gap in the same speed.

$$N(\text{rotor speed}) = N_s(1 - s) = 1200(1 - 0.03) = 1164 \text{ rpm}$$

The rotor speed is then 1164 rpm.

If frequency of rotor current is f_r ,

$$f_r = sf_s = 0.03 \times 60 = 1.8 \text{ Hz.}$$

Since rotor rotates at 1164 rpm while the speed of the rotor field is 1200 rpm, hence the field speed with respect to the rotor is ($N_s - N$) i.e., 36 rpm].

19. A three-phase 8-pole squirrel cage induction motor, connected to a 400 V ($L-L$) 50 Hz supply, rotates at 3% slip at full load. The copper and iron losses at the stator are 2 kW and 0.5 kW respectively. If the motor takes 50 kW at full load, find the full load developed torque at the rotor.

[Ans: 605 Nm]

$$[\text{Hint: } P_{ag} = P_{in} - P_{scu} - P_{sc} \\ = 50 - 2 - 0.5 = 47.5 \text{ kW}]$$

$$\therefore T = \frac{P_{ag}}{\omega_s} = \frac{47.5 \times 10^3}{2\pi \times \frac{120 \times 50}{8 \times 60}} = 605 \text{ Nm.}]$$

20. The power input to a three-phase induction motor is 50 kW. Stator loss is 1 kW. Find the gross mechanical power developed in the rotor and the rotor copper loss per phase when the motor has a full load slip of 4%.

$$[\text{Hint: } P_{in} = 50 \text{ kW}; s = 0.04; P_{scu} = 1 \text{ kW.}]$$

$$\therefore P_{ag} = P_{in} - P_{scu} = 49 \text{ kW}$$

$$P_{rcu} = s \times P_{ag} = 0.04 \times 49 = 1.96 \text{ kW} \left(= \frac{1.96}{3} \text{ kW per phase} \right)$$

$$\therefore P_m = P_{ag} - P_{rcu} = \left(\frac{49}{3} \right) - \frac{1.96}{3} = 15.68 \text{ kW.}]$$

21. The loss at the stator of a three-phase squirrel cage 25 HP, 1500 rpm induction motor is 2 kW. What is rotor mechanical power if the rotor copper loss is 1 kW? What is the running slip? [Ans: 15.65 kW; 6%]

$$[\text{Hint: } P_{in} = 25 \times 746 \times 10^{-3} = 18.65 \text{ kW}]$$

$$\therefore P_{ag} = 18.65 - 2 = 16.65 \text{ kW}$$

$$P_m = P_{ag} - P_{rcu} = 16.65 - 1 = 15.65 \text{ kW.}]$$

$$\therefore P_{rcu} = s \times P_{ag}; s = \frac{P_{rcu}}{P_{ag}} = \frac{1000}{16650} = 0.06 \text{ i.e., slip is 6\%.}]$$

22. The rotor of a 6-pole, 50 Hz, slip ring induction motor has a resistance of 0.3 Ω /phase and it runs at 960 rpm at full load. How much external resistance/phase must be added to the rotor circuit to reduce the speed to 800 rpm, the torque remaining constant? [Ans: 1.2 Ω]

[Hint: $N_s = \frac{120 f}{P} = 1000 \text{ rpm}$

$$s_{fl} (\text{full load slip}) = \frac{1000 - 960}{1000} = 0.04.$$

If r be the additional resistance per phase in rotor circuit, we can write

$$\frac{s_{new}}{s_{fl}} = \frac{R_2 + r}{R_2}.$$

Since the power input to the rotor and rotor current remain constant for constant torque and hence from the relation, $\text{slip} = \frac{\text{Rotor Cu loss}}{\text{Rotor input}}$, we have

$$\frac{s_{new}}{s_{fl}} = \frac{3I_2^2(R_2 + r)}{3I_2^2 R_2} = \frac{R_2 + r}{R_2}.$$

Substitution of the values of $s_{fl} = 0.04$,

$$s_{new} = \frac{1000 - 800}{1000} = 0.2 \text{ and } R_2 = 0.3, \text{ yields } r = 1.2 \Omega.]$$

23. A three-phase, 50 Hz induction motor has an output rating of 500 HP, 3.3 kV ($L-L$). Calculate the approximate full-load current at 0.85 p.f., locked rotor current and no-load current. What is the apparent power drawn under locked rotor condition? Assume the starting current to be 6 times full load current and no load current to be 30% of full load current.

[Ans: $I_{fl} = 76.78 \text{ A}$; $I_{no \text{ load}} = 23.093 \text{ A}$; $I_{\text{lock rotor}} = 460.68 \text{ A}$;
 $P_{\text{locked rotor}} = 2633 \text{ KVA}$]

[Hint: $I_{fl} = \frac{500 \times 746}{\sqrt{3} \times 3300 \times 0.85} = 76.78 \text{ A}$

$$\therefore I_{no \text{ load}} = 0.3 \times 76.78 = 23.03 \text{ A}$$

$$\because I_{\text{lock rotor}} \equiv I_{\text{start}}$$

$$\text{Hence } I_{\text{start}} = 6 \times I_{fl} = 460.68 \text{ A.}$$

Apparent power drawn during locked rotor condition is

$$P_A = \sqrt{3} \times V_L \times I_{st} = \sqrt{3} \times 3300 \times 460.68 = 2633 \text{ KVA.}]$$

24. A 4-pole, 60 Hz, 460 V, 5HP induction motor has the following equivalent circuit parameters:

$$R_s = 1.21 \Omega; \quad X_s = 3.10 \Omega$$

$$R_2' = 0.742 \Omega; \quad X_2' = 2.41 \Omega$$

$$X_0 = 65.6 \Omega$$

Find the starting and no-load current of the machine.

[Ans: $46.15 \angle -70.67^\circ \text{ A}$; $3.87 \angle -89^\circ \text{ A}$]

[Hint: With reference to the equivalent circuit of the induction motor, the input impedance looking from the input side is

$$\begin{aligned} Z_{in} &= (R_s + jX_s) + \frac{jX_0 (R_2' + jX_2')}{R_2' + jX_2' + jX_0} \\ &= \left[(1.21 + j3.1) + \frac{j65.6(0.742 + j2.41)}{0.742 + j2.41 + j65.6} \right] \Omega = 5.75 \angle 70.72^\circ \Omega. \end{aligned}$$

At start $s = 1.0$. This means the load resistor in equivalent circuit is, shorted, since $1 - s = 0$.

$$\therefore I_{st} = \frac{V_{L-L}}{\sqrt{3} Z_{in}} = 46.15 \angle -70.67^\circ \text{ A.}$$

At no load, $s = 0$, i.e., the load element in the equivalent circuit is open.

$$\therefore Z_{in} \text{ (no load)} = (R_s + jX_s) + jX_0 = (1.21 + j68.7) \Omega = 68.71 \angle 89^\circ \Omega$$

$$\therefore I_{NL} = \frac{V_{L-L}}{\sqrt{3} Z_{in(NL)}} = \frac{460 \angle 0^\circ}{\sqrt{3} (68.71 \angle 89^\circ)} = 3.87 \angle -89^\circ \text{ A.}$$

25. A 30 HP, 3-phase 6 pole, 50 Hz slip ring induction motor runs at full load at a speed of 960 rpm. The rotor current is 30 A. If the mechanical loss in the rotor is 1 kW while 200 W loss is being incurred by the rotor short circuiting system, find the rotor resistance per phase. [Ans: $R_2 = 0.287 \Omega$]

$$[\text{Hint: } N_s = 100 \text{ rpm; } s = \frac{N_s - N}{N_s} = 0.04]$$

\therefore Rotor Cu loss = $\frac{s}{1-s} \times$ gross mech power developed in rotor Hence we can write for this problem,

$$3I_2^2 R_2 + 200 = \frac{0.04}{1-0.04} (30 \times 746 + 1000)$$

$$\text{or, } 3 \times 30^2 \times R_2 = 774.17$$

$$\text{or, } R_2 = 0.287 \Omega$$

26. A 10 HP, 400 V(L-L), 50 Hz, 3-phase induction motor has a full load p.f. of 0.8 and efficiency of 0.9. The motor draws 7 A when a voltage of 160 V is applied directly across the live terminals, the motor being standstill. Determine the ratio of starting to full load current when a star-delta starter is used to start the motor. [Ans: $(I_{st}/I_{fl}) = 0.39$]

$$[\text{Hint: } I_{fl} = \frac{10 \times 746}{\sqrt{3} \times 400 \times 0.8 \times 0.9} = 15 \text{ A.}]$$

$$I_{sc} \text{ at 160 V input} = 7.0 \text{ A}$$

$$\therefore I_{scf} \text{ at 400 V(L-L) is } \frac{400}{160} \times 7.0 = 17.5 \text{ A.}$$

With star delta starter,

$$I_{\text{starting}} = \frac{1}{3} \times I_{scf} = \frac{1}{3} \times 17.5 = 5.833 \text{ A.}$$

$$\therefore \frac{I_{\text{starting}}}{I_{fl}} = \frac{5.833}{15} = 0.39.]$$

27. A 75 kW, three-phase induction motor has 1500 rpm synchronous speed. It is connected across a 440 V(L-L) supply and rotates at 1440 rpm at full load. The two wattmeter method is applied to measure the power input which shows that the motor absorbs 70 kW while the line current is 80 A. If the stator iron loss is 2 kW and rotor mechanical loss is 1.5 kW, find

$$\text{i.e.} \quad I_{st/ph} = \frac{1}{\sqrt{3}} \times \frac{6}{\sqrt{3}} \times I_{fl}$$

$$\therefore \quad \frac{I_{st}}{I_{fl}} = \frac{1}{\sqrt{3}} \times \frac{6}{\sqrt{3}} = 2$$

$$\text{Hence,} \quad \frac{T_s}{T_{fl}} = (2)^2 \times 0.05 = 0.2.$$

(ii) Auto-transformer starting with 60% tapping:

At start, stator winding remain in delta connection. However, only 60% voltage is made available at stator.

$$\therefore \quad I_s = \frac{60}{100} \times 6 I_{fl} = 3.6 I_{fl}$$

$$\text{Hence} \quad \frac{T_s}{T_{fl}} = (3.6)^2 \times 0.05 = 0.648.]$$



SYNCHRONOUS MACHINES

11.1 INTRODUCTION

A synchronous generator (or alternator) is the most commonly used machine for generation of electrical power. It generates alternating voltage which is stepped up and transmitted. A synchronous generator, like other electrical rotating machines, has two main components viz. the *stator* and the *rotor*. The component of the machine (the winding or the core) in which the alternating voltage is induced is called the *armature*. The armature winding is placed on the stator slots in the stator core. The rotor consists of the field poles which produce the magnetic lines of force. The poles are excited with dc supply (or may be permanent magnets in small alternator).

A synchronous machine works as an alternator when the rotor is rotated by a primemover. The same machine works as a synchronous motor, when a three-phase ac supply is applied to the armature winding, the field being excited by dc supply in both the cases.

The construction of a synchronous generator depends upon the type of primemover used to rotate the rotor. The types of primemovers are:

- (a) In thermal or nuclear power stations, steam turbines are used to rotate at a high speed (3000 rpm for a two pole 50 Hz. machine or 3600 rpm for a two pole 60 Hz. machine) as at high speeds the efficiency of steam turbine is comparatively higher.
- (b) For hydroelectric power stations hydraulic turbines of different types are used depending upon the water head available in that station.
- (c) In diesel stations, lower rating alternators are used with diesel engines as primemover at low speed.
- (d) In captive power plants, high speed gas turbines are employed as primemovers to rotate medium capacity alternators.

11.2 OPERATING PRINCIPLE

A synchronous generator essentially consists of two parts:

1. Field magnet system (rotor)
2. Armature (stator)

A 3-phase distributed winding is placed on the stator in slots of a synchronous generator to act as an armature. This machine works on the principle of electro-magnetic induction (Faraday's law). When there is a cutting of field flux by a conductor or when there is a change of flux linkage in a coil, emf is induced in the conductor.

The field magnet system is usually excited from a separate dc source of 110/125 or 250 V supply. In conventional generators it is provided by a dc shunt or compound generator called an *exciter*, mounted on the shaft of the alternator itself. The field system (also known as rotor) is rotated within the armature (stator). The exciting current is supplied to the alternator rotor through a slip ring and brushes in conventional alternators. In modern alternators *brushless excitation* and *static exciters* are also employed.

11.3 TYPES OF ROTORS

From the construction point of view there are two types of rotors:

- (a) Salient pole type
- (b) Cylindrical (or non-salient) rotor type.

11.3.1 Salient Pole Type

This type of rotor has a large number of projecting (salient) poles having their cores bolted on to a heavy magnetic core of cast iron or CRGO steel of good magnetic quality.

Alternators with salient pole rotors have the following features:

- (a) Salient pole machines are larger in diameter but smaller in axial length.
- (b) The pole shoes are wide and usually cover (2/3) pole-pitch.
- (c) Poles of these rotors are laminated in order to reduce eddy current loss.
- (d) These machines are suitable for medium speed (i.e. 120 to 500 rpm)

11.3.2 Cylindrical (or Non-salient) Type Rotor

A cylindrical rotor consists of a smooth solid forged steel cylinder having a number of slots for accommodating field coils. Such type of rotors are generally designed for 2-pole turbo-generators running at 3000 rpm (or 3600 rpm).

The salient features of non-salient type of alternators are:

- (a) They are smaller in diameter and larger in axial length.
- (b) Usually the number of poles on the rotor is two.
- (c) Windage loss is less.
- (d) Mechanically they are more balanced.
- (e) These machines are suitable for speeds from 1000 to 3000 rpm.

11.4 STATOR

Constructionally the stator for both types of alternators is identical. The stator is made of laminations of special magnetic iron or steel alloy and can accommodate armature conductors. The whole structure is fitted in a frame. The frame may be of cast iron or welded steel plate. The laminations in the stator are insulated from each other with paper or varnish depending upon the size of the machine. The stampings also have openings which make axial and radial ventilating ducts to provide efficient cooling.

Slots provided on the stator core are mainly of two types (a) Open type and (b) Semi-closed type. Open type slots are commonly used because the coils can be formed, wound and insulated prior to being placed in the slots. These slots also provide facility in removal and replacement maintenance of defective coil. However, these type of slots have the disadvantage of distributing the air gap flux into branches which tends to produce ripples in the emf wave. The semi-closed type slots are better in this respect but do not permit the use of pre-wound coils and lacks in ventilation as well as poses difficulty in maintenance.

11.5 FIELD AND ARMATURE CONFIGURATIONS

There are two arrangements of fields and armatures:

- (a) Revolving armature and stationary field.
- (b) Revolving field and stationary armature.

11.6 ADVANTAGES OF ROTATING FIELD

In large alternators, rotating field arrangement is usually forward due to the following advantages.

- (a) **Ease of Construction** Armature winding of large alternators being complex, the connection and bracing of the armature windings can be easily made for the stationary stator.
- (b) **Number of Slip Rings** If the armature be made rotating, the number of slip rings required for power transfer from armature to external circuit is atleast three. Also, heavy current flows through brush and slip rings cause problems and require more maintenance in large alternators. Insulation required for slip rings from rotating shaft is difficult with the rotating armature system.
- (c) **Better Insulation to Armature** Insulation arrangement of armature windings can easily be made from core on stator.
- (d) **Reduced Rotor Weight and Rotor Inertia** The field system being placed on rotor, insulation requirement is less (for low dc voltage). Also rotational inertia is less. It takes lesser time to gain full speed.
- (e) **Improved Ventilation Arrangement** The cooling can be provided by enlarging the stator core with radial ducts. Water cooling is much easier if the armature is housed in the stator.

Hence in almost all of the alternators the armature is housed in the stator while the dc field system is placed in the rotor.

11.7 EXPRESSION OF FREQUENCY

The rotor being rotated at a steady speed by means of a primemover, the magnetic field of the rotors will also rotate to cut the stationary armature conductors. This will change the flux linkage in the stator conductors and induce an alternating emf in stator conductors. The direction of induced emf is given by "Fleming's right hand rule". One cycle of emf will induce in a conductor when one pair of poles passes over it (or when the angular distance travelled by the armature is twice the pole pitch).

Let P = Number of magnetic poles
 N = Rotating speed of rotor in rpm.
 f = Frequency of generated emf in Hz.
 \therefore Number of cycles/revolution = $P/2$ and
 number of revolution per second = $N/60$

\therefore Frequency $f = \frac{N}{60} \times \frac{P}{2} = \frac{PN}{120}$ Hz.

[For 3000 rpm two-pole alternators, thus f becomes 50 Hz. while for 3600 rpm, two-pole alternators, f is 60 Hz.]

11.8 DISTRIBUTED ARMATURE WINDING

The armature consists of the distributed winding.

In the distributed winding, the conductors of the coil are placed in several armature slots under one pole. The induced emf per phase in the distributed winding is to some extent less than the case when winding in such a way that the number of slots is equal to the number of poles.

There are some specific advantages for the distributed winding.

- (a) Voltage waveform is improved and wave form is more sinusoidal in nature.
- (b) Distorting harmonics are eliminated.
- (c) Distributed winding is helpful in reducing armature reaction and armature reactance too.
- (d) Heat dissipation is better.
- (e) The core is better utilised.
- (f) It is suitable for higher current density due to even distribution of copper.

11.9 SHORT-PITCH ARMATURE WINDING

In short-pitch windings, two coil sides (forming a coil) are not exactly 180° electrically apart; the emf induced in the two sides are thus not in phase and the resultant of induced emf in the coil is less than the arithmetic sum of the emf induced in the coil sides of the full-pitched winding.

This winding is advantageous as the voltage waveform is improved and distorting harmonic emf is further reduced thus making the output wave more sinusoidal. Also, copper is saved in the coil ends. The inductance of the armature winding is reduced due to lesser length of coil.

Number of conductors (or coil sides) in series/phase ($= Z$)
 $= 2T$ (T is the number of turns)

Frequency of induced emf in Hz $= f$

Flux per pole in weber $= \phi$

Coil span factor $K_p = \cos \frac{\alpha}{2}$

Distribution factor $= \frac{\sin \frac{m\beta}{2}}{m \sin \frac{\beta}{2}}$

Speed of rotor in rpm $= N$

Form factor (if emf is sinusoidal) $K_f = 1.11$.

In one revolution of rotor ($60/N$ second) each stator conductor is cut by a flux of $(P\phi)$ Wb.

$\therefore d\phi = P\phi$

Time taken by rotor poles to make one revolution $dt = \frac{60}{N}$ s.

\therefore Flux cut/sec. by stator conductor $= \frac{d\phi}{dt}$

(according to principle of electromagnetic inductions),

we can write, $\frac{d\phi}{dt} = \frac{P\phi}{60/N} = \frac{P\phi N}{60}$ Wb/sec.

\therefore Average emf induced in conductor of the armature $= \frac{d\phi}{dt} = (P\phi N/60)$ V

i.e., Average emf/phase in the armature $= \frac{P\phi N}{60} \times (2T)$ V

or $E_{av}/\text{phase} = \left(\frac{P\phi N}{60} \times Z \right)$ V

[Z being total number of conductors ($= 2T$)].

$\therefore E_{rms} = \left(1.11 \times \frac{P\phi N}{60} \times 2T \right)$ V $= \left(2.22 \frac{P\phi NT}{60} \right)$ V

or $E_{rms} = \left(2.22 \times \frac{P\phi}{60} \times \frac{120 f}{P} \times T \right)$ V $\left[\therefore f = \frac{PN}{120} \text{ Hz or } N = \frac{120 f}{P} \right]$

Hence $E_{rms} = (4.44 f \phi T)$ V. (11.1)

This would have been the actual value if the winding per phase is full pitched and concentrated. The winding being short pitched and distributed, the actual voltage available/phase

$$V_{ph} = (4.44 K_p K_d \phi f T)$$
 V $= (2.22 K_p K_d \phi f Z)$ V

Since most of the industrial synchronous generators are three phase, we can write,

Line voltage $V_L = \sqrt{3} V_{ph}$ and $I_L = I_{ph}$ (for star connection) while $V_L = V_{ph}$; $I_L = \sqrt{3} I_{ph}$ (for delta connection of armature).

$$\text{Distribution factor } K_d = \frac{\sin \frac{m\beta}{2}}{m \sin \frac{\beta}{2}} = \frac{\sin \frac{4 \times 15^\circ}{2}}{4 \sin \frac{15^\circ}{2}} = 0.9576.$$

As the coil pitch is 2 slots less to a pole pitch hence the winding is short pitched by an angle $\alpha = 15^\circ \times 2 = 30^\circ$.

$$\text{Pitch factor } K_p = \cos \frac{\alpha}{2} = \cos 15^\circ = 0.9659$$

$$V_p = 4.44 K_p K_d \phi f T, \text{ where } \phi \text{ is the flux per pole}$$

$$\therefore \phi = \frac{3810.62}{4.44 \times 0.9659 \times 0.9576 \times 60 \times 1536} = 0.01 \text{ Wb.} \quad \text{.....}$$

11.5 A 4-pole, three-phase 50 Hz. star connected alternator has a single layer winding in 36 slots with 30 conductors per slot. The flux per pole is 0.05 Wb and winding is full pitched. Find the synchronous speed and line voltage.

Solution

$$\text{Given: } P = 4, f = 50 \text{ Hz}$$

$$\text{Number of slots } S = 36.$$

$$\therefore \text{Number of slots per pole per phase } m = \frac{36}{4 \times 3} = 3$$

$$\text{Number of conductors } z = 30 \times 36 = 1080.$$

$$\text{Number of turns per phase } T = \frac{1080}{3 \times 2} = 180$$

$$\phi = 0.05 \text{ Wb.}$$

As the winding is full pitched, hence pitch factor $K_p = 1$

$$\text{Slot angle } \beta = \frac{180^\circ}{\text{No. of slots per pole}} = \frac{180^\circ}{\frac{36}{4}} = 20^\circ$$

$$\text{Hence distribution factor } K_d = \frac{\sin \frac{m\beta}{2}}{m \sin \frac{\beta}{2}} = \frac{\sin \frac{3 \times 20^\circ}{2}}{3 \sin \frac{20^\circ}{2}} = \frac{0.5}{0.521} = 0.96.$$

Now, if N_s being the synchronous speed,

$$N_s = \frac{120 f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm.}$$

$$\therefore \text{Phase voltage } V_p = 4.44 K_p K_d \phi f T$$

$$= 4.44 \times 1 \times 0.96 \times 0.05 \times 50 \times 180 = 1918.08 \text{ V.}$$

$$\text{Line voltage } V_L = \sqrt{3} \times 1918.08 = 3322 \text{ V.} \quad \text{.....}$$

11.6 Find the rms value of the phase voltage of a three-phase synchronous machine having 30 poles, 180 slots, single layer winding and full pitch coils. Each coil has 8 turns. Flux per pole is 0.03 Wb.

Solution

$$\text{Number of slots per pole per phase } m = \frac{180}{30 \times 3} = 2$$

$$\text{Slot angle } \beta = \frac{180^\circ}{\text{No. of slots per pole}} = \frac{180^\circ}{\frac{180}{30}} = 30^\circ$$

$$\text{Distribution factor } K_d = \frac{\sin \frac{m\beta}{2}}{m \sin \frac{\beta}{2}} = \frac{\sin \frac{2 \times 30^\circ}{2}}{2 \sin \frac{30^\circ}{2}} = \frac{0.5}{2 \times 0.2588} = 0.9659.$$

As the coils are full pitched hence pitch factor $K_p = 1$

Since the machine has single layer winding, total number of coils = $\frac{1}{2} \times \text{No. of slots}$
 $= \frac{1}{2} \times 180 = 90.$

\therefore Total numbers of turns per phase $T = \frac{8 \times 90}{3} = 240.$

Hence rms value of the phase voltage V_p is given by

$$V_p = 4.44 K_p K_d \phi f T = 4.44 \times 1 \times 0.9659 \times 0.03 \times 50 \times 240 = 1543.89 \text{ V.}$$

11.12 ARMATURE REACTION AND ARMATURE WINDING REACTANCE

When a three-phase ac supply is given to the stator of the alternator, current I_a flows in each phase of the stator winding. This current I_a produces a rotating magnetic field in the air gap of the alternator. Hence the flux in the air gap is the resultant of the flux produced by field current I_f and armature current I_a . The net air gap flux ϕ is given by

$\phi = \phi_f + \phi_a$, where ϕ_f is the flux produced by I_f and ϕ_a is the flux produced by I_a . As ϕ_f is produced by I_f , ϕ_f and I_f are in phase. The emf induced in the stator winding E_f lags behind the field flux by 90° . If the stator current I_a lags behind E_f by an angle θ then ϕ_a also lags behind E_f by angle θ , as ϕ_a and I_a are in phase. The resultant flux ϕ_r is shown in Fig. 11.1.

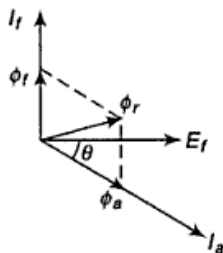


Fig. 11.1 Flux-current phasor diagram

It is clear that the main field flux ϕ_f is greatly affected by the stator flux ϕ_a produced by the stator current. This effect of the stator flux on the main field flux is termed as *armature reaction*. This effect is also dependent on the power factor of the load. The stator flux ϕ_a has a cross-magnetizing and demagnetizing effect upon the main flux ϕ_f . If ϕ_a is resolved into two components, one component will act in direct opposition to ϕ_f and reduces the net flux in the magnetic circuit. This is called the *demagnetizing effect*. The other component of ϕ_a is perpendicular to ϕ_f and it results in shifting the axis of the resultant flux. This is called the *cross-magnetizing effect*. Under lagging power factor operation ϕ_a has both demagnetizing and cross-magnetizing effect. But at unity p.f. load I_a and hence ϕ_a lies along E_f and the effect of ϕ_a on ϕ_f is purely cross-magnetizing. For leading p.f. operation cross magnetizing effect persists but the other effect becomes magnetizing.

A major part of the flux ϕ_a is thus armature reaction flux ϕ_{ar} and a small part of it is the leakage flux ϕ_{al} which links only the stator winding and not the rotor winding. This flux ϕ_{ar} induces a voltage E_{ar} in the stator winding which lags ϕ_{ar} by 90° . As I_a is in phase with ϕ_{ar} , hence E_{ar} lags I_a by 90° or it can be said that I_a lags $-E_{ar}$ by 90° . This voltage $-E_{ar}$ can be represented as a voltage drop across a fictitious equivalent reactance X_{ar} due to I_a .

Hence, $E_{ar} = j I_a X_{ar}$. X_{ar} is termed as *armature reaction reactance* or the *magnetizing reactance*.

11.13 ARMATURE LEAKAGE REACTANCE AND SYNCHRONOUS IMPEDANCE

A portion of the air gap flux ϕ_a produced by stator current I_a links only the stator winding and not the rotor winding. This flux ϕ_{al} is called the *leakage flux* which induces an emf E_{al} in the stator winding. The induced emf E_{al} can be considered equivalent to a voltage drop across a fictitious leakage reactance X_{al} .

Hence, $E_{al} = j I_a X_{al}$.

The effect of armature reaction and the effect of leakage flux can be represented by considering two fictitious reactances X_{ar} and X_{al} . *Synchronous reactance* X_s is thus the sum of armature reaction reactance and the leakage reactance, i.e.

$$X_s = (X_{ar} + X_{al})$$

As both X_{ar} and X_{al} are fictitious quantities, hence X_s is also a fictitious quantity. If R_a is the resistance of the armature winding then *synchronous impedance* Z_s is obtained as

$$Z_s = R_a + jX_s = \sqrt{R_a^2 + X_s^2} \angle \tan^{-1} \frac{X_s}{R_a} \Omega.$$

The magnitude of R_a is very small. Hence for practical purpose, Z_s is assumed to be equal to X_s .

11.14 EQUIVALENT CIRCUIT AND PHASOR DIAGRAM

The equivalent circuit of an alternator is shown in Fig. 11.2.

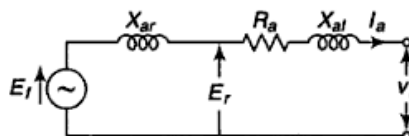


Fig. 11.2 Equivalent circuit of alternator

From the circuit diagram it is clear that the open circuit voltage E_f is the summation of the terminal voltage V_t and the drop across the synchronous impedance X_s and the armature resistance.

Hence, $E_f = V_t + I_a R_a + j I_a (X_{ar} + X_{al})$ [where, $X_s = (X_{ar} + X_{al})$]
 $= V_t + I_a Z_s$ [Z_s being equal to $\{R_a + j (X_{ar} + X_{al})\}$]

Also, $E_f = E_r + j X_{ar} I_a$

where E_r is the emf induced by the resultant flux ϕ_r .

Figure 11.3(a) and Fig. 11.3(b) show the phasor diagram of an alternator under lagging p.f. and leading p.f. operation respectively.

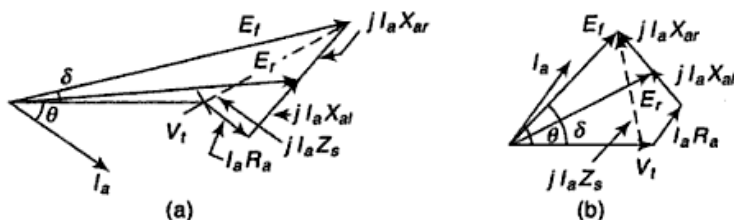


Fig. 11.3 Phasor diagram of cylindrical rotor alternator at (a) lagging p.f. (b) leading p.f.

[θ is the power factor angle and the angle between E_f and V_t , i.e. δ_f is called the *power angle*].

11.15 VOLTAGE REGULATION OF A SYNCHRONOUS GENERATOR

Voltage regulation of a synchronous generator may be defined as the percentage change in voltage from no load to full load when the field excitation and frequency remain constant.

$$\therefore \% \text{ regulation } (\Delta V) = \frac{V_o - V_{fl}}{V_{fl}} \times 100 \quad (11.2)$$

where, V_o is the no load voltage and V_{fl} is the full load voltage.

Expression for Voltage Regulation

With reference to the phasor diagram of an alternator operating at lagging p.f. load,

$$OH^2 = OC^2 + CH^2$$

$$\begin{aligned} \text{or } V_o &= \sqrt{(V_{fl} + AB + BC)^2 + (DH - DC)^2} \\ &= \sqrt{(V_{fl} + IR \cos \phi + IX_s \sin \phi)^2 + (IX_s \cos \phi - IR \sin \phi)^2} \end{aligned} \quad (11.3)$$

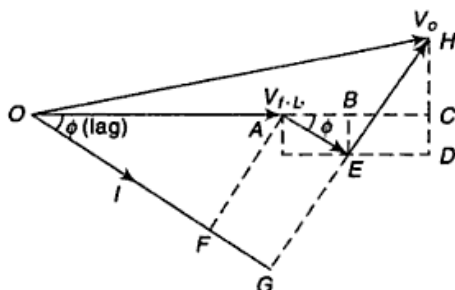


Fig. 11.4 Phasor diagram of an alternator operation at lagging load.

Field flux mmf (F_f) is opposed by F_{ar} , the armature reaction mmf and hence resultant field mmf F decreases, when the p.f. is lagging. With leading p.f. operation, the resultant field mmf increases due to the magnetising effect of armature reaction mmf F_{ar} being added to main field mmf F_f .

Again, for leading p.f. operation, the expression for V_o can be written as

$$V_o = \sqrt{(V_{fl} \times IR \cos \phi - IX_s \sin \phi)^2 + (IX_s \cos \phi + IR \sin \phi)^2} \quad (11.6)$$

Also, from Fig. 11.4 an alternate expression for regulation can be derived for operation both in lagging and leading loads. In Fig. 11.4.

$$\begin{aligned} V_o &= \sqrt{(OG)^2 + (GH)^2} = \sqrt{(OF + FG)^2 + (GE + EH)^2} \\ &= \sqrt{(V_{fl} \cos \phi + IR)^2 + (V_{fl} \sin \phi + IX_s)^2} \end{aligned}$$

(for lagging loads) and

$$V_o = \sqrt{(V_{fl} \cos \phi + IR)^2 + (V_{fl} \sin \phi - IX_s)^2} \quad (11.7)$$

(for leading loads)

Regulation can be determined in practical machines by first measuring the dc resistance of the stator at (which is say R ohms) and then finding Z_s (synchronous impedance) by obtaining the ratio of V_o and I_{sc} where V_o is the no load voltage at the machine output where it is being operated with full speed and normal excitation and I_{sc} is the short circuit current (being equal to the full load current) at the machine terminal for operation at reduced suitable excitation at normal speed

when the terminals are shorted. Obviously, $Z_s = \frac{V_o}{I_{sc}}$, all the quantities being expressed in per phase basis. Now we can find X_s (synchronous reactance) using the formula,

$$X_s = \sqrt{Z_s^2 - R^2}$$

11.7 A 440 V, three-phase alternator, running at rated speed, has a 2 A excitation current when short circuit is applied at its terminals. The short circuit magnitude is 50 A (full load current). At this excitation the open circuit voltage is 150 V/phase. Assuming the armature circuit resistance to be 0.5 Ω per phase, obtain the value of regulation of the alternator at (i) 0.8 p.f. lagging load and (ii) 0.8 p.f. leading load.

Solution

$$Z_s = \frac{150}{50} = 3 \Omega/\text{ph}$$

$$\therefore X_s = \sqrt{3^2 - 0.5^2} = 2.96 \Omega/\text{ph}. \quad (\because Z_s = \sqrt{X_s^2 + R^2})$$

For lagging p.f. operation,

$$\begin{aligned} V_o &= \sqrt{(V_{fl} + IR \cos \phi + IX_s \sin \phi)^2 + (IX_s \cos \phi - IR \sin \phi)^2} \\ &= \sqrt{\left\{ \left(\frac{440}{\sqrt{3}} \right) + 50 \times 0.5 \times 0.8 + 50 \times 2.96 \times 0.6 \right\}^2} \\ &\quad + (50 \times 2.96 \times 0.8 - 50 \times 0.50 \times 0.6)^2 \\ &= \sqrt{131654 + 10691.56} = 377.29 \text{ V/ph.} \end{aligned}$$

$$\therefore \Delta V (\text{regulation})\% = \frac{V_o - V_{fl}}{V_{fl}} \times 100 = \frac{377.29 - \frac{440}{\sqrt{3}}}{\frac{440}{\sqrt{3}}} \times 100 = 48.52\%.$$

If we use another formula of regulation, we can write,

$$\begin{aligned} V_o &= \sqrt{(V_{fl} \cos \phi + IR)^2 + (V_{fl} \sin \phi + IX_s)^2} \\ &= \sqrt{\left(\frac{440}{\sqrt{3}} \times 0.8 + 50 \times 0.5\right)^2 + \left(\frac{440}{\sqrt{3}} \times 0.6 + 50 \times 2.96\right)^2} \\ &= \sqrt{52087.7 + 90252.46} = 377.286 = 377.29 \text{ V/ph.} \end{aligned}$$

Hence V_o obtained is same for both the formula and any one can be used to find regulation of the given alternator at lagging p.f. We will find similarly that any of these formulae can be used for leading p.f. operation too to find V_o .

For leading p.f. operation,

$$\begin{aligned} V_o &= \sqrt{(V_{fl} + IR \cos \phi - IX_s \sin \phi)^2 + (IX_s \cos \phi + IR \sin \phi)^2} \\ &= \sqrt{(254.04 + 50 \times 0.5 \times 0.8 - 50 \times 0.6 \times 2.96)^2} \\ &\quad + \sqrt{(50 \times 2.96 \times 0.8 + 50 \times 0.5 \times 0.6)^2} \\ &= \sqrt{34313.86 + 17795.56} = 228.27 \text{ V/ph} \end{aligned}$$

Also, we can find V_o using another formula

$$\begin{aligned} V_o &= \sqrt{(V_{fl} \cos \phi + IR)^2 + (V_{fl} \sin \phi - IX_s)^2} \\ &= \sqrt{(254.04 \times 0.8 + 50 \times 0.5)^2 + (254.04 \times 0.6 - 50 \times 2.96)^2} \\ &= \sqrt{52089.85 + 19.57} = 228.27 \text{ V/ph} \end{aligned}$$

$$\therefore \Delta V(\%) = \frac{V_o - V_{fl}}{V_{fl}} \times 100 = \frac{228.27 - 254.04}{254.04} \times 100 = -10.14\%.$$

[Note: In subsequent examples, to maintain symmetry for the notations, we will replace

V_o by E_f and V_{fl} by V_t so that regulation is $\left(\frac{E_f - V_t}{V_t} \times 100\right)$ per phase.]

.....

11.8 A 1000 kVA, three-phase star connected alternator has a rated line to line terminal voltage of 3000 V. The resistance per phase is 0.5Ω and synchronous reactance 5Ω . Calculate the voltage regulation at full load and 0.8 p.f. lagging.

Solution

Power output $P = 1000 \times 10^3 \text{ VA}$

Line voltage $V_L = 3000 \text{ V}$

If I_L be the line current then

$$\sqrt{3} V_L I_L = 1000 \times 10^3$$

$$\text{or } I_L = \frac{1000 \times 10^3}{\sqrt{3} \times 3000} \text{ A} = 192.45 \text{ A.}$$

From the phasor diagram (Fig. 11.2), the no load voltage $E_f = V_t + I_a(R_a + jX_s)$ where, $X_s = X_{ar} + X_{al} = 5 \Omega$ and $R_a = 0.5 \Omega$. (V_t) is the terminal voltage per phase i.e. $V_t = \frac{3000}{\sqrt{3}} \text{ V}$.

Also, $I_a = I_L = 192.45 \text{ A}$.

$$\begin{aligned} \text{Hence, } E_f &= \frac{3000}{\sqrt{3}} \angle 0^\circ + 192.45 \angle -\cos^{-1} 0.8 (0.5 + j5) \\ &= 1732.1 + 192.45 \angle -36.87^\circ \times 5.025 \angle 84.29^\circ \\ &= 1732.1 + 967.06 \angle 47.72^\circ = 2386.43 + j715.5 \\ \therefore |E_f| &= 2491 \text{ V (per phase).} \end{aligned}$$

$$\text{Voltage regulation of full load} = \frac{2491 - \frac{3000}{\sqrt{3}}}{\frac{3000}{\sqrt{3}}} \times 100\% = 43.81\%$$

11.16 PHASOR DIAGRAM FOR A SALIENT POLE ALTERNATOR: TWO-REACTION THEORY

As discussed earlier the rotor of cylindrical pole machines has uniform air gap whereas in salient pole alternators the air gap is non-uniform. Figure 11.6 shows a two-pole salient pole alternator rotating in an anti-clockwise direction. From the figure it is clear that there are two axes of symmetry here. The axis of the rotor pole is called the *direct* or *d* axis and the axis perpendicular to the rotor pole is called the *quadrature* or *q* axis. The direct axis flux path includes two small air gaps under pole faces only whereas quadrature axis flux path has two larger air gaps in the inter-polar regions. Hence with direct axis flux path has minimum reluctance and quadrature axis flux path has maximum reluctance. According to the two-reaction theory, the armature mmf F_a produced by stator I_a is resolved into two components, one along the direct or *d*-axis and another along quadrature or *q*-axis. The direct axis component of F_a is F_{ad} and the quadrature axis component is F_{aq} . The effect of F_{ad} is either magnetizing or demagnetizing (depending whether the p.f. is leading or lagging), whereas the effect of F_{aq} is entirely cross-magnetizing. Similarly, flux ϕ_a produced by stator current I_a is resolved into two components ϕ_{ad} and ϕ_{aq} ; ϕ_{ad} induces direct axis armature reaction voltage E_{ad} and ϕ_{aq} induces quadrature axis armature reaction voltage E_{aq} . If I_d and I_q be the two components of current I_a along direct and quadrature axis respectively then

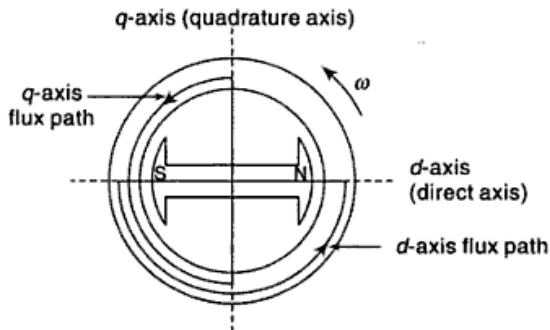


Fig. 11.6 2-pole salient pole alternator

$$P = V_d I_d + V_q I_q \quad (11.8)$$

From the phasor diagram in Fig. 11.6, we have

$$V_q = V_t \cos \delta \quad \text{and} \quad V_d = V_t \sin \delta \quad (11.9)$$

Also, $V_d = I_q X_q$

and $V_q = E_f - I_d X_d$

Hence, $I_d = \frac{E_f - V_q}{X_d}$ and $I_q = \frac{V_d}{X_q}$.

Substituting the values of I_d and I_q in Eq. (11.8) we get

$$\begin{aligned} P &= V_d \left(\frac{E_f - V_q}{X_d} \right) + V_q \left(\frac{V_d}{X_q} \right) \\ &= \frac{V_d E_f}{X_d} - \frac{V_d V_q}{X_d} + \frac{V_d V_q}{X_q} \end{aligned} \quad (11.10)$$

Substituting the values of V_d and V_q from Eq. (11.9) in Eq. (11.10), we have

$$\begin{aligned} P &= \frac{V_t E_f \sin \delta}{X_d} - \frac{V_t^2 \sin \delta \cos \delta}{X_d} + \frac{V_t^2 \sin \delta \cos \delta}{X_q} \\ &= \frac{V_t E_f \sin \delta}{X_d} - \frac{1}{2} V_t^2 \left[\frac{1}{X_d} - \frac{1}{X_q} \right] \sin 2\delta \\ &= \frac{V_t E_f \sin \delta}{X_d} + \frac{1}{2} V_t^2 \left[\frac{X_d - X_q}{X_d X_q} \right] \sin 2\delta \end{aligned} \quad (11.11)$$

For cylindrical rotor alternator $X_d = X_q$, hence

$$P = \frac{V_t E_f \sin \delta}{X_d} = \frac{V_t E_f \sin \delta}{X_s},$$

where X_s is the synchronous reactance. The power angle curve for cylindrical rotor alternator is shown in Fig. 11.9.

Equation (11.11) represents the expression of output power for salient pole alternators. The first component, i.e.

$\left(\frac{V_t E_f}{X_d} \sin \delta \right)$ represents the power output

due to field excitation. The second component of the power expression is due to the saliency of the alternator and is independent of the excitation. This component of power is called the *reluctance power* and it is directly proportional to $(\sin 2\delta)$. The power angle characteristic of the salient pole alternator is the resultant of two curves as shown in Fig. 11.10.

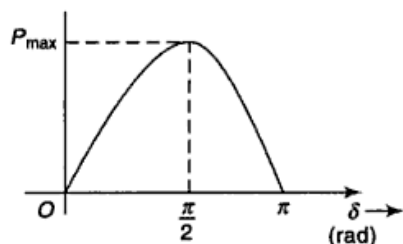


Fig. 11.9 Power angle characteristics for a cylindrical rotor alternator

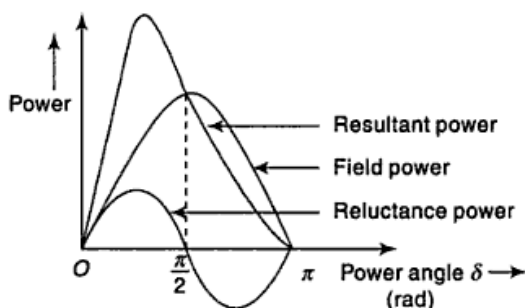


Fig. 11.10 Power angle characteristics for salient pole alternator

11.9 A salient pole synchronous generator is rated at 200 MVA and 11 kV. Its armature winding is star connected having negligible resistance; it is given that $X_d = 0.8$ p.u., $X_q = 0.5$ p.u. The generator is supplying rated MVA at rated voltage and at 0.8 p.f. lagging. Find power angle and open circuit emf in p.u.

Solution

$$X_d = 0.8 \text{ p.u.}; X_q = 0.5 \text{ p.u.}, R_a = 0 \text{ (given)}$$

Taking terminal voltage as the reference phasor, $V_t = 1 \angle 0^\circ$

As power factor is 0.8 lagging hence armature current I_a is given by

$$I_a = 1 \angle -36.87^\circ \text{ p.u.}$$

From phasor diagram (Fig. 11.8(b))

$$\begin{aligned} OA &= V_t + j I_a X_q \\ &= 1 \angle 0^\circ + 1 \angle -36.87^\circ \times 0.5 \angle 90^\circ \\ &= 1 \angle 0^\circ + 0.5 \angle 53.13^\circ = 1 + j 0.4 = 1.36 \angle 17.1^\circ \end{aligned}$$

Hence power angle $\delta = 17.1^\circ$;

again referring to Fig. 11.8(b),

$$I_d = I_a \sin(\delta + \theta) = 1 \sin(17.1^\circ + 36.87^\circ) = 0.809.$$

Open circuit emf E_f is obtained as

$$E_f = |OA| + |AB| = 1.36 + I_d(X_d - X_q) = 1.36 + 0.809(0.8 - 0.5) = 1.6027 \text{ p.u.}$$

11.10 A 70 MVA, 13.8 kV, three-phase star connected salient pole alternator has a direct axis reactance of 1.83Ω and quadrature axis reactance of 1.2Ω . It delivers a load of 0.8 p.f. lagging. Calculate the excitation voltage and voltage regulation.

Solution

$$X_d = 1.83 \Omega$$

$$X_q = 1.2 \Omega$$

$$\text{Phase voltage } V_t = \frac{13.8 \times 10^3}{\sqrt{3}} \text{ V} = 7967.67 \text{ V}$$

$$\text{Line current } I_L = \frac{70 \times 10^6}{\sqrt{3} \times 13.8 \times 10^3} \text{ A} = 2928.67 \text{ A}$$

From the phasor diagram in Fig. 11.8(b),

$$\begin{aligned} OA &= V_t + j I_a X_q \\ &= 7967.67 + 2928.67 \angle -36.87^\circ \times 1.2 \angle 90^\circ \\ &= 7967.67 + 3514.4 \angle 53.13^\circ = 10076.3 + j 2811.5 = 10461.19 \angle 15.6^\circ \end{aligned}$$

Power angle $\delta = 15.6^\circ$;

$$\therefore I_d = I_a \sin(\delta + \theta) = 2928.67 \sin(15.6^\circ + 36.87^\circ) = 2322.644 \text{ A.}$$

Excitation voltage is given by

$$\begin{aligned} |E_f| &= |V_t + I_a X_q + I_d (X_d - X_q)| \\ &= 10461.19 + 2322.536(1.83 - 1.2) = 11924.39 \text{ V} = 11.92 \text{ kV.} \end{aligned}$$

Voltage regulation is found to be

$$\Delta V = \frac{11.92 - \frac{13.8}{\sqrt{3}}}{\frac{13.8}{\sqrt{3}}} \times 100\% = 49.6\%.$$

11.11 A 50 MVA, 11 KV, 50 Hz, 6-pole alternator has an armature resistance of 0.001 p.u. and synchronous reactance of 0.75 p.u. At full load, the rated emf is 1.6 p.u. Find the torque angle and power factor.

Solution

Considering $I_a = 1 \text{ p.u.}$, $V = 1 \text{ p.u.}$
 $R_a = 0.001 \text{ p.u.}$ and $X_s = 0.75 \text{ p.u.}$,

we have

$$\begin{aligned} E^2 &= (V \cos \theta + I_a R_a)^2 + (V \sin \theta + I_a X_s)^2 \\ (1.6)^2 &= (1 \cos \theta + 1 \times 0.001)^2 + (1 \sin \theta + 1 \times 0.75)^2 \end{aligned}$$

$$\text{or } 2.56 = \cos^2 \theta + (0.001)^2 + 0.002 \cos \theta + \sin^2 \theta + 1.5 \sin \theta + 0.5625$$

$$\text{or } 1.5 \sin \theta + 0.002 \cos \theta = 2.56 - 1 - 0.5625 - (0.001)^2 = 0.9975.$$

By trial and error method solving the above equation $\cos \theta = 0.75$ lagging or power factor 0.75 lagging.

$$\text{Hence } E \cos \delta = V + I_a R_a \cos \theta + I_a X_s \sin \theta$$

$$\text{or } 1.6 \cos \delta = 1 \angle 0^\circ + 1 \times 0.001 \times 0.75 + 1 \times 0.75 \times 0.66 = 1.4968$$

or Torque angle (δ) = 20.69°.

[Torque angle is same as to power angle]

Parallel Operation of Synchronous Generators

Generators are run in parallel to cater increase of load demand. Whenever more power is needed, an additional generator is connected to the existing generator bus and synchronised. When a small generator is brought up to an existing network having a large generator, it is referred to as connecting this single generator to the infinite bus. The following conditions must be satisfied for parallel operation of a generator with an existing generator bus:

- the terminal voltage of the incoming machine should be identical to the existing bus bar voltage
- the frequency of both the generators must be identical during synchronisation
- the phase sequence of the incoming generator must be same as that of the existing bus voltage sequence
- the phase relations of the incoming generator and the existing one should coincide.

A synchroscope is usually used for synchronising two synchronous generators or a synchronous generator to the infinite bus. The pointer of the synchroscope rotates clockwise when an alternator is running faster and anticlockwise when it runs slower than the existing bus with which it is to be synchronised. When the pointer is stationary and pointing upward, it is the right moment for synchronising

the incoming alternator with the existing bus. The synchronising needs to be closed at this instant without any further delay.

11.19 SYNCHRONOUS MOTOR

Any alternator can be operated as a synchronous motor and a synchronous motor can also be operated as an alternator. For a given number of poles and fixed frequency, it operates at only one speed known as *synchronous speed*

$\left(N_s = \frac{120 f}{P} \right)$, so it works only at a constant speed. Damper winding is provided for making it self-starting and also to prevent hunting.

11.20 PRINCIPLE OF OPERATION

When a three-phase stator winding of a synchronous machine is fed by a balanced three-phase ac supply, then a magnetic flux of constant magnitude but rotating at synchronous speed is produced.

Let us assume that the rotor be rotating round the stator at synchronous speed having the same number of poles as stator. As the rotor is excited by an external dc source the poles of the rotor retain same polarity throughout but the polarity of the stator poles changes as it is connected to an ac supply, i.e. the polarity of the stator poles are alternating. Two similar poles of stator and rotor repel each other with the result that the rotor tends to rotate in a particular direction. After

$(T/2)$ sec. $\left(\text{i.e. } T = \frac{1}{f} \right)$, the polarity of stator poles is reversed but the polarity of

the rotor poles remains the same. Under this condition stator N-poles attract rotor S-poles and stator S-poles attract the rotor N-poles and hence the torque produced will be in the reverse direction and thus the rotor starts to rotate in the reverse direction.

For frequency 50 Hz., these changes will occur 100 times in one sec, thus the torque acting on the rotor of the synchronous motor is pulsating and the rotor does not move in any direction and remains stationary. Therefore, the synchronous motor is not self-starting.

Let us now consider that the rotor is rotated in a clockwise direction by some external means so that torque is clockwise. After half a period later, the stator N-pole and S-pole will become S-pole and N-pole. If the rotor speed is such that the N-pole of the rotor also turns by a pole pitch so that it is again under the N-pole then the torque acting on the rotor will again be clockwise. Hence in order to obtain a continuous and unidirectional torque, the rotor must be rotated with such a speed that it advances 1-pole pitch by the time the stator poles interchange their polarity. This means the rotor must rotate at synchronous speed with the stator. At this instant the stator and rotor poles get magnetically interlocked (i.e. N-pole of stator attract S-pole of rotor and vice versa). It is because of this magnetic locking acting between the two, the motor rotates. The motor can rotate at synchronous-speed only.

When the mechanical load is applied to a synchronous motor its speed cannot decrease since the rotor must operate at constant speed. Hence speed is independent of load and can be varied only by varying the supply frequency.

11.21 EFFECT OF CHANGE OF EXCITATION OF A SYNCHRONOUS MOTOR (V-CURVES) FOR THE MOTOR DRIVING A CONSTANT LOAD

If a synchronous motor is loaded with a constant load, the input power ($VI \cos \theta$) drawn from the supply will also remain constant. As the supply voltage is constant, hence ($I \cos \theta$) will also remain constant. Under this condition, the effect of change of field excitation on armature current, I can be studied.

As the dc excitation is changed, the magnitude of induced emf E changes. The torque angle δ , i.e. the angle of lag of E from the axis of V remains constant as long as the load on the motor remains constant.

Figure 11.11 shows the effect of varying excitation on the power factor of the motor. When the magnitude of E is less than V , the motor works at lagging p.f. (Fig. 11.11(a)), when E is greater than V , the motor works at leading p.f. (Fig. 11.11(b)) and when $E = V$, the motor works at unity p.f. (Fig. 11.11(c)).

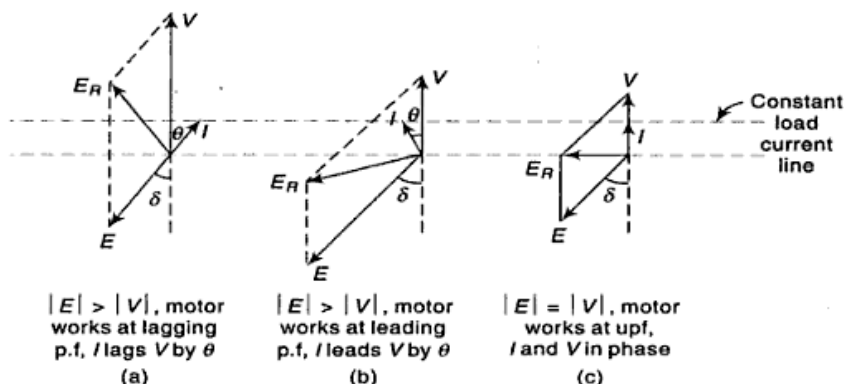


Fig. 11.11

The excitation corresponding to the unity p.f. current drawn by the motor is called *normal excitation*. Excitation higher than normal is called *over excitation* and the excitation lower than normal is called *under excitation*. It can be observed that the magnitude of current under normal excitation is the minimum.

Effect of change of excitation on armature current and p.f. at a constant load are shown in Fig. 11.12.

In Fig. 11.12 at normal excitation the p.f. of the motor is unity. The magnitude of armature current at this excitation is minimum. For excitation higher than the normal excitation, the magnitude of the armature current increases and p.f. is leading. For excitation lower than the normal excitation, the magnitude of the armature current still increases but the p.f. is lagging.

As the shape of graph I versus I_f is similar to the English alphabet "V", it is also known as the V-curve of the motor. A series of V-curves can be obtained by changing the load on the motor.

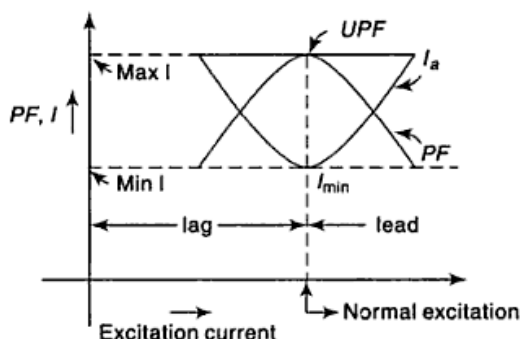


Fig. 11.12 Profile of power factor and current against excitation current in synchronous motor

11.22 STARTING OF SYNCHRONOUS MOTORS

It is now evident that a synchronous motor needs an auxiliary starting arrangement. The methods of starting of a synchronous motor are as follows:

- Starting with the help of a damper winding.
- Starting with the help of a separate small induction motor.
- Starting by using a dc motor coupled to the synchronous motor.
- Starting as induction motor and run as synchronous motor.

(a) Starting with the Help of a Damper Winding

In this method a synchronous motor is started independently using a damper winding. The damper winding is provided on the pole face slots in the field. Bars of aluminium, copper, bronze or similar alloys are inserted in slots of pole shoes. These bars are short-circuited by end-rings on each side of the poles. By short-circuiting of these bars, a squirrel cage winding is virtually formed. When a three-phase supply is given to the stator, a synchronous motor with damper winding will start as a three phase induction motor with the speed of rotation near to synchronous speed. Now the d.c. excitation to the field winding of rotor is applied and the rotor will be pulled into synchronism. A reduced supply voltage may be necessary, to limit the starting current drawn by the motor.

In this method since starting is done as an induction motor, the starting torque developed is rather low. Hence a large capacity synchronous motor may not be able to start on full load if damper winding starting is employed.

(b) Starting with the Help of a Separate Small Induction Motor

In this method, a separate induction motor is used to bring the speed of the synchronous motor to synchronous speed. The number of poles of the synchronous motor needs to be more than that of poles of the induction motor to enable the induction motor to rotate at the synchronous speed of the synchronous motor. As the set attains synchronous speed, dc excitation is applied and as the rotor and stator of the synchronous motor are pulled in synchronism, the induction motor is switched off.

(c) Starting by Using a dc Motor Coupled to a Synchronous Motor

In this method, the dc motor drives the synchronous motor and brings it to synchronous speed. Then the synchronous motor is synchronised with the supply.

(d) Starting as Induction Motor

In this method the rotor winding is shorted at start and no dc excitation is given. The stator receives the applied voltage in steps and when near full speed is attained by the rotor, the rotor short circuit is removed and dc voltage is applied. The motor continues to operate as a synchronous motor. Instead of keeping the rotor winding shorted at start, sometime there is one more additional winding which helps the machine to start as an induction motor. This winding remains open-circuited during the run of the machine as a synchronous motor.

Out of these three methods, the method of using a damper winding for starting the synchronous motor is mostly used, because it requires no external motor.

11.23 APPLICATION OF SYNCHRONOUS MOTOR

An over-excited synchronous motor operates at leading p.f. and takes a leading current from the bus bar; so it can be used to raise the overall power factor of the bus bar supplying load.

When the motor is run without load with over excitation for improving the voltage regulation of a transmission line it is called a *synchronous capacitor* or *synchronous condenser*. Synchronous motors can be used in electric clocks as it runs at constant speed.

11.24 COMPARISON BETWEEN SYNCHRONOUS AND INDUCTION MOTOR

<i>Synchronous motor</i>	<i>Induction motor</i>
1. It is internally not a self starting motor.	1. It is a self-starting motor.
2. It runs at constant speed called synchronous speed and this speed is independent of the load.	2. The speed of the motor is always less than the synchronous speed and its speed decreases as the shaft load increases.
3. It requires dc source for the field excitation.	3. No dc exciter is needed.
4. It can be operated under a wide range of power factors including lagging a leading p.f.	4. It runs with lagging p.f. only which may be very low at light loads.
5. It runs at synchronous speed only. The only way to change its speed is by varying the supply frequency.	5. Many power electronic methods are available with which speed can be varied.
6. It is used to improve the p.f. and in that case it is called as synchronous capacitor.	6. It is used only to drive a mechanical load.

(Contd)

Here V is the terminal voltage and E is the counter emf

$$V = E + I_a R_a + j I_a X_s \quad (11.12)$$

The corresponding phasor diagram is shown in Fig. 11.14.

The phasor diagram of a salient pole synchronous motor is shown in Fig. 11.15(a). From this phasor diagram the terminal voltage is obtained as

$$V = E + I_a R_a + j I_d X_d + j I_q X_q \quad (11.13)$$

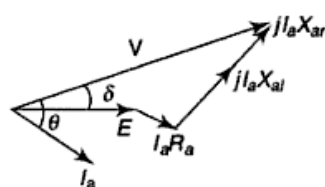


Fig. 11.14 Phasor diagram of a cylindrical rotor synchronous motor

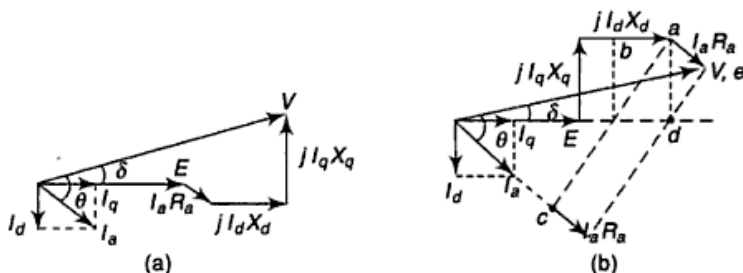


Fig. 11.15 Phasor diagram of a salient pole synchronous motor

The armature current I_a can be decomposed into two components: I_d , which is lagging phasor E by 90° and I_q , which is in phase with E .

Figure 11.15(b) shows the phasor diagram in terms of the known parameters. From this phasor diagram it is also evident that $V = E + j I_q X_q + j I_d X_d + I_a R_a$. Next, ac is drawn from point a perpendicular to I_a and $ac = j I_a X_q$. From point e , i.e. the terminal point of V , ed is drawn parallel to ac which meets the extended line of vector E at d .

Hence $cd = j I_d X_q$

Now, $ac = cd + da$

or $j I_a X_q = j I_d X_q + j I_q X_q$

or $j I_q X_q = j I_a X_q - j I_d X_q$

Hence
$$\begin{aligned} V &= E + j I_q X_q + j I_d X_d + I_a R_a \\ &= E + I_a R_a + j I_d X_d + j I_a X_q - j I_d X_q \\ &= E + I_a R_a + j I_a X_q + j I_d (X_d - X_q). \end{aligned} \quad (11.14)$$

The equivalent circuit of the salient pole synchronous motor is shown in Fig. 11.16.

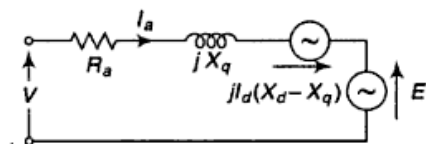


Fig. 11.16 Equivalent circuit of a salient pole synchronous motor

11.27 POWER AND TORQUE DEVELOPED IN A CYLINDRICAL ROTOR MOTOR

Let S represent the per phase complex power drawn by the cylindrical rotor synchronous motor.

$$S = V \cdot I_a^* = V \cdot \left| \frac{V - E}{Z_s} \right|^*$$

where Z_s is the synchronous impedance.

$$= V \cdot \left| \frac{V}{Z_s} \right|^* - V \cdot \left| \frac{E}{Z_s} \right|^*$$

Now $E = |E| \angle -\delta$

and $Z_s = |Z_s| \angle \phi = \sqrt{R_s^2 + X_s^2} \angle \tan^{-1} \frac{X_s}{R_s}$.

Hence

$$\begin{aligned} S &= |V| \angle 0^\circ \cdot \frac{|V| \angle 0^\circ}{|Z_s| \angle -\phi} - |V| \angle 0^\circ \cdot \frac{|E| \angle -\delta}{|Z_s| \angle -\phi} \\ &= \frac{|V|^2}{|Z_s|} \angle \phi - \frac{|V||E|}{|Z_s|} \angle \delta + \phi = P + jQ \end{aligned}$$

\therefore Active power P per phase is

$$P = \frac{|V|^2}{|Z_s|} \cos \phi - \frac{|V||E|}{|Z_s|} \cos (\delta + \phi) \quad (11.15)$$

and reactive power Q per phase is

$$Q = \frac{|V|^2}{|Z_s|} \sin \phi - \frac{|V||E|}{|Z_s|} \sin (\delta + \phi) \quad (11.16)$$

Neglecting stator resistance (i.e. $\phi = 90^\circ$)

$$P = \frac{|V||E|}{|X_s|} \sin \delta$$

where X_s is the synchronous reactance.

Total active power (or total mechanical power developed) by the motor is

$$\begin{aligned} P &= \frac{3|V||E|}{|X_s|} \sin \delta \\ &= P_{\max} \sin \delta, \text{ where } P_{\max} = \frac{3|V||E|}{|X_s|}. \end{aligned} \quad (11.17)$$

Mechanical torque developed by the motor

$$T = \frac{P_{\max} \sin \delta}{\omega_s},$$

where (ω_s) is the synchronous speed

$$\begin{aligned} \therefore T &= \frac{3|V||E|}{\omega_s |X_s|} \sin \delta \\ &= T_{\max} \sin \delta \end{aligned} \quad (11.18)$$

where (T_{\max}) is the *maximum torque* which is also known as *pull-out torque*.

The power angle characteristics is shown in Fig. 11.17.

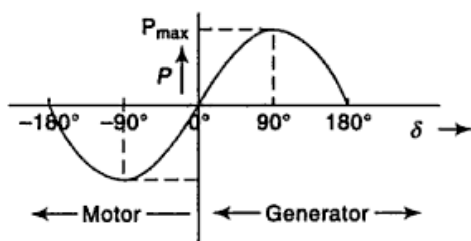


Fig. 11.17 Power angle characteristics of a cylindrical rotor synchronous motor

The synchronous motor can be loaded up to a maximum value of P_{\max} which is called the *static stability limit* and after which it will lose synchronism. In order to increase the stability limit at fixed applied voltage V the field current should be increased which in turn will increase the excitation voltage E .

11.28 POWER AND TORQUE DEVELOPED IN SALIENT POLE MOTOR

Neglecting the armature resistance, the simplified phasor diagram of salient pole motor is shown in Fig. 11.18.

From the phasor diagram

$$|V| \cos \delta = |E| + I_d X_d$$

and

$$|V| \sin \delta = I_q X_q$$

Hence

$$I_d = \frac{|V| \cos \delta - |E|}{X_d} \quad \text{and}$$

$$I_q = \frac{|V| \sin \delta}{X_q} \quad (11.19)$$

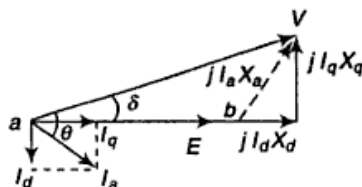


Fig. 11.18 Phasor diagram of a salient pole motor (neglecting R_a)

If V_d and V_q are the two components of V , then

$$V_d = -|V| \sin \delta$$

[$-ve$ sign appears as for motor δ is $-ve$ and $\sin(-\delta) = -\sin \delta$]

$$V_q = |V| \cos \delta$$

Per phase active power

$$\begin{aligned} P &= V_d I_d + V_q I_q \\ &= -|V| \sin \delta \cdot \frac{|V| \cos \delta - |E|}{X_d} + |V| \cos \delta \cdot \frac{|V| \sin \delta}{X_q} \\ &= \frac{|V||E| \sin \delta}{X_q} + |V|^2 \sin \delta \cos \delta \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \\ &= \frac{|V||E|}{X_d} \sin \delta + |V|^2 \frac{X_d - X_q}{2 X_d X_q} \sin 2\delta \end{aligned} \quad (11.20)$$

Hence total mechanical power developed

$$P_m = \frac{3|V||E|}{X_d} \sin \delta + 3|V|^2 \frac{X_d - X_q}{2 X_d X_q} \sin 2\delta \quad (11.21)$$

In a single layer winding machine number of coils = $\frac{1}{2}$ (number of slots)

$$= \frac{1}{2} \times 16 \times 10 = 80$$

Total number of turns = $20 \times 80 = 1600$

Number of turns per phase $T_{ph} = \frac{1600}{3} = 533$

Hence, emf induced per phase is

$$E = 4.44 f \phi T_{ph} = 4.44 \times 50 \times 0.025 \times 533 = 2958.15 \text{ V}$$

$$\text{Total kVA} = 3 \times 2958.15 \times 75 \times 10^{-3} = 665.58$$

Hence output of the stator winding is 665.58 kVA.

11.19 A 4 pole three-phase, 50 Hz, 2500 V synchronous machine has 48 slots. Each slot has two conductors. The coil pitch is 46 slots. Determine the flux per pole.

Solution

Number of slots per pole per phase $m = \frac{48}{4 \times 3} = 4$

Slot angle $\beta = \frac{180^\circ}{\text{Number of slots per pole}} = \frac{180^\circ \times 4}{48} = 15^\circ$

Distribution factor $K_d = \frac{\sin \frac{m\beta}{2}}{m \sin \frac{\beta}{2}} = \frac{\sin \frac{4 \times 15^\circ}{2}}{4 \sin \frac{15^\circ}{2}} = \frac{0.5}{0.522} = 0.9576$

Total number of slots = 48

but coil pitch = 46 slots.

Hence the coils are short pitched by $(48 - 46)$ i.e., 2 slots

Short pitching angle $\alpha = 2 \times 15^\circ = 30^\circ$

Hence pitch factor $K_p = \cos \frac{\alpha}{2} = \cos \frac{30^\circ}{2} = 0.9659$

Total number of conductors is (48×2) i.e. 96

Hence number of turns per phase $T_{ph} = \frac{96}{2 \times 3} = 16$

Emf per phase $E = \frac{2500}{\sqrt{3}} \text{ V} = 1443.42 \text{ V}$

If ϕ be the flux per pole,

$$E = 4.44 K_p K_d f (T_{ph}) \phi$$

Hence $\phi = \frac{1443.42}{4.44 \times 0.9659 \times 0.9576 \times 50 \times 16} = 0.439 \text{ Wb.}$

11.20 Find the number of series turns required for each phase of a three-phase, star connected 50 Hz, 10 pole alternator with 90 slots. The line voltage is 11 kV and the flux per pole is 0.2 Wb.

Solution

Given, $P = 10$ and $S = 90$

Voltage per phase = $\frac{11,000}{\sqrt{3}} = 6351 \text{ V}$

Also $\phi = 0.2 \text{ Wb}$.

If T is the series turns in each phase, we can write

$$6351 = 4.44 \times 0.2 \times 50 \times T$$

or

$$T = \frac{6351}{4.44 \times 0.2 \times 50} = 143$$

.....

11.21. A 2000 kVA, 11 kV, 50 Hz star connected synchronous generator has a no load voltage of 13 kV. At full load the power factor is 0.8 lagging. Determine the synchronous reactance, voltage regulation, torque angle and power developed. Neglect the armature resistance.

Solution

$$\text{Rated current } I = \frac{2000 \times 10^3}{\sqrt{3} \times 11 \times 10^3} \text{ A} = 105 \text{ A}$$

$$\text{Power factor } (\cos \theta) = 0.8 \text{ i.e., } \theta = \cos^{-1} 0.8 = 36.87^\circ$$

$$\text{No load voltage per phase } E = \frac{13,000}{\sqrt{3}} \text{ V} = 7505.8 \text{ V}$$

$$\text{Full load voltage per phase } V = \frac{11,000}{\sqrt{3}} \text{ V} = 6351 \text{ V}$$

If X_s be the synchronous reactance then

$$7505.8 \angle \delta = 6351 \angle 0^\circ + j105 \angle -36.87^\circ X_s$$

Equating the real and imaginary terms,

$$7505.8 \cos \delta = 6351 \angle 0^\circ + 105 \sin 36.87^\circ X_s = 6351 + 63 X_s \quad (i)$$

$$\text{and } 7505.8 \sin \delta = 105 \cos 36.87^\circ X_s = 84 X_s \quad (ii)$$

Squaring equations (i) and (ii) and then adding them

$$(7505.8)^2 = (6351)^2 + 2 \times 6351 \times 63 X_s + (63)^2 X_s^2 + (84)^2 X_s^2$$

$$\text{or } 11025 X_s^2 + 800226 X_s - 16001832 = 0$$

$$\text{or } X_s = 1.857 \Omega$$

$$\text{Voltage regulation} = \frac{13-11}{11} \times 100 = 18.18\%$$

Now, from equation (ii) we can write

$$\sin \delta = \frac{84 \times 1.806}{7505.8} = 0.0208$$

$$\therefore \text{Torque angle } (\delta) = 1.19^\circ$$

$$\text{Power developed } P = \sqrt{3} VI \cos \theta = \sqrt{3} \times 11 \times 105 \times 0.8 \text{ kW} = 1600 \text{ kW}.$$

.....

11.22. A three-phase alternator has reactance of 8Ω and armature current of 200 A at unity p.f. when running on 11 kV at constant frequency. If the emf is raised by 20%, input remaining unchanged, find the new value of machine current and power factor.

Solution

When $I = 200 \text{ A}$, $\cos \theta = 1$,

$$E = \frac{11,000}{\sqrt{3}} + j 200 \times 8 = 6549.30 \angle 14.14^\circ \text{ V}$$

New value of emf is given by

$$|E'| = 1.2 \times 6549.30 = 7859.16 \text{ V}$$

8. Derive an expression for power developed as a function of power angle δ for salient pole alternator.
9. Derive an expression for the torque developed in a three-phase cylindrical rotor synchronous motor.
10. Explain the principle of operation of synchronous motor.
11. Explain various methods of starting of a synchronous motor.
12. Compare between an induction motor and synchronous motor.
13. What do you mean by hunting of a synchronous motor? How do you prevent hunting?
14. A three-phase, delta connected, 16-pole, 50 Hz synchronous generator has 144 slots and 10 conductors/slot. Coils are full pitch and the flux/pole is 0.0248 Wb. What is the value of alternator speed and what is the value of no load voltage? [Ans: 1270 V]

$$[Hints: N = \frac{120 f}{P} = 375 \text{ rpm}]$$

$$\text{No. of slots/pole} = \frac{144}{16} = 9$$

$$\therefore m = \text{No. of slots/pole/ph} = 3$$

$$\beta = 180^\circ/9 = 20^\circ$$

$$K_d = \frac{\sin(3 \times 20/2)^\circ}{3 \times \sin(20/2)^\circ} = 0.96; K_p = 1$$

$$Z (\text{no. of conductors}) = \frac{144 \times 10}{3} = 480/\text{ph.}$$

$$\therefore E = 4.44 \times 0.96 \times 1.0 \times 0.0248 \times 50 \times \frac{480}{2} \left(\because T = \frac{Z}{2} \right)$$

$$= 1268.5 \text{ V/ph.}$$

$$\text{Hence } E_{L-L} = E_{ph} = 1270 \text{ V.}]$$

15. A 500 V, 50 kVA, 1-ph, 50 Hz, synchronous generator has armature resistance of $0.5 \Omega/\text{ph}$. An excitation current of 10 A produces 100 A armature current in any phase on short circuiting its terminals. At this same exciting currents the open circuit voltage is 400 V. Calculate synchronous reactance.

[Ans: $3.97 \Omega/\text{ph}$]

$$[Hints: Z_s/\text{ph} = \frac{V_{o/c}}{I_{s/c}} = \frac{400}{100} = 4 \Omega]$$

$$\therefore X_s/\text{ph} = \sqrt{Z_s^2 - R^2} = \sqrt{4^2 - 0.5^2} = 3.97 \Omega]$$

16. A single-phase alternator has six number of slots per pole. Obtain the value of distribution factor if (i) all the slots are wound and (ii) only two-third of the slots are wound.

[Ans: 0.64; 0.84]

$$[Hints: (i) \beta = \frac{180^\circ}{6} = 30^\circ, K_d = \frac{\sin\left(6 \times \frac{30^\circ}{2}\right)}{6 \sin\left(\frac{30^\circ}{2}\right)} = 0.64]$$

$$(ii) \beta = 30^\circ; m = \frac{2}{3} \text{ of } 6 = 4$$

$$\therefore K_d = \frac{\sin\left(4 \times \frac{30^\circ}{2}\right)}{4 \sin\left(\frac{30^\circ}{2}\right)} = 0.84.]$$

17. A Δ -connected, 3 ph, 50 Hz, 8000 V(L-L), 750 rpm alternator has 3 slots/pole/ph. Coil span is 7 slots. There are 10 turns/coil. Find the coil span, distribution factor and flux/pole. [Ans: 140° ; 0.94; 333 mWb]

[Hints: Pole pitch has $3 \times 3 = 9$ slots.]

$$\therefore \text{Coil span} = \frac{7}{9} \times 180^\circ = 140^\circ$$

$$K_C = \cos \frac{180^\circ - 140^\circ}{2} = 0.94$$

$$m = 3 \text{ (given); } \beta = \frac{180}{9} = 20^\circ$$

$$\therefore K_d = \frac{\sin\left(3 \times \frac{20^\circ}{2}\right)}{3 \sin \frac{20^\circ}{2}} = 0.96$$

$$\therefore E = 4.44 \phi K_C K_d f T$$

$$\text{Hence } \phi = \frac{E}{4.44 \phi K_C K_d f T} = \frac{8000}{4.44 \times 0.94 \times 0.96 \times 50 \times T}$$

$$\text{where } T = \text{No. of poles} \times \text{No. of slots/pole/ph} \times (\text{No. of turns/coil}) \div 2$$

$$= 8 \times 3 \times 10/2 = 120$$

$$\text{Thus, } \phi = 333 \text{ mWb.}]$$

18. A three-phase, 16 pole synchronous generator has a resultant air gap flux of 0.06 Wb per pole. The flux is distributed sinusoidally over the pole. The stator has two slots per pole per phase and four conductors per slot are accommodated in two layers. The coil span is 150° electrical. Calculate the phase and line induced voltages when the machine runs at 375 rpm.

$$[\text{Ans: } 795.3 \text{ V, } 1377.5 \text{ V}]$$

19. A three-phase star connected alternator is rated at 1600 kVA, 13.5 kV. The armature effective resistance and synchronous reactance are 1.5Ω and 30Ω respectively per phase. Determine the percentage regulation for a load of 1280 kW at p.f. of 0.8 leading.

$$[\text{Ans: } -12\%]$$

20. A 550 V, 55 kVA, 1 - ϕ alternator has dc resistance of 0.2Ω per phase. A field current of 10 A produces an armature current of 200 A on short circuit and 450 V on open circuit. Determine the synchronous reactance of the alternator armature winding and voltage regulation at full load with 0.8 p.f. (lag) load.

$$[\text{Ans: } 2.24 \Omega; 30.91\%]$$

$$[\text{Hints: } I = \frac{55 \times 10^3}{550} = 100 \text{ A}]$$

$$Z_s = \frac{V_{o/c}}{I_{s/c}} = \frac{450}{200} = 2.25 \Omega/\text{ph}$$



SINGLE-PHASE INDUCTION MOTORS

12.1 INTRODUCTION

Single-phase induction motors have numerous and diversified applications both in home and industry. It is probably safe to say that single-phase induction motor applications far outweigh the three-phase motor applications in the domestic sector. At home normally only single-phase power is provided, since power was originally generated and distributed to provide lighting. For this reason early motor-driven appliances in the home depended on the development of the single-phase motor. Single-phase induction motors are usually small sized motors of fractional kilowatt rating. They find wide applications in fans, washing machines, refrigerators, pumps, toys, hair dryers, etc. Single-phase induction motors operate at low power factors and are less efficient than three-phase induction motors.

12.2 PRODUCTION OF TORQUE

From the study of three-phase induction motors it is seen that the three-phase distributed stator winding sets up a rotating magnetic field which is fairly constant in magnitude and rotates at synchronous speed. In single-phase induction motor there is only single field winding excited with alternating current and therefore it is not inherently self-starting since it does not have a true revolving field. Various methods have been devised to initiate rotation of the squirrel cage rotor and the particular method employed to start the rotor of single phase motor will designate the specific type of motor.

Consider the behaviour of the magnetic field set up by an ac current in the single-phase winding. With reference to Fig. 12.1 when the current is flowing in the field winding, if the current is sinusoidal, neglecting the saturation effects of the magnetic iron circuit, the flux through the armature will vary sinusoidally with time. The magnetic field created at a particular instant of time, will reverse during the next half cycle of the ac supply voltage. Since the flux is pulsating it will induce currents in the rotor bars which in turn will create a rotor flux which

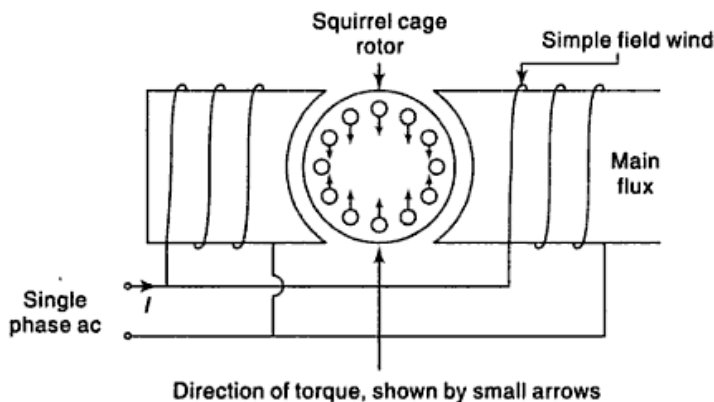


Fig. 12.1 Torque produced in the squirrel cage of a single-phase induction motor

by Lenz's law opposes that of the main field. The direction of the rotor current as well as the torque created can also be determined. It is apparent that the clockwise torque produced is counteracted by the counter-clockwise torque and so no motion results, i.e. the motor is at standstill.

However, any pulsating field can be resolved into two components, equal in magnitude but oppositely rotating phasors as shown in Fig. 12.2(a). The maximum value of the component fields equals half of the main field. A physical interpretation of the two oppositely rotating field components is predicted in Fig. 12.2(b). Each component field guides around the air gap in opposite directions with equal velocities, their instantaneous sum represents the instantaneous resultant magnetic field which changes from (ϕ_{\max}) to (ϕ_{\min}) . This method of field analysis is commonly known as the *double revolving field theory*. Each field component acts independently on the rotor and in a similar fashion as of the rotating field in a three-phase induction motor. The only difference is that here there are two fields, one tending to rotate the rotor clockwise and the other tending to rotate the rotor anticlockwise.

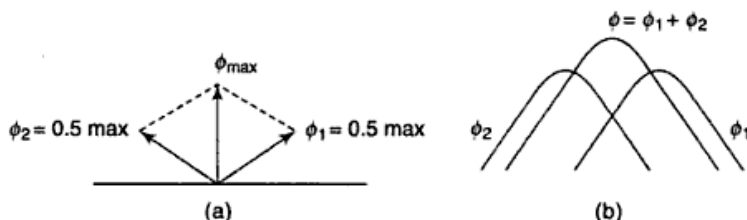


Fig. 12.2 Pulsating field resolved into two oppositely rotating fields

The torque slip curve of the actual motor can be obtained by applying the principle of superposition to the hypothetical constituent motor. The clockwise flux component produces torque called the *forward torque* which is operating at slip " s ". The counterclockwise flux component produces a backward torque which operates at slip $(2-s)$. Their individual torque slip curves will have the form shown in Fig. 12.3 and the algebraic sum of their ordinates will give the resultant

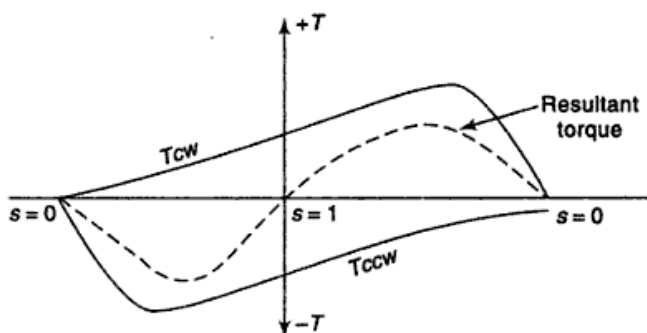


Fig. 12.3 Torque-speed characteristic of a single-phase squirrel cage induction motor

torque. It is observed that at standstill ($s = 1$) the two torque components produced are equal but acting in opposite direction. Although the net torque produced at standstill is zero, it is seen that if the rotor is advanced in either direction, a net torque will result and the rotor will continue to rotate in the direction in which it has been started. The component torque in the direction of rotation may be termed as forward torque while the other one may be treated as the backward torque.

Thus, once started the single-phase motor having a simple winding will continue to run in the direction in which it is started. The manual self-starting is not a desirable feature in practice, and modifications are introduced to obtain the torque required to start. To accomplish this, a quadrature flux component in time and space with the stator flux must be provided at standstill. *Auxiliary windings* are normally placed on the stator to provide starting torque. The auxiliary winding is also called *starting winding*.

12.3 EQUIVALENT CIRCUIT OF A SINGLE-PHASE INDUCTION MOTOR

At standstill the equivalent circuit of a single-phase induction motor is exactly similar to that of a transformer on short circuit. The equivalent circuit at standstill condition is shown in Fig. 12.4. R_c and X_ϕ represent the core loss and magnetizing reactance. r_1 and x_1 are the resistance and leakage reactance of the stator, r_2' and x_2' are the resistance and leakage reactance of the rotor referred to the stator.

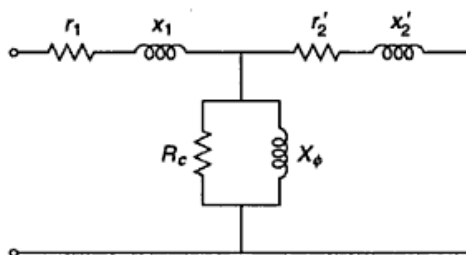


Fig. 12.4 Equivalent circuit of a single-phase induction motor at standstill

The air-gap flux can be resolved into two oppositely rotating components. These components at standstill are equal in magnitude, each one contributing an equal share to the resistive and reactive voltage drops in the rotor circuit. Hence r_2 and x_2 can be split into two parts, each one corresponding to the effects of one of the magnetic fields. E_f and E_b are the voltages set up by the two oppositely rotating fields, viz. *forward* and *backward* rotating fields respectively. The equivalent circuit considering the effect of forward and backward flux component is shown in Fig. 12.5.

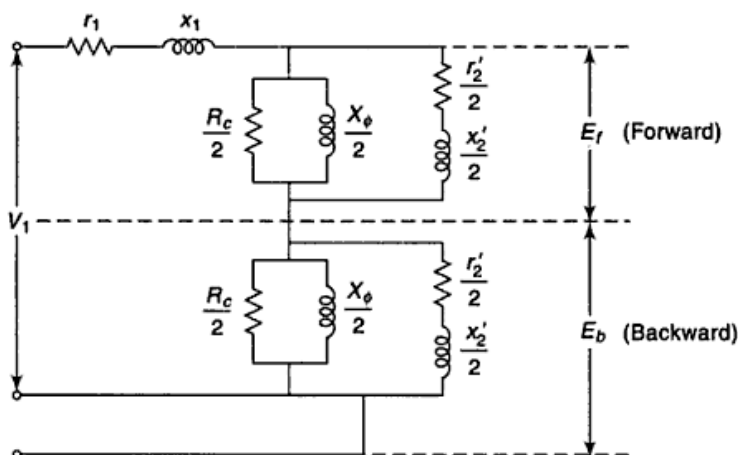


Fig. 12.5 Equivalent circuit at standstill showing the effect of forward and backward flux components

When the motor is running at a slip s , the slip for the forward field is s and for backward field is $(2 - s)$. Hence the resistance in the forward field becomes $\left(\frac{r_2'}{2s}\right)$ and in the backward field becomes $\left(\frac{r_2'}{2(2-s)}\right)$. As s is normally very small, $\left(\frac{r_2'}{2s}\right)$ is much higher than $\left(\frac{r_2'}{2(2-s)}\right)$. Hence E_f is much greater than E_b .

The equivalent circuit at any slip (s) is shown in Fig. 12.6.

From Fig. 12.6

$$P_{gf} = \text{air-gap power of forward field} = (I_{2f}')^2 \frac{r_2'}{2s} W$$

$$P_{gb} = \text{air-gap power of backward field} = (I_{2b}')^2 \frac{r_2'}{2(2-s)} W$$

$$T_f = \text{torque due to forward field} = \frac{P_{gf}}{2\pi n_s} \text{ Nm}$$

$$T_b = \text{torque due to backward field} = \frac{P_{gb}}{2\pi n_s} \text{ Nm}$$

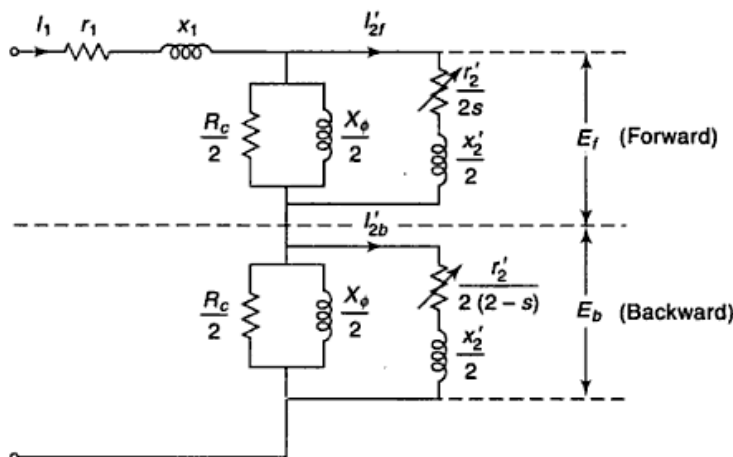


Fig. 12.6 Equivalent circuit of a single-phase induction motor at any slip s

Net torque, $T = T_f - T_b$

Rotor copper loss due to forward field $(P_{\text{cu(rot.)f}}) = sP_{gf}$

Rotor copper loss due to backward field $(P_{\text{cu(rot.)b}}) = (2-s)P_{gb}$

Total rotor copper loss $(P_{\text{cu(rot.)}}) = sP_{gf} + (2-s)P_{gb}$

Mechanical power developed $(= P_m) = (1-s)(P_{gf} - P_{gb})$.

12.4 DETERMINATION OF PARAMETERS OF EQUIVALENT CIRCUIT

The parameters of the equivalent circuit of a single-phase induction motor can be determined from the *no load* and *blocked rotor* test.

12.4.1 Blocked Rotor Test

In this test a very small voltage is applied to the stator and the rotor is blocked (Care is to be taken such that the stator current does not exceed the f.l. current). The voltage, current and power input to the stator are measured. When the rotor is blocked, $s = 1$ and hence parallel combination $\left(\frac{R_c}{2}\right)$ and $\left(\frac{X_\phi}{2}\right)$ is much

greater than $\left[\frac{r'_2}{2} + j\frac{x'_2}{2}\right]$ (in Fig. 12.6). Therefore under blocked rotor test the equivalent circuit reduces to that shown in Fig. 12.7. Since $(R_c/2)$ and $(X_\phi/2)$ are of very high values hence they can be neglected in the equivalent circuit.

Let V_{sc} , I_{sc} and W_{sc} be the input voltage, current and power during blocked rotor test.

The total resistance $(r_1 + r'_2) = \frac{W_{sc}}{I_{sc}^2} = R_{sc}$

Total impedance, $Z_{sc} = \frac{V_{sc}}{I_{sc}}$

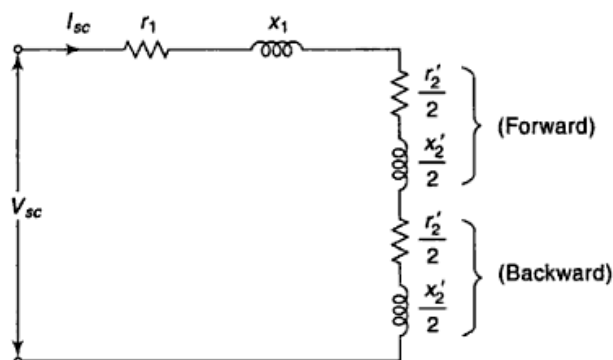


Fig. 12.7 Equivalent circuit under blocked rotor condition

Hence total reactance $(x_1 + x'_2) = \sqrt{Z_{sc}^2 - R_{sc}^2}$

Generally, $r_1 = r'_2$ and $x_1 = x'_2$. Hence r_1 , r'_2 , x_1 and x'_2 can be determined from this test.

12.4.2 No Load Test

In this test the motor is run on no load condition and voltage V_o , current I_o and power W_o to the stator are measured. At no load s is very small and core loss

resistance R_c is neglected. Hence from Fig. 12.6, $\left(\frac{r'_2}{s}\right)$ is much greater than

$\left(\frac{X_\phi}{2}\right)$. Also, $\frac{r'_2}{2(2-s)} \left(\approx \frac{r'_2}{4}\right)$ is much smaller than $X_\phi/2$. Therefore under no load condition the equivalent circuit can be reduced to that shown in Fig. 12.8.

Here, $\left(\frac{r'_2}{s}\right)$ and $\left(\frac{X_\phi}{2}\right)$ are thus neglected in equivalent circuit.

$$\text{No load p.f. } (\cos \theta_0) = \frac{W_o}{V_o I_o}$$

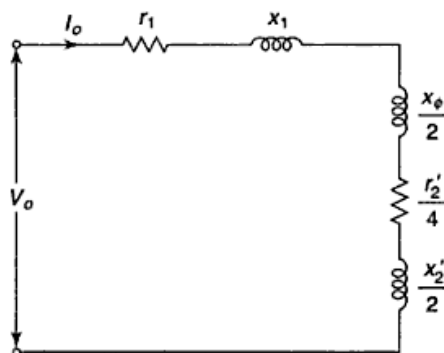


Fig. 12.8 Equivalent circuit under no load condition

Now voltage across $\left(\frac{X_\phi}{2}\right)$ is $\left[V_o - I_o \angle -\theta_o \left\{ \left(r_1 + \frac{r_2'}{4}\right) + j\left(x_1 + \frac{x_2'}{2}\right) \right\}\right]$

$$\text{Hence, } \frac{X_\phi}{2} = \frac{V_o - I_o \angle -\theta_o \left[\left(r_1 + \frac{r_2'}{4}\right) + j\left(x_1 + \frac{x_2'}{2}\right) \right]}{I_o}$$

and X_ϕ can thus be determined.

12.1 A 200 W, 240 V, 50 Hz single phase induction motor runs on rated load with a slip of 0.05 p.u. The parameters are

$$r_1 = 11.4 \, \Omega, x_1 = 14.5 \, \Omega,$$

$$r_2' = 13.8 \, \Omega, x_2' = 14.4 \, \Omega, X_\phi = 270 \, \Omega$$

Calculate (i) power factor, (ii) input power and (iii) efficiency.

Solution

From Fig. 12.6 neglecting the core loss resistance R_c the total series impedance

$$\begin{aligned} Z &= r_1 + jx_1 + \frac{j\frac{X_\phi}{2} \left(\frac{r_2'}{2s} + j\frac{x_2'}{2} \right)}{\frac{r_2'}{2s} + j\left(\frac{X_\phi}{2} + \frac{x_2'}{2} \right)} + \frac{j\frac{X_\phi}{2} \left(\frac{r_2'}{2(2-s)} + j\frac{x_2'}{2} \right)}{\frac{r_2'}{2(2-s)} + j\left(\frac{X_\phi}{2} + \frac{x_2'}{2} \right)} \\ &= 11.4 + j14.5 + \frac{-\frac{270 \times 14.4}{4} + j\frac{270 \times 13.8}{4 \times 0.05}}{\frac{13.8}{2 \times 0.05} + j\left(\frac{270}{2} + \frac{14.4}{2} \right)} + \frac{-\frac{270 \times 14.4}{4} + j\frac{270 \times 13.8}{4(2-0.05)}}{\frac{13.8}{2(2-0.05)} + j\frac{270 + 14.4}{2}} \\ &= 11.4 + j14.5 + \frac{-972 + j18630}{138 + j142.2} + \frac{-972 + j477.69}{3.538 + j142.2} \\ &= 11.4 + j14.5 + \frac{18655 \angle 92.98^\circ}{198 \angle 45.86^\circ} + \frac{1083 \angle 153.83^\circ}{142.24 \angle 88.57^\circ} \\ &= 11.4 + j14.5 + 94.22 \angle 47.12^\circ + 7.6 \angle 65.25^\circ \\ &= (11.4 + 64.11 + 3.18) + j(14.5 + 69 + 6.9) = (78.69 + j90.4) \, \Omega. \end{aligned}$$

$$\therefore \text{Input current} = \frac{240 \angle 0^\circ}{78.69 + j90.4} = \frac{240 \angle 0^\circ}{119.85 \angle 48.96^\circ} = 2 \angle -48.96^\circ \, \text{A}$$

Hence power factor is $(\cos 48.96^\circ)$ lagging, i.e. 0.656 lagging.

Input power = $240 \times 2 \times 0.656 \, \text{W}$, i.e. 314.88 W.

Output power is 200 W.

$$\text{Hence efficiency} = \frac{\text{Output}}{\text{Input}} = \frac{200}{314.88} = 0.635, \text{ i.e. } 63.5\%.$$

.....

12.2 A 230 V, 50 Hz, 4-pole single-phase induction motor has the following parameters:

$$r_1 = 2.51 \, \Omega, x_1 = 4.62 \, \Omega, r_2' = 7.81 \, \Omega, x_2' = 4.62 \, \Omega$$

and $X_\phi = 150.88 \, \Omega$

Determine the stator main winding current and power factor when the motor is running at a slip of 0.05.

Solution

The total series impedance is obtained as

$$\begin{aligned}
 Z &= 2.51 + j4.62 + \frac{j \frac{150.88}{2} \left(\frac{7.81}{2 \times 0.05} + j \frac{4.62}{2} \right)}{\frac{7.81}{2 \times 0.05} + j \left(\frac{4.62}{2} + \frac{150.88}{2} \right)} + \frac{j \frac{150.88}{2} \left\{ \frac{7.81}{2(2-0.05)} + j \frac{4.62}{2} \right\}}{\frac{7.81}{2(2-0.05)} + j \left(\frac{150.88}{2} + \frac{4.62}{2} \right)} \\
 &= 2.51 + j4.62 + \frac{-174.26 + j5891.86}{78.1 + j77.75} + \frac{-174.26 + j151.07}{2 + j77.75} \\
 &= 2.51 + j4.62 + \frac{5894.40 \angle 91.69^\circ}{110.20 \angle 44.87^\circ} + \frac{230.62 \angle 139.07^\circ}{77.77 \angle 88.50^\circ} \\
 &= 2.51 + j4.62 + 53.48 \angle 46.82^\circ + 2.965 \angle 50.58^\circ \\
 &= (2.51 + 36.596 + 1.88) + j(4.62 + 39 + 2.3) \\
 &= 40.986 + j45.92 = 61.54 \angle 48.25^\circ \Omega
 \end{aligned}$$

Stator main winding current is $\frac{230 \angle 0^\circ}{61.54 \angle 48.25^\circ}$ i.e. $3.73 \angle -48.25^\circ$ A.

Hence power factor is $(\cos 48.25^\circ)$ i.e. 0.666 lagging.

.....

12.3 In a 6-pole single-phase induction motor the gross power absorbed by the forward and backward fields are 160 W and 20 W respectively. If the motor speed is 950 rpm and the no load frictional loss is 75 W, find the shaft torque.

Solution

Air-gap power of forward field $P_{gf} = 160$ W

Air-gap power of backward field $P_{gb} = 20$ W.

Net power $= P_{gf} - P_{gb} = 160$ W $- 20$ W $= 140$ W.

Synchronous speed $N_s = \frac{120 \times 50}{6} = 1000$ rpm.

Speed of motor $N_r = 950$ rpm.

Hence slip $s = \frac{1000 - 950}{1000} = 0.05$.

Power output is $(1 - s) \times 140 - 75 = 58$ W (= shaft power).

Shaft torque $= \frac{\text{shaft power}}{2\pi \times \frac{950}{60}} = \frac{58}{2\pi \times \frac{95}{6}} = 0.58$ Nm.

.....

12.5 STARTING OF SINGLE-PHASE INDUCTION MOTORS

Since a single-phase induction motor does not have a starting torque, it needs special methods of starting. The stator is provided with two windings, called *main* and *auxiliary windings*, whose axes are space displaced by 90 electrical degrees. The auxiliary winding is excited by a current which is out of phase with the current in the main winding, both currents derived from the same supply. If the phase difference between the two currents is 90° and the mmfs created by them are equal, maximum starting torque is produced. If the phase difference is

not 90° and the mmfs are equal, the starting torque will be small, but in many applications it is still sufficient to start the motor. The auxiliary winding may be disconnected by a centrifugal switch after the motor has achieved about 75% speed.

Single-phase induction motors are usually classified according to the auxiliary means used to start the motors. They are classified as follows:

1. Split-phase motor
2. Capacitor start motor
3. Capacitor start capacitor run motor
4. Shaded pole motor.

12.6 SPLIT PHASE INDUCTION MOTORS

One of the most widely used types of single-phase motors is the *split phase* induction motor. Its service includes a wide variety of applications such as refrigerators, washing machines, portable hoists, small machine tools, blowers, fan, centrifugal pumps, etc.

The essential parts of the split phase motor is shown in Fig. 12.9(a). It shows the auxiliary winding, also called the starting winding, in space quadrature, i.e. 90° electrical degrees displacement with the main stator winding. The rotor is normally of squirrel cage type. The two stator windings are connected in parallel

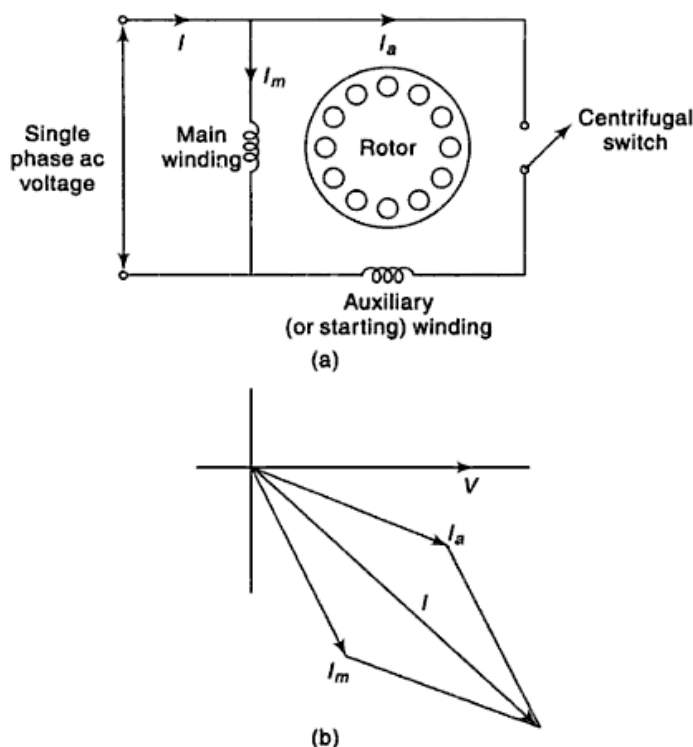


Fig. 12.9 Split phase motor (a) Schematic representation (b) Phasor diagram

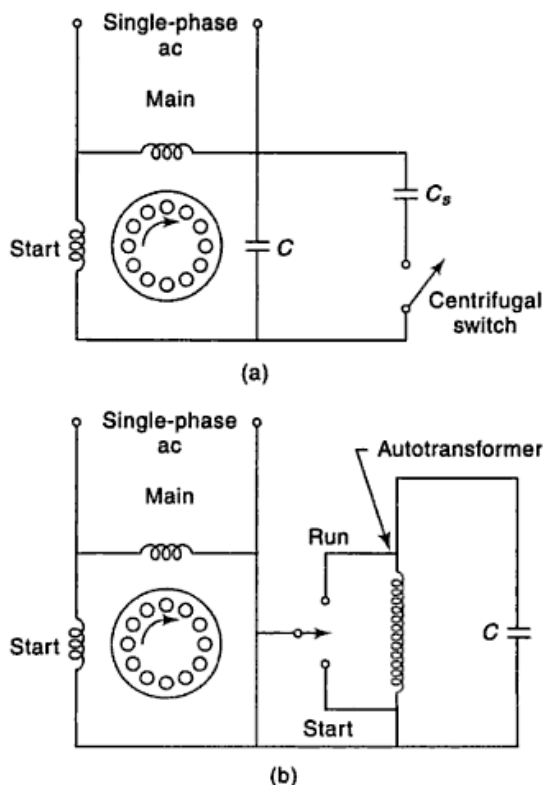


Fig. 12.12 Capacitor start capacitor run motor

classified as a reversible type motor. These motors are manufactured in a number of sizes from 1/8 to 3/4 hp and are used in compressors, conveyors, pumps and other high torque loads.

12.4 A 220 V single-phase induction motor gave the following test results:

Blocked rotor test: 100 V, 9 A, 380 W

No load test: 220 V, 5 A, 120 W

Find the parameters of the equivalent circuit neglecting the core loss resistance. Also find the iron, friction and windage loss.

Solution

From Art. 12.4.1

$$r_1 + r_2' = \frac{380}{9^2} \Omega = 4.69 \Omega;$$

$$Z_{sc} \left(= \frac{V_{sc}}{I_{sc}} \right) = \frac{100}{9} = 11.11 \Omega$$

Hence $x_1 + x_2' = \sqrt{(11.11)^2 - (4.69)^2} = 10 \Omega,$

$$r_1 = r_2' = \frac{4.69}{2} = 2.345 \Omega \text{ and}$$

$$x_1 = x_2' = \frac{10}{2} = 5 \Omega.$$

12.9 SHADED POLE MOTORS

Like any other induction motor, the *shaded pole* motor is caused to run by the action of the magnetic field set up by the stator windings. There is, however, one extremely important difference between the poly phase induction motor and the single-phase induction motor discussed so far. As discussed, these motors have a truly rotating magnetic field, either circular, as in three-phase machine, or of elliptical shape as encountered in most of the single-phase motors. In the shaded pole motor the field merely shifts from one side of the pole to the other. In other words, it does not have a rotating field but one that sweeps across the pole faces.

An elementary understanding of how the magnetic field is created may be gained from the simple circuit in Fig. 12.13, illustrating the shaded pole motor. As can be seen, the poles are divided into two parts, one of which is “shaded”, i.e., around the smaller of the two areas formed by a slot cut across the laminations, a heavy copper short circuited ring, called the *shading coil*, is placed. That part of the iron around which the *shading coil* is placed is called the shaded part of the pole. When the excitation winding is connected to an ac source, the magnetic field will sweep across the pole face from the unshaded to the shaded portion. This, in effect is equivalent to an actual physical motion of the pole, the result is that the squirrel cage rotor will rotate in the same direction.

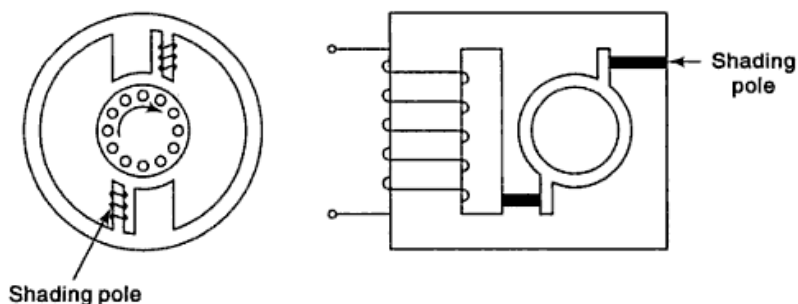


Fig. 12.13 Shaded pole motor

To understand how this sweeping action of the field across the pole face occurs, let us consider the instant of time when the current flowing in the excitation winding is starting to increase positively from zero, as illustrated in Fig. 12.14(a). In the unshaded part of the pole the flux will start to build up in phase with the current. Similarly, the flux ϕ , in the shaded portion of the pole will build up, but this flux change induces a voltage in the shading coil which causes current to flow. By Lenz's law, this current flows in such a direction as to oppose the flux change that induces it. Thus the building up of flux ϕ , in the shaded portion is delayed. It has the overall effect of shifting the axis of the resultant magnetic flux into the unshaded portion of the pole. When the current in the excitation coil is at or near the maximum value as indicated in Fig. 12.14(b), the flux does not change appreciably. With an almost constant flux, no voltage is induced in the shading coil and therefore it, in turn, does not influence the total flux. The result is that the resulting magnetic flux shifts to the centre of the pole.

Simple motors of this type cannot be reversed but must be assembled so that the rotor shaft extends from the correct end in order to drive the load in the proper direction. There are specially designed shaded pole motors which are reversible. One form of design is to use two main windings and a shading coil. For one direction of rotation one main winding is used and for the opposite rotation the other; such an arrangement is adaptable only to distributed windings, hence this necessitates a slotted stator.

Another method employed is to use two sets of open circuited shading coils, one set placed on each side of the pole. A switch is provided to short circuit either the shading coil, depending on the rotational direction desired offsetting the simple construction and a low cost of this motor. This motor has a low starting torque, little overload capacity and low efficiencies (5 to 35%).

These motors are built in sizes ranging from 1/250 hp upto about 1/20 hp. Typical applications of shaded pole motors are where efficiencies are of minor concern such as in toys and fans.

■ EXERCISES ■

1. A three-phase induction motor develops a starting torque, but a single phase induction motor does not. Why?
2. Explain the operation of a single-phase induction motor on the basis of double revolving field.
3. Draw and explain a typical torque speed curve of a single phase induction motor on the basis of the double revolving field theory.
4. Discuss the procedure to determine the parameters of equivalent circuit of single-phase induction motor.
5. Draw and explain the equivalent circuit of a single-phase induction motor.
6. Briefly discuss the different methods for starting single phase induction motors.
7. Discuss the differences between capacitor start, capacitor start capacitor run and permanent split capacitor motors.
8. Describe the construction and working principle of a shaded pole motor.
9. Discuss the procedure to determine the parameters of an equivalent circuit of a single-phase induction motor.
10. A 220 V 50 Hz single-phase induction motor gave the following test results:
Blocked rotor test: 110 V, 10 A, 400 W.
No load test: 220 V, 4 A, 100 W.
Find (a) the parameters of equivalent circuit (b) the iron friction and winding losses. [Ans: $r_1 = r_2' = 2 \Omega$, $x_1 = x_2' = 5.125 \Omega$, $X_\phi = 88.9 \Omega$, 60 W]
11. A 250 W, 230 V, 50 Hz capacitor motor has the following impedances at standstill:
Main winding: $(7 + j5) \Omega$
Auxiliary winding: $(11.5 + j5) \Omega$
Find the value of the capacitor to be connected in series with the auxiliary winding to give a phase displacement of 90° between the currents in the two windings. [Ans: 156 μF]



ELECTRICAL MEASURING INSTRUMENTS

13.1 INTRODUCTION

Instruments which measure electrical quantities like voltage, current, power, energy etc. are called electrical instruments. These instruments are generally named after the electrical quantity to be measured. The instruments which measure current, voltage, power and energy are called ammeter, voltmeter, wattmeter and energy meter respectively.

13.2 TYPES OF INSTRUMENTS

The following types of electrical instruments which are commonly used:

- (a) Indicating instruments
- (b) Integrating instruments
- (c) Recording instruments

(a) Indicating Instruments

The instruments which directly indicate the instantaneous value of an electrical quantity at the time when it is being measured are called indicating instruments.

Any indicating instrument has a pointer which sweeps over a calibrated scale and it directly gives the magnitude of the electrical quantity. Ammeters, voltmeters and wattmeters are examples of indicating instruments which are commonly used.

(b) Integrating Instruments

The instruments that measure the total quantity of electricity (like ampere-hours or electrical energy in watt-hours) for a given time are called integrating instruments. In such instruments there are sets of dials and pointers which register the total quantity of electricity or electrical energy supplied to the circuit in a given time.

However, the integrating instruments do not indicate the rate at which the quantity of electricity is flowing but only provide the summation of electrical quantity (or energy) being supplied for any given time.

(c) Recording Instruments

The instrument which gives a continuous record of the changes of the electrical quantity to be measured is called a recording instrument.

In recording type of instruments, the moving system usually bears an ink pen which rests on a paper wrapped over a drum. The drum rotates with a slow uniform speed and the motion of the drum is in a direction perpendicular to the direction of the pointer. The path traced out by the pen indicates the changes in the magnitude of electrical quantity under observation over the given time. An Electrocardiogram (ECG) machine is a typical example of these type of instruments.

13.3 WORKING PRINCIPLE OF ELECTRICAL INSTRUMENTS

Since an electrical quantity cannot be observed physically, it is necessary to convert the given electrical quantity into a mechanical force and then measure that force. This mechanical force moves the pointer on a calibrated scale and indicates the value of electrical quantity to be measured. This conversion of electrical quantity under measurement is achieved by utilising the following effects of electrical current:

- | | |
|--------------------------------------|---|
| (a) Magnetic effect | For voltmeters, ammeters and wattmeters. |
| (b) Thermal effect | For ammeters and voltmeters. |
| (c) Electrodynamic effect | For voltmeters, ammeters and wattmeters. |
| (d) Electromagnetic induction effect | For voltmeters, ammeters, wattmeters and energy meters. |
| (e) Chemical effect | For dc ampere hour meter. |

13.4 DIFFERENT TORQUES IN INDICATING INSTRUMENTS

An indicating instrument indicates the value of electrical quantity at the time when it is being measured. It consists of a pointer attached to the moving system pivoted in jewelled bearings which moves over a graduated scale. In order to have the proper operation of indicating instruments, the following torques are essential:

- Deflecting torque (or Operating torque) (T_o)
- Controlling (or Restraining torque) (T_c)
- Damping torque (T_d)

13.4.1 Deflecting Torque (T_o)

The deflecting torque (or operating torque) is an essential requirement of an indicating instrument in order to initiate the movement of the pointer. The

deflecting torque causes the moving system to move from zero position to the required value when the instrument is connected in the circuit to measure the electrical quantity. The deflecting torque is developed by utilising any of the known effects of current (or voltage).

13.4.2 Controlling Torque (T_c)

Once the deflecting torque is developed, the pointer will continue to move and will be independent of the value of electrical quantity to be measured. It is then essential to control the movement of the pointer and this requirement makes that the controlling torque must be provided. The controlling torque opposes the deflecting torque of the moving system so that the pointer comes to the rest position when the two opposing torques are equal. The purpose of providing the controlling torque is three-fold:

- to oppose the deflecting torque and get increased with the deflection of the moving system.
- to make the pointer to come to rest when $T_c = T_d$.
- to bring the pointer back to zero position when the deflecting torque is removed.

13.4.3 Generator of Controlling Torque

The following two methods are commonly used to provide controlling torque in indicating instruments:

- Spring control
- Gravity control

(a) Spring control

This is the most common method of providing controlling torque in electrical instruments. In this method, generally two spiral springs (*P* and *Q*) of phosphor bronze are attached to the moving system, as shown in Fig. 13.1 (springs are wound in the opposite direction of each other to compensate for changes in temperature). One end of each spring is attached to the spindle, while the other end is attached to a fixed point in the instrument. The two springs provide the necessary controlling torque as well as they provide electrical connection to the operating coil.

The moving system is statically balanced in all positions by balance weights and an arrangement, called *zero adjuster*, is provided on the pointer to adjust the zero of the pointer.

When the instrument is not in use, the two springs are in their natural position without any tension or compression and the controlling torque is zero. When the instrument is in the process of measuring of an electrical quantity with production

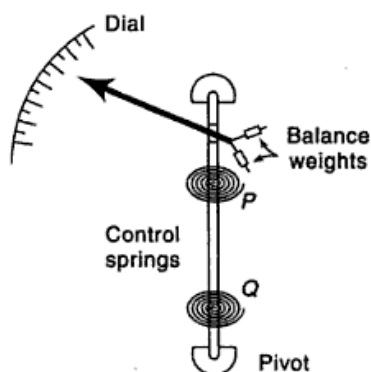


Fig. 13.1 Spring control method of providing controlling torque

of the deflection torque, the pointer moves and one of the springs is unwound while the other gets twisted. The resultant twist in the springs provides the controlling torque. More the deflection, more is the twist and hence greater will be the controlling torque. Hence the controlling torque becomes directly proportional to the deflection θ of the moving system, i.e.

$$T_c \propto \theta$$

The pointer comes to rest at a position when the controlling torque is equal to deflecting torque (i.e. $T_c = T_o$)

Advantages of Spring Control

- It is suitable for portable instrument as it works in any position of the instrument.
- There is practically no increase in the weight of the moving system.

Disadvantages of Spring Control

- Change in temperature may affect the spring length and hence the controlling torque.
- The controlling torque cannot be adjusted normally.

(b) Gravity Control

In this method, a small adjustable weight W (control weight) is attached to the spindle (moving system), as shown in Fig. 13.2. It provides the necessary controlling torque. The controlling torque can be varied by changing the position of weight W on the arm.

In the initial rest (or zero) position of the pointer, the control weight is suspended vertically downwards and, therefore, it does not produce any torque. However, under the action of a deflecting torque, the pointer moves from zero position (from left to right) and the control weight moves in the opposite direction, as shown in Fig. 13.2 (dotted). Due to gravity, the control weight would always try to come to its original position (i.e. vertical) and hence it produces a opposing torque on the moving system. This torque (controlling torque) opposes the deflecting torque and the pointer would come to rest at a position when the magnitude of controlling torque becomes equal to the deflecting torque.

As the pointer gets deflected through an angle θ from its zero position when measuring an electrical quantity, the control weight will also move through an angle θ but in the opposite direction as shown in Fig. 13.3.

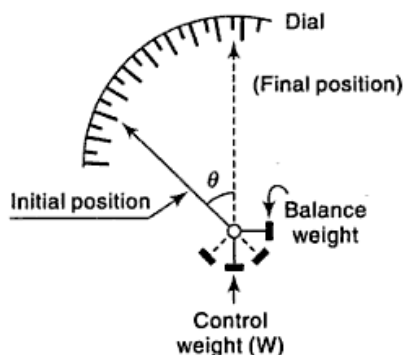


Fig. 13.2 Gravity control method of providing controlling torque

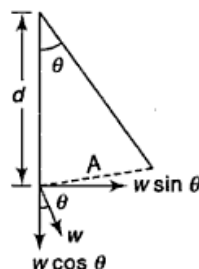


Fig. 13.3 Direction of movement of pointer in gravity control method

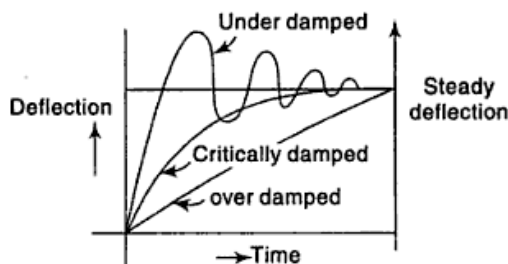


Fig. 13.4 Deflection profile showing underdamping, overdamping and critical damping conditions

13.5.1 Methods of Generating Damping Torque

The following are the common methods employed for providing damping torque:

- (a) Air friction damping
- (b) Eddy current damping

(a) Air Friction Damping

In this method, a light aluminium vane (or a piston) is attached to the spindle and it moves with a small clearance in a rectangular or circular air chamber closed at one end (as shown in Figs 13.5 and 13.6). As the pointer moves forward, the vane comes out of the chamber and a partial vacuum is created in the closed space. The atmospheric pressure then opposes the moving system in its rapid clockwise movement. When the pointer moves backward (i.e. anti-clockwise), the piston is pushed into the air chamber, compressing the air in the closed space. This compressed air tries to push out the piston and thus opposes the movement of the pointer in anti-clockwise direction. In this way, motion (backward or forward) of the pointer is opposed and hence, necessary damping is produced.

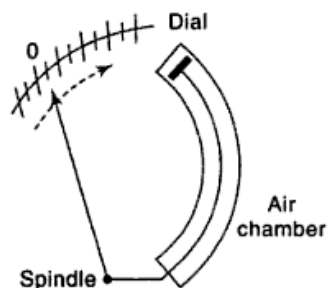


Fig. 13.5 Air friction damping

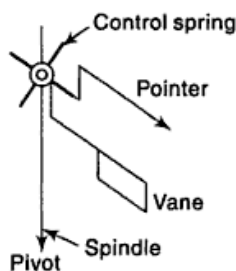


Fig. 13.6 Movement of pointer in air friction damping

(b) Eddy Current Damping

It is one of the most effective and efficient method of damping. We know that when a conducting (but non-magnetic material such as aluminium or copper) disc is rotated in a magnetic field, eddy currents are induced in the disc according to Faraday's laws of electromagnetic induction. These eddy currents counteract with the magnetic field to produce a force which opposes the motion providing the

necessary damping torque. The eddy currents and hence the damping torque exists as long as the moving system is in motion.

Figure 13.7(a) shows a form of eddy current damping. A thin aluminium disc is attached to the spindle and is allowed to rotate horizontally in the air gap of a permanent magnet. When the pointer (or the spindle) moves, the aluminium disc also moves and cuts the magnetic lines of force produced by the permanent magnet. This induces eddy currents that produces a force opposing the motion of the disc.

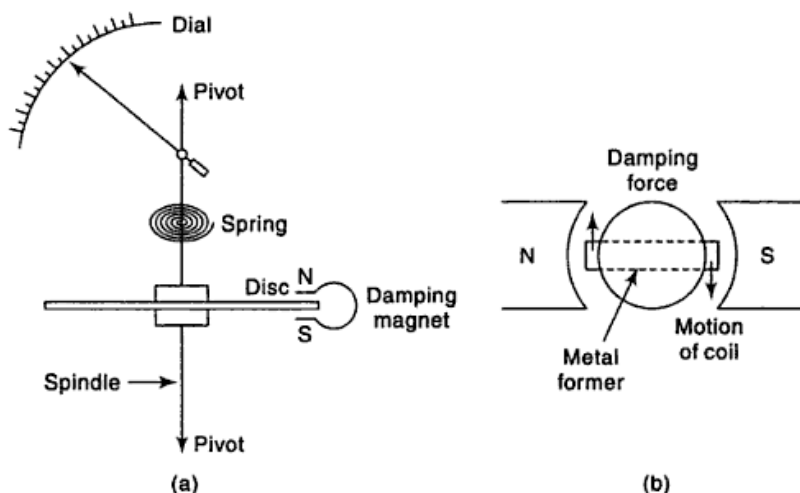


Fig. 13.7 Eddy current damping

In Fig. 13.7(b), the operating coil (coil which produces deflecting torque) is wound on an aluminium former. When the coil moves in the field of the permanent magnet, eddy currents are induced in the aluminium former, providing the necessary damping torque.

13.6 TYPES OF INDICATING INSTRUMENTS

The following types of instruments are commonly used:

- (a) Moving iron (MI) instruments.
- (b) Moving coil (MC) instruments.
- (c) Dynamometer instruments.
- (d) Electrostatic instruments.
- (e) Induction instruments.

13.6.1 Moving Iron Instruments

These instruments are reasonably accurate, cheaper and simple in construction. These instruments are widely used in laboratories and on electric panel boards. Moving iron instruments are usually used either as ammeters or voltmeters.

Moving iron instruments are of two types:

1. Attraction type
2. Repulsion type.

Attraction type Moving Iron Instruments

Principle The operation of these instruments are based on the following principle when an unmagnetised soft iron piece is placed in the magnetic field of a coil, the piece is attracted towards the coil. The moving system of the instrument is attached to a soft iron piece and the operating current is passed through a coil placed adjacent to it. The operating current sets up a magnetic field which attracts the iron piece and thus creates deflecting torque in the pointer to move over the scale.

Construction It consists of a hollow cylindrical coil (or solenoid) that is kept fixed (as shown in Fig. 13.8). An oval shaped soft iron piece is attached to the spindle in such a way that it can move in or out of the coil. The pointer is attached to the spindle so that it is deflected with the motion of the soft iron piece. The controlling torque on the moving system is usually provided by spring control method while damping is provided by air friction.

Working Principle When the instrument is connected in the circuit, the operating current flows through the coil. This current sets up a magnetic field in the coil. The coil then behaves like a magnet and it attracts the soft iron piece towards it. The pointer attached to the moving system moves from zero position across the dial.

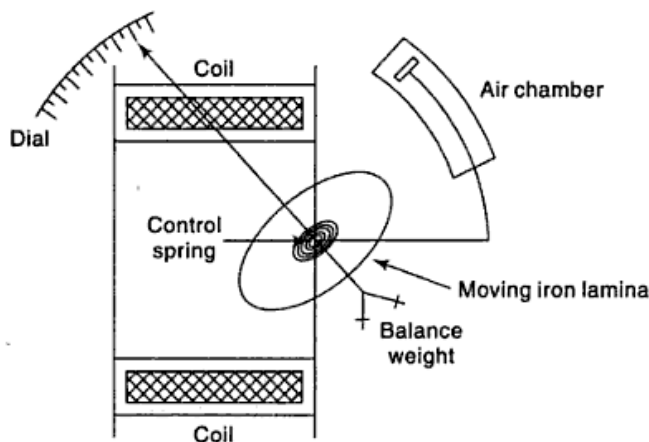


Fig. 13.8 Attraction type moving iron instruments

If current in the coil is reversed, the direction of magnetic field also reverses and so does the magnetism produced in soft iron piece. Hence the direction of deflecting torque remains unchanged. Therefore, such instruments can be used both for dc as well as ac measurement of current and voltage.

The force F pulling the soft iron piece towards the coil depends upon:

- The field strength H produced by the coil.
- The pole strength M developed by the iron piece

i.e. $F \propto MH$

$\therefore F \propto H^2$ ($\because M \propto H$)

Thus, deflecting torque (T_d) $\propto F \propto H^2$

If the permeability of iron is assumed to be constant, $H \propto I$

$$\therefore T_o \propto I^2$$

Since the controlling torque is provided by the springs, $T_c \propto \theta$ (deflection), and in the steady position of deflection,

$$T_o = T_c$$

$$\therefore \theta \propto I^2 \text{ (for dc)}$$

$$\text{and } \theta \propto I_{\text{rms}}^2 \text{ (for ac).}$$

Since the deflection $\theta \propto I^2$, hence scale of such instruments is non-uniform (being crowded in the beginning).

Repulsion type Moving Iron Instruments

Principle These instruments are based on the principle of repulsion between the two iron pieces magnetised with same polarity.

Construction Any repulsion instrument consists of a fixed cylindrical hollow coil that carries the operating current (Fig. 13.9). Inside the coil, there are two soft iron pieces of vanes, one of which is fixed and other is movable. The fixed iron vane is attached to the coil whereas the movable vane is attached to the spindle. Under the action of deflection torque, the pointer attached to the spindle moves over the scale.

The controlling torque is produced by spring control method and damping torque is provided by air friction damping in repulsion type of instruments.

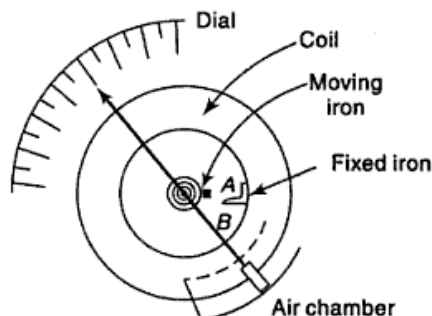


Fig. 13.9 Repulsion type moving iron instruments

Working Principle When the instrument is connected in a circuit and current is flowing through the circuit, current sets up a magnetic field in the coil within the instrument. The magnetic field magnetises both the iron vanes in the same direction (i.e. both pieces become magnets with the same polarity) they repel each other. Due to this force of repulsion, only movable iron vane can move as the other piece is fixed and cannot move. The result is that the pointer attached to the spindle moves from zero position.

If current in the coil is reversed, the direction of deflection torque remains unchanged. This is because both iron vanes are in the same magnetic field and so they will be magnetized similarly and consequently repel each other irrespective of the direction of magnetic field. Hence, such instruments can be used both for ac and dc measurements.

The deflection torque is generated due to the repulsion between the similarly charged iron pieces. If the two pieces develop pole strengths M_1 and M_2 respectively, we can write

$$\text{Instantaneous deflecting torque } (\propto \text{repulsive force}) \propto M_1 M_2$$

or Instantaneous deflecting torque, $T_o \propto H^2$ [Since pole strength developed are proportional to H .]

Assuming constant permeability of iron, $H \propto$ current through the coil.

\therefore Instantaneous deflecting torque, $T_o \propto i^2$

However, controlling torque provided by springs $T_c \propto \theta$.

\therefore In the steady position of deflection, when $T_o = T_c$,

$$\theta \propto i^2$$

i.e. $\theta \propto I^2$ (for dc)

$$\propto I_{\text{rms}}^2 \text{ (for ac)}$$

Since deflection θ is proportional to I^2 , therefore scale of such instruments is non-uniform (being crowded in the beginning). Scale of such instruments may be made uniform by using tongue shaped iron vanes.

13.6.2 Advantages and Disadvantages of Moving Iron Instruments

The moving iron instruments have the following advantages:

- (a) These are cheap, robust and simple in construction.
- (b) The instruments can be used for both ac as well as dc circuits.
- (c) These instruments have a high operating torque.
- (d) These instruments are reasonably accurate.

The following are the disadvantages of moving iron instruments:

- (a) These instruments have non-uniform scale.
- (b) These instruments are less sensitive to changes of operating variables.
- (c) Errors are introduced due to change in frequency in case of ac measurement.
- (d) Power consumption of these instruments are relatively higher.

13.6.3 Errors in Moving Iron Instruments

The errors which may occur in moving iron instruments can be divided into two categories:

- (a) Errors with both dc and ac measurement.
- (b) Errors with ac measurement only.

Errors with both dc and ac Measurement

(i) **Errors due to Hysteresis** Since the iron parts move in the magnetic field, hysteresis loss occurs in them. The effect of this error will result in higher readings when current increases than when it decreases. The hysteresis error can be eliminated by using "mumetal" or "permalloy" which have negligible hysteresis loss.

(ii) **Error due to Stray Fields** Since the operating magnetic field is comparatively weak, therefore such instruments are susceptible to stray fields. This may give rise to wrong readings. This error is eliminated by shielding the instrument with iron enclosure.

(iii) **Error due to Temperature** Changes in temperature affect the circuit resistance of the coil and stiffness of the control springs.

We can write

$$I_m R_m = (I - I_m) R_s \quad (\because I_s = I - I_m)$$

or
$$I_m (R_m + R_s) = I R_s$$

$$\therefore \frac{I}{I_m} = \frac{R_m + R_s}{R_s}$$

or
$$\therefore I = I_m \times \frac{R_m + R_s}{R_s}$$

i.e. Circuit current = Full scale deflection (f.s.d.) current $\times \frac{R_m + R_s}{R_s}$.

Instrument Constant The ratio of current to be measured to the full scale deflection current is called instrument constant i.e.,

$$\text{Instrument constant} = \frac{I}{I_m} = \frac{R_m + R_s}{R_s}$$

With different shunts, the same instrument will have different instrument constants.

2. Extension of Voltmeter Range

The range of a voltmeter can be extended by connecting a high resistance (R) in series with its coil as shown in Fig. 13.12. The voltmeter is connected with the two points (A and B) across a resistance (r) whose voltage drop is to be measured.

Theory

We consider the circuit shown in Fig. 13.12. Let (V) volts be the maximum voltage to be measured (i.e. the drop across r)

Let R_m = Voltmeter resistance

R = High resistance in series with voltmeter coil.

I_m = Full scale deflection current for voltmeter.

Since voltmeter is connected in parallel with resistance r , hence voltage across AB (i.e. across r) = Voltage across voltmeter

or
$$V = I_m (R + R_m)$$

or
$$R + R_m = \frac{V}{I_m}$$

$$\therefore R = \frac{V}{I_m} - R_m$$

Hence, required high resistance R

$$= \frac{\text{Max. voltage to be measured}}{\text{f.s.d. voltmeter current}} - \text{Voltmeter resistance.}$$

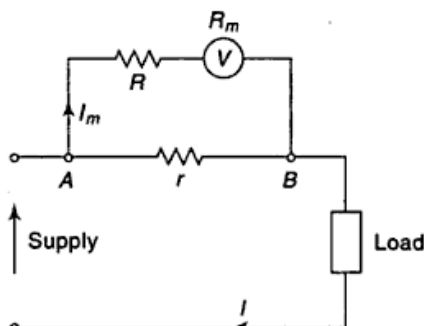


Fig. 13.12 Extension of range of voltmeter

unchanged. Therefore, such instruments can be used for both dc and ac measurements.

Let

I_F = Current through fixed coil.

I_M = Current through moving coil.

$$\therefore T_o \propto I_F I_M$$

Since $I_F = I_M = I$; the fixed and moving coils being in series,

$$\therefore T_o \propto I^2 \quad (i)$$

The control is by springs and hence the controlling torque is proportional to the angle of deflection i.e.

$$T_c \propto \theta \quad (ii)$$

The pointer comes to rest at a position when $T_o = T_c$

Thus comparing equation (i) and (ii), we get,

$$\theta \propto I^2$$

It is clear that deflection of the pointer is directly proportional to the square of the operating current. Hence, the scale of these instruments is non-uniform (being crowded in their lower parts and spread out at the higher side).

Advantages

1. These instruments can be used for both ac and dc measurements.
2. These instruments are free from hysteresis and eddy current errors.

Disadvantages

- (a) Since torque/weight ratio is small, therefore, such instruments have frictional errors which reduce the sensitivity.
- (b) Scale is not uniform (in case of ammeters and voltmeters)
- (c) A good amount of screening of the instrument is required to avoid the effect of stray fields.
- (d) These instruments are costlier than other types and therefore, they are rarely used as ammeters or voltmeters.

13.6.9 Dynamometer type Wattmeter

A dynamometer type wattmeter is most commonly employed for measurement of the power in a circuit. It can be used to measure power in ac as well as dc circuits.

Construction In a dynamometer type wattmeter (Fig. 13.14) the fixed coils are connected in series with the load and carry the circuit current. These coils are called *current coils*. The moving coil is connected across the load and carries current proportional to the voltage. It is called *potential coil*. Usually a high resistance is connected in series with the potential coil to limit the current through the potential coil.

The controlling torque is provided by springs. Springs also serve the additional purpose of leading current into and out of the moving coil. Air friction damping is employed in such instruments.

$$\begin{array}{ll}
 & T_o \propto I_M I_F \\
 \text{or} & T_o \propto VI \\
 \text{i.e.} & T_o \propto \text{power}
 \end{array}$$

AC Working of Dynamometer Wattmeter

Let us now suppose that in an ac circuit,

e = instantaneous voltage across load

i = instantaneous current through load

If the load has lagging power factor $\cos \phi$, we can write

$$e = E_m \sin \omega t$$

$$i = I_m \sin (\omega t - \phi)$$

Current through fixed coil, $I_F \propto i$

Current through moving foil, $I_M \propto e$

Due to large inertia of the moving system, the deflection will be proportional to the average torque.

\therefore Mean deflecting torque \propto Average of $I_M I_F$

i.e., $T_o \propto$ Average of $e \times i$

or, $T_o \propto$ Average of $(E_m \sin \omega t) \times (I_m \sin (\omega t - \phi))$
 $\propto EI \cos \phi$
 \propto Power (ac)

Hence, the dynamometer type wattmeter can be used for the measurement of both ac and dc power.

Since $T_o \propto$ power

and $T_o \propto \theta$

$\therefore \theta \propto$ power

Hence, such instruments have a uniform scale.

Advantages

A dynamometer wattmeter has the following advantages:

- It has uniform scale.
- By careful design, high accuracy can be obtained.
- It can be used for ac as well as dc measurements.

Disadvantages

A dynamometer wattmeter has the following disadvantages:

- At low power factors, the inductance of the potential coil causes error in measurement.
- The readings of the instruments may be affected by the stray fields acting on the moving coil. In order to prevent it, the instrument is shielded from external fields by enclosing it in a soft iron case.

13.6.10 Induction Type Energy Meter (Single-Phase)

Single-phase induction type energy meter (Fig. 13.16) is extensively used to measure the electric energy supplied to a single-phase ac circuit in a given time. This is suitable only for use with ac application.

The braking torque T_B is proportional to the disc speed N i.e.

$$T_B \propto N$$

or

$$T_B = K_2 N$$

(ii)

The disc achieves steady speed N when the braking torque is equal to the deflecting torque.

From equations (i) and (ii),

$$K_2 N = K_1 VI \cos \phi$$

Multiplying, both sides by time ' t '

$$K_2 Nt = K_1 (VI \cos \phi) t$$

or

$$Nt = K_3 Pt \quad \left[P = VI \cos \phi \text{ and } K_3 = \frac{K_1}{K_2} \right]$$

Since the product Nt represents the number of revolutions of the disc in time ' t ' and the product Pt represents the energy passing through the meter in time t , therefore, number of revolutions of the disc is proportional to the energy passing through the meter i.e.

Number of revolutions of disc \propto Electrical energy passing through the meter.

13.6.11 Errors of induction type energy-meters

The following are the common errors which may creep in an energy meter:

1. Phase and speed errors
2. Frictional error
3. Creeping error
4. Temperature error
5. Frequency error.

1. Phase and Speed Errors

(a) Phase Error This error is introduced because the shunt magnet flux does not lag behind the supply voltage by exactly 90° (due to some resistance of the coil and iron losses in the core).

In order to remove this error, flux due to the shunt magnet should be made to lag behind the supply voltage by exactly 90° . This is accomplished by adjusting the position of the shading ring filled on the central limb of the shunt magnet. Since the inductance of the shading loop is high as compared with its resistance, the current circulating in the loop will lag behind the supply voltage by nearly 90° . By altering the position of this ring on the central limb of the shunt magnet, 90° displacement can be adjusted.

(b) Speed Error Sometimes, the speed of the disc of the energy meter is either faster or slower, introducing an error.

The speed of the energy meter can be adjusted to the desired value by changing the position of the braking magnet. If the braking magnet is moved towards the center of spindle, the braking torque is reduced, increasing the speed of the disc and vice versa.

14

REVIEW PROBLEMS

In this chapter different types of worked-out examples are set covering the full syllabus of the basic electrical engineering course. The reader is referred to the following section for the worked-out examples.

14.1 A coil has a resistance of $10\ \Omega$ at 0°C and $15\ \Omega$ at 100°C . What is the temperature co-efficient of the resistance of the coil? At what temperature will its resistance be $30\ \Omega$?

Solution

Since $R = R_0(1 + \alpha_0 T)$ (i)

$$\therefore 15 = 10[1 + \alpha_0 \times 100]$$

$$\therefore \alpha_0 = 0.005 \text{ per } ^\circ\text{C at } 0^\circ\text{C}$$

Also, using Eq. (i) we have,

$$30 = 10(1 + 0.005 \times T)$$

$$\text{i.e. } T = 400^\circ\text{C}$$

14.2 A copper coil is found to have its resistance as $90\ \Omega$ at 20°C and is connected to a $230\ \text{V}$ supply. By how much must the voltage be increased to keep the current constant, if the temperature of the coil rises to 60°C . Take the temperature co-efficient of copper as $0.00428 \text{ per } ^\circ\text{C at } 0^\circ\text{C}$.

Solution

Since $R_{20} = R_0(1 + \alpha_0 \times 20)$ and

$$R_{60} = R_0(1 + \alpha_0 \times 60),$$

$$\text{we have } \frac{R_{20}}{R_{60}} = \frac{R_0(1 + \alpha_0 \times 20)}{R_0(1 + \alpha_0 \times 60)}$$

$$\therefore R_{60} = \frac{R_{20}[1 + (60 \times 0.00428)]}{[1 + (20 \times 0.00428)]} = \frac{90 \times [1 + (60 \times 0.00428)]}{[1 + (20 \times 0.00428)]} = 104.4\ \Omega$$

Current taken by coil at 20°C is thus, $I_{20^\circ\text{C}} = \frac{230}{90} = 2.56\ \text{A}$.

At 60°C to keep the current constant, the voltage must be (2.56×104.4) or, $267.26\ \text{V}$ therefore the voltage must be raised by $(267.26 - 230)$ i.e., $37.26\ \text{V}$.

14.3 The resistance of the field coil of a motor is $200\ \Omega$ at 15°C . After the motor worked for a few hours on full load, the resistance increases to $240\ \Omega$. Calculate the temperature rise of the field coil assuming the temperature co-efficient of resistance is 0.0042 per $^\circ\text{C}$ at 0°C .

Solution

We can write,
$$\frac{R_2}{R_1} = \frac{R_0(1 + \alpha_0 \times T_2)}{R_0(1 + \alpha_0 \times T_1)}$$

$$\therefore R_L = \frac{R_1(1 + \alpha_0 \times T_2)}{(1 + \alpha_0 \times T_1)}$$

or
$$(1 + \alpha_0 T_2) = \frac{R_2}{R_1} (1 + \alpha_0 T_1) = \frac{240}{200} [1 + 0.0042 \times 15]$$

$$\therefore \alpha_0 T_2 = 1.2 + 0.0756 - 1 = 0.2756$$

or
$$T_2 = \frac{0.2756}{0.0042} = 65.6^\circ\text{C}.$$

\therefore Temperature rise = $65.6 - 15 = 50.6^\circ\text{C}$

14.4 Two resistors are made of different materials and have temperature coefficients α_1 and $\alpha_2/^\circ\text{C}$ at 0°C . They are connected in parallel across voltage source and consume equal power at 25°C . If $\alpha_1 = 2\alpha_2$, while $\alpha_2 = 0.005$ per $^\circ\text{C}$, find the ratio of the power consumed for both the resistors at 60°C .

Solution

At 25°C , the resistors consume same power. Since both the resistors are connected across a single source hence we can write at 25°C , $V^2/R_1 = V^2/R_2$.

i.e. $R_1 = R_2$

Hence we have

$$R_{01}(1 + 25\alpha_1) = R_{02}(1 + 25\alpha_2)$$

i.e.
$$\frac{R_{01}}{R_{02}} = \frac{1 + 25\alpha_2}{1 + 25\alpha_1}$$

However, at 60°C we can write

$$\frac{V^2/R_2}{V^2/R_1} = \frac{R_1}{R_2} = \frac{R_{01}(1 + 60\alpha_1)}{R_{02}(1 + 60\alpha_2)}$$

or
$$\frac{P_2}{P_1} = \frac{(1 + 25\alpha_2)(1 + 60\alpha_1)}{(1 + 25\alpha_1)(1 + 60\alpha_2)}$$

where P_2 and P_1 are the power consumed by the second and first resistor at 60°C respectively.

Since $\alpha_1 = 2\alpha_2$ we have

$$\begin{aligned} \frac{P_2}{P_1} &= \frac{(1 + 25\alpha_2)(1 + 60 \times 2\alpha_2)}{(1 + 25 \times 2\alpha_2)(1 + 60\alpha_2)} \\ &= \frac{1 + 25\alpha_2 + 120\alpha_2 + 3000\alpha_2^2}{1 + 50\alpha_2 + 60\alpha_2 + 3000\alpha_2^2} = \frac{3000\alpha_2^2 + 145\alpha_2 + 1}{3000\alpha_2^2 + 110\alpha_2 + 1} \end{aligned}$$

with $\alpha_2 = 0.005/^\circ\text{C}$, we have at 60°C

$$\frac{P_2}{P_1} = \frac{3000 \times 0.005^2 + 145 \times 0.005 + 1}{3000 \times 0.005^2 + 110 \times 0.005 + 1}$$

or
$$\frac{P_2}{P_1} = 1.1076.$$

14.5 A cylindrical copper conductor has a resistivity ρ while the resistance between the opposite ends is (R). Assuming its volume to be v , length L and diameter D , find an expression for the length and diameter in terms of the resistivity.

Solution

$$R = \rho \frac{L}{A} = \frac{\rho L^2}{\frac{\pi D^2}{4} \cdot L} = \frac{\rho L^2}{v} \quad \left[\because \text{volume } (v) = \frac{\pi D^2 L}{4} \right]$$

Hence,
$$L = \sqrt{\left(\frac{Rv}{\rho} \right)}$$

Also,
$$R = \rho \frac{L}{\frac{\pi D^2}{4}} = \frac{\rho L \frac{\pi D^2}{4}}{\left(\frac{\pi D^2}{4} \right)^2} = \frac{\rho v}{\frac{\pi^2 D^4}{16}} = \frac{16 \rho v}{\pi^2 D^4}$$

$$\therefore D = \left[\frac{16 \rho v}{\pi^2 R} \right]^{1/4}$$

14.6 A solution of resistivity $22 \Omega \text{ cm}$ is poured to fill a glass container whose top and bottom ends are made up of two electrodes (Fig. 14.1). A dc voltage of 220 V is applied across the electrodes when the power absorbed by the liquid solution is 22 kW . If the area of each electrode is circular and of 100 cm^2 value, find the distance between the electrodes. Neglect the thickness and resistance of the electrodes.

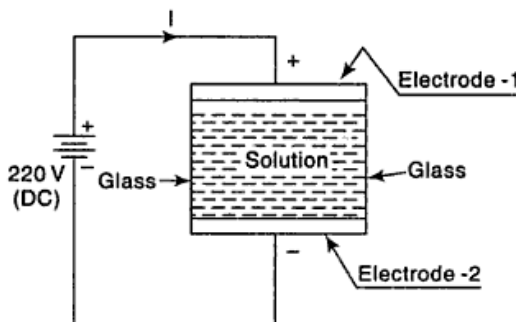


Fig. 14.1

Solution

Current I through the solution is obtained as

$$I = \frac{P}{V} = \frac{22 \times 10^3}{220} = 100 \text{ A}$$

From $R = \rho \frac{L}{A}$, we get

$$L = \frac{R \times A}{\rho} = \frac{(V/I) \times A}{\rho} = \frac{220}{100} \times \frac{100}{22} = 10 \text{ cm.}$$

Thus the length of the liquid path is 10 cm .

14.7 A resistor is wound using a wire of resistivity ρ_1 whose length is l_1 , and diameter d_1 . Due to some effect, it is subsequently needed to replace the original wire by another wire of resistivity ρ_2 . Assuming the diameter of the new wire being 1.5 times of the diameter of the original one, find the ratio of the resistivities of these two wires assuming the resistance and surface area of both as same at the operating temperature.

Solution

As per the question,

$$\frac{\rho_1 l_1}{A_1} = \frac{\rho_2 l_2}{A_2}$$

$$\text{i.e. } \frac{\rho_2}{\rho_1} = \frac{l_1}{A_1} \times \frac{A_2}{l_2} = \frac{l_1}{\pi d_1^2 / 4} \times \frac{\pi d_2^2 / 4}{l_2} = \frac{l_1}{l_2} \times \frac{d_2^2}{d_1^2}$$

$$\text{Also, } \pi d_2 l_2 = \pi d_1 l_1 (\text{surface area being same}).$$

$$\text{i.e. } \frac{l_1}{l_2} = \frac{d_2}{d_1}$$

$$\therefore \frac{\rho_2}{\rho_1} = \frac{d_2}{d_1} \times \frac{d_2^2}{d_1^2} = \frac{d_2^3}{d_1^3} = \frac{(1.5 d_1)^3}{d_1^3} = 3.375.$$

Thus the resistivity of the second wire is 3.375 times more than the resistivity of the first one.

.....

14.8 Determine the equivalent capacitance of the network shown in Fig. 14.2. All values shown in the figure are in μF .

Solution

The network shown in Fig. 14.2 is reduced to a simpler network as shown in Fig. 14.3.

Here,

$$C_1 = \frac{1}{\frac{1}{6} + \frac{1}{5} + \frac{1}{6}} = \frac{15}{8} \mu\text{F}$$

$$C_2 = \frac{2 \times 1}{2 + 1} = \frac{2}{3} \mu\text{F}$$

Further network reduction is shown in Fig. 14.4

where, $C_3 = \frac{15}{8} + 3 = 4.875 \mu\text{F}$.

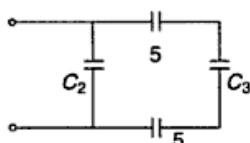


Fig. 14.4

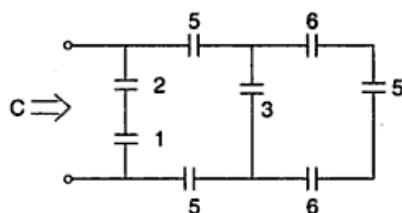


Fig. 14.2

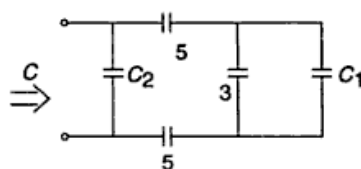


Fig. 14.3

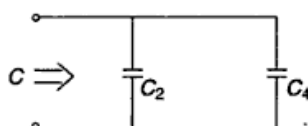


Fig. 14.5

Since two capacitances of $5 \mu\text{F}$ each and $4.875 \mu\text{F}$ are in series, we have the equivalent capacitance of these three capacitance as

$$C_4 = \frac{1}{\frac{1}{5} + \frac{1}{5} + \frac{1}{4.875}} = 1.65 \mu\text{F. (Fig. 14.5)}$$

Hence C , the equivalent capacitance is

$$C = C_2 + C_4 = \frac{2}{3} + 1.65 = 2.3167 \mu\text{F}.$$

14.9 A parallel plate capacitor has three identical parallel plates. The outer two plates are connected by metals. When the inner plate is at the middle of the two outer plates the capacitance is C_1 . When the inner plate is four times near to one plate as the outer, the capacitance is C_2 . Determine the ratio C_1/C_2 .

Solution

Let us assume the distance between the two outer plates be $5d$, area of cross-section of each plate A and the permittivity of the medium is ϵ .

$$\therefore C_1 = \frac{A\epsilon}{2.5d} + \frac{A\epsilon}{2.5d} = \frac{2A\epsilon}{2.5d}$$

$$\text{Again, } C_2 = \frac{A\epsilon}{d} + \frac{A\epsilon}{4d} = \frac{5A\epsilon}{4d}$$

$$\text{Hence, } \frac{C_1}{C_2} = \frac{2 \times 4}{2.5 \times 5} = \frac{8}{12.5} = 1 : 1.56.$$

14.10 A capacitor consists of two parallel circular metal discs of 15 cm radius and 20 mm apart. Between the discs there are three different layers of dielectrics having different thicknesses given as follows:

Thickness d	ϵ
7 mm	2
5 mm	5
8 mm	7

Determine the voltage gradient in each dielectric when 1000 V (dc) is applied across it.

Solution

Area of each plate $A = \pi r^2 = \pi(0.15)^2 = 0.0706 \text{ sq m}$.

$$\begin{aligned} \text{Capacitance } C &= \frac{A\epsilon_0}{\frac{d_1}{\epsilon_1} + \frac{d_2}{\epsilon_2} + \frac{d_3}{\epsilon_3}} = \frac{A \times \epsilon_0}{\frac{7}{2} + \frac{5}{5} + \frac{8}{7}} \times 10^3 \\ &= \frac{0.0706 \times 8.854 \times 10^{-12} \times 10^3}{\frac{7}{2} + 1 + \frac{8}{7}} \\ &= \frac{0.625}{5.643} \times 10^{-9} \text{ F} \\ &= 0.111 \times 10^{-9} \text{ F} = 111 \mu\text{F}. \end{aligned}$$

Charge $Q = VC = (1000 \times 0.111 \times 10^{-9}) \text{ Coulomb}$

$$\text{Charge density } D \left(= \frac{Q}{A} \right) = \frac{1000 \times 0.111 \times 10^{-9}}{0.0706} \text{ C/m}^2 = 1.572 \mu\text{C/m}^2.$$

\therefore Voltage gradient for the

$$\text{1st dielectric, } E_1 = \frac{D}{\epsilon_0 \epsilon_1} = \frac{1.572 \times 10^{-6}}{8.854 \times 10^{-12} \times 2} \text{ V/m} = 0.0888 \times 10^6 \text{ V/m}$$

$$\text{2nd dielectric, } E_2 = \frac{D}{\epsilon_0 \epsilon_2} = \frac{1.572 \times 10^{-6}}{8.854 \times 10^{-12} \times 5} \text{ V/m} = 0.0355 \times 10^6 \text{ V/m}$$

$$\text{3rd dielectric, } E_3 = \frac{D}{\epsilon_0 \epsilon_3} = \frac{1.572 \times 10^{-6}}{8.854 \times 10^{-12} \times 7} \text{ V/m} = 0.025 \times 10^6 \text{ V/m.}$$

14.11. An air capacitor consists of two parallel square plates of 60 cm side. When the two plates are 2 mm apart the capacitor is charged to a voltage of 240 V. Determine the work done in separating the plates from 2 mm to 5 mm.

Solution

When the separation between the plates is 2 mm;

$$C_1 = \frac{A\epsilon}{d_1} = \frac{(0.6 \times 0.6) \times \epsilon_0}{2 \times 10^{-3}} = 180 \epsilon_0$$

$$\text{Energy stored } W_1 = \frac{1}{2} C_1 V^2 = \frac{1}{2} \times 180 \times \epsilon_0 \times (240)^2 = \epsilon_0 \times 5184 \text{ kJ.}$$

When the separation between the plates is 5 mm;

$$C_2 = \frac{A\epsilon}{d_2} = \frac{(0.6 \times 0.6) \times \epsilon_0}{5 \times 10^{-3}} = 72 \epsilon_0$$

$$\text{Energy stored } W_2 = \frac{1}{2} C_2 V^2 = \frac{1}{2} \times 72 \epsilon_0 \times (240)^2 = \epsilon_0 \times 2073.6 \text{ kJ}$$

Work done in separating the plates from 2 mm to 5 mm is

$$(W_1 - W_2) = (5184 - 2073.6) \times 10^3 \times 8.854 \times 10^{-12} \text{ J} = 27.54 \text{ J.}$$

14.12. Two capacitors A and B have capacitances of 50 μF and 30 μF respectively. When 230 V, 50 Hz voltage is applied, find the current and maximum energy stored. Assume A and B are connected in (i) series and (ii) parallel.

Solution

(i) When the capacitances are connected in series the equivalent capacitance is

$$C = \frac{50 \times 30}{50 + 30} \mu\text{F} = \frac{150}{8} \mu\text{F}$$

$$\text{The current } I = V\omega C = 230 \times 2\pi \times 50 \times \frac{150}{8} \times 10^{-6} = 1.355 \text{ A.}$$

$$\text{Maximum energy stored} = \frac{1}{2} CV_{\max}^2 = \frac{1}{2} \times \frac{150}{8} \times 10^{-6} \times (230 \times \sqrt{2})^2 = 0.992 \text{ J.}$$

(ii) When the capacitances are connected in parallel the equivalent capacitance is

$$C = (50 + 30) \mu\text{F} = 80 \mu\text{F}$$

$$\text{Current } I = V\omega C = 230 \times 2\pi \times 50 \times 80 \times 10^{-6} \text{ A} = 5.78 \text{ A}$$

$$\text{Maximum energy stored} = \frac{1}{2} CV_{\max}^2 = \frac{1}{2} \times 80 \times 10^{-6} \times (\sqrt{2} \times 230)^2 = 4.232 \text{ J.}$$

\therefore When the capacitances are connected in series, the current is 1.355 A while the energy stored is 0.992 J. In parallel connection, the current is 5.78 A and the energy stored is 4.232 J.

14.13. A 10 μF capacitor is connected through a 2 M Ω resistance to a direct current source. After remaining on charge for 30s the capacitor is disconnected and discharged through a resistor. Find what percentage of the energy input from the supply is dissipated in the resistor.

Solution

Given,

$$C = 10 \times 10^{-6} \text{ F}$$

$$R = 2 \times 10^6 \Omega$$

$$\lambda = C.R = 20 \text{ s (time constant)}$$

$$\therefore v = V(1 - e^{-t/\lambda}), \text{ we have at } t = 30 \text{ s,}$$

$$v = V(1 - e^{-30/20}) = 0.7768 \text{ V.}$$

Energy stored in the capacitor (at $t = 30 \text{ s}$) is given by

$$\begin{aligned} \frac{1}{2} C v^2 &= \frac{1}{2} \times 10 \times 10^{-6} \times (0.7768)^2 \text{ V}^2 \\ &= 3.0326 \times 10^{-6} \text{ (= energy dissipated in the resistor)} \end{aligned}$$

But

$$\begin{aligned} i &= \frac{dq}{dt} = \frac{d}{dt} (Cv) \\ &= \frac{d}{dt} \{ CV(1 - e^{-t/\lambda}) \} = CV \times \frac{1}{\lambda} e^{-t/\lambda} = \frac{V}{R} e^{-t/\lambda} \quad [\because \lambda = RC] \end{aligned}$$

$$\begin{aligned} \therefore \text{Total energy input} &= \int_0^{30} V i dt = \frac{V^2}{R} \int_0^{30} e^{-t/20} dt = -\frac{V^2}{R} \times 20 [e^{-t/20}]_0^{30} \\ &= \frac{10V^2}{10^6} (0.7768) = 7.768 \times 10^{-6} \text{ V}^2. \end{aligned}$$

Percentage of the energy input from the supply dissipated in the resistor =

$$\frac{3.0326 \times 10^{-6} \text{ V}^2}{7.768 \times 10^{-6} \text{ V}^2} = 0.3904 \text{ or, } 39.04\%$$

.....

14.14 Calculate the maximum energy stored in the capacitor and energy dissipated in the resistor in the time interval $0 < t < 1 \text{ s}$ in the circuit shown in Fig. 14.6.

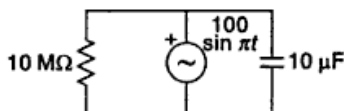


Fig. 14.6

Solution

The expression for the energy stored in the capacitor is,

$$\begin{aligned} E &= \frac{1}{2} C v_c^2 = \frac{1}{2} \times 10 \times 10^{-6} \times (100 \sin \pi t)^2 \\ &= \frac{1}{2} \times 10^{-1} \sin^2 \pi t = 0.05 \sin^2 \pi t. \text{ J} \end{aligned}$$

The energy will be maximum when $(\sin^2 \pi t) = 1$. Hence maximum energy stored in the capacitor is 0.05 J.

$$\text{The current through the resistor } i_R = \frac{100 \sin \pi t}{10 \times 10^6} = (10^{-5} \sin \pi t) \text{ A}$$

Energy dissipated in the resistor in the time interval $0 < t < 1 \text{ s}$

$$\begin{aligned} &= \int_0^1 i_R^2 R dt \\ &= \int_0^1 (10^{-5} \sin \pi t)^2 \times 10 \times 10^6 dt \\ &= \int_0^1 10^{-3} \sin^2 \pi t dt \end{aligned}$$

$$\begin{aligned}
 &= \frac{10^{-3}}{2} \int_0^1 (1 - \cos 2\pi t) dt \\
 &= \frac{10^{-3}}{2} \left[t - \frac{\sin 2\pi t}{2\pi} \right]_0^1 = \frac{10^{-3}}{2} \left[1 - \frac{\sin 2\pi}{2\pi} \right] = 0.5 \text{ mJ.}
 \end{aligned}$$

14.15 Determine the voltage across the capacitor when a current waveform shown in Fig. 14.7 is applied to a $10 \mu\text{F}$ capacitor.

Solution

We know, voltage across capacitor $v_C = \frac{1}{C} \int i dt$

Here, $i = 40 \text{ mA} = 0.04 \text{ A}$ (from 0 to 10 ms).

Hence, $v_C = \frac{1}{C} \int 0.04 dt$ (from 0 to 10 ms).

$$\begin{aligned}
 \text{or } v_C &= \frac{1}{10 \times 10^{-6}} \int 0.04 dt \\
 &= 10^5 \times 0.04t + K = 4000t + K, \text{ where } K \text{ is constant}
 \end{aligned}$$

At $t = 0$, $v_C = 0$; this gives $K = 0$.

With this the general expression become $v_C = 4000t$

\therefore At $t = 10 \text{ ms} (= 0.01 \text{ s})$, $v_C = 40 \text{ V}$.

When $t \geq 10 \text{ ms}$ then

$$i = 0$$

Hence, $v_C = \frac{1}{C} \int 0 \times dt + 40$ [\because At $t = 10 \text{ ms}$, $v_C = 40 \text{ V}$]

or $v_C = 40 \text{ volts at } t \geq 10 \text{ ms}$.

The voltage waveform across the capacitor is represented in Fig. 14.8.

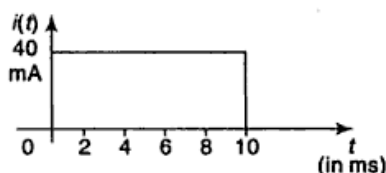


Fig. 14.7

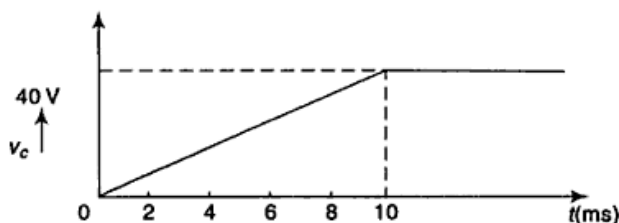


Fig. 14.8

14.16 A triangular voltage wave (shown in Fig. 14.9) with a peak amplitude of 150 V and frequency 75 KHz , is applied across a $0.03 \mu\text{F}$ capacitor. Determine the rms value of the current flowing in the capacitor.

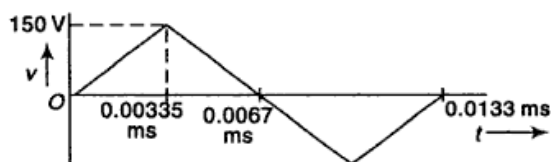


Fig. 14.9

Solution

From the given data,

Frequency $f = 75 \times 10^3$ Hz.

Time period $T = \frac{1}{f} = 0.0133$ ms

The voltage rises from 0 to 150 V in 0.00335 ms. Also, $C = 0.03 \times 10^{-6}$ F.

The peak value of the current flowing through the capacitor $\left(= C \frac{dv}{dt} \right) = 0.03 \times 10^{-6} \times$

$$\frac{150}{0.00335} = 0.001343 \text{ A.}$$

The current wave through the capacitor is rectangular when a triangular voltage waveform is applied.

Hence rms value of the current flowing through the capacitor is 0.001343 A.

14.17 Determine the current through a $20 \mu\text{F}$ capacitor when a voltage waveform shown in Fig. 14.10 is applied.

Solution

$$i = C \frac{dv_c}{dt}$$

From the given figure, for $t < 2$ ms,

$$v_c = 0.$$

Hence, $i = 0$ A.

For $2 \leq t \leq 3$ ms, we find $v_c = \left(\frac{5}{1 \times 10^{-3}} \times t \right)$ V

$$\therefore i \left(= C \frac{dv_c}{dt} \right) = 20 \times 10^{-6} \frac{d}{dt} \left(\frac{5}{1 \times 10^{-3}} t \right) = 20 \times 10^{-6} \times 5000 = 0.1 \text{ A.}$$

For $t > 3$ ms

$$i = 20 \times 10^{-6} \frac{d}{dt} (5) = 0 \text{ A.} \quad [\because v_c = 5 \text{ V (constant)}]$$

The current waveform is shown in Fig. 14.11.

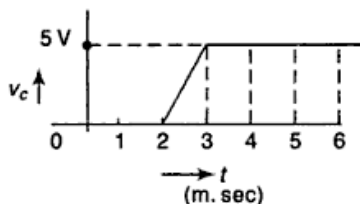


Fig. 14.10

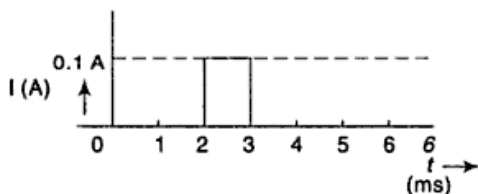


Fig. 14.11

14.18 The current waveform through a 0.5 H inductor is shown in Fig. 14.12. Calculate the voltage across the inductor at 0 ms, 8 ms and 14 ms.

Solution

We know that the voltage across the inductor is

$$v_L = L \frac{di}{dt}$$

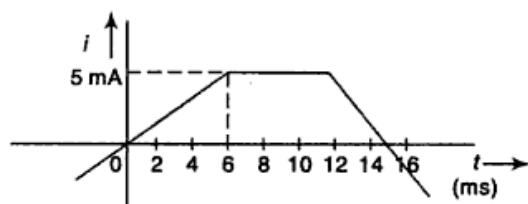


Fig. 14.12

For $t < 6$ ms, $i = \frac{5 \times 10^{-3}}{6 \times 10^{-3}} t$

$$\therefore v_L = 0.5 \frac{d}{dt} \left(\frac{5 \times 10^{-3}}{6 \times 10^{-3}} t \right) = \frac{0.5 \times 5 \times 10^{-3}}{6 \times 10^{-3}} = 0.4167 \text{ V.}$$

For $6 \leq t \leq 12$ ms

$$v_L = 0.5 \frac{d}{dt} (5 \times 10^{-3}) = 0$$

For $12 \leq t \leq 15$ ms, $i = -\frac{5 \times 10^{-3}}{3 \times 10^{-3}} t$

$$v_L = 0.5 \frac{d}{dt} \left(-\frac{5 \times 10^{-3}}{3 \times 10^{-3}} t \right) = -\frac{0.5 \times 5}{3} \text{ V} = -0.833 \text{ V.}$$

\therefore At $t = 0$, $v_L = 0.4167 \text{ V}$

At $t = 8$ ms, $v_L = 0$

At $t = 14$ ms, $v_L = -0.833 \text{ V.}$

.....

14.19 Simplify the diagram shown in Fig. 14.13.

Solution

Combining $2 \mu\text{F}$ and $6 \mu\text{F}$ capacitors in series, equivalent capacitance is $\left(\frac{1}{\frac{1}{2} + \frac{1}{6}} \right)$ or, $\frac{3}{2} \mu\text{F}$; there-

fore we see that the capacitances $5 \mu\text{F}$ and $\frac{3}{2} \mu\text{F}$ are in parallel. The equivalent capacitance is $\left(5 + \frac{3}{2} \right) = 6.5 \mu\text{F}$.

Again, it is observed that 7 H and 5 H inductors are in parallel. Their combined inductance becomes $\left(\frac{7 \times 5}{7 + 5} \right)$ or, $\frac{35}{12} \text{ H}$. However, $\left(\frac{35}{12} \text{ H} \right)$ and (1 H) inductors are in series.

The equivalent inductance is then $\left(1 + \frac{35}{12} \right)$ or, $\frac{47}{12} \text{ H}$ ($\approx 3.91 \text{ H}$).

The simplified diagram is shown in Fig. 14.13(a).

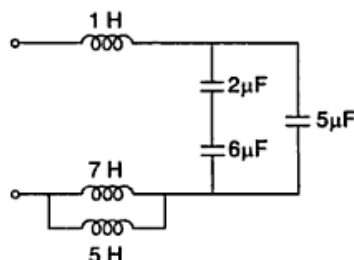


Fig. 14.13

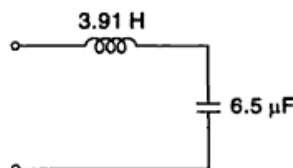


Fig. 14.13(a)

14.27 Determine the total energy stored in the passive network shown in Fig. 14.16 at $t = 0$. Assume $K = 0.5$ and terminals x and y (i) open circuited (ii) short circuited.

Solution

$$M = K \sqrt{L_1 L_2} = 0.5 \sqrt{0.3 \times 3} \text{ H} = 0.474 \text{ H}.$$

Let us consider the two mesh currents i_1 and i_2 are flowing the clockwise direction in the two meshes.

From Fig. 14.16, we have

$$i_1 = 5 \angle 0^\circ \text{ A}.$$

(i) When x and y are open circuited $i_2 = 0$

$$\text{Hence total energy stored is } \frac{1}{2} L_1 i_1^2 = \frac{1}{2} \times 0.3 \times 5^2 = 3.75 \text{ J}.$$

(ii) When x and y are short circuited,

$$i_1(t) = 5 \cos 15t \text{ and voltage } v_{xy} \text{ across } xy \text{ is } 0.$$

$$\text{Hence, } v_{xy} = 3 \frac{di_2}{dt} + 0.474 \frac{di_1}{dt} = 0$$

$$\text{or, } \frac{di_2}{dt} = -\frac{0.474}{3} \frac{d}{dt} (5 \cos 15t) = \frac{0.474}{3} \times 5 \times 15 \sin 15t = 11.85 \sin 15t.$$

$$\text{Hence } i_2(t) = \int_{-\infty}^t 11.85 \sin 15t \, dt = -0.75 \cos 15t \text{ (assuming zero initial point)}$$

Energy stored is

$$\left[\frac{1}{2} \times 0.3 \times 5^2 + \frac{1}{2} \times 3 \times (0.75)^2 + 0.474 \times 5 \times (-0.75) \right] = 2.817 \text{ J}.$$

14.28 In the circuit shown in Fig. 14.17 $L_1 = 2 \text{ H}$, $L_2 = 5 \text{ H}$ and $M = 1.8 \text{ H}$. Find the expression for the energy stored after the circuit is connected to a dc voltage of 30 V . Assume M to be positive.

Solution

If i_1 and i_2 be the currents in the two coils, we can write

$$30 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{(i)}$$

$$0 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \quad \text{(ii)}$$

From Eq. (ii), we get

$$\frac{di_2}{dt} = -\frac{M}{L_2} \frac{di_1}{dt}$$

\therefore From Eq. (i), we get

$$30 = \frac{di_1}{dt} L_1 + M \left(-\frac{M}{L_2} \frac{di_1}{dt} \right) = \frac{di_1}{dt} \left(L_1 - \frac{M^2}{L_2} \right) = \frac{di_1}{dt} \frac{L_1 L_2 - M^2}{L_2}$$

$$\text{The equivalent inductance} = \frac{L_1 L_2 - M^2}{L_2} = \frac{2 \times 5 - (1.8)^2}{5} = 1.352 \text{ H}.$$

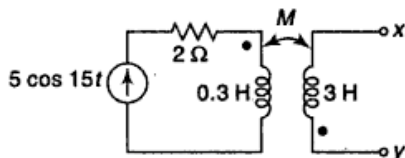


Fig. 14.16

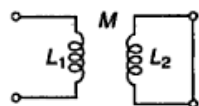


Fig. 14.17

Solution

Current $i = \left(15 \sin \frac{\pi}{3} t\right) \text{ A}$

\therefore Voltage (instantaneous) across the resistor is $\left(0.5 \times 15 \sin \frac{\pi}{3} t\right) \text{ V}.$

i.e. $v_R = \left(7.5 \sin \frac{\pi}{3} t\right) \text{ V}.$

Also, voltage across the inductor is given by

$$v_L = L \cdot \frac{di}{dt} = 5 \frac{d}{dt} \left(15 \sin \frac{\pi}{3} t\right) = 75 \cdot \frac{\pi}{3} \cos \frac{\pi}{3} t = \left(25 \pi \cos \frac{\pi}{3} t\right) \text{ V}.$$

Power across the resistor is

$$i^2 R = \left(225 \sin^2 \frac{\pi}{3} t\right) 0.5 = 112.5 \sin^2 \left(\frac{\pi}{3} t\right) \text{ W}.$$

The energy stored by the inductor is maximum when the current through it is maximum.

Current is maximum when $\left(\sin^2 \frac{\pi}{3} t\right) = 1$

i.e. $1 - \cos \left(\frac{2\pi}{3} t\right) = 2$ or, $\cos \frac{2\pi}{3} t = -1 = \cos \pi$

$\therefore \frac{2\pi}{3} t = \pi$ or, $t = \frac{3}{2} \text{ s}.$

Hence energy stored in the inductor is maximum at $t = 3/2 \text{ s}$. In another $3/2 \text{ s}$ energy will be recovered from the inductor.

$$\begin{aligned} \text{Hence in } \left(\frac{3}{2} + \frac{3}{2} = 3 \text{ s}\right) \text{ energy dissipated in the resistor is } & \int_0^3 \left(112.5 \sin^2 \frac{\pi}{3} t\right) dt \\ &= \frac{112.5}{2} \int_0^3 \left(1 - \cos \frac{2\pi}{3} t\right) dt \\ &= \frac{112.5}{2} \left[t - \frac{\sin \frac{2\pi}{3} t}{\frac{2\pi}{3}} \right]_0^3 = \frac{112.5}{2} \left[3 - \frac{\sin 2\pi}{\frac{2\pi}{3}} \right] = 168.75 \text{ J}. \end{aligned}$$

.....

14.31 Two coils having self-inductances of 0.3 H and 0.5 H are connected in series across a 230 V, 50 Hz supply. What current will flow if the coupling co-efficient of the coils is 0.45?

Solution

Mutual inductance $M = \sqrt{L_1 L_2} = 0.45 \sqrt{0.3 \times 0.5} = 0.1743$

When connected in series the equivalent impedance is given by

$$L = L_1 + L_2 \pm 2M = 0.3 + 0.5 \pm 2 \times 0.1743 = 1.1486 \text{ H or } 0.4514.$$

Hence $X_L = 100\pi \times 1.1486 = 360.84 \Omega$

or $X_L = 100\pi \times 0.4514 = 141.8 \Omega$

Current is, $\frac{230}{360.84} \text{ A} = 0.6374 \text{ A}$

or $\frac{230}{141.8} \text{ A} = 1.622 \text{ A}.$

14.32 Two coils are connected in series with same polarities and the combined inductance is found to be 0.567 H. When the coils are connected in series with reverse polarities then the combined inductance is 0.267 H. The self-inductance of one coil is 0.3 H. Determine the mutual inductance and the coupling coefficient.

Solution

Let L_1 and L_2 be the self-inductances of the two coils and M the mutual inductance. Then

$$L_1 + L_2 + M = 0.567$$

and $L_1 + L_2 - M = 0.267$

Hence $L_1 + L_2 = 0.417$

But $L_1 = 0.3 \text{ H},$

$\therefore L_2 = 0.417 - 0.3 = 0.117 \text{ H}$

and $M = 0.417 - 0.267 = 0.15 \text{ H}$

We know, $M = K\sqrt{L_1 L_2}$, where K is the coupling co-efficient

Hence $K = \frac{0.15}{\sqrt{0.3 \times 0.117}} = 0.8.$

14.33 Write three mesh equations for the circuit shown in Fig. 14.20.

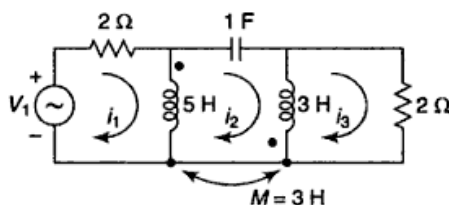


Fig. 14.20

Solution

The mutual inductance and the self inductances are replaced by their impedances and the corresponding circuit is shown in Fig. 14.21.

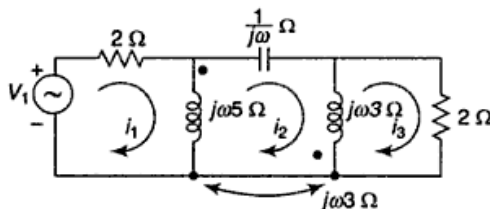


Fig. 14.21

Applying KVL in the first mesh (leftmost mesh),

$$2i_1 + j\omega 5(i_1 - i_2) + 3j\omega(i_3 - i_2) = V_1$$

or $(2 + 5j\omega)i_1 - 8j\omega i_2 + 3j\omega i_3 = V_1$

(i)

Applying KVL in the second mesh (middle mesh),

$$5j\omega(i_2 - i_1) + 3j\omega(i_2 - i_3) + \frac{1}{j\omega}i_2 + 3j\omega(i_2 - i_3) + 3j\omega(i_2 - i_1) = 0$$

$$\text{or} \quad -8j\omega i_1 + \left(14j\omega + \frac{1}{j\omega}\right)i_2 - 6j\omega i_3 = 0 \quad (\text{ii})$$

Applying KVL in the third mesh (rightmost mesh),

$$3j\omega(i_3 - i_2) + 3j\omega(i_1 - i_2) + 2i_3 = 0$$

$$\text{or} \quad 3j\omega i_1 - 6j\omega i_2 + (2 + 3j\omega)i_3 = 0. \quad (\text{iii})$$

14.34 When a coil of 1200 turns is linked with a flux of 4 m wb, a certain value of current flows through the circuit. When the circuit gets opened, the flux falls to its residual value of 1.5 m wb in 40 m secs. Find the average value of the induced emf.

Solution

Average emf in volts = Rate of change of flux linkages.

Change of flux = $(4 - 1.5) \times 10^{-3} = 2.5 \times 10^{-3}$ wb. ($= d\phi$)

Time for the change (dt) = 0.04 secs (given)

$$\therefore \text{Rate of change of flux linkage} \left(N \frac{d\phi}{dt}\right) = 1200 \times \frac{2.5 \times 10^{-3}}{4 \times 10^{-2}} = 75 \text{ V.}$$

14.35 A one-turn coil of axial length 0.4 m and a diameter of 0.2 m rotates at a speed of 500 rpm in a uniform flux density of 1.2 T. Calculate the induced emf.

Solution

Diameter of the armature = 0.2 m.

Circumference ($= 2\pi r$) = $\pi d = \pi \times 10^{-1} \times 2 = 0.628$ m

In one second the armature turns (500/60) revolutions.

$$\therefore \text{In one second a coil side travels } \frac{500}{60} \times 0.628 \text{ m.}$$

$$\text{i.e.} \quad v = 5.233 \text{ m/s.}$$

$$\therefore \text{induced emf } (E) = Blv = 1.2 \times (2 \times 0.4) \times 5.233 \text{ V}$$

$$= 5.024 \text{ V, in the entire coil having 2 turns.}$$

14.36 A straight horizontal conductor carries a current of 150 A at right angles to a uniform magnetic field of 0.6 Tesla. Find the force developed per meter length and the direction in which it acts.

Solution

$$F = (Bil) \text{ N} = 0.6 \times 150 \times 1 = 90 \text{ N/m.}$$

[Assuming the current flowing away from the observer, the force acts from right to left to move the conductor horizontally].

14.37 An armature conductor has an effective length of 400 m and carries a current of 25 A. The flux/pole is 0.5 Tesla. Determine the force in Newtons exerted on the armature conductor.

Solution

$$F = Bil \text{ N} = 0.5 \times 25 \times 400 \times 10^{-3} = 5 \text{ N.}$$

Thus $H = \frac{1000}{1.25} = 800 \text{ AT/m.}$

Also, $B = \frac{\phi}{A} = \frac{0.00075}{1500 \times 10^{-6}} = 0.5 \text{ T}$

Again, $B = \mu H$ or, $\mu = \frac{B}{H} = \frac{0.5 \times 1.25}{1000} = \frac{0.625}{1000}$

Also $\mu = \mu_r \cdot \mu_o \quad \therefore \mu_r = \frac{\mu}{\mu_o} = \frac{0.625}{1000 \times 4\pi \times 10^{-7}} = \frac{6250}{4\pi}$

Thus relative permeability of the iron sample = 497.5.

(ii) Reluctance of iron $S \left(= \frac{l}{\mu A} \right) = \frac{1.25 \times 10^3}{0.625 \times 1500 \times 10^{-6}} = 1.33 \times 10^6 \text{ AT/Wb}$

(iii) Since (Hl) is the m.m.f. we have the mmf in the given problem as $(800 \times 1.25) = 1000 \text{ AT.}$

14.42 An iron core has a cross-section of 500 mm^2 and having a length of 100 cm . A magnetizing force of 500 AT in it produces a magnetic flux of $400 \mu \text{ wb}$. Determine (i) the relative permeability of the material and (ii) the reluctance of the magnetic circuit. $\mu_o = 4\pi \times 10^{-7} \text{ H/m.}$

Solution

(i) $B = \frac{\phi}{A}$; Here $B = \frac{400 \times 10^{-6}}{500 \times 10^{-6}} = 0.8 \text{ T.}$

Also, as H is given by the ratio of total mmf and length hence,

$$H = \frac{F}{l} = \frac{500}{1} = 500 \text{ AT/m.}$$

Also, since $B (= \mu H) = \mu_o \cdot \mu_r \cdot H$, we have

$$\mu_r = \frac{B}{\mu_o H} = \frac{0.8}{4 \times \pi \times 10^{-7} \times 500} = 1275.$$

(ii) Reluctance $= \frac{\text{Length}}{\mu \times \text{Area}} = \frac{l}{\mu_o \mu_r \times A}$

$$= \frac{1}{4 \times \pi \times 10^{-7} \times 1275 \times 500 \times 10^{-6}} = 1.25 \times 10^6 \text{ AT/Wb.}$$

14.43 An air-gap of 3 mm thickness and area of 650 mm^2 is made by a cut in the iron of a magnetic circuit. If a flux of 0.05 Wb is required in the air-gap, find the ampere-turns required for the air-gap to produce the necessary flux. Assume $\mu_o = 4\pi \times 10^{-7} \text{ H/m.}$

Solution

Flux density in the air-gap is $B = \frac{0.05}{650 \times 10^{-6}} = \frac{5 \times 10^2}{6.5} \text{ T}$

Also we know $B = \mu_o \times H$

$$\therefore H \left(= \frac{B}{\mu_o} \right) = \frac{5 \times 10^2}{6.5 \times 4 \times \pi \times 10^{-7}} = 6.12 \times 10^7 \text{ AT/m}$$

Air-gap ($= 3 \text{ mm}$) $= 3 \times 10^{-3} \text{ m.}$

\therefore Required-ampere turns $= 6.12 \times 10^7 \times 3 \times 10^{-3} = 183600 \text{ AT.}$

Solution

Transforming 2A current source and 1A current source into voltage sources a new circuit is obtained (Fig. 14.34).

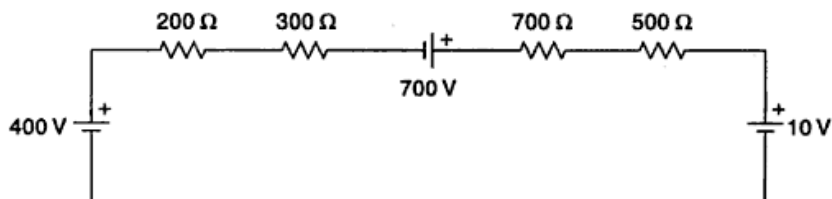


Fig. 14.34

Now, current through 500 Ω resistor is

$$\frac{400 + 700 - 10}{200 + 300 + 700 + 500} = \frac{1090}{1700} \text{ A} = 0.641176 \text{ A.}$$

The voltage across the 500 Ω resistor is $(500 \times 0.641176) = 320.59 \text{ V}$

14.62 By using source transformation technique find the current through the 8 Ω resistor in Fig. 14.35.

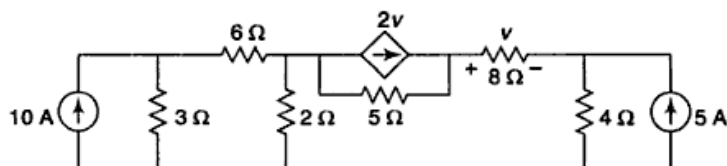


Fig. 14.35

Solution

As 3 Ω is in parallel with 10 A source and 4 Ω is parallel with 5 A source, the current sources can be transformed into voltage sources as shown in Fig. 14.35(a).

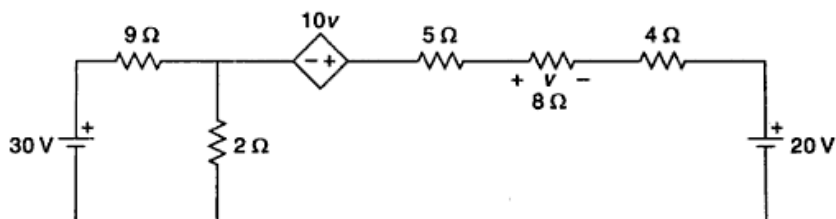


Fig. 14.35(a)

Transforming 30 V source into current source the circuit shown in Fig. 14.36 is obtained.

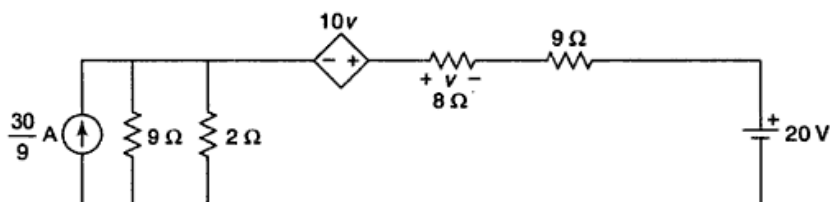


Fig. 14.36

Now, $9\ \Omega$ and $2\ \Omega$ are in parallel. Their combined resistance is $\left(\frac{9 \times 2}{9 + 2}\right)$ or, $\frac{18}{11}\ \Omega$.

Transforming the current source into voltage source the circuit in Fig. 14.36(a) is obtained.

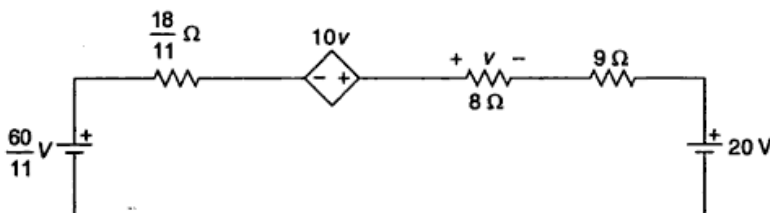


Fig. 14.36(a)

If current (i) flows through $8\ \Omega$ resistor then applying KVL

$$-\frac{60}{11} + \frac{18}{11}i - 10v + v + 9i + 20 = 0$$

$$\text{or} \quad 9v - \frac{117}{11}i = 20 - \frac{60}{11} \quad (i)$$

However from the circuit it is clear that $v = 8i$

Hence from Eq. (i) we have

$$9 \times 8i - \frac{117}{11}i = 20 - \frac{60}{11}$$

$$\text{or} \quad \frac{792 - 117}{11}i = \frac{220 - 60}{11}$$

$$\text{or,} \quad i = 0.237\ \text{A.}$$

14.63 In the circuit shown in Fig. 14.37(a) determine

- the power delivered in R_L , when $(R_L) = 500\ \Omega$
- the maximum power that can be delivered to (R_L) and value of (R_L) for maximum power transfer
- the possible values of R_L so that power across R_L is $0.5\ \text{W}$.

Solution

Let us first find the Thevenin's equivalent circuit. Removing the load resistance R_L the corresponding circuit is shown in Fig. 14.37(b).

$$\text{The mesh current } i = \frac{50 + 40}{100 + 200} = \frac{9}{20}\ \text{A.}$$

Hence Thevenin's voltage is

$$V_{Th} = 20 - 40 + 200 \times \frac{9}{30} = 40\ \text{V.}$$

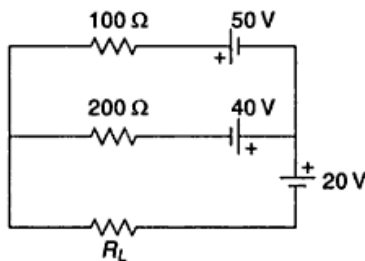


Fig. 14.37(a)

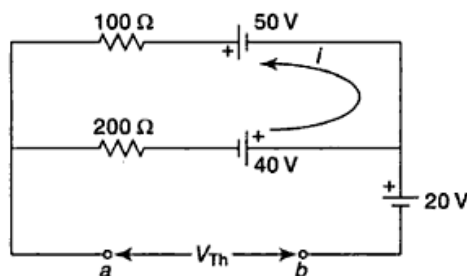


Fig. 14.37(b)

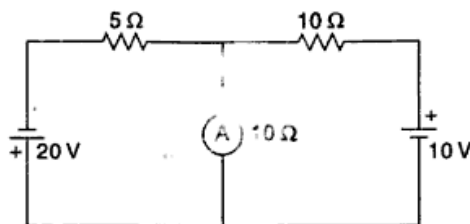


Fig. 14.38

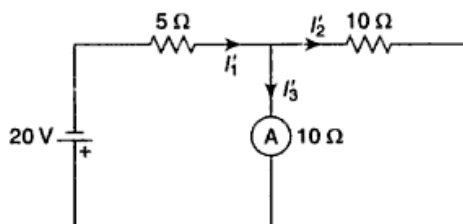


Fig. 14.39

Here
$$I_1' = -\frac{20\text{ V}}{5 + \frac{10 \times 10}{10 + 10}} = -2\text{ A}$$

Also,
$$I_3' = I_2' = 1\text{ A (-ve).}$$

Next we remove 20 V battery, shown in Fig. 14.40

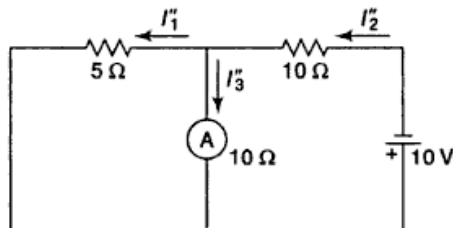


Fig. 14.40

Here,
$$I_2'' = \frac{10}{10 + \frac{5 \times 10}{5 + 10}} = \frac{10}{13.33}\text{ A}$$

$$I_3'' = I_2'' \times \frac{5}{10 + 5} = \frac{10}{13.33} \times \frac{5}{15} = 0.25\text{ A}$$

∴ Using superposition principle, the current through the ammeter is

$$I_3 = I_3' + I_3'' = -1 + 0.25 = -0.75\text{ A}$$

(negative sign indicates that the direction of the current is upwards through the ammeter in the corresponding figure.)

14.65 In the circuit of Fig. 14.41, find (I) using superposition theorem.

Solution

Let us first remove 2A source. See Fig. 14.42.

14.66 Determine the Thevenin's equivalent and Norton's equivalent of the circuit shown in Fig. 14.44.

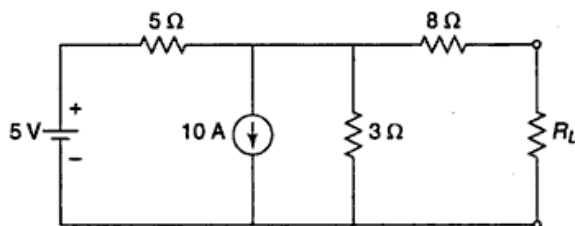


Fig. 14.44

Solution

Removing the load resistance R_L and transforming the 10 A current source into voltage source circuit shown in Fig. 14.45 is obtained.

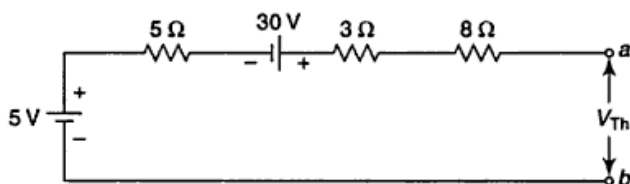


Fig. 14.45

The open circuit voltage is the Thevenin's equivalent voltage V_{Th} .

Here, $V_{Th} = V_{ab} = 5 + 30 = 35$ V.

Removing the sources, Thevenin's equivalent resistance can be obtained and the corresponding circuit is obtained as shown in Fig. 14.46.

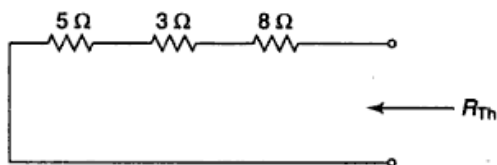


Fig. 14.46

Hence, $R_{Th} = 8 + 3 + 5 = 16$ Ω.

Therefore Thevenin's equivalent circuit can be obtained as shown in Fig. 14.47.

Now, to find Norton's equivalent current I_N the load resistance R_L is short circuited as shown in Fig. 14.48.

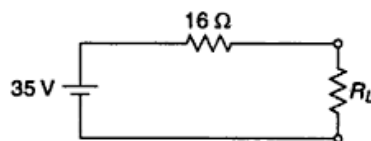


Fig. 14.47

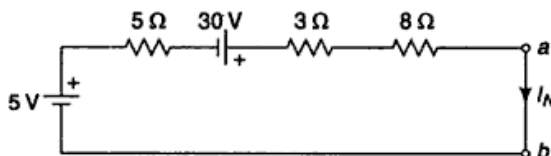


Fig. 14.48

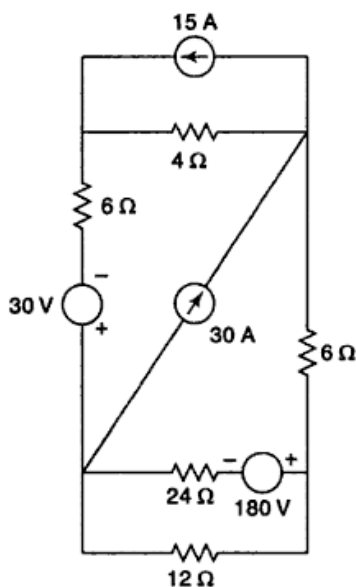


Fig. 14.53

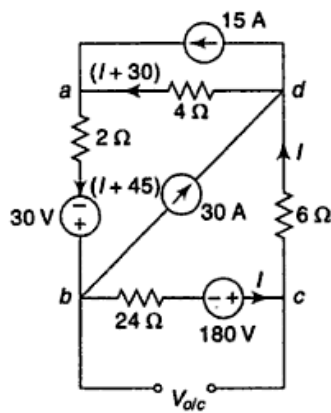


Fig. 14.54

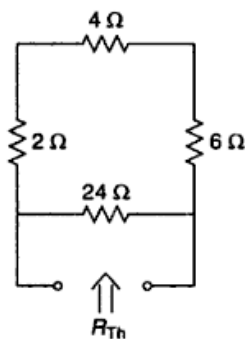


Fig. 14.55

14.69 In Fig. 14.56, find the current through the $2\ \Omega$ resistor and obtain power loss. Use Norton's theorem.

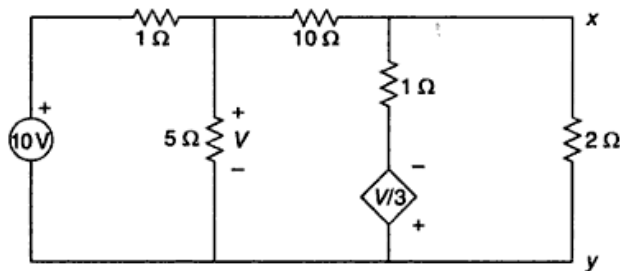


Fig. 14.56

Solution

Let us remove $2\ \Omega$ resistor and short the terminals x - y (Fig. 14.57).

- (i) $I = \frac{230}{300} = 0.766 \text{ A.}$
- (ii) $\text{P.f.} (= \cos \phi) = \frac{220}{300} = 0.733 \text{ (lagging) and } \phi = 42^\circ 36'.$
- (iii) Voltage across A, $v_A = 0.766 \times 143.4 = 109.8 \text{ V.}$
Voltage across B, $v_B = 0.766 \times 160.5 = 122.9 \text{ V.}$
- (iv) $\cos \phi_A = \frac{120}{143.4} = 0.837 \text{ (lagging) or, } \phi_A = 33.175^\circ$
and $\cos \phi_B = \frac{100}{160.5} = 0.623 \text{ (lagging) or, } \phi_B = 51.46^\circ.$
 $\therefore \text{ The phase difference } \phi = 51.46^\circ - 33.175^\circ = 18.285^\circ.$

14.72 Two coils are connected in series. When 2A d.c. is passed through the circuit, the voltage drop across the coils are 20 V, and 30 V respectively and when 2 A ac is passed at 40 Hz, the drop becomes 140 V and 100 V respectively. If two coils are connected to 230 V, 50 Hz mains, calculate the current flowing through the coils.

Solution

DC condition

$$R_A = \frac{20}{2} = 10 \Omega, \quad R_B = \frac{30}{2} = 15 \Omega.$$

AC condition

$$Z_A = \frac{140}{2} = 70 \text{ ohm, } Z_B = \frac{100}{2} = 50 \Omega.$$

$$\therefore X_A = \sqrt{70^2 - 10^2} = \sqrt{4900 - 100} = 69.3 \Omega.$$

$$\therefore X_B = \sqrt{50^2 - 15^2} = \sqrt{2500 - 225} = 47.7 \Omega.$$

Since X is proportional to frequency, therefore at 50 Hz,

$$X_A = 69.3 \times \frac{5}{4} = 86.6 \Omega.$$

$$X_B = 47.7 \times \frac{5}{4} = 59.7 \Omega.$$

For the total series circuit $(R) = 10 + 15 = 25 \Omega$

(since resistance is independent of frequency) and

$$X = 86.6 + 59.7 = 146.3 \Omega \text{ (at 50 Hz).}$$

$$\therefore \text{ Now } Z = \sqrt{25^2 + 146.3^2} = 148.1 \Omega.$$

$$\therefore \text{ Current } I = \frac{230}{148.1} = 1.55 \text{ A (at 50 Hz).}$$

14.73 A resistor of 8Ω is connected in series with an inductive load and the combination is placed across a 100 V supply mains. A voltmeter when connected across the load and then across the resistor and indicates 48 V and 64 V respectively.

Find

- the power consumed by the load.
- the power consumed by the resistor
- the total power taken by the supply
- the power factors of the load and the whole circuit.

Solution

- Current in 8Ω resistor (i.e., the current in the circuit) $= 64/8 = 8 \text{ A.}$

14.75 An inductance coil of $8\ \Omega$ resistance and $0.02\ \text{H}$ inductance is connected in parallel with another inductive coil of $10\ \Omega$ resistance $0.05\ \text{H}$ inductance. The combination is connected across a $10\ \text{V}$, $50\ \text{Hz}$ supply. A capacitor of $80\ \mu\text{F}$ is connected in series with a $20\ \Omega$ resistor and the combination is connected in parallel with the same supply. Calculate the total current taken from the mains and its phase angle with respect to the applied voltage.

Solution

Let the branches be A , B , C respectively.

then: $X_A = 2\pi fL = 2 \times 3.14 \times 50 \times 0.02 = 6.28\ \Omega$

$$Z_A = \sqrt{8^2 + 6.28^2} = 10.2\ \Omega.$$

and $\cos \phi_A = \frac{8}{10.2} = 0.785$ (lagging)

$$\sin \phi_A = \frac{6.28}{10.2} = 0.616.$$

$$I_A = \frac{100}{10.2} = 9.8\ \text{A}.$$

Next, $X_B = 2 \times 3.14 \times 50 \times 0.05 = 15.7\ \Omega.$

$$Z_B = \sqrt{10^2 + 15.7^2} = \sqrt{100 + 246.5} = 18.6\ \Omega.$$

$$\cos \phi_B = \frac{10}{18.6} = 0.537$$
 (lagging)

$$\sin \phi_B = \frac{15.7}{18.6} = 0.845$$

$$I_B = \frac{100}{18.6} = 5.37\ \text{A}.$$

In branch C , $X_C = \frac{1}{2\pi fC} = \frac{10^6}{2 \times 3.14 \times 50 \times 80} = 39.8\ \Omega.$

then, $Z_C = \sqrt{20^2 + 39.8^2} = 44.54\ \Omega.$

$$\cos \phi_C = \frac{20}{44.54} = 0.449$$
 (leading).

$$\sin \phi_C = \frac{39.8}{44.54} = 0.894$$

$$I_C = \frac{100}{44.54} = 2.24\ \text{A}.$$

Adding the active and reactive current components (I_a and I_r respectively)

$$I_a = I_A \cos \phi_A + I_B \cos \phi_B + I_C \cos \phi_C$$

$$= (9.8 \times 0.785) + (5.37 \times 0.537) + (2.24 \times 0.449) = 11.59\ \text{A}.$$

$$I_r = -I_A \sin \phi_A - I_B \sin \phi_B + I_C \sin \phi_C$$

$$= -(9.8 \times 0.616) - (5.37 \times 0.845) + (2.24 \times 0.894)$$

$$= -6.04 - 4.54 + 2.00 = -8.54.$$

Then $(I) = \sqrt{I_a^2 + I_r^2} = \sqrt{11.59^2 + 8.54^2} = 14.38\ \text{A};$

$$\cos \phi = \frac{11.59}{14.38} = 0.805$$
 (lagging), $\phi = 36^\circ$ (approx).

14.76 Three loads, $2\ \Omega$, $4\ \Omega$ and $5\ \Omega$ are connected across the ac lines as shown in Fig. 14.61. The resistances of the lines as well as the neutral has value of $1\ \Omega$ each. Obtain the amount of power delivered to each of the three loads as well as the power loss in the neutral wire and the lines.

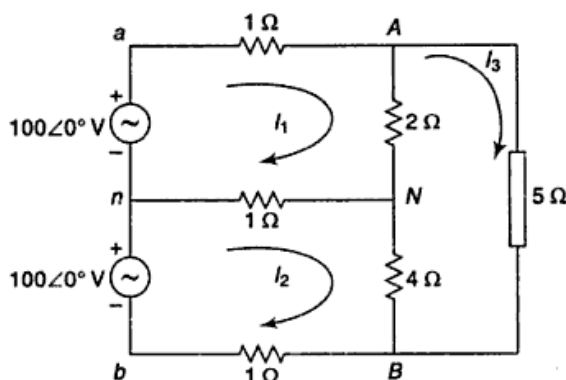


Fig. 14.61

Solution

The three loads in the circuit are $2\ \Omega$, $4\ \Omega$ and $5\ \Omega$. The two lines are aA and bB having resistance of $1\ \Omega$ each and neutral nN has resistance of $1\ \Omega$.

The mesh currents are respectively I_1 , I_2 and I_3 .

The three mesh equations are

$$-100\angle 0^\circ + I_1 + 2(I_1 - I_3) + (I_1 - I_2) = 0$$

$$-100\angle 0^\circ + (I_2 - I_1) + 4(I_2 - I_3) + I_2 = 0$$

$$5I_3 + 4(I_3 - I_2) + 2(I_3 - I_1) = 0$$

The above equations can be rearranged as

$$4I_1 - I_2 + 2I_3 = 100\angle 0^\circ$$

$$-I_1 + 6I_2 - 4I_3 = 100\angle 0^\circ$$

$$2I_1 + 4I_2 - 11I_3 = 0$$

Solving the equations we get

$$I_1 = 30.23\ \angle 0^\circ\ \text{A}$$

$$I_2 = 22.1\ \angle 0^\circ\ \text{A}$$

and

$$I_3 = 0.59\ \angle 0^\circ\ \text{A}.$$

\therefore Current through $1\ \Omega$ resistor in line aA is $30.23\ \angle 0^\circ\ \text{A}$, current through $1\ \Omega$ resistor in line bB is $-22.1\ \angle 0^\circ\ \text{A}$.

Also, I_n (current through neutral) = $I_2 - I_1 = -8.13\ \angle 0^\circ\ \text{A}$.

Hence power loss in the two lines and the neutral wire are:

$$P_{aA} = (30.23)^2 \times 1 = 913.853\ \text{W}.$$

$$P_{bB} = (22.1)^2 \times 1 = 488.4\ \text{W}.$$

$$P_{nN} = (8.13)^2 \times 1 = 66.097\ \text{W}.$$

Power delivered to the loads:

$$P_{2\Omega} = (I_1 - I_3)^2 \times 2 = (30.23 - 0.59)^2 \times 2 = 1757\ \text{W}.$$

$$P_{4\Omega} = (I_2 - I_3)^2 \times 4 = (22.1 - 0.59)^2 \times 4 = 1850.7\ \text{W}.$$

$$P_{5\Omega} = I_3^2 \times 5 = (0.59)^2 \times 5 = 1.7405\ \text{W}.$$

.....

14.77 Determine the value of v in the circuit shown in Fig. 14.62.

Solution

As $3\ \Omega$ and $2\ \Omega$ are in parallel, voltage across each of the resistances is v and combining them the circuit is redrawn as shown in Fig. 14.63.

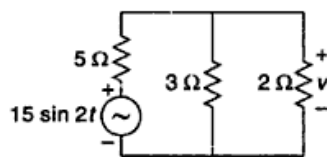


Fig. 14.62

14.83 Determine v and i_1 at $t = (0+)$ for the circuit shown in Fig. 14.74 if $v(0^-) = V_o$.

Solution

$5\ \Omega$ and $10\ \Omega$ resistors are in parallel and the combination is in series with $6\ \Omega$ resistor. The equivalent resistance is thus $\left[6 + \frac{5 \times 10}{5 + 10}\right]$ i.e., $9.33\ \Omega$. The simplified circuit is shown in Fig. 14.75.

$$\begin{aligned} \text{Now,} \quad v &= V_o e^{-\frac{t}{9.33C}} \\ \text{At} \quad t &= (0+), v = V_o \\ i &= C \frac{dv}{dt} = CV_o \left(-\frac{1}{9.33C} \right) e^{-\frac{t}{9.33C}} \\ \text{or} \quad i &= -\frac{V_o}{9.33} e^{-\frac{t}{9.33C}} \\ \text{At} \quad t &= 0+, i = -\frac{V_o}{9.33} \end{aligned}$$

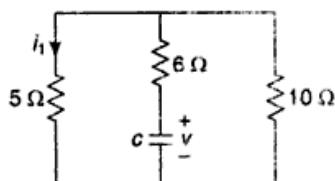


Fig. 14.74

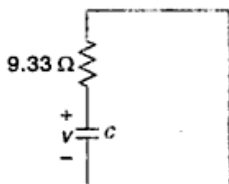


Fig. 14.75

14.84 Find the current i through the $50\ \Omega$ resistor in Fig. 14.76 at (i) $t = (0^-)$, (ii) $t = (0^+)$, (iii) $t = \infty$ and (iv) $t = 2\text{ ms}$.

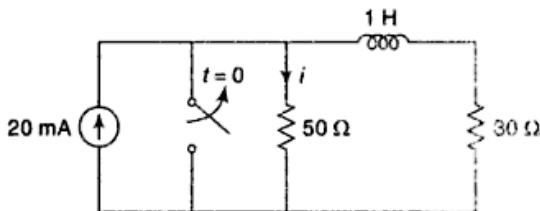


Fig. 14.76

Solution

(i) At $t = 0^-$

$i = 0$ (\because 20 mA will flow through the short circuited path i.e., through the switch)

(ii) At $t = 0^+$

There are two parallel paths: One is a $50\ \Omega$ resistor, another is a $30\ \Omega$ resistor in series with 1 H inductor. According to the property of the inductor no current will flow through it at $t = 0+$. Hence all current will flow through the $50\ \Omega$ resistor.

\therefore At $t = 0+, i = 20\text{ mA}$.

(iii) At $t = \infty$, inductor will act as a short circuit.

Hence current i at $t = \infty$ is $20 \times \frac{30}{30 + 50} = \frac{600}{80} = 7.5\text{ mA}$ (flowing through $50\ \Omega$ resistor).

(iv) Current through the $30\ \Omega$ resistor at $t = \infty$ is $I_o = 20 \times \frac{50}{50 + 30} = 12.5\text{ mA}$.

At any time t , current through the inductor is, $I_o e^{-t/\lambda} = 12.5 e^{-(t/30)} = 12.5 e^{-30t}$ mA. At $t = 2\text{ ms}$ current through the $30\ \Omega$ resistor is thus $12.5 e^{-30 \times 2 \times 10^{-3}}$ mA i.e., 11.77 mA . Thus current through $50\ \Omega$ resistor at $t = 2\text{ ms}$, is $(20\text{ mA} - 11.77\text{ mA})$ i.e., 8.23 mA .

14.85 What is reading shown by the wattmeter in the circuit of Fig. 14.77? Identify the source s generating this power. The positive terminal of the potential coil of the wattmeter is connected separately to (i) x , (ii) y and (iii) z . Check your result in each case.

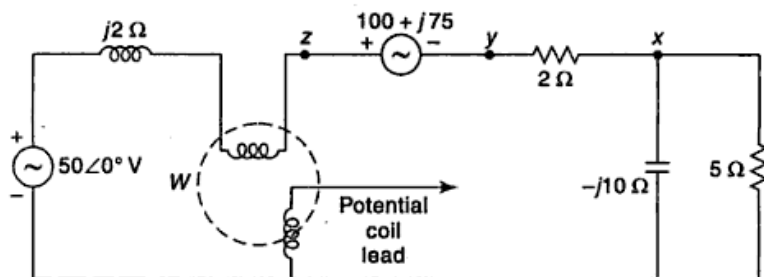


Fig. 14.77

Solution

The parallel combination of $5\ \Omega$ and $-j10\ \Omega$ is

$$\frac{5(-j10)}{5 - j10} = \frac{50\angle -90^\circ}{11.18\angle -63.43^\circ} = 4.472\angle -26.56^\circ\ \Omega = (4 - j2)\ \Omega.$$

Let us consider that a current I flows through the mesh. Hence applying KVL we get $-50\angle 0^\circ + j2I + (100 + j75) + 2I + (4 - j2)I = 0$

$$\text{or } -50 - j75 - 6I = 0$$

$$\text{or } I = -\frac{50 + j75}{6} = -8.33 - j12.5 = 15\angle -123.68^\circ\ \text{A}.$$

- (i) When the potential coil lead is connected at point x the wattmeter measures the potential given by

$$\begin{aligned} \frac{5(-j10)}{5 - j10} \times 15\angle -123.68^\circ &= 4.472\angle -26.56^\circ \times 15\angle -123.68^\circ \\ &= 67.08\angle -150.24^\circ\ \text{V}. \end{aligned}$$

The wattmeter reading is: $67.08 \times 15 \cos(-150.24^\circ + 123.68^\circ) = 900\ \text{W}$.

As the potential coil is in parallel with the $5\ \Omega$ resistor this power is absorbed by $5\ \Omega$ resistor.

- (ii) When the potential coil lead is connected at point y wattmeter measures the potential:

$$\begin{aligned} 50\angle 0^\circ - j2I - (100 + j75) &= 50 - j2 \times 15\angle -123.68^\circ - 100 - j75 \\ &= -50 - j75 + j16.636 - 24.96 \\ &= (-74.96 - j58.364) = 95\angle -142.1^\circ\ \text{V}. \end{aligned}$$

The wattmeter reading is thus, $[95 \times 15 \cos(-142.1^\circ + 123.68^\circ)]$ or $1352\ \text{W}$.

This power is absorbed by the $2\ \Omega$ and $5\ \Omega$ resistor.

- (iii) When the potential coil lead is connected at point Z , the wattmeter measures the potential:

$$(50 - j2I)\ \text{V, i.e., } 50 - j2 \times 15\angle -123.68^\circ\ \text{V}.$$

The measured potential is thus $(50 - 30\angle -33.68^\circ)$ or, $(25 + j16.63)\ \text{V}$ or, $30\angle 33.65^\circ\ \text{V}$.

The wattmeter reading is therefore $[30 \times 15 \cos(33.53^\circ + 123.68^\circ)]\ \text{W}$ or, $(-415.172)\ \text{W}$.

As the reading is negative this power is absorbed by a $50\ \text{V}$ source.

$$\begin{aligned}
 &= \left[\frac{1}{T} \int_0^T 36 \cos^2 (25t) dt + \frac{1}{T} \int_0^T 60 \cos^3 (25t) dt + \frac{1}{T} \int_0^T 25 \cos^4 (25t) dt \right]^{1/2} \\
 &= \left[\frac{36}{T} \int_0^T \left(\frac{1}{2} + \frac{1}{2} \cos (50t) \right) dt + \frac{60}{T} \int_0^T \left(\frac{1}{2} \cos (25t) + \frac{1}{4} \cos (75t) + \frac{1}{4} \cos (25t) \right) dt \right. \\
 &\quad \left. + \frac{25}{T} \int_0^T \left(\frac{1}{4} + \frac{1}{2} \cos (50t) + \frac{1}{8} + \frac{1}{8} \cos (100t) \right) dt \right]^{1/2} \\
 &= \left[\frac{36 \times 25}{2} \left(\frac{1}{25} \right) + 60 \times 25 \times 0 + 25 \times 25 \left(\frac{1}{4} + \frac{1}{8} \right) \times \frac{1}{25} \right]^{1/2} \quad \left[\because T = \frac{1}{25} \text{ s} \right] \\
 &= \sqrt{18 + \frac{75}{8}} = 5.232 \text{ V.}
 \end{aligned}$$

14.89 For the circuit shown in Fig. 14.79 determine the power factor of the combined load if load impedance $Z_L = 15 \Omega$.

Solution

$$\begin{aligned}
 \text{Current through the circuit, } I &= \frac{100 \angle 30^\circ}{5 - j8 + 15} \\
 &= \frac{100 \angle 30^\circ}{20 - j8} \\
 &= \frac{100 \angle 30^\circ}{21.54 \angle -21.8^\circ} = 4.64 \angle 51.8^\circ \text{ A.}
 \end{aligned}$$

Hence power factor is $\cos (51.8^\circ - 30^\circ) = 0.928$ leading.
(since current is leading w.r.t. voltage)

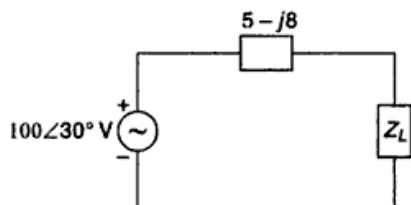


Fig. 14.79

14.90 Calculate the average power delivered to each passive element for the circuit shown in Fig. 14.80.

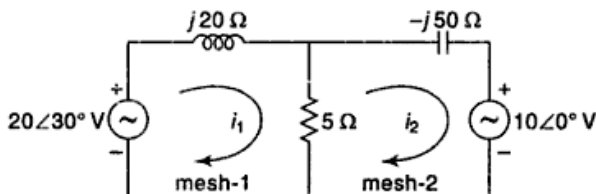


Fig. 14.80

Solution

Applying KVL in mesh 1,

$$-20 \angle 30^\circ + j20i_1 + 5(i_1 - i_2) = 0 \quad (i)$$

Applying KVL in mesh 2,

$$-j50i_2 + 10 \angle 0^\circ + 5(i_2 - i_1) = 0 \quad (ii)$$

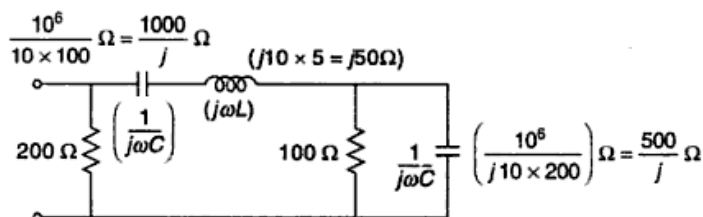


Fig. 14.91

Here, 100Ω and $500/j \Omega$ (or $-j500 \Omega$) are in parallel. Their combined impedance is $\left(\frac{100(-j500)}{100 - j500} \right)$ or $\left(\frac{-j500}{1 - j5} \right)$.

Also, $j50 \Omega$ and $\left(\frac{1000}{j} \right) \Omega$ or, $(-j1000 \Omega)$ are in series with $\left(\frac{-j500}{1 - j5} \right) \Omega$.

Their combined impedance is obtained as

$$\begin{aligned} Z_1 &= j50 - j1000 - \frac{j500}{(1 - j5)} \\ &= -j950 - \frac{500 \angle 90^\circ}{5.099 \angle -78.69^\circ} \\ &= -j950 - 98.058 \angle 168.69^\circ = (96.15 - j969.23) \Omega = 973.99 \angle -84.33^\circ \Omega. \end{aligned}$$

However, Z_1 is in parallel with 200Ω . hence the equivalent impedance of the network is

$$\frac{200 \times 973.99 \angle -84.33^\circ}{200 + 973.99 \angle -84.33^\circ} = \frac{200 \times 973.99 \angle -84.33^\circ}{296.15 - j969.23} = 192.2 \angle -11.32^\circ \Omega.$$

.....

14.102 Determine the voltage across the series combination of a resistor of 100Ω and inductor of 100 mH when a current of $10e^{j4000t} \text{ mA}$ flows through them.

Solution

The phasor form of current of $(10e^{j4000t}) \text{ mA}$ can be written as

$$I = 10 \angle 0^\circ \text{ mA with angular velocity of } 4000 \text{ rad/s.}$$

Impedance $Z = R + j\omega L = 100 + j \times 4000 \times 0.1 = 100 + j400 = 412.3 \angle 75.96^\circ \Omega$.

Voltage across the series combination is $10 \angle 0^\circ \times 10^{-3} \times 412.3 \angle 75.96^\circ = 4.123 \angle 75.96^\circ \text{ A}$.

or, we can say the voltage across the series combination is $4.123e^{j(4000t + 75.96^\circ)} \text{ V}$.

.....

14.103 Determine the values of i_1 , i_2 and i_3 in the circuit shown in Fig. 14.92 at $t = 0.2 \text{ s}$.

.....

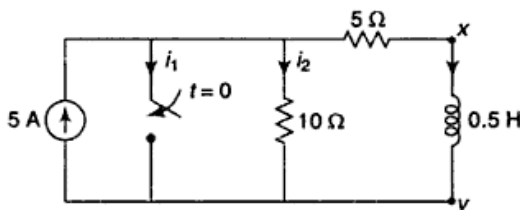


Fig. 14.92

Solution

For $t < 0$,

$$i_1 = 0$$

$$i_2 = 5 \times \frac{5}{5+10} = \frac{25}{15} = \frac{5}{3} \text{ A}$$

$$i_3 = 5 \times \frac{10}{10+5} = \frac{50}{15} = \frac{10}{3} \text{ A}$$

For $t > 0$, total current of 5 A from current source flows through the short circuited path and 10Ω resistor is shorted out.

Hence for $t > 0$ (at $t = 0.2$ s) $i_2 = 0$ A. Now, at $t < 0$ current through the inductor is

$$I_0 = i_3 = \frac{10}{3} \text{ A}.$$

Hence, at $t > 0$,

$$i_3 = I_0 e^{-\lambda t}, \text{ where } \lambda = \frac{0.5}{5} = 0.1 \text{ s}^{-1}.$$

\therefore At $t = 0.2$ s

$$i_3 = \frac{10}{3} e^{-\frac{0.2}{0.1}} = 0.45 \text{ A}.$$

The current 0.45 completes its path through the short circuited path.

Hence, $i_1 = 5 - 0.45 = 4.55$ A at $t = 0.2$ s.

[At $t = 0+$, i_3 will continue to flow in the same direction before switching as the current through the inductance will not change instantly following switching, thus i_3 will have direction flowing from node x to node y during $t = 0(-)$ as well as during $t = 0(+)$.]

14.104 A voltage $v = 3000 \sin \omega t + 500 \sin 3\omega t + 200 \sin 5\omega t$ is applied to a series R - L - C circuit having a resistance of 15Ω , capacitance of $50 \mu\text{F}$ and a variable inductance. Determine the value of the inductance that will give resonance with the third harmonic. Find the rms values of voltage and current with this value of inductance in the circuit. Assume $\omega = 300 \text{ rad/s}$. Also find the rms value of the total current.

Solution

For resonance with the third harmonic,

$$(3\omega)^2 = \frac{1}{LC} \quad \left[\because \omega_n = \frac{1}{\sqrt{LC}}; \text{ here } \omega_n = (3\omega) \right]$$

$$\text{or } (3 \times 300)^2 = \frac{1}{LC}$$

$$\text{or } L = \frac{1}{(900)^2 \times 50 \times 10^{-6}} = 0.0247 \text{ H}.$$

$$\text{Rms value of voltage} = \frac{1}{\sqrt{2}} \sqrt{(3000)^2 + (500)^2 + (200)^2} = 2155.23 \text{ V}.$$

For the third harmonic

$$X_L (=X_C) = 3 \times 300 \times 0.0247 = 22.23 \Omega$$

Peak value of third harmonic current is $\frac{500}{15}$ A, or, 33.33 A.

For fundamental frequency

$$\begin{aligned} Z_1 &= 15 + j \left(\omega L - \frac{1}{\omega C} \right) = 15 + j \left(\frac{22.23}{3} - 3 \times 22.23 \right) \\ &= 15 - j59.28 = 61.15 \angle -75.8^\circ \text{ W} \end{aligned}$$

Peak value of fundamental current is thus $\frac{3000}{61.15}$ A, 49.06 A.

For the fifth harmonic, we have

$$\begin{aligned} Z_5 &= 15 + j \left(\frac{22.23}{3} \times 5 - \frac{3 \times 22.23}{5} \right) \\ &= 15 + j23.712 = 28.06 \angle 57.68^\circ \Omega. \end{aligned}$$

Peak value of the fifth harmonic current is $\left(\frac{200}{28.06} \right)$ A or, 7.127 A.

∴ Rms value of the total current

$$\frac{1}{\sqrt{2}} \sqrt{(33.33)^2 + (49.06)^2 + (7.127)^2} = 42.25 \text{ A.}$$

.....

14.105 A voltage $v = 100 \sin \omega t + 75 \sin \left(3\omega t + \frac{\pi}{3} \right) + 40 \sin \left(5\omega t + \frac{5\pi}{6} \right)$ is applied to a circuit of resistance 30Ω and inductance 0.075 H . Derive (i) expression for current (ii) the rms value of current and voltage (iii) total power supplied and power factor. Assume $\omega = 314 \text{ rad/s}$.

Solution

Fundamental reactance, $X_1 (= \omega L) = 314 \times 0.075 \Omega = 23.55 \Omega$.

Fundamental impedance, $Z_1 = \sqrt{(30)^2 + (23.55)^2} \angle \tan^{-1} \left(\frac{23.55}{30} \right) = 38.14 \angle 38.14^\circ \Omega$.

Fundamental current, $i_1 = \frac{100}{38.14} \sin (\omega t - 38.14^\circ) = 2.622 \sin (\omega t - 38.14^\circ) \text{ A}$

rms value of fundamental current is $\frac{2.622}{\sqrt{2}} = 1.854 \text{ A}$.

rms value of fundamental voltage is $\frac{100}{\sqrt{2}} \text{ V} = 70.71 \text{ V}$.

Fundamental power $(= i_1^2 R) = (1.854)^2 \times 30 = 103.12 \text{ W}$.

Similarly for third harmonic $X_3 (= 3 \omega L) = 3 \times 23.55 \Omega = 70.65 \Omega$.

$$Z_3 = \sqrt{(30)^2 + (70.65)^2} \angle \tan^{-1} \left(\frac{70.65}{30} \right) = 76.755 \angle 67^\circ \Omega$$

$$i_3 = \frac{75}{76.755} \sin \left(3\omega t + \frac{\pi}{3} - 67^\circ \right) = 0.977 \sin (3\omega t - 7^\circ) \text{ A.}$$

rms value of current is $\frac{0.977}{\sqrt{2}} \text{ A} = 0.691 \text{ A}$.

rms value of voltage is $\frac{75}{\sqrt{2}} \text{ A} = 53 \text{ V}$.

Power $i_3^2 R = (0.691)^2 \times 30 \text{ W} = 14.32 \text{ W}$

For the 5th harmonic,

$$X_5 (= 5 \omega L) = 5 \times 23.55 = 117.75 \Omega$$

$$Z_5 = \sqrt{(30)^2 + (117.75)^2} \angle \tan^{-1} \frac{117.75}{30} = 121.51 \angle 75.7^\circ \Omega$$

$$i_5 = \left(\frac{40}{121.51} \right) \sin \left(5\omega t + \frac{5\pi}{6} - 75.7^\circ \right) = 0.329 \sin (5\omega t + 74.3^\circ)$$

Solution

In a parallel ac circuit resonance occurs when the net susceptance of the circuit is zero.

$$\begin{aligned}\text{However, admittance } y &= \frac{1}{R + j\omega L} + j\omega C \\ &= \frac{R - j\omega L}{R^2 + \omega^2 L^2} + j\omega C = \frac{R - j\omega L + j\omega C (R^2 + \omega^2 L^2)}{R^2 + \omega^2 L^2}\end{aligned}$$

∴ At resonance,

$$C(R^2 + \omega^2 L^2) = L$$

$$\text{or } \omega^2 = \frac{L - CR^2}{CL^2} = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\text{or } \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\therefore \text{At resonance, } y = \frac{R}{R^2 + \omega^2 L^2} = \frac{R}{R^2 + L^2 \left(\frac{1}{LC} - \frac{R^2}{L^2} \right)} = \frac{R}{R^2 + \left(\frac{L}{C} - R^2 \right)}$$

Here, $R = 2 \, \Omega$, $L = 20 \times 10^{-6} \, \text{H}$ and $C = 1 \times 10^{-6} \, \text{F}$.

$$\text{Hence } (y) = \frac{2}{2^2 + \left(\frac{20 \times 10^{-6}}{1 \times 10^{-6}} - 2^2 \right)} = \frac{2}{4 + (20 - 4)} = 0.1 \, \text{S}.$$

Current input for resonance frequency is $I = Vy = 230 \times 0.1 = 23 \, \text{A}$.

At 90% of resonant frequency, the frequency is

$$\begin{aligned}\omega_1 &= 0.9 \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = 0.9 \sqrt{\frac{10^{12}}{20 \times 1} - \frac{2^2}{400 \times 10^{-12}}} \\ &= 0.9 \times 10^6 \sqrt{\frac{1}{20} - \frac{4}{400}} = 0.18 \times 10^6 \, \text{rad/s}.\end{aligned}$$

$$\begin{aligned}\therefore y_1 &= \frac{R + j\omega_1 (R^2 C + \omega_1^2 L^2 C - L)}{R^2 + \omega_1^2 L^2} \\ &= \frac{2 + j\omega_1 \{ (4 \times 10^{-6} + (0.18 \times 20)^2 10^{-6} - 20 \times 10^{-6}) \}}{2^2 + (0.18 \times 20)^2} \\ &= (0.1179 - j0.032) \, \text{S} = 0.122 \angle -15.185^\circ \, \text{S}\end{aligned}$$

Hence current input is $Vy_1 (= 230 \times 0.122)$ or, 28.06 A.

14.108 Determine the impedance of the circuit shown in Fig. 14.93 and the power consumed in each branch.

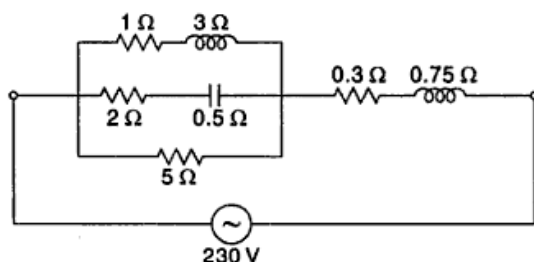


Fig. 14.93

$$\text{i.e.} \quad R = \frac{8}{0.05 \omega^2 C} \quad \text{and} \quad \omega^2 C = \frac{1}{0.05}.$$

$$\text{Hence,} \quad R = \frac{8}{0.05 \times \frac{1}{0.05}} = 8 \, \Omega$$

$$\text{Total impedance is} \quad \left[\frac{8R + \frac{0.05}{C}}{8 + R} \right] \text{ i.e., } \left[\frac{64 + \frac{0.05}{C}}{8 + 8} \right] \Omega.$$

$$\therefore Z = \frac{64 + (0.05/C)}{16} \Omega.$$

$$\text{Also,} \quad Z = \frac{V}{I} = \frac{150}{25} = 6 \, \Omega$$

$$\therefore 6 = \frac{64 + (0.05/C)}{16}$$

$$\text{or} \quad C = 1.56 \, \text{mF}.$$

Hence the resistance and capacitance of the shunt circuit is $8 \, \Omega$ and $1.56 \, \text{mF}$ respectively.

14.112. Two impedances having the same magnitude are joined in parallel. The p.f. of one impedance is 0.7 and that of other is 0.6. Determine the p.f. of the combination.

Solution

Let (Z) be the magnitude of each impedance. For the first impedance we have

$$\cos \theta_1 = 0.7 \text{ and hence } \sin \theta_1 = 0.714$$

$$\text{Hence,} \quad Z_1 = Z(0.7 + j0.714)$$

$$\text{Similarly,} \quad Z_2 = Z\{0.6 + j \sin(\cos^{-1} 0.6)\} = Z(0.6 + j0.8)$$

The impedance of the parallel combination

$$\begin{aligned} \frac{Z_1 Z_2}{Z_1 + Z_2} &= \frac{Z^2 (0.7 + j0.714)(0.6 + j0.8)}{Z(0.7 + 0.6 + j0.714 + j0.8)} \\ &= Z \cdot \frac{0.999 \angle 98.7^\circ}{1.995 \angle 49.35^\circ} = Z(0.5 \angle 49.35^\circ) \, \Omega \end{aligned}$$

Hence the power factor of the combination is $\cos 49.35^\circ = 0.65$

14.113. An inductive coil is connected across a variable frequency alternating current source of 230 V. When the frequency is 100 Hz, the current is 20 A and when the frequency is 60 Hz, the current is 25 A. Determine the coil parameters and the time constant of the coil.

Solution

Let R and L be the resistance and inductance of the coil.

When the frequency is 100 Hz

$$\frac{230}{20} = \sqrt{R^2 + (2\pi \times 100L)^2}$$

$$\text{or} \quad R^2 + 394784.2 L^2 = 132.25 \quad (\text{i})$$

When the frequency is 60 Hz

$$\frac{230}{25} = \sqrt{R^2 + (2\pi \times 60L)^2}$$

$$\text{or} \quad R^2 + 142122.3 L^2 = 84.64 \quad (\text{ii})$$

Solving equation (i) and equation (ii) we get

$$L = 0.01373 \text{ H}$$

and $R = 7.61 \Omega$.

Time constant of the coil is $\left(\frac{L}{R}\right) = \frac{0.01373}{7.61} \text{ s} = 0.0018 \text{ s} = 1.8 \text{ ms}$.

14.114 An inductive coil takes 20 A and dissipates 1500 W when connected to a 230 V, 50 Hz. supply. Determine the impedance, resistance, reactance and power factor of the circuit.

Solution

Given $I = 20 \text{ A}$
 $P = 1500 \text{ W}$
 $V = 230 \text{ V}$

Impedance, $ZI = \frac{|V|}{|I|} = \frac{230}{20} = 11.5 \Omega$.
 $P = VI \cos \theta$.

Hence p.f. $(\cos \theta) = \frac{P}{VI} = \frac{1500}{230 \times 20} = 0.326$.

Resistance, $R = Z \cos \theta = 11.5 \times 0.326 = 3.749 \Omega$

Reactance, $X = Z \sin \theta = 11.5 \times \sin (\cos^{-1} 0.326) = 10.87 \Omega$

14.115 An iron cored coil of resistance 8Ω takes 12 A when connected to a 230 V, 50 Hz mains. The power dissipated is 1500 W. Determine the iron loss, inductance and power factor. Assume the coil to be equivalent to a series impedance.

Solution

Resistance of the coil, $R = 8 \Omega$.

$I = 12 \text{ A}$
 $V = 230 \text{ V}$

Impedance $Z = \frac{|V|}{|I|} = \frac{230}{12} \Omega = 19.17 \Omega$

Ohmic loss is, $I^2 R = (12)^2 \times 8 = 1152 \text{ W}$

Total power dissipated is 1500 W.

Hence iron loss = $(1500 - 1152) = 348 \text{ W}$.

Total resistance (resistance of coil + resistance of core) = $\frac{1500}{(12)^2} \Omega = 10.42 \Omega$.

Inductive reactance $X = \sqrt{(19.17)^2 - (10.42)^2} = 16.09 \Omega$.

Inductance = $\frac{16.09}{2\pi \times 50} = 0.05 \text{ H}$.

p.f. of the circuit = $\frac{10.42}{19.17} = 0.543$.

14.116 An alternating voltage of $(100 + j80)$ is applied to a circuit and current through the circuit is $(10 + j15) \text{ A}$. Determine the impedance of the circuit, power consumed and the phase angle.

Solution

Impedance $Z = \frac{V}{I} = \frac{100 + j80}{10 + j15} = \frac{128.06 \angle 38.66^\circ}{18.03 \angle 56.31^\circ} = 7.103 \angle -17.65^\circ \Omega$.

Power consumed $P = VI \cos \theta = 128.06 \times 18.03 \cos 17.65^\circ = 2200 \text{ W}$.

Phase angle is 17.65° .

14.117 An attracted armature type of relay operating at 250 V, 50 Hz single phase ac supply draws a current of 4 A at p.f. 0.15 lag to attract the plunger from open to closed position. The same relay draws 1.5 A at p.f. of 0.07 lag when the armature operates (i.e. in closed position). How much energy is spent in operating the relay?

Solution

When the plunger is at open position, the impedance

$$Z = \frac{V}{I} = \frac{250}{4} \Omega = 62.5 \Omega.$$

Power factor ($\cos \theta$) = 0.15

Inductive reactance $X = Z \sin \theta = 62.5 \sin (\cos^{-1} 0.15) = 61.8 \Omega$.

Inductance $L = \frac{61.8}{2\pi \times 50} = 0.196 \text{ H}$

Hence energy stored is $\left(\frac{1}{2} LI^2\right) = \frac{1}{2} \times 0.196 \times (4)^2 = 1.57 \text{ J}$

When the plunger is at closed position

Impedance $Z = \frac{V}{I} = \frac{250}{1.5} \Omega = 167 \Omega$

Power factor ($\cos \theta$) = 0.07.

Inductive reactance $X = Z \sin \theta = 167 \sin (\cos^{-1} 0.07) = 166.5 \Omega$.

Inductance $L = \frac{166.5}{2\pi \times 50} \text{ H} = 0.53 \text{ H}$.

Hence energy stored is $\left(\frac{1}{2} LI^2\right) = \frac{1}{2} \times 0.53 \times (1.5)^2 = 0.59 \text{ J}$.

Energy spent in operating the relay is $(1.57 - 0.59) \text{ or, } 0.98 \text{ J}$.

14.118 The load taken from a single-phase supply consists of a filament lamp load of 10 kW at unity power factor, motor load of 80 kVA at 0.8 p.f. (lagging) and motor load of 40 kVA at 0.7 p.f. (leading). Find the total load taken from the supply in kW and in kVA and the p.f. of the combined load. Also calculate the main current if the supply voltage is 250 V.

Solution

Load (a): Apparent power, $S_a = \frac{\text{Active power}}{\text{Power factor}} = \frac{10}{1} = 10 \text{ kVA}$.

Active power $P_a = 10 \times 10 = \text{kW}$

Reactive power, $Q_a = S_a \times \sin \theta = 10 \times 0 = 0 \text{ KVAR}$.

Load (b): Apparent power, $S_b = 80 \text{ kVA}$ at a power factor of 0.8 (lagging).

Active power, $P_b = 80 \times 0.8 = 64 \text{ kW}$

Reactive power, $Q_b = 80 \times 0.6 = 48 \text{ KVAR (lagging)}$.

Load (c): Apparent power, $S_c = 40 \text{ kVA}$ at a power factor of 0.7 (leading).

Active power, $P_c = 28 \text{ kW}$

Reactive power, $Q_c = 40 \times 0.7143 = 28.57 \text{ KVAR}$

\therefore Total power taken from the supply (the net apparent power)

$= 10 + 80 + 40 = 130 \text{ kVA}$.

Total active power $= 10 + 64 + 28 = 102 \text{ kW}$

Total reactive power $= 0 + 48 - 28.57 = 19.40 \text{ KVAR}$

When one of the resistors is removed as shown in Fig. 14.95(a) and Fig. 14.95(b).

$$\text{Line current } I = \frac{V}{2R}$$

$$\text{Total power} = 2 \left(\frac{V}{2R} \right)^2 R = \frac{V^2}{R}$$

Hence, reduction in power is

$$\left(\frac{V^2}{R} \right) - \left(\frac{V^2}{2R} \right) = \frac{V^2}{2R} \text{ or } 50\%.$$

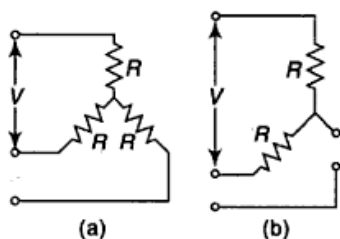


Fig. 14.95

(ii) When the load is delta connected,

$$\text{Phase current } I = \frac{V}{R}$$

$$\text{Total power is } \left[3 \left(\frac{V}{R} \right)^2 R \right] \text{ or } \frac{3V^2}{R}.$$

When one resistor is removed as shown in Fig. 14.96(a) and Fig. 14.96(b), then current in each

$$\text{resistor is } \frac{V}{R}.$$

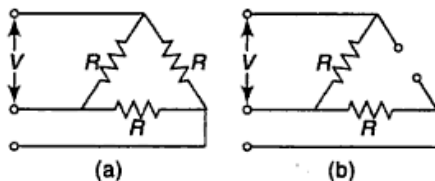


Fig. 14.96

$$\text{Total power is } 2 \left(\frac{V}{R} \right)^2 R \text{ or } \frac{2V^2}{R}$$

$$\text{Hence reduction in power is } \left(\frac{3V^2}{R} \right) - \left(\frac{2V^2}{R} \right), \text{ or, } \frac{V^2}{R}, \text{ i.e. } 33.3\%.$$

14.126 A three-phase star connected alternator supplied a 1500 H.P. delta connected induction motor having a power factor 0.8 and efficiency 90%. Determine the active and reactive components of the phase current of alternator and motor. Assume line voltage to be 1000 V.

Solution

$$\text{Output of the induction motor is } = (1500 \times 735.5) \text{ W} = 1103250 \text{ W}$$

$$\text{Input of the induction motor is } \frac{1103250}{0.9} \text{ W, or } 1225.83 \text{ kW.}$$

If the line current of induction motor be I then

$$\sqrt{3} VI \cos \theta = 1225.83 \times 10^3$$

$$\text{or } I = \frac{1225.83 \times 10^3}{\sqrt{3} \times 1000 \times 0.8} \text{ A} = 884.69 \text{ A}$$

Line current of the alternator is also (884.69) A

As alternator is star connected, hence phase current of alternator (= line current) = 884.69 A

Active component of current is $(884.69 \times 0.8) = 707.752 \text{ A}$

Reactive component of current is $[884.69 \sin (\cos^{-1} 0.8)] = 530.8 \text{ A}$

As motor is delta connected, we have,

$$\text{Phase current of motor} = \frac{884.69}{\sqrt{3}} \text{ A} = 510.776 \text{ A}$$

Active component of current = $(510.776 \times 0.8) 408.62 \text{ A.}$

Reactive component of current = $(510.776 \times 0.6) 306.46 \text{ A.}$

Solution

The three-phase system is shown in Fig. 14.99.

Considering E_R as reference, we can write

$$E_R = \frac{440}{\sqrt{3}} \angle 0^\circ \text{ V}; \quad E_Y = \frac{440}{\sqrt{3}} \angle -120^\circ$$

and $E_B = \frac{440}{\sqrt{3}} \angle -240^\circ$.

$$\begin{aligned} \text{Current through the } R \text{ branch } I_R &= \frac{440}{\sqrt{3}} \angle 0^\circ / j10 \\ &= 25.4 \angle -90^\circ \text{ A.} \end{aligned}$$

$$\text{Current through the } Y \text{ branch } I_Y = \left(\frac{440}{\sqrt{3}} \angle -120^\circ \right) / (-j15) = 16.935 \angle -30^\circ \text{ A.}$$

$$\text{Current through the } B \text{ branch } I_B = \frac{440}{\sqrt{3}} \angle -240^\circ / 20 = 12.7 \angle -240^\circ \text{ A.}$$

$$\begin{aligned} \text{The resultant current } I &= I_R + I_Y + I_B = 25.4 \angle -90^\circ + 16.935 \angle -30^\circ + 12.7 \angle -240^\circ \\ &= -j25.4 + 14.67 - j8.467 - 6.35 + j11 \\ &= 8.32 - j22.87 = 24.336 \angle -70^\circ \end{aligned}$$

Potential of the neutral point to earth

$$\begin{aligned} E_N &= \frac{24.336 \angle -70^\circ}{\frac{1}{j10} + \frac{1}{-j15} + \frac{1}{20}} = \frac{24.336 \angle -70^\circ}{0.05 - j0.1 + j0.067} = \frac{24.336 \angle -70^\circ}{0.05 - j0.033} \\ &= 404.975 \angle -36.575^\circ \text{ V.} \end{aligned}$$

$$\begin{aligned} \text{Voltage across load in phase } R \text{ is } (E_{RN}) &= E_R - E_N = \frac{440}{\sqrt{3}} \angle 0^\circ - 404.975 \angle -36.575^\circ \\ &= -73.22 + j241.31 \\ &= 252.17 \angle 106.88^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} \text{Voltage across load in phase } Y \text{ is } (E_{YN}) &= E_Y - E_N = \frac{440}{\sqrt{3}} \angle -120^\circ - 404.975 \angle -36.575^\circ \\ &= 450.724 \angle 177.29^\circ \text{ V.} \end{aligned}$$

Voltage across load in phase B is

$$(E_{BN}) = E_B - E_N = \frac{440}{\sqrt{3}} \angle 240^\circ - 404.975 \angle -36.575^\circ = 646 \angle 134.43^\circ \text{ V.}$$

14.130 Three equal inductors connected in star take 10 kW at power factor of 0.85 when connected to a 440 V, 3-wire supply. If one inductor is short circuited, determine the line currents.

Solution

$$\text{Line current before short circuit is } I_L = \frac{10,000}{\sqrt{3} \times 440 \times 0.85} = 15.437 \text{ A}$$

$$\text{Impedance in each phase } Z = \frac{440/\sqrt{3}}{15.437} \Omega = 16.456 \Omega$$

Power factor is $\cos \theta = 0.85$.

Hence, $\theta = 31.788^\circ$.

Suppose phase B is short-circuited. Hence star point N and phase B are now at same potential (ground potential).

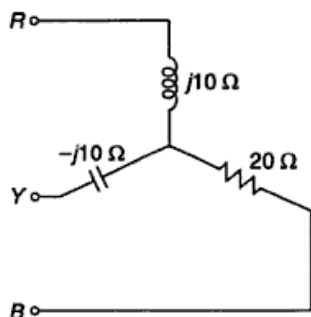


Fig. 14.99

The three line voltages before short are

$$V_{12} = 440 \angle 0^\circ \text{ V}$$

$$V_{23} = 440 \angle -120^\circ \text{ V}$$

$$V_{31} = 440 \angle -240^\circ \text{ V}$$

Since one inductor is shorted,

$$\begin{aligned} \text{Hence, } I_1 &= \left(\frac{V_{13}}{Z} \right) = \frac{-440 \angle -240^\circ}{16.456 \angle 31.788^\circ} \quad [\because V_{13} = -V_{31}] \\ &= -26.738 \angle -271.788^\circ \\ &= -0.834 - j26.72 = 26.738 \angle -91.787^\circ \text{ A} \end{aligned}$$

$$I_2 = \frac{V_{23}}{Z} = \frac{440 \angle -120^\circ}{16.456 \angle 31.788^\circ} = 26.738 \angle -151.788^\circ \text{ A}$$

$$\begin{aligned} \text{and } I_3 &= -(I_1 + I_2) = 0.834 + j26.72 + 23.56 + j12.64 \\ &= 24.394 + j39.36 = 46.3 \angle 58.21^\circ \text{ A.} \end{aligned}$$

14.131. Three equal impedances of 10Ω each and with a phase angle of 30° (lagging) makes a load on a three-phase alternator generating 100 V per phase. Calculate the current per line and the total power when connected as (i) alternator in star and load in star, (ii) load in delta but alternator in star, (iii) alternator as well as load in delta and (iv) alternator in delta but load in star.

Solution

(i) Given: Phase voltage = 100 V , impedance per phase of load = 10Ω .

$$\therefore \text{ Load current per phase} = \frac{100}{10} = 10 \text{ A}$$

$$\text{Line current (= phase current)} = 10 \text{ A}$$

$$\text{Total power } P = \sqrt{3} VI \cos \phi.$$

$$\text{But, } V_{\text{ph}} = \frac{1}{\sqrt{3}} V_{\text{line}} = 1.732 \times 100 = 173.2 \text{ V and } I = 10 \text{ A.}$$

$$\therefore P = \frac{\sqrt{3} \times 173.2 \times 10 \times \cos 30^\circ}{1000} = 2.598 \text{ kW.}$$

(ii) Line voltage = $(\sqrt{3} \times 100) \text{ V}$

$$\therefore \text{ Voltage per phase of load} = \frac{1}{\sqrt{3}} \times 100 \text{ V.}$$

$$\text{Current per phase of load} = \frac{V_{\text{ph}}}{Z_{\text{ph}}} = \frac{\frac{1}{\sqrt{3}} \times 100}{10} \text{ A}$$

$$\text{Line current (= phase current)} = \sqrt{3} \times \frac{1}{\sqrt{3}} \times 10 = 10 \text{ A}$$

$$\text{Total Power, } P = \sqrt{3} VI \cos \phi = \frac{\sqrt{3} \times 100 \times 10 \times 0.866}{1000} = 7.794 \text{ kW.}$$

(iii) Line voltage = 100 V

$$\text{Voltage per phase of load} = 100 \text{ V}$$

$$\text{Current per phase of load} = \frac{100}{10} = 10 \text{ A}$$

$$\text{Line current } (\sqrt{3} I_{\text{ph}}) = 1.732 \times 10 = 17.32$$

$$\text{Total power} = \sqrt{3} VI \cos \phi = \frac{\sqrt{3} \times 100 \times 17.32 \times 0.866}{1000} = 2.598 \text{ kW}$$

- (ii) If the machine is operated as a shunt generator with the same field flux, the armature and field resistance being 1.0Ω and 200Ω , determine the output current when the armature current is 25 A .
- (iii) If due to a drop in speed the emf becomes 380 V , determine the load current if a 40Ω load is connected at its terminals.

Solution

- (i) Here $Z = 90 \times 6 = 540$

$$\therefore E = \frac{540 \times 0.03 \times 1500}{60} \times \frac{4}{4} = 405 \text{ V}$$

$$[\because E = \frac{\phi Z N}{60} \cdot \frac{P}{A} \text{ and for lap wound } A = P]$$

- (ii) If $I_a = 25 \text{ A}$, the armature voltage drop is $(25 \times 1.0) = 25 \text{ V}$. Since the same field flux and speed are to be assumed, then the same emf is being generated.

From $V = E - I_a R_a$, we have

$$V = 405 - 25 \times 1 = 380 \text{ V}$$

$$\therefore I_{sh} = \frac{380}{200} = 1.9 \text{ A.}$$

Hence machine output current $= (I_a - I_{sh}) = (25 - 1.9) = 23.1 \text{ A}$.

- (iii) Let I_L = the load current

then $I_L \times 40 = V$ (the terminal voltage)

Also, $V = E - I_a R_a$

$$\text{or } V = 380 - I_a \times 1.0$$

$$\text{or } V = 380 - 1.0 (I_{sh} + I_L)$$

$$\therefore I_L \times 40 = 380 - I_{sh} - I_L$$

$$\text{or } 41 I_L = 380 - I_{sh} \quad (i)$$

$$\text{Also, } I_{sh} = \frac{V}{R_f} = \frac{V}{200} = \frac{40 I_L}{200} = \frac{I_L}{5} \quad (ii)$$

$$\therefore \text{ we have, } 41 I_L = 380 - \frac{I_L}{5} \quad [\text{using (ii) in (i)}]$$

$$\text{i.e. } I_L = \frac{1900}{206} = 9.22 \text{ A}$$

.....

14.139 A short shunt dc compound generator develops 250 V at its terminals and delivers a load current of 50 A . the resistances of the armature, series field and shunt field are 0.05Ω , 0.04Ω and 100Ω respectively. Find the emf generated and armature current if there is a drop of 1 V at each of its brushes.

Solution

Refer Fig. 14.102

Here, $V = 250 \text{ V} = V_{XY}$ (in Fig. 14.102); $I = 50 \text{ A}$

$$R_{se} = 0.04 \Omega; R_{sh} = 100 \Omega; R_a = 0.05 \Omega.$$

$$\therefore V_{ZY} = V_{XY} + I R_{se} = 250 + 50 \times 0.04 = 252 \text{ V}$$

$$I_{sh} = \frac{V_{ZY}}{R_{sh}} = 2.52 \text{ A}$$

$$\therefore I_a = I_{load} + I_{sh} = 50 + 2.52 = 52.52 \text{ A.}$$

Hence, generated emf $E = V_{ZY} + I_a R_a + \text{brush drop}$

$$= 252 + 52.52 \times 0.05 + 2 \times 1 = 256.626 \text{ V}$$

Hence emf generated = 256.626 V

and armature current = 52.52 A .

14.142 A 24 kW, 240 V dc self-excited shunt generator driven at 1000 rpm has an armature resistance of 0.1Ω while the field current is 2.5 A. The rotational losses are 750 W. Assuming constant speed and neglecting armature reaction, determine

- the armature induced emf
- the developed full load torque
- the full load efficiency.

Solution

$$(i) \text{ At full load, } I_L = \frac{\text{Power (KW)} \times 10^3}{V} = \frac{24 \times 10^3}{240} = 100 \text{ A.}$$

$$I_a = I_L + I_{sh} = 100 + 2.5 = 102.5 \text{ A}$$

$$E = V + I_a R_a = 240 + 102.5 \times 0.1 = 250.25 \text{ V.}$$

- (ii) Electrical power developed

$$P_g = E \times I_a = 250.25 \times 102.5 = 25650.625 \text{ W.}$$

$$\therefore \text{ Torque developed } T = \frac{E \cdot I_a}{2\pi N} = \frac{25650.625}{2\pi \times \frac{1000}{60}} = 244.84 \text{ Nm.}$$

$$(iii) \text{ Total losses} = P_{(rot)} + I_a^2 R_a + V \cdot I_{sh} \\ = 750 + (102.5)^2 \times 0.1 + 240 \times 2.5 = 2400.63 \text{ W.}$$

$$\therefore \text{ Efficiency } (\eta) = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{24 \times 10^3 \times 100}{24 \times 10^3 + 2400.63} = 90.90\%.$$

.....

14.143 A 400 V long shunt compound generator has a constant loss (rotational + shunt excitation losses) of 4 kW. The armature, series field and shunt field resistances are 0.08, 0.02 and 100Ω respectively. Calculate the maximum efficiency and the load at which it occurs.

Solution

For maximum efficiency, we know that Constant loss = Variable losses. Let the armature current for the maximum efficiency load be I_a .

$$\text{Here, } \underbrace{I_a^2 (0.08 + 0.02)}_{\text{variable loss}} = \underbrace{4000}_{\text{constant loss}}$$

$$\therefore I_a = \sqrt{\frac{4000}{0.1}} = 200 \text{ A}$$

$$\therefore \text{ Corresponding load current is } I_L = I_a - I_{sh} = 200 - \frac{400}{100} = 196 \text{ A}$$

$$\therefore \text{ Required load} = 196 \times 400 = 78.4 \text{ kW. Hence the output is 78.4 kW.}$$

$$\therefore \text{ Maximum efficiency} = \frac{\text{Output}}{\text{Output} + \text{Losses}} = \frac{78400 \times 100}{78400 + 2 \times 4000} = 90.74\%.$$

.....

14.144 An over-compounded dc generator is supplying a load at 220 V. If the machine terminal voltage is 220.2 V when the load current is 10 A, what will be the machine terminal voltage when the load is 600 A?

Solution

When the load current is 10 A, the voltage drop in the cables, between machine terminals and load = $(220.2 - 220) = 0.2 \text{ V}$.

$$\text{By proportion, the voltage drop for 600 A would be } \left(0.2 \times \frac{600}{10}\right) = 12 \text{ V.}$$

If the load voltage is still to be 220 V, the terminal voltage would need to be raised to $(220 + 12) = 232$ V.

∴ The machine terminal voltage is 232 V.

14.145 A dc shunt generator delivers 50 kW at 250 V when the speed is 400 rpm. The field resistance and armature resistance are 50 Ω and 0.02 Ω respectively. Determine the machine's speed when running as a shunt motor taking 50 kW input at 250 V. Consider 2 V for brush-contact drop.

Solution

As a shunt generator:

$$50 \text{ kW at } 250 \text{ V gives a load current of } (I_L) = \frac{50 \times 10^3}{250} = 200 \text{ A}$$

$$\text{Field current } I_{sh} = \frac{250}{50} = 5 \text{ A} \quad \left[\because I_{sh} = \frac{V}{R_f} \right]$$

$$\therefore \text{Armature current } (I_a) = I_L + I_{sh} = 200 + 5 = 205 \text{ A.}$$

$$\therefore E = V + I_a R_a + \text{brush voltage drop,}$$

$$\text{we get, } E = 250 + (205 \times 0.02) + 2.0 = 250 + 4.1 + 2.0 = 256.1 \text{ V.}$$

As a shunt motor:

$$\text{Input current} = \frac{250}{50} = 5 \text{ A.}$$

$$\therefore \text{Armature current } I_a = I_L - I_{sh} = 200 - 5 = 195 \text{ A}$$

$$\begin{aligned} \text{Back emf, } E_b &= V - I_a R_a - \text{brush voltage drop} \\ &= 250 - 3.9 - 2 = 244.1 \text{ V.} \end{aligned}$$

Again, E and E_b being proportional to flux and speed, we can write,

$$E = K \phi N \quad \text{and also } E_b = K \phi N$$

$$\text{Thus } \frac{E}{E_b} = \frac{5 \times 400}{5 \times N} \quad \text{or } N = 382 \text{ rpm.}$$

[ϕ can be substituted by field current as flux is assumed to be proportional to field ampere turns and hence the exciting current.]

14.146 The emf induced in the armature of a 450 kW, 250 V dc shunt generator is 260 V when the field current is 20 A. The armature circuit resistance is 0.004 Ω. Calculate:

- The load current I_L
- The power generated P_g
- The power output
- The electrical efficiency η .

Solution

- (i) Let the load current be I_L

$$\therefore \text{Armature current } I_a = I_L + 20 \quad [\because I_a = I_s + I_{sh}]$$

$$\therefore \text{Induced emf } E = \text{Terminal voltage } V + I_a R_a \text{ drop, we have}$$

$$260 = 250 + (I_L + 20) \times 0.004$$

$$\therefore I_L = \frac{260 - 250}{0.004} - 20 = 2480 \text{ A.}$$

(ii) Power generated $P_g = EI_a = 260 (2480 + 20) = 650 \text{ kW.}$

(iii) Power output $VI_L = (250 \times 2480) \text{ W} = 620 \text{ kW.}$

(iv) Electrical efficiency $(\eta) = \frac{\text{Output}}{\text{Input}} \times 100 = \frac{620.0}{650.0} \times 100 = 95.38\%$

14.147 A 4-pole dc motor whose armature is 0.36 m in diameter and has 720 conductors has effective length of 0.3 m. The flux density of the field under the poles is 0.7T. Each conductor carries 30 A. If the armature rotates at 680 rpm, calculate the torque in Nm and the power developed if only two-thirds of the conductors are effective.

Solution

Force developed by one conductor is given by $F = (BIL) = 0.7 \times 30 \times 0.3 = 6.3 \text{ N}$.

Number of conductors in the field at any instant = $2/3 \times 720 = 480$.

Total force = $480 \times 6.3 = 3024 \text{ N}$.

Torque = force \times radius = $3024 \times 0.18 = 544.32 \text{ Nm}$

i.e., Torque exerted = 544 N-m.

$$\begin{aligned} \text{Power developed} &= \frac{2\pi NT}{60} = \frac{2 \times 3.14 \times 680 \times 544}{60} \\ &= 3.14 \times 68 \times 181.333 \text{ W} = 38.7 \text{ kW}. \end{aligned}$$

14.148 A 220 V dc shunt motor draws a current of 3 A on light load at 1250 rpm and draws of current of 40 A on full load at the same speed. Calculate the speed on full-load, if the armature resistance is 0.29Ω and the field resistance is 165Ω . Due to the armature reaction, the flux per pole is 4% less than the no-load value.

Solution

At no load

Voltage across the shunt field = 220 V.

Current through the shunt field, $I_{sh} = \frac{220}{165} = 1.33 \text{ A}$.

Armature current $I_a = I - I_{sh} = 3.0 - 1.33 = 1.67 \text{ A}$.

Voltage drop across the armature ($= I_a R_a$) = $1.67 \times 0.29 = 0.484 \text{ V}$

Back emf $E_{b0} = 220 - 0.484 = 219.515 \text{ V}$. [$\because E_b = V - I_a R_a$]

At full load:

Current through shunt field remains same and hence $I_{sh} = 1.33 \text{ A}$.

Armature current $I_a = 40 - 1.33 = 38.67 \text{ A}$.

Voltage drop across armature = $I_a R_a = 38.67 \times 0.29 = 11.23 \text{ V}$.

Back emf is obtained as $E_{b1} = 220 - 11.23 = 208.77 \text{ V}$.

Since, $E_b \propto \phi N$, we can write $E_b = K \phi N$

Hence for no-load and full load condition, $\frac{E_{b0}}{E_{b1}} = \frac{\phi_0 N_0}{\phi_1 N_1}$.

But

$$\begin{aligned} \phi_1 &= 0.96 \phi_0 \\ \therefore \frac{E_{b0}}{E_{b1}} &= \frac{\phi_0 N_0}{0.96 \times \phi_0 \cdot N_1} \quad \text{or,} \quad N_1 = \frac{N_0 \times E_{b1}}{0.96 \times E_{b0}} \\ &= \frac{1250 \times 208.77}{0.96 \times 219.515} = 1238.3 = 1238 \text{ rpm} \end{aligned}$$

\therefore speed on full load is 1238 rpm.

14.149 A dc shunt motor is rated for 220 V and has an armature winding resistance of 0.4Ω . It draws armature current of 2 A at no-load and 50 A at full-load, the full-load speed being 500 rpm. Assuming the flux to be constant for no-load and full-load operations, find the no-load speed of the motor.

Solution

At no-load, $E_{b_0} = V - I_a R_a = 200 - (2 \times 0.4) = 199.2 \text{ V}$

At full-load, $E_{b_1} = 200 - (50 \times 0.4) = 180 \text{ V}$.

Since this is a shunt motor, the field current is constant and therefore the same constant flux can be assumed for the no-load and full-load conditions.

Since $E_{b_0} = K\phi_0 N_0$ and $E_{b_1} = K\phi_1 N_1$, while $\phi_0 = \phi_1$,

we can write,

$$\frac{E_{b_0}}{E_{b_1}} = \frac{K\phi_0 N_0}{K\phi_1 N_1} \quad \therefore N_0 = \frac{N_1 \times E_{b_0}}{E_{b_1}}$$

$$N_0 = 500 \times \frac{199.2}{180} = 553 \text{ rpm.}$$

.....

14.150. A 200 V, 4-pole lap wound dc motor has 600 conductors in the armature winding and has a resistance of 0.3Ω . The resistance of the shunt field circuit is 100Ω while the flux per pole is 0.02 Wb . At no load, the input current is 3 A , while the normal full-load current in the armature is 50 A . Determine the speed regulation of the motor from no-load to full-load. Ignore the armature reaction effect.

Solution

Back emf on no-load $E_{b_0} = 200 - I_{a_0} R_a$

Shunt field current $I_{sh} = 2 \text{ A}$

$$I_{a_0} = I_L - I_{sh} = 3 - 2 = 1 \text{ A}$$

$$\therefore E_{b_0} = 200 - (1 \times 0.3) = 199.7 \text{ V.}$$

No load speed of the motor is given by (N_0) where $E_{b_0} = \frac{Z \cdot \phi_0 N_0}{60} \cdot \frac{P}{A}$

$$\text{or} \quad 199.7 = \frac{600 \times 0.02 \times N_0}{60} \quad [\because \text{for lap-winding } A = P]$$

$$\text{or} \quad 199.7 = 0.2 \times N_0$$

$$\therefore N_0 = \frac{1997}{2} = 998.5 \text{ rpm.}$$

Again, Back emf E_{b_1} on full-load is given by:

$$E_{b_1} = 200 - I_{a_1} R_a = 200 - (50 - 2) \times 0.3 = 185.6 \text{ V.}$$

Since, $E_{b_1} = K\phi_1 N_1$ assuming a constant flux and with $\phi_0 = \phi_1$,

we have

$$\frac{E_{b_1}}{E_{b_0}} = \frac{K\phi_1 N_1}{K\phi_0 N_0}, \quad \text{where } N_1 = \frac{N_0 \cdot E_{b_1}}{E_{b_0}}$$

$$\therefore N_1 = \frac{998.5 \times 185.6}{199.7} = 928 \text{ rpm}$$

\therefore Full load speed = 928 rpm.

$$\begin{aligned} \text{Thus speed regulation} &= \frac{\text{No-load speed} - \text{Full load speed}}{\text{Full-load speed}} \times 100 \\ &= \frac{998.5 - 928}{928} \times 100 = 7.6\% \end{aligned}$$

.....

14.151 A 105 V, 3 kW dc shunt motor has a full-load efficiency of 82%. The field and armature resistances are $90\ \Omega$ and $0.25\ \Omega$ respectively. The full-load speed of the motor is 1000 rpm. Determine the speed at which the motor will run at no-load if the line current at no load is 3.5 A. Also determine the resistance to be added to the armature circuit, in order to reduce the speed to 800 rpm, the torque remaining constant at full-load value. Ignore the armature reaction and brush drop.

Solution

On no-load,

$$I_{sh} \left(= \frac{V}{R_f} \right) = \frac{105}{90} = 1.17\text{ A}$$

No-load current $I_{L_0} = 3.5\text{ A}$ (given)

$$\therefore I_{a0} = 3.5 - 1.17 = 2.33\text{ A} \quad [\because I_a = I_L - I_{sh}]$$

$$\text{and } E_{b0} = V - I_{a0}R_a = 105 - (2.33 \times 0.25) = 105 - 0.58 = 104.42\text{ V.}$$

On full-load, output = $3 \times 1000\text{ W}$.

$$\therefore \text{Input} = \frac{\text{Output}}{\text{Efficiency}} = \frac{3 \times 1000 \times 100}{82} = 3660\text{ W}$$

$$\text{Input line current } I_{L_1} = \frac{3660}{105} = 34.86\text{ A.}$$

$$\therefore I_{a1} = 34.86 - 1.17 = 33.7\text{ A and } E_{b1} = 105 - (33.7 \times 0.25) = 96.57\text{ V.}$$

$$\therefore E \propto \phi N \text{ or } E = K \phi N, \text{ we can write } \frac{E_{b0}}{E_{b1}} = \frac{K \phi_0 N_0}{K \phi_1 N_1}$$

$$\therefore N_0 = \frac{E_{b0} \times \phi_1 \times N_1}{E_{b1} \times \phi_0} = 1080\text{ rpm.}$$

Again, since T is constant and $T \propto \phi I_a$, we can write

$$T_2 = K \phi_2 I_{a2} \text{ and } T_1 = K \phi_1 I_{a1}$$

$$\therefore \frac{T_2}{T_1} = \frac{K \cdot \phi_2 \cdot I_{a2}}{K \cdot \phi_1 \cdot I_{a1}} \text{ but}$$

$$\text{But } T_2 = T_1 \text{ and } \phi_2 = \phi_1.$$

$$\therefore I_{a2} = I_{a1} = 33.7\text{ A.}$$

If R is the added resistance to reduce speed then we can write

$$E_{b2} = V - I_{a2} \times (R + R_a) = 105 - 33.7 (R + 0.25)$$

Also $E_b \propto \phi N$; since flux is constant, we can write

$$\frac{E_{b2}}{E_{b1}} = \frac{800}{1000} \text{ or, } E_{b2} = 96.57 \times \frac{800}{1000}$$

$$\therefore \text{Back emf (at reduced speed)} = 77.26\text{ V,}$$

$$\text{thus we have } 77.26 = 105 - 33.7 (R + 0.25)$$

$$\therefore R = \frac{19.31}{33.7} = 0.57\ \Omega.$$

.....

14.152 A 4-pole dc shunt motor has a wave wound armature with 294 conductors. The flux per pole is 0.03 Wb and the resistance of the armature is $0.35\ \Omega$. Determine (i) the speed of the armature and (ii) the torque developed, when the armature current is 200 A and the supply is 230 V dc.

Solution

$$(i) V = E_b + I_a R_a;$$

$$\text{or } E_b = V - I_a R_a = 230 - (200 \times 0.35) = 160 \text{ V}$$

$$\text{Since } E_b = \frac{Z \phi N}{60} \times \frac{P}{A}$$

$$\text{Here, } N = \frac{E_b}{Z \phi} \times \frac{60 \cdot A}{P} = \frac{160 \times 60 \times 2}{294 \times 0.03 \times 4} = 544 \text{ rpm.}$$

(ii) Again torque is given by:

$$\begin{aligned} T &= 0.159 \times Z \phi I_a \left(\frac{P}{A} \right) \text{ Nm} \\ &= 0.159 \times 294 \times 0.03 \times 200 \times 4/2 = 560.95 \text{ Nm.} \end{aligned}$$

.....

14.153. A 230 V dc shunt motor runs at 600 rpm when taking a line current of 50 A. The field and armature resistances of the motor are 104.5 Ω and 0.4 Ω respectively. Determine (i) the no-load speed if the no-load line current is 5 A. (ii) The resistance to be placed in the armature circuit in order to reduce the speed to 500 rpm when taking a line current of 50 A. (iii) The percentage reduction in the flux per pole in order that the speed may be 750 rpm, when taking an armature current of 30 A with no added resistance in the armature circuit. Ignore the effect of armature reaction but allowing a brush drop of 2 V.

Solution

$$I_{sh_0} = \frac{230}{104.5} = 2.2 \text{ A}; I_{a_0} = 5 - 2.2 = 2.8 \text{ A}$$

$$\text{Also, } I_{sh_1} = 2.2 \text{ A}; I_{a_1} = 50 - 2.2 = 47.8 \text{ A}$$

$$\text{Again, } E_{b_1} = 230 - (47.8 \times 0.4) - 2 = 208.88 \text{ V}$$

$$\text{and } E_{b_0} = 230 - (2.8 \times 0.4) - 2 = 226.88 \text{ V.}$$

$$(i) \text{ Since } \frac{E_{b_1}}{E_{b_0}} = \frac{K \phi_1 N_1}{K \phi_0 N_0}, \text{ here } N_0 = \frac{E_{b_0} \cdot N_1}{E_{b_1}} = \frac{226.88 \times 600}{208.88} = 651 \text{ rpm.}$$

$$(ii) \text{ At 600 rpm, } E_{b_1} = 208.88 \text{ V.}$$

Assuming a constant flux, then for 500 rpm.

$$E_{b_2} = 208.88 \times \frac{5}{6} = 174.07 \text{ V.}$$

\therefore The voltage across the armature has to be reduced by $(230 - 174.07) = 55.93 \text{ V}$

$$\text{Since } V = E_b + I_a(R_a + R) + 2$$

$$V - E_b = I_a(R_a + R) + 2$$

$$\text{or } 55.93 = I_a R_a + I_a R + 2$$

$$\therefore I_a \cdot R = 55.93 - 2 - (47.8 \times 0.4) = 34.81 \text{ V.}$$

$$\therefore R = \frac{34.81}{47.8} = 0.73 \Omega.$$

(iii) Let the reduced flux be ϕ_3 .

$$\therefore \frac{E_{b_3}}{E_{b_1}} = \frac{K \phi_3 N_3}{K \phi_1 N_1}$$

$$\text{or } E_{b_3} = 230 - (30 \times 0.4) - 2 = 216 \text{ V.}$$

$$\therefore \frac{216.0}{208.88} = \frac{I_{sh_3} \times 750}{2.2 \times 600} \text{ or } I_{sh_3} = 1.82 \text{ A}$$

Thus current (and therefore flux) is to be reduced to $\frac{1.82}{2.2} = 82.7\%$.

.....

14.154. A 250 V dc shunt motor drives a load whose torque varies as the cube of the speed. This motor takes 20 A when running at 1200 rpm. If the field current is kept constant and the speed is varied by external resistance in the armature circuit, determine the resistance needed to bring the speed down to 900 rpm. Ignore the armature resistance.

Solution

From the given conditions, we can write $T \propto \phi I_a \propto N^3$. Here ϕ is constant.

$$\therefore \frac{I_{a1}}{I_{a2}} = \left(\frac{N_1}{N_2} \right)^3$$

$$\therefore I_{a2} = \left(\frac{N_2}{N_1} \right)^3 \times I_{a1} = \left(\frac{900}{1200} \right)^3 \times 20 = 8.4375.$$

$$\therefore \frac{E_{b2}}{E_{b1}} = \frac{\phi_2 N_2}{\phi_1 N_1} = \frac{N_2}{N_1}$$

$$\text{Here, } \left(\frac{E_{b2}}{E_{b1}} \right) = \left(\frac{900}{1200} \right) = 0.75.$$

$$\text{or, } E_{b2} = 0.75 \times E_{b1} = 0.75 \times 250 = 187.5 \text{ V.}$$

$$\text{But } E_b = V - I_a R_a$$

$$\text{Here, } 187.5 = V - I_{a2} (R_a + R_e) = 250 - 8.4375 (R_a + R_e)$$

$$\text{Since } R_a = 0 \text{ (given)}$$

$$\therefore R_e = 7.40 \Omega.$$

14.155. A shunt connected dc motor draws a total current of 56 A from a 650 V supply when delivering its rated output at its rated speed of 1000 rpm. The resistance of the field circuit and armature are 300 Ω and 0.50 Ω respectively and the mechanical losses are 1.90 kW. Determine the useful power output, torque and efficiency.

Solution

$$\text{Field current } (I_{sh}) = \frac{V}{R_{sh}} = \frac{650}{300} = 2.16 \text{ A.}$$

$$\text{Hence armature current } (I_a) = I_L - I_{sh} = 56 - 2.16 = 53.83.$$

Let the suffix 1 denote the initial condition of rated output and rated speed,

$$\text{then } E_1 = V - I_{a1} R_a = 650 - 53.83 \times 0.50 = 623.08 \text{ V}$$

$$\text{Gross power output } E_1 I_{a1} = 623.08 \times 53.83 = 33.54 \text{ kW}$$

$$\text{Thus net power output} = \text{Gross power} - \text{Mechanical loss} = 33.54 - 1.90 = 31.64 \text{ kW}$$

(i.e. the useful power output is 31.64 kW)

$$\text{Since speed} = 1000 \text{ rpm} = 2\pi \times \frac{1000}{60} = 104.7 \text{ rad/sec.}$$

$$\text{Hence torque } T = \frac{31.64 \times 10^3}{104.7} = 302.3 \text{ N-m.}$$

i.e. useful torque is 302 N-m.

$$\text{Again, input power} = (V \times I_{L1}) = 650 \times 56 = 36.4 \text{ kW, while output power} = 31.64 \text{ kW.}$$

$$\therefore \text{Efficiency } \eta = \frac{31.64}{36.4} \times 100$$

\therefore the percentage efficiency is 86.92%.

14.156 A dc shunt motor of 500 V has a full load armature current of 20 A. 3% of the input power to the motor is dissipated as heat energy. What would be the armature current on starting if 500 V is supplied across the armature?

Calculate also the value of starting resistance required to limit the starting current to twice the full load current.

Solution

Since the field current is small, we can ignore the field current.

∴ Input power ($= VI$) = $500 \times 20 = 10,000$ W.

Again, 3% of the input power (i.e. $(3/100) \times 10,000.00$) is 300 W which is dissipated as heat in the armature. This is copper (or I^2R loss).

∴ $I^2 R_a = 300$ or, $20^2 \cdot R_a = 300$

∴ $R_a = \frac{300}{400} = \frac{3}{4} = 0.75 \Omega$.

The starting current with only armature resistance to limit the armature current is given

by, $(I_{as}) = \frac{500}{0.75} = 666.6$ A.

∴ The twice full load current will be $20 \times 2 = 40$ A.

Total resistance required in the armature circuit to limit starting current to 40 A is

$\left(\frac{500}{40}\right)$ or 12.5Ω . Since $R_a = 0.75 \Omega$, the series resistance would be $12.5 - 0.75 = 11.75 \Omega$. *****

14.157 A belt driven 250 kW dc shunt generator running at 500 rpm which supplies full load power to a 500 V bus bar. When the belt breaks down, it continues to run as motor taking 20 kW from the bus bar. What would be new speed and torque developed? Given:

$$R_a = 0.02 \Omega$$

$$R_{sh} = 100 \Omega$$

Assume a constant voltage drop in each brush as 1.5 V. Ignore the armature reaction effect.

Solution

I_{L_1} (as shunt generator) = $\frac{250 \times 10^3}{500} = 500$ A and $I_{sh} = \frac{500}{100} = 5$ A.

∴ $I_{a_1} = 500 + 5 = 505$ A [∵ $I_{a_1} = I_{L_1} + I_{sh}$]

$$E_1 = 500 + (505 \times 0.02) + (2 \times 1.5) = 513.10 \text{ V.}$$

$$[\because E = V + I_{a_1} R_a + \text{brush drop for generator}]$$

∴ I_{L_2} (as motor) = $\frac{20,000}{500} = 40$ A.

Also $I_{a_2} (= I_{L_2} - I_{sh}) = 40 - 5 = 35$ A.

∴ $\frac{E_1}{E_2} = \frac{N_1}{N_2}$ or $\frac{513.10}{496.3} = \frac{500}{N_2}$

∴ $N_2 = 483.63$ rpm

∴ $T = \frac{E_b \cdot I_A}{2\pi N}$

∴ $T = \frac{E_2 \cdot I_{a_2}}{2\pi \cdot N_2} = \frac{496.3 \times 35 \times 60}{2\pi \times 483.63} = 342.84 \text{ Nm.}$

14.158 A 440 V dc shunt motor runs at a speed of 1000 rpm when on no-load. After a few hours of loading its temperature rises by 28°C and the supply voltage falls to 436 V.

Calculate the new speed of the motor when the armature current is 85 A. The cold armature resistance is 0.04 Ω. Temperature co-efficient of the armature and field conductor is 0.4% per degree centigrade.

Solution

Let $R_{sh(c)}$ be the cold resistance of the field winding and $R_{sh(H)}$ and $R_{A(H)}$ be the hot field winding and armature winding resistances respectively.

$$\therefore R_{sh(H)} = R_{sh(c)} (1 + 28 \times 0.0044) = 1.1232 R_{sh(c)}$$

$$\text{and } R_{A(H)} = 0.04 (1 + 28 \times 0.0044) = 0.0449 \Omega.$$

Assuming armature current on no load to be zero, we can write

$$E_1 = V_1 = 440 \text{ V (at no load-condition)}$$

$$E_2 = V_2 - I_A R_{A(H)} = 436 - 85 \times 0.0449 = 432.1835 \text{ V.}$$

$$\therefore \frac{E_1}{E_2} = \frac{\phi_1 N_1}{\phi_2 N_2} = \frac{I_{sh1}}{I_{sh2}} \times \frac{N_1}{N_2} = \frac{V_1 / R_{sh(c)}}{V_2 / R_{sh(H)}} \times \frac{N_1}{N_2}$$

$$\therefore \frac{440}{432.1835} = \frac{440 / R_{sh(c)}}{436 / 1.1232 R_{sh(c)}} \times \frac{1000}{N_2}$$

$$\therefore N_2 = 1113 \text{ rpm.}$$

.....

14.159 A 240 V dc series motor develops a shaft torque of 200 N-m at 92% efficiency while running at 600 rpm. Calculate the motor current.

Solution

$$\text{Power output} = 2\pi NT = 2\pi \times \frac{600}{60} \times 200 = 12566 \text{ W.}$$

$$\text{Power input } W = \frac{12566}{0.92} = 13659 \text{ W}$$

$$\therefore \text{The motor current } (I) = \frac{13659}{240} = 56.91 \text{ A.}$$

.....

14.160 A 220 V dc series motor takes 60 A. The armature resistance is 0.1 Ω and the series field resistance is 0.08 Ω. If the iron and friction losses are equal to the copper losses at this load, calculate the BHP (brake horsepower) and electrical efficiency.

Solution

$$\text{Motor resistance} = 0.1 + 0.08 = 0.18 \Omega.$$

$$E_b = V - I_a R_m = 220 - (60 \times 0.18) = 209.2 \text{ V.}$$

$$\text{Input power} = 220 \times 60 = 13200 \text{ W.}$$

$$\text{Copper losses} = 648 \text{ W } [(60)^2 \times 0.18 = 648 \text{ W}]$$

$$\text{Output} = 11904 \text{ W } [13200 - 2 \times 648 = 11904 \text{ W}]$$

$$\therefore \text{BHP} = \frac{11904}{735.5} = 16.18.$$

$$\text{Efficiency } (\eta) = \frac{11904}{13200} \times 100 = 90.18\%.$$

.....

14.161 A dc series motor develops 40000 W and takes a current of 80 A when running at 1200 rpm. Calculate starting torque if the starting current is 150% of the rated current. Magnetic circuit remains unsaturated.

Solution

Output of dc series motor = 40000 W (given).

$$\therefore 2\pi NT = 2\pi \times \frac{1200}{60} \times T = 40000$$

$$T = \frac{40000 \times 60}{2\pi \times 1200} = \frac{1000}{\pi} \text{ Nm.}$$

For a series motor (with unsaturated field), $T \propto I_a^2$

$$\therefore \frac{1000}{\pi} = K \cdot (80)^2$$

At starting $I_a = 120$ A (starting current = 150% rated current)

$$\therefore \frac{T_s}{1000/\pi} = \left(\frac{120}{80}\right)^2 \quad [T_s \text{ being the starting torque.}]$$

$$\therefore T_s = \left(\frac{120}{80}\right)^2 \times \frac{1000}{\pi} = 715.90 \text{ Nm.}$$

14.162 A 220 V dc series motor is working with an unsaturated field taking a current of 100 A at 800 rpm. Calculate the speed of the motor when it develops half the torque. [Given: the total resistance of the motor is 0.1 ohm]

Solution

For dc series motor,

$$\text{Torque } T = KI_a^2$$

$$\therefore \frac{T_1}{T_2} = \frac{T_{a_1}^2}{T_{a_2}^2}$$

But $T_2 = 0.5T_1$ (as per the given condition)

$$\therefore \frac{T_1}{0.5T_1} = \frac{100^2}{I_{a_2}^2} \quad \text{or} \quad I_{a_2}^2 = 100^2 \times 0.5 = 5000.$$

$$\therefore I_{a_2} = 10\sqrt{50} = 10 \times 7.07 = 70.7 \text{ A.}$$

Under the first condition,

$$E_{b_1} = V - I_{a_1}(R_a + R_{se}) = 220 - (100 \times 0.1) = 210 \text{ V.}$$

Under the second condition

$$E_{b_2} = V - I_{a_2}(R_a + R_{se}) = 220 - 70.7 \times 0.1 = 212.93 \text{ V.}$$

However, $E_b = K \phi N$.

$$\therefore \frac{E_{b_1}}{E_{b_2}} = \frac{\phi_1 N_1}{\phi_2 N_2} \quad \text{and also } \phi \propto I_a$$

$$\text{i.e.} \quad \frac{E_{b_1}}{E_{b_2}} = \frac{I_{a_1} \cdot N_1}{I_{a_2} \cdot N_2}$$

$$\therefore N_2 = \frac{I_{a_1} N_1 E_{b_2}}{I_{a_2} E_{b_1}} = \frac{100 \times 800 \times 212.93}{70.7 \times 210} = 1147 \text{ rpm}$$

\therefore Speed at half torque = 1147 rpm.

Solution

Here full-load resistance drop = $1.5\% = \frac{IR}{V} \times 100$.

and $W_C = I^2 R = I^2 \times 0.015 \times \frac{V}{I} = 0.015 VI = 1.5\% \text{ of } VI$.

Also, full load copper loss = 1.5%

\therefore Copper loss at half load = $\left(\frac{1}{2}\right)^2 \times 1.5 = 0.375\%$

Since maximum efficiency also occurs at full load, therefore, iron loss are also = 1.5% .

Hence efficiency η at half load = $\frac{50}{50 + 1.5 + 0.375} \times 100 = 96.39\%$.

.....

14.170 A single-phase transformer of 500 kVA capacity has an iron loss of 4.5 kW and a full-load copper loss of 7.8 kW.

Calculate (i) The efficiency of the transformer at half-load for a power factor of unity.
(ii) Also calculate the load for maximum efficiency and the value of maximum efficiency when the power factor is (a) unity (b) 0.7 (lagging).

Solution

Since copper loss $\propto (\text{current})^2$

\therefore Copper loss $\propto (\text{kVA})^2$

(i) Half-load copper loss at unity power factor = $7.8 \times 0.5^2 = 1.95 \text{ kW}$

Iron loss = 4.5 kW (given).

\therefore The total losses = $1.95 + 4.5 = 6.45 \text{ kW}$

Transformer output (at unity p.f.) = $0.5 \times 500 = 250 \text{ kW}$.

\therefore Efficiency $\eta = \frac{\text{Output power}}{\text{Input power}} = \frac{250}{250 + 6.45} \times 100 = 97.5\%$

We know the condition of maximum efficiency occurs when copper loss equals the iron loss. Let the maximum efficiency occurs at $1/x$ of the full-load kVA, thus

$$\text{Iron loss} = \frac{\text{Full-load copper loss}}{x^2}$$

$$\text{Thus } x = \sqrt{\frac{\text{Full-load copper loss}}{\text{Iron loss}}} = \sqrt{\frac{7.8}{4.5}} = 1.317.$$

\therefore kVA for maximum efficiency = $500 \times \frac{1}{1.317} = 380 \text{ kVA}$.

and total losses at maximum efficiency = $2 \times \text{Iron loss} = 9.0 \text{ kW}$.

(ii) (a) When p.f. is unity

Output power = $\text{kVA} \times 1 = 380 \text{ kW}$

Total losses = 9 kW

\therefore Efficiency = $\frac{380}{380 + 9} \times 100 = 97.7\%$.

(b) When p.f. is 0.7 lagging

Output power = $380 \times 0.7 = 266 \text{ kW}$

Total losses = 9 kW .

\therefore efficiency = $\frac{266}{(266 + 9)} \times 100 = 96.7\%$.

.....

Secondary current $I_2 = \frac{22}{220} = 0.1 \text{ A}$.

Primary current I_1 is to be found out.

Now for an 'ideal' transformer, Output power = Input power.

$$\therefore V_2 \cdot I_2 = V_1 \times I_1$$

$$\therefore I_1 = \frac{V_2 \cdot I_2}{V_1} = \frac{22 \times 0.1}{220} = 0.01 \text{ A}.$$

14.173. A transformer with 100% efficiency has 200 turns in the primary and 40000 turns in the secondary. It is connected to a 220 V, 50 Hz main supply and the secondary feeds to a 100 k Ω resistance. Calculate the secondary potential difference per turn and the power delivered to the load.

Solution

Primary turns $N_1 = 220$

Secondary turns $N_2 = 40000$

Primary voltage $V_1 = 220 \text{ V}$

Load resistance = 100 k Ω = $10^5 \Omega$.

$$\therefore \frac{V_2}{V_1} = \frac{N_2}{N_1},$$

$$\therefore V_2 = V_1 \cdot \frac{N_2}{N_1} = 220 \times \frac{40000}{200} = 44000 \text{ V}.$$

$$\therefore \text{The secondary potential difference per turn is: } \frac{V_2}{N_2} = \frac{44000}{40000} = 1.1 \text{ V}.$$

The power delivered by the 'ideal' (100% efficiency) transformer to the load is

$$V_2 \times I_2 = V_2 \times \frac{V_2}{\text{load resistance}} = \frac{V_2^2}{\text{load resistance}} = \frac{(44000)^2}{10^5} = 19.36 \text{ kW}$$

14.174. A residential area requires 800 kW of electric power at 220 V and is 3 km away from the generating source. The source is generating power at 440 V, the resistance of the line carrying power is 0.5 ohm/km. The area gets power from the line through a (4000/220) V step-down transformer at a sub-station in the load area.

Determine:

- the line ohmic power loss
- how much power must the plant supply
- find the ratio of the step-up transformer at the plant.

Solution

The resistance of the two-wire line is:

$$R = 0.5 \times 3 = 1.5 \Omega.$$

The 800 kW power is transmitted at 4000 V through the line. Thus, the rms current in the line is:

$$I_{\text{rms}} = \frac{P}{V_1} = \frac{800 \times 10^3}{4000} = 200 \text{ A}.$$

- The line power loss is

$$(I_{\text{rms}})^2 \cdot R = (200)^2 \times 1.5 = 60 \text{ kW}$$

- The power to be supplied by the plant is power required + power loss = (800) kW + (60) kW = 860 kW.

(iii) The voltage drop across the line is

$$I_{rms} \times R = 200 \times 1.5 = 300 \text{ V}$$

The plant generates power at 440 V. It has to be stepped up so that after suffering a line drop of 300 V it reaches the substation in the town at 4000 V.

Hence the step-up transformer at the plant should be (440/4300) V voltage ratio.

14.175 A single-phase step down transformer of (1200/400) V, 50 Hz, have the following parameters:

$$R_1 = 0.2 \, \Omega, X_1 = 0.5 \, \Omega.$$

$$R_2 = 0.02 \, \Omega, X_2 = 0.06 \, \Omega.$$

$$R_0 = 12000 \, \Omega, \text{ and } X_0 = 2000 \, \Omega.$$

Calculate:

(i) The primary current and power factor of a transformer when a load impedance of $(8 + j6) \, \Omega$ is connected across its secondary terminals and its primary is connected to a 1200 V supply mains.

(ii) The short-circuit current and short circuit power factor of the transformer.

Solution

$$I_0 = I_w + I_m = \frac{V_1}{R_0} + \frac{V_1}{jX_0} = \frac{1200}{12000} + \frac{1}{j} \times \frac{1200}{2000} = (0.1 - j0.6) \text{ A}.$$

$$\begin{aligned} \therefore R_{01} &= R_1 + K^2 \cdot R_2 + K^2 R_L \\ &= 0.2 + 0.02 \times \left(\frac{1200}{400}\right)^2 + \left(\frac{1200}{400}\right)^2 \times 8 = 72.38 \, \Omega. \end{aligned}$$

Similarly,

$$\begin{aligned} X_{01} &= X_1 + K^2 X_2 + K^2 X_L \\ &= 0.5 + 3^2 \times 0.06 + 3^2 \times 6 = 55.04 \, \Omega. \end{aligned} \quad \left[\because K = \frac{1200}{400} = 3 \right]$$

$$\therefore I_{01} = \frac{V_1}{R_{01} + jX_{01}} = \frac{1200}{72.38 + j55.04} = (10.5 - j7.99) \text{ A}$$

$$\therefore \text{Primary current } I_1 = I_0 + I_{01} = (0.1 - j0.6) + (10.5 - j7.99) = (10.6 - j8.59) \text{ A}$$

The magnitude of the primary current is $I_1 = 13.6 \text{ A}$ while the power factor is $\left(\frac{10.6}{13.6}\right)$

or 0.78 (lag)

Again, $R'_L = X'_L = 0$ (given)

$$\begin{aligned} \text{and } Z'_{eq} \text{ (Z referred to primary)} &= (R_1 + K^2 \cdot R_2) + j(X_1 + K^2 X_2) \\ &= R_{eq'} + jX_{eq'} = (0.38 + j1.04) \, \Omega. \end{aligned}$$

$$\therefore I_{01} \text{ (on short circuit)} = \frac{1200}{0.38 + j1.04} = \frac{1200}{1.107} = 1085.8 \text{ A}.$$

This is the primary short circuit current as I_0 is extremely negligible in comparison to this. Power factor (on short circuit) is $\left(\frac{R_{eq'}}{Z'_{eq}}\right)$ i.e., $\frac{0.38}{1.107}$, or, 0.343.

14.176 A 2300/575/230 V three-winding (P/S/T) transformer has a total of 300 turns on its high voltage primary side. Each of the two secondary windings (say A and B) is rated for 200 kVA. Calculate the primary current, (i) when the 230 V secondary winding carries its rated current at unity power factor. (ii) when the 575 V winding carries its rated current at 0.5 lagging. Ignore the magnetizing current, internal drops and losses.

Solution

Let 2300/575/230 V be the voltages of windings P , S , T respectively.

$$\therefore \text{The rated current for } S \text{ is } I_{2A} = \frac{200000}{575} = 347.8 \text{ A}$$

$$\therefore \text{The rated current for } T \text{ is } I_{2B} = \frac{200000}{230} = 869.6 \text{ A}$$

Since I_{2A} is at p.f. 0.5 (lagging),

$$\therefore I_{2A} = (173.9 - j301.2) \text{ A.}$$

I_{2B} is at unity p.f.

$$I_{2B} = (869.6 - j0) \text{ A.}$$

$$\therefore I'_{2A} = (173.9 - j301.2) \times \frac{2300}{575} = (695.6 - j1204.8) \text{ A [referred to } P \text{ side]}$$

$$\text{and } I'_{2B} = (869.6 - j0.0) \times \frac{2300}{230} = 8696 \text{ A [(referred to } P \text{ side)]}$$

$$\therefore I'_2 = I'_{2A} + I'_{2B} = 695.6 - j1204.8 + 8696 = 9391.6 - j1204.8$$

$$\therefore |I'_2| = 9468.46 \text{ A [total primary load current]}$$

14.177 A transformer has maximum efficiency η at 95% at a load of 100 kW. Determine the constant loss of the transformer.

Solution

We know at maximum efficiency.

$$\text{Constant loss } W_i = \text{copper loss } W_c$$

$$\therefore (\text{efficiency})_{\max} = \frac{\text{output power}}{\text{output power} + 2W_i}$$

$$\text{or } 0.95 = \frac{100 \times 10^3}{100 \times 10^3 + 2 \cdot W_i}$$

$$\text{or } 2 \cdot W_i \times 0.95 = 100 \times 10^3 - 0.95 \times 100 \times 10^3$$

$$W_i = \frac{100 \times 10^3 (1 - 0.95)}{2 \times 0.95} = 2631.58 \text{ W} = 2.63 \text{ kW.}$$

14.178 A single-phase transformer on open circuit gave the following test results:

216 V	45 Hz	58.2 W
264 V	55 Hz	73.2 W

Calculate the eddy current and hysteresis losses separately at 240 V, 50 Hz.

Solution

$$\text{For the first test, } \frac{V}{f} = \frac{216}{45} = 4.8$$

$$\text{For the second test, } \frac{V}{f} = \frac{264}{55} = 4.8$$

$$\text{At 240 V, } \frac{V}{f} = \frac{240}{50} = 4.8$$

$$\text{Since } V = E = 4.44 f N \phi_m$$

$$\text{then } \frac{V}{f} = K \phi_m \text{ where } K \text{ is a constant } (K = 4.44 \text{ N}).$$

As V is constant, the flux and flux density are constant.

We know, hysteresis loss (P_h) $\propto f$ or, $P_h = af$

$$\text{Slip at maximum torque } s_m = \frac{R_2}{X_2} = \frac{0.3}{1.5} = 0.2.$$

$$\therefore \text{ Speed } N_r \text{ at maximum torque} = N_s(1 - s_m) = \frac{120 \times 50}{6} (1 - 0.2) = 800 \text{ rpm.}$$

14.183 An 8-pole, 50 Hz squirrel cage induction motor has a rotor resistance and standstill reactance of 0.05Ω and 0.5Ω per phase respectively. Determine the speed at maximum torque condition and the external rotor resistance per phase to give two thirds of maximum torque at starting.

Solution

$$\text{Slip at maximum torque } s_m = \frac{R_2}{X_2} = \frac{0.05}{0.5} = 0.1$$

$$\therefore \text{ Speed } (N_r) \text{ at maximum torque} = (1 - 0.1) \times \frac{120 \times 50}{8} = 675 \text{ rpm.}$$

$$\text{Maximum torque } T_m = \frac{3}{2} \frac{E_2^2}{\omega_s X_2} \quad [\omega_s \text{ is synchronous speed.}]$$

$$\text{The required torque } T = \frac{2}{3} T_m = \frac{E_2^2}{2\omega_s X_2}; \text{ at starting i.e. at } s = 1,$$

$$\therefore T = \frac{3s E_2^2 R_2'}{\omega_s (R_2'^2 + s^2 X_2^2)},$$

where R_2' is the new rotor resistance

$$= \frac{3 E_2^2 R_2'}{\omega_s (R_2'^2 + X_2^2)}$$

$$\text{Now, } \frac{3 E_2^2 R_2'}{\omega_s (R_2'^2 + X_2^2)} = \frac{E_2^2}{2\omega_s X_2}$$

$$\therefore 6R_2' X_2 = R_2'^2 + X_2^2$$

$$\text{or } R_2'^2 - 6 \times 0.5 R_2' + (0.5)^2 = 0$$

$$\text{or } R_2'^2 - 3R_2' + 0.25 = 0$$

$$\text{or } R_2' = \frac{3 \pm \sqrt{9-1}}{2} = 1.5 \pm 1.414 = 0.086 \Omega \text{ or } 2.914 \Omega$$

\therefore External rotor resistance per phase is $(0.086 - 0.05) \Omega = 0.036 \Omega$ or $(2.914 - 0.05) \Omega = 2.864 \Omega$.

14.184 A 11 kV star connected squirrel cage induction motor has full load slip of 4% and standstill impedance of 8Ω . The full load current is 30 A and the maximum starting current which can be drawn from the line is 75 A. Find the tapping on the auto transformer used for starting the motor. Also give the value of the starting torque in terms of the full load torque.

Solution

$$\text{Without auto transformer the current at standstill condition is } \frac{11000/\sqrt{3}}{8} = 793.85 \text{ A.}$$

Let the tapping on the auto transformer be x .

Hence, $793.85 x^2 = 75$

$\therefore x = 0.307$

Therefore the tapping on the autotransformer is 30.7%

If T_{st} is the starting torque and T_{fl} is the full load torque then,

$$\frac{T_{st}}{T_{fl}} = \left(\frac{75}{30}\right)^2 \times 0.04 = 0.25.$$

14.185 The input power to the rotor of a three-phase, 50 Hz, 4-pole induction motor is 50 kW. The rotor emf makes 120 alternations per minute. Determine (i) slip (ii) speed (iii) mechanical power developed (iv) rotor copper loss per phase (v) rotor resistance per phase if rotor current is 50 A and (vi) torque developed.

Solution

(i) If (s) be the slip then

$$sf = \frac{120}{60}$$

or $s = \frac{120}{60 \times 50} = 0.04.$

(ii) Speed $= (1 - s) N_s = (1 - 0.04) \times \frac{120 \times 50}{4} = 1440 \text{ rpm.}$

(iii) Now, $P_{ag} = 50 \text{ kW.}$

\therefore Mechanical power developed (P_m) $= (1 - s) P_{ag} = (1 - 0.04) \times 50 = 48 \text{ kW.}$

(iv) Rotor copper loss (P_{cur}) $= s P_{ag} = 0.04 \times 50 = 2 \text{ kW}$

Hence rotor copper loss per phase $= \frac{2}{3} \text{ kW} = 0.667 \text{ kW} = 667 \text{ W}$

(v) Rotor copper loss per phase $(= I_2^2 R_2) = (50)^2 \times R_2 = 667$

\therefore Rotor resistance $R_2 = \frac{667}{(50)^2} = 0.2668 \Omega.$

(vi) Torque developed $T = \frac{P_{ag}}{\omega_s} = \frac{50,000}{2\pi \frac{120 \times 50}{4 \times 60}} = 318.47 \text{ N-m.}$ $\left[\because \omega_s = \frac{2\pi N_s}{60} \right]$

14.186 The power input to a three-phase, 6-pole, 440 V, 50 Hz induction motor is 50 kW at 970 rpm. The mechanical loss and the total stator losses are 1.5 kW and 2 kW respectively. Determine the rotor copper loss, gross torque and the rotor resistance per phase if the rotor phase current is 110 A.

Solution

Air-gap power $P_{ag} = 50 - 2 = 48 \text{ kW}$

$$\text{Slip } (s) \left(1 - \frac{N_r}{N_s} \right) = 1 - \frac{970}{\frac{120 \times 50}{6}} = 1 - 0.97 = 0.03.$$

\therefore Rotor copper loss $P_{cur} = s P_{ag} = 0.03 \times 48 = 1.44 \text{ kW}$

Mechanical power developed $P_m = (1 - s) P_{ag} = 0.97 \times 48 = 46.56 \text{ kW.}$

Power output $= 46.56 - 1.56 = 45.06 \text{ kW.}$

\therefore Gross torque $= \frac{45.06 \times 10^3}{2\pi \times \frac{60}{60}} = 430.5 \text{ Nm.}$ $\left[\because \omega_s = \frac{2\pi N_s}{60} \text{ and } T = \frac{P}{\omega_s} \right]$

If rotor resistance is R_2 ,

$$I_2^2 R_2 = \frac{1440}{3}$$

$$\therefore R_2 = \frac{1440}{3 \times (110)^2} \Omega = 0.039 \Omega.$$

14.187. A 50 Hz slip ring induction motor having star connected rotor gives 750 V at standstill between the slip rings. Rotor resistance and reactance per phase are 0.3Ω and 5Ω respectively. Calculate the rotor current and p.f. at standstill when an external impedance of $(3 + j10) \Omega$ is connected with the rotor. Also calculate the current and p.f. when the slip rings are short-circuited and the motor is running at a slip of 3%.

Solution

$$E_2 = \frac{750}{\sqrt{3}} \text{ V} = 433 \text{ V}.$$

When external impedance is connected the total rotor impedance at standstill is (Z_2) = $\sqrt{(3 + 0.3)^2 + (5 + 10)^2} = 15.3 \Omega$.

$$\text{At standstill, rotor current} = \frac{433}{15.3} \text{ A} = 28.3 \text{ A}.$$

$$\text{p.f.} \left(= \frac{R}{Z} \right) = \frac{3 + 0.3}{15.3} = 0.216.$$

when the slip rings are short circuited and the motor is running at a slip of 3%,

$$Z_2 = \sqrt{(0.3)^2 + (0.03 \times 5)^2} = 0.3354 \Omega.$$

$$\text{Rotor current } I_2 = \frac{s E_2}{Z_2} = \frac{0.03 \times 433}{0.3354} \text{ A} = 38.73 \text{ A}$$

$$\text{Power factor} = \frac{0.3}{0.3354} = 0.89 \text{ (lag).}$$

14.188. The rotor of a three-phase induction motor has 0.03Ω resistance and 0.5Ω standstill reactance per phase. Determine the external resistance to be connected in the rotor circuit to get one third of the maximum torque at starting. Neglect stator impedance. By what percentage will the external resistance change the current and p.f. at starting?

Solution

$$\frac{T_{st}}{T_m} = \frac{2}{\frac{1}{s_m} + s_m} = \frac{1}{3}$$

$$\therefore \frac{1}{s_m} + s_m = 6$$

$$\text{or } s_m^2 - 6s_m + 1 = 0$$

$$\text{or } s_m = \frac{6 \pm \sqrt{36 - 4}}{2} = 5.82 \text{ or } 0.18$$

As induction motor cannot have slip more than 1, hence value of s_m is 0.18.

$$\text{For negligible stator impedance } \frac{R_2}{s_m} = X_2$$

$$\text{or } R_2 = 0.18 \times 0.5 = 0.09$$

$$\therefore \text{External resistance to be connected in the rotor circuit is } (0.09 - 0.03) = 0.06 \Omega.$$

Number of turns (T) = $(2 \times 90) = 180$.

$$\text{Slots/pole} = \frac{180}{20} = 9$$

$$\text{Slot angle } \beta = \frac{180^\circ}{9} = 20^\circ.$$

$$\text{Number of slots in a phase group} = \frac{60^\circ}{20^\circ} = 3. (= m)$$

$$\therefore \text{hence } (K_d) = \frac{\sin \frac{m\beta}{2}}{m \sin \frac{\beta}{2}} = 0.9598.$$

$$\therefore V_{ph} = 4.44 K_p K_d \phi f T = 4.44 \times 1 \times 0.9598 \times 0.03 \times 50 \times 180 = 1150.6 \text{ V.}$$

$$\therefore \text{Open circuit line voltage } V_L = \sqrt{3} \times 1150.6 = 1992.85 \text{ V.} \quad \dots\dots\dots$$

14.200 An 11 kV star connected synchronous motor has an input current of 100 A. The synchronous reactance and resistance are 25Ω and 0.5Ω respectively. Determine the power input to the motor and the induced emf for a p.f. of 0.75 lagging.

Solution

Line voltage $V_L = 11 \text{ kV}$.

Armature current $I_a = 100 \angle -\cos^{-1} 0.75^\circ = 100 \angle -41.41^\circ \text{ A}$.

$X_s = 25 \Omega$ and $R_a = 1 \Omega$.

$$\therefore \text{Power input to the motor} = \sqrt{3} V_L I_a \cos \theta = (\sqrt{3} \times 11000 \times 100 \times 0.75) \\ = 1428941.916 = 1428.94 \text{ kW.}$$

Induced emf per phase

$$E = V_{ph} - I_a(R_a + jX_s) \\ = \frac{11000}{\sqrt{3}} - 100 \angle -41.41^\circ (0.5 + j25) \\ = 6351 - 100 \angle -41.41^\circ \times 25.005 \angle 88.25^\circ \\ = 6351 - 2500.5 \angle 47.44^\circ = 5010.7 \angle -21.567^\circ \text{ V.} \quad \dots\dots\dots$$

14.201 The full-load current of a 3.3 kV star connected synchronous motor is 100 A at 0.8 p.f. lagging. The mechanical loss is 25 kW and the per phase resistance and reactance of the motor is 0.3Ω and 10Ω respectively. Determine the excitation emf, torque angle, efficiency and shaft output of the motor.

Solution

Given :

$$R_a = 0.3 \Omega$$

$$X_s = 10 \Omega$$

$$V_{ph} = \frac{3300}{\sqrt{3}} \text{ V} = 1905.3 \text{ V}$$

$$I_a = 100 \text{ A; } \cos \theta = 0.8 \text{ (lagging).}$$

$$\text{The excitation emf is } E = 1905.3 - 100 \angle -\cos^{-1} 0.8 (0.3 + j10) \\ = 1281.41 - j782.09 = 1501.22 \angle -31.397^\circ \text{ V/ph}$$

\therefore Excitation emf is 1501.22 V per phase and the torque angle is 31.397° .

Let ϕ be the angle between E and I_a . Mechanical power developed is $(3 E I_a \cos \phi)$,
i.e., $P = 3 \times 1501.22 \times 100 \cos (-36.87^\circ + 31.397^\circ)$
 $= 448312.89 \text{ W} = 448.31 \text{ kW}$



MULTIPLE CHOICE QUESTIONS

.....

15.1 CIRCUIT ELEMENTS, KIRCHHOFF'S LAWS, AND NETWORK THEOREMS

- Identify the passive elements among the following.
(a) voltage source (b) current source
(c) inductor (d) transistor
- Determine the total inductance of a parallel combination of 100 mH, 50 mH and 10 mH.
(a) 7.69 mH (b) 160 mH (c) 60 mH (d) 110 mH
- If the voltage across a given capacitor is increased, the amount of stored charge
(a) increases (b) decreases
(c) remains same (d) is exactly doubled
- How much energy is stored by a 100 mH inductance with a current of 1 A?
(a) 100 J (b) 1 J (c) 0.05 J (d) 0.01 J
- The following voltage drops are measured across each of three resistors in series 5.2 V, 8.5 V and 12.3 V. What is the value of the source voltage to which these resistors are connected?
(a) 8.2 V (b) 12.3 V (c) 5.2 V (d) 26 V
- A certain series circuit has 100 Ω , 270 Ω and 330 Ω resistors in series. If the 270 Ω resistor is removed, the current will
(a) increase (b) become zero
(c) decrease (d) remain constant
- A series circuit consists of a 4.7 k Ω , 5.6 k Ω , 9 k Ω and 10 k Ω resistors. Which resistor has the highest voltage across it?
(a) 4.7 k Ω (b) 5.6 k Ω (c) 9 k Ω (d) 10 k Ω
- The total power in a series circuit is 10 W. There are five equal value resistors in the circuit. How much power does each resistor dissipate?
(a) 10 W (b) 5 W (c) 2 W (d) 1 W

9. When a $1.2\text{ k}\Omega$ resistor, $100\text{ }\Omega$ resistor, $1\text{ k}\Omega$ resistor and $50\text{ }\Omega$ resistor are in parallel, the total resistance is less than
 (a) $100\text{ }\Omega$ (b) $50\text{ }\Omega$ (c) $1.2\text{ k}\Omega$ (d) $1\text{ k}\Omega$
10. If one of the resistors in a parallel circuit is removed, what happens to the total resistance?
 (a) decreases (b) increases
 (c) exactly doubles (d) remains constant
11. Six light bulbs are connected in parallel across 110 V . Each bulb is rated at 75 W . How much current flows through each bulb?
 (a) 0.682 A (b) 0.7 A (c) 75 A (d) 110 A
12. Superposition theorem is valid only for
 (a) linear circuits (b) non-linear circuits
 (c) both (a) and (b) (d) neither (a) nor (b)
13. When superposition theorem is applied to any circuit, the dependent voltage source is always
 (a) opened (b) shorted
 (c) active (d) none of the above.
14. Maximum power is transferred when the load resistance is
 (a) equal to source in resistance
 (b) equal to half of the source resistance
 (c) equal to zero
 (d) none of the above
15. The superposition theorem is not valid for
 (a) voltage responses (b) current responses
 (c) power responses (d) all the above.
16. Determine the current I in the circuit (Fig. 15.1)
 (a) 2.5 A (b) 1 A
 (c) 12 A (d) 4.5 A

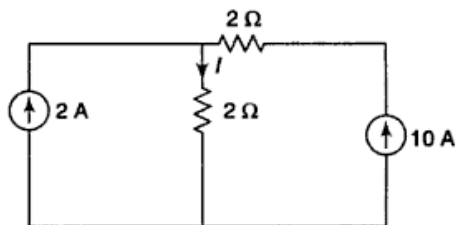


Fig. 15.1

17. The reciprocity theorem is applicable to
 (a) linear networks only
 (b) bilateral networks only
 (c) both (a) and (b)
 (d) neither (a) nor (b)
18. Thevenin voltage in the circuit shown in Fig. 15.2 is
 (a) 3 V (b) 2.5 V
 (c) 2 V (d) 0.1 V
19. Three equal resistances of $3\text{ }\Omega$ are connected in star what is the resistance in one of the arms in an equivalent delta circuit?
 (a) $10\text{ }\Omega$ (b) $3\text{ }\Omega$
 (c) $9\text{ }\Omega$ (d) $27\text{ }\Omega$

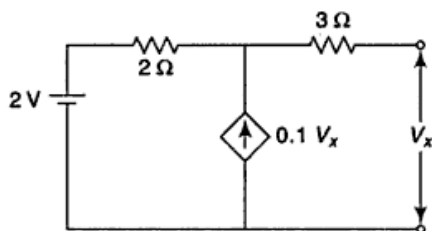


Fig. 15.2

20. Three equal resistances of $5\text{ }\Omega$ are connected in delta. What is the resistance in one of the arms of the equivalent star circuit?
 (a) $5\text{ }\Omega$ (b) $1.67\text{ }\Omega$ (c) $10\text{ }\Omega$ (d) $15\text{ }\Omega$

21. Norton's current in the circuit (Fig. 15.3) is given by
 (a) $(2i/5)$ (b) zero
 (c) infinite (d) none

22. The nodal method of circuit analysis is based on
 (a) KVL and Ohm's law
 (b) KCL and Ohm's law
 (c) KVL and KCL
 (d) both (a) and (b)

23. A practical voltage source consists of an ideal voltage source in
 (a) series with an internal resistance
 (b) parallel with an internal resistance
 (c) both (a) and (b)
 (d) neither (a) nor (b)

24. Find the voltage between A and B in a voltage divider network (Fig. 15.4)
 (a) 90 V (b) 9 V
 (c) 100 V (d) 0 V

25. The algebraic sum of all the currents meeting a junction is equal to
 (a) 1 (b) -1 (c) zero (d) can't say

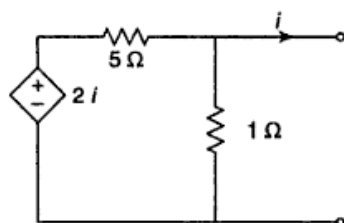


Fig. 15.3

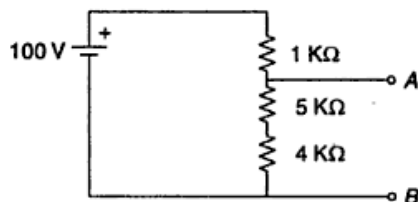


Fig. 15.4

Answer (15.1)

1. (c) 2. (a) 3. (a) 4. (c) 5. (d) 6. (a) 7. (d) 8. (c)
 9. (b) 10. (b) 11. (a) 12. (a) 13. (c) 14. (a) 15. (c) 16. (c)
 17. (c) 18. (b) 19. (c) 20. (b) 21. (a) 22. (b) 23. (a) 24. (a)
 25. (c)

15.2 ELECTROMAGNETIC INDUCTION AND INDUCTANCE

- In electrical machine laminated cores are used with a view to reduce
 (a) copper loss (b) hysteresis loss
 (c) eddy current loss (d) all of the above
- The unit of retentivity is
 (a) dimension less (b) ampere turn
 (c) ampere turn/meter (d) ampere turn/weber
- The permeability of all non-magnetic materials including air is
 (a) $2\pi \times 10^{-7}$ H/m (b) $4\pi \times 10^{-7}$ H/m
 (c) $\pi \times 10^{-7}$ H/m (d) $6\pi \times 10^{-7}$ H/m
- A coil of 400 turns has a flux of 0.5 mWb linking with it when carrying a current of 2A. What is the value of inductance if the coil?
 (a) 100 H (b) 10 H (c) 0.001 H (d) 0.1 H

5. The magnetism left in the iron after exciting field has been removed is known as
 - (a) reluctance
 - (b) performace
 - (c) susceptance
 - (d) residual magnetism
6. The initial permeability of an iron rod is
 - (a) the permeability almost in non-magnetised state
 - (b) the lowest permeability of the iron rod
 - (c) the highest permability of iron rod
 - (d) the permeability at the end of the rod
7. A crack in the magnetic path of the inductor will
 - (a) not affect the inductance of the coil
 - (b) increase the inductance value
 - (c) decrease the inductance value
8. Magnetic moment is the
 - (a) pole strength
 - (b) vector quantity
 - (c) scalar quantity
 - (d) universal constant
9. A conductor of length 1 m moves at right angles to a magnetic field of flux density 1 wb/m^2 with a velocity of 20 m/s. The induced emf in conductor will be
 - (a) 100 V
 - (b) 20 V
 - (c) 2 V
 - (d) 40 V
10. The tubes of force within the magnetic material are known as
 - (a) tubes of induction
 - (b) electric flux
 - (c) lines of force
 - (d) none of the above
11. A magnetic field exists around
 - (a) copper
 - (b) iron
 - (c) moving charges
 - (d) aluminium
12. Reciprocal of permeability is
 - (a) conductivity
 - (b) reluctivity
 - (c) susceptibility
 - (d) permittivity
13. When the current in a circuit is constant, what will be the value of induced voltage?
 - (a) same value as current
 - (b) can't say
 - (c) half of the current value
 - (d) zero
14. Presence of magnetic flux in a magnetic circuit is due to
 - (a) mmf
 - (b) emf
 - (c) low reluctance path
 - (d) none of the above
15. In the left hand rule, forefinger always represents
 - (a) voltage
 - (b) current
 - (c) magnetic field
 - (d) direction of force on the conductor
16. At radio frequencies, the iron core material of inductors
 - (a) has a low permeability
 - (b) is laminated
 - (c) is called ferrite
 - (d) reduces inductance as well as losses

17. Susceptibility is positive for
 - (a) ferromagnetic substances
 - (b) Paramagnetic substances
 - (c) non-magnetic substances
 - (d) none of these
18. The area of the face of a pole is 1.5 m^2 and the total flux is 0.18 webers. The flux density in the air gap
 - (a) 0.12 tesla
 - (b) 120 tesla
 - (c) 1.2 tesla
 - (d) 1.2×10^{-2} tesla
19. A conductor of 0.2 m long carries a current of 3 A. at right angle to a magnetic field of 0.5 tesla. The force acting on the conductor will be
 - (a) 30 N
 - (b) 3.0 N
 - (c) 1.0 N
 - (d) 0.3 N
20. Reluctivity is analogous to
 - (a) resistivity
 - (b) permeability
 - (c) conductivity
 - (d) none of these
21. Which of the following magnetic path will require the largest mmf?
 - (a) iron core
 - (b) air-gap
 - (c) filament
 - (d) inductance coil
22. Two parallel long conductors will carry 100 A. If the conductors are separated by 200 m, the force per meter of the length of the each conductor will be
 - (a) 100 N
 - (b) 10 N
 - (c) 1 N
 - (d) 0.1 N
23. The reciprocal of reluctance is
 - (a) permeance
 - (b) conductance
 - (c) susceptance
 - (d) admittance
24. The area of hysteresis loop is the measure of
 - (a) permittivity
 - (b) permeance
 - (c) energy loss per cycle
 - (d) magnetic flux
25. Sparking occurs when a load is switched off because the circuit has
 - (a) high capacitance
 - (b) high impedance
 - (c) high inductance
 - (d) high resistance

Answers (15.2)

1. (c) 2. (d) 3. (b) 4. (d) 5. (d) 6. (a) 7. (c) 8. (b)
9. (b) 10. (a) 11. (c) 12. (b) 13. (d) 14. (a) 15. (c) 16. (c)
17. (a) 18. (a) 19. (d) 20. (a) 21. (b) 22. (d) 23. (a) 24. (c)
25. (a)

15.3 FUNDAMENTALS OF AC CIRCUITS

1. Peak value being the same, which of the following will have the highest rms value?
 - (a) sine wave
 - (b) half wave rectified sine wave
 - (c) triangular wave
 - (d) square wave
2. The peak value of a sine wave is 400 V. The average value is
 - (a) 254.8 V
 - (b) 565.6 V
 - (c) 282.8 V
 - (d) 400 V

14. When the current and voltage in a circuit are out of phase by 90° , the power is
(a) zero (b) undefined (c) maximum (d) minimum
15. The positive maximum of a sine wave occurs at
(a) 180° (b) 90° (c) 45° (d) 0°
16. In purely inductive circuit
(a) reactive power is zero (b) apparent power is zero
(c) actual power is zero (d) none of above
17. Form factor of a sine wave is
(a) 0.637 (b) 0.707 (c) 1.11 (d) 1.414
18. What is the periodic time of a system with a frequency of 50 Hz?
(a) 0.2 s (b) 2 s (c) 0.02 s (d) 20 s
19. For the same peak value, which wave will have the least rms value?
(a) square wave (b) triangular wave
(c) sine wave (d) full wave rectified sine wave
20. Inductive reactance of a circuit is more when
(a) inductance is more and frequency of supply is more
(b) inductance is more and frequency is less.
(c) inductance is less and frequency is less
(d) inductance is less and frequency is more
21. Inductance affects the direct current flow at the time of
(a) turning on and off (b) operation
(c) turning on (d) turning off
22. In a series RC circuit as frequency increases
(a) current decreases (b) current remains unaltered
(c) current increases
23. Which of the following waves has unity form factor?
(a) triangular (b) square (c) sine wave (d) square wave
24. The current in a circuit is given by $i = 50 \sin \omega t$. If the frequency be 25 Hz, how long will it take for the current to rise to 25 amp?
(a) 0.02 sec (b) 0.05 sec
(c) 3.33×10^{-3} sec (d) 0.033 sec
25. In a parallel RC circuit, the supply current always _____ the applied voltage
(a) lags (b) leads
(c) remains on phase with (d) none of the above
26. For a given power factor of the load, if the p.f. of the load decreases, it will draw from the supply
(a) less current (b) more current
(c) same current
27. In a series circuit on resonance, the following will occur:
(a) $X_L = X_C$ (b) $V_L = V_C$
(c) $Z = R$ and $V = V_R$ (d) all above
28. P.F. of following circuit will be zero when the circuit contains
(a) capacitance only (b) resistance only
(c) inductance only (d) capacitance and inductance

22. In the armature, dc generator generates
(a) ac voltage (b) oscillating emf
(c) dc voltage (d) ac superimposed over dc
23. The commutator segments of a dc machine are made of
(a) iron (b) carbon
(c) stainless steel (d) hard copper
24. In dc machines, lap winding is used for
(a) high voltage low current (b) low voltage low current
(c) high voltage high current (d) low voltage high current
25. Fractional pitch winding is used in dc machine
(a) to reduce sparking
(b) to increase the generated voltage
(c) to save the copper because of shorter end connection
(d) due to (a) and (c) above
26. Magnetic field in a dc generator is produced by
(a) electromagnets (b) both (a) and (c)
(c) permanent magnet (d) none of these
27. The sparking at the brushes of a dc generator is due to
(a) reactance voltage (b) armature reaction
(c) light load (d) high resistance of the brushes
28. In dc generators, current to the external circuit from armature comes out from
(a) commutator (b) slip rings
(c) brush connection (d) none of above
29. What type of compounding would be desirable in a dc generator feeding a long transmission line?
(a) over compounding (b) flat compounding
(c) under compounding (d) any one of the above
30. Which would have the highest percentage of voltage regulation?
(a) a shunt generator (b) a series generator
(c) a compound generator (d) a separately excited generator
31. The ripples in a dc generator are reduced by
(a) using equalizer rings
(b) using conductor of annealed copper
(c) using carbon brushes of superior quality
(d) using commutator with large number of segments
32. Which of the following speed control methods of dc motor require auxiliary motor?
(a) flux control (b) voltage control
(c) armature control (d) Ward Leonard control
33. Compensation winding in a dc machine is connected
(a) in series of field winding (b) directly across the supply
(c) in series of interpole winding (d) in series of armature winding
34. While pole flux remains constant, if the speed of the generator is doubled, the emf generated will be
(a) twice (b) half
(c) nominal value (d) slightly less than nominal

35. The critical resistance of a dc generator refers to the resistance of
(a) load (b) brushes (c) field (d) armature
36. If the supply voltage in a shunt motor is increased, which of the following will decrease?
(a) full load current (b) starting torque
(c) full load speed (d) none of the above
37. Which device changes the alternating emf generated by the dc generator in its armature coil, to dc?
(a) rectifier (b) rotary converter
(c) commutator (d) slip ring
38. In a dc generator probable cause of failure to build up voltage is
(a) imperfect brush contact
(b) field resistance higher than critical resistance
(c) no residual magnetism in the generator due to faulty shunt connection
(d) all of the above
39. Stray losses in dc machine are
(a) magnetic losses (b) mechanical losses
(c) windage loss (d) all of these
40. Which of the following parts of a dc motor can sustain the maximum temperature rise?
(a) slip rings (b) armature winding
(c) commutator (d) field winding
41. If the resistance of the field winding of a dc generator is increased the output voltage will
(a) decrease (b) increase
(c) remain same (d) fluctuate heavily
42. The voltage between commutator segments should exceed than
(a) 2 V (b) 15 V (c) 0.002 V (d) 10 V
43. What is the flux in the armature core section of dc machine if the air gap flux be f
(a) ϕ (b) 1.5ϕ (c) $\phi/2$ (d) 0.1ϕ
44. Full load speed of a dc motor being 1000 rpm, and speed regulation being 9%, no load speed will be
(a) 900 rpm (b) 1000 rpm (c) 1110 rpm (d) 1200 rpm
45. The conventional exciter of a turbo generator is basically a
(a) shunt generator (b) separately excited generator
(c) series generator (d) compound generator
46. The flux set up by armature current has a
(a) magnetizing affect (b) demagnetizing effect
(c) cross-magnetizing effect (d) both (b) and (c)
47. If residual magnetism is not present in a dc generator, the induced emf at zero speed
(a) 10% of rated voltage (b) impracticable
(c) zero (d) the same as rated voltage
48. Which motor will have the least percentage increase of input current for the same percentage increase in torque?
(a) shunt motor (b) separately excited motor
(c) series motor (d) cumulatively compound motors

6. Distribution transformers have core losses
 - (a) more than full load copper loss
 - (b) equal to full load copper loss
 - (c) less than full load copper loss
 - (d) negligible compared to full load copper loss
7. The high frequency hum in a transformer is mainly due to
 - (a) lamination is not proper
 - (b) magnetostriction
 - (c) tank walls
 - (d) oil of the transformer
8. A single-phase transformer when supplied from 220 V, 50 Hz has eddy current loss of 50 W. If the transformer is connected to a voltage of 330 V, 50 Hz, the eddy current loss will be
 - (a) 168.75 W
 - (b) 112.5 W
 - (c) 75 W
 - (d) 50 W
9. Low voltage windings are placed nearer the core in the case of concentric windings because
 - (a) it reduces leakage flux
 - (b) it reduces hysteresis loss
 - (c) it reduces eddy current loss
 - (d) it reduces insulation requirement
10. Continuous disc winding is suitable for
 - (a) high voltage winding of large transformer
 - (b) low voltage winding of large transformer
 - (c) high voltage winding of small transformer
 - (d) low voltage winding of small transformer.
11. Short heat run test on transformers is performed by means of
 - (a) short circuit test
 - (b) half time on short circuit and half time an open circuit
 - (c) Sumpner's test
 - (d) open circuit test
12. The amount of leakage flux in the transformer windings depends upon
 - (a) mutual flux
 - (b) load current
 - (c) applied voltage
 - (d) turn ratio
13. The efficiency of a transformer at full load 0.85 p.f. (lag) is 95%. Its efficiency at full load 0.85 p.f. (lead) will be
 - (a) 95%
 - (b) more than 95%
 - (c) 100%
 - (d) less than 95%
14. For small power transformers, it is preferable to use
 - (a) corrugated tank
 - (b) tubed tanks
 - (c) radiator tank
 - (d) tank with separate coolers.
15. The core in a large power transformer is built of
 - (a) mild steel
 - (b) ferrite
 - (c) cast iron
 - (d) silicon steel
16. For all sizes of distribution transformers, it is preferable to use
 - (a) radiator tank
 - (b) plain sheet steel tank
 - (c) tubed tanks
 - (d) corrugated tank
17. When a two-winding transformer is connected as an auto transformer its efficiency (full load)
 - (a) increases
 - (b) remains same
 - (c) decreases
 - (d) rises to 100%

18. In an ideal transformer, the impedance transforms from one side to the other:
- (a) in direct ratio of turns
 - (b) in direct square ratio of turns
 - (c) in inverse ratio of turns
 - (d) in direct ratio of square root of turns.
19. Distribution transformers have core losses
- (a) negligible compared to full load copper loss
 - (b) more than full load copper loss
 - (c) less than full load copper loss
 - (d) equal to full load copper loss
20. Cross-over winding is suitable for
- (a) high voltage winding of large transformer
 - (b) high voltage winding of small transformer
 - (c) low voltage winding of small transformer
 - (d) low voltage winding of large transformer
21. Transformer oil is used as
- (a) an inert medium
 - (b) an insulant only
 - (c) a coolant only
 - (d) both as an insulant and a coolant
22. A transformer may have two or more ratings depending upon the type of
- (a) insulation used
 - (b) winding used
 - (c) core used
 - (d) cooling used
23. Breather mounted on transformer tank contains
- (a) calcium
 - (b) oil
 - (c) water
 - (d) liquid
24. Buchholz relay is a
- (a) gas actuated device
 - (b) voltage sensitive device
 - (c) frequency sensitive device
 - (d) current sensitive device
25. A transformer operates most efficiently at $3/4$ th full load. Its iron loss (P_i) and full load copper loss (P_c) are related as
- (a) $P_i/P_c = 4/3$
 - (b) $P_i/P_c = 16/9$
 - (c) $P_i/P_c = 3/4$
 - (d) $P_i/P_c = 9/16$
26. A $2/1$ ratio, two winding transformer is connected as an auto transformer. Its KVA rating as an auto transformer compared to a two-winding transformer is
- (a) 3 times
 - (b) 2 times
 - (c) same
 - (d) 1.5 times
27. The load of a certain transformer is reduced to 50%; the copper loss would become
- (a) 0.25 times
 - (b) 0.5 times
 - (c) same as before
 - (d) 2 times
28. A transformer has negligible resistance and a p.u. reactance of 0.1. Its voltage regulation on full load with a leading p.f. angle of 30° leading is
- (a) -10%
 - (b) 10%
 - (c) 5%
 - (d) -5%
29. During SC test at full load current the power input to a transformer comprises predominantly
- (a) eddy current loss
 - (b) copper loss
 - (c) core loss
 - (d) both (b) & (c)
30. The power transformer is a constant _____ device.
- (a) current
 - (b) voltage
 - (c) main flux
 - (d) power

31. The colour of fresh dielectric oil for a transformer is
 (a) grey (b) dark brown
 (c) pale yellow (d) colourless
32. A conservator is used
 (a) for better cooling
 (b) to act as an oil storage
 (c) to take up the expansion of oil due to temperature rise
 (d) none of the above.
33. On the two sides of a star/delta transformer
 (a) the voltage and currents both differ in phase by 30°
 (b) the voltage & currents are both in phase
 (c) the currents differ in phase by 30° but voltages are in phase
34. With peaked emf in the transformer windings, the hysteresis loss is,
 (a) reduced (b) increased (c) constant (d) zero
35. R = equivalent resistance, X = equivalent reactance, P_i = core loss. The load current for maximum efficiency operation of a transformer is given by
 (a) $\sqrt{P_i/R}$ (b) P_i/X (c) $\sqrt{P_i/X}$ (d) P_i/R
36. When the supply frequency to the transformer is increased, the iron loss will
 (a) increase (b) fluctuate (c) decrease (d) not change
37. The best method to obtain the efficiency of two identical transformers under load conditions is
 (a) a open circuit test (b) a back to back test
 (c) a short circuit test (d) none of the above
38. Spacers are provided between the adjacent coils
 (a) to provide free passage to the cooling oil
 (b) to insulate the coils from each other
 (c) due to both reasons
 (d) no use at all
39. If full load Cu loss of a transformer is 1600 W, its Cu loss at half load will be
 (a) 400 W (b) 800 W (c) 1600 W (d) 200 W
40. Which of the following gives the highest secondary voltage for a given primary voltage?
 (a) Y- Δ connection (b) Y-Y connection
 (c) Δ - Δ connection (d) Δ -Y connection
41. The main purpose of using magnetic core in a transformer is to
 (a) prevent eddy current loss
 (b) eliminate magnetic hysteresis
 (c) decrease iron losses
 (d) decrease reluctance of the common magnetic flux path
42. Greater the secondary leakage flux
 (a) less will be the primary induced emf
 (b) less will be the secondary induced emf
 (c) less will be the secondary terminal voltage

Answer (15.5)

1. (c) 2. (d) 3. (d) 4. (c) 5. (a) 6. (c) 7. (b) 8. (d)
 9. (d) 10. (a) 11. (c) 12. (b) 13. (a) 14. (c) 15. (d) 16. (c)
 17. (a) 18. (b) 19. (c) 20. (b) 21. (d) 22. (d) 23. (a) 24. (a)
 25. (d) 26. (a) 27. (c) 28. (d) 29. (b) 30. (c) 31. (c) 32. (c)
 33. (a) 34. (a) 35. (a) 36. (a) 37. (b) 38. (a) 39. (a) 40. (d)
 41. (d) 42. (b) 43. (c) 44. (c) 45. (b) 46. (c) 47. (c) 48. (c)
 49. (c) 50. (c) 51. (a) 52. (b) 53. (a) 54. (a) 55. (a) 56. (b)
 57. (a) 58. (d) 59. (b) 60. (b) 61. (c) 62. (d) 63. (b) 64. (d)
 65. (a) 66. (d) 67. (b) 68. (d) 69. (a) 70. (b)

15.6 INDUCTION MOTOR

- For a 3-phase induction motor, what frequency of rotor currents would you observe?
 - slip frequency (sf)
 - same as stator frequency (f)
 - $sf + f$
 - $f - sf$
- For 4% drop in supply voltage, the torque of an induction motor decreased by
 - 4%
 - 8%
 - 16%
 - 2%
- The power factor of star connected induction motor is 0.5. On being connected in delta, the power factor will
 - become zero
 - remain the same
 - reduces
 - increases
- In a double cage induction motor, the inner cage has
 - Low R and low X
 - Low R and high X
 - High R and high X
 - High R and low X
- The direction of rotation of a three phase induction motor is reversed by
 - rewinding the motor
 - adding a capacitor in any phase
 - interchanging the connection of any two phases
 - interchanging the connection of all the three phases
- The resistance R_0 of the exciting branch of the equivalent ckt. of a 3ϕ induction motor represents
 - stator core loss
 - stator copper loss
 - friction and windage losses
 - rotor copper loss.
- For controlling the speed of an Induction motor the frequency of supply is increased by 10%. For magnetizing current to remain the same, the supply voltage must
 - remain constant
 - be increased by 10%
 - be reduced by 10%
 - reduced by 20%
- For maximum starting torque in an induction motor
 - $r_2 = x_2$
 - $r_2 = 5x_2$
 - $r_2 = 0.5x_2$
 - $2r_2 = 3x_2$
- The double cage rotors are used to
 - increase pull out torque
 - increase starting torque
 - improve efficiency
 - reduce rotor core losses

Basic Electrical Engineering

This book on *Basic Electrical Engineering*, meant for the undergraduate students of all disciplines, encompasses every detail about the required topics in a lucid and very student friendly manner. A wide variety of problems with the right theoretical depth makes this book a perfect offering on the subject.

Salient features

- ✚ Exhaustive coverage of Power Transmission, Transformers and DC Machines
- ✚ Step-by-step problem solving methodology
- ✚ Quality illustrations to aid better understanding of the subject
- ✚ Rich pedagogy
 - 774 Solved examples
 - 359 Review questions

URL: <http://www.mhhe.com/chakrabarti/bee>



Tata McGraw-Hill

Visit us at : www.tatamcgrawhill.com

ISBN-13: 978-0-07-066930-7

ISBN-10: 0-07-066930-9



9 780070 669307

Urheberrechtlich geschütztes Material

